
***ECE 2C, notes set 5:
Fundamentals of
Transistor Amplifiers (part II)***

Mark Rodwell

University of California, Santa Barbara

Goals:

Practice DC bias analysis of transistor* circuits

Practice AC small - signal analysis of transistor* circuits

* or any nonlinear circuit element

(diode, Vacuum tube, tunnel junction, ...)


Comment (1): DC bias design in real circuits.

In developing our simple amplifier study,
we have provided DC input bias with a battery.


Clearly not real. But OK for now.

Bias structures in real ICs: as shown


1950's style
RC biasing

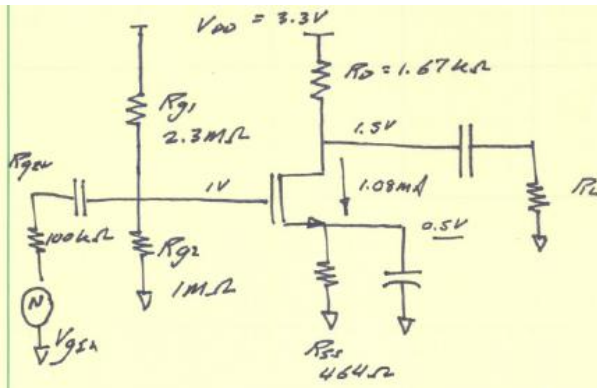


Direct coupled (IC style)

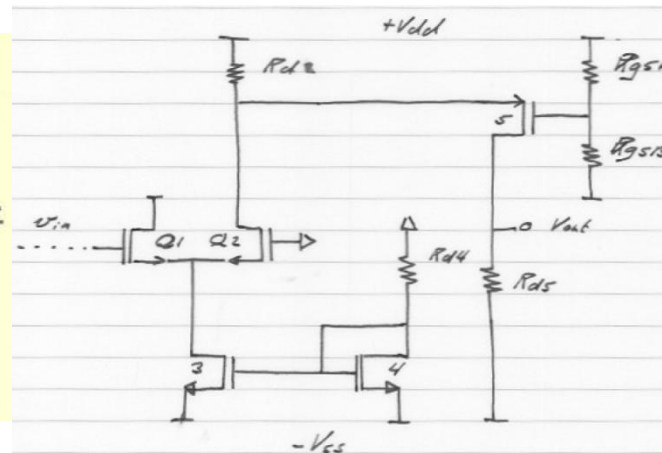


Tutorial amplifier

 

LC biased (and tuned)
RF-IC style

 

Comment (2): bias design: DC-coupling.

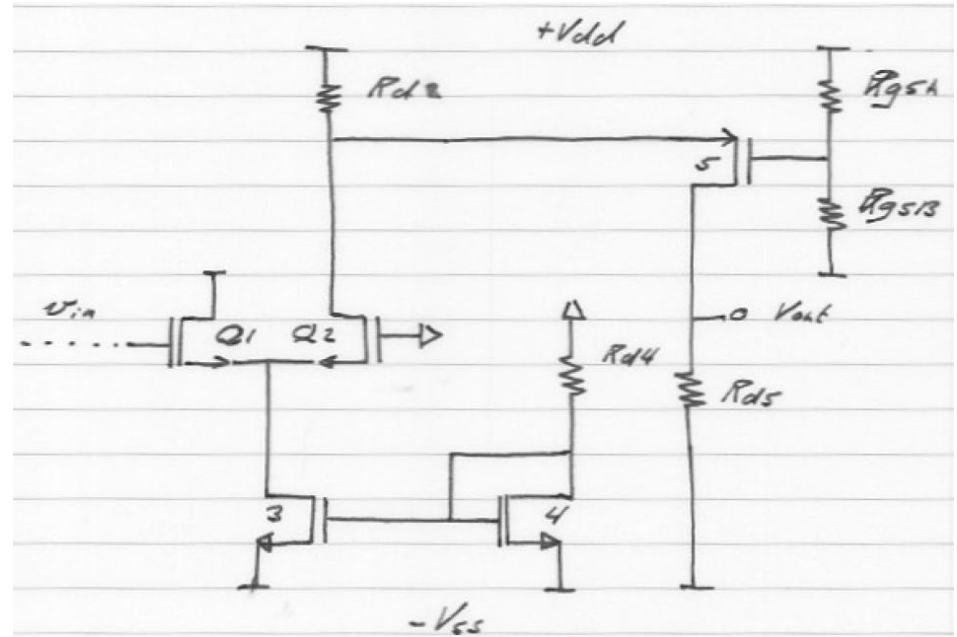


Direct - Coupled amplifier/IC designs :

DC output voltage on one stage = DC input voltage of the next.

Need skill & creativity to fit together DC bias requirements of all stages

→ ECE137AB

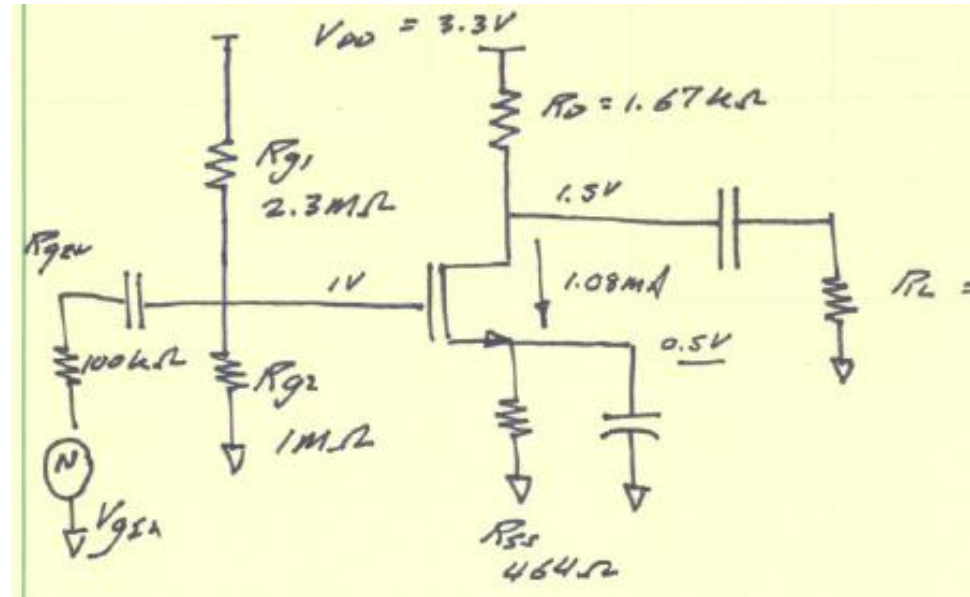Comment (3): bias design: AC/RC-coupling.



AC - Coupled amplifiers :

DC bias conditions set by resistors

Blocking capacitors isolate DC levels between stages.

Very low - frequency signals are not amplified..

We will *briefly* study such circuits


...mostly as an exercise in frequency response analysis.

Again, more detailed study in ECE137AB


Current Mirrors: First Treatment

Used in DC coupled circuits :
to provide (to set) DC bias currents.
as an active load (discuss later)

We now consider only basic operation

 

Current mirror DC bias analysis (1)

 

Example Parameters :

FET Q1:

$$(\mu c_{ox} W_g / 2L_g) = 1 \text{ mA/V}^2$$

$$V_{th} = 0.3 \text{ V}$$

$$1/\lambda = 10 \text{ V}$$

FET Q2:

$$(\mu c_{ox} W_g / 2L_g) = 2 \text{ mA/V}^2$$

$$V_{th} = 0.3 \text{ V}$$

$$1/\lambda = 10 \text{ V}$$

Circuit

$$V_{dd} = 2.5 \text{ V}$$

$$R_L = 1.0 \text{ k}\Omega$$

* we are again ignoring the $(1 + \lambda V_{DS})$ term in the bias analysis.

Doing this causes some significant error.

In ECE137A we will learn some tricks to calculate this quickly yet fairly accurately.

Do not ignore the $(1 + \lambda V_{DS})$ term in the small signal analysis.

Let us set $I_{D1} = 0.1 \text{ mA}$.

Analysis:

$$I_{D1} = (\mu c_{ox} W_g / 2L_g) (V_{gs} - V_{th})^2 (1 + \lambda V_{DS})$$

$$0.1 \text{ mA} = (1 \text{ mA/V}^2) (V_{gs} - 0.3 \text{ V})^2 (\lambda V_{DS} \text{ term neglected})$$


$$(V_{gs} - 0.3 \text{ V}) = \sqrt{0.1 \text{ mA} / 1 \text{ mA/V}^2} = 0.316 \text{ V}$$

$$V_{gs} = 0.616 \text{ V}$$

$$R_{ref} = (V_{DD} - V_{gs}) / I_{D1} = (2.5 \text{ V} - 0.616 \text{ V}) / (0.1 \text{ mA})$$

$$R_{ref} = 18.8 \text{ k}\Omega$$

Current mirror DC bias analysis (2)

 

Example Parameters :

FET Q1:

$$(\mu c_{ox} W_g / 2L_g) = 1 \text{ mA/V}^2$$

$$V_{th} = 0.3 \text{ V}$$

$$1/\lambda = 10 \text{ V}$$

FET Q2:

$$(\mu c_{ox} W_g / 2L_g) = 2 \text{ mA/V}^2$$

$$V_{th} = 0.3 \text{ V}$$

$$1/\lambda = 10 \text{ V}$$

Circuit

$$V_{dd} = 2.5 \text{ V}$$

$$R_L = 1.0 \text{ k}\Omega$$

* we are again ignoring the $(1 + \lambda V_{DS})$ term in the bias analysis.

Doing this causes some significant error.

In ECE137A we will learn some tricks to calculate this quickly yet fairly accurately.

Do not ignore the $(1 + \lambda V_{DS})$ term in the small signal analysis.

Now find the current in the output branch.

Analysis:

$$I_{D2} = (\mu c_{ox} W_g / 2L_g) (V_{gs} - V_{th})^2 (1 + \lambda V_{DS})$$

$$I_{D2} = (2 \text{ mA/V}^2) (0.613 \text{ V} - 0.3 \text{ V})^2 (\lambda V_{DS} \text{ term neglected})$$


$$I_{D2} = 0.2 \text{ mA}$$

$$V_{D2} = V_{DD} - I_{D2} R_L = 2.5 \text{ V} - (0.2 \text{ mA})(1 \text{ k}\Omega)$$

$$V_{D2} = 2.3 \text{ V}$$



If R_L is not large, V_{DS} of Q2 will be more than the knee voltage and will provide 1 mA to the load regardless of the value of R_L .
 → constant - current source

Current Mirrors: Constant-Current Source

 

If the $(1 + \lambda V_{DS})$ term is small, mirror provides nearly constant current over a wide range of load resistances, i.e. over a wide range of voltages.

  
The $(1 + \lambda V_{DS})$ term causes a significant variation of load current as the output voltage (or the load resistance) is varied.



Differential Amplifiers


Amplifies the difference between two input voltages V_{in}^+ and V_{in}^- .

 Also makes DC-coupled IC design easier. Widely used.




Current source :
typically a current mirror.

 Here : treat it as and
ideal DC current source.



Differential Amplifier: DC bias analysis

 

FETs Q_1, Q_2 :

$$(\mu c_{ox} W_g / 2L_g) = 1\text{mA/V}^2$$

$$V_{th} = 0.3\text{V}$$

$$1/\lambda = 10\text{V}$$

Circuit

$$V_{dd} = 2.5\text{V}$$

$$R_L = 8\text{k}\Omega$$

$$I_{SS} = 1/2\text{mA}$$

From symmetry: $I_{D1} = I_{D2} = I_{SS} / 2 = 0.25\text{mA}$

$$I_{D2} = (\mu c_{ox} W_g / 2L_g)(V_{gs} - V_{th})^2(1 + \lambda V_{DS})$$




$$0.25\text{mA} = (1\text{mA/V}^2)(V_{gs} - 0.3\text{V})^2(\lambda V_{DS} \text{ term neglected})$$

$$(V_{gs} - 0.3\text{V}) = \sqrt{(0.25\text{mA}) / (1\text{mA/V}^2)} \rightarrow V_{gs} = 0.80\text{V}$$

$$V_s = V_g - V_{gs} = 0\text{V} - 0.80\text{V} = -0.80\text{V}$$

$$V_D = V_{DD} - I_D R_L = 2.5\text{V} - (0.25\text{mA})(8\text{k}\Omega) = 0.5\text{V}$$

   Differential Amplifier: FET Small Signal Parameters



FETs Q_1, Q_2 :

$$(\mu c_{ox} W_g / 2L_g) = 1 \text{ mA/V}^2$$

$$V_{th} = 0.3 \text{ V} \quad I_D = 1/4 \text{ mA}$$

$$1/\lambda = 10 \text{ V} \quad V_{gs} = 0.8 \text{ V}$$

Once again, we must use the DC bias conditions to calculate the FET small-signal parameters

$$I_D = (\mu c_{ox} W_g / 2L_g) (V_{gs} - V_{th})^2 (1 + \lambda V_{DS})$$


$$g_m = (\mu c_{ox} W_g / L_g) (V_{gs} - V_{th}) (1 + \lambda V_{DS})$$

$$= (2 \text{ mA/V}^2) (0.8 \text{ V} - 0.3 \text{ V}) (1 + 1.3 \text{ V}/10 \text{ V})$$

$$= 1.13 \text{ mS}$$

$$G_{ds} = \frac{1}{R_{ds}} \cong \lambda I_D = \frac{0.25 \text{ mA}}{10 \text{ V}} = 25 \mu\text{S} = \frac{1}{40 \text{ k}\Omega}$$

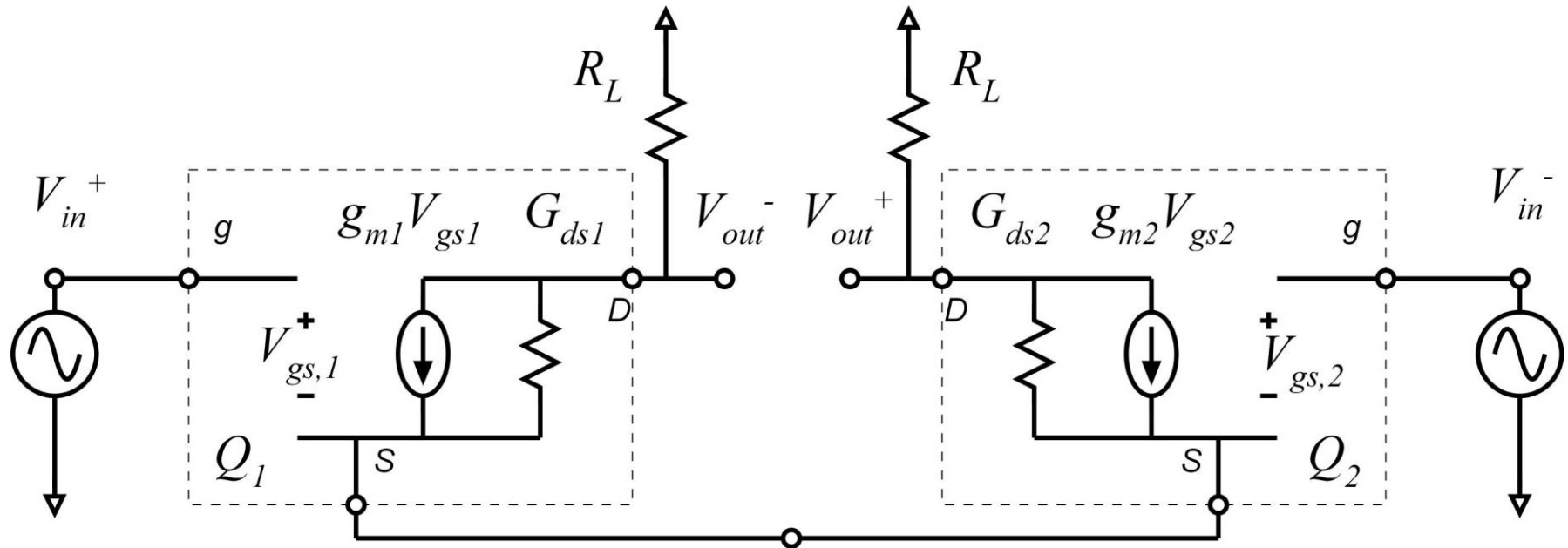
Differential Amplifier: Small Signal Equivalent Circuit



Before we analyze this problem,
let us make it simpler.

→ differential and common - mode signals

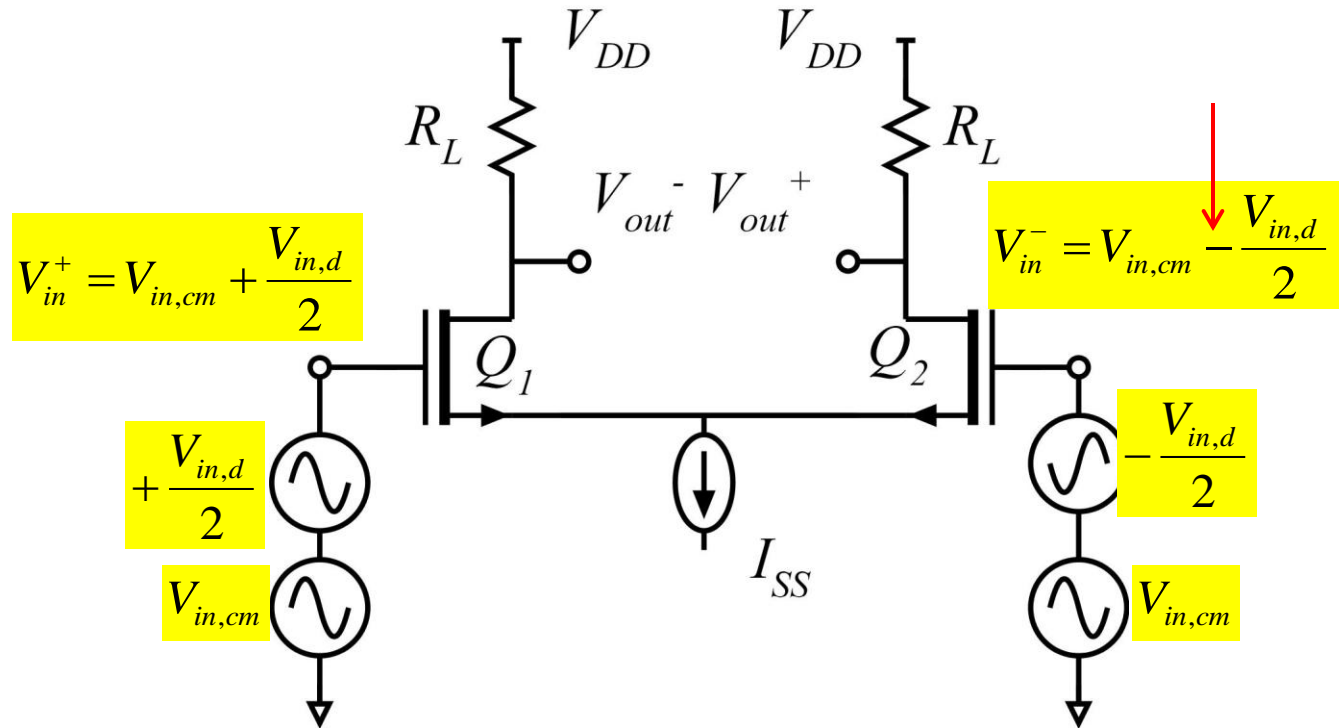Differential and Common-Mode Signals: Input




$V_{in,D}$ = differential input voltage = $V_{in}^+ - V_{in}^-$

$V_{in,CM}$ = common - mode (average) input voltage = $(V_{in}^+ + V_{in}^-) / 2$

$$\left. \begin{array}{l} V_{in,d} = V_{in}^+ - V_{in}^- \\ V_{in,cm} = (V_{in}^+ + V_{in}^-) / 2 \end{array} \right\} \rightarrow \begin{cases} V_{in}^+ = V_{in,cm} + V_{in,d} / 2 \\ V_{in}^- = V_{in,cm} - V_{in,d} / 2 \end{cases}$$

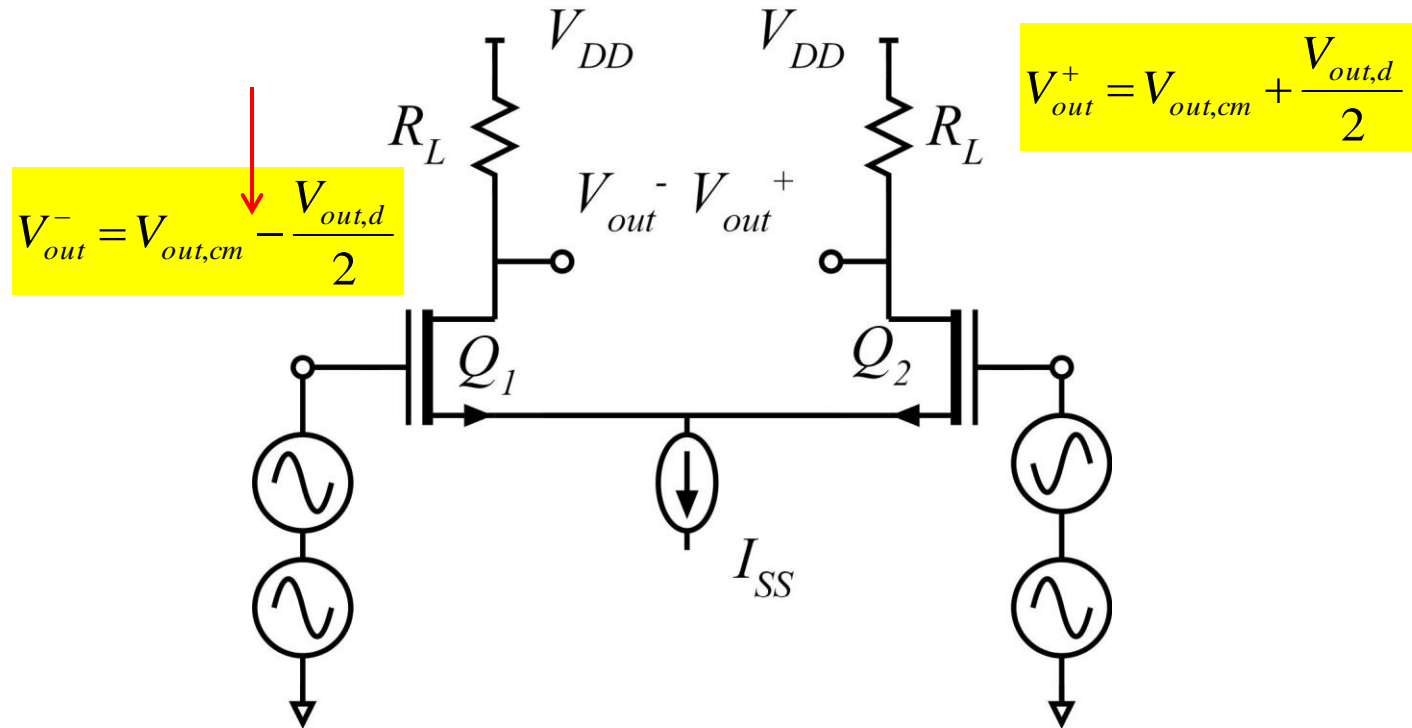Differential and Common-Mode Signals: Output




$V_{out,d}$ = differential output voltage = $V_{out}^+ - V_{out}^-$

$V_{out,cm}$ = common - mode (average) output voltage = $(V_{out}^+ - V_{out}^-) / 2$

$$\left. \begin{array}{l} V_{out,d} = V_{out}^+ - V_{out}^- \\ V_{out,cm} = (V_{out}^+ - V_{out}^-) / 2 \end{array} \right\} \rightarrow \begin{cases} V_{out}^+ = V_{out,cm} + V_{out,d} / 2 \\ V_{out}^- = V_{out,cm} - V_{out,d} / 2 \end{cases}$$

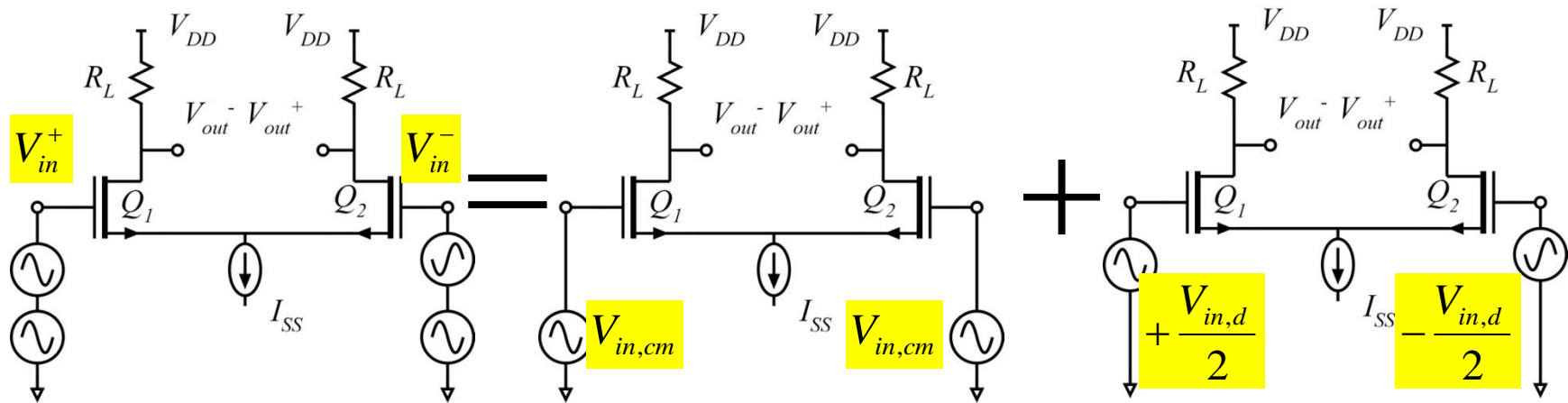Analysis: Use the principle of superposition



The (V_{in}^+, V_{in}^-) inputs can always be written as a superposition of V_d and V_{cm} .

So, analyze the circuit for *differential* and *common-mode* gain.

To find V_{out}^+ and V_{out}^- , write the input as sum of $V_{in,d}$ and $V_{in,cm}$,


multiply $V_{in,d}$ by the differential gain to get $V_{out,d}$,

multiply $V_{in,cm}$ by the common-mode gain to get $V_{out,cm}$,


(if you want) find V_{out}^+ and V_{out}^- using

$$V_{out}^+ = V_{out,cm} + V_{out,d}/2, \quad V_{out}^- = V_{out,cm} - V_{out,d}/2$$

Differential gain

 


 From symmetry, the small - signal voltage at this point must be zero.




So, it makes no difference if we ground this point. This is called a virtual ground.

Differential gain


 


 From symmetry, all the voltages on the right side are negatives of those on the left
 ..and, the virtual ground has broken the connection between the 2 sides of the circuit



So, we can throw the right side away !

Differential gain: analysis

  

The circuit is now the same as a common - source stage.

Be careful, however :

V_{in} has become $V_d / 2$, V_{out} has become $-V_d / 2$

Parameters :

FET :

Circuit

$$g_m = 1.13 \text{ mS}$$

$$R_L = 8 \text{ k}\Omega$$

$$R_{DS} = 40 \text{ k}\Omega$$

Equivalent load resistance

$$\begin{aligned} R_{L,eq} &= R_L \parallel R_{DS} = 40 \text{ k}\Omega \parallel 8 \text{ k}\Omega \\ &= 6.666 \text{ k}\Omega \end{aligned}$$

Voltage gain


$$\frac{V_{out}}{V_{in}} = -g_m R_{Leq} = -(1.13 \text{ mS})(6.66 \text{ k}\Omega) = -7.53$$

But $V_{in} = V_{in,d} / 2$ and $V_{out} = -V_{out,D} / 2$, so:


$$A_D = \frac{V_{out,D}}{V_{in,D}} = -\frac{V_{out}}{V_{in}} = +g_m R_{Leq} = +7.53$$

The circuit has a differential gain of 7.53

Common-mode gain

 


 From symmetry, the small - signal current in this wire must be zero.




So, it makes no difference if we cut this wire. This (should be) called a virtual open.

Common-mode gain

 


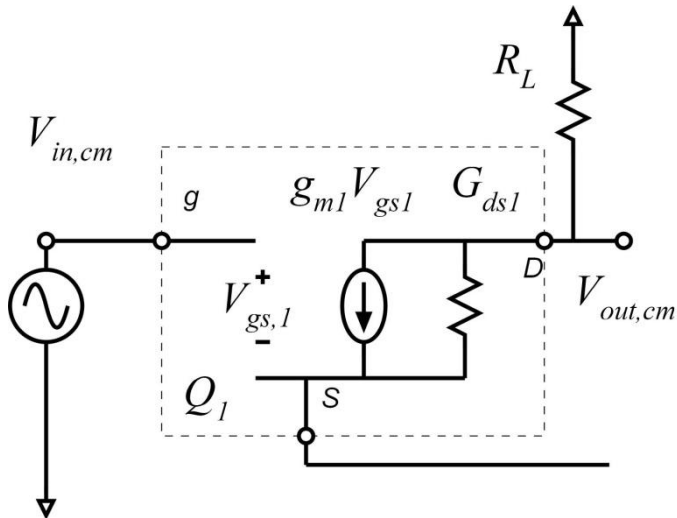From symmetry, all the voltages on the right side are * the same as * those on the left
 ..and, the virtual open has broken the connection between the 2 sides of the circuit



So, again, we can throw the right side away !

Common-mode: analysis

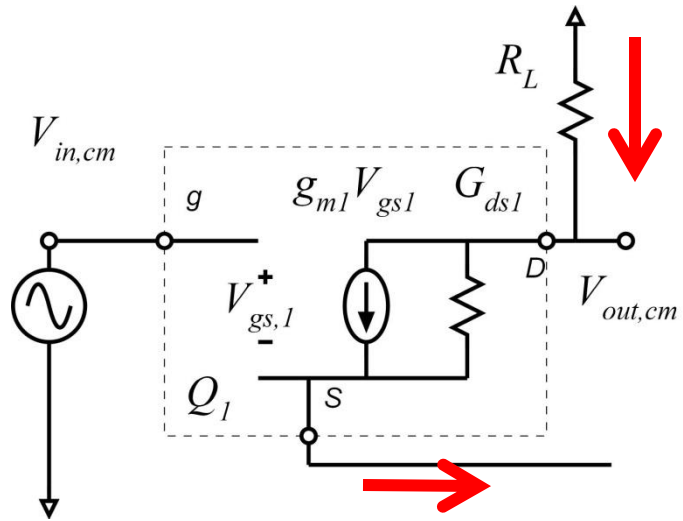

The FET source has no connection

→ the source current is zero.

→ the drain current is zero.

→ the common - mode output voltage is zero.

$$\rightarrow A_{cm} = \frac{V_{out,cm}}{V_{in,cm}} = 0$$

Note:

This is an extremely idealized analysis.


We have assumed that the small - signal impedance of the current source is infinite.

This results in zero common - mode gain.

With a finite output resistance to the current source the common - mode gain will be small, but not zero.

We will analyze this in ECE137AB

Differential Amplifiers: Recap

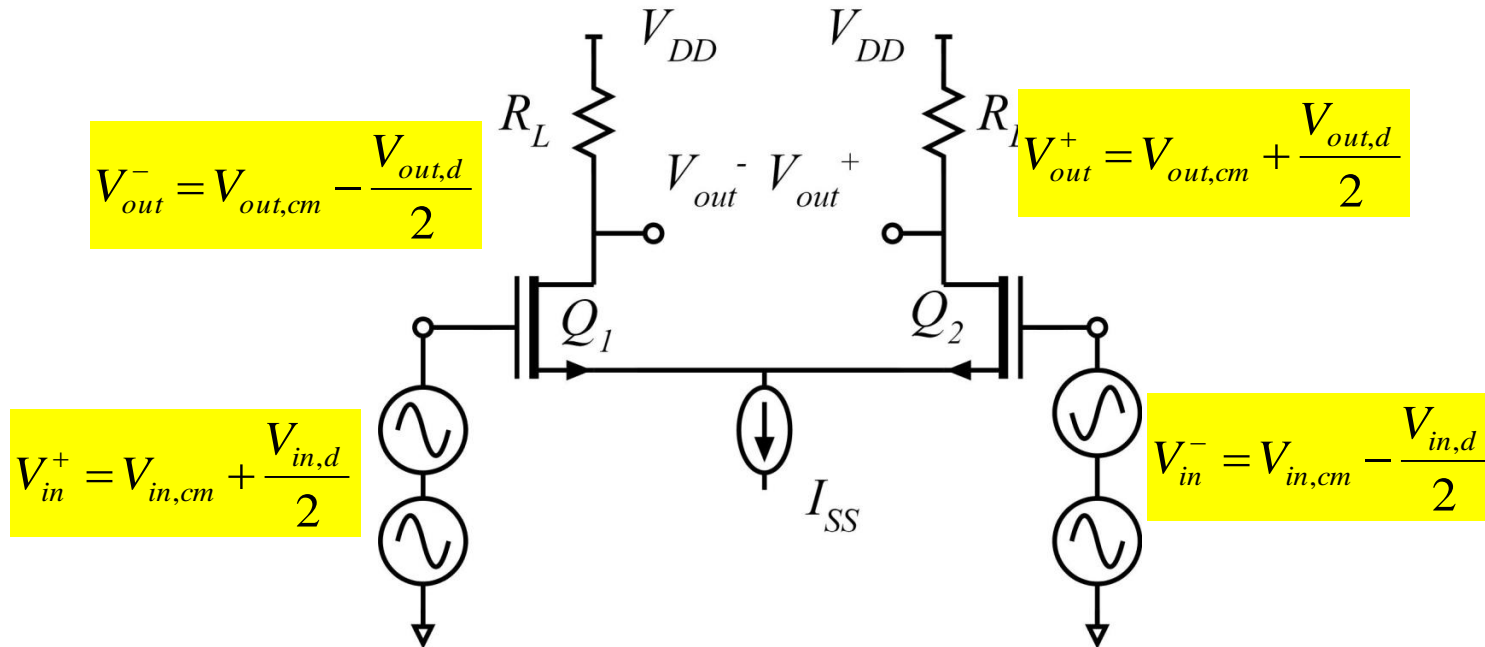

$$\left. \begin{aligned} V_{in,d} &= V_{in}^+ - V_{in}^- \\ V_{in,cm} &= (V_{in}^+ + V_{in}^-) / 2 \end{aligned} \right\} \leftrightarrow \begin{cases} V_{in}^+ = V_{in,cm} + V_{in,d} / 2 \\ V_{in}^- = V_{in,cm} - V_{in,d} / 2 \end{cases}$$

$$V_{out,d} = A_d V_{in,d} \quad \text{where } A_d = g_m R_{Leq}$$

$$V_{out,cm} = A_{cm} V_{in,cm} \quad \text{where } A_{cm} \rightarrow 0 \text{ if the current - source impedance is high}$$

$$\left. \begin{aligned} V_{out,d} &= V_{out}^+ - V_{out}^- \\ V_{out,cm} &= (V_{out}^+ + V_{out}^-) / 2 \end{aligned} \right\} \leftrightarrow \begin{cases} V_{out}^+ = V_{out,cm} + V_{out,d} / 2 \\ V_{out}^- = V_{out,cm} - V_{out,d} / 2 \end{cases}$$


Differential Amplifiers: Applications

One application : amplifying the difference between two voltages seen in precision instrumentation, in op - amp input stages.

Another application : ease of design of DC - coupled stages.

→ Look at one simple example.

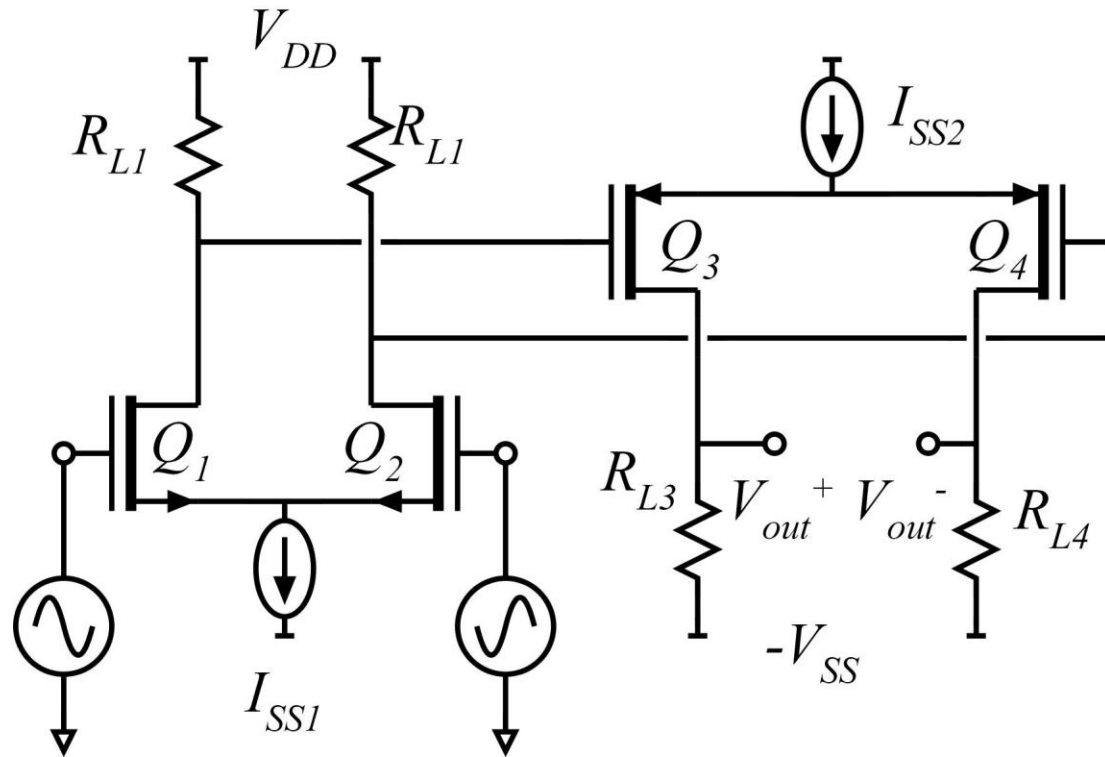
Example: Two-Stage Differential Amplifier



A pair of cascaded differential stages.

The differential design, and the NFET/PFET alternation, make it easy to design an amplifier with DC coupling and with zero volts DC at input and output.

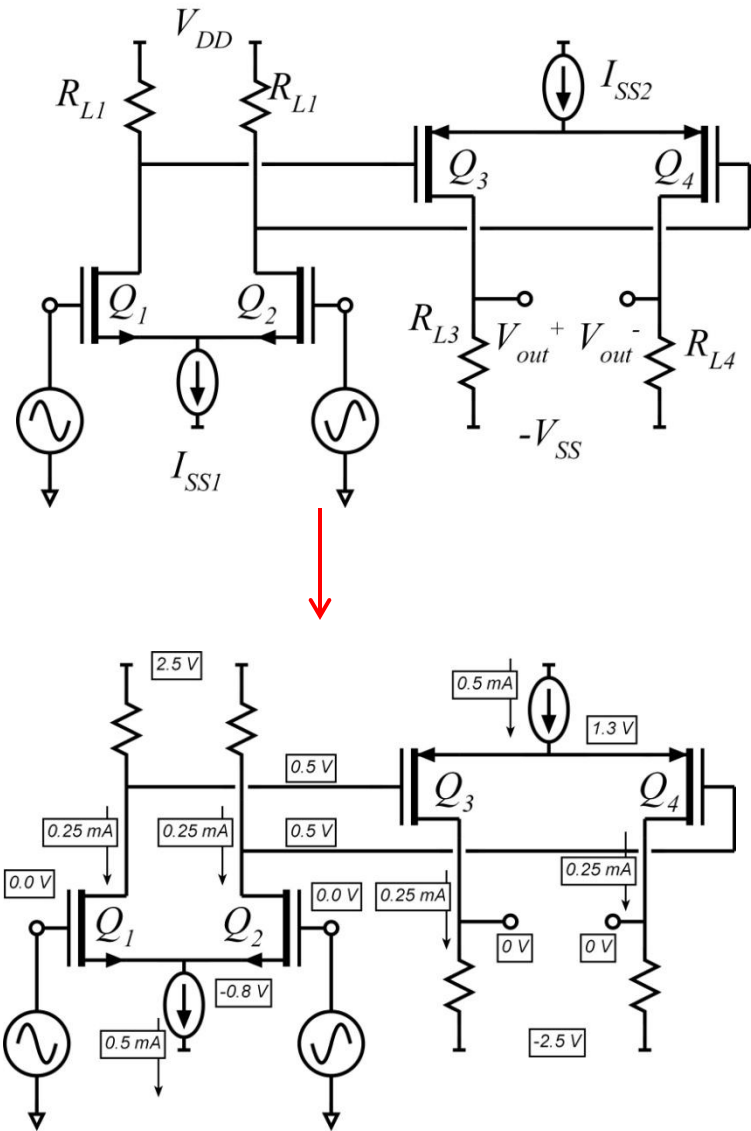Two-stage differential amplifier: DC bias analysis



All FETs

$$(\mu c_{ox} W_g / 2L_g) = 1\text{mA/V}^2$$

$$|V_{th}| = 0.3\text{ V}$$

$$1/\lambda = 10\text{V}$$

Circuit

$$V_{dd} = 2.5\text{ V} \quad V_{ss} = -2.5\text{ V}$$

$$R_{L1,2} = 8\text{ k}\Omega \quad R_{L3,4} = 10\text{ k}\Omega$$

$$I_{SS1} = 1/2\text{ mA} \quad I_{SS2} = 1/2\text{ mA}$$

The 1st stage is taken from the prior example.

→ same DC bias conditions

Second stage bias conditions

From symmetry: $I_{D3} = I_{D4} = I_{SS2} / 2 = 0.25\text{ mA}$

$$I_{D2} = (\mu c_{ox} W_g / 2L_g)(V_{gs} - V_{th})^2(1 + \lambda V_{DS})$$

$$0.25\text{mA} = (1\text{ mA/V}^2)(V_{gs} - 0.3\text{V})^2(\lambda V_{DS} \text{ term neglected})$$


$$(V_{gs} - 0.3\text{V}) = \sqrt{(0.25\text{mA}) / (1\text{ mA/V}^2)} \rightarrow V_{gs} = 0.80\text{V}$$

The gate is * more negative * than the source, so

$$V_s = V_g + V_{gs} = 0.5\text{V} + 0.80\text{V} = 1.30\text{V}$$

$$V_D = -V_{SS} + I_D R_L = -2.5\text{V} - (0.25\text{ mA})(10\text{k}\Omega) = 0.0\text{V}$$

 Two-stage differential amplifier: s.s. parameters




The calculations are identical to those of the previous example, and all FETs have the same values for $(\mu c_{ox} W_g / 2L_g)$ and λ .

$$\rightarrow g_m = 1.13 \text{ mS}$$


$$\rightarrow G_{ds} = \frac{1}{R_{ds}} = 25 \mu\text{S} = \frac{1}{40\text{k}\Omega}$$

 Two-stage differential amplifier: s.s. analysis




In the small signal diagram at left, the supply voltages have been replaced by short-circuits, the supply currents have been replaced by open-circuits, but the transistors have not yet been replaced by their small-signal models.

This is a convention.

 


For a differential input, the indicated points have zero AC voltages and so can be connected to virtual grounds.

 Two-stage differential amplifier: s.s. analysis



Again, the virtual grounds allow us to delete half the circuit.

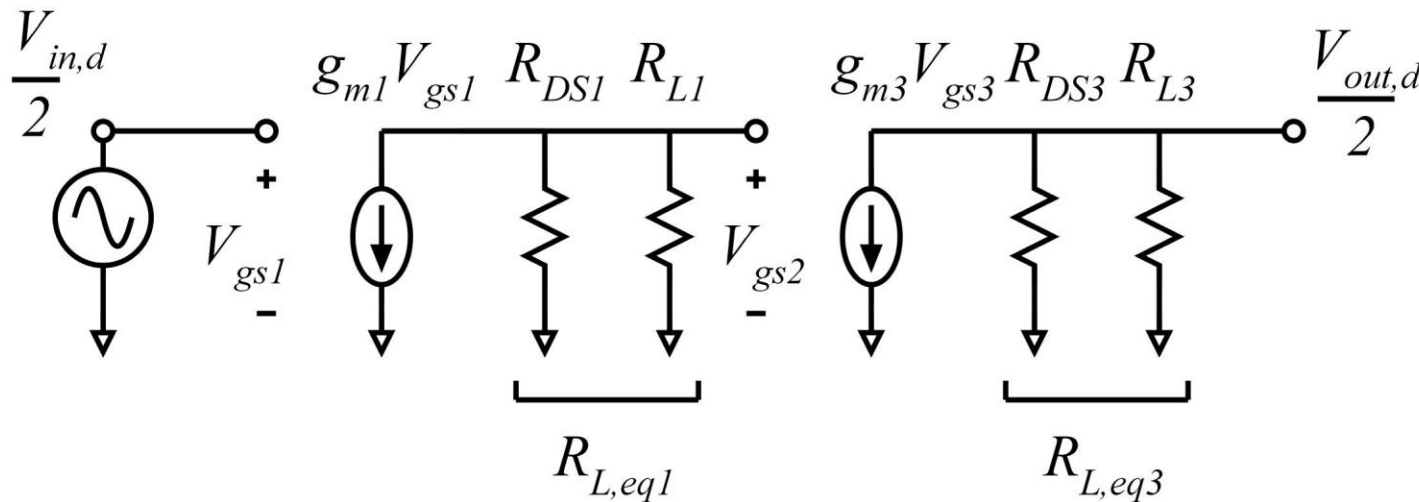
This leaves us with two cascade common - source stages.



Replace transistor symbols with small - signal models

→ AC small signal equivalent circuit

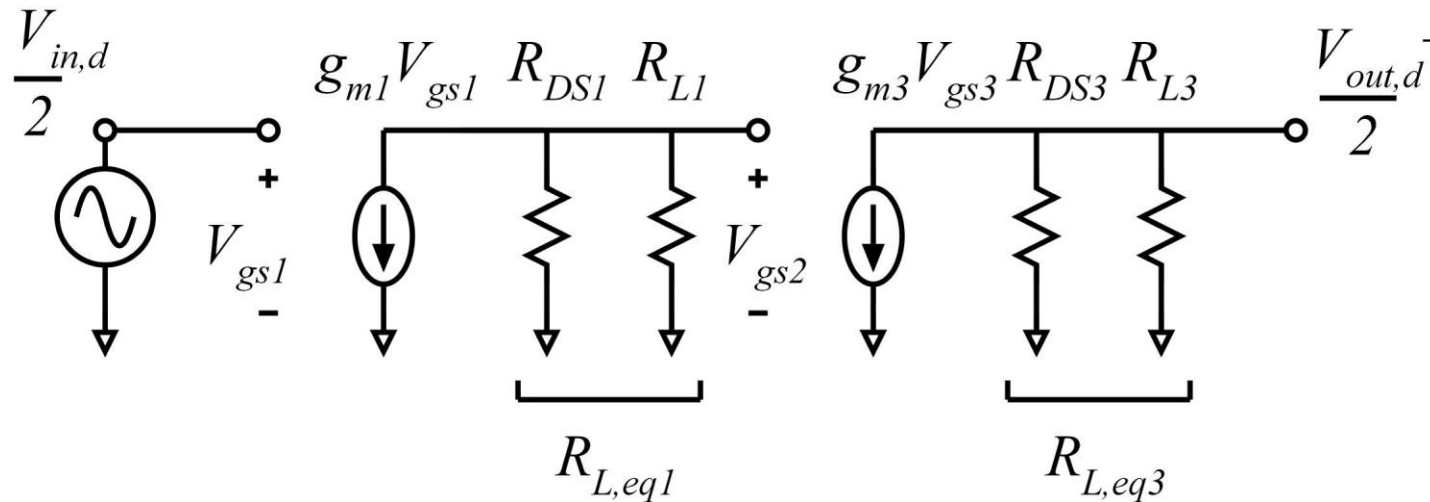Two-stage differential amplifier: s.s. analysis



First stage (as before)

Equivalent load resistance

$$R_{L,eq1} = R_{L1} \parallel R_{DS1} = 40\text{k}\Omega \parallel 8\text{k}\Omega \\ = 6.666 \text{ k}\Omega$$

Voltage gain

$$\left. \frac{V_{out}}{V_{in}} \right|_{stage1} = g_{m1} R_{Leq1} \\ = (1.13\text{mS})(6.66 \text{ k}\Omega) \\ = 7.53$$

Second stage

Equivalent load resistance

$$R_{L,eq2} = R_{L2} \parallel R_{DS2} = 40\text{k}\Omega \parallel 10\text{k}\Omega \\ = 8.0 \text{ k}\Omega$$

Voltage gain

$$\left. \frac{V_{out}}{V_{in}} \right|_{stage2} = g_{m2} R_{Leq2} \\ = (1.13\text{mS})(8.0 \text{ k}\Omega) \\ = 9.04$$

2-stage amplifier

Overall Voltage gain

$$\left. \frac{V_{out}}{V_{in}} \right|_{2stages} = A_{v1} A_{v2} \\ = (7.53)(9.04) \\ = 68.1$$