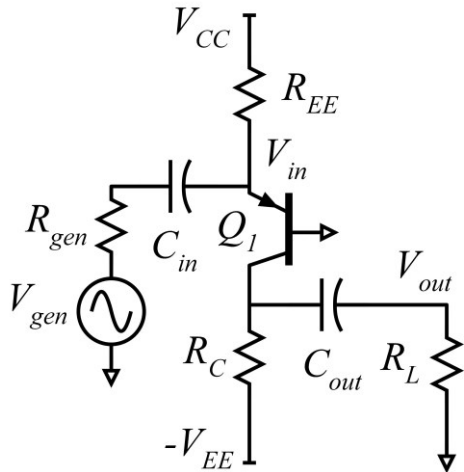



ECE137A Problem set #4



a) Give all resistor values

1) Common base amplifier. $Q1: \beta = 100, V_A = \text{infinity V}, V_{ce,sat} = 0.5V$
 The supplies are +10V and -10 V.
 You will bias the transistor with 1mA collector current. The DC collector bias voltage is -5V.
 R_L is 1 k Ω , R_{gen} is 100 Ω ,
 C_{out} and C_{in} are very large (AC short-circuit at the signal frequency)

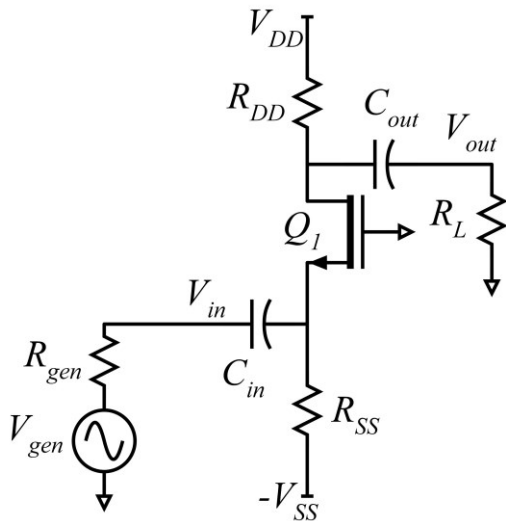b) Find the small signal V_{out}/V_{in} , V_{in}/V_{gen} and V_{out}/V_{gen}




a) Give all resistor values

b) Find the small signal V_{out}/V_{in} , V_{in}/V_{gen} and V_{out}/V_{gen}


2) Common gate amplifier.
 The transistor has $v_{th} = 0.25$ Volt,
 $K_{\mu} = 0.55 \text{mA/V}^2 \cdot (W_g / 1\mu\text{m})$,
 $K_v = 0.69 \text{mA/V} \cdot (W_g / 1\mu\text{m})$
 $\Delta V = 0.625V$ and $1/\lambda = 10$ Volts
 The supplies are +2V and -2 V
 You are to bias the transistor at 5mA drain current, with -0.5 V DC source voltage and +0.5V drain voltage
 $R_{gen} = 300 \Omega$, $R_L = 5k \Omega$

c) Find the amplifier input and output impedances

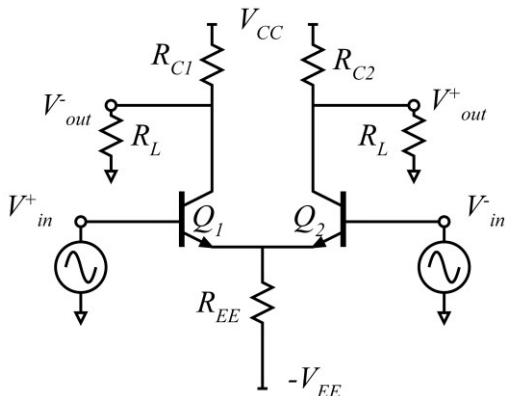
d) Find the maximum positive-going and negative going outputs.



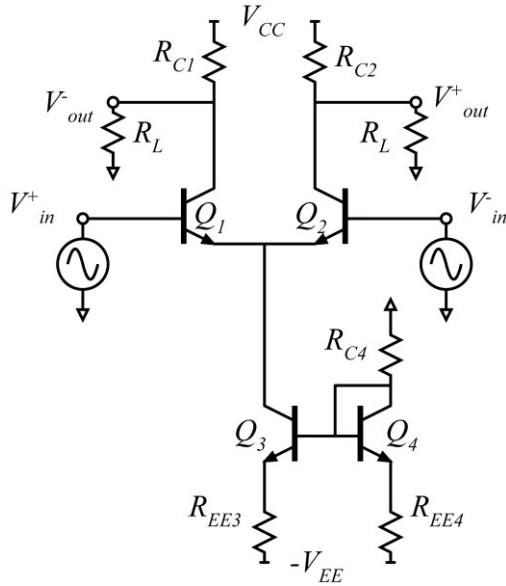Problem 3 The circuit above uses 2n3904 bjts. -
 -uses datasheet values for beta and Rce. For DC bias, V_{in+} and V_{in-} are zero volts. $V_{cc} = +5V$, $V_{ee} = -5V$. The DC emitter currents are each 0.5 mA, and the DC collector voltages are 0.0 V. $R_{L1,2}$ are 10 k Ω . Find all resistor values. Find the bias conditions, the differential input impedance, the differential gain, and the common-mode rejection ratio.



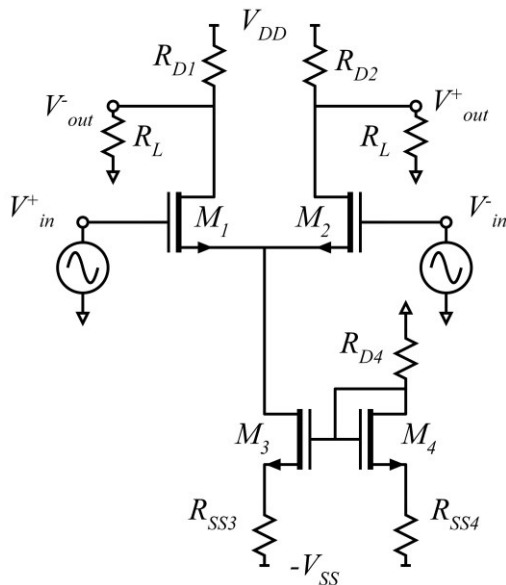Problem 4 The circuit now uses a constant current source to bias the differential amplifier. For Q1 and Q2 the DC collector voltages and DC collector currents remain the same as in problem 2. There is a 0.30 V IR drop across REE3, while the DC current in REE4 is 1/10th of the emitter current of REE3. Find all resistor values. Find the bias conditions, the differential and common-mode gains, and the common-mode rejection ratio. The diode has the same "on" voltage as the transistors.



Problem 5 The NMOSFETs have $v_{th} = 0.25$ V
 $K_{\mu} = 10 \text{ mA/V}^2 \cdot (W_g / 1 \mu\text{m})$
 $K_v = 2.0 \text{ mA/V} \cdot (W_g / 1 \mu\text{m})$
 $\Delta V = 100 \text{ mV}$, $1/\lambda = 5$ Volts
 The supplies are + and - 1.0 Volts. M1 and M2 are to carry 0.2 mA drain current at $V_{gs} = 0.35$ V. M3 and M4 have equal gate widths and have $V_{gs} = 0.35$ V. The drain voltages of M1 and M2 are to be 0.25 Volts. The load resistances (R_{L1} , R_{L2}) are 100 kOhm. Find all resistor values. Find the bias conditions, FET widths, the differential and common-mode gains, and the common-mode rejection ratio.