

## Mid-Term Exam, ECE-137B

May 12 , 2006

### Closed-Book Exam

There are 2 problems on this exam , and you have 50 minutes.

**1) show all work. Full credit will not be given for correct answers if supporting work is not shown.**

2) please write answers in provided blanks

3) Don't Panic !

4) 137a, 137b crib sheets, and 2 pages personal sheets permitted.

**Do not turn over the cover page until requested to do so.**

Name:


\_\_\_\_\_

Use any and all reasonable approximations. 5% accuracy is fine if the method is correct.

Time function	LaPlace Transform
$\delta(t)$	1
$U(t)$	$1/s$
$e^{-\alpha t}U(t)$	$\frac{1}{s + \alpha}$
$e^{-\alpha t} \cos(\omega_d t)U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha t} \sin(\omega_d t)U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Problem	Points Received	Points Possible
1a		25
1b		25
1c		50
total		100

**Problem 1, 100 points**

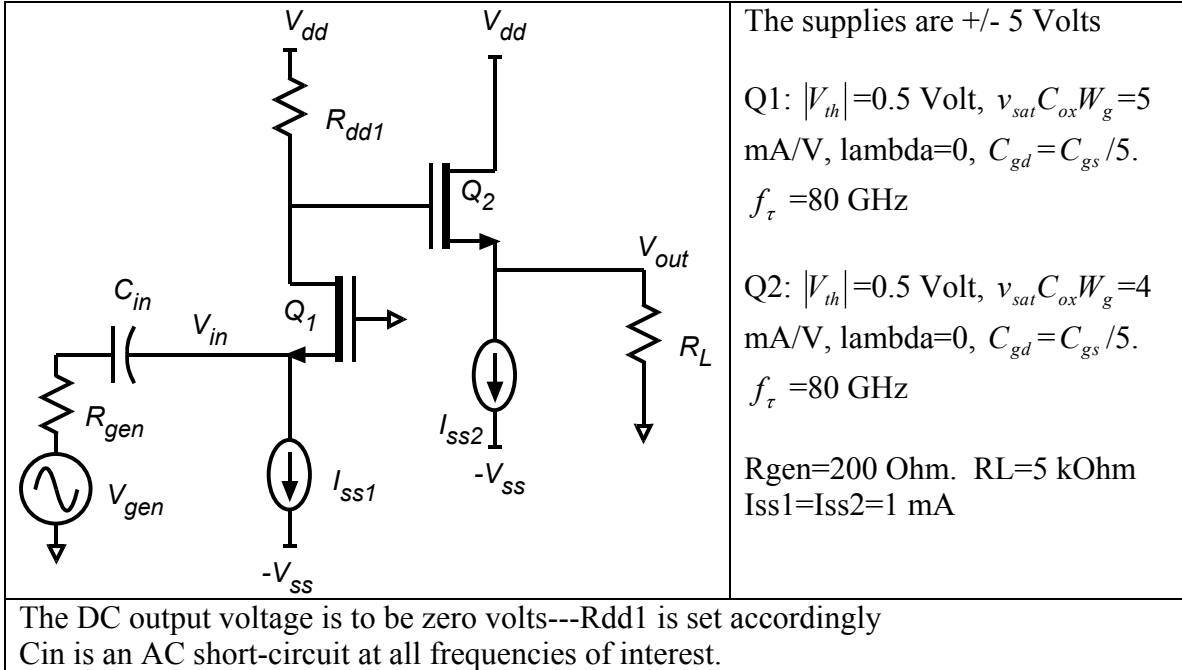

Part a, 25 points

Find the following

$R_{dd1} =$  \_\_\_\_\_ DC voltage at the drain of Q1 = \_\_\_\_\_

$C_{gd}$  of Q1 = \_\_\_\_\_  $C_{gs}$  of Q1 = \_\_\_\_\_

$C_{gd}$  of Q2 = \_\_\_\_\_  $C_{gs}$  of Q2 = \_\_\_\_\_

Part b, 25 points

*Mid Band Analysis:*

Find the mid-band small signal voltage gain of Q2 (the small signal voltage at the source of Q2 divided by the small signal voltage at the gate of Q2)

$A_{v2} = \underline{\hspace{2cm}}$

Find the mid-band small signal voltage gain of Q1 (the small signal voltage at the drain of Q1 divided by the small signal voltage at the source of Q1)

$A_{v1} = \underline{\hspace{2cm}}$

Find  $V_{in}/V_{gen}$

$V_{in}/V_{gen} = \underline{\hspace{2cm}}$



Part c:50 points

The circuit has 3 poles and one zero in its transfer function.

Give the frequencies of these in Hz:

$$f_{p1} = \underline{\hspace{2cm}}, f_{p2} = \underline{\hspace{2cm}}$$

$$f_{p3} = \underline{\hspace{2cm}} \quad f_z = \underline{\hspace{2cm}}$$



