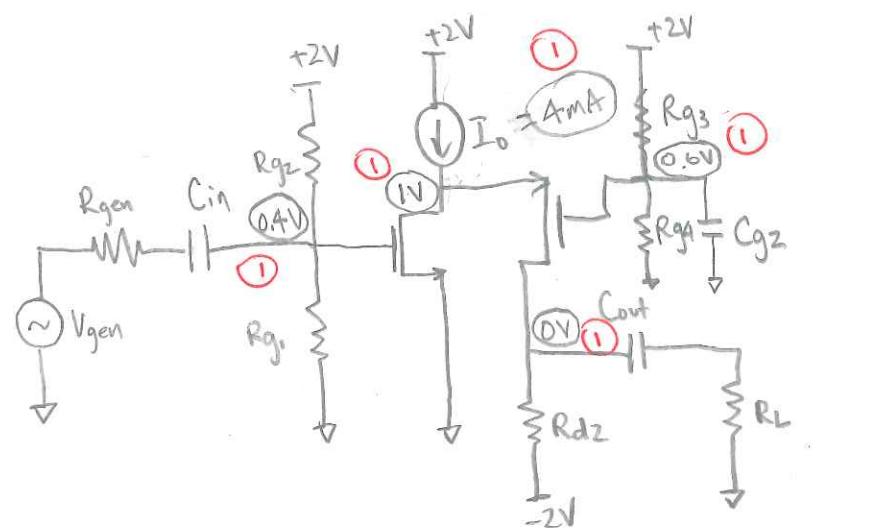


137B Midterm B

Solutions

Problem 1g

10 pts



~~RE=2~~

$$R_{g1} = 1 M\Omega$$

$$\frac{R_{g1}}{R_{g1} + R_{g2}} = \frac{0.4}{2} = \frac{1}{5}$$

$$R_{g2} = 4 M\Omega$$

(2)

$$R_{g4} = 1 M\Omega$$

$$\frac{R_{g4}}{R_{g4} + R_{g3}} = \frac{0.6}{2}$$

$$R_{g3} = 2.33 M\Omega$$

(2)

$$R_{d2} = \frac{(0 - (-2V))}{2mA} = 1k\Omega$$

(1)

Problem 1b

10 pts

For Q<sub>1</sub>:  $g_{m1} = \frac{\partial I_{DS}}{\partial V_{GS}} = (2)(3.7) \left( \frac{W_g}{1\mu m} \right) (V_{GS} - V_{th}) = 40 \text{ mS}$

$$W_g = \frac{\frac{I_D}{2mA}}{(V_{GS} - V_T)^2 (3.7 \frac{mA}{V^2})} \cdot 1\mu m = 54\mu m$$

$\downarrow$   
 $= 0.1V$

For Q<sub>2</sub>:  $g_{m2} = \frac{\partial I_{DS}}{\partial V_{GS}} = (-2)(3.7) \left( \frac{W_g}{2\mu m} \right) (V_{GS} - V_T) = 40 \text{ mS}$

$$W_g = \frac{\frac{I_D}{2mA}}{(V_{GS} - V_T)^2 (3.7 \frac{mA}{V^2})} \cdot 2\mu m = 108\mu m$$

For Q<sub>2</sub>: Common Gate ①

$$\frac{V_{d2}}{V_{S2}} = \frac{R_{L,EQ}}{R_{in}} = \frac{230\Omega}{25\Omega} = 9.2 = A_{V_1}$$

$$R_{in,2} \approx \frac{1}{g_m} = 25\Omega \quad R_{L,EQ} = R_{S2} \parallel R_L = 230\Omega$$

For Q<sub>1</sub>: Common Source ①

$$\frac{V_{d1}}{V_{G1}} = -g_m R_{L,EQ} = -g_m R_{in,2} = -1 = A_{V_2} \quad ①$$

$$R_{in,1} = R_{g1} \parallel R_{g2} = 800k\Omega \quad ①$$

$$\frac{V_{out}}{V_{in}} = (A_{v_1})(A_{v_2}) = \boxed{-9.2} \quad \textcircled{1}$$

$$\frac{V_{out}}{V_{gen}} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_{gen}} = (-9.2) \left( \frac{800\text{ k}}{800\text{k}+1\text{k}} \right) = \boxed{-9.19} \quad \textcircled{1}$$

### Problem 1c

10 pts

$$C_{ox} = \frac{\epsilon_0 (3.8)}{t_{ox}} = \frac{(8.85 \times 10^{-12})(3.8)}{10^{-9}} = 0.0336 \text{ F/m}^2 \quad \textcircled{2}$$


$$C_{gs_1} = C_{ox} L_{g_1} W_{g_1} = (0.0336)(54 \times 10^{-6} \text{ m})(180 \times 10^{-9} \text{ m}) = \boxed{326.6 \text{ fF}} \quad \textcircled{2}$$

$$C_{gd_1} = \frac{1 \text{ fF}}{\mu\text{m}} \cdot W_g = \left( \frac{W_{g_1}}{1 \mu\text{m}} \right) \cdot 1 \text{ fF} = \boxed{54 \text{ fF}} \quad \textcircled{2}$$


$$C_{gs_2} = C_{ox} L_{g_2} W_{g_2} = \boxed{653.2 \text{ fF}} \quad \textcircled{2}$$

$$C_{gd_2} = \left( \frac{W_{g_2}}{1 \mu\text{m}} \right) \cdot 1 \text{ fF} = \boxed{108 \text{ fF}} \quad \textcircled{2}$$

## Problem 1d

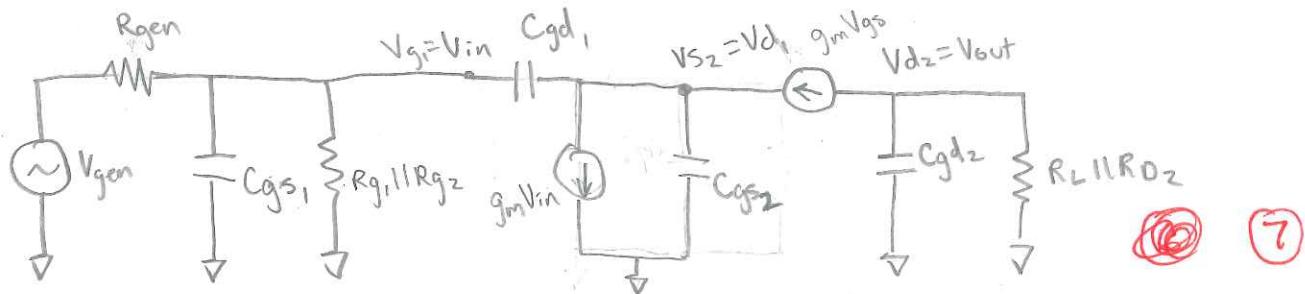

Using the T-model,

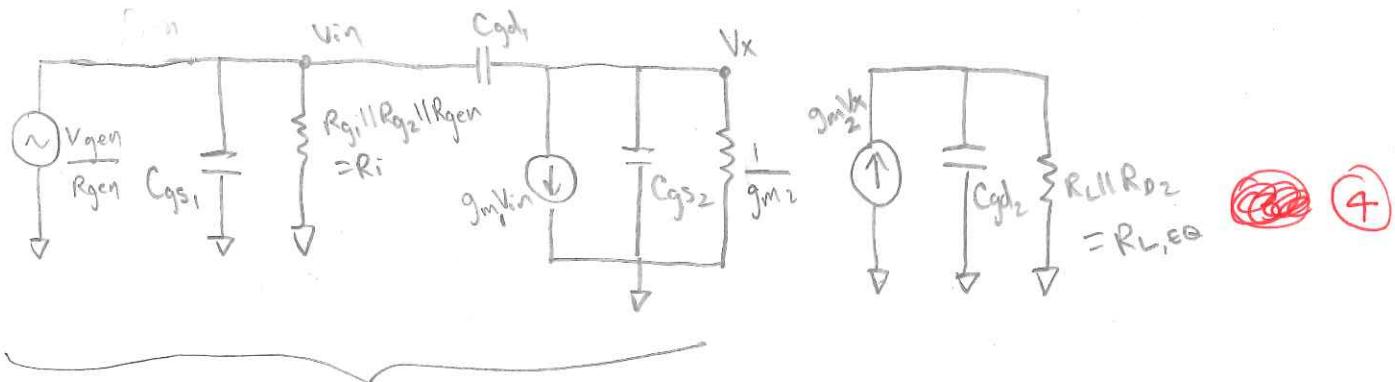

Common Source (1<sup>st</sup> stage)

$$a_1 = C_{gs}R_i + C_{gd}(R_i(1+g_{m1}\frac{1}{g_{m2}}) + \frac{1}{g_{m2}})$$

$$+ \frac{C_{gs2}}{g_{m2}}$$

$$\frac{V_x}{V_{gen}} = A_{v1} \frac{1 + b_1 s}{1 + a_1 s + g_2 s^2}$$

$$R_i \sim R_{gen} = 1 k\Omega$$

$$= (326 fF)(1 k\Omega) + (54 fF)(2 k\Omega + 25 \Omega) + (25 \Omega)(653.2 fF)$$

$$= \underline{4.52 \times 10^{-10}} = 452 \text{ ps} \quad (1)$$

$$a_2 = R_i \left( \frac{1}{g_m z} \right) \left[ (C_{gs1})(C_{gd1}) + (C_{gs1})(C_{gs2}) + (C_{gd1})(C_{gs2}) \right]$$

$$= (1 \text{ k}\Omega)(25 \text{ }\Omega) \left[ (326.6 \text{ fF})(54 \text{ fF}) + (326.6 \text{ fF})(653.2 \text{ fF}) + (653.2 \text{ fF})(54 \text{ fF}) \right]$$

$$= \frac{6.656 \times 10^{-21} \text{ s}}{\text{ }} \quad (1)$$

$$b_1 = -\frac{C_{gd1}}{g_m} = -\frac{(54 \text{ fF})}{40 \text{ mS}} = \frac{1.35 \text{ ps}}{\text{ }} \quad (1)$$

First stage introduces a zero @  $\frac{1}{2\pi b_1} = 117.9 \text{ GHz}$  (1)

$$\text{pole } @ \frac{1}{2\pi a_1} = 352.1 \text{ MHz} \quad \} \quad (3)$$

$$\text{pole } @ \frac{1}{2\pi \left( \frac{a_2}{a_1} \right)} = 10.8 \text{ GHz} \quad \}$$

## Common Gate (2<sup>nd</sup> stage)


$$\frac{V_{out}}{V_x} = g_m z (C_{gd2} || R_{L,eq}) = A v_z \frac{1}{1 + R_{L,eq} C_{gd2} \cdot s} \xrightarrow{24.8 \text{ ps}} \quad (1)$$

So this adds a pole at  $\frac{1}{2\pi (R_{L,eq} C_{gd2})} = \frac{1}{2\pi (230 \Omega \cdot 108 \text{ fF})}$

$$= 6.41 \text{ GHz} \quad (1)$$

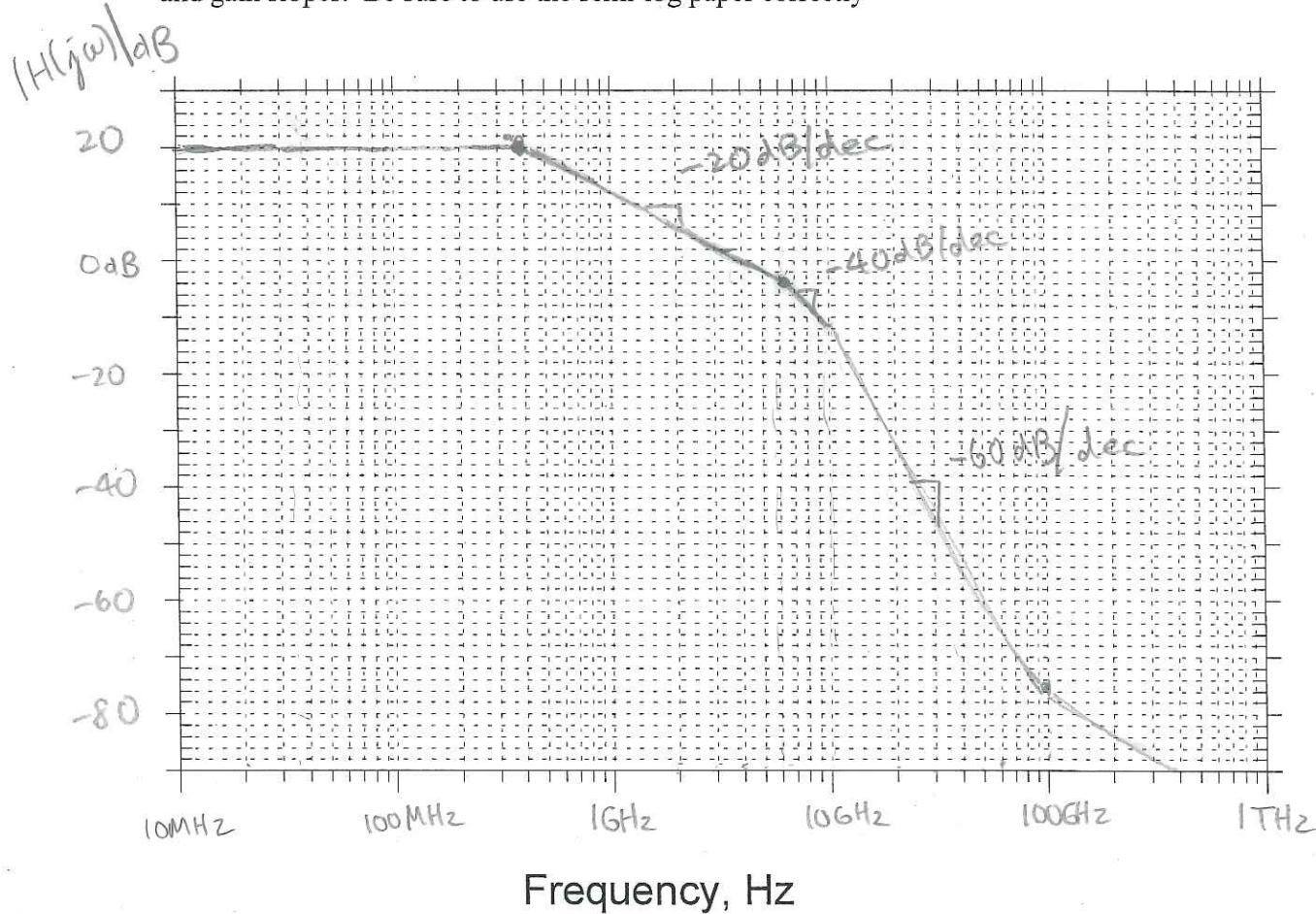Part e: 10 points

Draw a clean asymptotic Bode Magnitude plot of  $V_{out}/V_{gen}$  as a function of frequency in Hz. Be sure to label and dimension the axes clearly, label pole and zero frequencies and gain slopes. Be sure to use the semi-log paper correctly



$$\text{Midband Gain} = 20 \log(9.2) = 19.28 \text{ dB}$$

Poles @ 352 MHz, 6.4 GHz, 10.8 GHz

Zero @ 11.8 GHz

axis ②

flat low-freq ①



low-freq mag ①

pole/zero locations ③

pole/zero slopes ③

Problem 2, 40 points

Part a 10 points

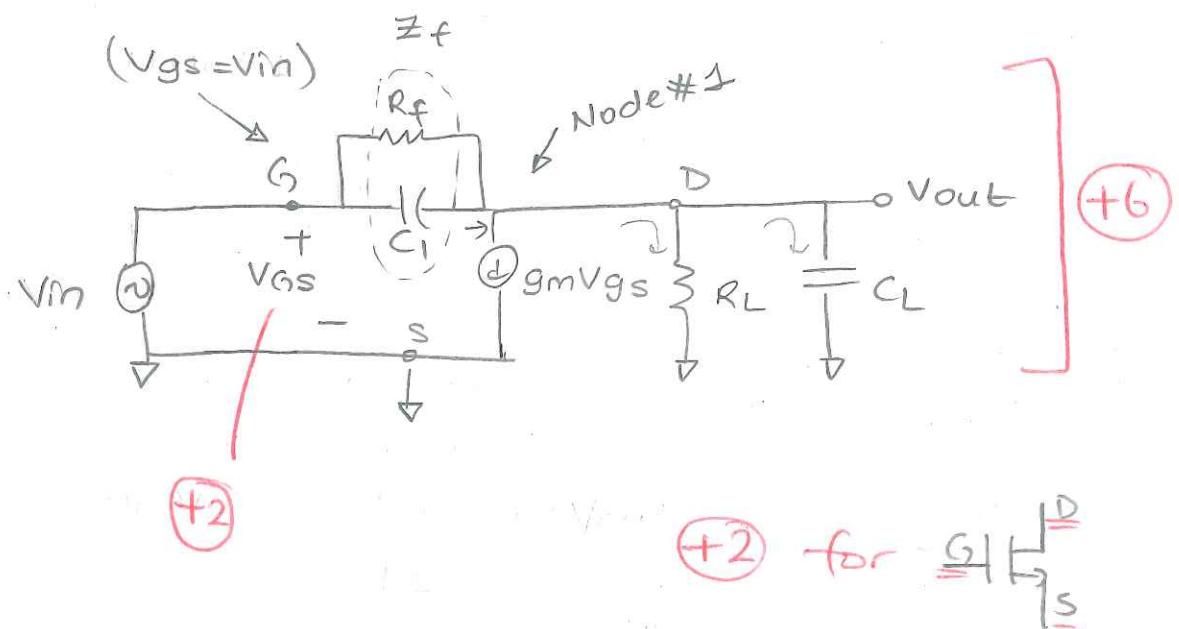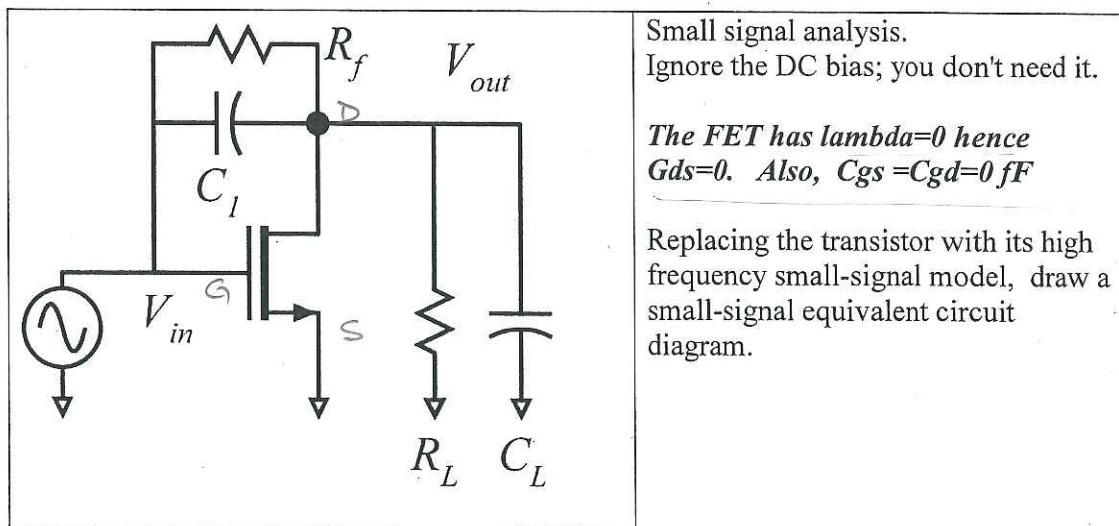

Part b, 10 points

**USING NODAL ANALYSIS**, compute  $V_{out}(s)/V_{gen}(s)$  in ratio-of-polynomials form:

$$\frac{V_{out}(s)}{V_{gen}(s)} = \left. \frac{V_{out}}{V_{gen}} \right|_{mid-band} \times (s\tau)^m \times \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots} = \frac{\dots}{\dots}$$

here  $m$ , an integer, can be positive or negative or zero

$\sum I = 0$  @ node #1:

$$gmV_{gs} + \frac{V_{out}}{R_L} + V_{out} \cdot sC_L = \frac{V_{in} - V_{out}}{Z_f} \quad (6)$$

where  $V_{gs} = V_{in}$

$$Z_f = R_f \parallel \frac{1}{sC_1} = \frac{R_f \cdot \frac{1}{sC_1}}{R_f + \frac{1}{sC_1}} = \frac{R_f}{1 + sC_1 R_f}$$

$$V_{out} \left( \frac{1}{R_L} + sC_L + \frac{1 + sC_1 R_f}{R_f} \right) = V_{in} \left( \frac{1 + sC_1 R_f}{R_f} - gm \right)$$

$$V_{out} \left( \frac{1}{R_L} + sC_L + \frac{1}{R_f} + sC_1 \right) = V_{in} \left( \frac{1}{R_f} + sC_1 - gm \right)$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{(1 + sC_1 R_f - gm R_f) R_L}{(R_f + sC_L R_f R_L + R_L + sC_1 R_f R_L)}$$

$$= \frac{(1 - gm R_f) R_L \left[ 1 + s \frac{C_1 R_f}{1 - gm R_f} \right]}{(R_f + R_L) \left[ 1 + s \frac{R_f R_L (C_L + C_1)}{R_f + R_L} \right]}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{(1-gmR_f) R_L}{R_f + R_L} \quad \frac{1 + s \left( C_1 R_f / (1-gmR_f) \right)}{1 + s \left( \frac{R_f R_L (C_L + C_1)}{R_f + R_L} \right)}$$

①

③

Part c, 10 points

$gm = 10 \text{ mS}$ ,  $R_L = 1000 \text{ Ohm}$ ,  $R_f = 2000 \text{ Ohm}$ ,  $C_1 = 1 \text{ pF}$ ,  $C_L = 2 \text{ pF}$ .

Find the frequencies of any zeros (there may be zero, one or two present) in the transfer function:

$$f_{z1} = \underline{1.516 \text{ Hz}}, f_{z2} = \underline{\cancel{X}}, \dots$$

There may be either 1 or 2 poles of the transfer function.

If the poles are real, give the 1 or 2 pole frequencies in Hz:

$$f_{p1} = \underline{79.6 \text{ MHz}}, f_{p2} = \underline{\cancel{X}}$$

If there are 2 poles, and they are complex, give  $f_n = \omega_n / 2\pi$  and the damping factor  $\zeta$ :

$$f_n = \omega_n / 2\pi = \underline{\cancel{X}}, \zeta = \underline{\cancel{X}}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-\frac{19}{3}}{-6.33} \cdot \frac{1 - s/9.5 \times 10^9 \frac{1}{\text{sec}}}{1 + s/0.5 \times 10^9 \frac{1}{\text{sec}}} \quad \text{①}$$

One zero &  
One pole ①

$$Z_1 = -9.5 \times 10^9 \frac{1}{\text{sec}}$$


$$f_{z1} = \left| \frac{Z_1}{2\pi} \right| = 1.51 \times 10^9 \text{ Hz} = \underline{\underline{1.516 \text{ Hz}}} \quad \text{④}$$

$$P_1 = -0.5 \times 10^9 \frac{1}{\text{sec}}$$

$$f_{p1} = \left| \frac{P_1}{2\pi} \right| = 7.96 \times 10^7 \text{ Hz} = \underline{\underline{79.6 \text{ MHz}}} \quad \text{④}$$

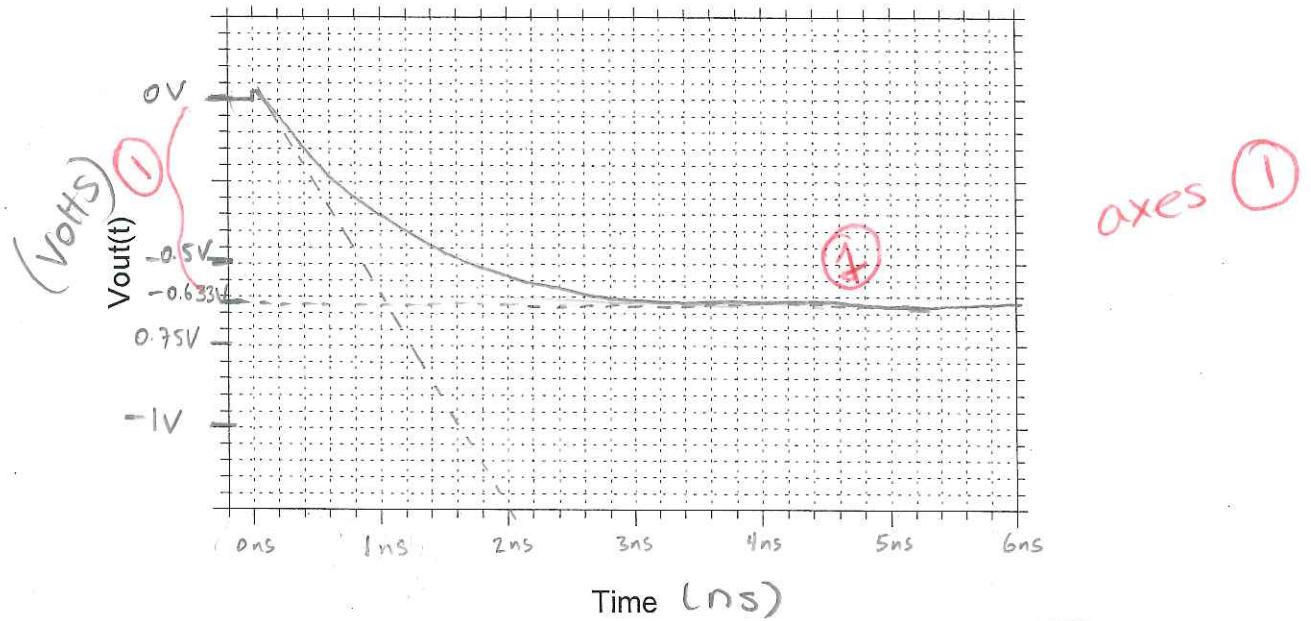Part d, 10 points

If  $V_{in}(t)$  is a 100mV step-function, find and plot  $V_{out}(t)$ . Be sure to label and dimension the axes clearly, and to clearly label key features of the time waveform.



$$V_{in}(+) = 0.1V u(t) \Rightarrow V_{in}(s) = \frac{0.1V}{s} \quad ①$$

$$V_{out}(s) = V_{in}(s) \cdot \frac{V_{out}(s)}{V_{in}(s)} = \frac{0.1V}{s} \cdot (-6.33) \quad \frac{1 - s/(9.5 \times 10^9 \text{ sec})}{1 + s/(0.5 \times 10^9 \text{ sec})} \quad ①$$

$$= (-0.633V) \frac{1 - s/(9.5 \times 10^9 \text{ sec})}{s(1 + s/(0.5 \times 10^9 \text{ sec}))}$$

Partial fraction:

$$\frac{1 - s(1.05 \times 10^{-10} \text{ seconds})}{s(1 + s(2 \times 10^{-9} \text{ seconds}))} = \frac{A}{s} + \frac{B}{1 + s(2 \times 10^{-9} \text{ sec})}$$

$$1 - s(1.05 \times 10^{-10} \text{ sec}) = A + s(A \cdot 2 \times 10^{-9} \text{ sec}) + sB$$

$$\Rightarrow \boxed{A=1}$$

$$2 \times 10^{-9} \text{ sec} + B = -1.05 \times 10^{-10} \text{ sec} \quad \textcircled{1}$$

$$\boxed{B = -2.105 \times 10^{-9} \text{ sec}}$$

$$V_{out}(s) = (-633 \text{ mV}) \left[ \frac{1}{s} - \frac{\frac{1.05}{2.1 \text{ nsec}}}{1 + s(2 \text{ nsec})} \right] \quad \textcircled{2}$$

$$U_{out}(s) = (-633 \text{ mV}) \left[ \frac{1}{s} - \frac{\frac{1.05}{2 \text{ nsec}}}{1 + s} \right]$$

$$\boxed{V_{out}(t) = -\frac{0.633 \text{ V}}{0.633 \text{ V}} u(t) \left[ 1 - 1.05 e^{-t/2 \times 10^{-9} \text{ sec}} \right]} \quad \textcircled{1}$$

$$= -633 \text{ mV } u(t) + 665 \text{ mV } e^{-t/2 \text{ nsec}} u(t)$$