

**ECE137B Final Exam**

6/11/2015, 8-11AM.

There are 4 problems on this exam and you have 3 hours  
 There are pages 1-21 in the exam: please make sure all are there.

Do not open this exam until told to do so.

Show all work.

Credit will not be given for correct answers if supporting work is not shown.

Class Crib sheets and 3 pages (front and back → 6 surfaces) of your own notes permitted.  
 Don't panic.

Time function	LaPlace Transform
$\delta(t)$	1
$U(t)$	$1/s$
$e^{-\alpha t} \cdot U(t)$	$\frac{1}{s + \alpha}$ or $\frac{1}{1 + s/\alpha}$
$e^{-\alpha t} \cos(\omega t) \cdot U(t)$	$\frac{s + \alpha}{s^2 + \omega^2 + \alpha^2}$
$e^{-\alpha t} \sin(\omega t) \cdot U(t)$	$\frac{\omega}{s^2 + \omega^2 + \alpha^2}$

*Solution - Exam (a)*

Name: \_\_\_\_\_

Problem	points	possible	Problem	points	possible
1a	5	5	2c	5	5
1b	5	5	3a	10	10
1c	15	15	3b	10	10
1d	10	10	4a	10	10
1e	5	5	4b	10	10
2a	5	5			
2b	10	10	total		

$$\Rightarrow A_{\infty} = \frac{v_o}{v_{in}} = \frac{R_1}{R_1 + R_2} = 10$$

$$v_T = v^- = \frac{R_1}{R_1 + R_2} v_{out}$$


$A_{\infty}$  corresponds to the gain when  $A_d \rightarrow \infty$  hence when  $v^+ = v^- \rightarrow$  no current in  $C_{gs2}$

$$A_{\infty} = \frac{v_o}{v_{in}}$$

In the relationship  $A_{CL} = A_{\infty} \frac{1}{1+T}$ , what is  $A_{\infty}$  for this circuit?

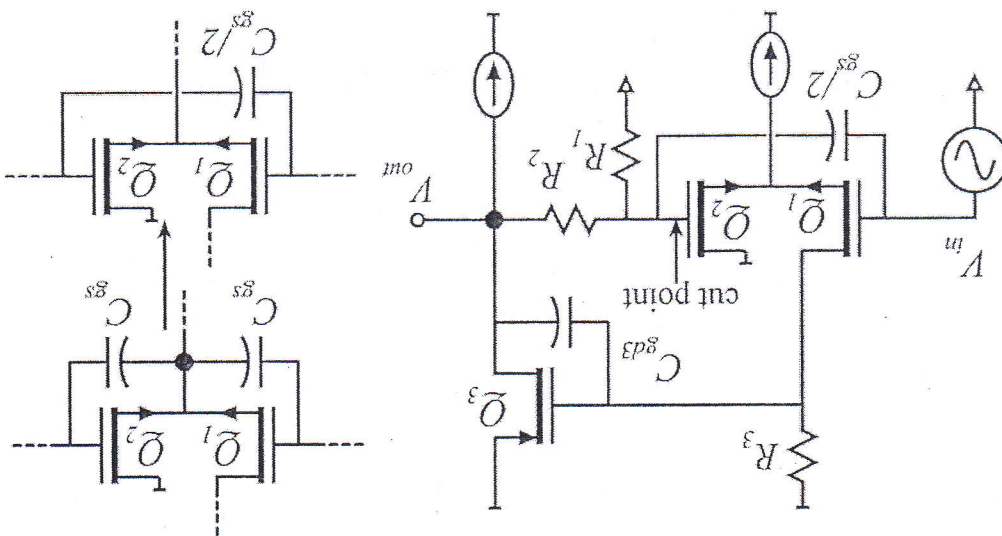Part a. 5 points  
feedback relationships

Note: simplify the problem by using the approximation shown above right.  
 $C_{gs1} = C_{gs2} = 127 \text{ fF}$ ,  $C_{gd1} = C_{gd2} = 0 \text{ fF}$ ,  $C_{gs3} = 0 \text{ fF}$ ,  $C_{gd3} = 159 \text{ fF}$ .  
 $R_3 = 10 \text{ k}\Omega$ ,  $R_{DS} = \text{infinity } \Omega$  for all FETs  
 In the circuit above  $g_{m1} = g_{m2} = 20 \text{ mS}$ ,  $g_{m3} = 10 \text{ mS}$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 9 \text{ k}\Omega$ .




Problem 1, 40 points  
frequency response, negative feedback

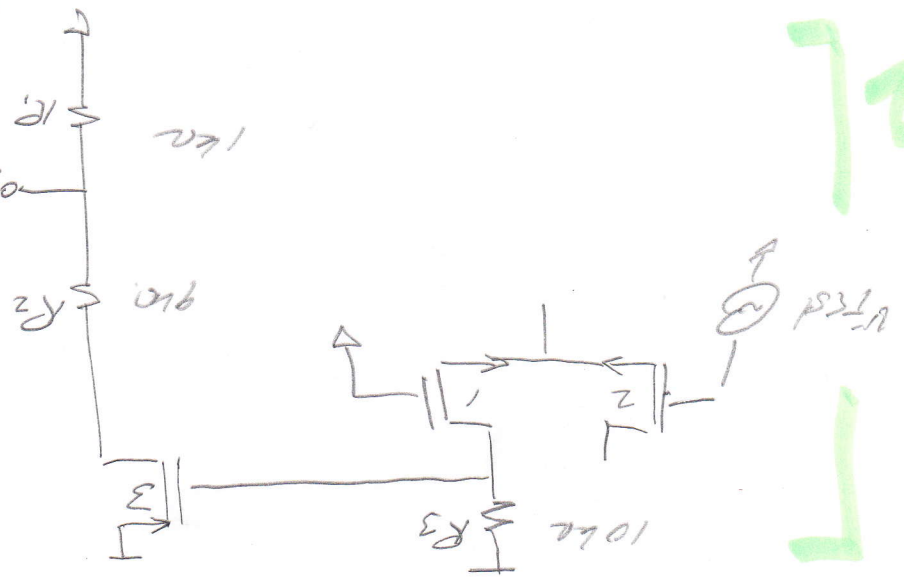Part b, 5 points  
feedback relationships

Find the value of the loop transmission at DC and the closed loop gain at DC.  
Hint---I recommend using the indicated cut point.

$$T = \frac{10^3}{A_{cl}} = \frac{10^3}{9.9990}$$



$$g_{m1} = g_{m2} = 20\text{mS}$$

$$g_{m1,2} = (g_{m1} + g_{m2})^{-1} = 10\text{mS}$$

$$g_{m3} = 10\text{mS}$$

$$T = g_{m1,2} \cdot R_3 \cdot g_{m3} \cdot R_1$$

$$= 10\text{mS} \cdot 10\text{k}\Omega \cdot 10\text{mS} \cdot 1\text{k}\Omega$$

$$= 100 \cdot 100 = 10^3$$

$$A_{cl} = \frac{1}{1+T} = \frac{1}{1+10^3} \approx \frac{1}{10^3}$$

$$= 10 \cdot (1-10^{-4}) = 10(0.9999) = 9.9990$$

Part c. 15 points

transistor circuit frequency response.

Find the first two pole frequencies of the loop transmission  $T$ .

$$f_{p1} = 1 \text{ MHz} \quad f_{p2} = 2.8 \text{ GHz}$$


$$R_3 = 10 \text{ k}\Omega$$

$$g_{m2} = (g_{m1} + g_{m2})^{-1}$$

$$= 10 \text{ mS}$$

$$g_{m3} = 100 \text{ mS}$$

$$C_{gd3} = 15 \text{ pF}$$

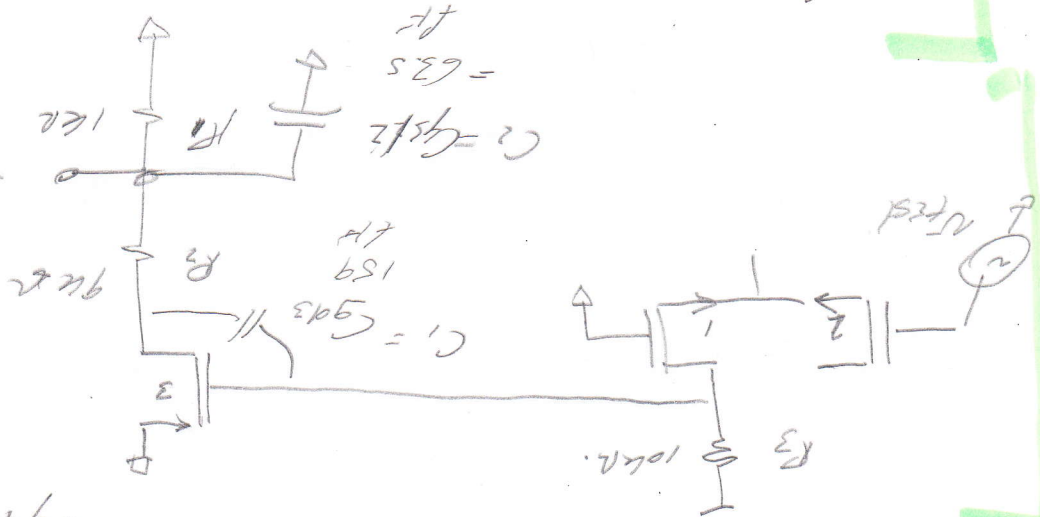

$$R_{in} = [R_3 (1 + g_{m3} (R_1 + R_2)) + (R_1 + R_2)]$$

$$= [10 \text{ k}\Omega (101) + 10 \text{ k}\Omega]$$

$$= 102 [10 \text{ k}\Omega] = 1 \text{ M}\Omega + 20 \text{ k}\Omega = 1.02 \text{ M}\Omega$$

$$\approx 1 \text{ M}\Omega$$

$$R_{OC1} = 1 \text{ M}\Omega \cdot 15 \text{ pF} = 15 \text{ nSec}$$

$$R_{OC2} = 1 \text{ k}\Omega \quad (\text{not } 1 \text{ k}\Omega // 9 \text{ k}\Omega!)$$


$$R_{OC2} C_2 = 1 \text{ k}\Omega \cdot 63.5 \text{ pF} = 63.5 \text{ pSec}$$

$$a_1 = 15 \text{ nS} + 63.5 \text{ pS} = 159.063 \text{ nS} \approx 159 \text{ nS}$$

other approach for  $a_2$

$$R_{11}^2 C_1 C_2 R_{22}^0 = 9.19 \mu s \cdot 159 \mu s \cdot (63.5 \mu s) = 9.28 \cdot 10^{-16} \text{ sec}^2$$

$$= 9.19 \mu s$$

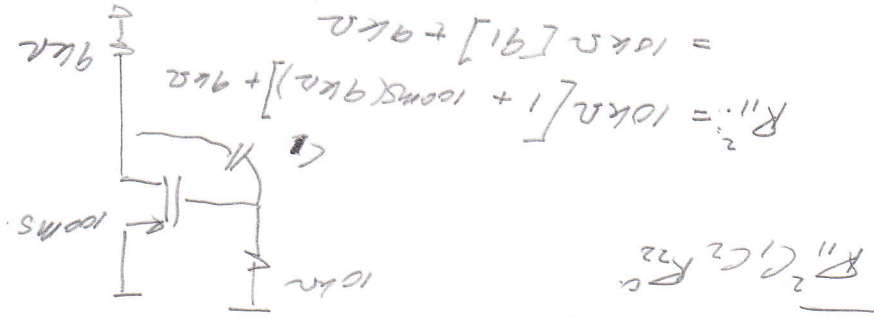


2

SPA:  $a_1 = 159 \mu s$   
 $a_2/a_1 = (159 \mu s) / (57.2 \mu s) = 2.78$   
 $f_{p1} = 0.159 / (2\pi \cdot 159 \mu s) = 1 \text{ MHz}$   
 $f_{p2} = 0.159 / (2\pi \cdot 9.19 \mu s) = 2.78 \text{ GHz}$

SPA objective

one approach for  $a_2$

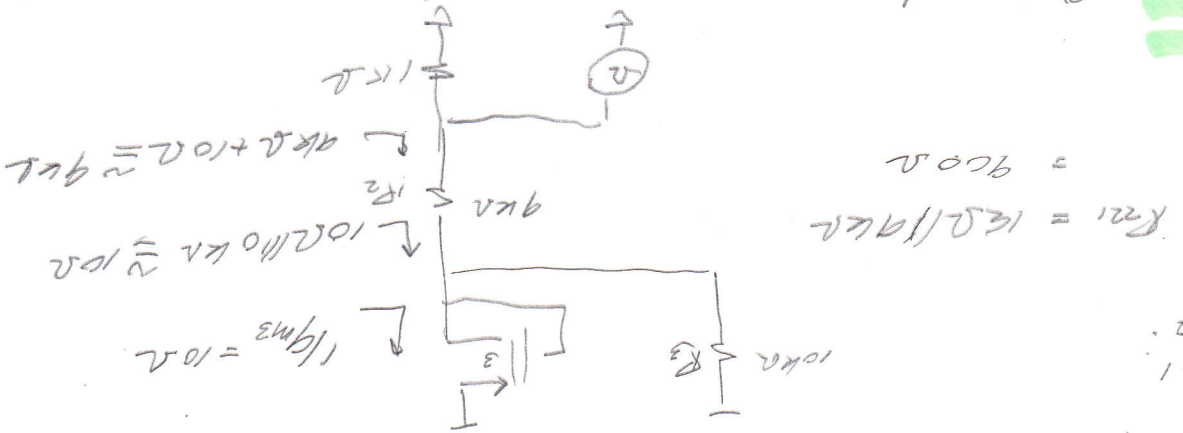more useful form!  
 $R_{11}^0 C_1 C_2 R_{22}^1 = (159 \mu s) (63.5 \mu s) 900 \mu s = 9.09 \cdot 10^{-18} \text{ sec}^2 = (301 \text{ ns})^2$




now for  $a_2$  - there are two approaches

3



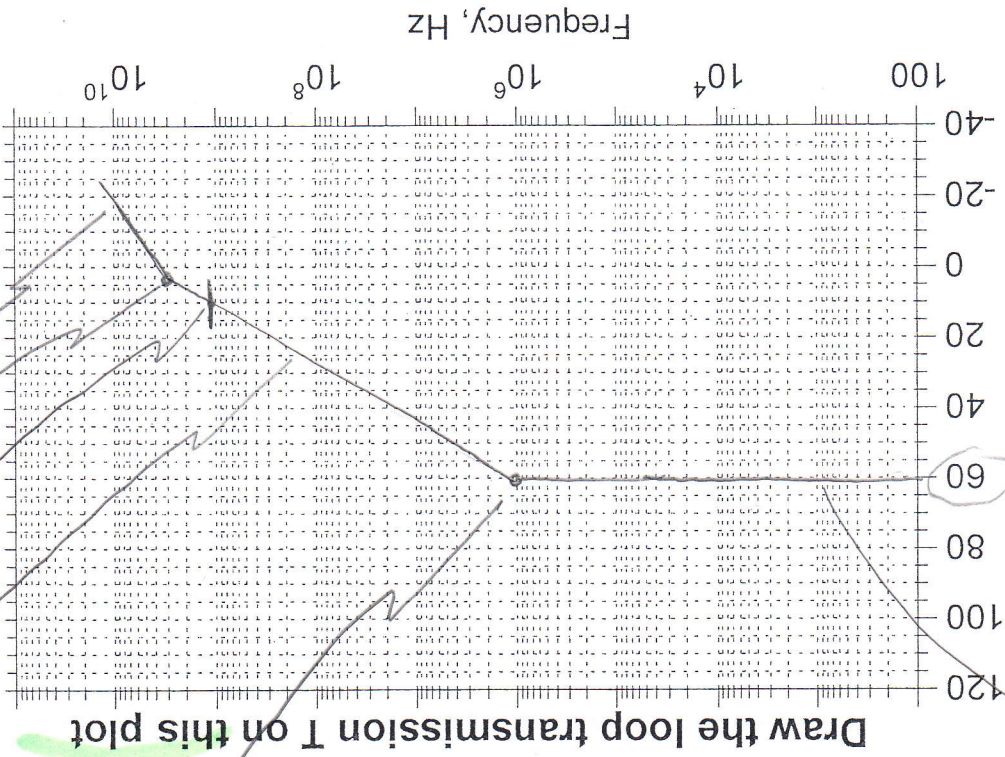$\angle T = -90^\circ - \arctan(1 \text{ GHz} / 2.5 \text{ GHz}) = -90^\circ - 21.1^\circ = -111.1^\circ$   
 $= -90^\circ - 19.65^\circ = -109.65^\circ$   
 Phase margin =  $90 - 19.65 = 71.35^\circ$



$f_{p1} = 1 \text{ GHz}$   
 $f_{p2} = 2.5 \text{ GHz}$   
 $-40 \text{ dB/dec}$   
 $-20 \text{ dB/dec}$

Draw the loop transmission T on this plot

$f_{p2} = 1 \text{ MHz}$

$f_{loop} = 1 \text{ GHz}$ , phase margin =  $71.35^\circ$   
 Determine the loop bandwidth and phase margin

Plot the loop transmission (label slopes, label critical frequencies)

loop bandwidth and stability.

Part d. 10 points

$T_{DC} = 10^3 = 60 \text{ dB}$   
 $f_{p1} = 1 \text{ MHz}$   
 $f_{p2} = 2.8 \text{ GHz}$   
 $T_{DC} \cdot f_{p1} = 1 \text{ GHz} < f_{p2}$   
 $f_{loop} = 1 \text{ GHz}$

$60 \text{ dB}$   
 $T_{DC} = 60 \text{ dB}$

Part e, 5 points

closed-loop bandwidth

$$A_{cl} = A_{oc} \frac{1}{1+T}$$

for  $T \gg 1$   
 $A_{oc}(e^{j\omega})(1+e^{j\omega})$  for  $T = e^{j\omega} (N+1)$


for  $T \ll 1$

Plot the closed-loop gain vs. frequency, estimating the gain peaking at  $f_{loop}$

Estimate the amplifier's closed loop bandwidth

closed-loop bandwidth =

Draw the closed loop gain on this plot

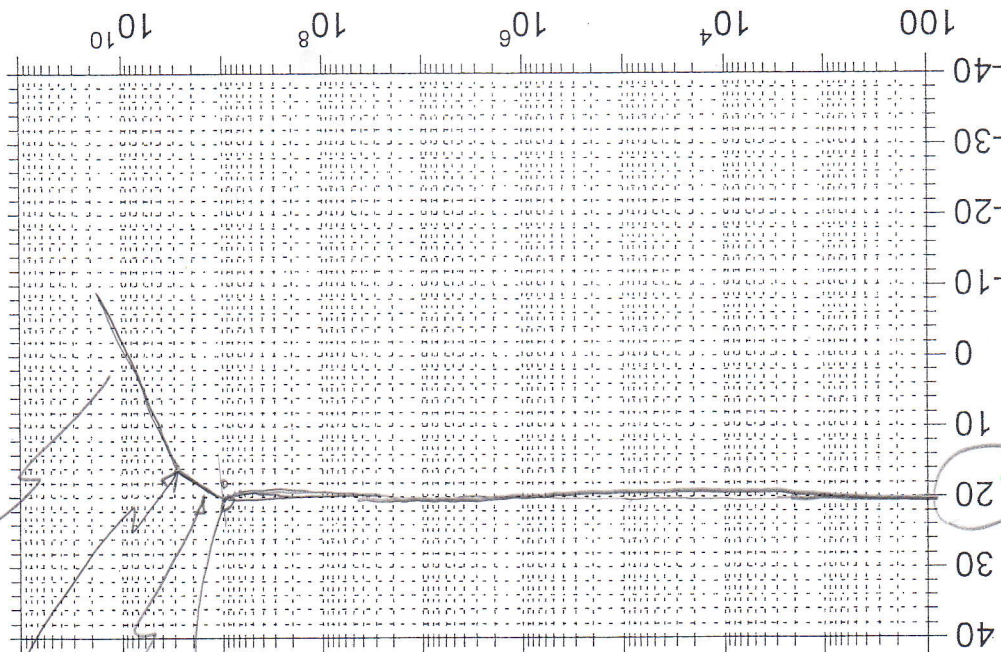

at  $f_{loop}$ ,  $\angle T = -109.68^\circ = -1.91 \text{ rad.ans.} = \theta$

$$\left| \frac{e^{j\omega} T}{1+T} \right| = \left| \frac{e^{j\omega}}{1+e^{j\omega}} \right| = \frac{1}{|1+e^{j\omega}|} = \frac{1}{\sqrt{1+\cos\theta + j\sin\theta}}$$

$\cos\theta = -0.336$   
 $\sin\theta = 0.94$

$$\frac{1-0.336 + j0.94}{1-0.336 + j0.94} = 1$$


$= -1.23 \text{ dB}$

Negligible peaking

no peaking at  $f_{loop}$  (possibly tiny peaking @  $f_{in}$ )

Problem 2, 20 points

Circuit frequency response by MOTC.

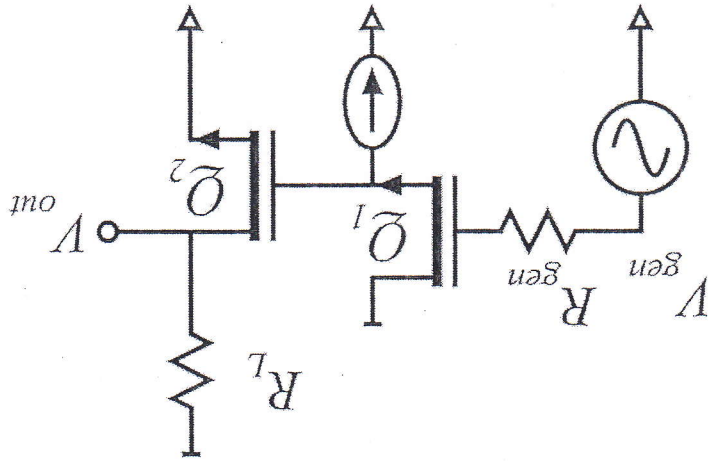

In the circuit above  $g_{m1}=10\text{mS}$ ,  $g_{m2}=50\text{mS}$ .

$R_{gen}=1000\ \Omega$ ,  $C_{gs1}=15.9\text{fF}$ ,  $C_{gs2}=79.5\text{fF}$ ,  $C_{gd1}=C_{gd2}=0\text{fF}$ .

$R_{DS} = \text{infinity}\ \Omega$  for both FETs

$R_L = 1\text{ k}\Omega$ .

part a. 5 points

midband analysis

Find the gain  $V_{out}/V_{gen}$  at low frequencies.  $V_{out}/V_{gen} =$  50

$V_{gs}/V_{gen} = 1$

$A_{v01} = 1$

$A_{v2} = -g_{m2} R_L = -50\text{mS} \cdot 1\text{k}\Omega = -50$




part b. 10 points  
frequency response analysis

Find  $a_1, a_2$ . If the poles are real, find  $f_{p1}$  and  $f_{p2}$ ; if they are complex, find  $f_n$  and  $\zeta$

$$a_1 = \frac{23.9 \text{ pps}}{1.3 \times 10^{-21} \text{ sec}^2}$$

$$a_2 = \frac{f_{p2}}{f_{p1}} = \frac{4.5 \text{ GHz}}{0.33}$$

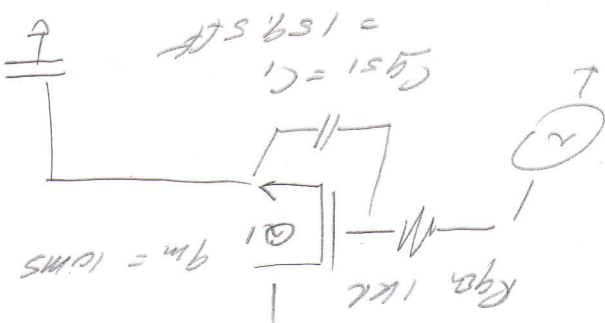real poles:  $f_{p1} = 4.5 \text{ GHz}$   
complex poles  $f_n = 0.33$



$$C_{gs1} = C_1 = 159.5 \text{ pF}$$

$$C_{gs2} = C_2 = 79.5 \text{ pF}$$


$$R_{11}^0 C_1 = 100n(1 - Av) + 1/g_{m1} = 1/g_{m1} = 100n$$

$$R_{11}^0 C_1 = 100n \cdot 159.5 \text{ pF} = 15.9 \text{ pps}$$

$$R_{22}^0 = 1/g_{m2} = 100n$$

$$R_{22}^0 C_2 = 100n \cdot 79.5 \text{ pF} = 7.9 \text{ pps}$$
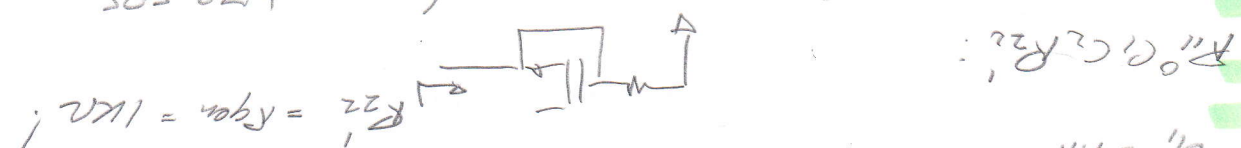
$$a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 = 23.8 \text{ pps}$$



$$R_{22}' = R_{22} = R_{21} = 100n$$

$$R_{22}' = (15.9 \text{ pps}) + (7.9 \text{ pps}) = 23.8 \text{ pps}$$

$$= 1.3 \times 10^{-21} \text{ sec}^2 = (36 \text{ pps})^2$$

$$1 + a_1 \lambda + a_2 \lambda^2 = 1 + 2 \frac{\lambda}{\omega_n} \lambda + \lambda^2$$

$$\Rightarrow \omega_n = 1 / \sqrt{a_2} = 2.8 \cdot 10^{10} \text{ rad/sec} \rightarrow f_n = \frac{\omega_n}{2\pi} = 4.5 \text{ GHz}$$

$$\Rightarrow \zeta = a_1 \omega_n = \frac{a_1}{a_2} = 0.331$$

part c. 5 points


another frequency response analysis

Using any correct method, find the transfer function  $V_{out}(s)/V_{gen}(s)$ .

The answer must be in standard form  $\frac{V_{out}(s)}{V_{gen}(s)} = \frac{1}{1 + b_1s + a_2s^2}$

Hint: Nodal analysis will be slow and painful.

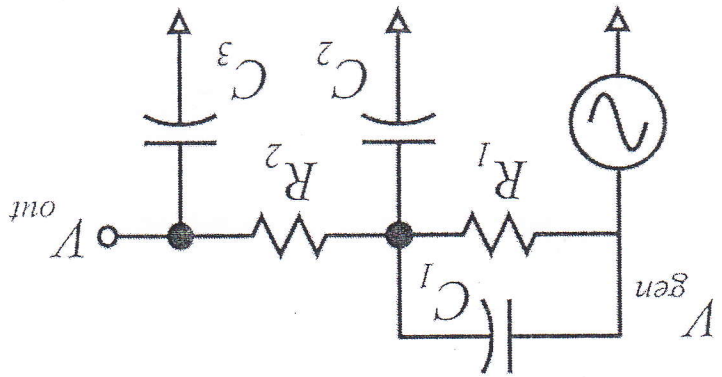$R_1 = 1k\Omega, R_2 = 1k\Omega, C_1 = 1\mu F, C_2 = 2\mu F, C_3 = 3\mu F$



$$\frac{V_{out}}{V_{gen}} \Big|_{DC} = \frac{1}{1 + a_1s + a_2s^2}$$

$a_1 = 9 \mu s, a_2 = 9.10 \cdot 10^{-12} s^2$

DC gain is 1.


$b_1$ : Note that, if the parallel combination has infinite impedance, then  $V_{out} = 0$ .





2)  $\Rightarrow H(\omega) = 0$  when  $1/j\omega C_1 \parallel R_1 = \infty$ .

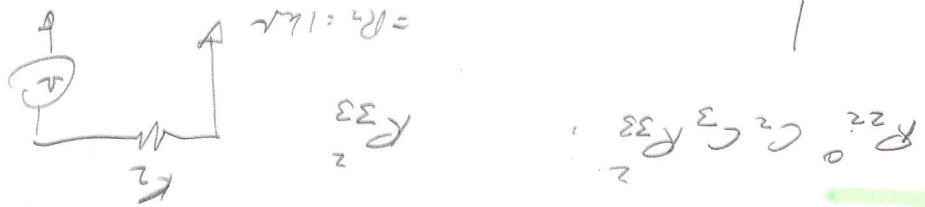3)  $\Rightarrow b_1 = CR_1 = 1k\Omega \cdot 1\mu F = 1\mu s$ .

$a_2 = \text{sum of above} = 9 \cdot 10^{-12} \text{ sec}^2$   
 $\tau = (R_{22}^0 C_2) C_3 \cdot 1k\Omega = 2\mu s \cdot 3\mu s = 6 \cdot 10^{-12} \text{ sec}^2$



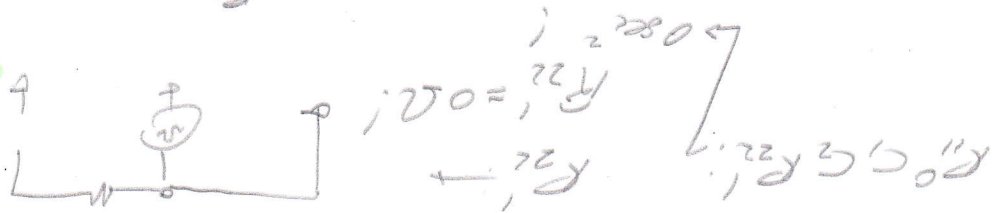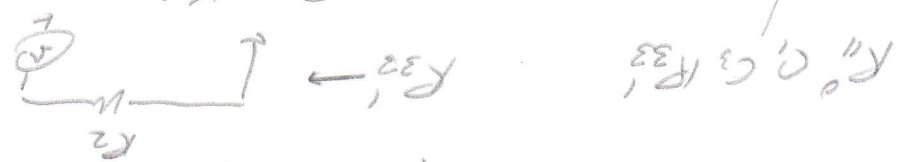$\tau = 1\mu s \cdot 3\mu s = 3 \cdot 10^{-12} \text{ sec}^2$   
 $\tau = (R_{11}^0 C_1) C_3 \cdot 1k\Omega = 1\mu s \cdot 3\mu s \cdot 1k\Omega$



$\Rightarrow a_1 = (1 + 2 + 6) \mu s = 9 \mu s$

$R_{33}^0 C_3: R_{33}^0 = R_1 + R_2 = 2k\Omega$

$R_{22}^0 C_2: R_{22}^0 = R_1 = 1k\Omega$


$R_{11}^0 C_1: R_{11}^0 = 1k\Omega \cdot 2\mu s = 2\mu s$

$R_{11}^1 C_1: R_{11}^1 = 1k\Omega \cdot 1\mu s = 1\mu s$

Handwritten green annotations on the right margin, including large brackets and the number 1/2.



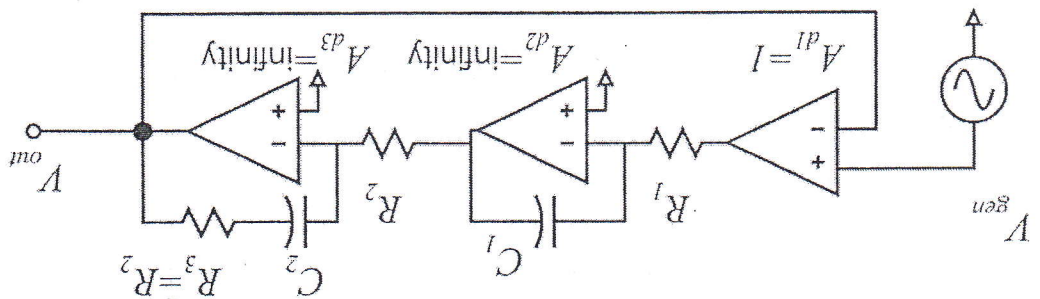**Problem 3: 20 points**  
negative feedback and stability



In the circuit above,  $A_{d2}$  and  $A_{d3}$  are ideal, infinite-gain op-amps.  $A_{d1}$  is a differential amplifier with a voltage gain of 1.  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 4 \text{ k}\Omega$ ,  $C_1 = 15.9 \text{ pF}$ ,  $C_2 = 15.9 \text{ pF}$ .

Part a. 10 points

simple nodal analysis

Find the loop transmission  $T(s)$ .

The answer must be in standard form:  $T(s) = T_{dc} \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$

or if there are  $N$  poles at DC,  $T(s) = \frac{1}{(s^2)^N} \frac{1 + a_1s + a_2s^2 + \dots}{1 + b_1s + b_2s^2 + \dots}$

$$T(s) = \frac{1 + A(63.6 \text{ nS})}{A^2(31.8 \text{ nS})^2}$$

$$= 1.01 \cdot 10^{-15} \text{ sec}^2$$

If we ignored the zeros, then  $T(s) = \frac{1}{s^2(3.18s)^2}$   
 $\rightarrow$   $\omega_{TL}$  would occur when  $f = 0.159/2.18ms \rightarrow$  small.  
 and  $\omega_{TL} = (f/5mHz)^2$  at frequencies below the zero.  
 this occurs as -40 dB/decade, and is the first asymptote on the plot

part B of problem

$$= \frac{\sqrt{(3.18ms)^2}}{1 + A(63.6ms)}$$

$$T(s) = \frac{1}{1 + A(63.6ms)} \cdot \frac{A(15.9ms)}{1} \cdot \frac{A(4)(15.9ms)}{1}$$

$$= \frac{A \cdot R_2}{(1 + A R_2)} = \frac{A(4)(15.9ms)}{1 + A(4)(15.9ms)}$$

2nd block:  $gain = \frac{R_2}{(R_2 + 1/A R_2)} = -(1 + 1/A R_2)$

1st block:  $gain = \frac{R_1}{-1/A R_1} = \frac{A(4)(15.9ms)}{-1}$



key-note: that the op-amp blocks have gains  $-z_2/z_1$


3  
3  
3

Part 10 points

feedback stability analysis

Plot the loop transmission (label slopes, label critical frequencies)  
 Determine the loop bandwidth and phase margin =  $76.0^\circ$   
 $f_{loop} = 10 \text{ Mhz}$

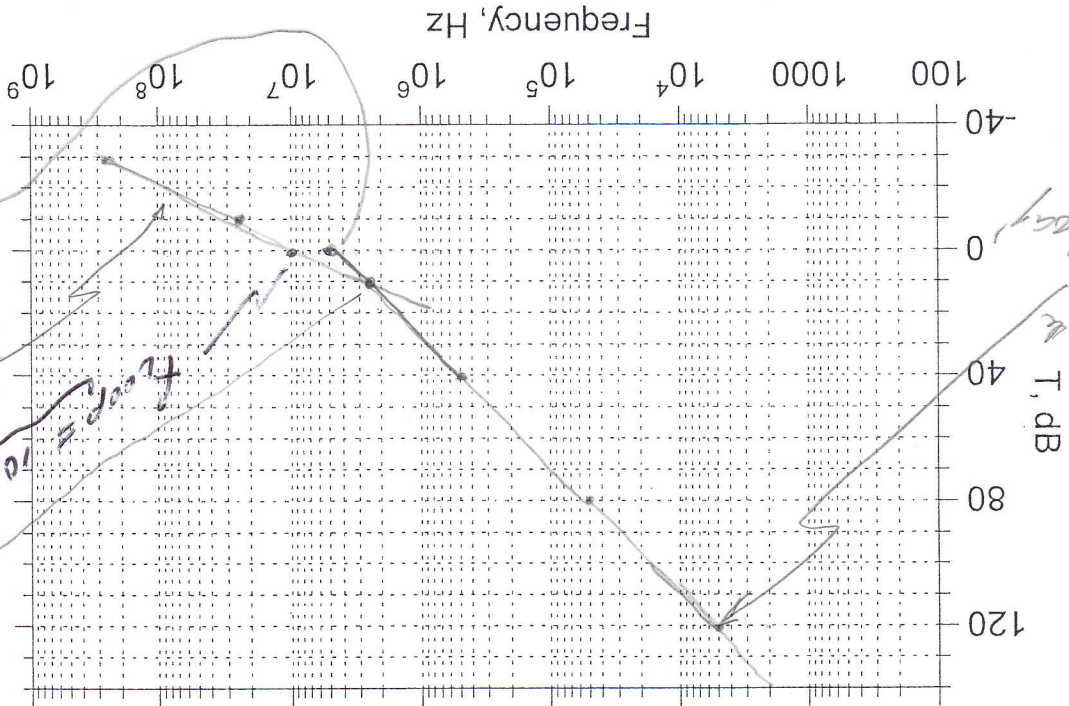Draw the loop transmission T on this plot



there is also a zero @  $f_z = 0.159 / 63.6 \text{ ns} = 2.5 \text{ Mhz}$ .  
 - so, gain decreases at -20 dB/decade above 2.5 Mhz.  
 this is our second asymptote.

By eye, this passes through 0 dB @ 10 Mhz. Lets check.

$$|T| = 1 = \left| \frac{1 + j\omega(63.6 \text{ ns})}{j\omega(63.6 \text{ ns})} \right| = \frac{\omega^2(31.8 \text{ ns})^2}{\omega^2(31.8 \text{ ns})^2}$$

Open loop

$$\Rightarrow |G| = \frac{(31.8 \text{ ns})^2}{31.8 \text{ ns} \cdot 15.9 \text{ ns}} = \frac{63.6 \text{ ns}}{31.8 \text{ ns}} = 2 \Rightarrow |G| = 0.159 = 10 \text{ Mhz}$$

16


$$\angle T @ f_{loop} = -180^\circ + \arctan\left(\frac{2.5 \text{ Mhz}}{10 \text{ Mhz}}\right) = -180^\circ + 14.0^\circ = -166^\circ$$

$$PM = 76.0^\circ$$

**Problem 4, 20 points**  
frequency and transient response

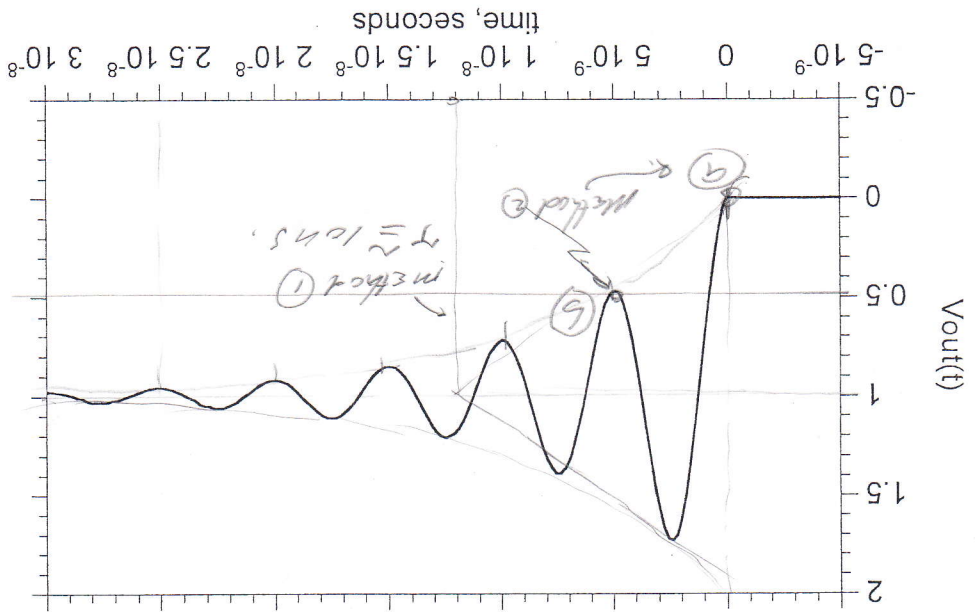part a, 10 points  
transient response

A circuit has the response to a 1V step-function input:



Determine the frequency and damping factor of the dominant poles of the transfer function.

Natural resonant frequency = \_\_\_\_\_ Hz

estimated damping factor = \_\_\_\_\_

their are 6 cycles of oscillation between  $t=0$  &  $T=2 \text{ SNS}$ .  
=> damped resonant frequency has 416ns period => 240 MHz



Since these are by-eye estimates  
 any similar method is ok - answer  
 can be rough if principal are ok

$$\Rightarrow \sum = \dots$$

$$\Rightarrow \frac{Y}{SNS} = \ln 2 \rightarrow Y = \frac{SNS}{\ln 2} = 7NS$$

$$\Rightarrow e^{-SNT/Y} = 1/2 \Rightarrow e = \frac{SNT}{Y} = 2$$

at point (b)  $\rightarrow \cos(\omega t + \theta) e^{-SNT/Y} = -0.5$

at point (a)  $\rightarrow \cos(\omega t + \theta) e^{-0.1T} = -1$

points a, b, correspond to successive minima

where  $T = 1/\omega$   
 $H(f) = 1 - e^{-\cos(\omega t + \theta)}$

Method 2) look @ points (a) (b) of wave form

for  $f_d = 2000$

$$\frac{1}{Y} = \frac{1}{\ln(SNS/Y)} = \frac{\ln(SNS(2T)/Y)}{0.5}$$




Method 1)  $T = 1/\omega = \ln(SNS/Y)$

To get  $Y$

5. or

5.

part b, 10 points  
transient response

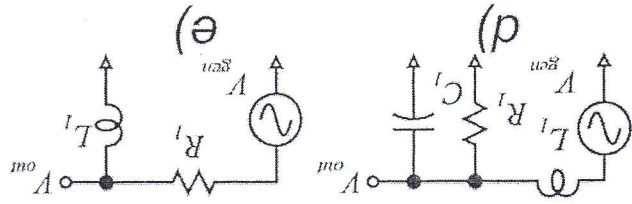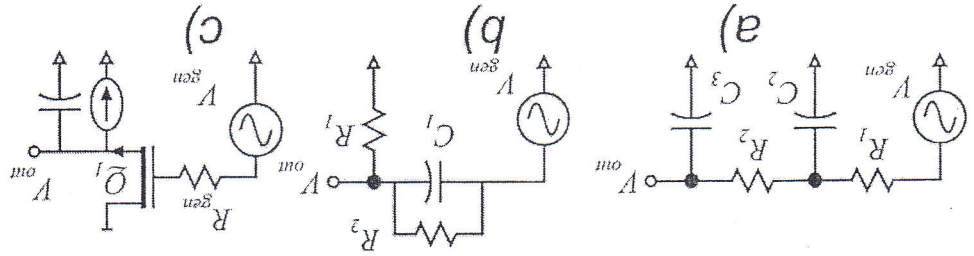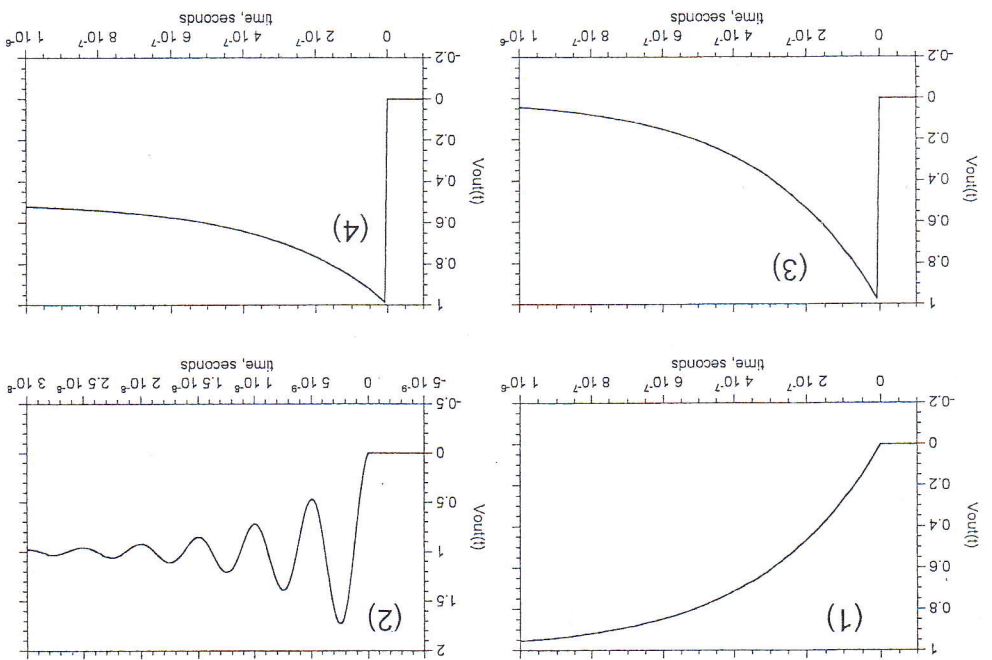

You have four unknown circuits (1-4) whose response to a 1V step-function is as above. For each, you must identify, giving your reasons clearly, which possible circuits (a-e) *might* give this observed response. (Consider the possibility that some elements in the circuits a-e might have negligible values)

response #1: circuits

a, c, d, x

why: circuit 1 has a single real pole, and is high-pass

a)  $\rightarrow$  yes, if  $c_2$  or  $c_3$  is negligible, not both.

b)  $\rightarrow$  no - zero below pole.

c) yes, if (small  $c_2$ , large  $c_3$ ).

c, d

response #2: circuits

why: this has complex poles

a) it can't have complex poles

b) cut order

d) yes RLC with  $\frac{1}{2}$  cl.

e) no  $\rightarrow$  single high-pass

response #3: circuits

b, e

why: high pass, zero @ DC, one real pole

D) C) A) no dc zero  $\rightarrow$  no

b) yes, if  $R_2 \rightarrow \infty$

e) yes

response #4: circuits

b

why: this has a real pole & a real zero

the zero has a lower frequency than the pole

a) no - no zeros

b) yes

c) no - because DC gain of  $Q_1$  is 1  $\rightarrow$  DC gain of  $a$  is  $1/2$

D) no - no poles

e) no - zero is at DC

DC gain is zero

normalize support for

- each missing answer

- each answer which shouldn't be there

