

## ECE137B Final Exam

6/11/2015, 8-11AM.

There are 4 problems on this exam and you have 3 hours  
 There are pages 1-21 in the exam: please make sure all are there.

Do not open this exam until told to do so.

Show all work.

Credit will not be given for correct answers if supporting work is not shown.

Class Crib sheets and 3 pages (front and back → 6 surfaces) of your own notes permitted.

Don't panic.


Time function	LaPlace Transform
$\delta(t)$	1
$U(t)$	$1/s$
$e^{-\alpha t} \cdot U(t)$	$\frac{1}{s+\alpha}$ or $\frac{1/\alpha}{1+s/\alpha}$
$e^{-\alpha t} \cos(\omega_d t) \cdot U(t)$	$\frac{s+\alpha}{(s+\alpha)^2 + \omega_d^2}$
$e^{-\alpha t} \sin(\omega_d t) \cdot U(t)$	$\frac{\omega_d}{(s+\alpha)^2 + \omega_d^2}$

Name: solution, EXAM 6.

Problem	points	possible	Problem	points	possible
1a		5	2c		5
1b		5	3a		10
1c		15	3b		10
1d		10	4a		10
1e		5	4b		10
2a		5			
2b		10	total		

**Problem 1, 40 points**

frequency response, negative feedback

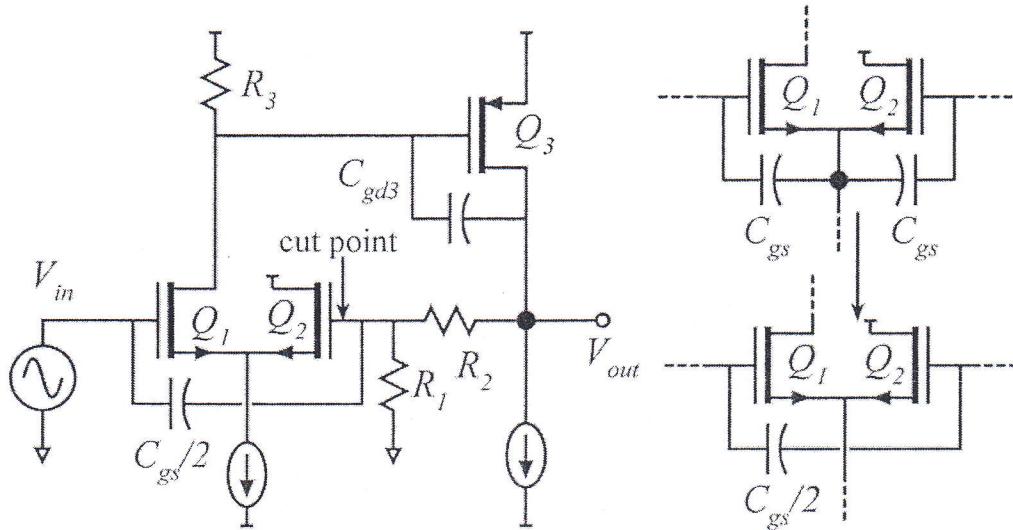

In the circuit above  $g_{m1} = g_{m2} = 20 \text{ mS}$ ,  $g_{m3} = 100 \text{ mS}$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 9 \text{ k}\Omega$ .

$R_3 = 10 \text{ k}\Omega$ ,  $R_{DS} = \infty \Omega$  for all FETs

$C_{gs1} = C_{gs2} = 31.8 \text{ fF}$ ,  $C_{gd1} = C_{gd2} = 0 \text{ fF}$ ,  $C_{gs3} = 0 \text{ fF}$ ,  $C_{gd3} = 31.8 \text{ fF}$ .

Note: simplify the problem by using the approximation shown above right.

Part a, 5 points

feedback relationships

In the relationship  $A_{CL} = A_\infty \frac{T}{1+T}$ , what is  $A_\infty$  for this circuit?

$$A_\infty = \underline{\hspace{5cm}}$$

3  
Ac corresponds to the gain when  $S_{DD} = 0$   
hence  $V^+ = V^-$ , no current in  $G_{ds}$

$$V^+ = V^- \frac{R_1}{R_1 + R_2} \cdot V_{out}$$

2.  $\Rightarrow A_\infty = \frac{V_0}{V_{in}} = \frac{R_1 + R_2}{R_1} = 10$

$$g_{m1} = g_{m7} =$$


Part b, 5 points

*feedback relationships*

Find the value of the loop transmission at DC and the closed loop gain at DC.

Hint---I recommend using the indicated cut point.
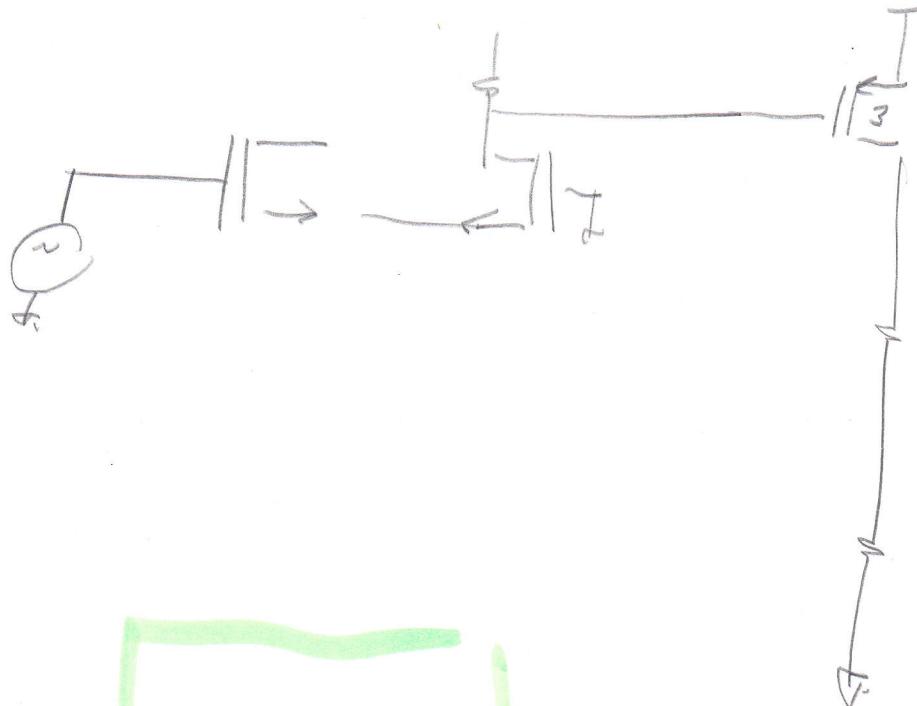
$$T = \underline{\hspace{2cm}} \quad A_{CL} = \underline{\hspace{2cm}}$$



Solve as

solution 1.

$$C_{gs/2} = 15.9 \text{ fF}$$

$$C_{gs1} = C_{gs2} = 31.8 \text{ fF}$$

$$C_{gd3} = 31.8 \text{ fF}$$

Part c, 15 points

transistor circuit frequency response.

$$R_3 = 10 \text{ k}\Omega$$


$$g_{m1,2} = (g_{m1} + g_{m2})^{-1} = 10 \text{ mS}$$

$$g_{m3} = 100 \text{ mS}$$

~~Eqn 3.27 & 3.29~~

Find the first two pole frequencies of the loop transmission  $T$ .
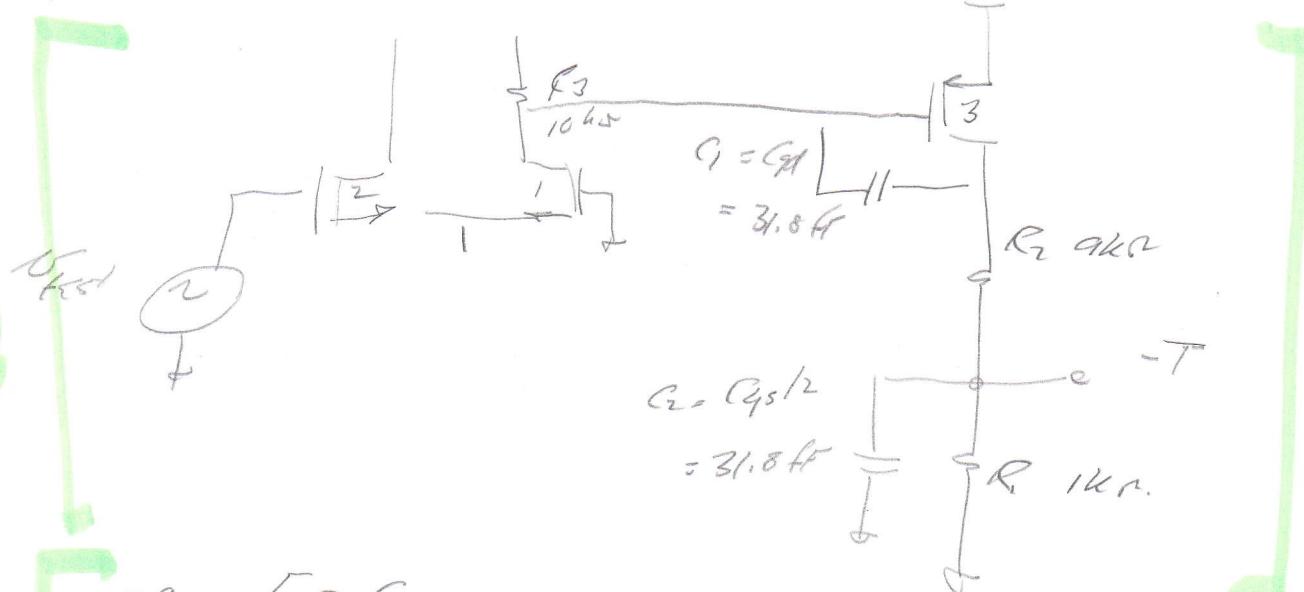
$$f_{p1} = 5 \text{ MHz} \quad f_{p2} = 5.5 \text{ GHz}$$



$$R_{in}^o = [R_3(1 + g_{m3}(R_1 + R_2)) + (R_1 + R_2)] \\ = 10 \text{ k}\Omega \cdot (101) + 10 \text{ k}\Omega \Omega = 1.02 \text{ M}\Omega \approx 1 \text{ M}\Omega.$$

$$R_{in}^o G_o = 1 \text{ M}\Omega \cdot 31.8 \text{ fF} = 31.8 \text{ nS}.$$

$$R_{out}^o = 1 \text{ k}\Omega \text{ (not } 1 \text{ k}\Omega/\text{fA/k}\Omega\text{!})$$

$$R_{out}^o G_o = 1 \text{ k}\Omega \cdot 31.8 \text{ fF} = 31.8 \text{ pS}.$$

$$G_o = 31.8 \text{ nS} + 31.8 \text{ pS} \approx 31.8 \text{ nS}.$$


$R_{11}^0 C_1 C_2 R_{22}'$

3

$$R_{22}' \rightarrow$$

$$R_{22}' \approx 1k\Omega \text{ or } 19k\Omega$$

$$= 900\Omega$$

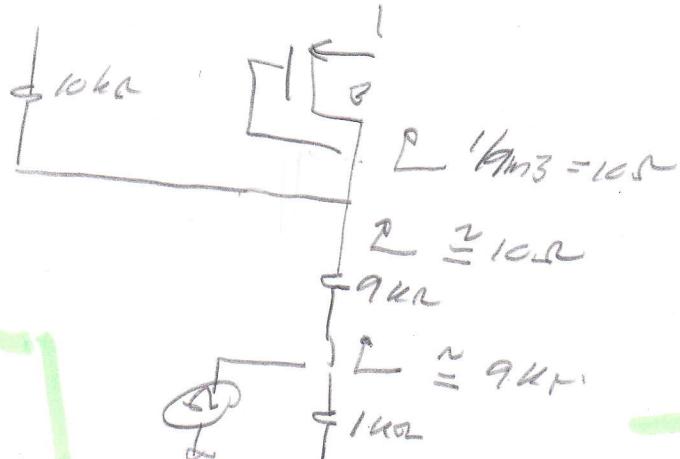

$R_{11}^0 C_1 C_2 R_{22}'$

$$= (31.8ns) 31.8 \times 10 \cdot 900\Omega$$

$$= (31.8ns)(28.6ps) = 91 \cdot 10^{-19} \text{ sec}^2 = (0.95ns)^2$$

more useful form!

SPS:  $a_1 = 31.8ns$

$$a_2/a_1 = 31.8ns \cdot 28.6ps / 31.8ns = 28.6ps.$$

$$f_{p1} = 0.159/a_1 = 5MHz.$$

$$f_{p2} = 0.159/(a_2/a_1) = 5.6GHz. \quad \text{SPS } \underline{\text{closed}}$$

(For not shown the  
 $R_{11}^0 C_1 C_2 R_{22}'$  method - see "sch A")

5 MHz

5.6 GHz

$$T_{DC} = 10^3 = 60 \text{ dB}$$

$$f_{P1} = 5 \text{ MHz}$$

$$f_{P2} = 5.6 \text{ GHz}$$

Part d, 10 points

loop bandwidth and stability.

$$T_{DC} \cdot f_{P1} = 56 \text{ dB} \approx f_{loop}$$

$f_{P2}$  barely above this.


Plot the loop transmission (labels slopes, label critical frequencies)

Determine the loop bandwidth and phase margin

$$f_{loop} = 5 \text{ GHz}^*$$

$$T_{DC} = 60 \text{ dB}$$

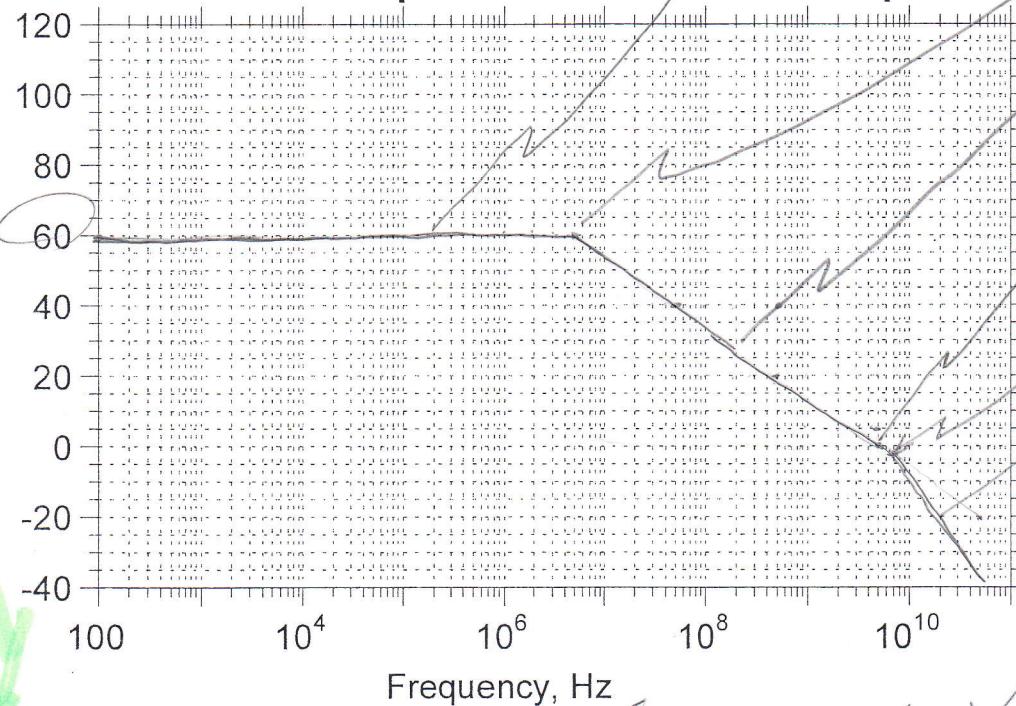Draw the loop transmission  $T$  on this plot



Note - we determined  $f_{loop}$  using straight-line asymptotes.  
 Check answer, also full point (better)  
 could solve for  $|T| = 1$  @  $f_{loop} \rightarrow f_{loop}$  would  
 then be slightly below 56 MHz (3 or 4 GHz...?)

angle of  $T$  @  $f_{loop}$

$$\angle T = -90^\circ - \arctan(56 \text{ MHz} / 5.6 \text{ GHz})$$

$$= -90^\circ - 42^\circ$$

$$\text{Phase margin} = 90^\circ - 42^\circ = 58^\circ$$

$$f_{loop} = 50 \text{ Hz}, \text{ ph} = 58^\circ$$

$$A_{cl} = A_{\infty} \frac{T}{1+T} = \begin{cases} A_{\infty} \text{ for } T \gg 1 \\ A_{\infty} e^{j\theta} / (1 + e^{j\theta}) \text{ for } T = e^{j\theta} \end{cases}$$

$$A_{\infty} T \text{ for } T \ll 1$$

Part e, 5 points  
closed-loop bandwidth


Plot the closed-loop gain vs. frequency, estimating the gain peaking at  $f_{loop}$

Estimate the amplifier's closed-loop bandwidth

closed-loop bandwidth = \_\_\_\_\_

$A_{cl}$  has a pole @  $\approx f_{pe}$ !

Draw the closed-loop gain on this plot

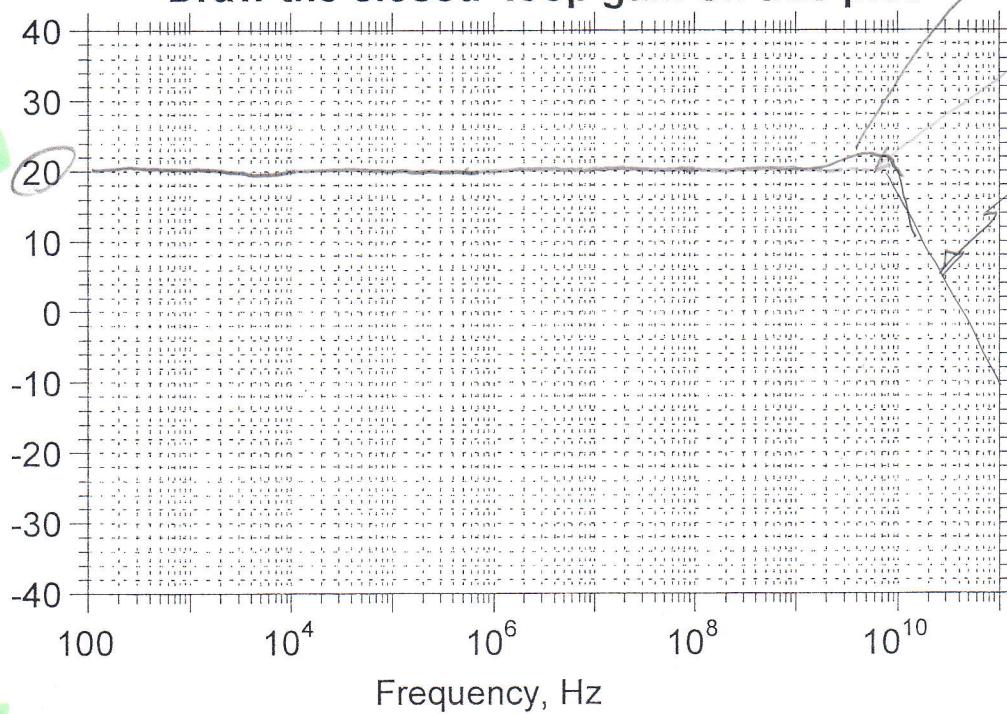

at  $f_{loop}$ ,  $\angle T = -132^\circ = -2.30 \text{ radians} = \theta$

$$\left| \frac{1}{1+T} \right| = \left| \frac{e^{j\theta}}{1+e^{j\theta}} \right| = \frac{1}{\sqrt{(1+\cos\theta)^2 + (\sin\theta)^2}} = \frac{1}{\sqrt{1+2\cos\theta}}$$

$$\approx 1.23 \rightarrow 20 \log_{10}(1.23) = 1.8 \text{ dB}$$

$\Rightarrow 1.8 \text{ dB gain peaking } @ f_{loop}$


given that I used asymptotes to find freq,  
my method is approx. meth.

$\Rightarrow$  reasonable answers for [gain peaking] are ok

8

Problem 2, 20 points

Circuit frequency response by MOTC.

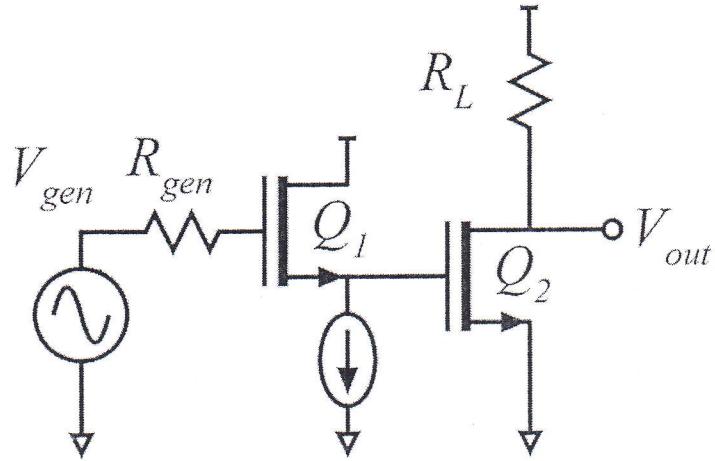

In the circuit above  $g_{m1} = 10 \text{ mS}$ ,  $g_{m2} = 50 \text{ mS}$ .

$R_{gen} = 1000 \Omega$ ,  $C_{gs1} = 15.9 \text{ fF}$ ,  $C_{gs2} = 79.5 \text{ fF}$ ,  $C_{gd1} = C_{gd2} = 0 \text{ fF}$ .


$R_{DS} = \infty \Omega$  for both FETs

$R_L = 1 \text{ k}\Omega$ .

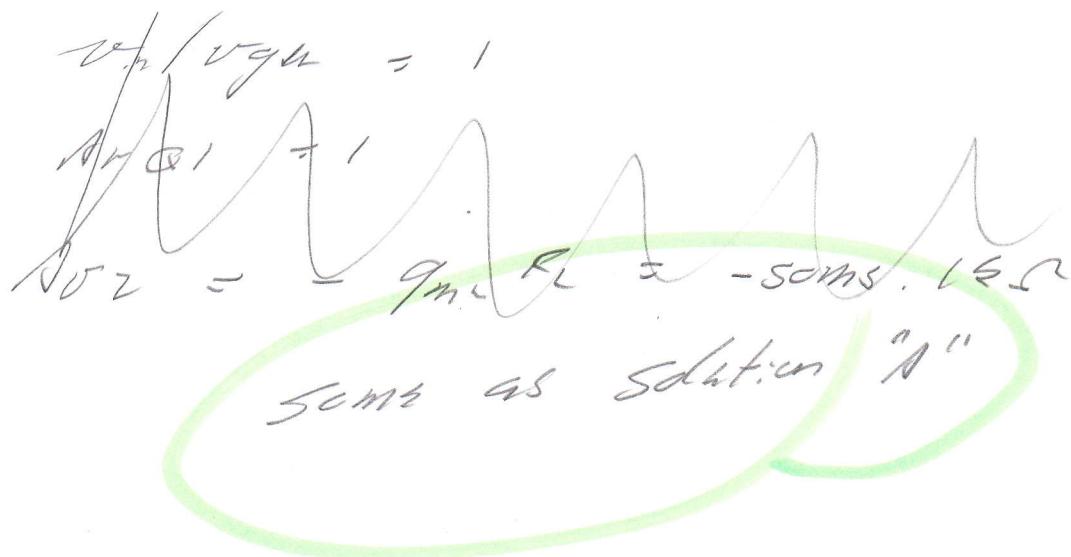part a, 5 points

midband analysis

find the gain  $V_{out}/V_{gen}$  at low frequencies.  $V_{out}/V_{gen} = \underline{\hspace{10mm}}$



part b, 10 points

*frequency reponse analysis*

Find  $a_1$ ,  $a_2$ . If the poles are real, find  $f_{p1}$  and  $f_{p2}$ ; if they are complex, find  $f_n$  and  $\zeta$

$$a_1 = \underline{\hspace{2cm}} \quad a_2 = \underline{\hspace{2cm}}$$

$$\text{real poles: } f_{p1} = \underline{\hspace{2cm}} \quad f_{p2} = \underline{\hspace{2cm}}$$

$$\text{complex poles } f_n = \underline{\hspace{2cm}} \quad \zeta = \underline{\hspace{2cm}}$$

Same as solution A.

part c, 5 points


another frequency response analysis

Using any correct method, find the transfer function  $V_{out}(s)/V_{gen}(s)$ .

$$\text{The answer must be in standard form } \frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}} \Big|_{DC} \frac{1 + b_1 s}{1 + a_1 s + a_2 s^2}$$

$$R_1 = 1k\Omega, R_2 = 1k\Omega, C_1 = 1nF, C_2 = 2nF, C_3 = 3nF$$

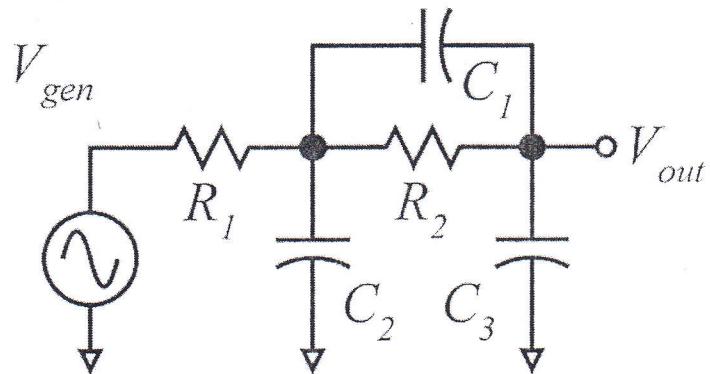Hint: Nodal analysis will be slow and painful.



$$\frac{V_{out}}{V_{gen}} \Big|_{DC} = \frac{1}{1 + a_1 s + a_2 s^2}, \quad a_1 = \frac{1}{2 \mu s}, \quad a_2 = \frac{1.1 \cdot 10^{-11} \text{ See}^2}{1 \mu s}$$

$$b_1 = \frac{1}{2 \mu s}$$

DC gain is 1

S<sub>1</sub>: (1) note that  $\frac{1}{j\omega C_1} \parallel R_2$  is infinite  
that v<sub>ad</sub> is zero.

(2) ~~H(s)~~  $\Rightarrow H(0) = \text{zero when } \frac{1}{j\omega C_1} \parallel R_2 = \infty$

$$(3) \Rightarrow S_1 = C_1 R_2 \\ = 1 \text{ nF} \cdot 1 \text{ k}\Omega = 1 \mu\text{s}$$

$\boxed{R_{11}^0 C_1}$ :  $R_{11}^0 = R_2 = 1\text{ k}\Omega$   $R_{11}^0 C_1 = 1\text{ NF}, 1\text{ k}\Omega$   
 $= 1\mu\text{s}$


$\boxed{R_{22}^0 C_2}$ :  $R_{22}^0 = R_1 = 1\text{ k}\Omega$   $R_{22}^0 C_2 = 1\text{ k}\Omega \cdot 2\text{nF}$   
 $= 2\mu\text{s}$ .

$\boxed{R_{33}^0 C_3}$ :  $R_{33}^0 = R_1 + R_2 = 2\text{k}\Omega$   $R_{33}^0 C_3 = 2\text{k}\Omega \cdot 3\text{nF}$   
 $= 6\mu\text{s}$ .

$a_1 = \text{sum of above} = 9\mu\text{s}$


$a_{eff}$

$R_{11}^0 C_1 C_2 R_{22}'$

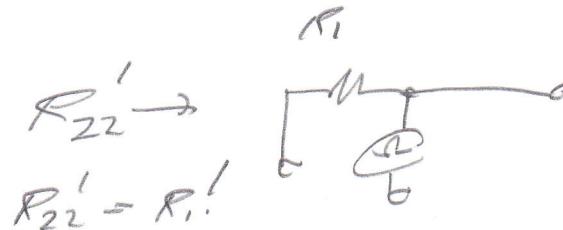


$\rightarrow R_{11}^0 C_1 C_2 R_{22}' = 1\mu\text{s} \cdot (2\text{nF}) 1\text{k}\Omega = 1\mu\text{s} \cdot 2\mu\text{s}$   
 $= 2 \cdot 10^{-12} \text{ sec}^2$

$R_{11}^0 C_1 C_3 R_{33}'$

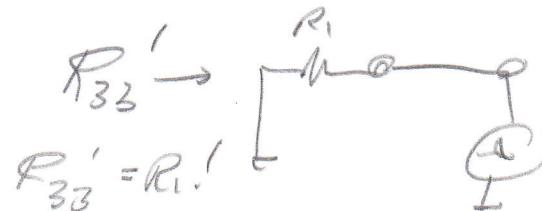

$R_{11}^0 C_1 C_3 R_{33}' = 1\mu\text{s} \cdot 3\text{nF} \cdot 1\text{k}\Omega = 1\mu\text{s} \cdot 3\mu\text{s}$   
 $= 3 \cdot 10^{-12} \text{ sec}^2$

$R_{22}^0 C_2 C_3 R_{33}^2$

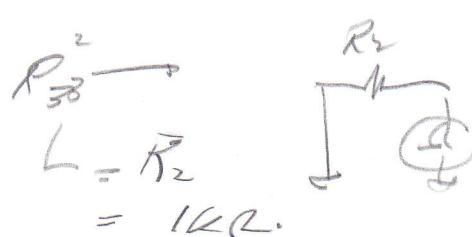


$= 1\text{k}\Omega \cdot$

$R_{22}^0 C_2 C_3 R_{33}^2 = (2\mu\text{s}) 3\text{nF} \cdot 1\text{k}\Omega = 2\mu\text{s} \cdot 3\mu\text{s} = 6 \cdot 10^{-12} \text{ sec}^2$

$a_2 = \text{sum of above} = 11 \cdot 10^{-12} \text{ sec}^2 = 1.1 \cdot 10^{-11} \text{ sec}^2$

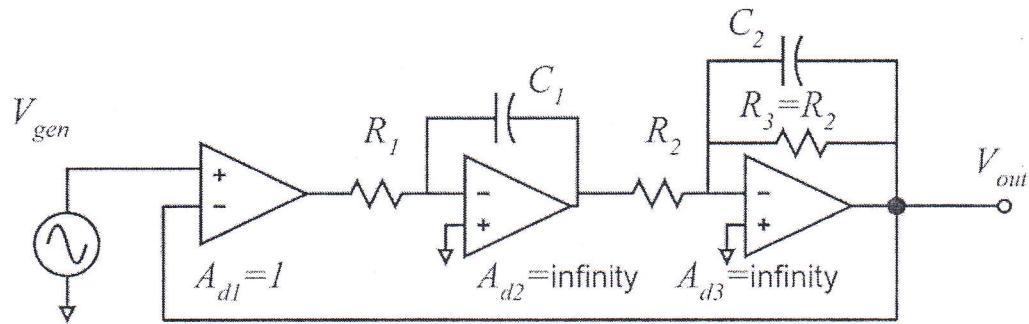**Problem 3: 20 points**  
*negative feedback and stability*



In the circuit above,  $A_{d2}$  and  $A_{d3}$  are ideal, infinite-gain op-amps.

$A_{d1}$  is a differential amplifier with a voltage gain of 1.

$R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 0.5 \text{ k}\Omega$ ,  $C_1 = 15.9 \text{ pF}$ ,  $C_2 = 15.9 \text{ pF}$ .

Part a, 10 points  
*simple nodal analysis*

find the loop transmission  $T(s)$ .

The answer must be in standard form:  $T(s) = T_{DC} \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$ ,

or if there are N poles at DC,  $T(s) = \frac{1}{(s\tau)^N} \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$

$$T(s) = \frac{1}{s(15.9 \mu s)(1 + 10 \cdot 7.95 \mu s)}$$

Key - note that op-amp blocks have gains  
 $g_{A,21} = -Z_2/Z_1 \rightarrow -[Z_1] \rightarrow [Z_2]$

First block -  $g_{A,11} = 1$

3 [ 2nd block:  $g_{A,1} = -1/\Delta G = -\frac{1}{R_1} = \frac{-1}{\Delta C_1 R_1} = \frac{-1}{\Delta(15.9ns)}$  ]

3 [ 3rd block:  $g_{A,2} = -\frac{(-\Delta C_2)(R_2)}{R_2} = \frac{\Delta C_2 R_2}{1 + \Delta C_2 R_2}$   
 $= \frac{-1}{1 + \Delta(7.95ns)}$  ]

4 [  $T(s) = \frac{1}{\Delta(15.9ns)} \frac{1}{1 + \Delta(7.95ns)}$  ]

goes to unity  
at  $10MHz$  pole @  $20MHz$

NOTE: I have used straight line approximations to find  $f_{loop}$ . If the student has solved for  $f_{loop}$  exactly, that of course is also OK!

Part a, 10 points


feedback stability analysis

Plot the loop transmission (labels slopes, label critical frequencies)

Determine the loop bandwidth and phase margin

$$f_{loop} = \underline{10 \text{ mHz}}, \text{ phase margin} = \underline{33.4^\circ}$$

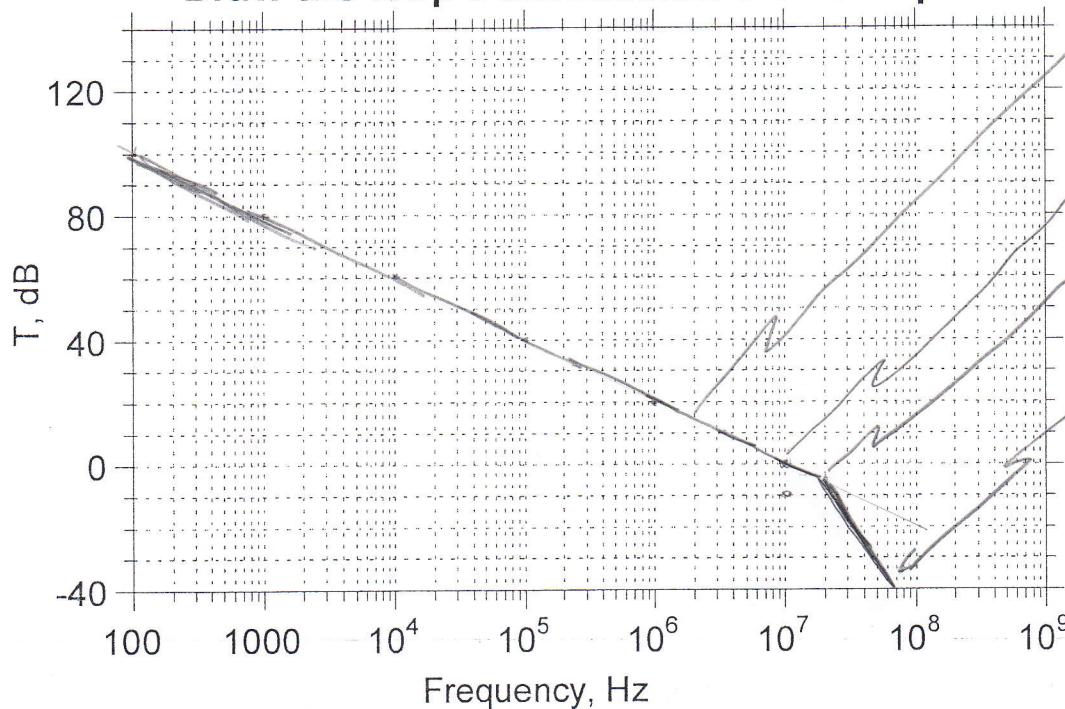Draw the loop transmission  $T$  on this plot




$$\begin{aligned} \text{LT @ } f_{loop} &= -90^\circ - \arctan\left(\frac{10 \text{ mHz}}{20 \text{ mHz}}\right) \\ &= -90^\circ - 26.6^\circ \\ \text{phase margin} &= 90 - 26.6 = \underline{\underline{33.4^\circ}} \end{aligned}$$

**Problem 4, 20 points**  
*frequency and transient response*

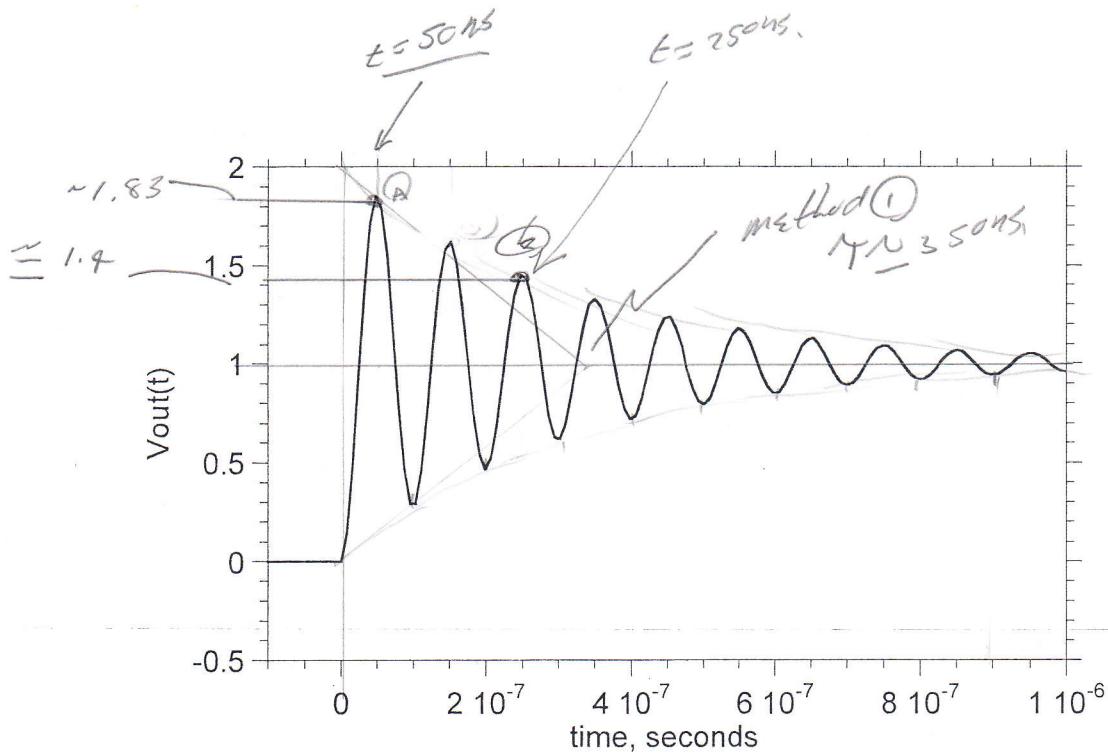part a, 10 points  
*transient response*

A circuit has the response to a 1V step-function input:



Determine the frequency and damping factor of the dominant poles of the transfer function.

Natural resonant frequency = \_\_\_\_\_ Hz  
 estimated damping factor = \_\_\_\_\_

**S** There are (9) cycles of ringing between  $t=0$  &  $t=0 \mu s$   
 $\Rightarrow$  damped resonant frequency has  $0 \mu s = 10 \frac{1}{10.3} 5 \text{ } 100 \text{ ns}$  period.  
 $\Rightarrow 10 \text{ MHz} = f_d$  (not exactly  $f_n$ ).

To get  $\gamma$

Method ①.

5 [  $\gamma = 1/\tau_{\text{wh}} \approx 350\text{ns by eye} (!)$

$$\gamma = \frac{1}{350\text{ns wh}} = \frac{\cancel{0.046}}{350\text{ns (27th)}} = 0.046$$

Method ② (or your similar method)

look at points a, b of waveform

$$A(t) = 1 - e^{-t/\tau} \cos(\omega t + \theta) \quad \text{where } \tau = 1/\gamma_{\text{wh}}$$

points a, b correspond to maxima  
of  $\cos(\omega t + \theta)$

point a:  $\underbrace{\cos(\omega t_1 + \theta)}_{= 0.83} e^{-t_1/\tau} = 0.83$  where  $t_1 = 50\text{ns}$

point b  $\underbrace{\cos(\omega t_2 + \theta)}_{= 0.4} e^{-t_2/\tau} = 0.4$  where  $t_2 = 250\text{ns}$

$$\frac{e^{-t_2/\tau}}{e^{-t_1/\tau}} = e^{-\frac{(t_2-t_1)/\tau}{\tau}} = 0.83/0.4$$

$$\Rightarrow \frac{t_2-t_1}{\tau} = \ln\left(\frac{0.83}{0.4}\right)$$

$$\Rightarrow \tau = \frac{t_2-t_1}{\ln(0.83/0.4)} = 270\text{ns}$$










$$\Rightarrow \gamma = \frac{1}{\tau} = 0.0036$$

Since these are by-eye

estimates any similar method is ok

answer can be rough if principles are ok

part b, 10 points  
*transient response*

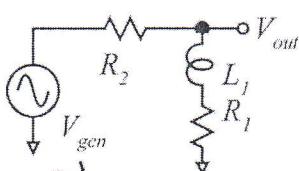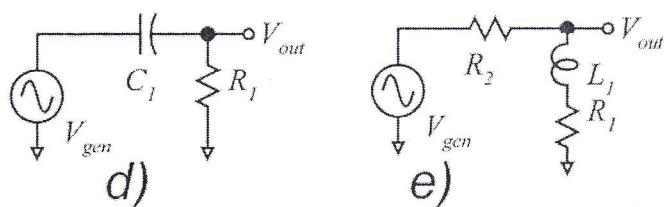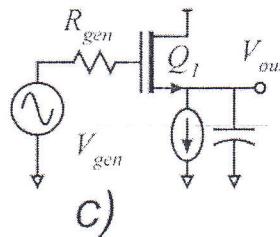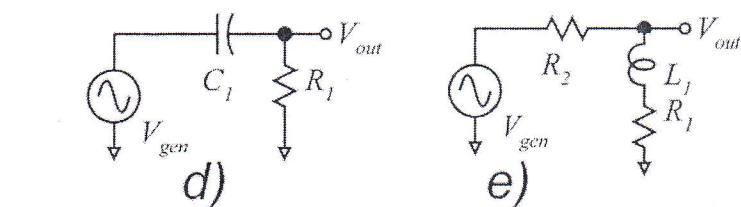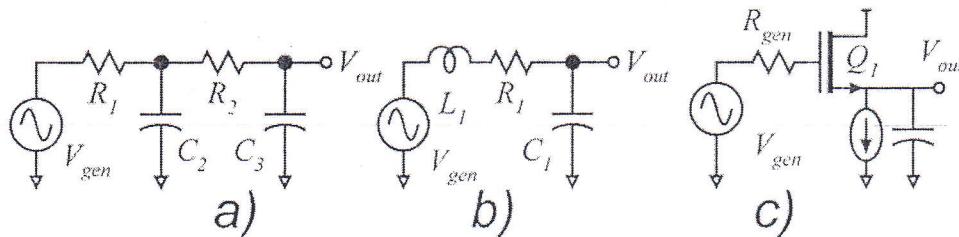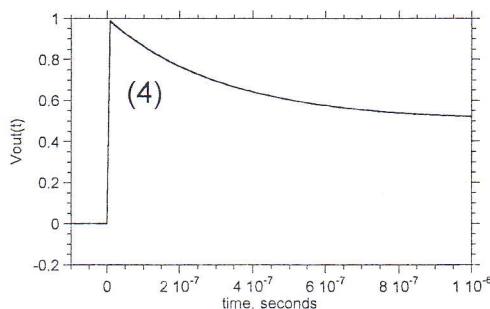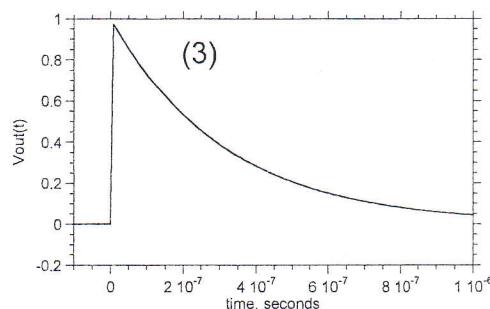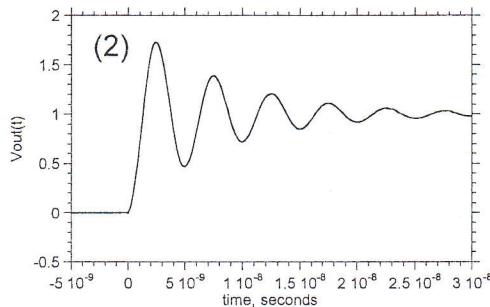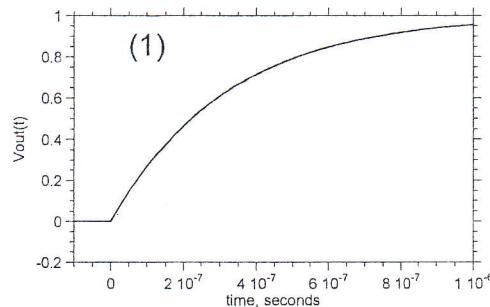

You have four unknown circuits (1-4) whose response to a 1V step-function is as above.  
 For each, you must identify, giving your reasons clearly, which possible circuits (a-e) *might* give this observed response. (Consider the possibility that some elements in the circuits a-e might have negligible values)

[ pencilize 3/4 point for  
- each missing answer  
- each answer which should not be there.]

a, b, c, e.

response #1: circuits \_\_\_\_\_

why: circuit 1 has a single real pole.

a) YES, if  $C_2$  or  $C_3$  is negligible.

b) Yes  $\rightarrow$  if  $L \rightarrow \infty$

c) Yes, if  $C_3$  negligible

d) No - zero @ dc.

e) YES, if  $R_s \ll R_L$ .

response #2: circuits B, C

why: circuit 2 has complex poles.

a)  $\rightarrow$  No - can't have complex...

b) YES  $\rightarrow$   $R_C \rightarrow$  can have  $\zeta < 1$

c) YES - if  $C_2, C_3$  both large

d) No - zero @ DC

e) No - Real pole

D, E

response #3: circuits \_\_\_\_\_

why: circuit 3 has zero @ DC real pole.

a) No  $\rightarrow$  no dc zero

b) No  $\rightarrow$  no dc zero

c) No - dc gain = 1

d) YES!  $\rightarrow$  zero @ dc

e) YES  $\rightarrow$  If  $R_1 \gg R$

response #4: circuits E

why: circuit 4 has real pole at zero, zero lower than  $\zeta \omega_0$ .

a) No - no zeros

b) No - no zeros

c) No - DC gain = 1

d) No - DC gain = 0

e) YES