

**Mid-Term Exam, ECE-137B**  
 Tuesday, May 3, 2016

**Closed-Book Exam**

There are 2 problems on this exam , and you have 75 minutes.

**1) show all work. Full credit will not be given for correct answers if supporting work is not shown.**

2) please write answers in provided blanks

3) Don't Panic !

4) 137a, 137b crib sheets, and 2 pages personal sheets permitted.

Use any, all reasonable approximations. After stating them. 5% accuracy is fine if the method is correct.

**Do not turn over cover page until requested to do so.**


Name: \_\_\_\_\_

Time function	LaPlace Transform
$\delta(t)$	1
$U(t)$	$1/s$
$e^{-\alpha t}U(t)$	$\frac{1}{s + \alpha}$
$e^{-\alpha t} \cos(\omega_d t)U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha t} \sin(\omega_d t)U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Problem	Points Received	Points Possible
1a		2
1b		5
1c		4
1d		15
1e		7
1f		7
1g		5
2a		4
2b		6
2c		10
2d		5
3a		5
3b		5
3c		10
3d		10
3e		5
total		100

check here - which exam is this?

**Problem 1, 45 points**

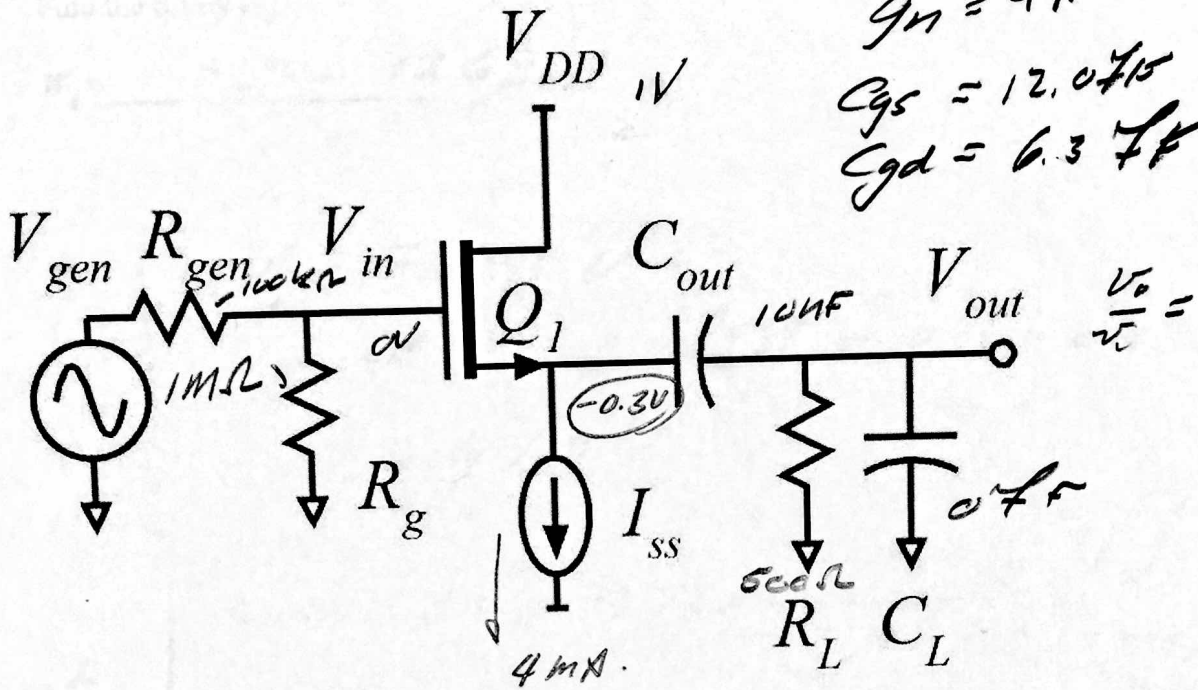

$g_m = 47.1 \text{ mS} = \frac{1}{21.2 \Omega}$   
 $C_{gs} = 12.0 \text{ fF}$   
 $C_{gd} = 6.3 \text{ fF}$

Q1 has 0.9 nm oxide thickness,  $\epsilon_r = 3.8$ , 12 nm gate length, and a 0.2 V threshold. Mobility is  $400 \text{ cm}^2/(\text{V}\cdot\text{s})$ , saturation drift velocity is  $1\text{E}7 \text{ cm/s}$ ,  $\lambda = 0 \text{ Volts}^{-1}$ ,  $C_{gs} = \epsilon_r \epsilon_{ox} L_g W_g / T_{ox} + (0.5 \text{ fF} / \mu\text{m}) \cdot W_g$  and  $C_{gd} = (0.5 \text{ fF} / \mu\text{m}) \cdot W_g$ .

calculated for you:

$\epsilon_r \epsilon_{ox} / T_{ox} = 3.74 \cdot 10^{-2} \text{ F/m}^2$ ,  $(\mu c_{ox} W_g / 2L_g) = (6.23 \cdot 10^{-2} \text{ A/V}^2) \cdot (W_g / 1 \mu\text{m})$   
 $(c_{ox} v_{sat} W_g) = (3.74 \cdot 10^{-3} \text{ A/V}^1) \cdot (W_g / 1 \mu\text{m})$ ,  $(v_{sat} L_g / \mu) = 30 \text{ mV}$ .

$V_{DD} = +1\text{V}$ ,  $I_{SS} = 4 \text{ mA}$ .  
 \*\*You will pick the FET width  $W_g$  such that  $V_{gs} = 0.3 \text{ Volts}$ \*\*\*  
 $R_{gen} = 100 \text{ kOhm}$ ,  $R_g = 1 \text{ MOhm}$ ,  $R_L = 500 \text{ Ohms}$ ,  $C_L = 0 \text{ fF}$ .  
 $C_{out} = 10 \text{ nF}$ .

$\frac{V_o}{V_i} = 0.95932$

$W_g = 12.6 \mu\text{m}$

$f_{p1} = 257 \text{ kHz}$   
 $f_{p2} = 699 \text{ kHz}$

$f_3 = 1.4 \text{ THz}$

$f_{low} = 30.4 \text{ kHz}$

(9)

Part a, 2 points

Find the following:

$$W_g = \underline{\cancel{1.57 \mu m}} \cdot 12.6 \mu m.$$

1 pt

$$\left[ \begin{array}{l} V_{gs} = 0.3 \text{ V} \\ \text{let } V_{el} + \frac{V_{ed} L_g}{2 \mu} = 0.2 \text{ V} + 0.015 \text{ V} = \overset{0.215 \text{ V}}{\cancel{2.015 \text{ V}}} \\ \Rightarrow \text{Velocity limited.} \end{array} \right.$$

1 pt

$$\left[ \begin{array}{l} 4 \text{ mA} = I_d = 3.74 \frac{\text{mA}}{\text{V} \mu\text{m}} \cdot W_g \cdot \underbrace{(V_{gs} - 0.215 \text{ V})}_{0.085 \text{ V}} \\ W_g = \frac{4 \text{ mA}}{3.74 \frac{\text{mA}}{\text{V} \mu\text{m}} \cdot 85 \text{ mV}} = 12.58 \mu\text{m} \end{array} \right.$$

Part b, 5 points

small-signal parameters

Find the following

$$C_{gs} = \frac{11.95 \text{ fF}}{47.1 \text{ ms}} \quad C_{gd} = \frac{6.3 \text{ fF}}{410 \text{ GHz}}$$

2pt

$$C_{gs} = 3.74 \cdot 10^{-2} \frac{\text{f}}{\text{m}^2} \cdot 12.6 \mu\text{m} \cdot 12 \mu\text{m} + 0.5 \text{ fF}/\mu\text{m} \cdot 12.6 \mu\text{m} = 5.65 \text{ fF} + 6.3 \text{ fF} = 11.95 \text{ fF}$$

1pt

$$C_{gd} = 0.5 \text{ fF}/\mu\text{m} \cdot 12.6 \mu\text{m} = 6.3 \text{ fF}$$

1pt

$$g_m = 3.74 \frac{\text{mA}}{\text{V} \cdot \mu\text{m}} \cdot 12.6 \mu\text{m} = 47.1 \text{ mA/V}$$

1pt

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} = 410 \text{ GHz}$$

Part c: 4 points

Mid Band Analysis:

Find the following:

$$R_{in, \text{Amplifier}} = \underline{1 \text{ M}\Omega} \quad R_{L, \text{eq}} = \underline{500 \Omega}$$
$$V_{out} / V_{in} = \underline{0.95932} \quad V_{in} / V_{gen} = \underline{0.91}$$

1 pt.  $\left[ R_{in, \text{Amplifier}} = R_g = 1 \text{ M}\Omega \right]$

1 pt  $\left[ R_{L, \text{eq}} = R_L \parallel R_{DS} \# = R_L \parallel \infty = 500 \Omega \right]$

1 pt  $\left[ \frac{V_o}{V_{in}} = \frac{R_{L, \text{eq}}}{R_{L, \text{eq}} + 1/g_m} = \frac{500 \Omega}{500 \Omega + 21.2 \Omega} = 0.95932 \right]$

1 pt  $\left[ \frac{V_{in}}{V_{gen}} = \frac{1 \text{ M}\Omega}{1 \text{ M}\Omega + 100 \text{ k}\Omega} = 0.90909 \right]$

$\left[ \frac{V_o}{V_{gen}} = 0.872 \right]$  not requested.

9

Part d: 15 points

High-Frequency Analysis: Poles

Find the frequencies, in Hz, of the two poles limiting the high-frequency response of the amplifier. You can either use MOTC, or use the results derived in class (and written down on the class amplifier crib sheet). Hint: assume  $C_{out}$  is a short-circuit for this calculation

If the poles are real, give the 1 or 2 pole frequencies in Hz:

$f_{p1, HF} = \underline{257 \text{ MHz}}$      $f_{p2, HF} = \underline{699 \text{ GHz}}$

If there are 2 poles, and they are complex, give  $f_n = \omega_n / 2\pi$  and the damping factor  $\zeta$ :

$f_n = \omega_n / 2\pi = \underline{\hspace{2cm}}$ ,  $\zeta = \underline{\hspace{2cm}}$

mo Notation: Call  $C_1 = C_{gs}$ ,  $C_2 = C_{gd}$ .

$a_1 = R_{11}^0 C_1 + R_{22}^0 C_2$

1  $[R_{22}^0 = 100 \text{ k}\Omega \parallel 1 \text{ M}\Omega = 90.91 \text{ k}\Omega$


1  $[R_{22}^0 C_2 = 90.91 \text{ k}\Omega \cdot 6.3 \text{ fF} = 573 \text{ pS}$

2  $[R_{11}^0 = 90.91 \text{ k}\Omega [1 - A_v] + \frac{1}{g_m} \parallel R_{sig} = 3.7 \text{ k}\Omega$   
 $= 3.72 \text{ k}\Omega$   $+ \underbrace{21.2 \text{ nH} / 500 \text{ pS}}_{20.3 \text{ n}}$

1  $[R_{11}^0 C_1 = 3.72 \text{ k}\Omega \cdot 12.0 \text{ fF} = 44.6 \text{ pS}$

1  $[a_1 = 618 \text{ pS}$

1  $[a_2 = R_{11}^0 C_1 C_2 R_{22}^0$

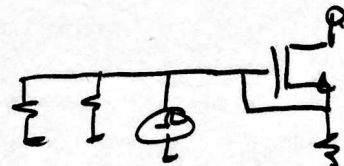

2  $[R_{22}^0 = R_{gs} \parallel R_{g'} \parallel R_L$   
 $= 90.9 \text{ k}\Omega \parallel 500 \Omega = 297 \Omega \approx 500 \Omega$

2  $[a_2 = (R_{11}^0 C_1) C_2 R_{22}^0 = 44.6 \text{ pS} \cdot 6.3 \text{ fF} \cdot 500 \Omega$   
 $= 1.4 \cdot 10^{-22} \text{ sec}^2 = (11.9 \text{ pS})^2$

2  $[T_{19} \text{ sFA } a_2 / a_1 = (11.9 \text{ pS})^2 / 618 \text{ pS} = 0.23 \text{ pS}$  well separate.

2  $[f_{p1} = \frac{0.159}{a_1} = \frac{257 \text{ MHz}}{6}$

$f_{p2} = \frac{0.159}{a_2 / a_1} = 699 \text{ GHz}$   
9

Part e: 7 points

High-Frequency Analysis: Zeros

Find the frequencies of any zeros (there may be zero, one or two present) in the transfer function. You can either use nodal analysis, or use the results derived in class (and written down on the class amplifier crib sheet).

$$f_{z1} = \underline{1.2 \text{ THz}}, f_{z2} = \underline{\quad \quad \quad}, \dots$$

*only one zero.*


$$f_{z1} = \frac{g_m}{2\pi C_{gd}} = 1.2 \text{ THz}$$

Part f: 7 points

Low-Frequency Analysis:

Find the frequency in Hz, of the pole, due to  $C_{out}$ , limiting the low-frequency response of the amplifier. Use any method of analysis you choose.
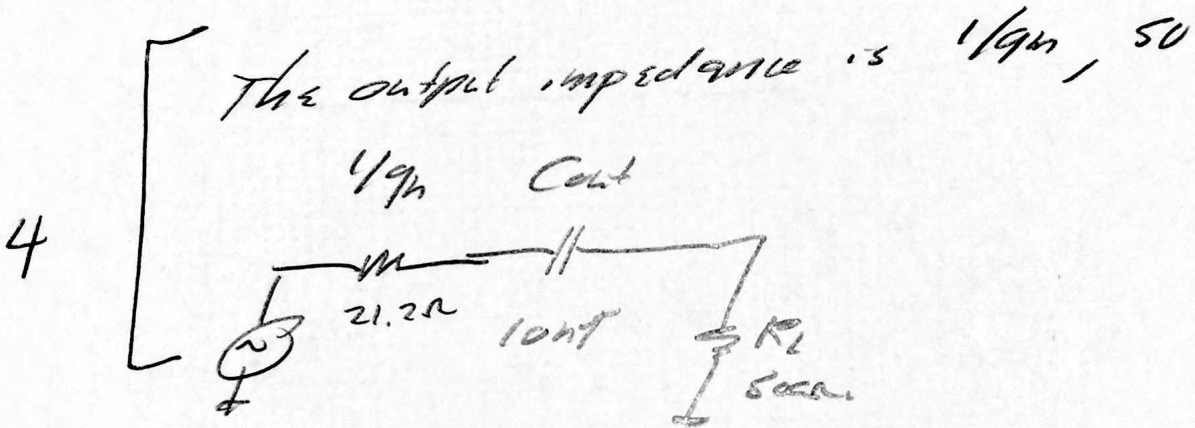
$$f_{p1,LF} = \underline{30.4 \text{ kHz}}$$



3

$$f_{low} = \frac{0.159}{10nF (521.2\Omega)} = 30.4 \text{ kHz}$$


9

9  
a



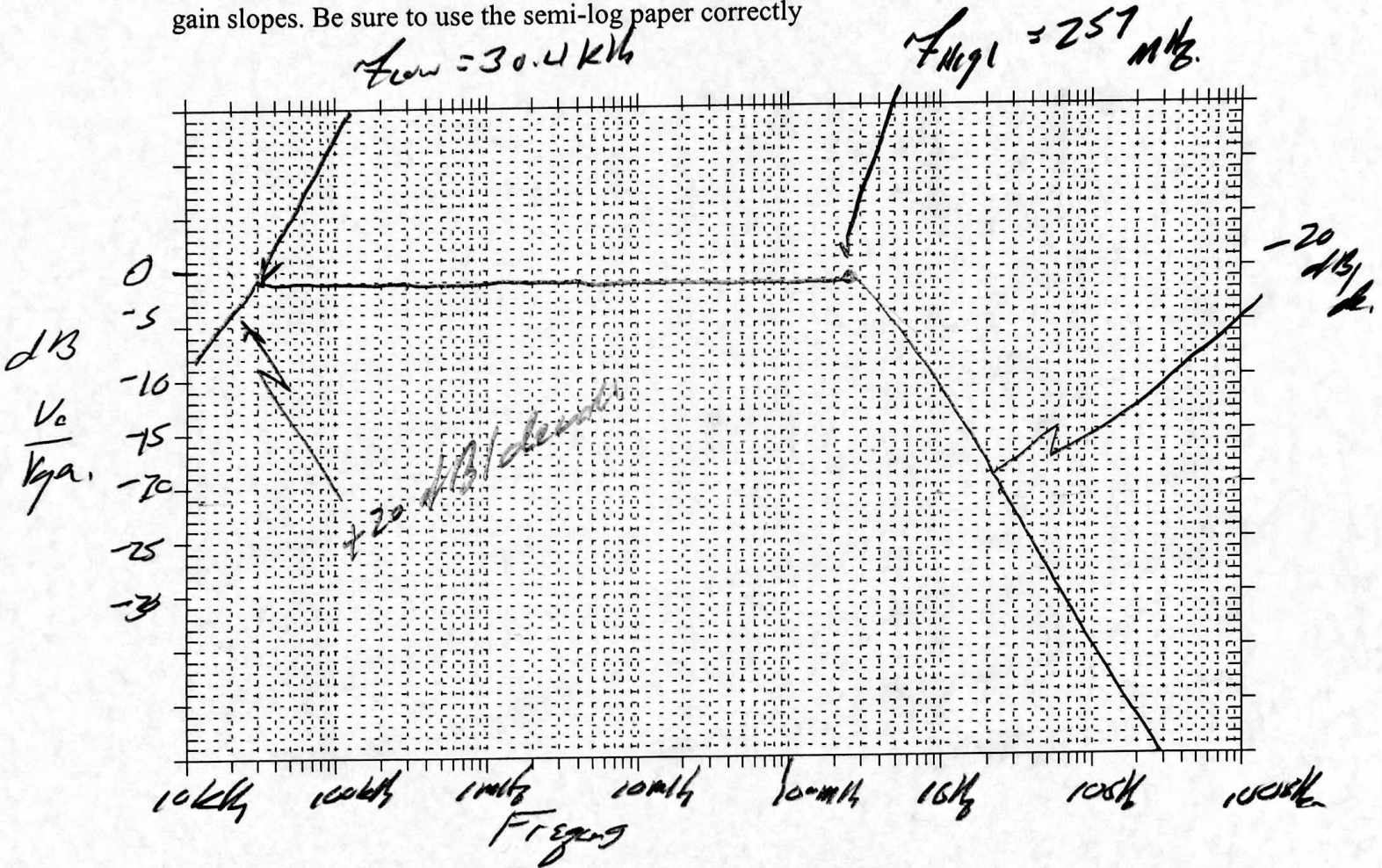Part g: 5 points

Draw a clean asymptotic Bode Magnitude plot of  $V_{out}/V_{gen}$  as a function of frequency in Hz. Be sure to label and dimension the axes clearly, label pole and zero frequencies and gain slopes. Be sure to use the semi-log paper correctly



$$\frac{V_o}{V_{in}} = 0.959 \cdot \frac{10}{11} = 0.872$$

$$\approx -1.2 \text{ dB}$$

$$\text{LE pole} = 30.4 \text{ kHz}$$


$$M_p = 257 \text{ MHz}$$

points above for having the feature  
 - in the right place  
 - labelled.



A


**Problem 2, 25 points**

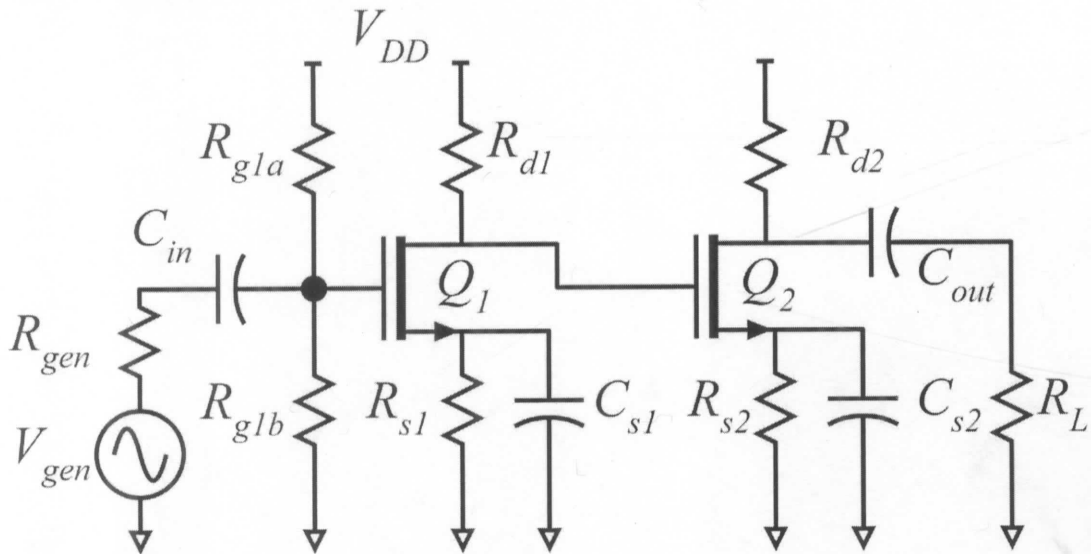

In the amplifier above,  
 $R_{gen}=100\text{k}\Omega$ ,  $R_{g1a}=R_{g1b}=500\text{k}\Omega$ ,  
 $R_{s1}=R_{s2}=100\ \Omega$ .  $V_{DD}=5\text{Volts}$   
 $g_{m1}=5\ \text{mS}$ ,  $g_{m2}=10\text{mS}$   
 $R_{d1}=1\ \text{k}\Omega$ ,  $R_{d2}=2\text{k}\Omega$ ,  $R_L=10\text{k}\Omega$ .  
 $C_{in}$ ,  $C_{out}$ ,  $C_{s1}$ ,  $C_{s2}$  are all very large  
 $C_{gs1}=0\text{fF}$ ,  $C_{gd1}=5\text{fF}$ ,  $C_{gs2}=20\ \text{fF}$ ,  $C_{gd2}=0\text{fF}$   
 $G_{ds1}=G_{ds2}=0\text{mS}$

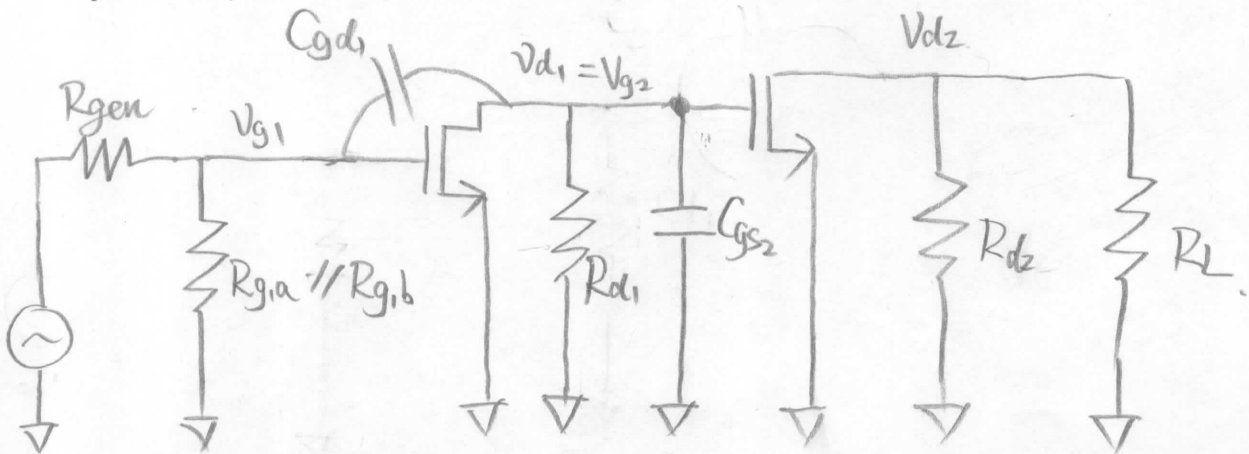**Part a: 4 points**

draw below a small-signal representation of the circuit, but with the transistors represented by transistor symbols, not small-signal hybrid-pi models



Part b, 6 points

Find the small-signal voltage gain of the two stages:

$$\begin{aligned} V_{out1}/V_{in1} &= V_{d1}/V_{g1} = \underline{\underline{-5}} \\ V_{out}/V_{in2} &= V_{d2}/V_{g2} = \underline{\underline{-16.7}} \end{aligned}$$

$$A_{v1} = -g_{m1} \cdot R_{Leq1} = -g_{m1} \cdot R_{d1} = -5 \text{ mS} \times 1 \text{ k}\Omega = -5$$

$$\begin{aligned} A_{v2} &= -g_{m2} \cdot R_{Leq2} = -g_{m2} \cdot (R_{d2} \parallel R_L) = -10 \text{ mS} \cdot 1.67 \text{ k}\Omega \\ &= -16.7 \end{aligned}$$

Part c, 10 points

using the method of time constants, find  $a_1$  and  $a_2$  of the circuit transfer function:

$$a_1 = \underline{2.17 \text{ ns}}$$

$$a_2 = \underline{7.14 \times 10^{-21} \text{ s}^2}$$

$$C_1 = C_{gd1} \quad C_2 = C_{gs2}$$

$$a_1 = R_{11}^0 \cdot C_1 + R_{22}^0 C_2$$

$$R_{11}^0 = (R_{gen} \parallel R_{g,a} \parallel R_{g,b}) (1 - A_{v1}) + R_{d1}$$

$$= 71.43 \text{ k}\Omega \times [1 - (-5)] + 1 \text{ k}\Omega$$

$$= 429.57 \text{ k}\Omega$$

$$R_{22}^0 = R_{d1} = 1 \text{ k}\Omega$$

$$a_1 = 429.57 \text{ k}\Omega \cdot 5 \text{ fF} + 1 \text{ k}\Omega \times 20 \text{ fF}$$

$$= 2.15 \text{ ns} + 20 \text{ ps} = 2.17 \text{ ns}$$

$$a_2 = R_{11}^0 C_1 C_2 R_{22}^1$$

$$R_{22}^1 = (R_{gen} \parallel R_{g,a} \parallel R_{g,b}) \parallel (1/g_{m1}) \parallel R_{d1}$$

$$= 71.43 \text{ k}\Omega \parallel 200 \Omega \parallel 1 \text{ k}\Omega = 166.28 \Omega$$

$$a_2 = 429.57 \text{ k}\Omega \times 5 \text{ fF} \times 20 \text{ fF} \times 166.28 \Omega$$

$$= 7.14 \times 10^{-21} \text{ s}^2$$

Part d, 5 points

There may be either 1 or 2 poles of the transfer function.

If the poles are real, give the 1 or 2 pole frequencies in Hz:

$$f_{p1} = \underline{73.27 \text{ MHz}}, f_{p2} = \underline{48.25 \text{ GHz}}$$

If there are 2 poles, and they are complex, give  $f_n = \omega_n / 2\pi$  and the damping factor  $\zeta$ :

$$f_n = \omega_n / 2\pi = \underline{\hspace{2cm}}, \zeta = \underline{\hspace{2cm}}$$

$$\frac{a_2}{a_1} = \frac{7.14 \times 10^{-21} \text{ s}^2}{2.17 \text{ ns}} = 3.29 \text{ ps} \ll a_1$$


$\Rightarrow$  2 real separated poles.

$$f_{p1} = \frac{1}{2\tau a_1} = 73.27 \text{ MHz}$$

$$f_{p2} = \frac{a_1}{2\tau a_2} = 48.25 \text{ GHz}$$

**Problem 3, 30 points**

**Part a 5 points**

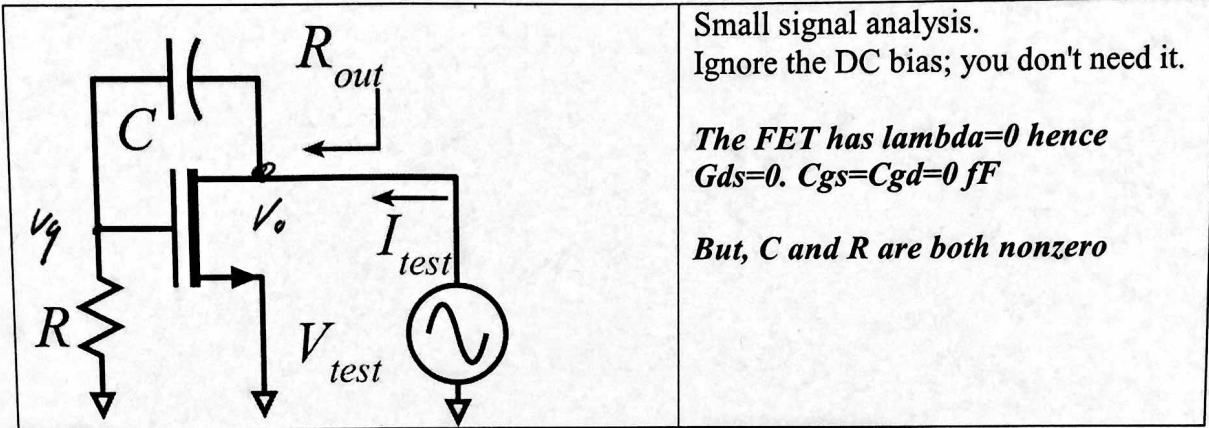

Small signal analysis.  
Ignore the DC bias; you don't need it.

The FET has  $\lambda=0$  hence  $G_{ds}=0$ .  $C_{gs}=C_{gd}=0$  fF

But,  $C$  and  $R$  are both nonzero

Replacing the transistor with its high frequency small-signal model, draw a small-signal equivalent circuit diagram.

③

$$\begin{aligned} \sum I &= 0 \Rightarrow V_g \\ V_g (R + (V_g - V_{test}) \Delta C) &= 0 \\ V_g [G + \Delta C] &= V_{test} \Delta C \\ V_g &= V_{test} \cdot \frac{\Delta C}{G + \Delta C} = V_{test} \cdot \frac{\Delta RC}{1 + \Delta RC} \end{aligned}$$

3 pts For correct KCL  
2 pt For correct answer.

$$\begin{aligned} I_{test} &= g_m V_g + \Delta C (V_{test} - V_g) \\ &= \Delta C \cdot V_{test} + (g_m - \Delta C) V_g = \Delta C V_{test} + \frac{(g_m - \Delta C) \Delta RC}{1 + \Delta RC} V_{test} \end{aligned}$$

$$\begin{aligned} Y(\Delta) = \frac{I_{test}}{V_{test}} &= \Delta C \left[ 1 + \frac{g_m - \Delta C}{1 + \Delta RC} R \right] = \Delta C \left[ \frac{1 + \Delta RC + g_m R - \Delta RC}{1 + \Delta RC} \right] \\ &= \Delta C \left[ \frac{1 + g_m R}{1 + \Delta RC} \right] \end{aligned}$$

$$Z(\Delta) = \frac{1}{\Delta C} \frac{1 + \Delta RC}{1 + g_m R}$$

Part c, 10 points

$g_m = 1 \text{ mS}$ ,  $R = 100 \text{ k}\Omega$ ,  $C = 1 \text{ pF}$

Find the frequencies of any zeros (there may be zero, one or two present) in  $Z(s)$ :

$f_{z1} = 1.59 \text{ MHz}$ ,  $f_{z2} = \underline{\hspace{2cm}}$ , ....

There may be either 1 or 2 poles in  $Z(s)$ .

If the poles are real, give the 1 or 2 pole frequencies in Hz:

$f_{p1} = 0 \text{ Hz}$ ,  $f_{p2} = \underline{\hspace{2cm}}$

If there are 2 poles, and they are complex, give  $f_n = \omega_n / 2\pi$  and the damping factor  $\zeta$ :


$f_n = \omega_n / 2\pi = \underline{\hspace{2cm}}$ ,  $\zeta = \underline{\hspace{2cm}}$

$$f_{z1} = \frac{1}{2\pi b_1} = \frac{1}{2\pi RC} = 1.59 \text{ MHz}$$

Part d, 5 points


Can you describe the behavior of  $Z(s)$  in terms of a simpler equivalent circuit?

- In low frequency,  $C$  is like open:

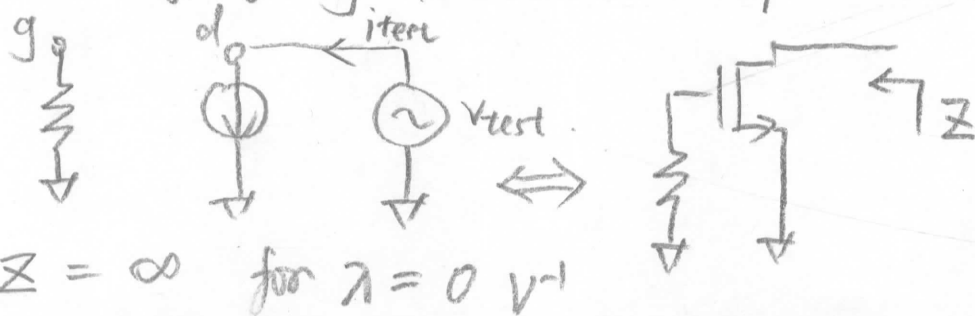

- As frequency increases,  $Z(s)$  drops as  $C$  starts to cause signal leakage

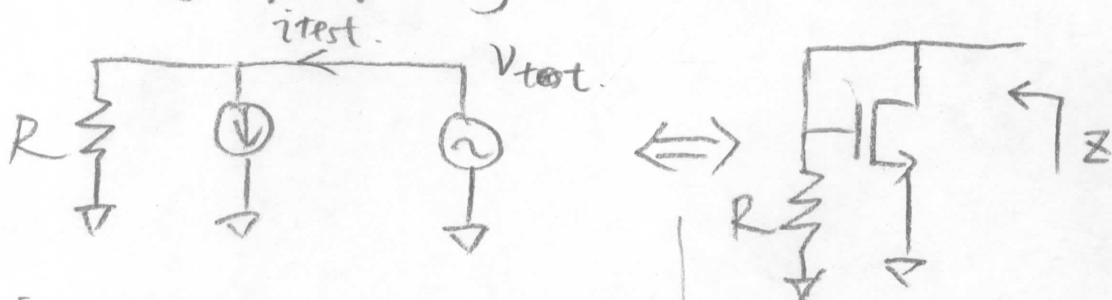- In high frequency,  $C$  is like short:



$$i_{test} = v_{test} \cdot g_m + v_{test} / R$$

$$Z = \frac{v_{test}}{i_{test}} = \frac{1}{g_m + \frac{1}{R}}$$

diode connected!

$$Z = \frac{1}{g_m} \parallel R$$