

Mid-Term Exam, ECE-137B
Tuesday, April 28, 2015

Closed-Book Exam

There are 2 problems on this exam , and you have 75 minutes.

1) show all work. Full credit will not be given for correct answers if supporting work is not shown.

2) please write answers in provided blanks

3) Don't Panic !

4) 137a, 137b crib sheets, and 2 pages personal sheets permitted.

Use any, all reasonable approximations. 5% accuracy is fine if the method is correct.

Do not turn over the cover page until requested to do


so.

Name: Selcicm **A**

Time function	LaPlace Transform
$\delta(t)$	1
$U(t)$	$1/s$
$e^{-\alpha t}U(t)$	$\frac{1}{s + \alpha}$
$e^{-\alpha t} \cos(\omega_d t)U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha t} \sin(\omega_d t)U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Problem	Points Received	Points Possible
1a		6
1b		8
1c		8
1d		14
1e		14
1f		10
2a		10
2b		10
2c		10
2d		10
total		100

Problem 1, 60 points

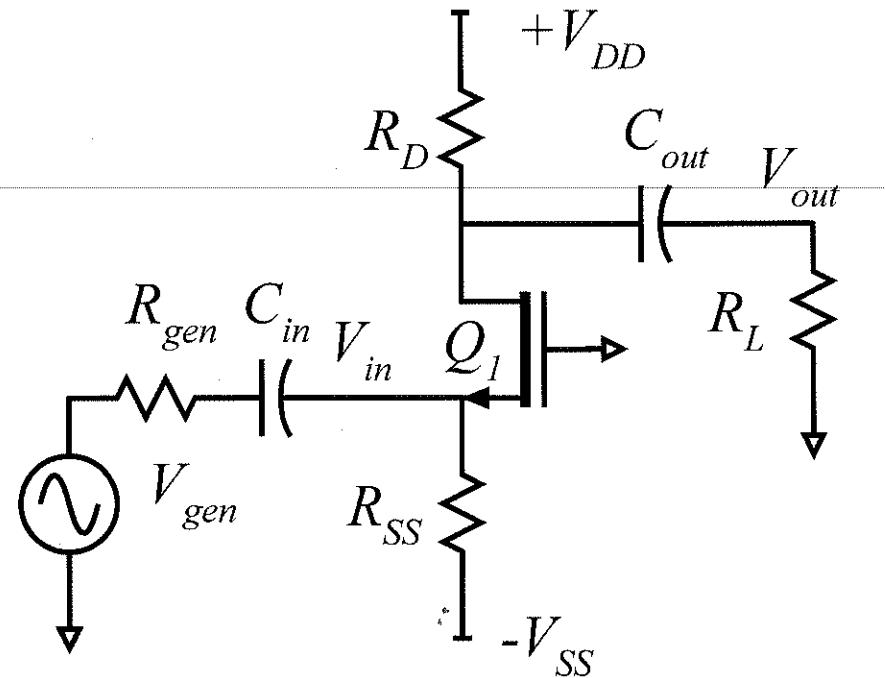

Q_1 has 1.0 nm oxide thickness, $\varepsilon_r = 3.8$, 22 nm gate length, and a 0.2 V threshold.

Mobility is $400 \text{ cm}^2/(\text{V}\cdot\text{s})$, saturation drift velocity is $1\text{E}7 \text{ cm/s}$, $\lambda = 0 \text{ Volts}^{-1}$,

$$C_{gs} = \varepsilon_r \varepsilon_{ox} L_g W_g / T_{ox} + (0.5\text{fF}/\mu\text{m}) \cdot W_g \quad \text{and} \quad C_{gd} = (0.5\text{fF}/\mu\text{m}) \cdot W_g .$$

Hints:

$$\varepsilon_r \varepsilon_{ox} / T_{ox} = 3.36 \cdot 10^{-2} \text{ F/m}^2, (\mu c_{ox} W_g / 2L_g) = (3.06 \cdot 10^{-2} \text{ A/V}^2) \cdot (W_g / 1\mu\text{m})$$

$$(c_{ox} v_{sat} W_g) = (3.36 \cdot 10^{-3} \text{ A/V}^1) \cdot (W_g / 1\mu\text{m}), (v_{sat} L_g / \mu) = 55 \text{ mV}.$$

The power supplies are +2V and -2V. The drain currents of Q_1 is 2 mA.

V_{gs} of Q_1 is 0.30 V. The drain of Q_1 is at +1.0V.

$$R_{gen} = 50\text{Ohm}, R_L = 3 \cdot R_D$$

$$C_{in} = 1 \text{ nF}, C_{out} = 2 \text{ nF}$$


Part a, 6 points

Find the following:

$$R_{ss} = \frac{850\Omega}{8.3\mu m} \quad R_D = \frac{500\Omega}{1500\Omega}$$

$$3.36 \frac{mA}{V} \cdot \frac{W}{\mu m}$$

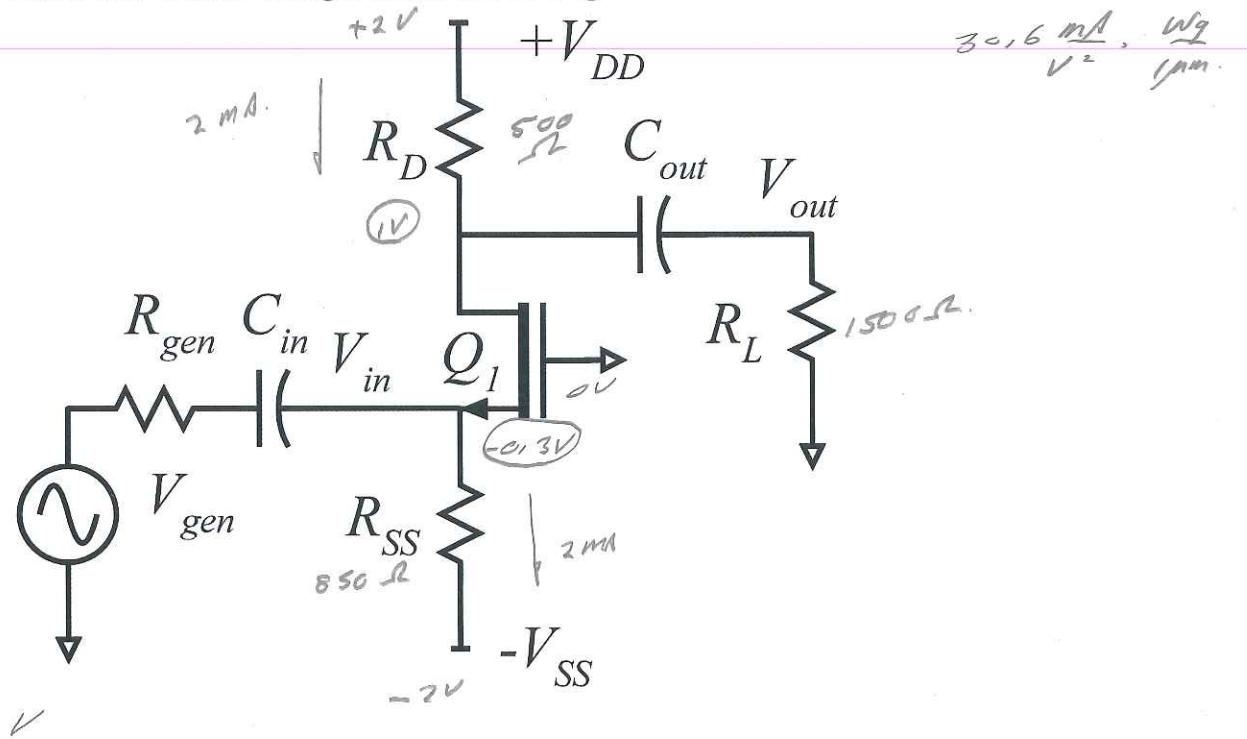Draw all DC node voltages on the circuit diagram below.



$$30.6 \frac{mA}{V^2} \cdot \frac{W}{\mu m}$$

$$V_{th} = 0.2V, \quad V_{gs} = 0.6V \approx V_{gs} + \Delta V \\ \rightarrow \text{velocity limit}$$

$$\frac{I_D}{2} = 3.36 \frac{mA}{V} \cdot \frac{W}{\mu m} (V_{gs} - 0.228V) \\ \Rightarrow W = 8.23 \mu m \\ \Rightarrow I_D = 27.8 \frac{mA}{V} (V_{gs} - 0.228V)$$

$$R_D = 1V / 2mA = 500\Omega$$

$$R_{SS} = \frac{1.7V}{2mA} = 850\Omega$$

$$R_L = 3 \cdot R_D = 1500\Omega$$

Part b, 8 points

small-signal parameters

Find the following

$$C_{gs} = \frac{66.1 \text{ fF}}{27.8 \text{ ms}} \quad C_{gd} = \frac{4.15 \text{ fF}}{\cancel{65.0 \text{ GHz}}} \quad 305 \text{ GHz}$$

$$\begin{aligned} C_{qs} &= 3.36 \cdot 10^{-2} \frac{\text{fF}}{\text{m}^2} \cdot \frac{L}{w_g} + 0.567 \mu\text{m} \cdot w_g \\ &\quad \frac{1}{22 \mu\text{m}} \quad \frac{1}{8.3 \mu\text{m}} \quad \frac{1}{8.3 \mu\text{m}} \\ &= 6.19 \text{ fF} + 4.15 \text{ fF} \\ &= \cancel{66.1 \text{ fF}} \quad 10.34 \text{ fF} \end{aligned}$$

$$C_{gd} = 0.567 \mu\text{m} \cdot w_g = 4.15 \text{ fF}$$

$$I_D = 27.8 \frac{\text{mA}}{\text{V}} \cdot (V_{GS} - 0.228 \text{ V}) \Rightarrow g_m = \underline{27.8 \text{ ms}}$$

$$\begin{aligned} f_T &= \frac{1}{2\pi} \frac{g_m}{R_{DS} + C_{gd}} = 0.159 \frac{27.8 \text{ ms}}{\cancel{65.0 \text{ GHz}}} \\ &= \cancel{65.0 \text{ GHz}} \quad 305.35 \text{ GHz} \end{aligned}$$

Part c: 8 points

Mid Band Analysis:


Find the following:

$$R_{in, \text{Amplifier}} = \frac{34.5\Omega}{50\Omega}$$

$$V_{out}/V_{in} = \frac{10.42}{375\Omega}$$

$$V_{in}/V_{gen} = \frac{0.408}{4.25}$$

$$V_{in}/V_{gen} = \underline{4.25}$$

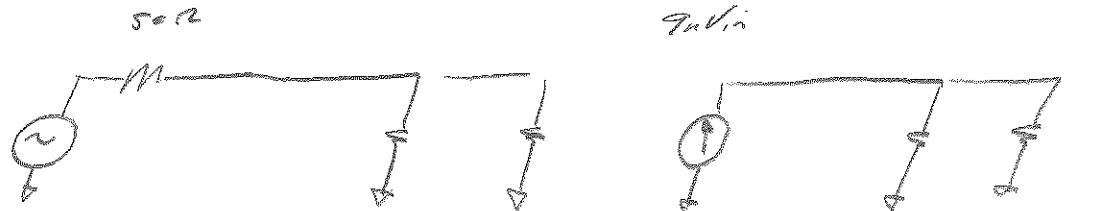

$$R_M = 850\Omega$$

$$V_{gen} = 35.97\Omega$$

$$R_B = 850\Omega$$

$$R_L = 1500\Omega$$

$$R_{in, \text{Amp}} = 35.97\Omega // 850\Omega$$

$$= 34.5\Omega$$

$$R_{eq} = R_B // R_L = 500\Omega // 1500\Omega = 325\Omega$$

$$R_T = R_{in, \text{Amp}} // R_{eq} = 20.4\Omega$$

$$V_{in}/V_{gen} = \frac{R_{in, \text{Amp}}}{R_{in, \text{Amp}} + R_{eq}} = \frac{34.5\Omega}{34.5\Omega + 325\Omega} = 0.408$$


$$V_{in}/V_{gen} = g_m R_{eq} = \frac{375\Omega}{35.97\Omega} = 10.42$$

Part d: 14 points

High-Frequency Analysis:

Find the frequencies, in Hz, of the two poles limiting the high-frequency response of the amplifier. Show your analysis (do not simply state that the input pole of a common-gate amplifier is approximately at f_τ)
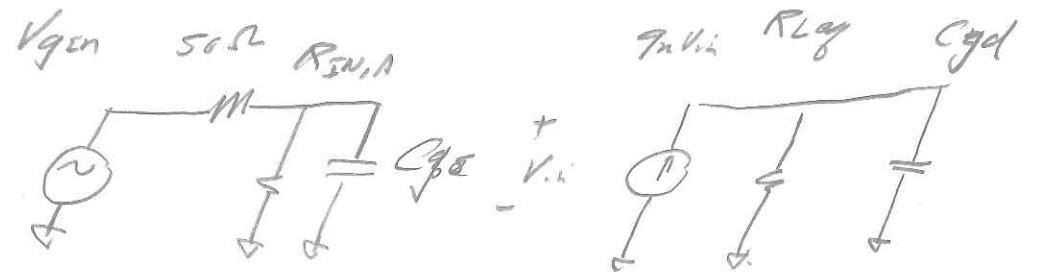
$$f_{p1,HF} = \frac{754}{118.6 \text{ Hz}} \quad f_{p2,HF} = \underline{102.6 \text{ Hz}}$$



$$\begin{aligned} T_{\tau_1} &= R_I \cdot C_{gs} \\ &= 20.4 \Omega \cdot \cancel{10.34 \text{ fF}} \quad 10.34 \text{ fF} \\ &\approx 1.35 \text{ ps} \quad 21.1 \text{ pS} \end{aligned}$$

$$f_{p1,HF} = \frac{0.1159}{\tau} = \cancel{118.6 \text{ Hz}} \quad 754.5 \text{ GHz}$$

$$\begin{aligned} T_{\tau_2} &= R_{load} \cdot C_{gd} \\ &= 375 \Omega \cdot 41.15 \text{ fF} \\ &\approx 1.56 \text{ ps} \end{aligned}$$


$$f_{p2,HF} = \frac{0.1159}{\tau} = 102.6 \text{ Hz}$$

Part e: 14 points

Low-Frequency Analysis:

Find the frequencies, in Hz, of the two poles limiting the low-frequency response of the amplifier. Show your analysis.
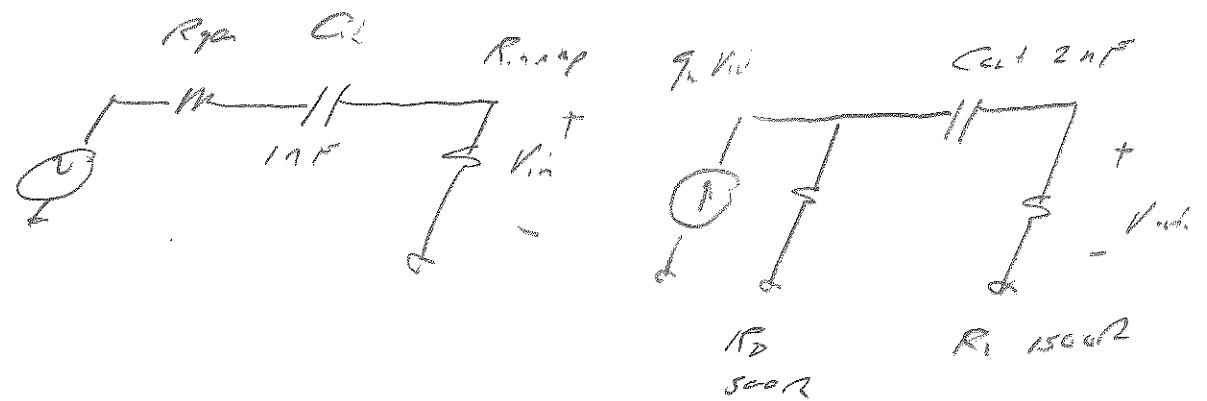
$$f_{p1,LF} = \frac{1.88 \text{ kHz}}{110} \quad f_{p2,LF} = \frac{39.8 \text{ kHz}}{15000}$$



$$\begin{aligned} T_{1,L} &= R_1 C_1 \\ &= (R_{3\text{in}} + R_{1\text{out}}) C_1 \\ &= 84.5 \text{ s} \cdot 1 \text{ nF} \\ &= 84.5 \text{ ms} \end{aligned}$$


$$f_{p1,LF} = 1.88 \text{ kHz} = \frac{0.159}{T} = \frac{0.159}{84.5 \text{ ms}}$$

$$\begin{aligned} T_{2,L} &= (R_5 + R_4) C_2 \\ &= 20000 \cdot 2 \text{ nF} \\ &= 4 \text{ ms} \end{aligned}$$

$$f_{p2,LF} = \frac{0.159}{4 \text{ ms}} = 39.8 \text{ kHz}$$

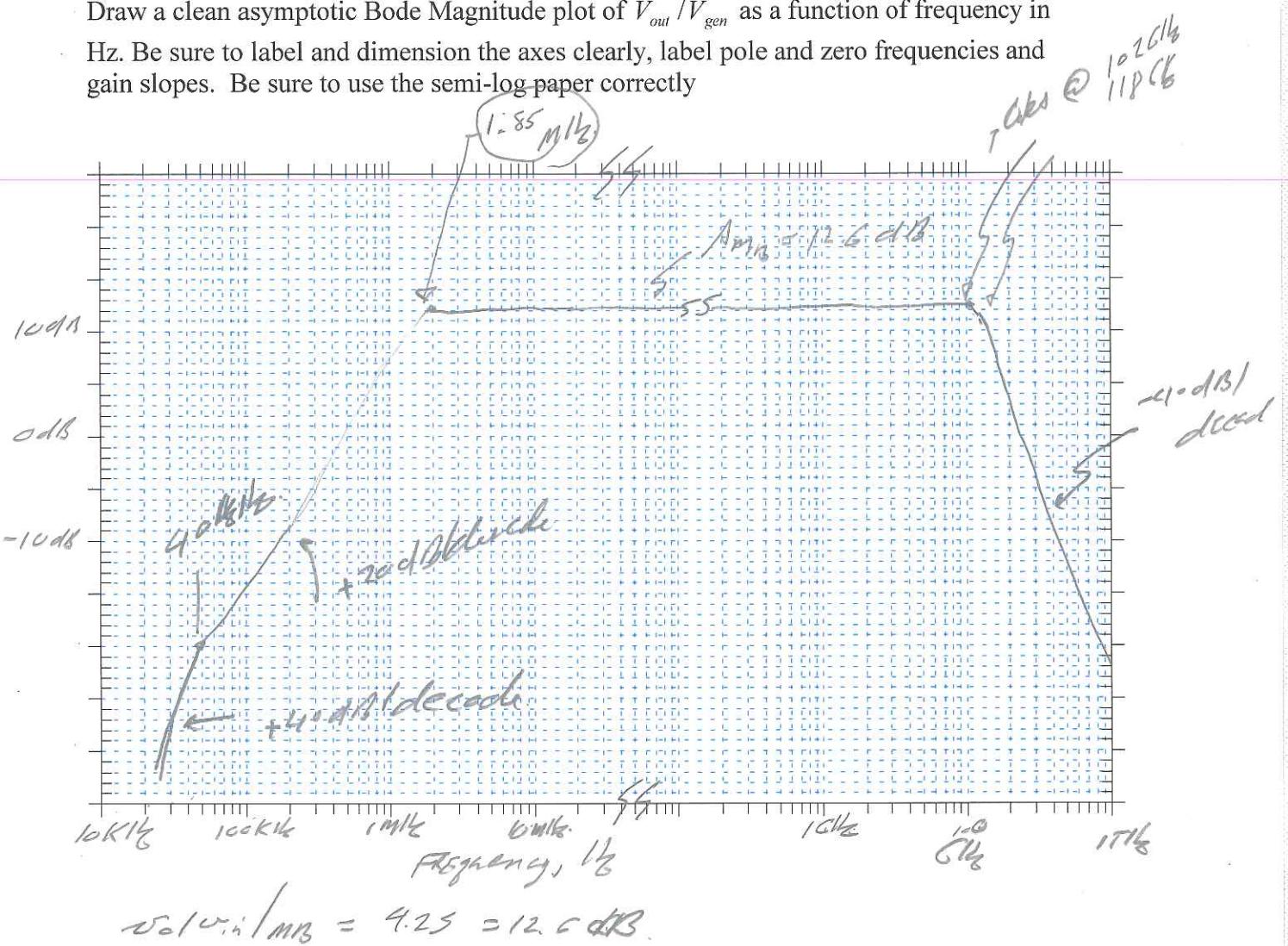Part f: 10 points

- Draw a clean asymptotic Bode Magnitude plot of V_{out} / V_{gen} as a function of frequency in Hz. Be sure to label and dimension the axes clearly, label pole and zero frequencies and gain slopes. Be sure to use the semi-log paper correctly





LF: 1.85MHz, 37.8MHz

HF: 118MHz, 102.6GHz

(plot has too small a range, therefore had to split scales)

Problem 2, 40 points

Part a 10 points

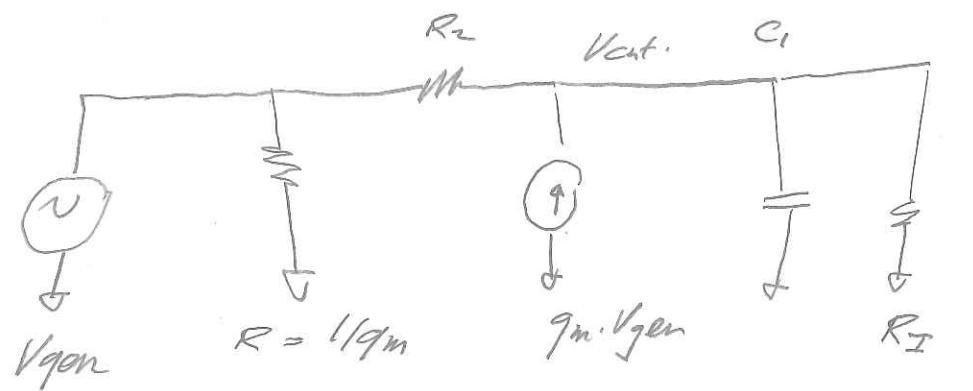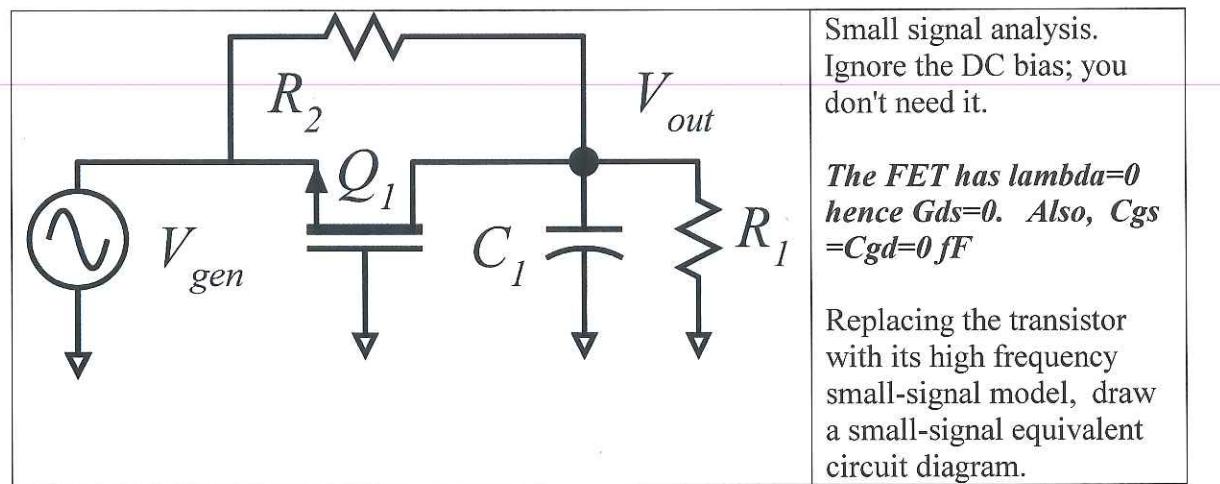

Part b, 10 points

USING NODAL ANALYSIS, compute $V_{out}(s)/V_{gen}(s)$ in ratio-of-polynomials form:

$$\frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}} \Big|_{mid-band} \times (s\tau)^m \times \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$$

here m , an integer, can be positive or negative or zero

$$ZI = 0 \quad @ \quad V_{out}$$

$$V_{out}[G_2 + G_1 + AC_1] + V_{gen}[-G_2 - g_m] = 0.$$

$$\frac{V_{out}}{V_{gen}} = \frac{G_2 + g_m}{G_1 + G_2 + AC_1}$$

$$= \frac{G_2 + g_m}{G_1 + G_2} \cdot \frac{1}{1 + s C_1 (G_1 + G_2)}$$

$$\boxed{\frac{V_{out}}{V_{gen}} = (g_m + 1/R_2) R_1 // R_2 \cdot \frac{1}{1 + s C_1 (R_1 // R_2)}}$$

Part c, 10 points

$$g_m = 10 \text{ mS}, R_1 = 1 \text{ kOhm}, R_2 = 3 \text{ kOhm}, C_1 = 1 \text{ pF}$$

Find the frequencies of any zeros (there may be zero, one or two present) in the transfer function:

$$f_{z1} = \cancel{\text{_____}}, f_{z2} = \cancel{\text{_____}}, \dots$$

There may be either 1 or 2 poles of the transfer function.

If the poles are real, give the 1 or 2 pole frequencies in Hz:

$$f_{p1} = \cancel{212 \text{ mHz}}, f_{p2} = \cancel{\text{_____}}$$

If there are 2 poles, and they are complex, give $f_n = \omega_n / 2\pi$ and the damping factor ζ :

$$f_n = \omega_n / 2\pi = \text{_____}, \zeta = \text{_____}$$

There is a single, real pole in the transfer function.

$$\begin{aligned} T_p &= (R_1 \| R_2) C_1 \\ &= 750 \Omega \cdot 1 \text{ pF} \\ &= 750 \text{ ps} \end{aligned}$$

$$\frac{1}{T_p} = \frac{0.159}{\gamma} = 212 \text{ mHz}$$

low frequency gain

$$= (g_m + 1/R_2)(R_1/R_2)$$

$$= 10.333 \text{ mS} (750 \Omega)$$

$$= 7.73$$

Part d, 10 points

If $V_{in}(t)$ is a 100mV step-function, find and plot $V_{out}(t)$. Be sure to label and dimension the axes clearly, and to clearly label key features of the time waveform.



by inspection:

$$v_o(t) = 0.1 \cdot 7.73 \cdot \text{act} \left[1 - e^{-t/\tau} \right]$$

$$= 0.773 \cdot \text{act} \left[1 - e^{-t/750 \text{ ps}} \right]$$