

Mid-Term Exam, ECE-137B
Tuesday, April 28, 2015

Closed-Book Exam

There are 2 problems on this exam , and you have 75minutes.

1) show all work. Full credit will not be given for correct answers if supporting work is not shown.

2) please write answers in provided blanks

3) Don't Panic !

4) 137a, 137b crib sheets, and 2 pages personal sheets permitted.

Use any, all reasonable approximations. 5% accuracy is fine if the method is correct.


Do not turn over the cover page until requested to do so.

Name: Solution **B**

Time function	LaPlace Transform
$\delta(t)$	1
$U(t)$	$1/s$
$e^{-\alpha t}U(t)$	$\frac{1}{s + \alpha}$
$e^{-\alpha t} \cos(\omega_d t)U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha t} \sin(\omega_d t)U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Problem	Points Received	Points Possible
1a		6
1b		8
1c		8
1d		14
1e		14
1f		10
2a		10
2b		10
2c		10
2d		10
total		100

Problem 1, 60 points

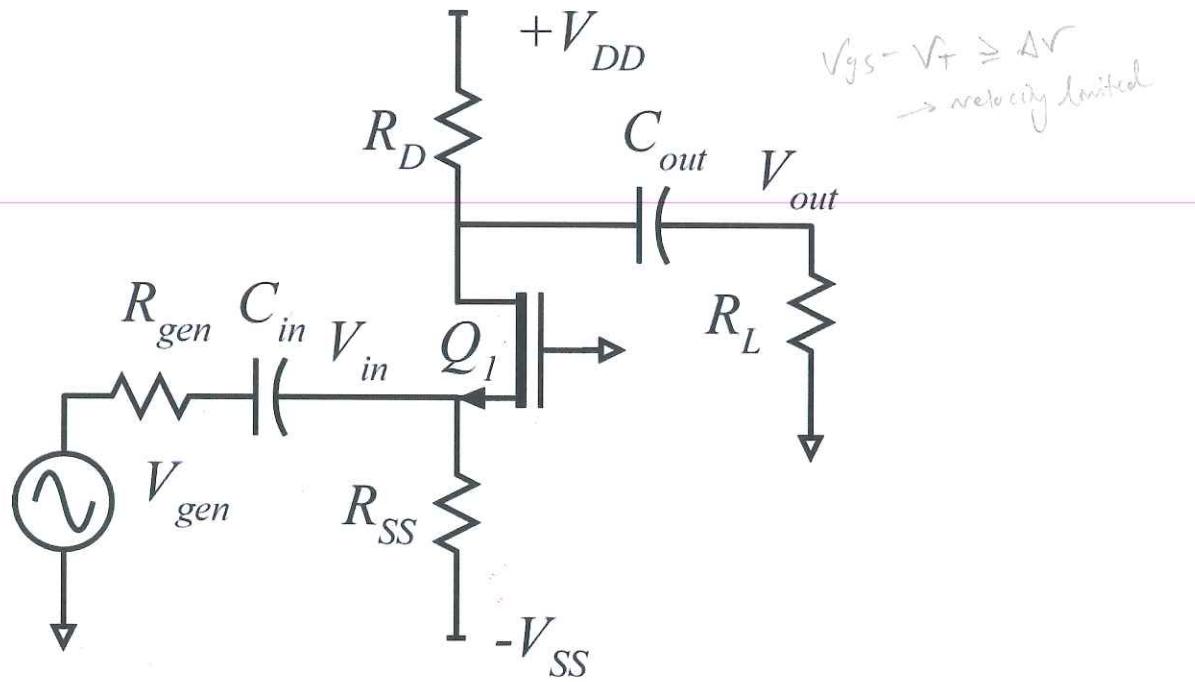

Q1 has 1.0 nm oxide thickness, $\epsilon_r = 3.8$, 22 nm gate length, and a 0.2 V threshold.

Mobility is $400 \text{ cm}^2/(\text{V}\cdot\text{s})$, saturation drift velocity is $1\text{E}7 \text{ cm/s}$, $\lambda = 0 \text{ Volts}^{-1}$,

$$C_{gs} = \epsilon_r \epsilon_{ox} L_g W_g / T_{ox} + (0.5 \text{ fF}/\mu\text{m}) \cdot W_g \quad \text{and} \quad C_{gd} = (0.5 \text{ fF}/\mu\text{m}) \cdot W_g$$

Hints:

$$\epsilon_r \epsilon_{ox} / T_{ox} = 3.36 \cdot 10^{-2} \text{ F/m}^2, (\mu c_{ox} W_g / 2L_g) = (3.06 \cdot 10^{-2} \text{ A/V}^2) \cdot (W_g / 1\mu\text{m})$$

$$(c_{ox} v_{sat} W_g) = (3.36 \cdot 10^{-3} \text{ A/V}^1) \cdot (W_g / 1\mu\text{m}), (v_{sat} L_g / \mu) = 55 \text{ mV}.$$

The power supplies are +2V and -2V. The drain currents of Q1 is 1mA.

V_{gs} of Q1 is 0.24 V. The drain of Q1 is at +1.0V.

$$R_{gen} = 50 \Omega$$


$$C_{in} = 1 \text{ nF}, C_{out} = 2 \text{ nF}$$

Part a, 6 points

Find the following:

$$R_{ss} = \frac{1.76 \text{ k}\Omega}{20.4 \mu\text{m}} \quad R_D = \frac{1 \text{ k}\Omega}{3 \text{ k}\Omega}$$

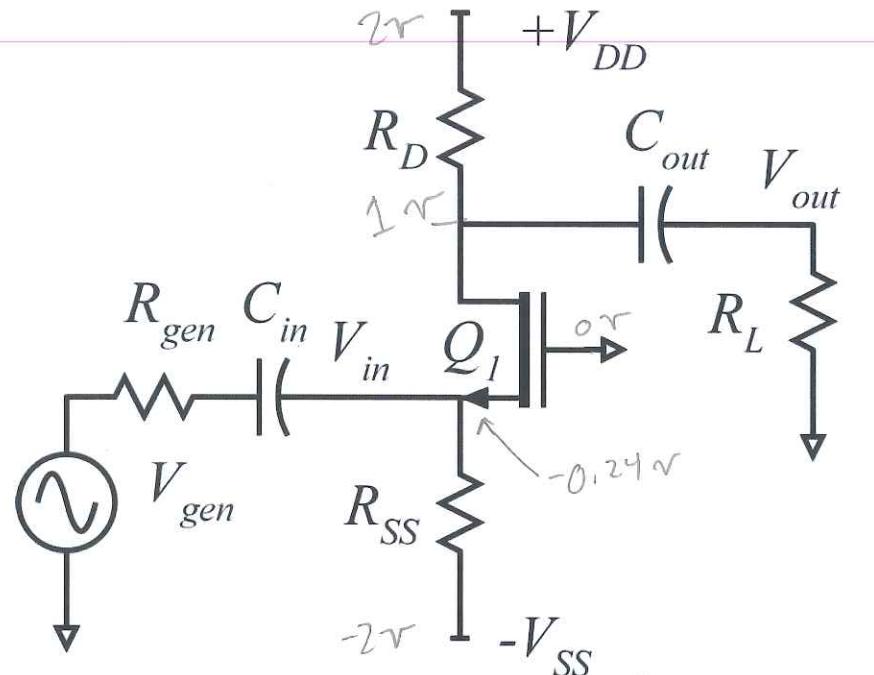Draw all DC node voltages on the circuit diagram below.



$$V_{th} = 0.2 \text{ volts}$$

$$V_{gs} = 0.24 \text{ volts}$$

$$V_{gs} = 0.24 \text{ volts} < 0.255 \text{ volts}$$

\rightarrow mobility limited

$$\Delta V = \frac{Lg V_{sat}}{\mu} = \frac{(22 \times 10^{-7} \text{ cm})(1 \times 10^7 \text{ cm})}{400 \text{ cm}^2/\text{V}\cdot\text{s}}$$

$$\Delta V = 0.055 \text{ mV}$$

also given in problem

$$I_d = \left(\frac{\mu C_{ox} W_g}{2 L_g} \right) (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

$$1 \text{ mA} = \left(3.06 \times 10^{-2} \frac{\text{A}}{\text{V}^2} \right) \left(\frac{W_g}{1 \mu\text{m}} \right) (0.24 \text{ volts} - 0.2 \text{ volts})^2$$

$$W_g = 20.423 \mu\text{m}$$

$$V_g = 0, \text{ so } V_s = -0.24 \text{ volts}$$

$$\frac{V_s - (-V_{ss})}{R_{ss}} = 1 \text{ mA} = I_d$$

$$R_{ss} = 1760 \Omega$$

$$V_D = 1.0 \text{ volts} \quad \frac{V_{DD} - V_D}{R_D} = 1 \text{ mA} = I_d$$

$$R_D = 100 \Omega$$

3

$$R_L = 3 R_D$$

$$R_L = 3 \text{ k}\Omega$$

b

Part b, 8 points

small-signal parameters

Find the following

$$C_{gs} = \frac{25.28 \text{ fF}}{49.9 \text{ mS}} \quad C_{gd} = \frac{10.2 \text{ fF}}{224 \text{ GHz}}$$

$$\begin{aligned} C_{gs} &= \left[\underbrace{\frac{\epsilon_r \epsilon_{ox} L_g}{T_{ox}}}_{\text{Eqn 1}} + \left(0.5 \frac{\text{fF}}{\mu\text{m}} \right) \right] \cdot W_g \\ &= \left[\frac{(3.36 \times 10^{-2} \frac{\text{F}}{\mu\text{m}^2})(22 \times 10^{-9} \text{ m})}{(1 \times 10^{-9} \text{ m})} + 0.5 \times 10^{-9} \frac{\text{F}}{\text{m}} \right] (20.4 \times 10^{-6} \text{ m}) \\ &= (1.239 \times 10^{-9} \frac{\text{F}}{\text{m}}) (20.4 \times 10^{-6} \text{ m}) \end{aligned}$$

$$\underline{C_{gs} = 25.28 \text{ fF}}$$

$$\begin{aligned} f_T &= \frac{1}{2\pi} \frac{g_m}{C_{gs} + C_{gd}} \\ &= \left(\frac{1}{2\pi} \right) \frac{0.04994 \text{ A/V}}{(25.28 \text{ fF} + 10.2 \text{ fF})} \end{aligned}$$

$$\begin{aligned} C_{gd} &= (0.5 \text{ fF}/\mu\text{m}) \cdot W_g \\ &= (0.5 \times 10^{-9} \frac{\text{F}}{\text{m}}) (20.4 \times 10^{-6} \text{ m}) \end{aligned}$$

$$\underline{C_{gd} = 10.2 \text{ fF}}$$

$$\underline{f_T = 224.02 \text{ GHz}}$$

$$\begin{aligned} g_m &= \left(\frac{\mu C_{ox} W_g}{L_g} \right) (V_{gs} - V_{th}) \\ &= 2 \left(3.06 \times 10^{-2} \frac{\text{A}}{\text{V}^2} \right) \left(\frac{20.4 \text{ mV}}{1 \text{ mV}} \right) (0.24 \text{ mV} - 0.2 \text{ mV}) \end{aligned}$$

$$\underline{g_m = 0.04994 \text{ A/V}}$$


Part c: 8 points

Mid Band Analysis:

Find the following:

$$R_{in, \text{Amplifier}} = \underline{19.8\Omega} \quad R_{L,eq} = \underline{750\Omega}$$
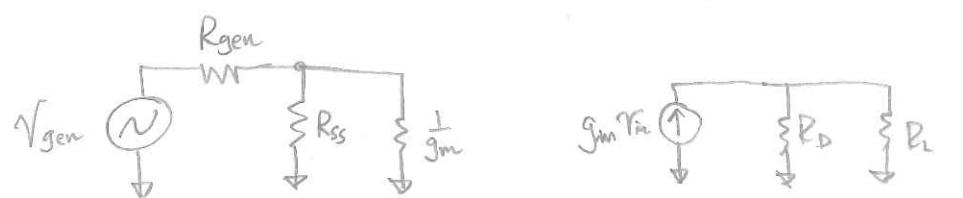
$$V_{out}/V_{in} = \underline{37.45} \quad V_{in}/V_{gen} = \underline{0.2837}$$



$$\begin{aligned} R_{gen} &= 50\Omega \\ R_{ss} &= 1760\Omega \\ R_D &= 1000\Omega \\ R_L &= 3000\Omega \\ \frac{1}{g_m} &= 20.0243\Omega \end{aligned}$$

$$R_{in, \text{Amp}} = R_{ss} \parallel \frac{1}{g_m} = 1760\Omega \parallel 20.0243\Omega$$

$$\underline{R_{in, \text{Amp}} = 19.8\Omega}$$

$$R_{L,eq} = R_D \parallel R_L = 1k\Omega \parallel 3k\Omega$$

$$\underline{R_{L,eq} = 750\Omega}$$

$$R_I = R_{in, \text{Amp}} \parallel R_{gen} = 19.8\Omega \parallel 50\Omega$$

$$\underline{R_I = 14.183\Omega}$$

$$\frac{V_m}{V_{gen}} = \frac{R_{in, \text{Amp}}}{R_{in, \text{Amp}} + R_{gen}} = \frac{19.8\Omega}{19.8\Omega + 50\Omega} = 0.2837 = \underline{\frac{V_m}{V_{gen}}}$$


$$\frac{V_{out}}{V_{in}} = g_m R_{L,eq} = \left(\frac{1}{20.0243\Omega}\right)(750\Omega) = 37.45 = \underline{\frac{V_{out}}{V_{in}}}$$

Part d: 14 points

High-Frequency Analysis:

Find the frequencies, in Hz, of the two poles limiting the high-frequency response of the amplifier. Show your analysis (do not simply state that the input pole of a common-gate amplifier is approximately at f_t)
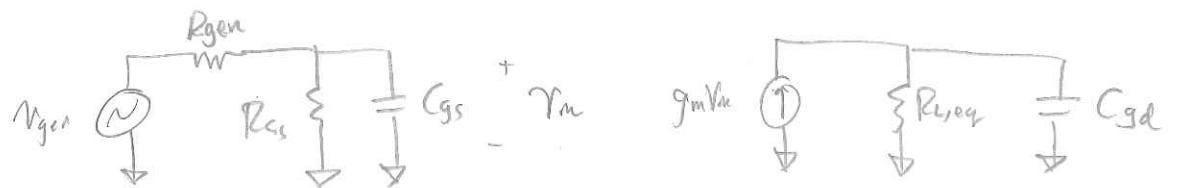
$$f_{p1,HF} = \underline{20.805 \text{ GHz}} \quad f_{p2,HF} = \underline{438.1 \text{ GHz}}.$$



$$\begin{aligned} Y_{in} &= R_s + C_{gs} \\ &= (14.183\Omega) (25.28fF) \end{aligned}$$

$$T_{in} = 3.585 \times 10^{-13} \text{ seconds}$$

$$\begin{aligned} T_{out} &= R_{L,eq} C_{gd} \\ &= (750\Omega) (10.2fF) \end{aligned}$$

$$T_{out} = 7.65 \times 10^{-12} \text{ seconds}$$

$$f_{p1} = \underline{\left(\frac{1}{2\pi T_1}\right)} = 438.1 \text{ GHz}$$

$$f_{p2} = \underline{\frac{1}{2\pi T_2}} = 20.805 \text{ GHz}$$

Part e: 14 points

Low-Frequency Analysis:

Find the frequencies, in Hz, of the two poles limiting the low-frequency response of the amplifier. Show your analysis.

$$f_{p1,LF} = \underline{19.894 \text{ kHz}} \quad f_{p2,LF} = \underline{2.28 \text{ MHz}}$$



$$\begin{aligned} T_{in} &= (R_{gen} + R_{in,Amp}) C_{in} \\ &= (50\Omega + 19.8\Omega) (1\text{nF}) \end{aligned}$$

$$T_{in} = 69.8 \text{ ns}$$

$$f_{p1} = \underline{\frac{1}{2\pi T_1} = 2.28 \text{ MHz}}$$


$$\begin{aligned} T_{out} &= (R_D + R_L) C_{out} \\ &= (1k\Omega + 3k\Omega) (2\text{nF}) \end{aligned}$$

$$T_{out} = 8 \mu\text{s}$$

$$f_{p2} = \underline{\frac{1}{2\pi T_2} = 19.894 \text{ kHz}}$$

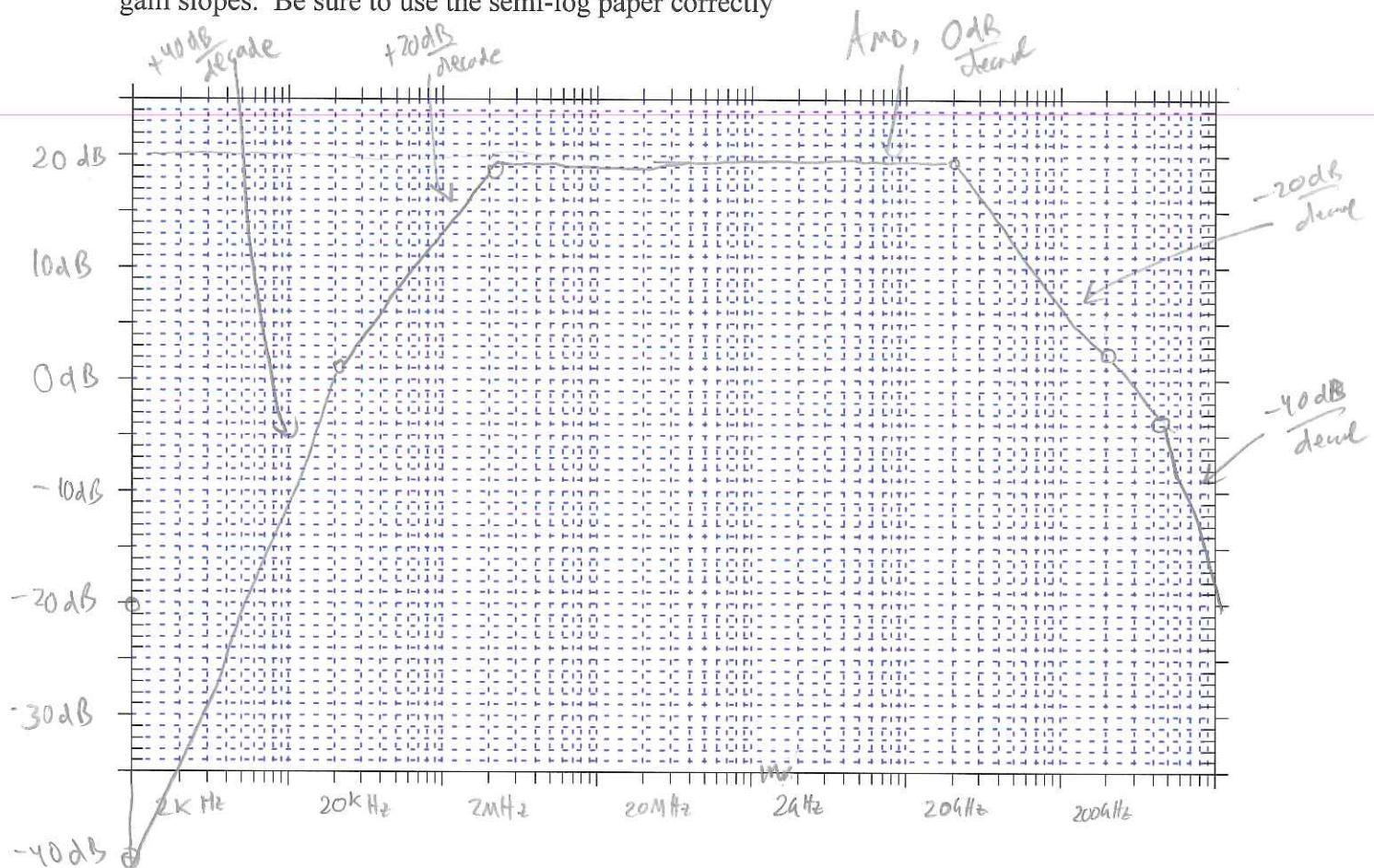Part f: 10 points

Draw a clean asymptotic Bode Magnitude plot of V_{out}/V_{gen} as a function of frequency in Hz. Be sure to label and dimension the axes clearly, label pole and zero frequencies and gain slopes. Be sure to use the semi-log paper correctly





$$\left(\frac{V_{out}}{V_{gen}}\right)_{MB} = (37.45)(0.2837) = 10.6245 \Rightarrow 20.526 \text{ dB}$$

LF: 19.894 kHz, 2.28 MHz

HF: 20.805 GHz, 438.1 GHz

Problem 2, 40 points

Part a 10 points

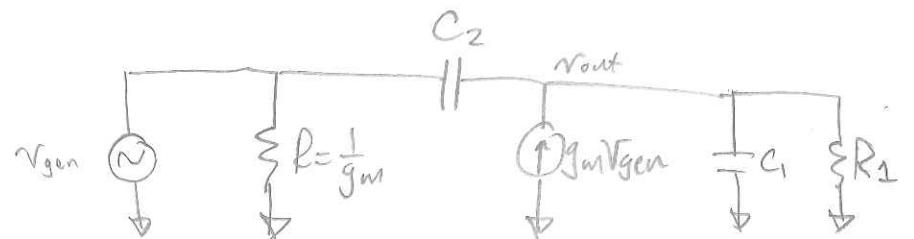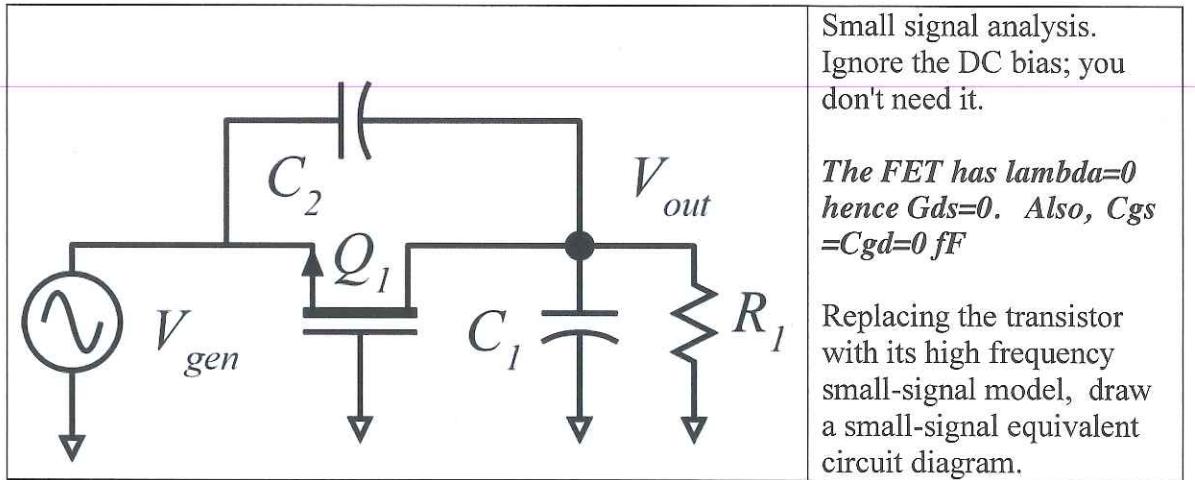

Part b, 10 points

USING NODAL ANALYSIS, compute $V_{out}(s)/V_{gen}(s)$ in ratio-of-polynomials form:

$$\frac{V_{out}(s)}{V_{gen}(s)} = \left. \frac{V_{out}}{V_{gen}} \right|_{mid-band} \times (s\tau)^m \times \frac{1+b_1s+b_2s^2+\dots}{1+a_1s+a_2s^2+\dots} = \underline{\hspace{10cm}}$$

here m , an integer, can be positive or negative or zero

$$\sum I = 0 @ V_{out}$$

$$\underbrace{\left(\frac{V_{out} - V_{gen}}{\frac{1}{sC_2}} \right)}_{\text{Going out}} + \underbrace{\left(-g_m V_{gen} \right)}_{\text{Going out}} + \underbrace{\left(\frac{V_{out} - 0}{\frac{1}{sC_1}} \right) + \left(\frac{V_{out} - 0}{R_1} \right)}_{\text{Going out}} = 0$$

$$V_{out} \left(sC_2 + sC_1 + \frac{1}{R_1} \right) - V_{gen} \left(sC_2 + g_m \right) = 0$$

$$\frac{V_{out}}{V_{gen}} = \frac{sC_2 + g_m}{s(C_1 + C_2) + \frac{1}{R_1}}$$

$$\boxed{\frac{V_{out}}{V_{gen}} = \left(g_m R_1 \right) \cdot \frac{\left(1 + s \frac{C_2}{g_m} \right)}{\left(1 + s R(C_1 + C_2) \right)}}$$

Part c, 10 points

$$g_m = 10 \text{ mS}, R_1 = 1 \text{ kOhm}, C_1 = 1 \text{ pF}, C_2 = 2 \text{ pF}$$

Find the frequencies of any zeros (there may be zero, one or two present) in the transfer function:

$$f_{z1} = \underline{796 \text{ MHz}}, f_{z2} = \underline{\quad}, \dots$$

There may be either 1 or 2 poles of the transfer function.

If the poles are real, give the 1 or 2 pole frequencies in Hz:

$$f_{p1} = \underline{53.05 \text{ MHz}}, f_{p2} = \underline{\quad}$$

If there are 2 poles, and they are complex, give $f_n = \omega_n / 2\pi$ and the damping factor ζ :

$$f_n = \omega_n / 2\pi = \underline{\quad}, \zeta = \underline{\quad}$$

$$H(s) = (g_m R_2) \cdot \frac{1 + s \left(\frac{C_2}{g_m} \right)}{1 + s(R_1(C_1 + C_2))}$$


$$\tau_{z1} = \frac{C_2}{g_m} = 200 \text{ ps} \quad f_{z1} = \underline{\frac{1}{2\pi\tau_{z1}}} = 795.77 \text{ MHz}$$

$$\tau_{p1} = R_1(C_1 + C_2) = 3 \text{ ns} \quad f_p = \underline{\frac{1}{2\pi\tau_{p1}}} = 53.05 \text{ MHz}$$

$$LF_{\text{gain}} = g_m R_1 = 10$$

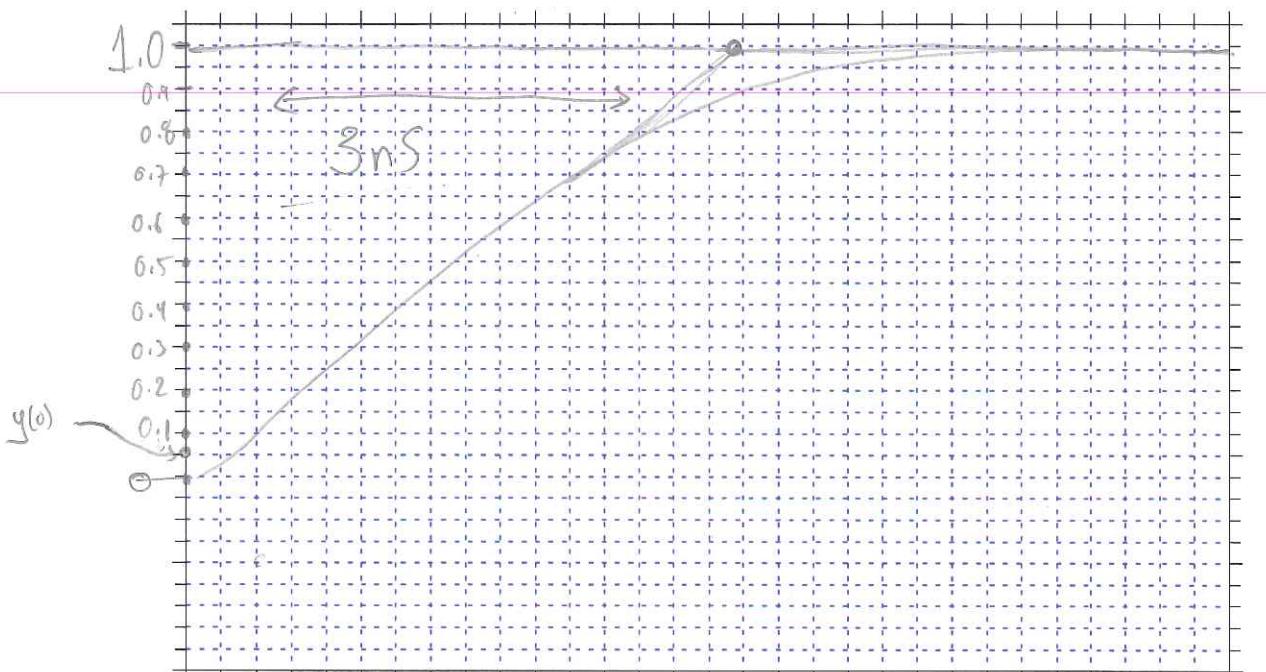Part d, 10 points

If $V_{in}(t)$ is a 100mV step-function, find and plot $V_{out}(t)$. Be sure to label and dimension the axes clearly, and to clearly label key features of the time waveform.



$$H(s) = (10) \frac{1 + s(200\mu s)}{1 + s(3\mu s)} \quad X(s) = (100mV) \left(\frac{1}{s}\right)$$

$$\begin{aligned} Y(s) &= H(s)X(s) = (10) \frac{1 + s(200\mu s)}{1 + s(3\mu s)} \left(\frac{1}{s}\right)(100mV) \\ &= (1) \left[\frac{1}{1 + s(3\mu s)} + \frac{s(200\mu s)}{1 + s(3\mu s)} \right] \left(\frac{1}{s}\right) \text{ volt} \end{aligned}$$

$$Y(s) = \left[\frac{1}{1 + s(3\mu s)} + \frac{\frac{(200\mu s)}{3\mu s}}{1 + s(3\mu s)} \right] \text{ volt}$$

$$y_u(t) = \left[\left(1 - e^{-\frac{t}{3\mu s}}\right) + \left(\frac{200\mu s}{3\mu s}\right) e^{-\frac{t}{3\mu s}} \right] \text{ volt}$$

$$y(t) = 1 \cdot \left[1 - 0.933 e^{-\frac{t}{3\mu s}} \right] \text{ volt}$$

$$y(0) = 0.0667 \text{ volt}$$

$$y(\infty) = 1 \text{ volt} \quad t = 3\mu s$$