

ECE137B Final Exam

There are 5 problems on this exam and you have 3 hours
 There are pages 1-19 in the exam: please make sure all are there.

Do not open this exam until told to do so

Show all work:

Credit will not be given for correct answers if supporting work is not shown.

Class Crib sheets and 2 pages (front and back → 4 surfaces) of your own notes permitted.

Don't panic.


Time function	LaPlace Transform
$\delta(t)$	1
$U(t)$	1/s
$e^{-\alpha} \cdot U(t)$	$\frac{1}{s + \alpha}$ or $\frac{1/\alpha}{1 + s/\alpha}$
$e^{-\alpha} \cos(\omega_d t) \cdot U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha} \sin(\omega_d t) \cdot U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Name: Solution "A"

Problem	points	possible	Problem	points	possible
1a		3	2		10
1b		2	3a		7
1c		8	3b		13
1d		5	4a		10
1e		12	4b		5
1f		5	5a		5
1g		5	5b		5
			5c		5

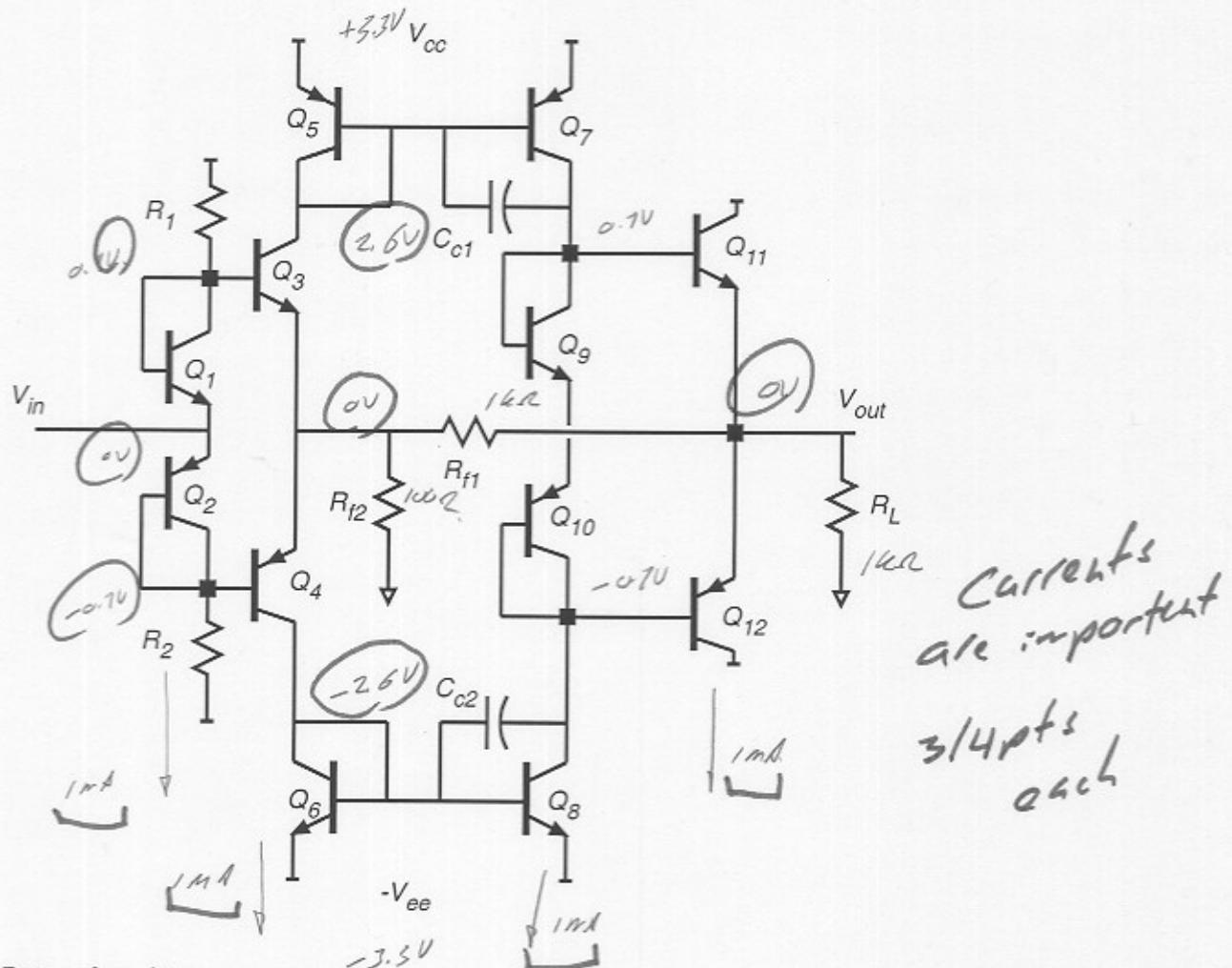Problem 1, 40 points

method of first-order and second-order time constants, some feedback theory



Part a, 3 points

DC analysis

Find all transistor DC emitter currents, find all node voltages. Make these on the circuit diagram.

$\beta : \text{infinity, for all transistors.}$	
$V_a=200 V$ for Q_7 and Q_8	$V_a=\text{infinity}$ for all other transistors
$C_{cb} = \text{zero, for all transistors.}$	$C_{c1} = C_{c2} = 10 \text{ fF}$
$\tau_f = 2 \text{ ps}$ and $C_{je} = 10 \text{ fF}$ for Q_7, Q_8, Q_{11}, Q_{12} .	
$\tau_f = 0 \text{ ps}$ and $C_{je} = 0 \text{ fF}$ for all other transistors	
All transistors have identical I_s , the DC component of V_{in} is zero volts	
The supplies are ± 3.3 Volts.	$R_f1=1 \text{ kOhm}, R_f2=100 \text{ Ohm}, R_L=1 \text{ kOhm}$
$R_1=R_2$: select their value so that the DC emitter currents in Q_1 and Q_2 are 1 mA	

$$R_1 = R_2 = \frac{3.3V - 0.7V}{1mA} = 2.6k\Omega$$

Part b, 2 points

small signal parameters

Find the following:

	$r_e = 1/g_m$	R_{be}	R_{ce}	C_{be}	C_{cb}	f_T
Q1	26 m	∞	∞	0	0	∞
Q3			∞	0		∞
Q5			∞	0		∞
Q7			200 k	87 fF		706 kHz
Q9			∞	0		∞
Q11			↓	87 fF		706 kHz.

$$C_{be} = g_e + g_m \tau_f = 10 fF + \frac{2 ps}{26 m} = 87 fF$$


$$f_T = \frac{g_m}{2\pi(C_{be} + C_L)} = 70 \text{ kHz}$$

Part c, 8 points
mid-band analysis


Find the low-frequency loop transmission:


$$T(f=0 \text{ Hz}) = \underline{85}$$

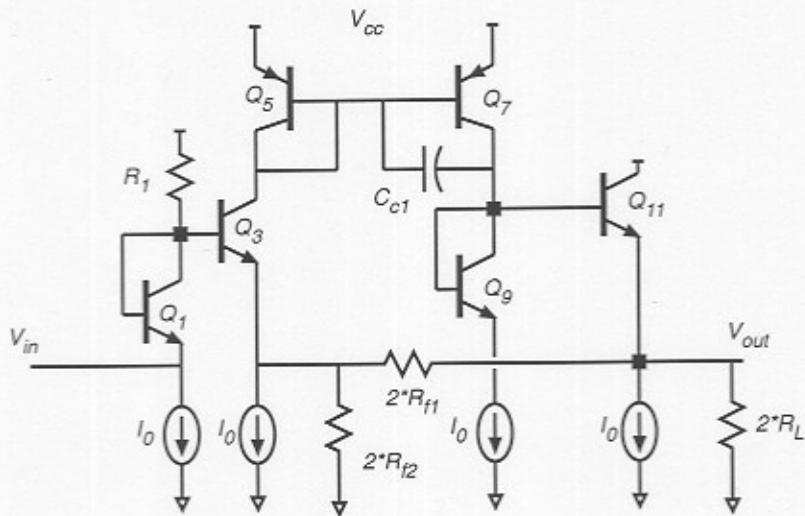To do this, you must make 2 changes to the circuit. First, the circuit is symmetric, and can be thus simplified, where I_o is the value of the DC current in R_1 .



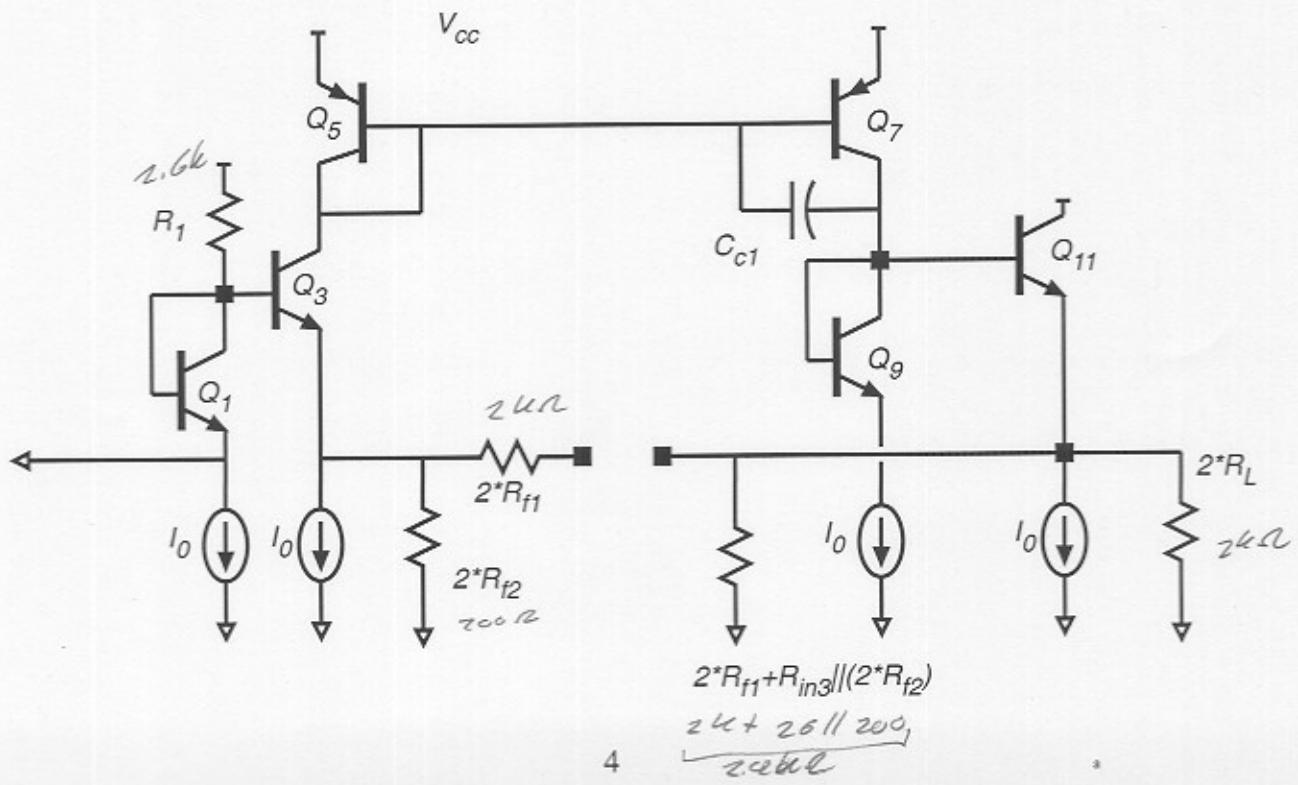Second, you need to cut the feedback loop, thus, to find the loop transmission



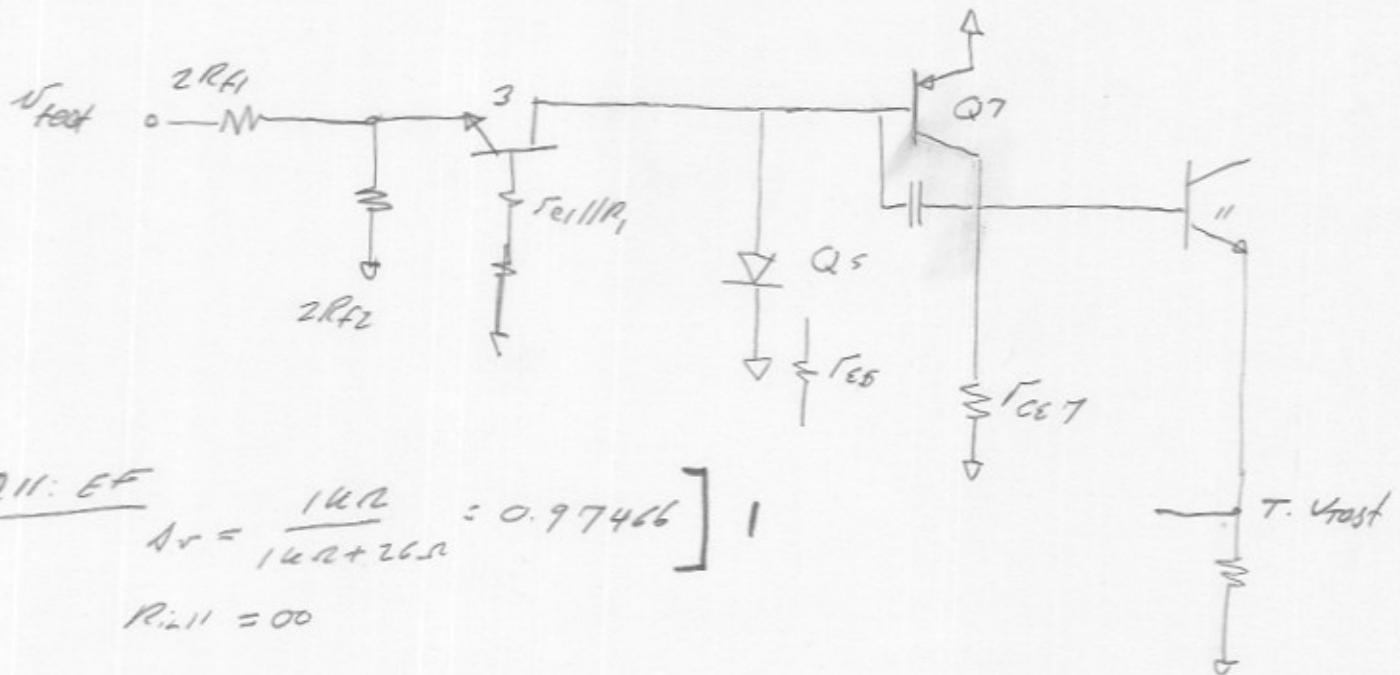

$$\underline{Q11: EF} \quad A_v = \frac{14\Omega}{14\Omega + 26\Omega} = 0.97466 \quad] 1$$

$$R_{L11} = 0\Omega$$

$$\underline{Q7: CE} \quad A_v = \frac{r_{e7}}{r_{e7}} = \frac{200\mu\Omega}{26\Omega} = 7,700 \quad] 2$$

$$2R_e \parallel (2R_{f1} + \underbrace{R_{L11} \parallel 2R_{f1}}_{14\Omega})$$

$$\underline{Q3 CS} \quad \frac{1}{2} \left[A_v = \frac{R_{L11}}{r_e} = \frac{r_{e5}}{r_{e7}} = 1 \right. , r_{L3} = 26\Omega$$

$$\underline{\text{feedback network}} \quad \text{two terms} = \frac{r_{L3} \parallel 2R_{f2}}{r_{L3} \parallel 2R_{f2} + 2R_{f1}} = \frac{26\Omega \parallel 200\Omega}{26\Omega \parallel 200\Omega + 26\Omega} \\ = \frac{23\Omega}{23\Omega + 26\Omega} = 0.0114 \quad] 2$$

loop transmission = product of these terms

$$= 0.0114 \cdot 1 \cdot 7,700 \cdot 0.97466 = \underline{85.36} \quad] 1$$

Part d, 5 points
feedback theory


At low frequencies, what is the closed-loop gain V_{out}/V_{in} ?

$$V_{out}/V_{in} = \underline{10.87}$$

2

$$A_{oc} = A_{\infty} \frac{T}{1+T}$$

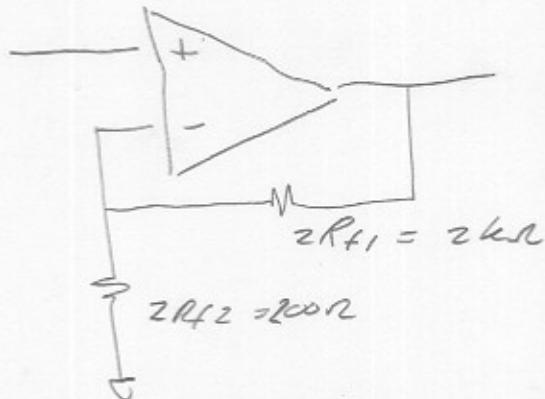\checkmark $T = 85.4$ at low frequencies.



If $T \rightarrow \infty$, $V^+ = V^- = V_L$
 but $V^- = \frac{2R_{f2}}{2R_{f2} + 2R_{f1}} \cdot V^+$
 so:
 $A_{oc} = \frac{R_{f1} + R_{f2}}{R_{f1}} = 11$] 2

$$A_{oc} = 11 \cdot \frac{85.4}{86.4} = 10.87]^1$$


Part e, 12 points

motc

Using MOTC, you will find the frequency, in Hz (not rad/sec), of the *two* major poles in the transfer function.

capacitor 1:	capacitor 2:	capacitor 3:
$R_{11}^0 = 400 \text{ k}\Omega$	$R_{22}^0 = 26 \text{ }\Omega$	$R_{33}^0 = 5093 \text{ }\Omega$
$R_{22}^1 = 13 \text{ }\Omega$	$R_{33}^1 = 26.6 \text{ }\Omega$ (26 is ok)	$R_{33}^2 = 5093 \text{ }\Omega$
$f_{p1} = 35.8 \text{ MHz}$	$f_{p2} = 47.1 \text{ GHz}$	

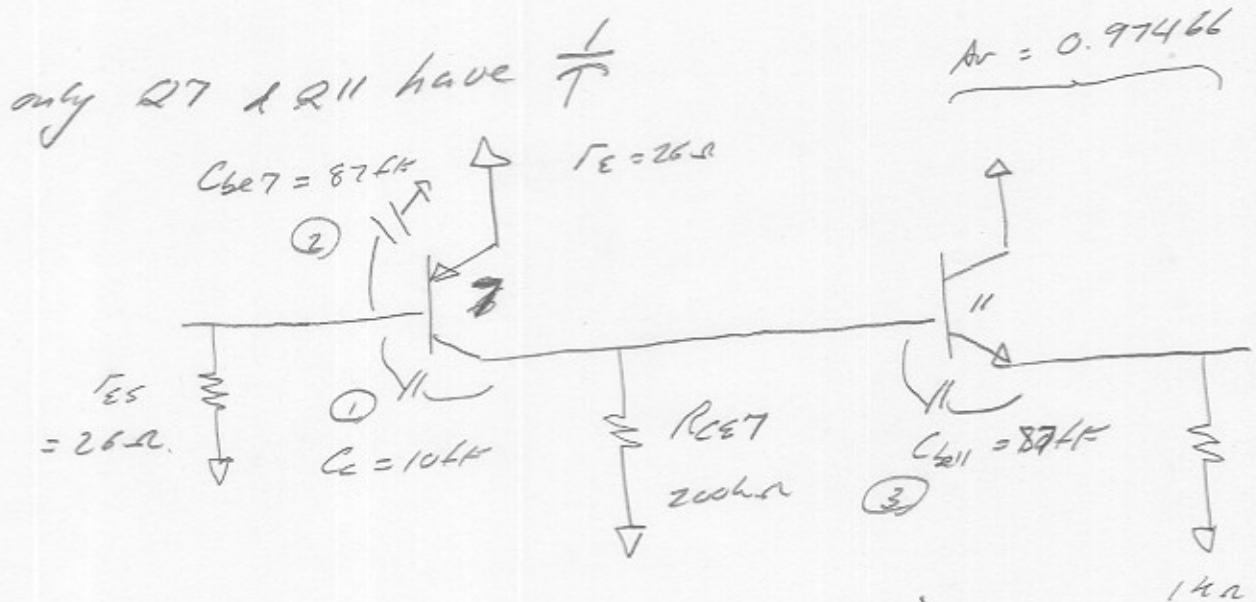capacitor 1 is the compensation capacitance
 capacitor 2 is the capacitance between base & emitter of transistor Q₇
 capacitor 3 is the capacitance between base & emitter of transistor Q₁₁



$$1 \left[\begin{aligned} r_{11}^0 &= 26 \Omega (1 - A_{v7}) + R_{CE7} = 26 \Omega (1 + 7700) + 200 \text{ k}\Omega \\ &= 400 \text{ k}\Omega \end{aligned} \right]$$

$$1 \left[\begin{aligned} r_{22}^0 &= 26 \text{ }\Omega \end{aligned} \right]$$

$$1 \left[\begin{aligned} r_{33}^0 &= 200 \text{ k}\Omega (1 - A_{v11}) + r_{CE11} 11 \text{ k}\Omega = 5068 \text{ }\Omega + 25.3 \text{ }\Omega = 5093 \text{ }\Omega \end{aligned} \right]$$

$$1 \left[\begin{aligned} a_1 &= r_{11}^0 C_1 + r_{22}^0 C_2 + r_{33}^0 C_3 = 400 \text{ k}\Omega (10 \text{ pF}) + 26 \text{ }\Omega (87 \text{ fF}) + 5.14 \text{ }\Omega (87 \text{ fF}) \\ &= 4 \text{ ns} + 2.26 \text{ ps} + 0.444 \text{ ns} = \underline{\underline{4.44 \text{ ns}}} \end{aligned} \right]$$

$$2 \left[\frac{R_{22}'}{1} \right]$$

$$R_{22}' = R_{E5} \parallel R_{E7} \parallel R_{CE7}$$

$$= 26\Omega \parallel 26\Omega \parallel 200\text{k}\Omega$$

$$\approx 13\Omega$$

$$2 \left[\frac{R_{33}'}{1} \right]$$

$$R_{33}' = (R_{E5} \parallel R_{E7} \parallel R_{CE7})(1 - A_{vH}) + R_{E4} \parallel 1\text{k}\Omega$$

$$= 26\Omega(1 - 0.97466) + 26\Omega$$

$$= 26.6\Omega.$$

$$2 \left[\frac{R_{33}^2}{1} \right]: \text{ by inspection, } R_{33}^2 = R_{33}'^2 = 5093\Omega$$

$$A_2 = R_{11}^0 C_1 C_2 R_{22}' + R_{11}^0 C_1 C_3 R_{33}' + R_{22}^0 C_2 C_3 R_{33}^2$$

$$= 400\text{k}\Omega (10\text{fF}) (87\text{fF}) (13\Omega) + 400\text{k}\Omega (10\text{fF}) (87\text{fF}) 26.6\Omega$$

$$+ 26\Omega (87\text{fF}) (87\text{fF}) 5093\Omega$$

$$= 4.52 \cdot 10^{-21} + 9.25 (10^{-21}) + 1.00 (10^{-21}) \text{ sec}^2$$

$$= 1.5 \cdot 10^{-20} \text{ sec}^2 = (0.122\text{ns})^2$$

$$1 \left[\frac{\text{use SPA}}{1} \right]$$

$$f_{p1} = \frac{0.159}{a_1} = 35.8\text{MHz}$$



$$f_{p2} = ? \quad \frac{0.159 a_1}{a_2} = 47.16\text{Hz}$$

SPA checks!

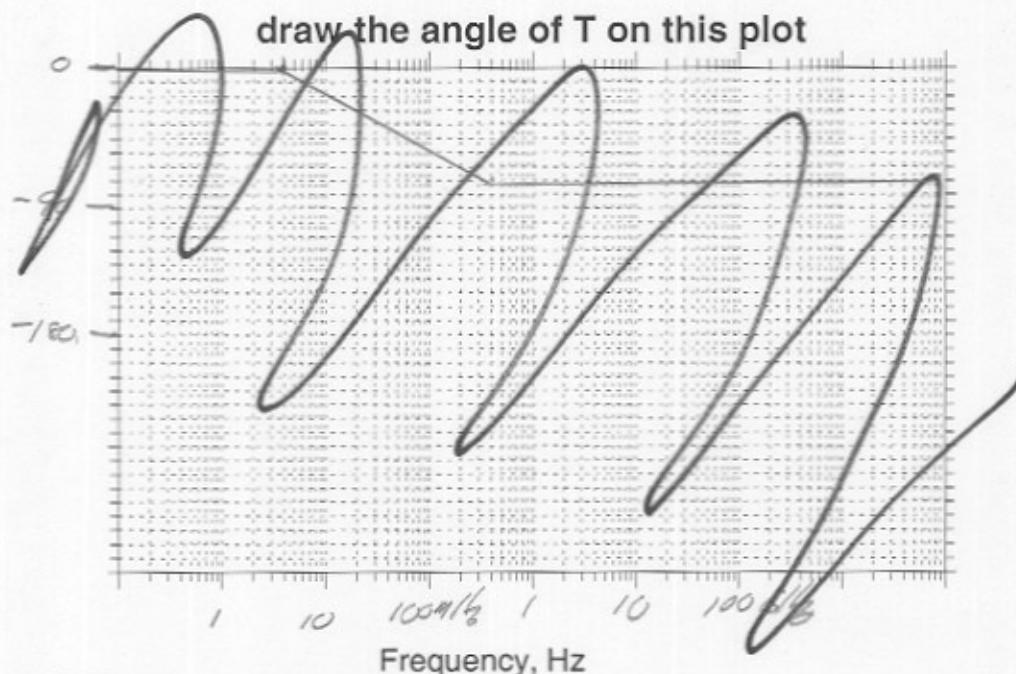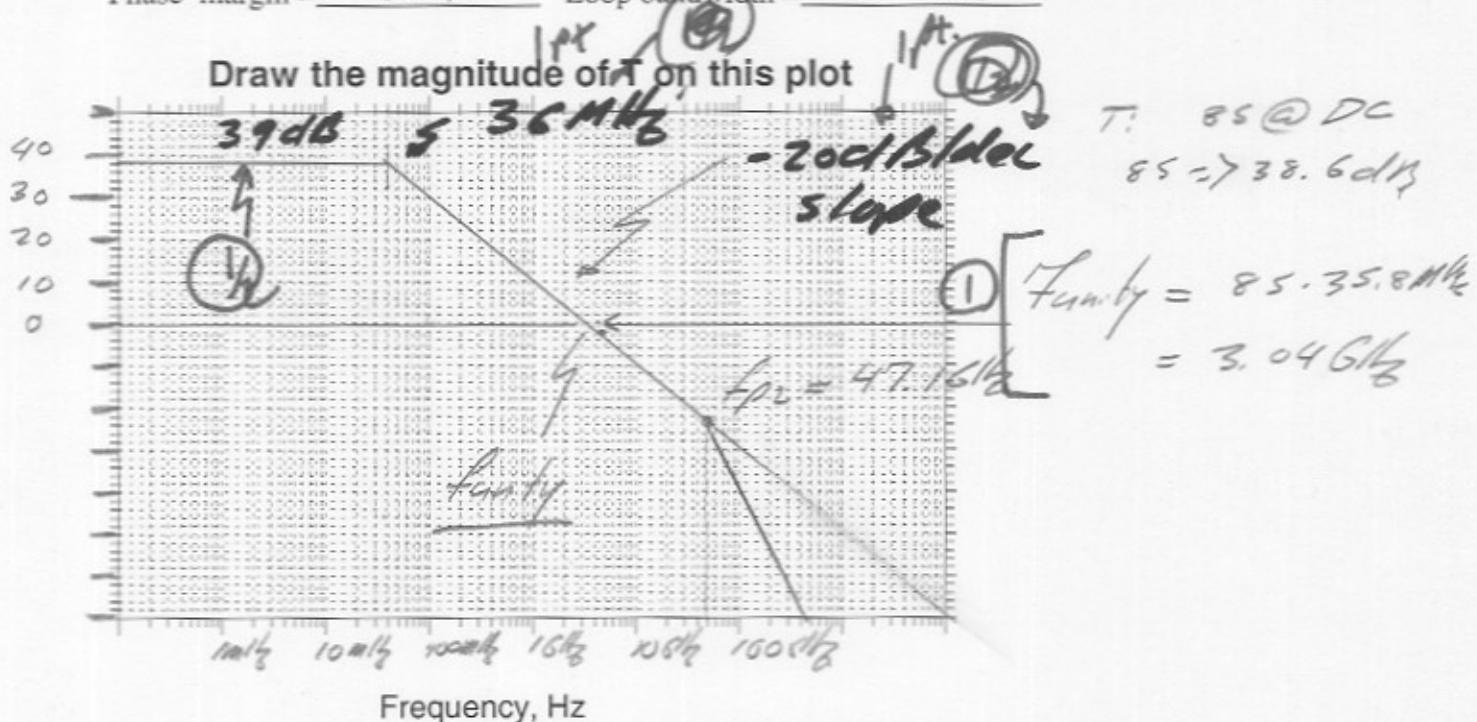Part f, 5 points

Make accurate asymptotic plots of T . Find the phase margin and the loop bandwidth.

Phase margin = 86.4° . Loop bandwidth = 3.04 GHz



$1/k$ [$\angle T @ 3.04 \text{ GHz} = -90^\circ (\text{pole}) - \arctan(3.04 \text{ GHz} / 47.16 \text{ Hz})$
 $= -90 - 3.64^\circ$


$1/k$ [Phase margin = $180 - (90 + 3.64) = 86.4^\circ$

Part g, 5 points


What is the gain and bandwidth of the closed-loop amplifier ?

low frequency Vout/Vgen= 10.87 bandwidth of Vout/Vgen= 3.046 Hz

draw closed loop gain on this bode plot

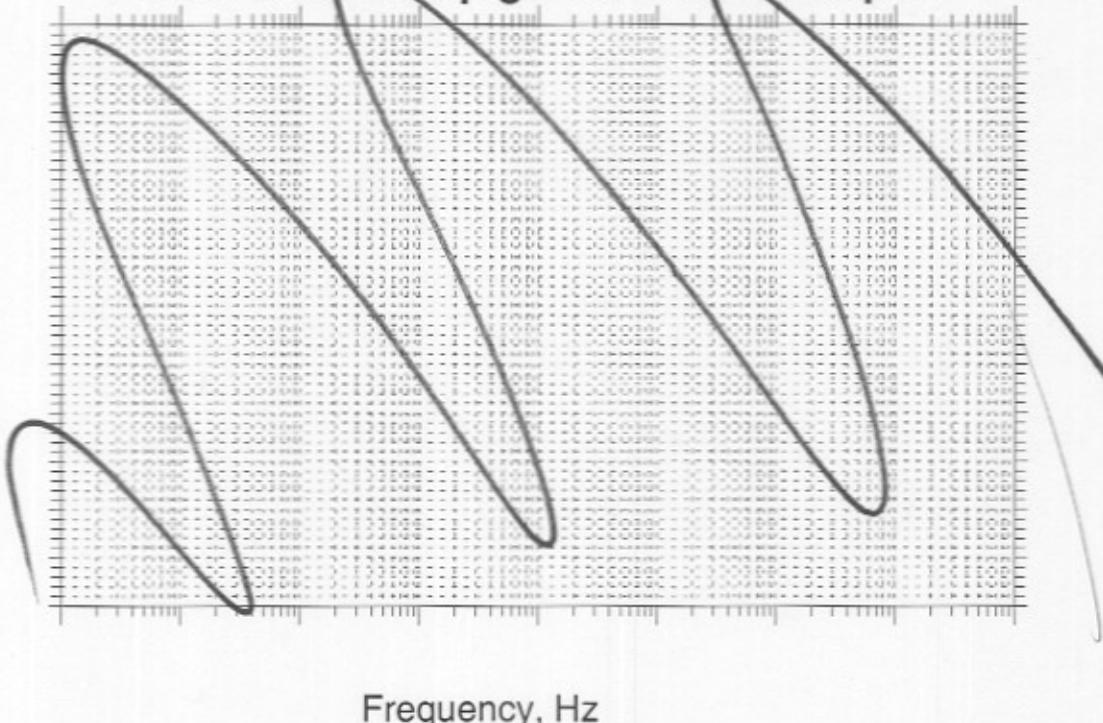

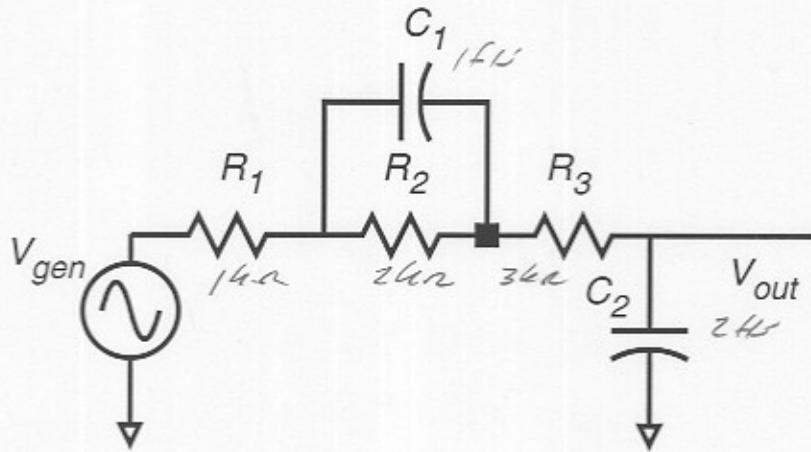Problem 2: 10 points
method of time constants analysis



R₁=1 KOhm, R₂=2kOhm, R₃=3kOhm C₁= 1 fF C₂=2 fF

Using MOTC, find the coefficients a₁ and a₂ of transfer function V_{out}(s)/V_{gen}(s), given a

$$\text{transfer function in the standard form } \frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}} \Big|_{DC} \frac{1+b_1 s + b_2 s^2 + \dots}{1+a_1 s + a_2 s^2 + \dots}$$

$$R_{11}^0 = \frac{1.33 \text{ k}\Omega}{\frac{V_{out}}{V_{gen}} \Big|_{DC} = 1.0}$$

$$R_{22}^0 = \frac{6 \text{ k}\Omega}{a_1 = 13.33 \mu\text{s}}$$

$$R_{22}^1 = \frac{4 \text{ k}\Omega}{a_2 = 1.06(10^{-23}) \text{ sec}^2}$$

$$2[R_{11}^0 = 2\text{k}\Omega \parallel (1\text{k}\Omega + 3\text{k}\Omega) = 2\text{k}\Omega \parallel 4\text{k}\Omega = 1.33 \text{ k}\Omega]$$

$$2[R_{22}^0 = 1\text{k}\Omega + 2\text{k}\Omega + 3\text{k}\Omega = 6\text{k}\Omega]$$


$$2[R_{22}^1 = 1\text{k}\Omega + 3\text{k}\Omega = 4\text{k}\Omega]$$

$$2[a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 = 1.33 \text{ k}\Omega \cdot 1 \text{ fF} + 6 \text{ k}\Omega \cdot 2 \text{ fF} = 13.33 \mu\text{s}]$$

$$2[a_2 = R_{11}^0 C_1 R_{22}^1 = (1.33 \text{ k}\Omega \cdot 1 \text{ fF}) (2 \text{ fF}) (4 \text{ k}\Omega) = 1.06(10^{-23}) \text{ sec}^2 = (3.26 \mu\text{s})^2]$$

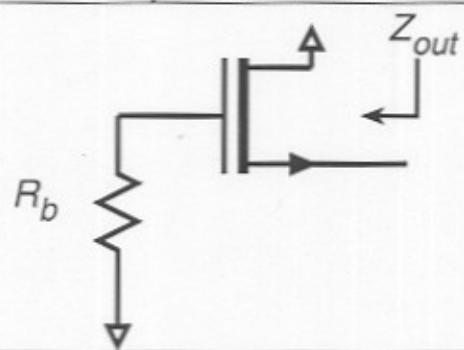Problem 3: 20 points

Nodal analysis and transistor circuit models




Ignore DC bias; you don't need it.

$C_{gs} = 10 \text{ fF}$ $C_{gd} = 0$. $R_{ds} = \text{infinity}$.

$g_m = 10 \text{ mS}$, $R_b = 10 \text{ kOhm}$

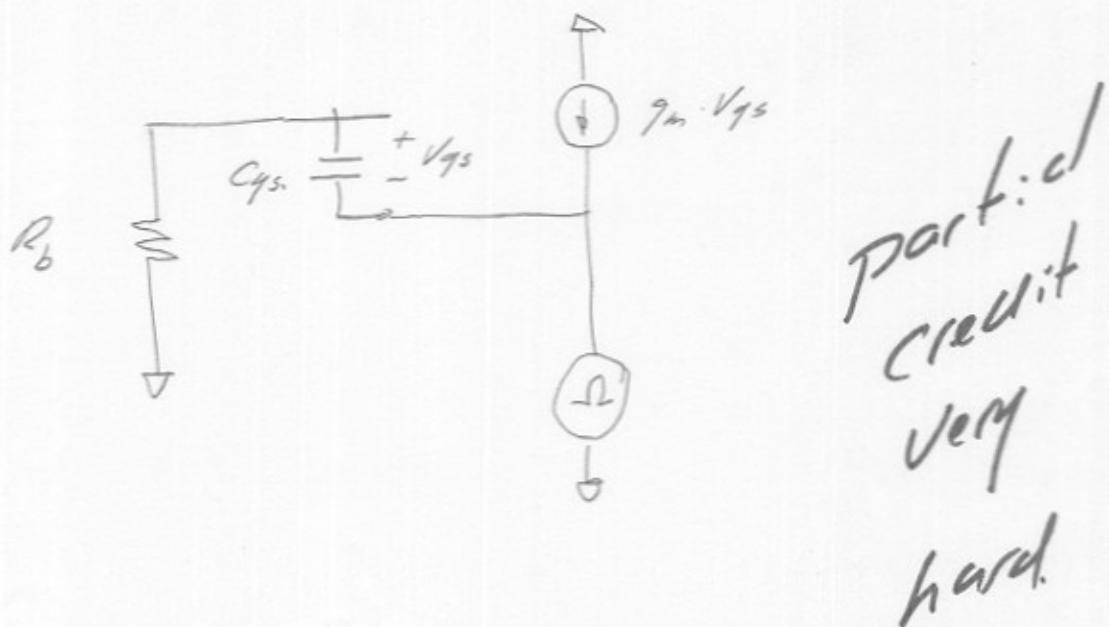Part a. 7 points

Draw an accurate small-signal equivalent circuit model of the circuit above. Represent the Z_{out} measurement by connecting an Ohm meter. Do not show components whose element values are zero or infinity (!).




Part b, 13 points

Using NODAL ANALYSIS, find the frequency-dependent output impedance $Z_{out}(s)$

The answer must be in standard form $Z_{out}(s) = Z_1 * s^n * \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$,

where n might be 0, 1, or 2, or -1 or -2.
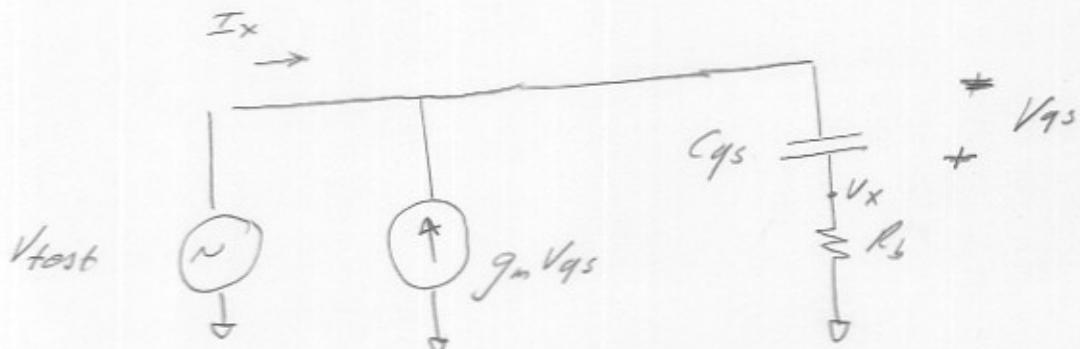
$$Z_{out}(s) = \underline{\hspace{10cm}}$$



$$\text{by inspection: } V_x = V_{test} \cdot \frac{1}{1 + jT} \\ \text{where } T = C_{gs} \cdot R_s \\ \Rightarrow V_{gs} = -V_{test} / (1 + jT)$$

$$\text{so } I_x / V_{test} = \frac{1}{R + j1\omega c} + \frac{jm}{1 + jT}$$


$$= \frac{jc}{1 + jT} + \frac{jm}{1 + jT} = \frac{jm + jc}{1 + jT R_b C_{gs}}$$

$$Z_{out} = \frac{1 + jT R_b C_{gs}}{jm + jc} = \frac{1}{jm} \frac{1 + jT R_b C_{gs}}{1 + jc/m}$$

if by N.A.: 6 pts for $\sum I = 0$ eqn
7 pts for answer.

Problem 4, 15 points
negative feedback

part a, 10 points

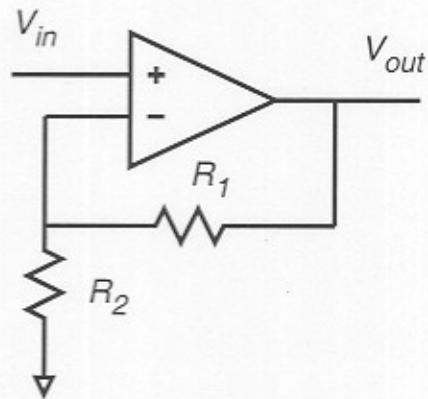

The amplifier has a differential gain of 10^5 .
 R₁=99 kOhm, R₂=1 kOhm. The op-amp has infinite differential input impedance and zero differential output impedance.


The differential amplifier has 1 pole in its open-loop transfer function at 1 kHz, and one pole at 2 MHz.

Using the Bode plot on the next page, plot the open-loop gain (A_d or A_{ol}), the inverse of the feedback factor ($1/\beta$), closed loop gain (A_{CL}). *Label all axes, slopes, pole/zero frequencies, etc.* Determine the following:

Loop bandwidth= 11116 phase margin= 64°
 V_{out}/V_{gen} at DC= 100

1p.l.
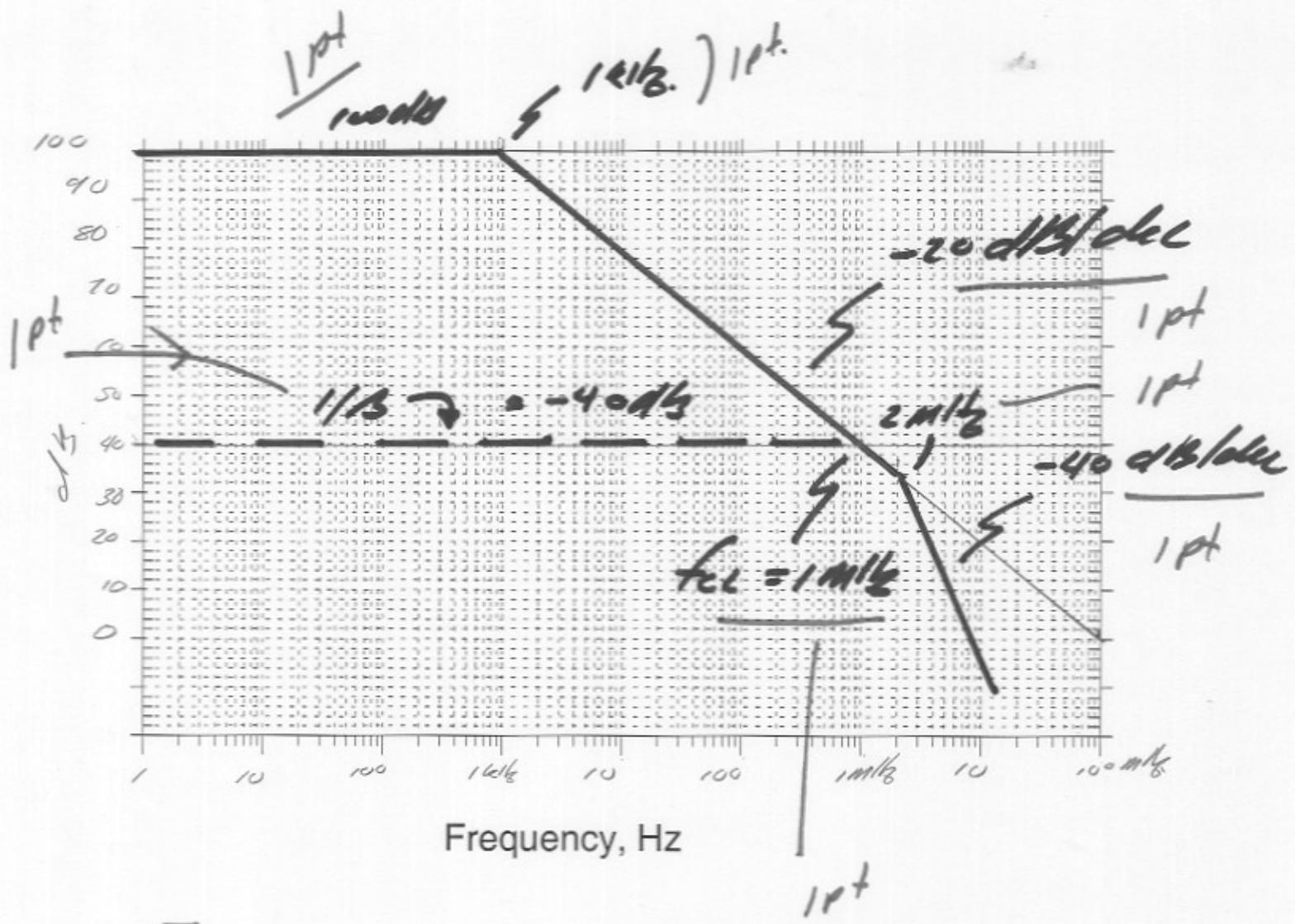
$$\beta = \frac{1}{1+99} = \frac{1}{100} \Rightarrow -40\text{dB}$$



$$10^{\text{pt}} \left[f_{\text{unif}} = 1 \text{ mHz} \right]$$

$$\begin{aligned} \angle \Theta @ 1 \text{ mHz} &= -90^\circ - \arctan(1 \text{ mHz}/2 \text{ mHz}) \\ &= -90 - 26.6^\circ \end{aligned}$$

$$10^{\text{pt}} \left[\rho_m = 180 - 90 - 26.6 = 63.4^\circ \right]$$

part b, 5 points


What is the gain and bandwidth of the closed-loop amplifier?

low frequency $V_{out}/V_{gen} = \underline{100}$

bandwidth of $V_{out}/V_{gen} = \underline{1\text{MHz}}$

Draw a plot of the closed loop gain, labeling all axes, slopes, pole/zero frequencies, etc.

draw closed loop gain on this bode plot

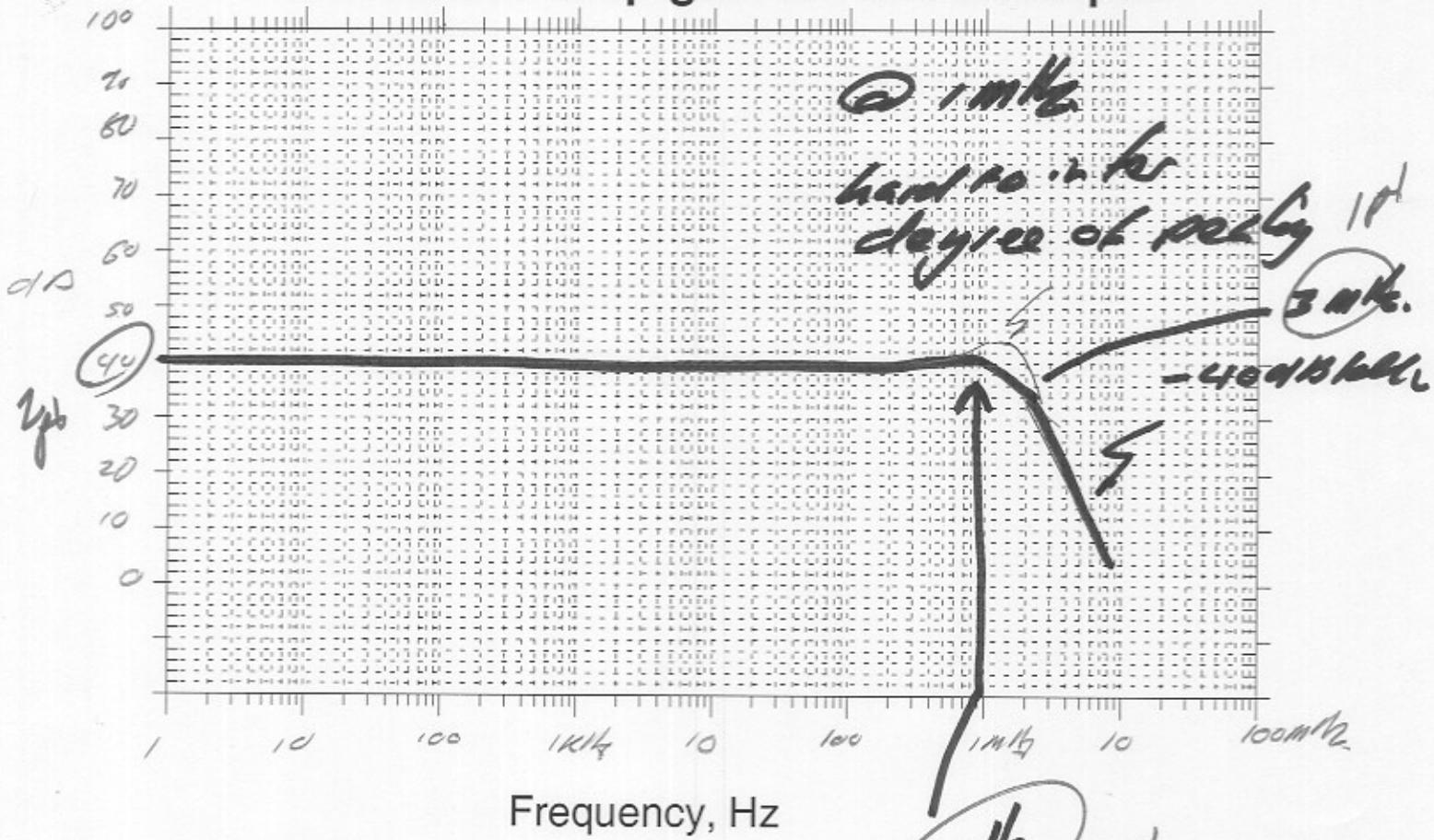


$$A_{cl} = \begin{cases} 1/\beta & T \gg 1 \\ \frac{1/\beta}{1 + e^{j\omega T}} & \text{when } T=1 \end{cases} \Rightarrow \text{constant at low freq.}$$

$\Rightarrow -40\text{dB/dec} @ \text{high freq.}$

Problem 5: 15 points
transfer functions

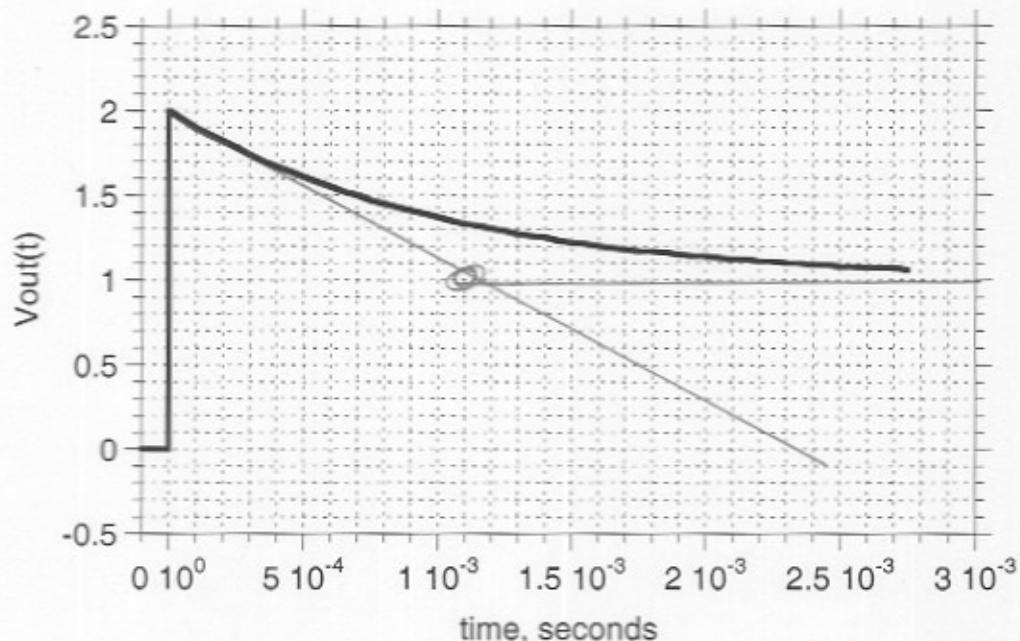Part a, 5 points

A transistor circuit has a step response (input is a 1-V step function) as shown.



3 [function is $a(t) + a(t) e^{-t/1ms}$

identify all pole and zero frequencies in the transfer function

pole frequencies: 159, X, X Hz

zero frequencies: 80, X, X Hz

Part b. 5 points

Give the transfer function

$$V_{out}(s)/V_{gen}(s). \text{ Give the answer in standard form } \frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}} \Big|_{DC} \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$$

$$V_{out}(s)/V_{gen}(s) = \underline{\hspace{10cm}}$$

$$\begin{aligned} 2 \quad & V_o(s) = IV/s + \frac{IV \cdot T}{1+AT} \\ 1 \quad & V_i(s) = IV/s \\ H(s) &= \frac{IV + \frac{T}{1+AT}}{IV} = 1 + \frac{AT}{1+AT} = \frac{1+AT + AT}{1+AT} \\ &= \frac{1+AT \cdot 2}{1+AT} = \left[\frac{1+AT \cdot 2T}{1+AT} \right] = H(s) \\ & \text{where } T = 10^{-3} \text{ sec} = 1 \text{ ms.} \end{aligned}$$

4) pole @ $f_{p1} = \frac{0.159}{1 \text{ ms}} = 159 \text{ Hz.}$




4) zero @ $f_{z1} = \frac{0.159}{2 \text{ ms}} = 79.5 \text{ Hz.}$

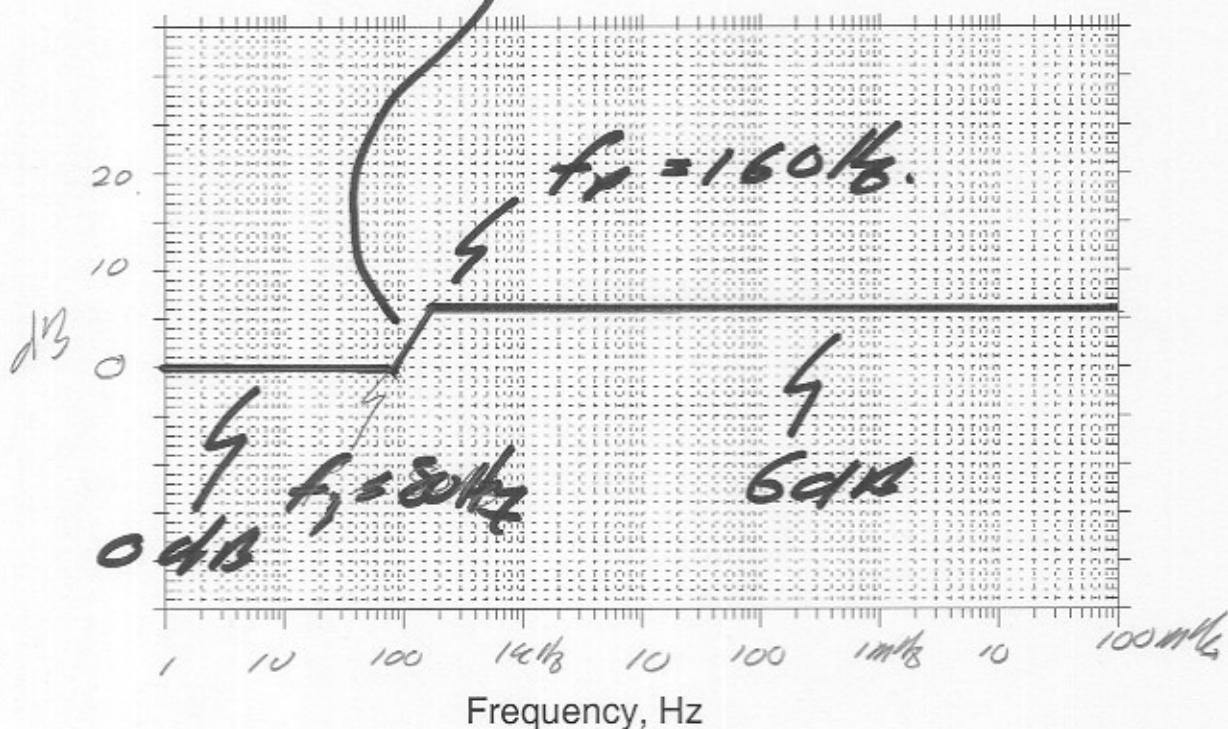Part c. 5 points

+20dB/Dec.

Draw an accurate Bode plot of the transfer function



(f_p, f_z) 1pt each factor