

## ECE137B Final Exam

There are 5 problems on this exam and you have 3 hours  
 There are pages 1-19 in the exam: please make sure all are there.

Do not open this exam until told to do so

Show all work:

Credit will not be given for correct answers if supporting work is not shown.

Class Crib sheets and 2 pages (front and back → 4 surfaces) of your own notes permitted.

Don't panic.


Time function	LaPlace Transform
$\delta(t)$	1
$U(t)$	$1/s$
$e^{-\alpha} \cdot U(t)$	$\frac{1}{s+\alpha}$ or $\frac{1/\alpha}{1+s/\alpha}$
$e^{-\alpha} \cos(\omega_d t) \cdot U(t)$	$\frac{s+\alpha}{(s+\alpha)^2 + \omega_d^2}$
$e^{-\alpha} \sin(\omega_d t) \cdot U(t)$	$\frac{\omega_d}{(s+\alpha)^2 + \omega_d^2}$

Name: "Solution A"

Problem	points	possible	Problem	points	possible
1a		4	3a		10
1b		5	3b		20
1c		4	4		20
1d		12	5a		7
2		10	5b		8

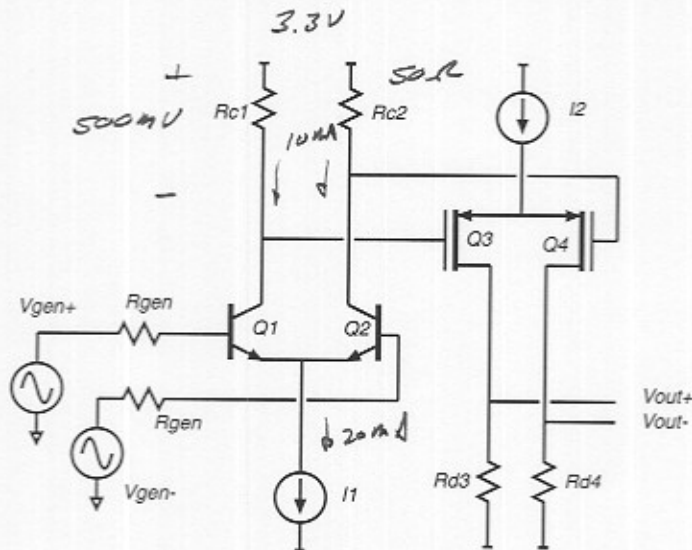**Problem 1, 25 points**

method of first-order and second-order time constants



Q1 and Q2 have  $\beta = \text{infinity}$ ,  
 $V_a = \text{infinity}$ ,  $\tau_f = 1 \text{ ps}$ ,  $C_{je} = 1 \text{ fF}$ ,  
 $C_{cb} = 1 \text{ fF}$ .

Q3 and Q4 have  $v_{sat} C_{ox} W_g = 100 \text{ mS}$ ,  
 $|V_t| = 0.25 \text{ volts}$ ,  $\lambda = 0 \text{ V}^{-1}$ ,  
 $C_{gs} = 160 \text{ fF}$ ,  $C_{gd} = 0 \text{ fF}$

The supplies are  $\pm 3.3 \text{ Volts}$ .  
 $R_{gen} = 25 \text{ Ohms}$

The input is fully differential, with  
 $V_{gen+} = -1 * V_{gen-}$

Part a, 4 points

The DC voltage drops across Rc1 and Rc2 are both 500 mV.

Rc1, Rc2, are both 50 Ohms.

Rd3 and Rd4 are both 100 Ohms.

The DC voltage drops across Rd3 and Rd4 are both 1 V.


Find I1 and I2

$I_1 = 20 \mu A$        $I_2 = 20 \mu A$   
 $R_{d1} = \underline{\hspace{2cm}}$        $R_{d3} = \underline{\hspace{2cm}}$

$I_1 = 2 \cdot 500 \text{ mV} / 50 \Omega = 20 \mu A$

$I_2 = 2 \cdot 1 \text{ V} / 100 \Omega = 20 \mu A$

Part b, 5 points

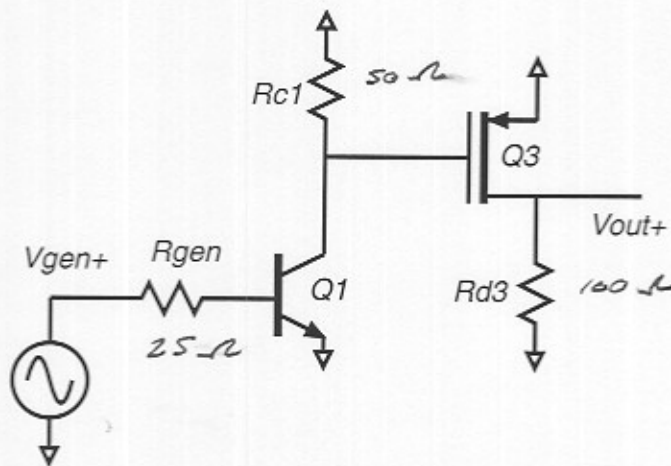

Because the input is fully differential, with  $V_{gen+} = -1 * V_{gen-}$ , the circuit can be analyzed using a half-circuit equivalent.

Find the following quantities at mid-band  
 $V_{out}/V_{gen+} = \underline{-192.3}$

small-signal voltage gain of Q3 =  $\underline{-10}$

small-signal voltage gain of Q1 =  $\underline{-19.23}$

$$I_{c1} = 10 \text{ mA} \rightarrow g_{m1} = I_{c1}/V_{T1} = 1/2.6 \Omega$$

$$Q3, \text{ CS: } A_v = -g_m R_{eq} = -100 \text{ MS} \cdot 100 \Omega = -10$$

$$Q1, \text{ CE: } A_v = -g_m R_{eq} = -50 \Omega / 2.6 \Omega = -19.23$$

$$v_i / v_{gen+} = 1 \text{ because } R_{in} = \infty$$

$$v_o / v_{gen+} = -192.3$$

Part c, 4 points

Find the following:

$$Q1: f_r = \underline{158 \text{ GHz}} \quad Q3: f_r = \underline{99.4 \text{ GHz}}$$

$$C_{be1} = \underline{386 \text{ fF}}$$

$$\begin{aligned} Q1: C_{be} &= C_{je} + g_m \tau_f \\ &= 1 \text{ fF} + 1 \text{ pS} / 2.6 \text{ ns} \\ &= 386 \text{ fF} \end{aligned}$$


$$\begin{aligned} f_T &= (1/2\pi) g_m (C_{cb} + C_{cbd})^{-1} \\ &= 158 \text{ GHz} \end{aligned}$$

$$\begin{aligned} Q3 \quad f_T &= \frac{g_m}{2\pi (C_{gs} + C_{gd})} \\ &= \frac{100 \text{ mS}}{2\pi (160 \text{ fF})} \\ &= 99.4 \text{ GHz} \end{aligned}$$

Part d, 12 points

Using MOTC, you will find the frequency, in Hz (not rad/sec), of the *two* major poles in the transfer function.

capacitor 1:	capacitor 2:	capacitor 3:
$R_{11}^0 = 25 \Omega$	$R_{22}^0 = 556 \Omega$	$R_{33}^0 = 50 \Omega$
$R_{22}^1 = 50 \Omega$	$R_{33}^1 = 50 \Omega$	$R_{33}^2 = 2.25 \Omega$
$f_{p1} = 14.6168$	$f_{p2} = 23.2 \text{ GHz}$	
capacitor 1 is the capacitance between	<u>base &amp; emitter</u>	of transistor <u>Q1</u>
capacitor 2 is the capacitance between	<u>base &amp; emitter</u>	of transistor <u>Q1</u>
capacitor 3 is the capacitance between	<u>gate &amp; source</u>	of transistor <u>Q3</u>

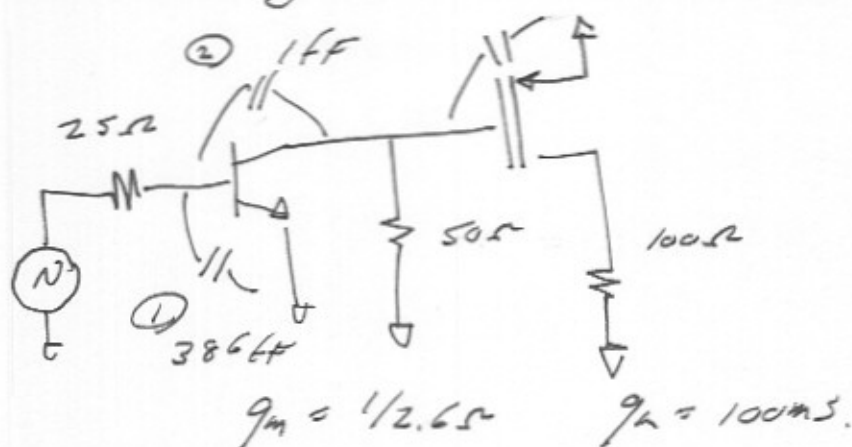

$$R_{11}^0 = 25 \Omega \quad R_{11}^0 C_1 = 25 \Omega \cdot 386 \text{ fF} = 9.65 \text{ ps}$$

$$R_{22}^0 = 25 \Omega (1 + 50 \Omega / 2.6 \Omega) + 50 \Omega = 556 \Omega$$

$$R_{22}^0 C_2 = 556 \Omega \cdot 1 \text{ fF} = 556 \text{ fs}$$

$$R_{33}^0 = 50 \Omega$$

$$R_{33}^0 C_3 = 50 \Omega \cdot 160 \text{ fF} = 8 \text{ ps}$$

$$R_{22}^1 = 50 \Omega (1 + 50 \Omega / 2.6 \Omega) + 50 \Omega = 50 \Omega$$

$$R_{11}^0 R_{22}^1 C_1 C_2 = 25 \Omega \cdot 50 \Omega \cdot 386 \text{ fF} \cdot 1 \text{ fF} = 4.825 (10^{-25}) \text{ sec}^2$$

$$R_{33}^1 = R_{33}^0 = 50 \Omega$$

$$R_{11}^0 C_1 C_2 R_{33}^1 = 7.72 (10^{-23}) \text{ sec}^2$$

$$R_{33}^2 = 50 \Omega // 25 \Omega // 1/9 \mu\text{A} = 2.25 \Omega$$

$$R_{22}^0 C_2 C_3 R_{33}^2 = 2.00 \cdot 10^{-29} \text{ sec}^2$$

$$a_1 = 18.21 \text{ ps}$$

$$a_2 = 7.79 (10^{-23}) / \text{sec}^2 = (8.83 \text{ ps})^2$$

SFA does not work because  $\sqrt{a_2} \approx a_1$

$$1 + a_1 s_p + a_2 s_p^2 = 0$$

$$s_p = \frac{-a_1 \pm \sqrt{a_1^2 - 4 \cdot 1 \cdot a_2}}{2 a_2}$$


$$= -1.457 (10^{11}) / \text{sec}^{-1} \text{ and}$$

$$-8.83 (10^{10}) / \text{sec}^{-1}$$

$$f_p = \frac{\omega_p}{2\pi} = 23.2 \text{ GHz}, 14.0 \text{ GHz}$$

**Problem 2: 10 points**

method of time constants analysis

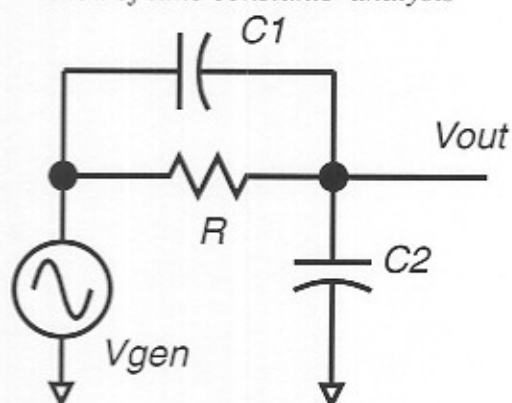

$R=1\text{ k}\Omega$   $C_1=1\text{ fF}$   $C_2=0.5\text{ fF}$

Using MOTC, find the transfer function  $V_{out}(s)/V_{gen}(s)$ . Give the answer in standard form

$$\frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}|_{DC}} \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$$

HINT:  $b_1 = R C_1$  and  $0 = b_2 = b_3 = \dots$

$$R_{11}^0 = \underline{1\text{ k}\Omega}$$

$$R_{22}^0 = \underline{1\text{ k}\Omega}$$

$$R_{22}^1 = \underline{0\ \Omega}$$

$$\frac{V_{out}}{V_{gen}|_{DC}} = \underline{1}$$

$$a_1 = \underline{1.5\ \mu\text{s}}$$

$$a_2 = \underline{0}$$

$$R_{11}^0 = R_{22}^0 = 1\text{ k}\Omega$$


$$R_{22}^1 = 0\ \Omega$$

$$a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 = 1.5\ \mu\text{s}$$

$$a_2 = R_{11}^0 C_1 C_2 R_{22}^1 = 0,$$

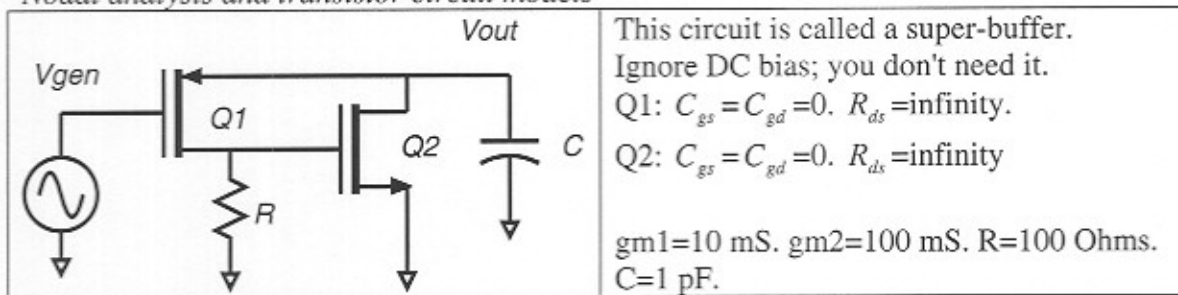**Problem 3 30 points**


*Nodal analysis and transistor circuit models*



This circuit is called a super-buffer.  
 Ignore DC bias; you don't need it.  
 Q1:  $C_{gs} = C_{gd} = 0$ .  $R_{ds} = \text{infinity}$ .  
 Q2:  $C_{gs} = C_{gd} = 0$ .  $R_{ds} = \text{infinity}$   
 $g_{m1} = 10 \text{ mS}$ .  $g_{m2} = 100 \text{ mS}$ .  $R = 100 \text{ Ohms}$ .  
 $C = 1 \text{ pF}$ .

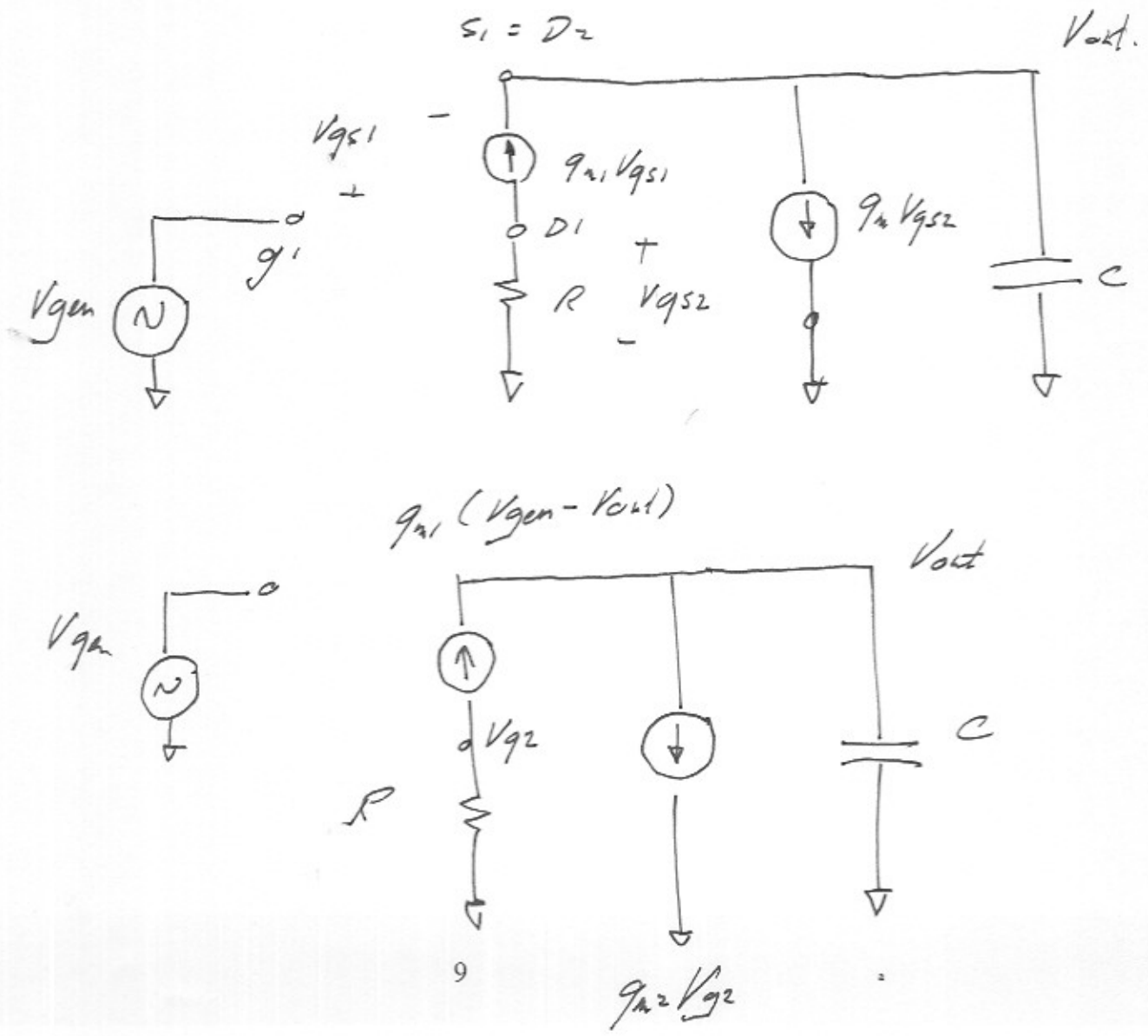Part a, 10 points

Draw an accurate small-signal equivalent circuit model of the circuit above. Do not show components whose element values are zero or infinity (!).





Part b. 20 points

Using NODAL ANALYSIS, find the transfer function  $V_{out}(s)/V_{gen}(s)$ .

The answer must be in standard form  $\frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}|_{DC}}{V_{gen}|_{DC}} \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$

$$\frac{V_{out}}{V_{gen}|_{DC}} = \frac{1}{0}, a_1 = 9.1ps, a_2 = 0$$

$$b_1 = 0, b_2 = 0$$

(note that  $a_3, a_4, \dots, b_3, b_4, \dots$  are all zero)

$$\underline{\Sigma I = 0 @ V_{g2}}$$

$$g_{m1} (V_{gen} - V_{out}) + V_{g2} / R = 0$$

$$\Rightarrow V_{out} (-g_{m1}) + V_{g2} (1/R) = V_{gen} (-g_{m1})$$

$$\underline{\Sigma I = 0 @ V_{out}}$$

$$V_{out} AC + g_{m2} V_{g2} + g_{m1} (V_{out} - V_{gen}) = 0$$

$$\Rightarrow V_{out} (AC + g_{m1}) + V_{g2} (g_{m2}) = g_{m1} V_{gen}$$

$$\begin{bmatrix} -g_{m1} & -1/R \\ sC + g_{m1} & g_{m2} \end{bmatrix} \begin{bmatrix} V_{out} \\ V_{g2} \end{bmatrix} = \begin{bmatrix} -g_{m1} \\ g_{m1} \end{bmatrix} V_{gen}$$

$V_{out}/V_{gen} = N/D$  where

$$N = \begin{vmatrix} -g_{m1} & 1/R \\ g_{m1} & g_{m2} \end{vmatrix} = -g_{m1}(g_{m2} + 1/R)$$

$$D = \begin{vmatrix} -g_{m1} & 1/R \\ sC + g_{m1} & g_{m2} \end{vmatrix} = -g_{m1}(g_{m2} + 1/R) - sC/R$$


$$\frac{V_{out}}{V_{gen}} = \frac{N}{D} = \frac{1}{1 + sC/R}$$

$$\text{where } a_1 = \frac{C}{g_{m1}(1 + g_{m2}R)} = \frac{1 \text{ pF}}{10 \text{ mS}(1 + 100 \mu\text{S} \cdot 100 \Omega)}$$

$$= 9.1 \text{ pS}$$

**Problem 4, 20 points**

negative feedback

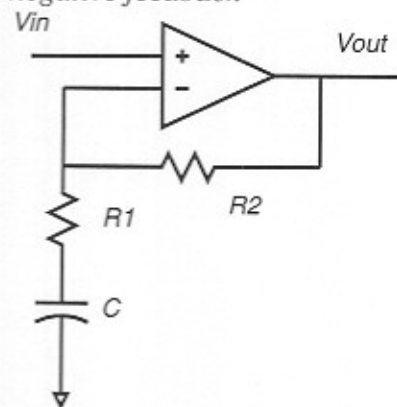

The amplifier has a differential gain of  $10^6$ .  $R_1=1\text{ k}\Omega$ ,  $R_2=9\text{ k}\Omega$ . The op-amp has infinite differential input impedance and zero differential output impedance.

The differential amplifier has 1 pole in its open-loop transfer function at 10 Hz, and one pole at 10 MHz.

$C=1\text{ nF}$

Using the Bode plot on the next page, plot the open-loop gain ( $A_d$  or  $A_{ol}$ ), the inverse of the feedback factor ( $1/\beta$ ), closed loop gain ( $A_{CL}$ ), and determine the following:

Loop bandwidth = 1 Mhz      phase margin = 76.2°  
 $V_{out}/V_{gen}$  at DC = 1

$$\beta = \frac{R_1 + 1/sC}{R_1 + R_2 + 1/sC} = \frac{1 + sCR_1}{1 + sC(R_1 + R_2)} = \frac{1 + jf/f_{z\beta}}{1 + jf/f_{p\beta}}$$

$$f_{z\beta} = 1/2\pi R_1 C = 159\text{ kHz}$$


$$f_{p\beta} = 1/2\pi (R_1 + R_2) C = 15.9\text{ kHz}$$

phase margin:


$$= 180^\circ - \arctan(1\text{ Mhz}/10\text{ kHz}) - \arctan(1\text{ Mhz}/15.9\text{ kHz}) + \arctan(1\text{ Mhz}/159\text{ kHz}) - \arctan(1\text{ Mhz}/10\text{ Mhz})$$

$\approx 76.2^\circ$

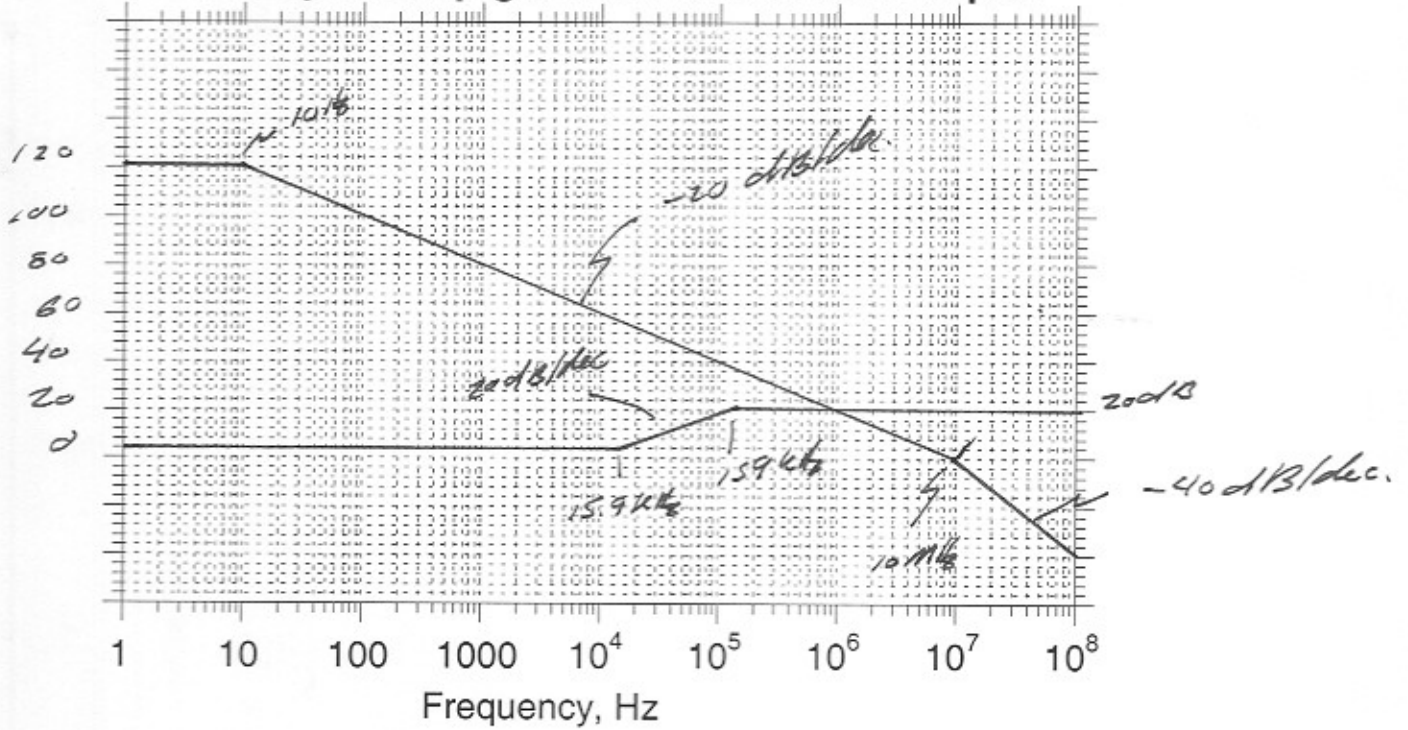Draw open loop gain and 1/beta on this plot




draw closed loop gain on this bode plot

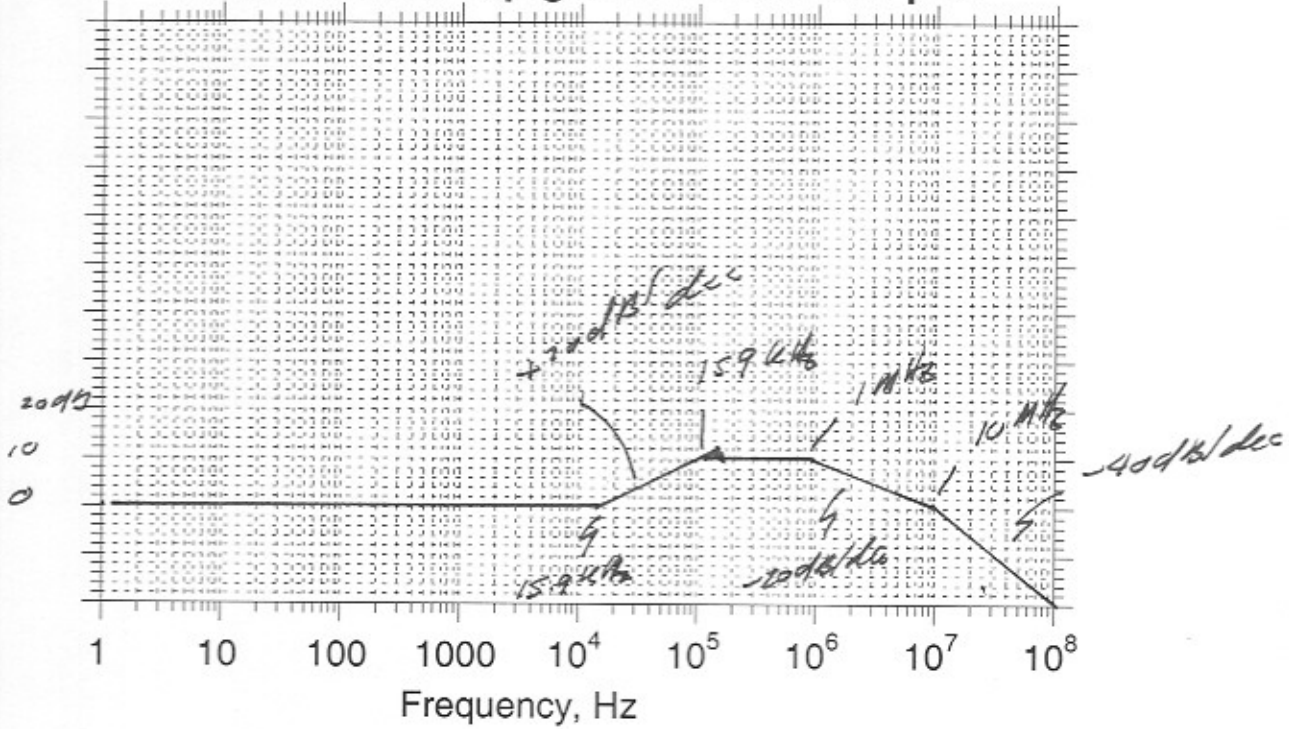

**Problem 5: 15 points**  
*transfer functions*

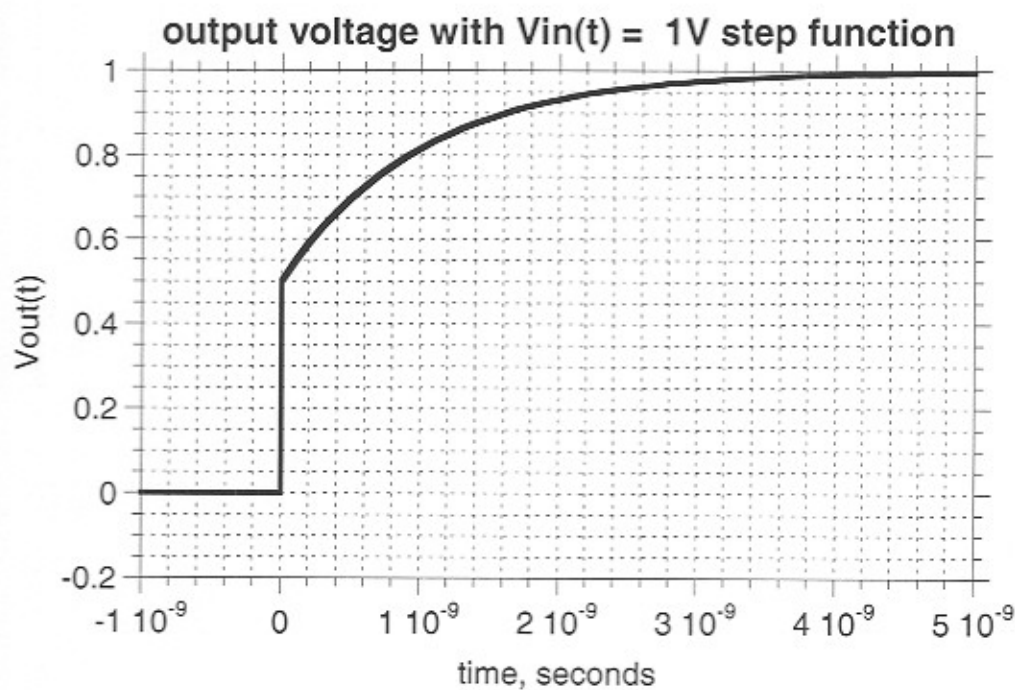Part a, 7 points


A transistor circuit has a step response (input is a 1-V step function) as shown.



identify all pole and zero frequencies in the transfer function


Draw a Bode Plot (Straight-line asymptotes) of the circuit transfer function  $V_{out}/V_{gen}$ , labeling all pole and zero frequencies and labeling the slopes of all asymptotes.
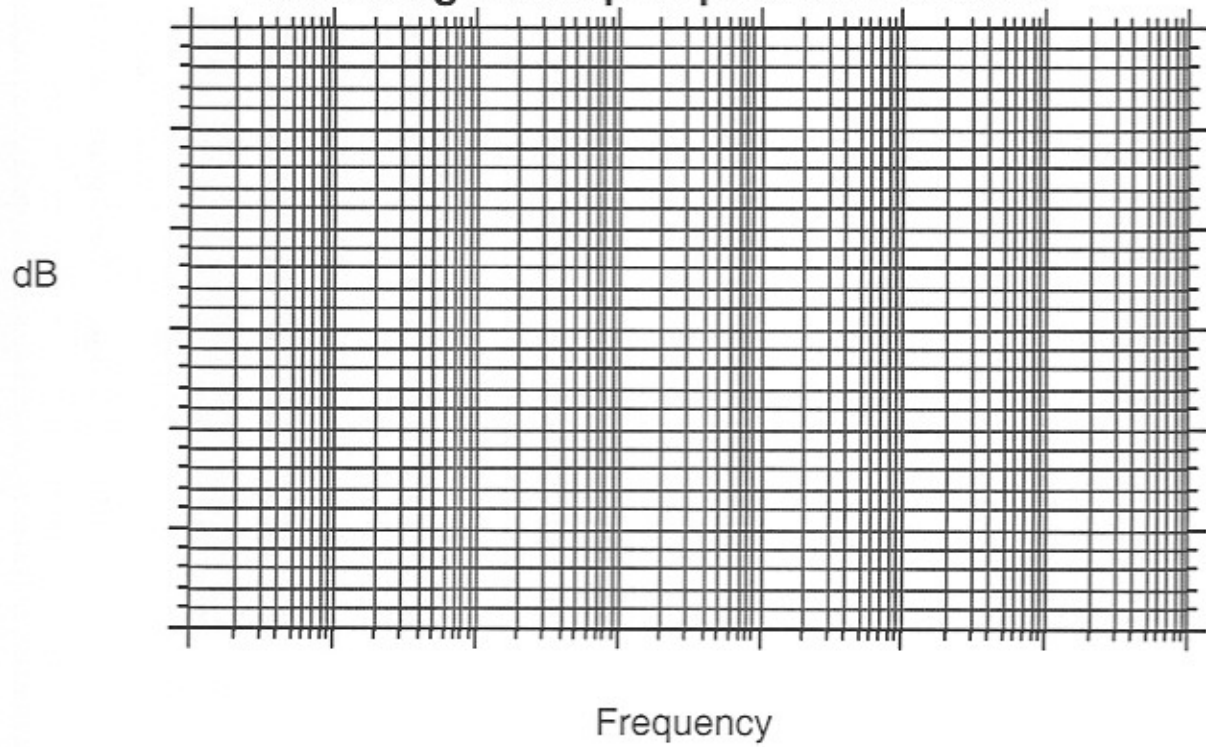
### Bode Magnitude plot-please label axes



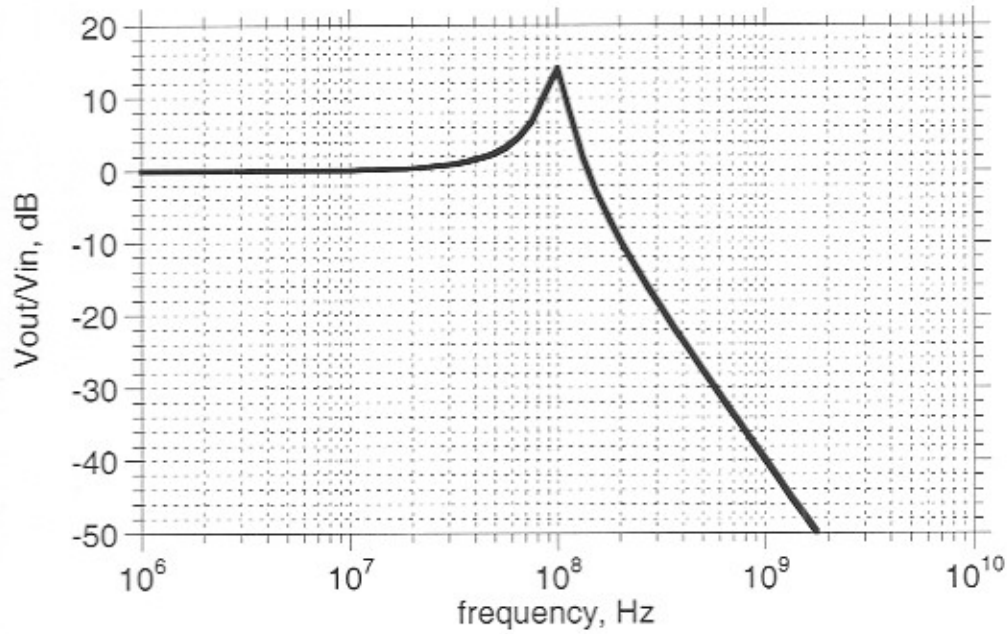Part b, 8 points

Another transistor circuit has a frequency response as shown.



Identify the frequency of all significant poles in the transfer function.

\_\_\_\_\_ Hz, \_\_\_\_\_ Hz, (etc)

If the poles are complex, please give the damping factor \_\_\_\_\_

Draw the output voltage given that the input is a 1-V step function. Clearly label and dimension the axes, and show and label clearly all key features of the waveform.

