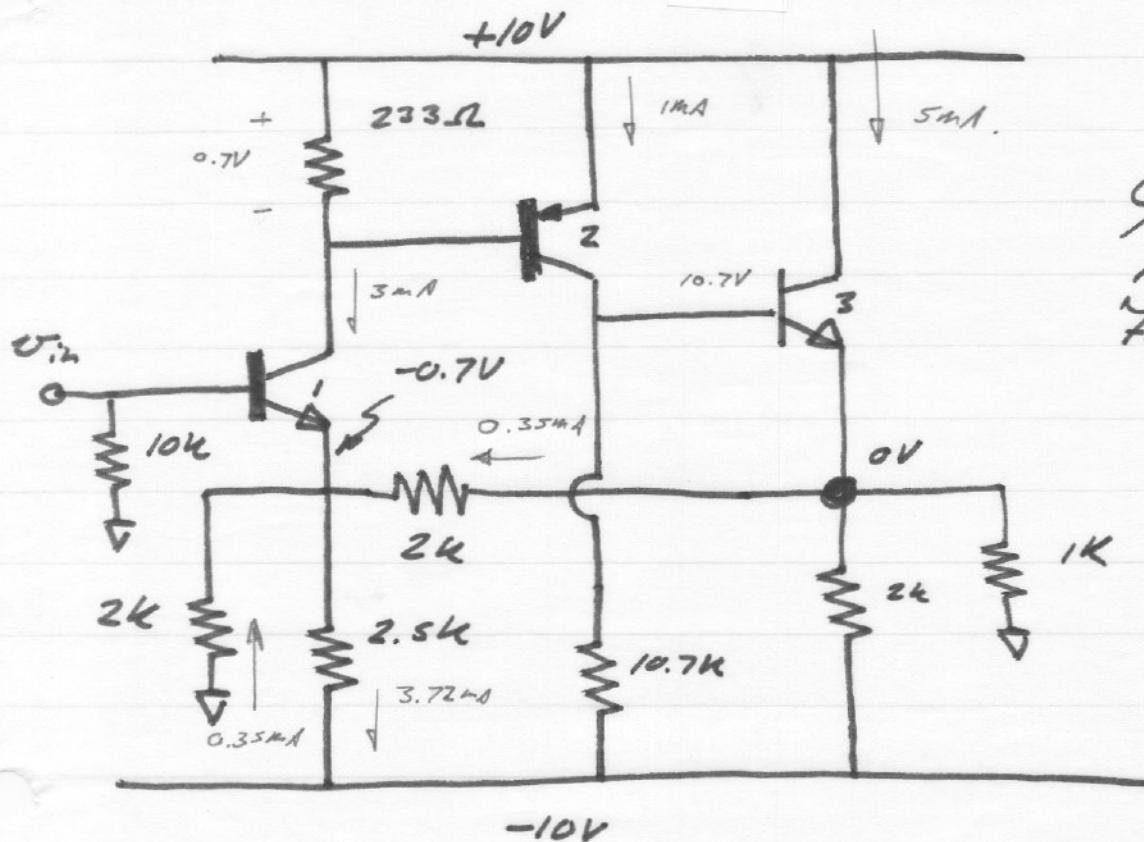


(1)

ECE1371B Notes Set 16 : Feedback example




First find $A_{\infty} = \frac{V_0}{V_i}$ / $A_d \rightarrow \infty$

$$A_{\infty} = \frac{2k + 2k//2.5k}{2k//2.5k} = 2.8$$

z

Now find T:

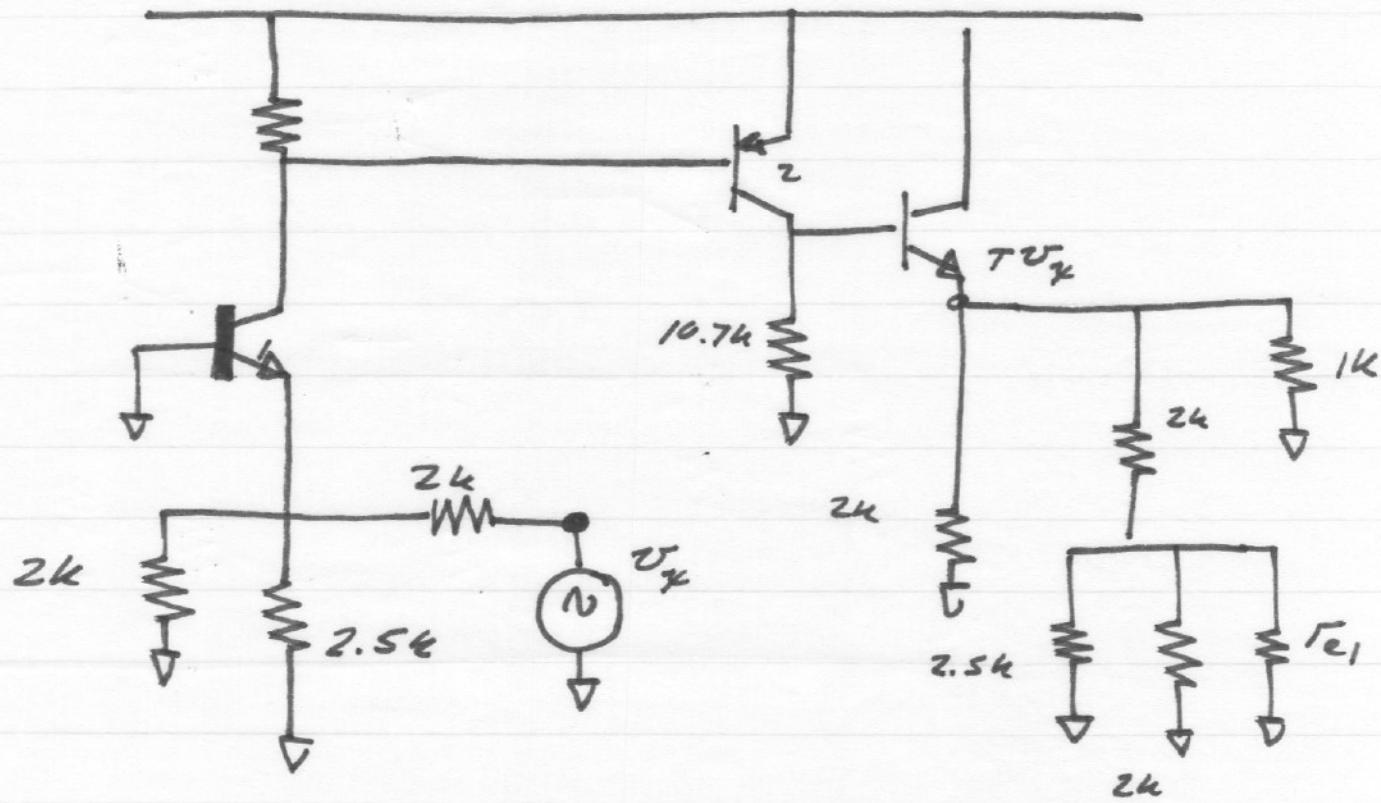

(3)

Lets calculate T at mid-band:

$$\frac{V_{e1}}{V_x} = \frac{r_e // 2k // 2.5k}{r_e // 2k // 2.5k + 2k} = 0.0043$$

$$Q_3: R_{leg3} = 670\Omega, Av_3 = 0.992, R_{L3} = 151k\Omega$$

$$Q_2: R_{leg2} = 10.0k\Omega, r_e = 26\Omega, Av = 384$$

$$Q_{1/2}: R_{leg} = 223\Omega, r_e = 8.7\Omega, Av = 25.7$$

$$\hookrightarrow \boxed{T_0 = 42}$$


$$A_{OL}(DC) = A_{in} \frac{T}{1+T} = 2.8 \cdot \frac{42}{43}$$

$$= 2.73$$

(4)

First lets rough-out the high-frequency response using the Node-by-Node Miller approximations.

Pole @ emitter of Q1

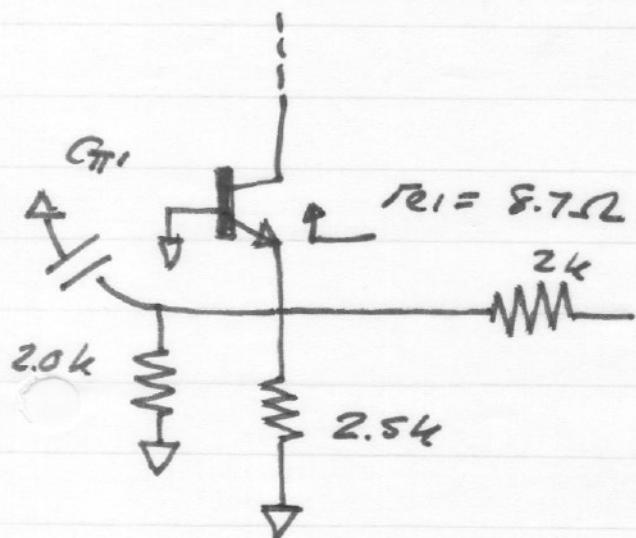

$$C = C_{pi1} = \frac{1}{2\pi f_T r_{e1}} - C_{ui} = 34\text{pF}$$

$$R = 8.7\Omega // 2k // 2k // 2.54\Omega \\ \approx 8.7\Omega$$


$$f_{pole} = 1/(2\pi(34\text{pF})(8.7\Omega)) \\ = 535\text{MHz}$$

which is somewhat larger than f_T .

\Rightarrow Pole at or near f_T .

(4a)

Pole at base of Q2 - Miller effect

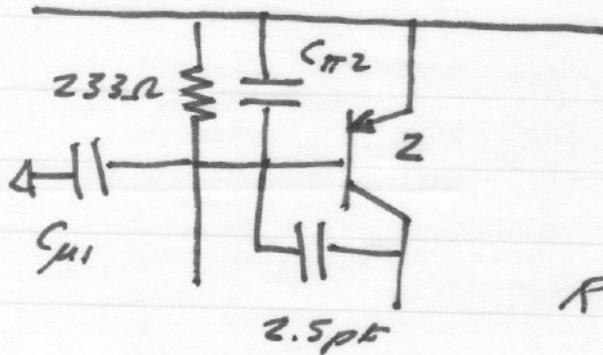

$$A_{v2} = \frac{-104\Omega}{26\Omega} = -385$$


$$R = 233\Omega // R_{pi2} = 226\Omega$$

$$\begin{aligned} C &= 386(2.5\text{pF}) + 2.5\text{pF} + 9.7\text{pF} \\ &= 977 \text{ pF} \end{aligned}$$

$$\begin{aligned} f_{pole} &= 1/2\pi(226\Omega)(977\text{pF}) \\ &= 720 \text{ kHz} \end{aligned}$$

(5)

Pole at collector of Q2 - Miller

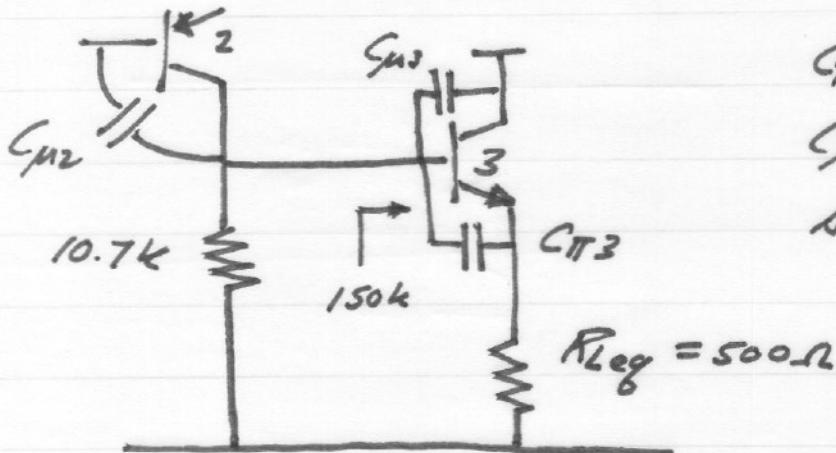

$$C_{\pi 3} = 59 \text{ pF}$$

$$C_{\mu 3} = 2.5 \text{ pF}$$

$$\Delta v_3 = 0.992$$

$$R_{leg} = 500\Omega$$

$$R_{node} = 10.7k \parallel 150k = 10k\Omega$$

$$C_{node} = 2.5 \text{ pF} + (1 - 0.992) 59 \text{ pF} + 2.5 \text{ pF}$$

$$= 5.47 \text{ pF}$$


$$f_{pole} = 1/2\pi(10k\Omega)(5.47 \text{ pF}) = 2.9 \text{ MHz}$$

Danger - this has no neglected pole-splitting.

We really must use a more accurate method.

(6)

Let's do it all instead by N.O.T.C. :

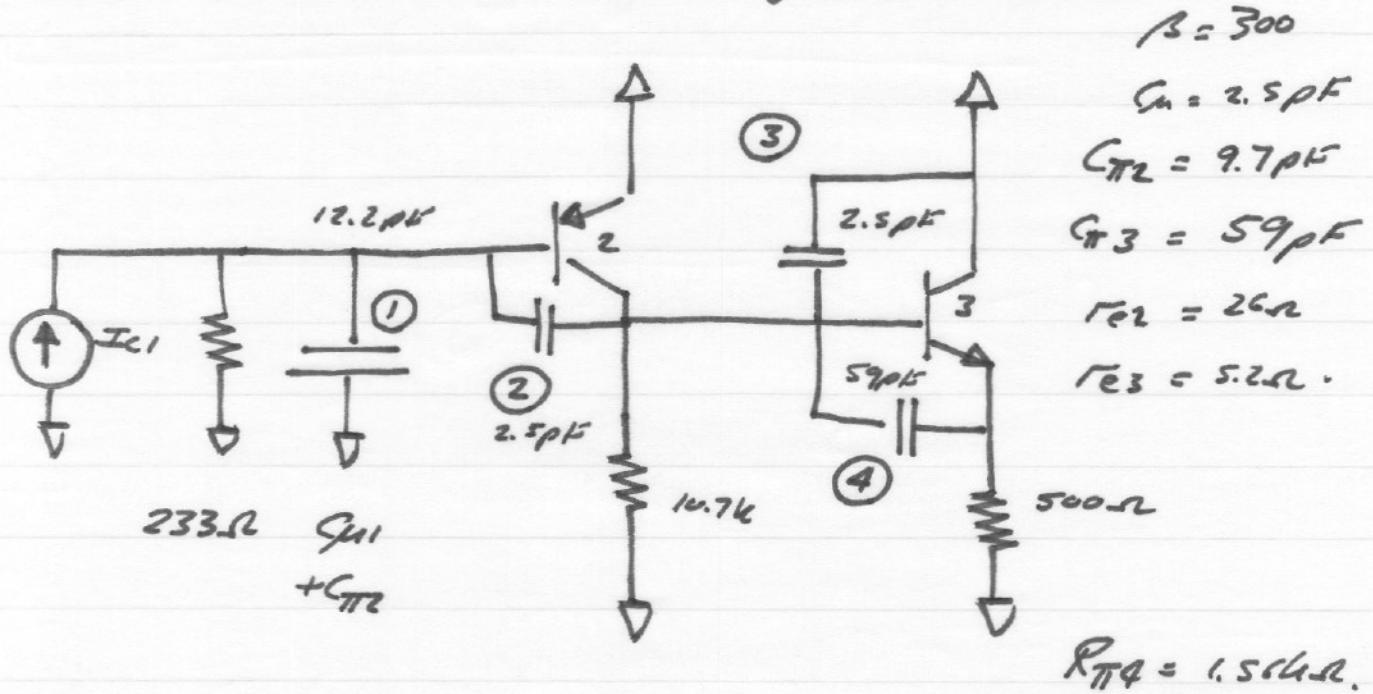

... and there is a pole @ the emitter

of Q, @ $f = 500 \text{ MHz}$.

$$\underline{R_{11}^{\circ}C_1 :} \quad R_{11}^{\circ} = 233\Omega // R_{i1} = 226\Omega \\ R_{11}^{\circ} C_1 = 2.76\mu s$$

$$\underline{R_{22}^{\circ}C_2 :} \quad R_{22}^{\circ} = 10k \\ R_{22}^{\circ} = 226\Omega \left(1 + \frac{10k}{226\Omega}\right) + 10k = 97.1\Omega$$

$$R_{22}^{\circ} C_2 = 0.243\mu s$$

$$\underline{R_{33}^{\circ} C_3 :} - R_{33}^{\circ} = 10k \\ R_{33}^{\circ} C_3 = 25\mu s$$

$$\underline{R_{44}^{\circ} C_4 :} \quad R_{44}^{\circ} = 1.56k\Omega // \left\{ 5.2\Omega // 500\Omega + 10k(1 - 0.992) \right\} \\ = 1.56k\Omega // \{ 5.14\Omega + 80\Omega \} \\ = 80.7\Omega$$

$$R_{44}^{\circ} C_4 = 4.76\mu s$$

$$A_1 = 2.76\mu s + 0.243\mu s + 25\mu s + 4.76\mu s$$

$$A_1 = 0.275\mu s$$

$$\underline{R_{11}^0 R_{22}' C_1 C_2}$$

$$R_{22}' = 104 \Omega$$

$$R_{11}^0 R_{22}' C_1 C_2 = 6.89 (10^{-17}) \text{ s}^2$$

$$\underline{R_{11}^0 R_{33}' C_1 C_3}$$

$$R_{33}' = R_{33}^0 = 104$$

$$R_{11}^0 R_{33}' C_1 C_3 = 6.9 (10^{-17}) \text{ s}^2$$

$$\underline{R_{11}^0 R_{44}' C_1 C_4}$$

$$R_{44}' = R_{44}^0 = 80.7 \Omega$$

$$R_{11}^0 R_{44}' C_1 C_4 = 1.31 (10^{-17}) \text{ s}^2$$

$$\underline{R_{22}^0 R_{33}^{2'} C_2 C_3}$$

$$R_{33}^{2'} = 233 \Omega // 10.7 \Omega // R_{13} // r_{e2} \approx r_{e2} = 26 \Omega$$

$$R_{22}^0 R_{33}^{2'} C_2 C_3 = 1.58 (10^{-17}) \text{ sec}^2$$

(9)

$$\underline{R_{22}^0 R_{44}^2 C_2 C_4}$$

$$R_{44}^2 = 1.564 \Omega // \left\{ 5.2 \Omega // 500 \Omega + 2 \Omega (1 - 0.992) \right\}$$

$$= 1.564 // (5.14 \Omega + 0.21 \Omega)$$

$$= 5.33 \Omega$$

$$R_{22}^0 R_{44}^2 C_2 C_4 = 7.6 (10^{-17}) \text{ s}^2$$

$$\underline{R_{33}^0 R_{44}^3 C_3 C_4}$$

$$R_{44}^3 = 500 \Omega // 1 \Omega = 5.1 \Omega$$

$$R_{33}^0 R_{44}^3 C_3 C_4 = 0.76 (10^{-17}) \text{ sec}^2.$$

$$a_2 = 2.5 (10^{-16}) \text{ sec}^2 = [1.59 (10^{-8}) \text{ sec}]^2 = (15.8 \text{ ns})^2$$

Note terms $C_1 C_2, C_1 C_3, C_2 C_4$ are the largest in a_2

$$\alpha_1 = 0.275 \mu\text{s}$$

$$\alpha_2 = (15.8 \text{ ns})^2$$

Try the separated-pole approximation:


$$f_{p1} = 1/2\pi\alpha_1 = 578 \text{ kHz}$$

$$f_{p2} = \alpha_1/2\pi\alpha_2 = 175 \text{ MHz}$$

} clearly very
separated, so
approximation is ok

also at emitter of Q1: $f_{pole} = 500 \text{ MHz}$.

Compare answers:

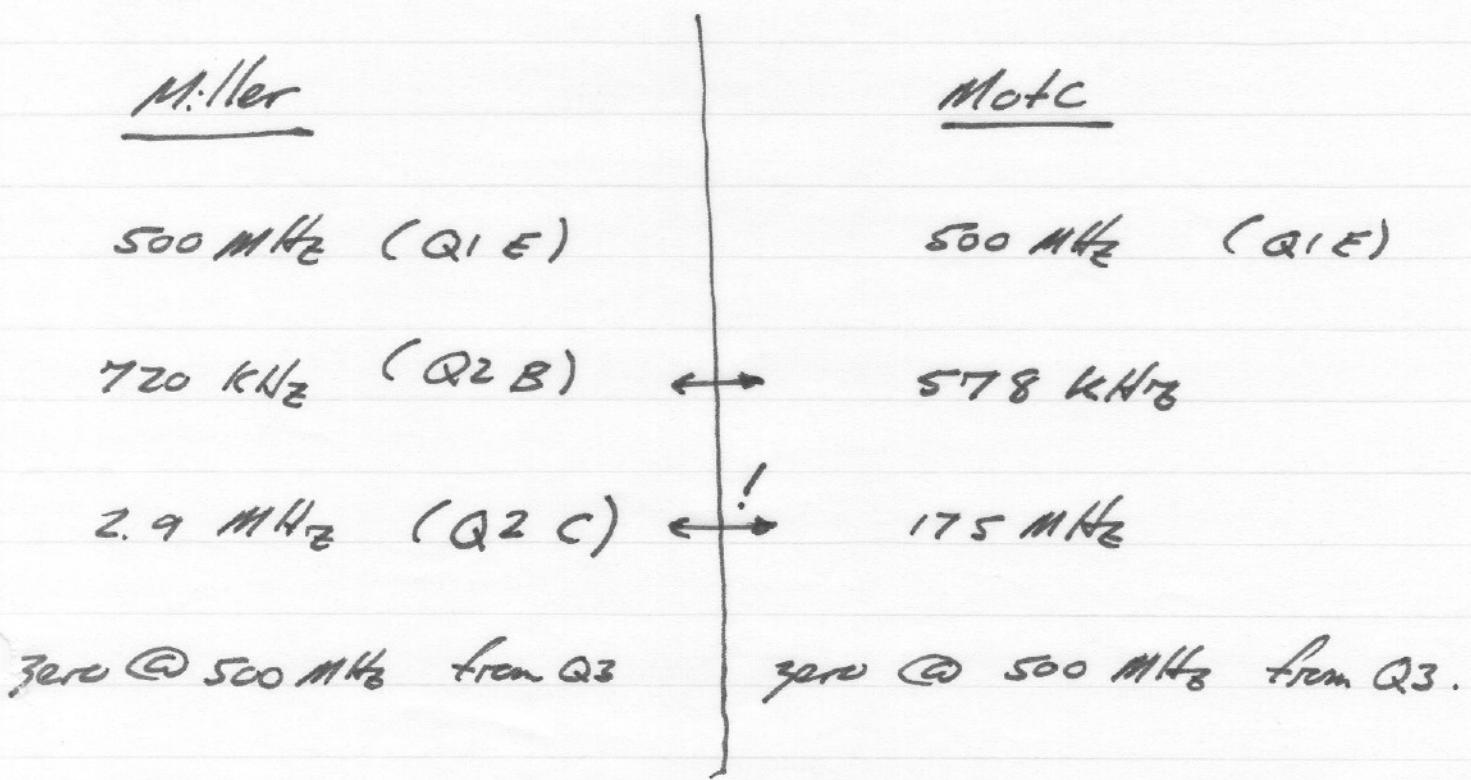

Again note that the node-by-node Miller approximations got the first pole nearly right - but got the second pole amazingly wrong. This is because of pole interaction - pole splitting. We would have got wildly wrong conclusions regarding the loop phase margin if we had just used the Miller Methods.


Despite this, I still personally use the Miller Methods first, to get a quick mental picture

so overall loop transfer function has:

$$T_0 = 42 \quad \text{dc loops transmission.}$$

& poles at 578 kHz & 175 MHz.

lets do a Bode plot:

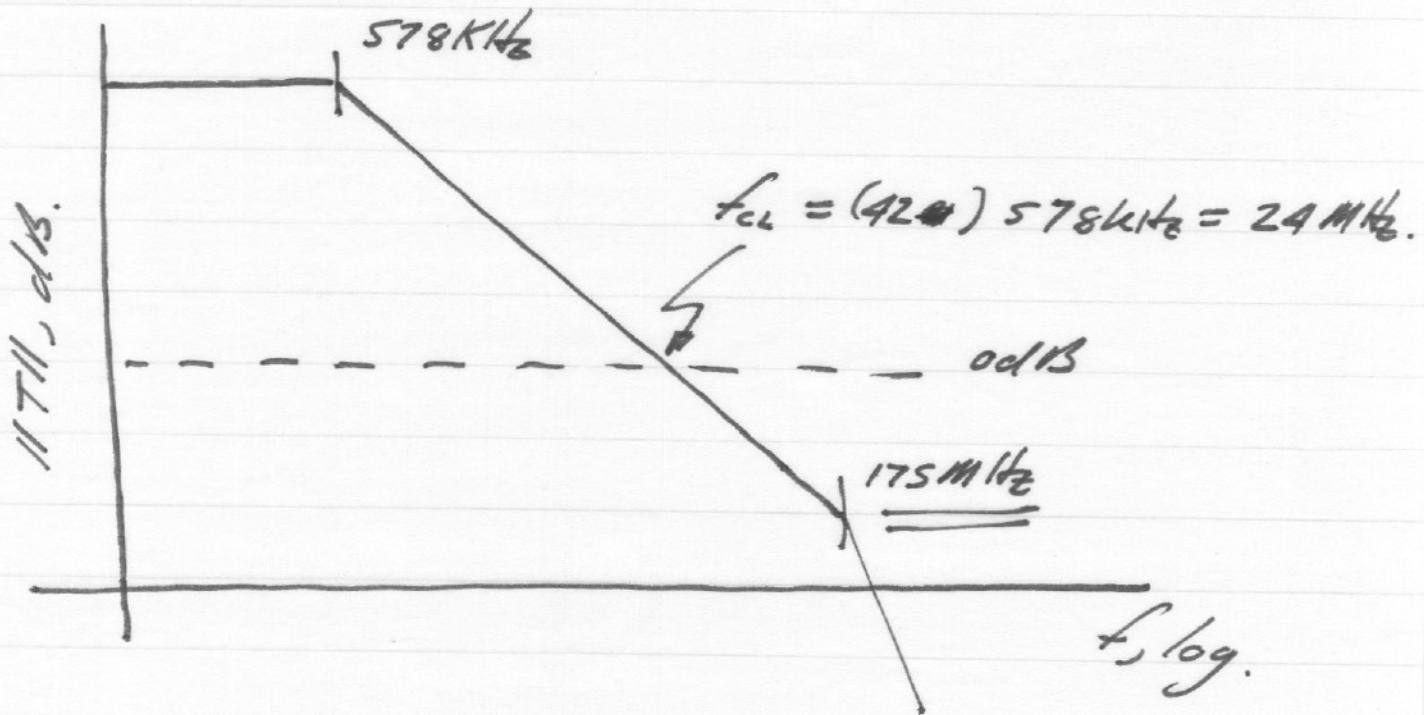

$$\text{Phase Margin} \approx 180^\circ - \arctan \frac{29 \text{ MHz}}{175 \text{ MHz}} - \arctan \frac{24 \text{ MHz}}{578 \text{ kHz}}$$

$$= 180^\circ - 7.8^\circ - 88.6^\circ$$

$$= 83.6^\circ \leftarrow \text{very stable!}$$

Bode Stability analysis, example from last lecture

