

ECE 137 B: Notes Set 3

Common-emitter/source with emitter/source degeneration

Mark Rodwell

Doluca Family Chair


University of California, Santa Barbara

rodwell@ucsb.edu 805-893-3244

High-frequency analysis of emitter degeneration

How to treat the effect of emitter degeneration R_{EAC} on high-frequency transfer function.

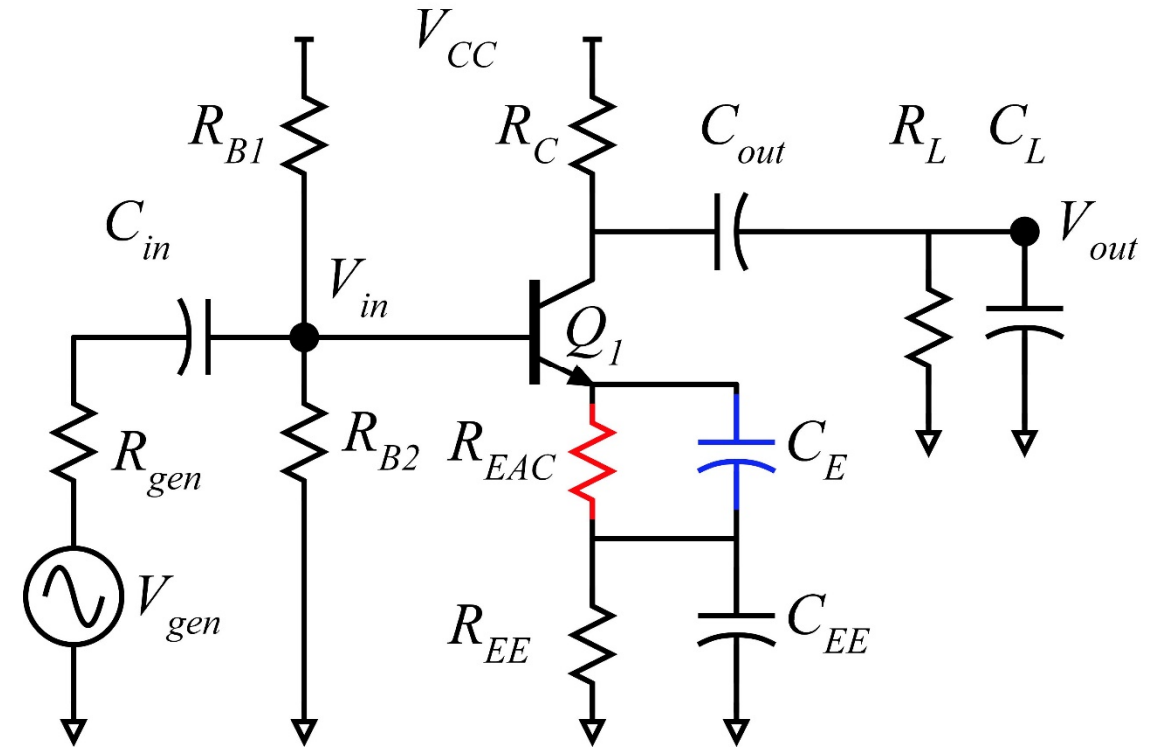To simplify the analysis, we will add an additional small capacitor C_E , that may or may not actually be present in the circuit; if it is not, then the analysis is approximate.



The answer, before we get started

We will show that a transistor
in common emitter mode,
with emitter degeneration.


Can be modelled as a transistor,
without emitter degeneration.

Where

$$\frac{\tilde{C}_{be}}{C_{be}} = \frac{\tilde{g}_m}{g_m} = \frac{\tilde{R}_{be}}{R_{be}} = \frac{\tilde{R}_{ce}}{R_{ce}} = \frac{1}{1 + g_m R_{EAC}}$$

note that all impedances got bigger,
and all admittances got smaller,
by the same ratio.

Except that C_{cb} *did not change*

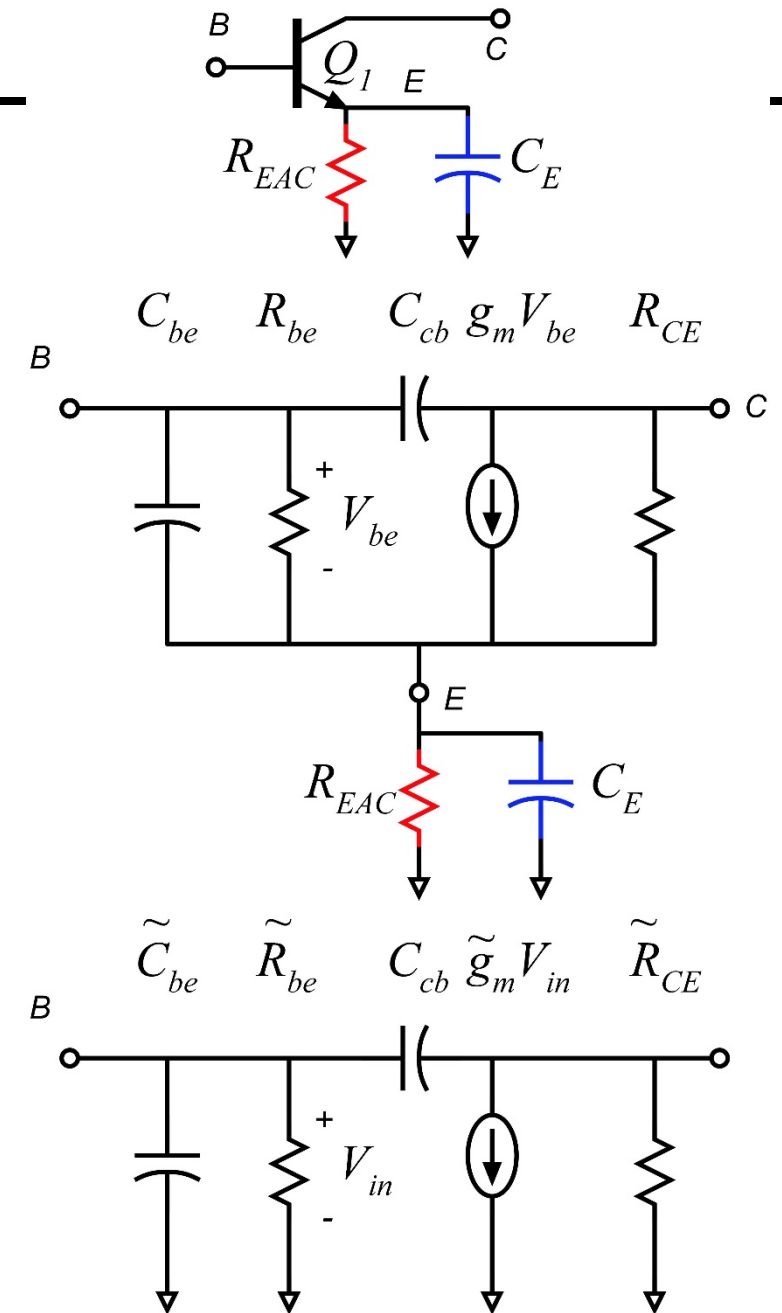

The answer, before we get started

We will show that a transistor
in common source mode,
with source degeneration.


Can be modelled as a transistor,
without source degeneration.

Where

$$\frac{\tilde{C}_{gs}}{C_{gs}} = \frac{\tilde{g}_m}{g_m} = \frac{R_{DS}}{\tilde{R}_{DS}} = \frac{1}{1 + g_m R_{SAC}}$$

note that all impedances got bigger,
and all admittances got smaller,
by the same ratio.

Except that C_{gd} did not change.


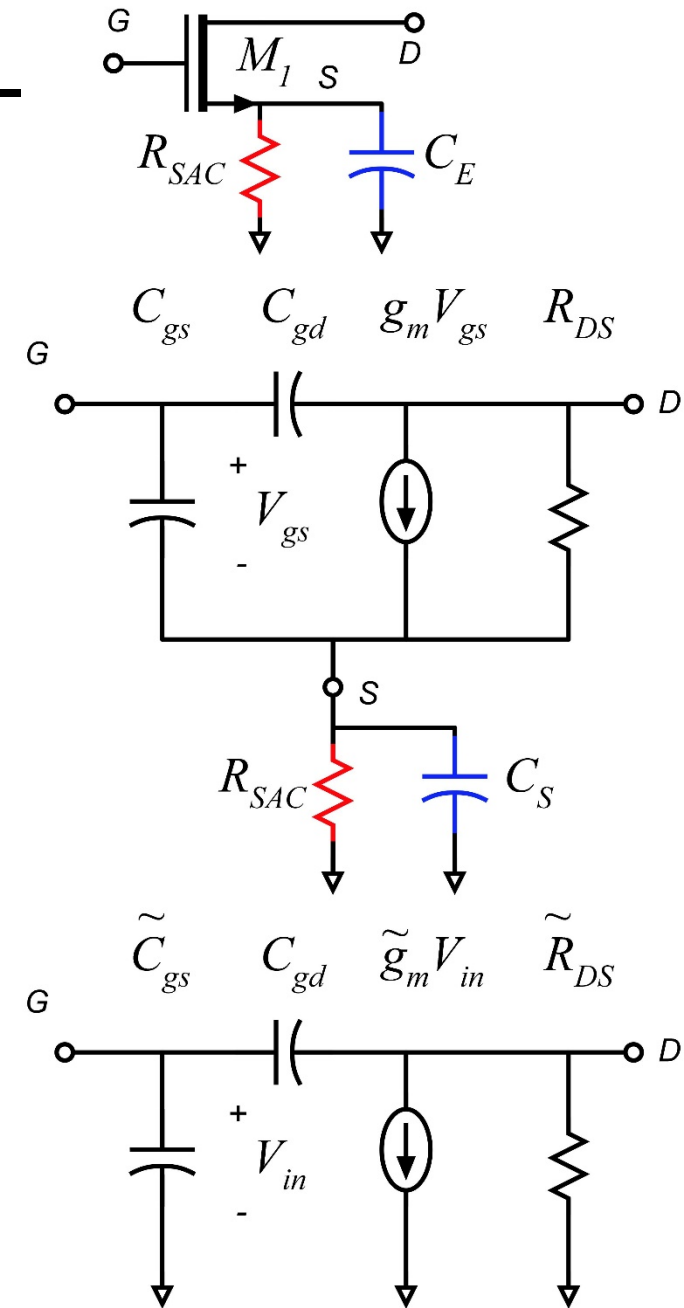


The sub-circuit to be analyzed

Model of bipolar transistor with emitter degeneration.

Note that C_{cb} can be temporarily removed (disconnected) from the network, ...and then put back later.

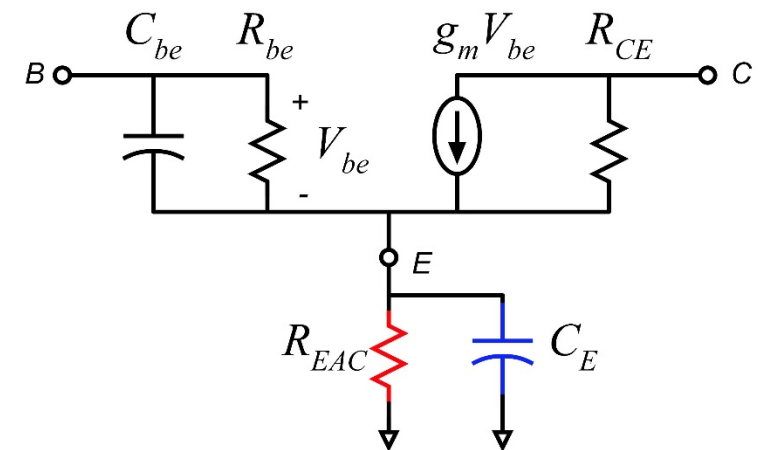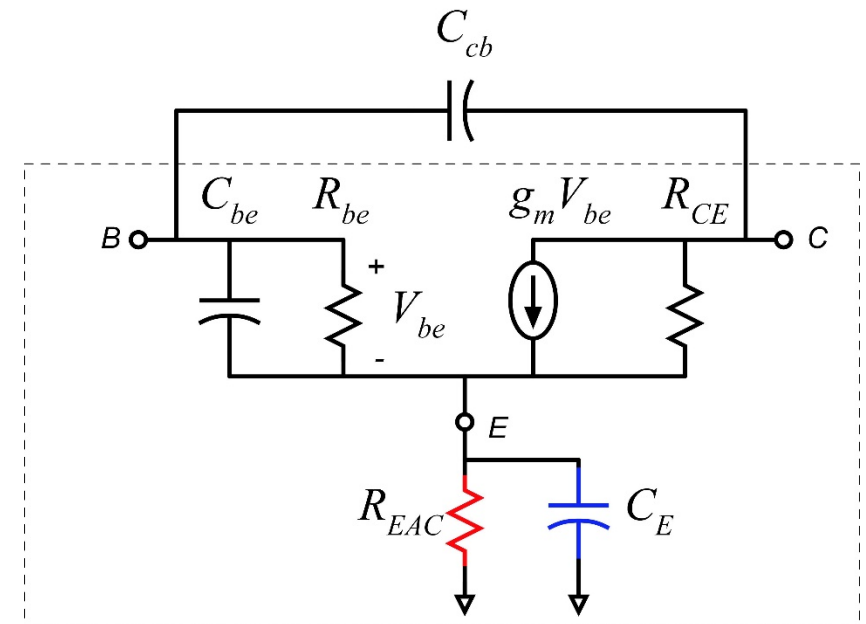This is why degeneration does not change the effective value of C_{cb} .



Deriving high-frequency model of emitter degeneration

Simplify the problem by setting $R_{be} = R_{CE} = \infty \Omega$.

Key assumption: $R_{EAC} C_E = C_{be} / g_m$

$$Z_E = R_{EAC} \parallel (1 / sC_E) = \frac{R_{EAC}}{1 + sR_{EAC} C_E} = \frac{R_{EAC}}{1 + sC_{be} / g_m}$$

Apply input current I_{in}

step 1: $V_{be} = I_{in} / sC_{be}$



step 2: $I_{out} = I_C = g_m V_{be} = I_{in} \cdot g_m / sC_{be}$

step 3: $I_E = I_{out} + I_{in} = I_{in} (1 + g_m / sC_{be})$

step 4: $V_E = I_E Z_E = \frac{R_{EAC} I_{in} (1 + g_m / sC_{be})}{1 + sC_{be} / g_m}$
 $= \frac{g_m R_{EAC} I_{in} (1 + sC_{be} / g_m)}{sC_{be} (1 + sC_{be} / g_m)} = \frac{g_m R_{EAC}}{sC_{be}} I_{in}$

step 5: $V_{in} = V_{be} + V_E = \frac{I_{in}}{sC_{be}} + \frac{g_m R_{EAC}}{sC_{be}} I_{in} = I_{in} \left(\frac{1 + g_m R_{EAC}}{sC_{be}} \right)$
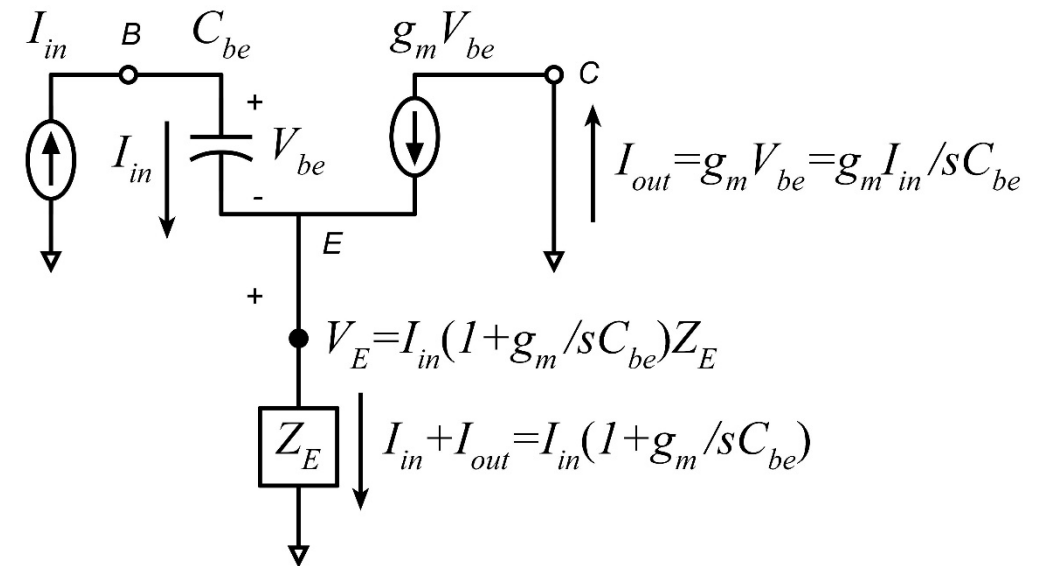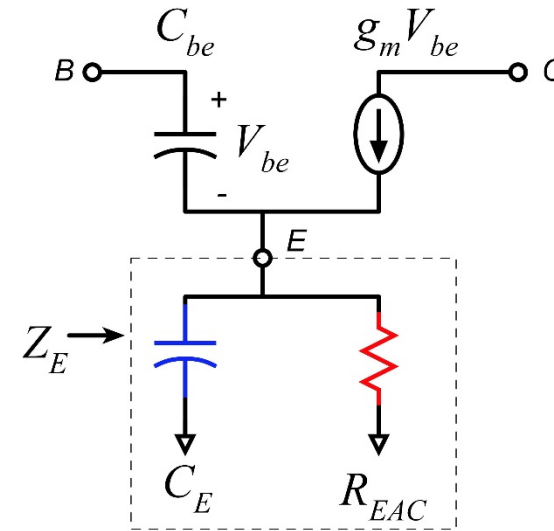
$$\frac{V_{in}}{I_{in}} = Z_{in} = \left(\frac{1}{s\tilde{C}_{be}} \right) \text{ where } \tilde{C}_{be} = \frac{C_{be}}{1 + g_m R_{EAC}}$$





Deriving high-frequency model of emitter degeneration

$$\frac{V_{in}}{I_{in}} = Z_{in} = \left(\frac{1}{s\tilde{C}_{be}} \right) \text{ where } \tilde{C}_{be} = \frac{C_{be}}{1 + g_m R_{EAC}}$$

$$\text{step 7: } I_{out} = g_m V_{be} = \frac{g_m}{sC_{be}} I_{in} = \frac{g_m}{sC_{be}} \frac{V_{in}}{Z_{in}} = g_m V_{in} \frac{s\tilde{C}_{be}}{sC_{be}}$$


$$I_{out} = V_{in} \frac{g_m}{1 + g_m R_{EAC}}$$
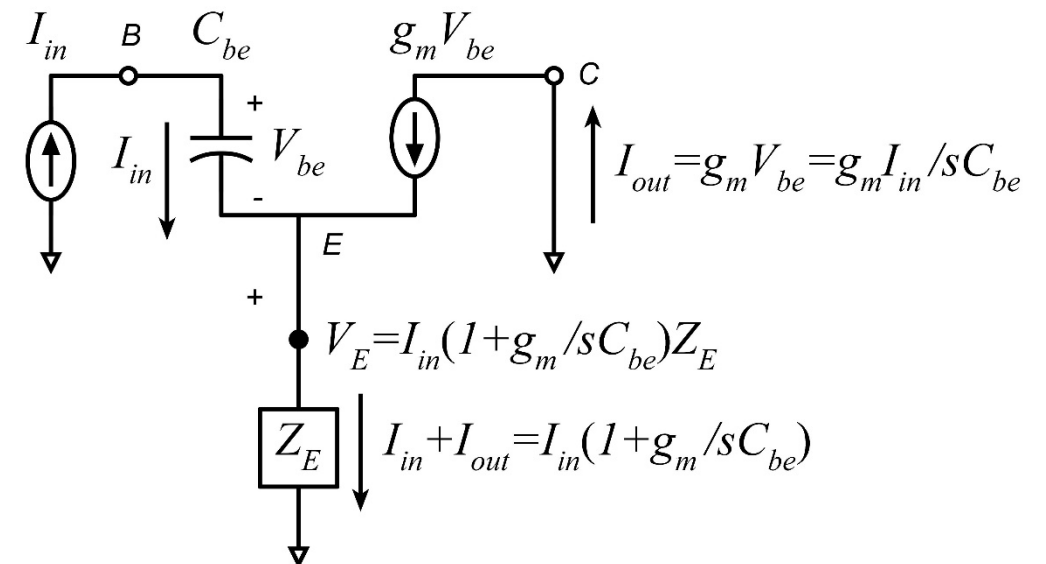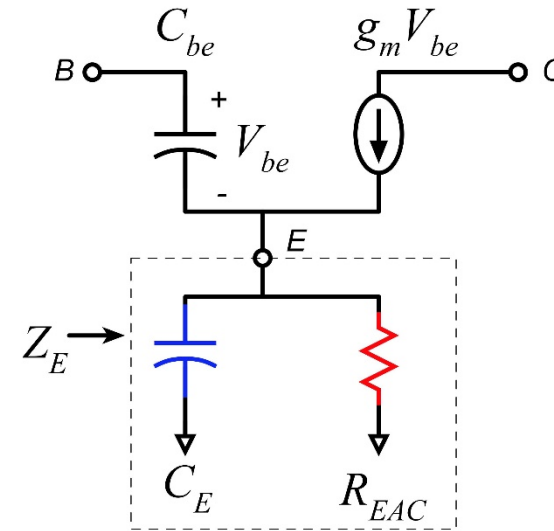
$$I_{out} = \tilde{g}_m V_{in} \text{ where } \tilde{g}_m = \frac{g_m}{1 + g_m R_{EAC}}$$



Deriving high-frequency model of emitter degeneration

So this...

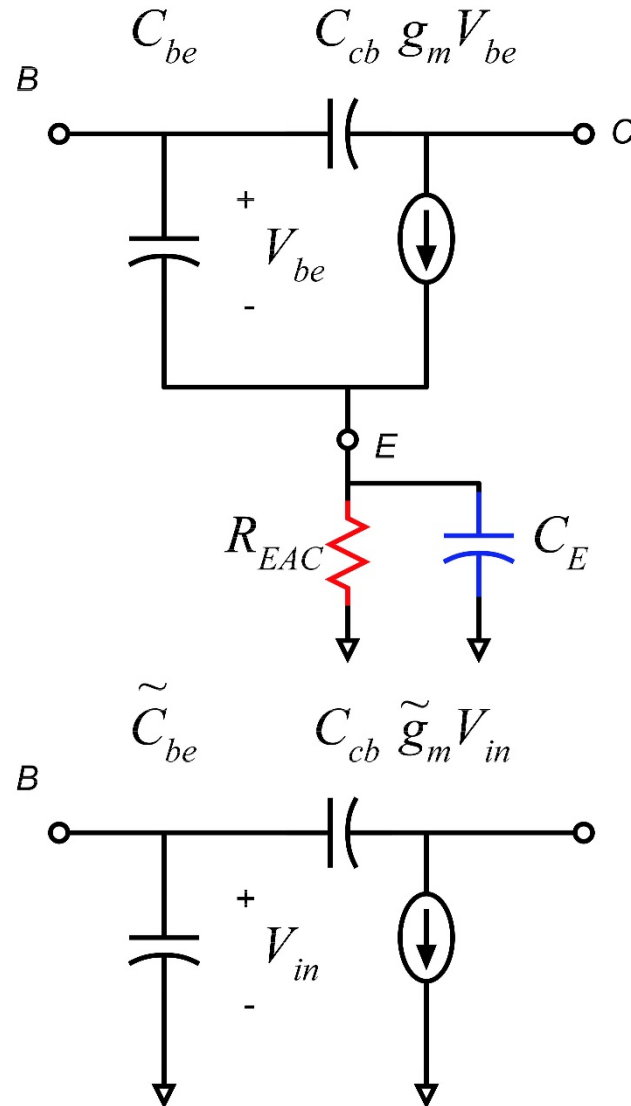

$$\text{where } \tilde{C}_{be} = \frac{C_{be}}{1 + g_m R_{EAC}}$$

and

$$\tilde{g}_m = \frac{g_m}{1 + g_m R_{EAC}}$$

...has the same characteristics as
(can be replaced by) this.

Combining this with the low-frequency result:

A transistor
in common emitter mode,
with emitter degeneration.


Can be modelled as a transistor,
without emitter degeneration.

Where

$$\frac{\tilde{C}_{be}}{C_{be}} = \frac{\tilde{g}_m}{g_m} = \frac{\tilde{R}_{be}}{R_{be}} = \frac{\tilde{R}_{ce}}{R_{ce}} = \frac{1}{1 + g_m R_{EAC}}$$

note that all impedances got bigger,
and all admittances got smaller,
by the same ratio.

Except that C_{cb} *did not change*

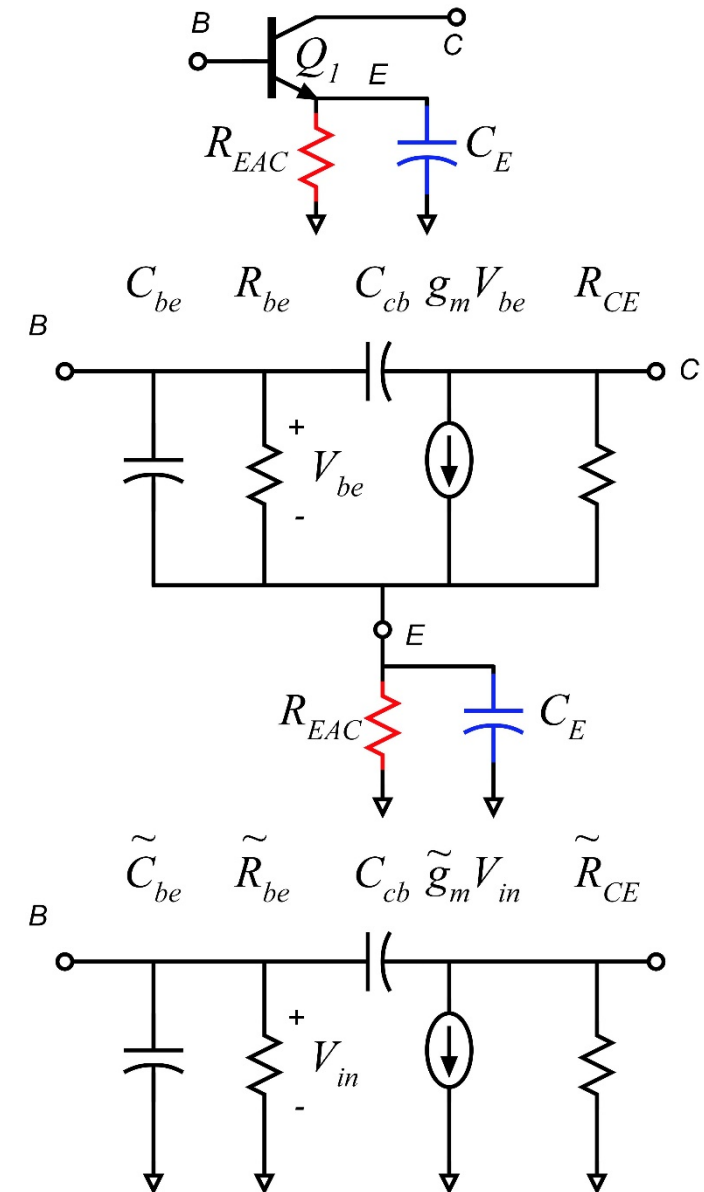


What about the capacitor C_E ?

We have added the capacitor C_E with the assumption

$$R_{EAC} C_E = C_{be} / g_m$$

Note that $R_{EAC} C_E < 1 / 2\pi f_\tau$; a very small time constant.

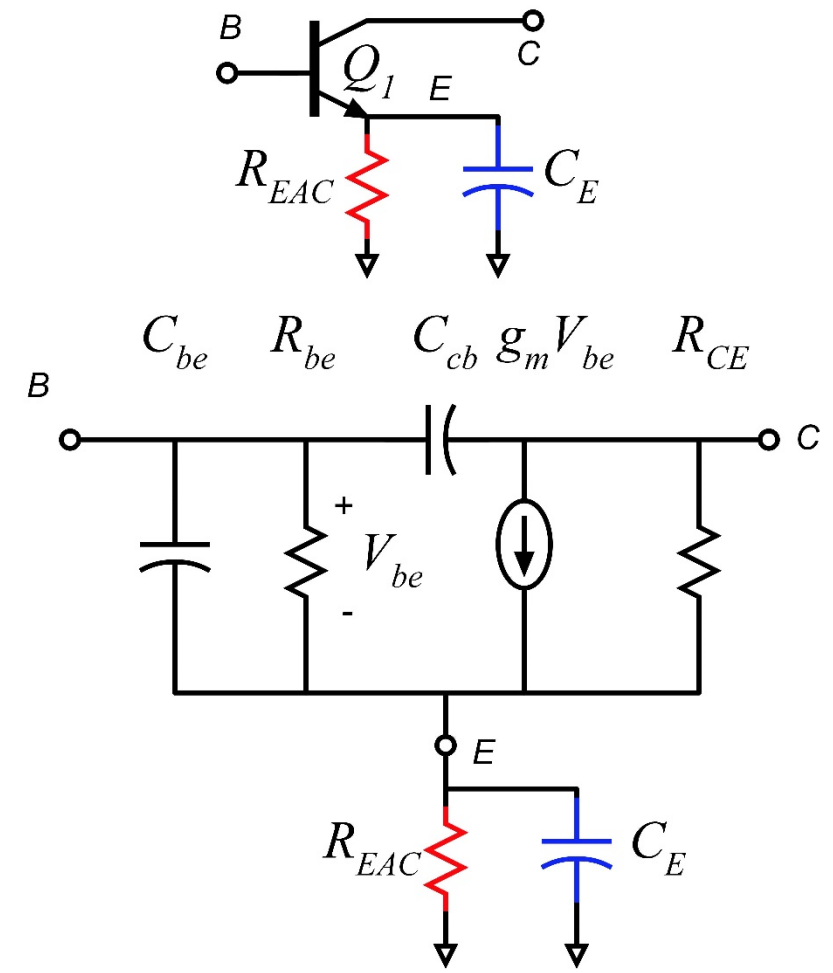→ Removing C_E only has significant effect at frequencies near f_τ




What about the capacitor C_E ?

It is too detailed for ECE137B, but a more careful analysis shows that, if C_E is not present, then the circuit can be accurately modelled as shown to the right.


Note the presence of R_{EAC} in the *base* of the resulting equivalent circuit.
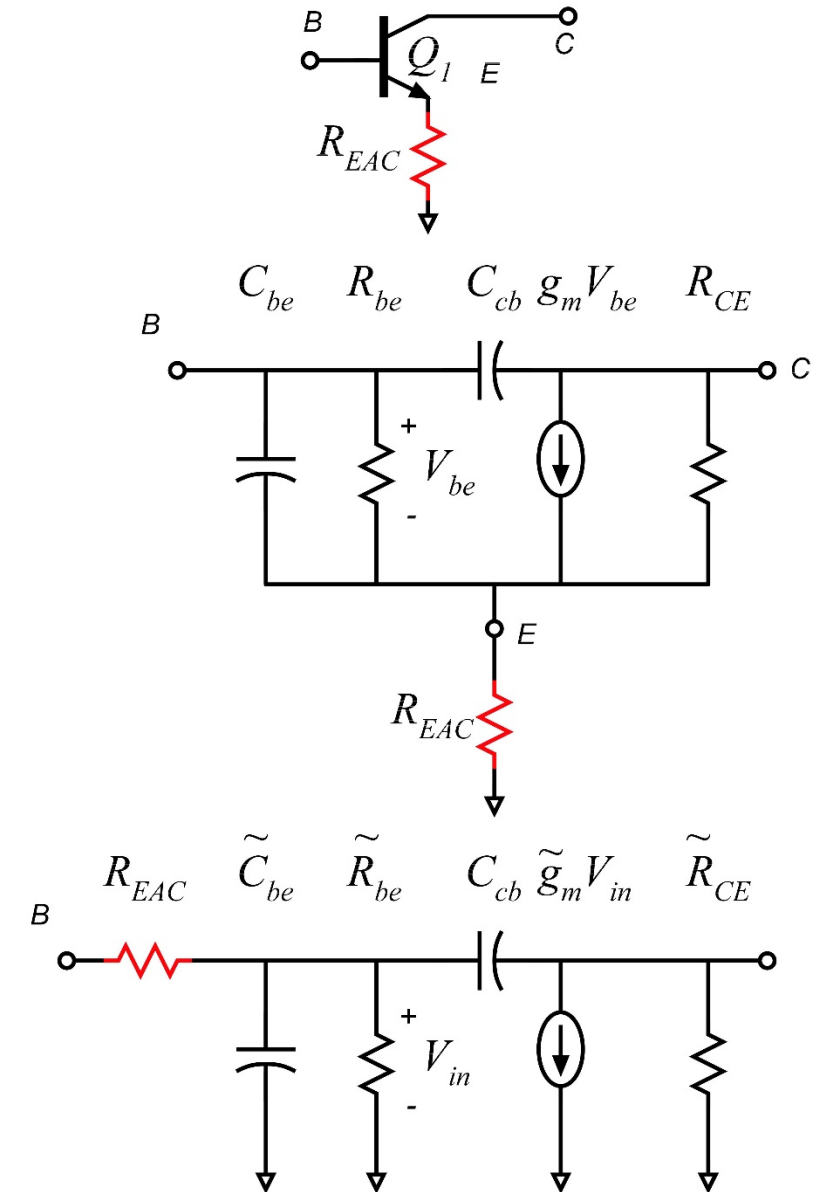
$$\frac{\tilde{C}_{be}}{C_{be}} = \frac{\tilde{g}_m}{g_m} = \frac{R_{be}}{\tilde{R}_{be}} = \frac{R_{ce}}{\tilde{R}_{ce}} = \frac{1}{1 + g_m R_{EAC}}$$



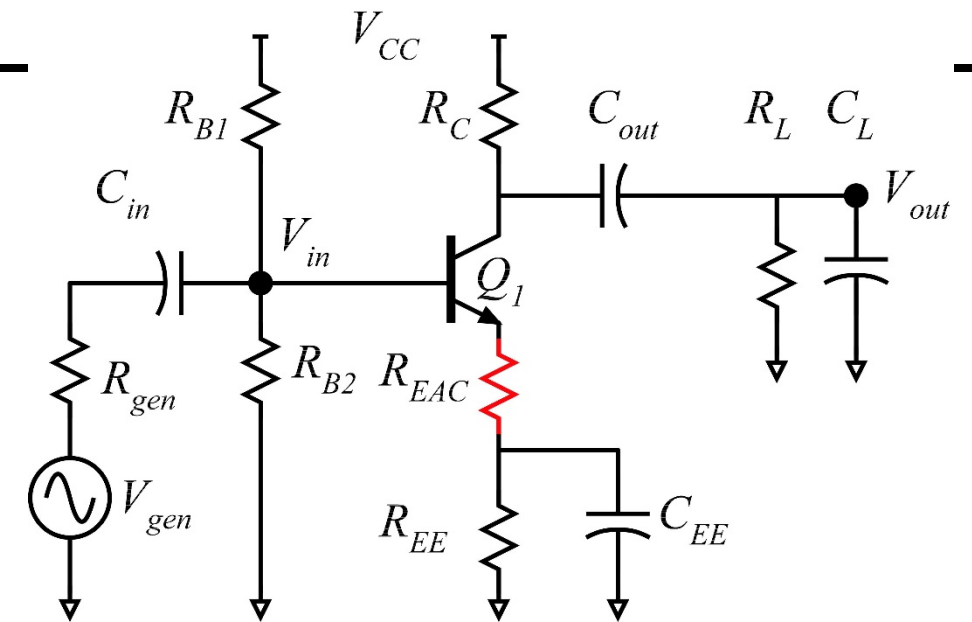Example (1)

For now, low-frequency rolloff due to DC blocking and emitter bypass capacitance is ignored.



$$C_E = C_{in} = C_{out} = \infty \text{ F}$$

$$V_A = 100 \text{ V.}$$

$$\beta = 100$$

$$f_\tau = 100 \text{ MHz @ } I_C = 1 \text{ mA}$$

$$C_{cb} = 10 \text{ pF}$$

$$R_{b1} = 123 \text{ k}\Omega$$

$$R_{b2} = 64 \text{ k}\Omega$$

$$R_{gen} = 1 \text{ k}\Omega$$

$$R_C = 8 \text{ k}\Omega$$

$$R_{EAC} = 48 \text{ }\Omega$$

$$R_{EE} = 5 \text{ k}\Omega$$

$$R_L = 1 \text{ k}\Omega$$

Example (2): Mid-band equivalent circuit

For now, low-frequency rolloff due to DC blocking and emitter bypass capacitance is ignored.

$$V_{gen} / R_{gen} = V_{gen} / 1 \text{ k}\Omega$$

$$R_{inAmp} = 10 \text{ k}\Omega \parallel 123 \text{ k}\Omega \parallel 64 \text{ k}\Omega$$


$$R_i = R_{inAmp} \parallel R_{gen} = R_{inAmp} \parallel 1 \text{ k}\Omega = 890 \Omega$$

$$\tilde{g}_m V_{in} = \frac{V_{in}}{48 \Omega + 52 \Omega} = \frac{V_{in}}{100 \Omega}$$

$$R_{Leq} = R_{CE} \parallel R_C \parallel R_L \approx R_C \parallel R_L = 1 \text{ k}\Omega \parallel 8 \text{ k}\Omega = 890 \Omega$$

Midband gain

$$\left. \frac{V_{out}}{V_{in}} \right|_{mid-band} = \frac{-890 \Omega}{100 \Omega} = -8.9$$

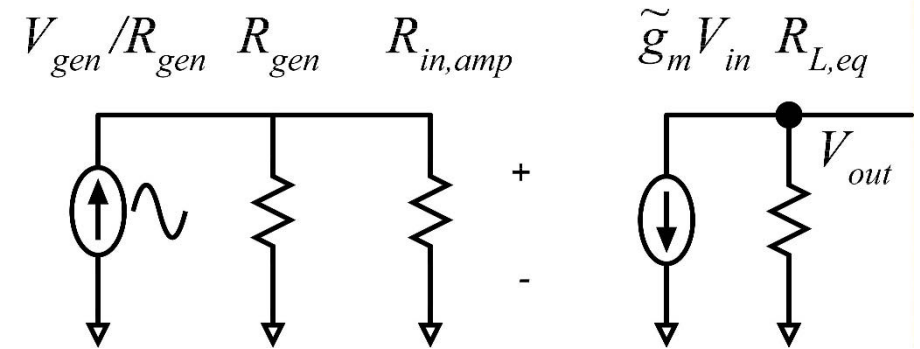

Small-signal parameters

$$C_{cb} = 10 \text{ pF}$$

$$1/g_m = 26 \text{ mV}/0.5 \text{ mA} = 52 \Omega$$

$$C_{be} = g_m / 2\pi f_\tau - C_{cb} = 20.6 \text{ pF}$$

Example (2): high-frequency response

$$\tilde{C}_{be} = C_{be} \left(r_e / (r_e + R_{EAC}) \right) = 20.6 \text{ pF} (48/100) = 9.9 \text{ pF}$$

$$\frac{v_{out}(s)}{v_{gen}(s)} = -8.9 \frac{1 + b_1 s}{1 + a_1 s + a_2 s^2}$$

$$a_1 = 890 \Omega \tilde{C}_{be} + 890 \Omega (1 + \tilde{g}_m R_{leg}) C_{cb} + 890 \Omega (C_{cb} + C_L)$$

$$= 114 \text{ ns}$$


$$b_1 = -10 \text{ pF} / \tilde{g}_m = -10 \text{ pF} \cdot 100 \Omega = -1 \text{ ns}$$

$$a_2 = 890 \Omega \cdot 890 \Omega \left[9.9 \text{ pF} \cdot 10 \text{ pF} + 9.9 \text{ pF} \cdot 10 \text{ pF} + 10 \text{ pF} \cdot 10 \text{ pF} \right]$$

$$= 2.36 (10^{-16}) \text{ sec}^2 = (15.4 \text{ ns})^2$$

$$v_o/v_{gen} = \frac{-8.9 (1 - A \cdot 1 \text{ ns})}{(1 + A \cdot 114 \text{ ns} + A^2 (15.4 \text{ ns})^2)}$$
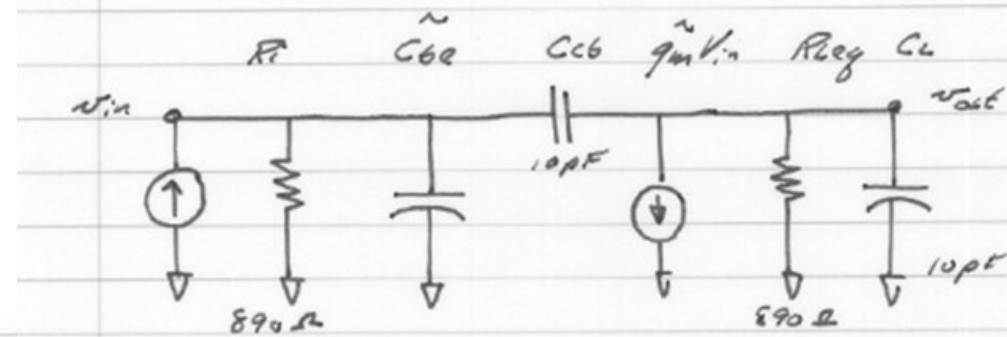
$$\approx -8.9 \frac{1 - A(1 \text{ ns})}{(1 + A \cdot 114 \text{ ns})(1 + A \cdot 2(1 \text{ ns}))} \quad \text{using SPA}$$



$$\tilde{g}_m = (100 \Omega)^{-1}$$

Example (3): high-frequency response

$$\frac{V_{out}(j2\pi f)}{V_{in}(j2\pi f)} = -8.9 \cdot \frac{1 - jf / 160 \text{ MHz}}{(1 + jf / 1.4 \text{ MHz})(1 + jf / 176 \text{ MHz})}$$

