

ECE137B notes set 8. Multistage analysis

Methods of analysis of multistage Frequency response.

1) breaking into individual stages

- does not work, because Z_{in} of most stages is very complex.
Only exception: break in center of common-base stage.
Even this is not realistic if $R_{bb} \neq 0$.

2) Nodal analysis

- Learn to do! valuable for simple circuits
- very hard for complex circuits
- answers can be hard or impossible to interpret.
→ limits understanding

3) Computer analysis (SPICE)

Good final check on design predictions

No understanding

No good for choosing a design.

4) MOTE

Easy. Quick.

Gets 1st pole right.

Gets 2nd pole approx. mately.

Good insights.



(2)

MOSFET: $C_{ox} V_{sat} = 1 \text{ mS}/\mu\text{m}$ $V_{th} = 0.25 \text{ V}$ $\lambda = 0$ for simplicity

$W_g = 20 \mu\text{m}$, $L_g = 200 \text{ nm}$, $V_{sat} = 10^7 \text{ cm/sec}$

$\Rightarrow C_{gs} = 40 \text{ fF}$, $C_{gd} = 10 \text{ fF}$, $g_m = 20 \text{ mS}$ ($f_T = 80.6 \text{ Hz}$)

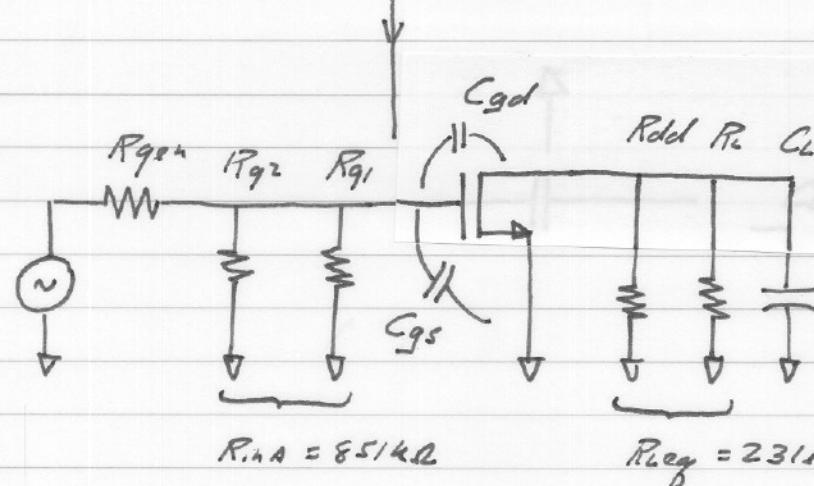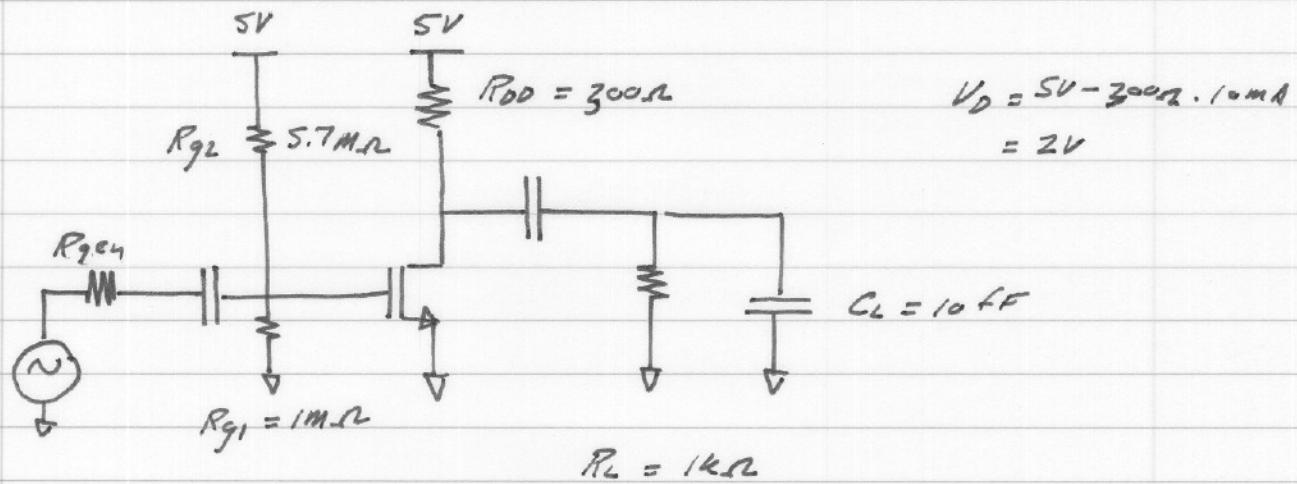Bias at $I_D = 10 \text{ mA} \rightarrow V_{gs} = 0.75 \text{ V}$



$$R_i = R_{gen} // R_{inA} = 9.9 \text{ k}\Omega$$

(3)

Mid-band analysis

$$\left. \begin{aligned} w_{in/v_{gen}} &= 851/861 = 0.99 \\ w_o/w_{in} &= -g_m R_{leg} = -4.62 \end{aligned} \right\} w_{v_{gen}} = -4.57 \approx -4.6$$

High Frequency analysis: dominant pole only:

$$a_1 = R_i (C_S + \underbrace{C_{gd} [R_i (1 - A_V) + R_{leg}]}_{5.62}) + C_o \cdot R_{leg}$$



$$= 188 \text{ ps} + \underline{559 \text{ ps}} + 2.3 \text{ ps} = 749 \text{ ps}$$

$$f_{p1} \approx 1/2\pi a_1 = \underline{212 \text{ MHz}}$$

note that Miller multiplication has made C_{gd} the dominant bandwidth limit

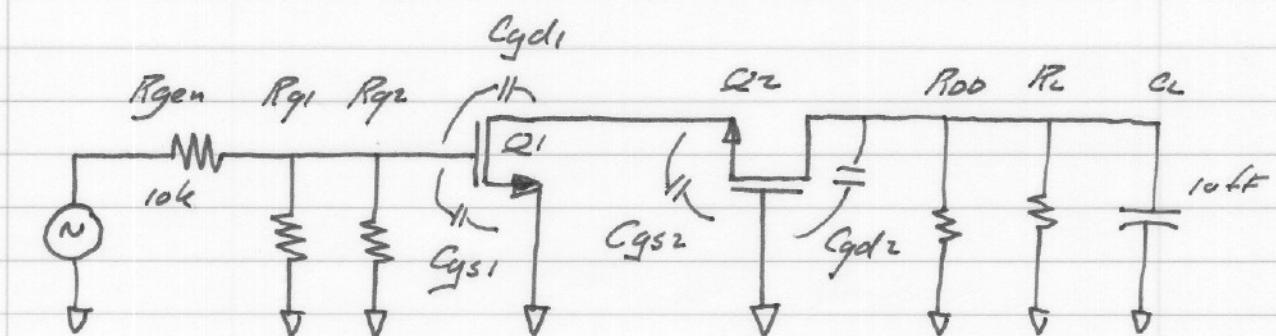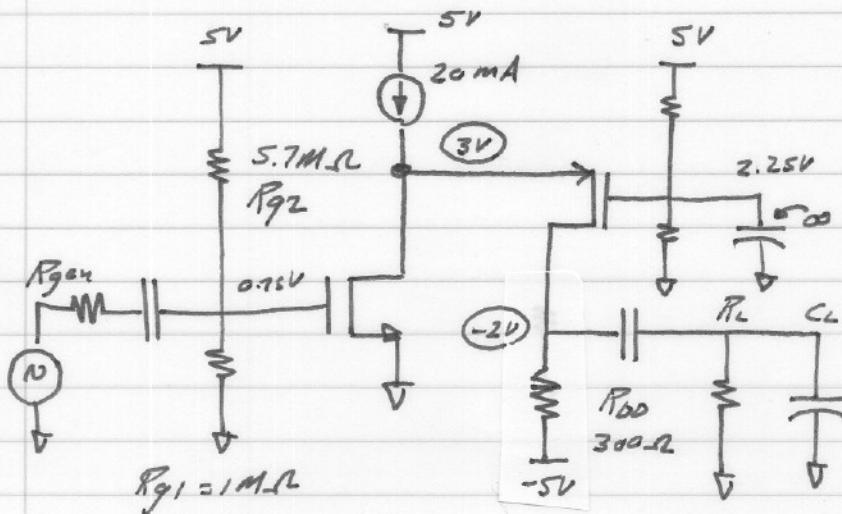(4)

Compare to Cascode stage: (use same #'s for PMOSFET)



Mid-band analysis

$$C_{gs} = 40 \text{ fF}$$

$$C_{gd} = 10 \text{ fF}$$

$$Q_2: R_{load} = R_{dd} // R_L = 231\Omega$$

$$R_{in} = 1/g_m = 50\Omega$$

$$Av = R_{load} / R_{in} = 4.62$$

$$Q_1: R_{load} = R_{in2} = 50\Omega$$

$$Av = -g_m R_{load} = -1$$


$$R_i = R_{gen} // R_{g1} // R_{g2} = 9.9 k\Omega$$

$$V_{in} / V_{gen} = 0.99$$

$$\rightarrow V_o / V_{gen} = -4.6$$

(5)

High Frequency analysis:

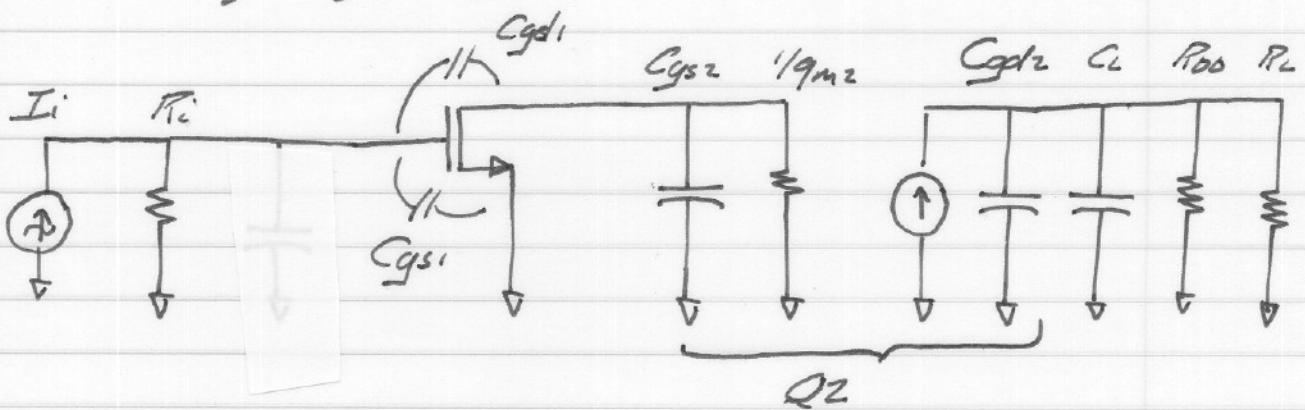

Part 1 of problem can be completely separated from part 2 of problem.

Part 1

$$\frac{a_1}{a_1} = R_i (C_{gs1} + C_{gd1} (R_i (1 - \alpha_m) + 1/g_m2) + C_{gs2} \cdot 1/g_m2 \\ = 396 \text{ ps} + 198 \text{ ps} + 2 \text{ ps} = 596 \text{ ps}$$

$$a_2 = R_i \cdot (1/g_m2) [C_{gs1} C_{gd1} + C_{gs1} C_{gs2} + C_{gd1} C_{gs2}] \\ = 1.19 (10^{-12}) \text{ sec}^2 \\ = (34.5 \text{ ps})^2$$

$$\text{SPA: } f_{p1} \approx 1/2\pi a_1 = 266 \text{ MHz.}$$

$$f_{p2} \approx a_1 / 2\pi a_2 = 80.6 \text{ Hz.}$$


Part 2 $a_1 = (C_{gd2} + C_L) (R_o || R_L) = 4.6 \text{ ps}$

$$f_p = 1/2\pi a_1 = 34 \text{ GHz.}$$

Cascode stage has eliminated (no-reduced) Miller multiplication of $C_{gd1} \rightarrow$ increased bandwidth

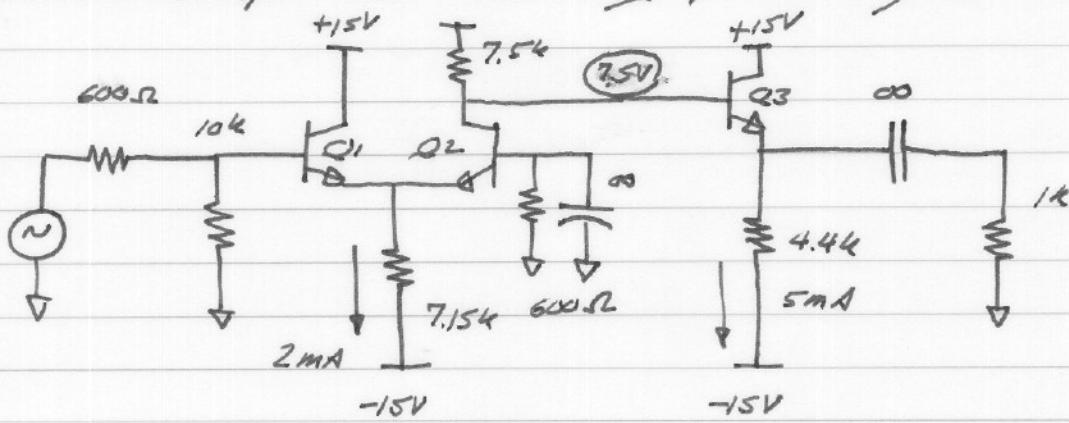(6)

Second example - this illustrating partitioning at C.R.B. stage



Transistors are typical of those used in the lab,
~1000:1 slower than state of art BJTs circa 2004.

$f_T = 350 \text{ MHz}$

$$T_f = 0.5 \text{ ns}, \beta = 100, C_{cs} = 4 \text{ pF}, C_{je} = 4 \text{ pF}, V_A = 100 \text{ V}$$

$$\text{use } C_{be} = g_m T_f + C_{je} ; \quad g_m = 1/r_e = I_c / V_T$$

	I_c	r_e	g_m	T_f	C_{cs}	C_{be}
Q1	1mA	26Ω	38mS	223 MHz	4pF	23pF

Q2	1mA	26	38mS	223 MHz	4pF	23pF
----	-----	----	------	---------	-----	------

Q3	5mA	5.2	192mS	293 MHz	4pF	100pF
----	-----	-----	-------	---------	-----	-------

Q4 1mA

$$f_T \text{ from } g_m / 2\pi(C_{cs} + C_{be})$$

(7)

Moc band analysis

$$\underline{Q3:} \quad R_{leg3} = 1k \parallel 4.4k = 815\Omega$$

$$Av_3 = R_{leg3} / (R_{leg3} + r_{e3}) = 0.994 \leftarrow \text{Don't round!!}$$

$$R_{in3} = \beta (R_{leg3} + r_{e3}) = 82.3k\Omega$$

$$\underline{Q2:} \quad R_{leg2} = 82.3k \parallel 7.5k = 6.9k\Omega$$

$$R_{in2} = r_{e2} = 26\Omega$$

$$Av_2 = 6.9k / 26\Omega = 264$$

$$\underline{Q1:} \quad R_{leg1} = r_{e2} \parallel 7.5k \approx r_{e2} = 26\Omega$$

$$Av_1 = r_{e2} / (r_{e2} + r_{e1}) = 1/2$$

$$R_{in1} = (\beta)(26 + 26\Omega) = 5.2k\Omega$$

$$R_{inA} = R_{in1} \parallel 10k = 3.4k$$

$$R_i = R_{inA} \parallel R_{gen} = 510\Omega$$


$$\underline{\text{Input}} \quad V_{in} / V_{gen} = R_{inA} / (R_{inA} + R_{gen}) = 0.85$$

Overall gain


$$No / V_{gen} = 0.85 \cdot 1/2 \cdot 264 \cdot 0.994 = 112$$

(8)


High Frequency analysis

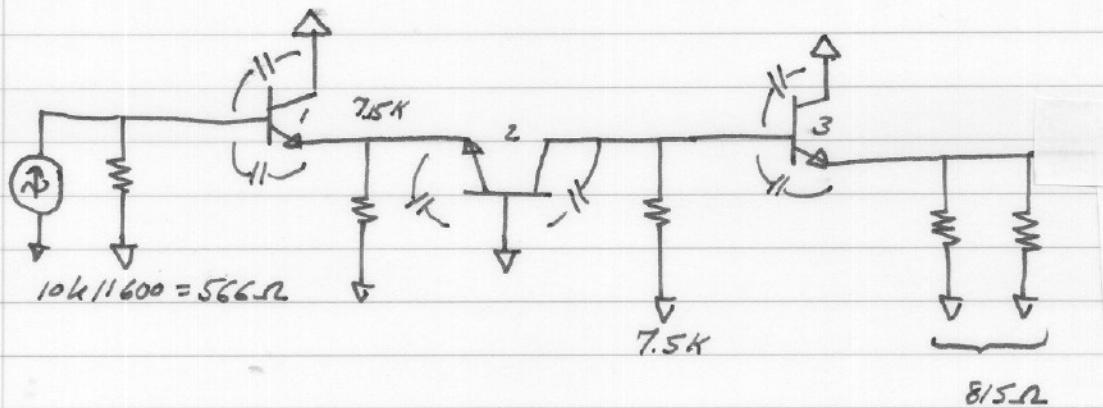

Note g₂ common-base T model:

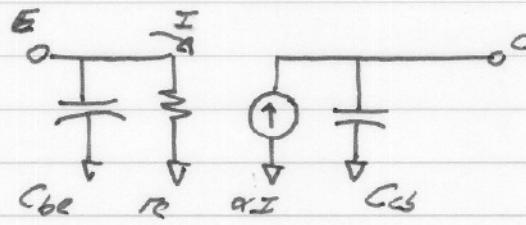

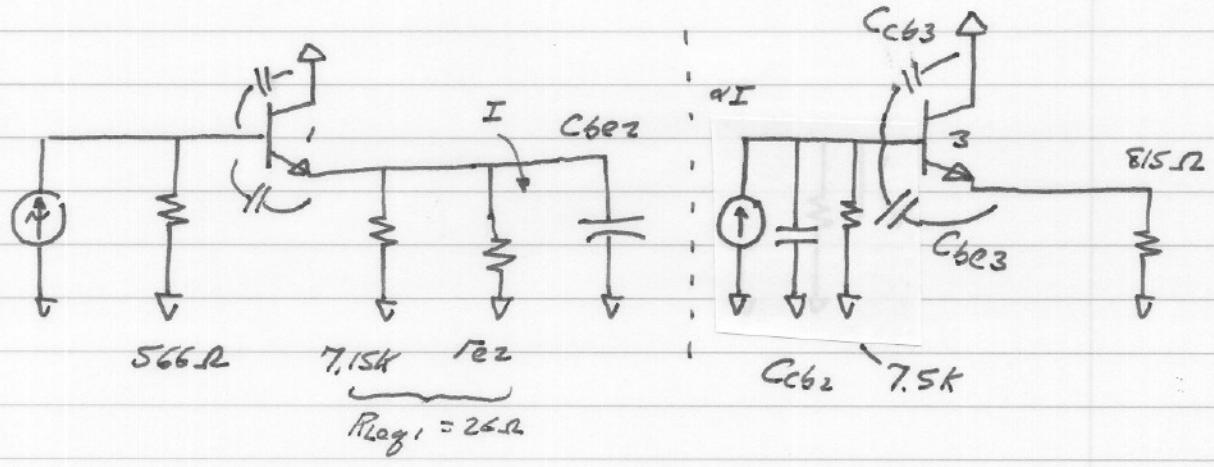Overall Model: can be separated into 2 parts



Part A: We have the choice of substituting into the E.F. gain expressions we have derived, or of doing more step-by-step. Let's do substitution:

$$\begin{aligned}
 a_1 &= C_{cb1} \left(R_i \parallel R_{in1} \right) + C_{be1} \left[R_{leg1} \parallel \left(r_{e1} + R_i / \beta \right) \right] \\
 &\quad + C_{be1} \left[\beta r_{e1} \parallel \left[R_i (1 - A_{v1}) + R_{leg1} \parallel \frac{1}{g_m1} \right] \right] \\
 &= 4\text{PF} \cdot 510\Omega + 23\text{PF} \left[26\Omega \parallel \left(26\Omega + \frac{566\Omega}{100} \right) \right] \\
 &\quad + 23\text{PF} \left[2.6k \parallel \left[566\Omega (1 - 1/2) + 26\Omega \parallel 26\Omega \right] \right] \\
 &= 2.04\text{ns} + 0.33\text{ns} + 6.11\text{ns} = 8.48\text{ns}
 \end{aligned}$$

$$\begin{aligned}
 a_2 &= \left(R_i \parallel R_{in1} \right) \left(R_{leg1} \parallel \frac{1}{g_m1} \right) \left[C_{be1} C_{cb1} + C_{be1} C_{be2} + C_{cb1} C_{be2} \right] \\
 &= (510\Omega)(13\Omega) \left[23\text{PF} \cdot 4\text{PF} + 23\text{PF} \cdot 23\text{PF} + 4\text{PF} \cdot 23\text{PF} \right] \\
 &= 4.7(10^{-18}) \text{sec}^2 = (2.17\text{ns})^2
 \end{aligned}$$


use SPA:

$$\left. \begin{aligned}
 f_{pi} &\approx 1/2\pi G_1 = 18.7 \text{MHz} \\
 f_{pz} &\approx a_1 / 2\pi G_2 = 286 \text{MHz}
 \end{aligned} \right\} \begin{array}{l} \text{use of SPA a little risky} \\ \text{here: ok if 10:1 separation.} \end{array}$$

There is also a zero @ $f_3 = g_m / 2\pi C_{be} = 260 \text{MHz}$.

(10)

Part B Let's work this by MOTC:

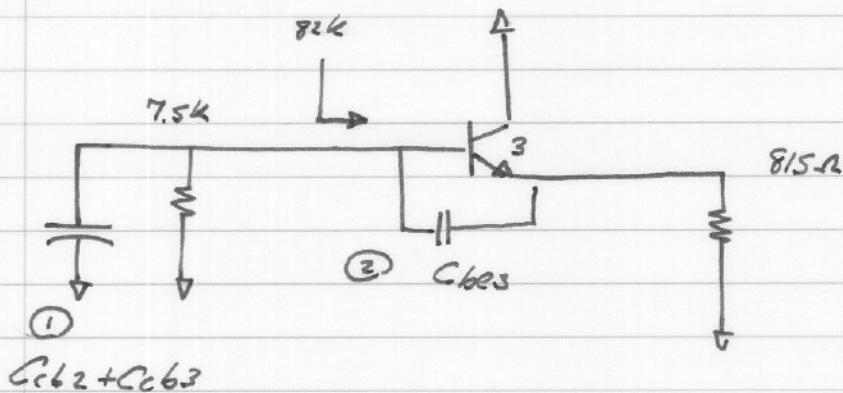

$$a_1 = R_{11}^o C_1 + R_{22}^o C_2$$

$$\text{Charging resistance for } C_1 : 7.5k \parallel 82k = R_{\text{charge}} = 6.9k$$

$$R_{11}^o C_1 = 6.9k \cdot 8\text{pF} = 55.2 \text{ nS}$$

$$\begin{aligned} \text{Charging resistance for } C_2 : & \left\{ 7.5k [1 - A_{v3}] + r_{e3} \parallel 815\Omega \right\} \parallel \beta r_{e3} \\ & = \left\{ 7.5k (1 - 0.994) + 5.2 \parallel 815 \right\} \parallel 520\Omega \end{aligned}$$

$$= 45.7\Omega$$

$$R_{22}^o C_2 = 45.7\Omega \cdot 100\text{pF} = 4.57\text{nS}$$

$$\rightarrow a_1 = 60 \text{ nS}$$

$$a_2 = R_{11}^o C_1 C_2 R_{22}' = 6.9k \cdot 8\text{pF} \cdot 100\text{pF} \cdot 5.1\Omega = 2.8(10^7)\text{s}^{-1}$$

$$= (5.3\text{nS})^2$$

$$R_{22}' = 5.2 \parallel 815 \parallel 520\Omega = 5.1\Omega$$

use SPA again

$$f_{p1} \approx 1/2\pi a_1 = 2.65\text{MHz}$$

$$f_{p2} \approx a_1 / 2\pi a_2 = 340\text{MHz}; \text{ also a zero @ } f_c = g_m / 2\pi C_{6e3} = 305\text{MHz}$$


(11)

Part A poles: 18.7 MHz, 286 MHz

zero: 260 MHz


Part B. poles: 2.65 MHz, 340 MHz

zero: 305 MHz.

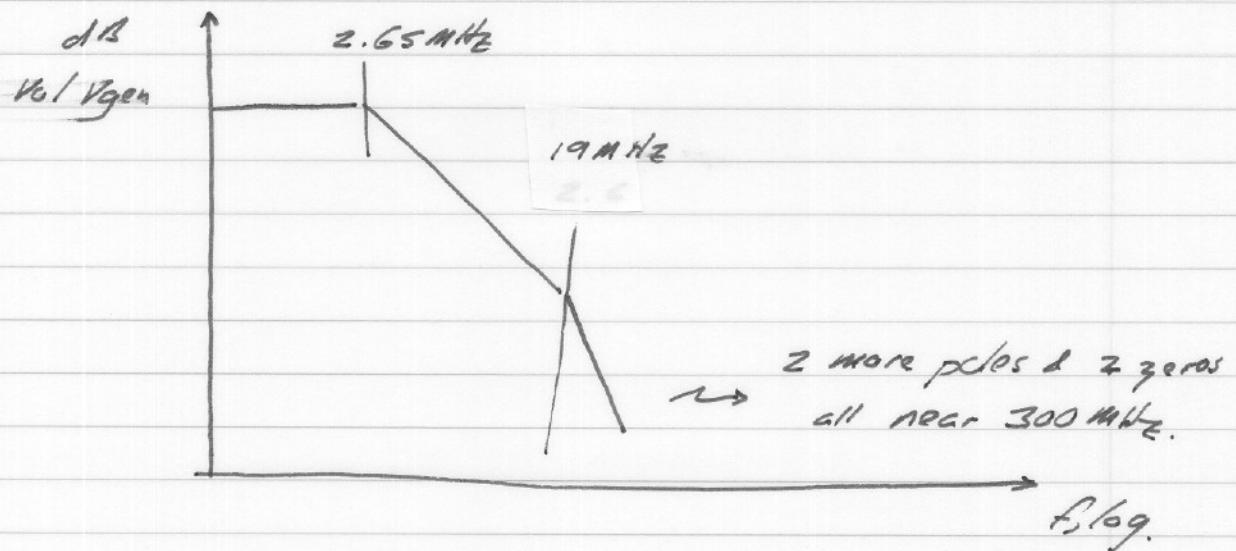


Now lets look at a very approximate
way of estimating bandwidth very quickly

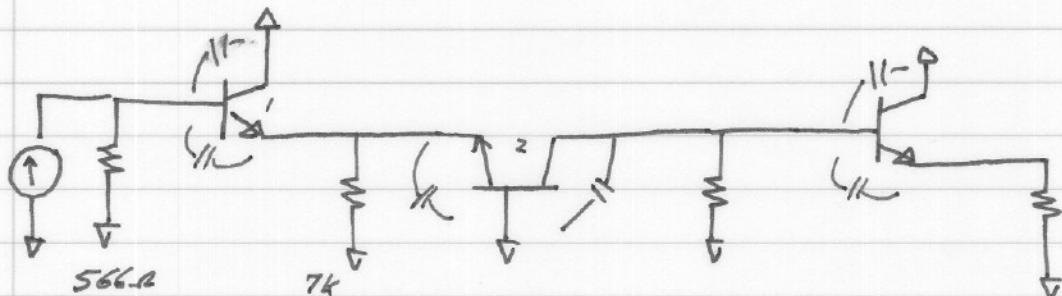use of Miller Approximations Node-by-Node.



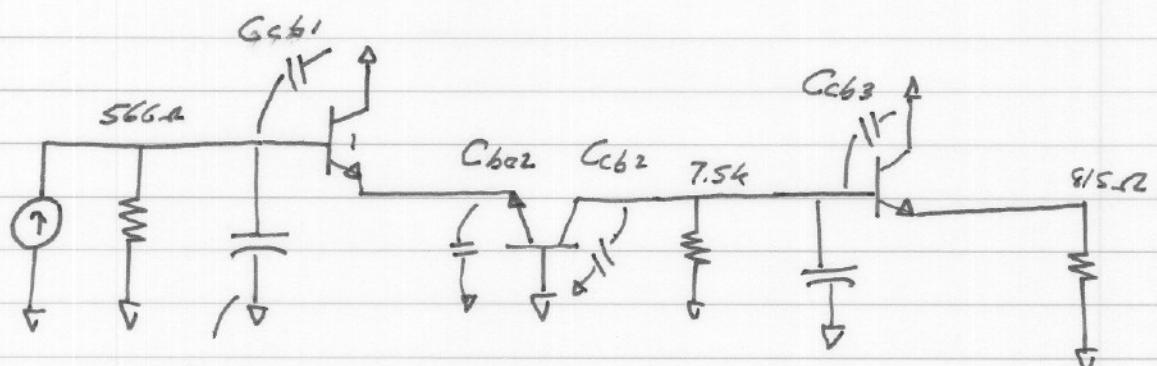Replace each capacitor not-to-ground with a Miller capacitor $C(1-A) = C_{Miller}$.



$$C_{Miller_1} = C_{be1}(1 - A_{v1}) = 11.5 \text{ pF}$$

$$= C_{be3}(1 - A_{v3}) = 0.6 \text{ pF}$$

We can now calculate time constants node by node

(13)

Node: base of Q1

$$R = 566\Omega \parallel R_{in1} = 510\Omega$$

$$C = C_{C61} + C_{Miller1} = 4\text{pF} + 11.5\text{pF} = 15.5\text{pF}$$

$$T = RC = 7.9\text{ns}$$

$$f_p = 1/2\pi T = 20.1\text{MHz} \quad \leftarrow$$

Node: emitter of Q1

$$R = r_{o61} \parallel R_{in2} = (566\Omega/\beta + r_{e1}) \parallel r_{e2} = 14.3\Omega$$

$$C = C_{be2} = 23\text{pF}$$

$$T = RC = 328\text{ps}$$

$$f_p = 1/2\pi T = 484\text{MHz}.$$

Node: collector of Q2

$$R = 7.5k \parallel R_{in3} = 6.9k$$

$$C = C_{C63} + C_{Miller2} = 4\text{pF} + 0.6\text{pF} = 4.6\text{pF}$$

$$T = RC = 31.7\text{ns}$$

$$f_p = 1/2\pi T = 5.0\text{MHz}.$$

Node: emitter of Q3: no capacitances.

This method gave poles at 5 & 20MHz & at 484MHz.

One pole & 2 zeros have been lost.

Method is good for quick checks when doing designs,
but usually gets $\alpha_2/2\pi\alpha_1$ pole wrong by vast amount.