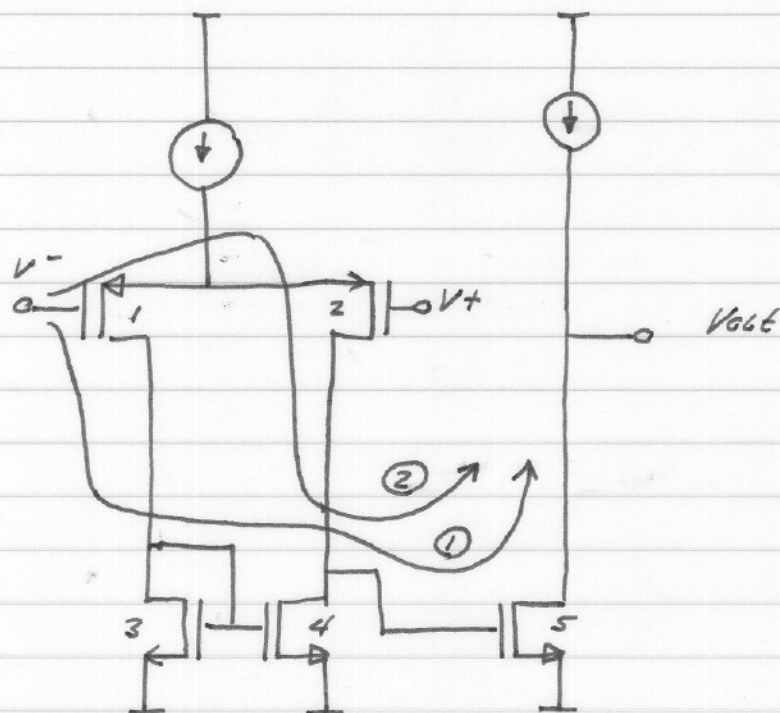


ECE137B Multistage example: notes set 9



This is a simplified MOSFET op-AMP.

There are 2 paths, ① & ②, from V^- to output.


If there are 2 such paths, then

$$\frac{V_{out}}{V^-} = A_{dc1} \frac{1 + b_1 A + b_2 A^2 + \dots}{1 + g_1 A + g_2 A^2 + \dots} \Big|_{\text{path 1}} + A_{dc2} \frac{1 + \tilde{b}_1 A + \tilde{b}_2 A^2}{1 + \tilde{g}_1 A + \tilde{g}_2 A^2} \Big|_{\text{path 2}}$$

lets solve both these paths.


Recall: op-amps are analyzed assuming $v_{out} = 0V$.

HF analysis; path 1

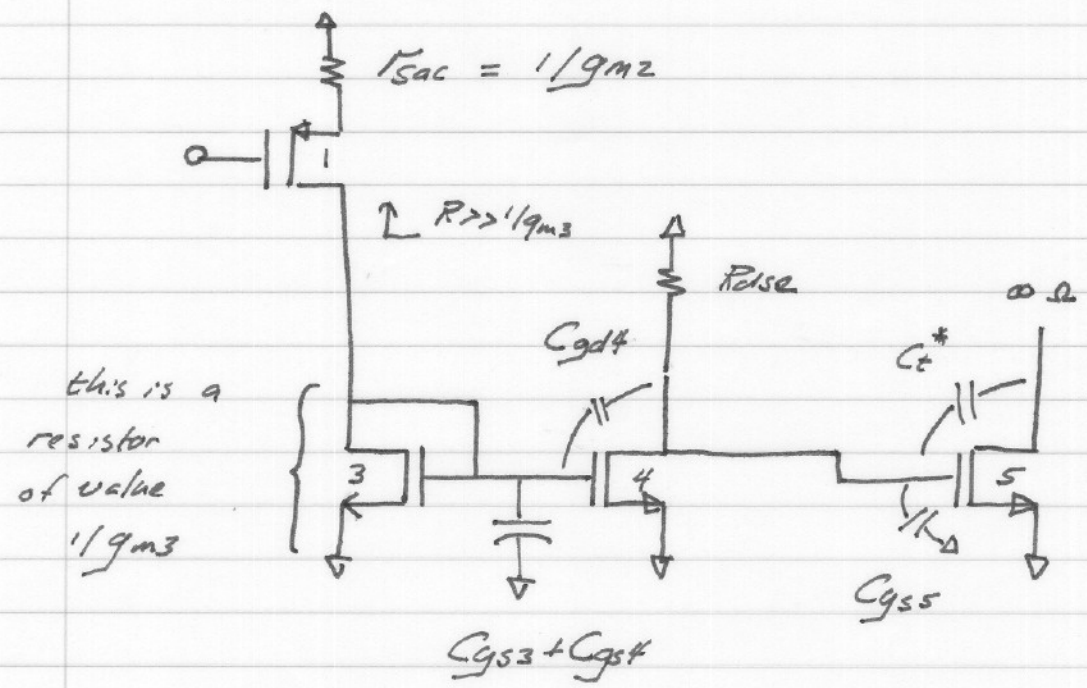

$C_t = C_{gs5} + C_c \Rightarrow$ pick C_c so that $C_t = 160 \text{ fF}$

160

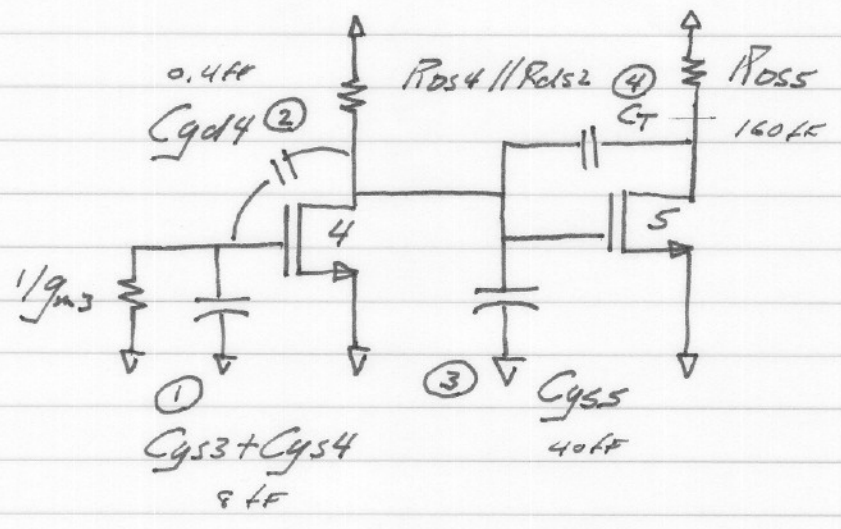

(4)

first calculate $a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 + R_{33}^0 C_3 + R_{44}^0 C_4$

$$\frac{R_{11}^0 C_1}{R_{11}^0 = 1/g_{m3}, C_1 = C_{gs3} + C_{gs4} \rightarrow R_{11}^0 C_1 = 4 \text{ ps}}$$

$R_{22}^0 C_2$

$$C_2 = C_{gd4} = 0.4 \text{ fF} \quad R_{22}^0 = (1/g_{m3}) (1 + g_{m4} \cdot R_{ds4} \parallel R_{ds2}) + R_{ds4} \parallel R_{ds2}$$

$$= 5.5 \text{ k}\Omega + 5 \text{ k}\Omega = 10.5 \text{ k}\Omega$$

$$R_{22}^0 C_2 = 4.2 \text{ ps}$$

$R_{33}^0 C_3$

$$R_{33}^0 = R_{ds4} \parallel R_{ds2} = 5 \text{ k}\Omega, C_3 = C_{gs5} = 40 \text{ fF}$$

$$\rightarrow R_{33}^0 C_3 = 200 \text{ ps}$$

$R_{44}^0 C_4$

$$R_{44}^0 = (R_{ds4} \parallel R_{ds2}) (1 + A_{vs}) + R_{ds5}$$

$$= 5 \text{ k}\Omega (1 + 20) + 1 \text{ k}\Omega = 106 \text{ k}\Omega$$

$$C_4 = 160 \text{ fF}$$


$$\rightarrow R_{44}^0 C_4 = 17.0 \text{ ns}$$

$$a_1 = \text{sum of these terms} = 17.2 \text{ ns}$$


$$f_{p1} = 1/2\pi a_1 = 9.2 \text{ MHz} \quad \text{assuming SPA will hold}$$

Now calculate a_2

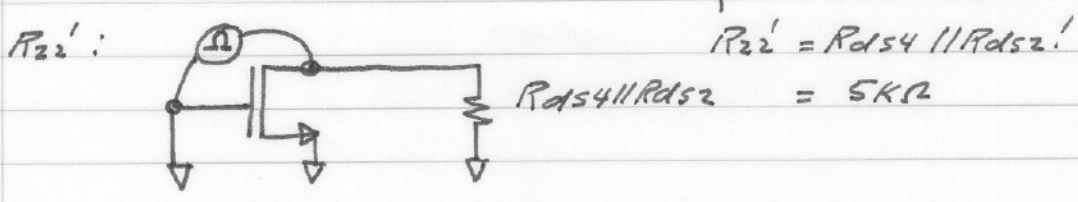
$$\underline{R_{11}^0 C_1 C_2 R_{22}^1} = 500\Omega \cdot 8fF \cdot 0.4fF \cdot 5K\Omega = 8 \cdot 10^{-24} \text{ Sec}^2$$



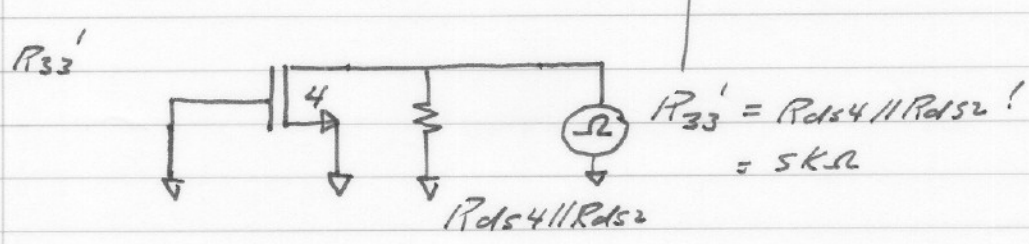
$$\underline{R_{11}^0 C_1 C_3 R_{33}^1} = 500\Omega \cdot 8fF \cdot 40fF \cdot 5K\Omega = 8 \cdot 10^{-22} \text{ Sec}^2$$



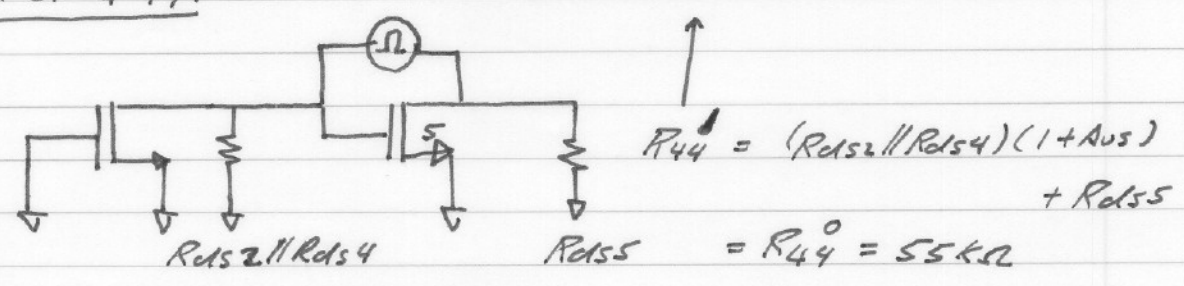
$$\underline{R_{11}^0 C_1 C_4 R_{44}^1} = 500\Omega \cdot 8fF \cdot 160fF \cdot 55K\Omega = 3.52 \cdot 10^{-20} \text{ Sec}^2$$


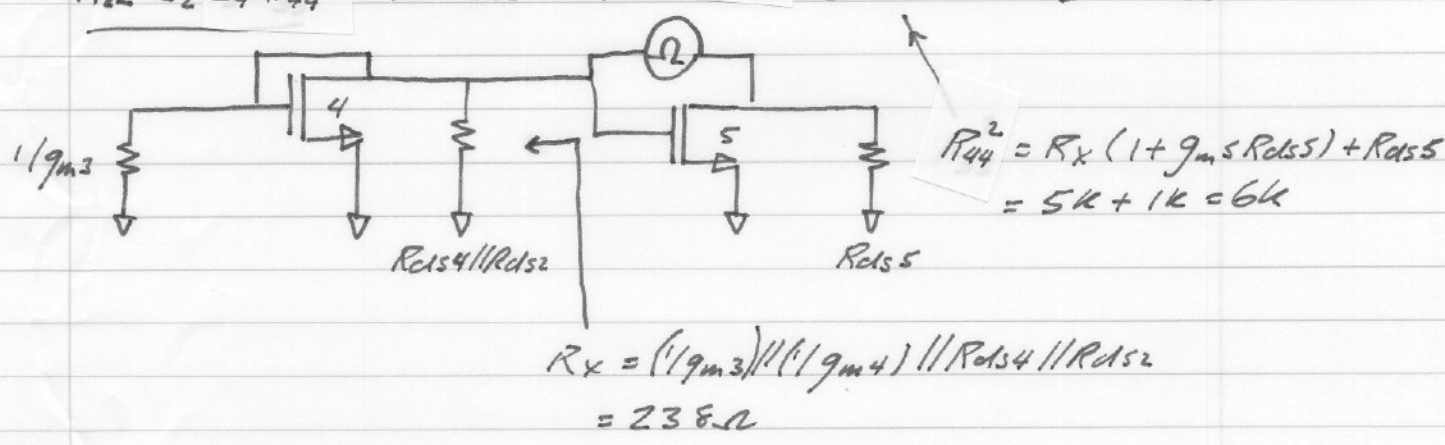
$$\underline{R_{22}^0 C_2 C_4 R_{44}^2} = 10.5K\Omega \cdot 0.4fF \cdot 160fF \cdot 6K\Omega = 4.03 \cdot 10^{-21} \text{ Sec}^2$$



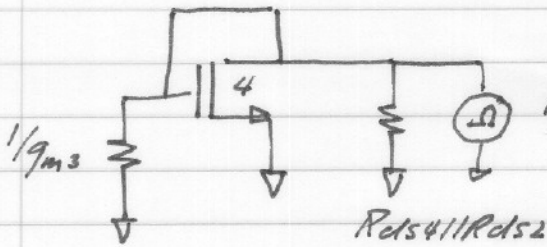
$$R_{22}^0 C_2 C_3 R_{33}^2 = 10.5 \text{ k}\Omega \cdot 0.4 \text{ pF} \cdot 40 \text{ fF} \cdot 238 \Omega = 4.0 \cdot 10^{-23} \text{ sec}^2$$



$$R_{33}^2 = \frac{1}{g_{m3}} \parallel \frac{1}{g_{m4}} \parallel R_{ds4} \parallel R_{ds2} = 238 \Omega$$
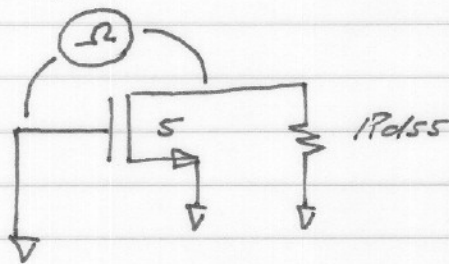
$$R_{33}^0 C_3 C_4 R_{44}^3 = 5 \text{ k}\Omega \cdot 40 \text{ fF} \cdot 160 \text{ fF} \cdot 1 \text{ k}\Omega = 3.2 \cdot 10^{-20} \text{ sec}^2$$



$$R_{44}^3 = R_{ds5} = 1 \text{ k}\Omega$$


$$a_2 = \text{sum of terms} = 7.26 \cdot 10^{-20} \text{ sec}^2 = (0.27 \text{ ns})^2$$

SPA:

$$f_{p1} \approx \frac{1}{2\pi a_1} = \frac{1}{2\pi (17 \text{ ns})} = 9.2 \text{ MHz}$$



↓ SPA works.
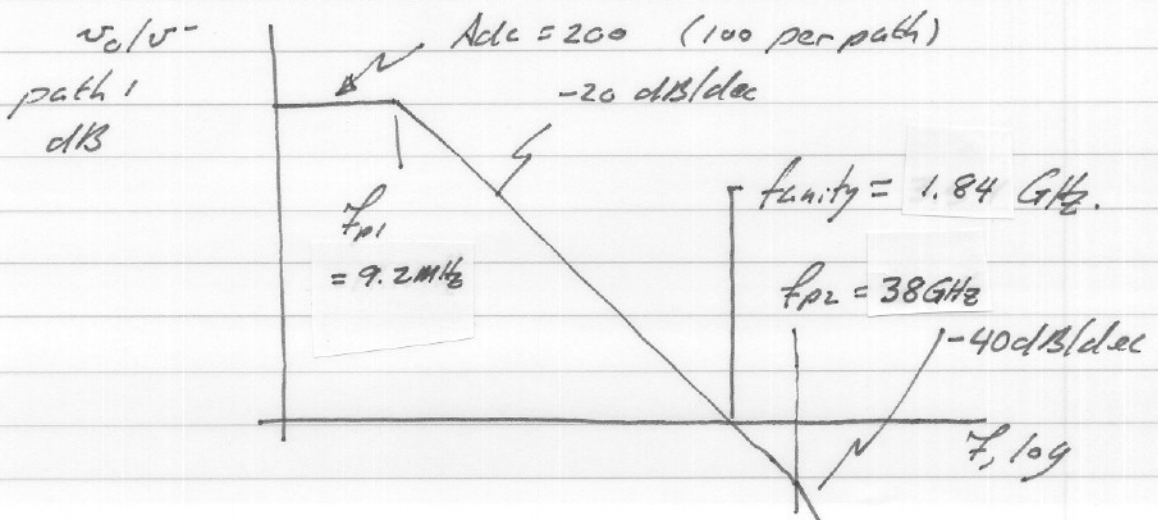
$$f_{p2} \approx \frac{a_1}{2\pi a_2} = 37.5 \text{ GHz}$$



HF Analysis; path 2


$C_T = 160 \text{ fF}$

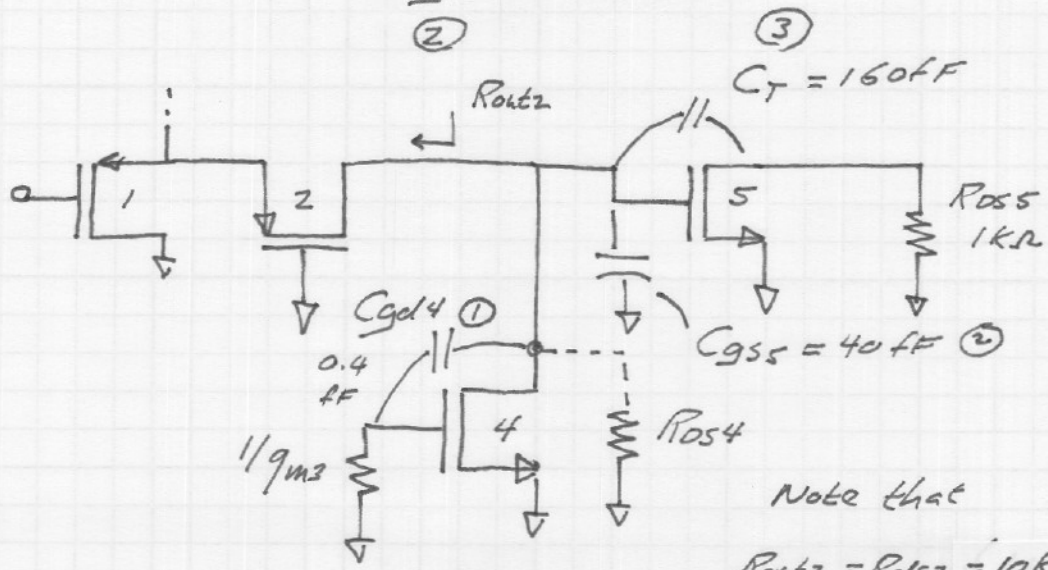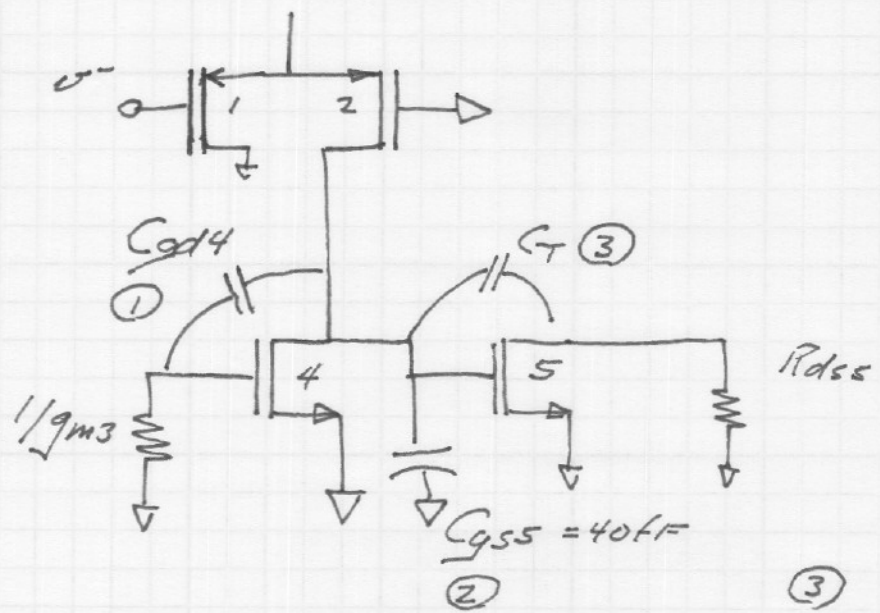

Note that
 $R_{out2} = R_{ds2} = 10 \text{ k}\Omega$ (p. 4)
 $= 20 \text{ k}\Omega$

now find $a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 + R_{33}^0 C_3$


$R_{11}^0 C_1$

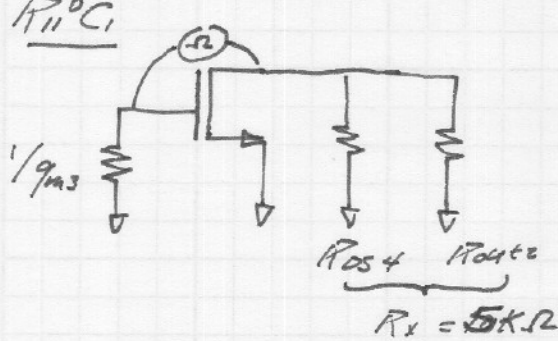

$R_{11}^0 C_1 = 0.4 \text{ fF} \cdot 10.5 \text{ k}\Omega = 4.2 \text{ ps}$


$R_{11}^0 = (1/g_{m3})(1 + g_{m4} R_x) + R_x = 10.5 \text{ k}\Omega$

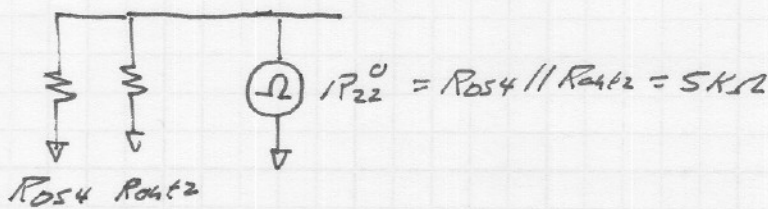$R_{22}^0 C_2 = 5 \text{ k}\Omega \cdot 40 \text{ fF} = 200 \text{ ps}$



$R_{22}^0 = R_{ds4} \parallel R_{ds2} = 5 \text{ k}\Omega$

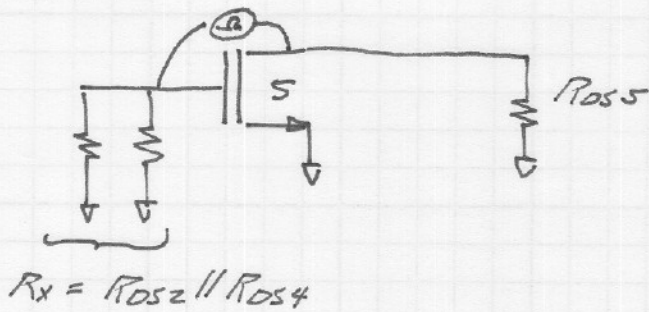$R_{33}^0 C_3 = 106 \text{ k}\Omega \cdot 160 \text{ fF} = 17 \text{ ns}$




$R_{33}^0 = R_x (1 + A_{vs}) + R_{ds5} = 106 \text{ k}\Omega$

$R_x = R_{ds2} \parallel R_{ds4}$

$a_1 = \text{sum of these} = 17.2 \text{ ns} \leftarrow \text{same as for other path.}$


$$a_2 = R_{11}^0 C_1 C_2 R_{22}' + R_{11}^0 C_1 C_3 R_{33}' + R_{22}^0 C_2 C_3 R_{33}^2$$
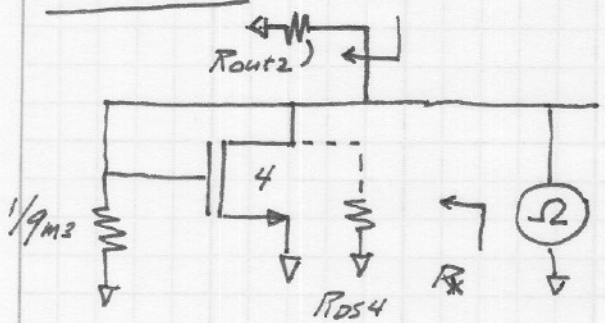
$$R_{11}^0 C_1 C_2 R_{22}' = 10.5 \text{ k}\Omega \cdot 0.4 \text{ fF} \cdot 40 \text{ fF} \cdot 238 \Omega = 4.0 \cdot 10^{-23} \text{ sec}^2$$




$$R_{22}' = R_x = R_{out2} \parallel \frac{1}{g_{m3}} \parallel \frac{1}{g_{m4}} \parallel R_{DS4} = 238 \Omega$$
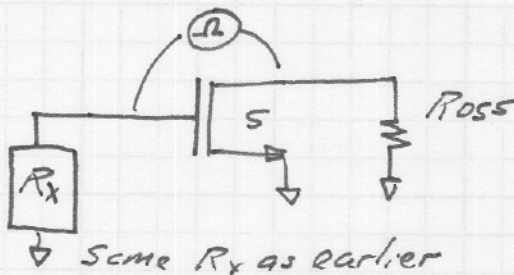
$$R_{11}^0 C_1 C_3 R_{33}' = 10.5 \text{ k}\Omega \cdot 0.4 \text{ fF} \cdot 160 \text{ fF} \cdot 6 \text{ k}\Omega = 4.03 \cdot 10^{-21} \text{ sec}^2$$



$$R_{33}' = R_x (1 + g_{m5} R_{DS5}) + R_{DS5} = 6 \text{ k}\Omega$$
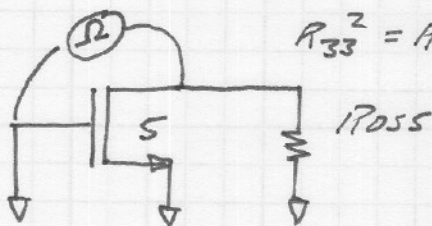
$$R_{22}^0 C_2 C_3 R_{33}^2 = 5 \text{ k}\Omega \cdot 40 \text{ fF} \cdot 160 \text{ fF} \cdot 1 \text{ k}\Omega = 3.2 \cdot 10^{-20} \text{ sec}^2$$



$$R_{33}^2 = R_{DS5} = 1 \text{ k}\Omega$$

$$a_2 = \text{sum of terms} = 3.6 (10^{-20}) \text{ sec}^2 = (190 \text{ ps})^2$$

$$f_{p1} \approx 1/2\pi a_1 = 9.2 \text{ MHz} \quad \text{assuming SPA}$$

$$f_{p2} \approx a_1/2\pi a_2 = 76 \text{ GHz}$$

Note that both paths have the same dominant pole, but secondary pole is at higher frequency in path 2.