

Problem 1: Ignore DC bias analysis. You don't need it. The two transistors have transconductance g_{m1} and g_{m2} and respectively. Their output resistances R_{ds1} and R_{ds2} are both infinity, while the transistor capacitances $C_{gs} = C_{gd} = 0$.

a) Draw a small-signal equivalent circuit of the circuit

(b) USING NODAL ANALYSIS, compute $V_{out}(s)/V_{in}(s)$ in ratio-of-polynomials form

$$V_{out}(s)/V_{in}(s) = A_{v,mid-band} \times (s\tau)^m \times \frac{1+b_1s+b_2s^2+\dots}{1+a_1s+a_2s^2+\dots}$$


here m, an integer, can be positive or negative or zero.

(b) Now set $g_{m1}=1$ mS. $g_{m2}=2$ mS. $R_F=10$ kOhm. $C_1=100$ fF

c) Find any/all pole and zero frequencies of the transfer function, in Hz:

d) Draw a clean Bode Plot of $\|V_{out}\|/\|V_{in}\|$ in dB vs. frequency (log scale)

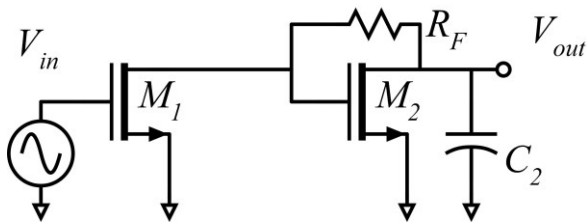LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes



Problem 2: Ignore DC bias analysis. You don't need it. The two transistors have transconductance g_{m1} and g_{m2} respectively. Their output resistances R_{ds1} and R_{ds2} are both infinity, while the transistor capacitances $C_{gs} = C_{gd} = 0$.

a) Draw a small-signal equivalent circuit of the circuit

(b) USING NODAL ANALYSIS, compute $V_{out}(s)/V_{in}(s)$ in ratio-of-polynomials form

$$V_{out}(s)/V_{in}(s) = A_{v,mid-band} \times (s\tau)^m \times \frac{1+b_1s+b_2s^2+\dots}{1+a_1s+a_2s^2+\dots}$$


here m, an integer, can be positive or negative or zero.

(b) Now set $g_{m1}=1$ mS. $g_{m2}=2$ mS. $R_F=10$ kOhm. $C_2=200$ fF

c) Find any/all pole and zero frequencies of the transfer function, in Hz:

d) Draw a clean Bode Plot of $\|V_{out}\|/\|V_{in}\|$ in dB vs. frequency (log scale)

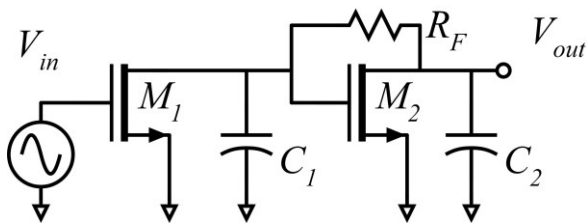LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes



Problem 3: Ignore DC bias analysis. You don't need it. The two transistors have transconductance g_{m1} and g_{m2} respectively. Their output resistances R_{ds1} and R_{ds2} are both infinity, while the transistor capacitances $C_{gs} = C_{gd} = 0$.

a) Draw a small-signal equivalent circuit of the circuit

(b) USING NODAL ANALYSIS, compute $V_{out}(s)/V_{in}(s)$ in ratio-of-polynomials form

$$V_{out}(s)/V_{in}(s) = A_{v,mid-band} \times (s\tau)^m \times \frac{1+b_1s+b_2s^2+\dots}{1+a_1s+a_2s^2+\dots}$$


here m, an integer, can be positive or negative or zero.

(b) Now set gm1=1 mS. gm2=2 mS. RF=10 kOhm. C1=100 fF, C2=200 fF

c) Find any/all pole and zero frequencies of the transfer function, in Hz:

d) Draw a clean Bode Plot of ||Vout||/||Vin|| in dB vs. frequency (log scale)

LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes

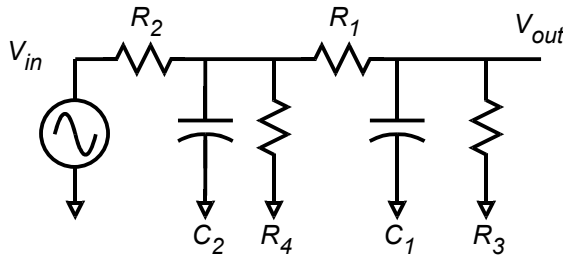

Problem 4: R1=2 KOhm, R2=3kOhm,
R3=4kOhm, R4=8 kOhm, C1= 1 fF
C2=2 fF

Using Nodal analysis , find the transfer function Vout(s)/Vgen(s). Give the answer in standard form

$$\frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}} \bigg|_{DC} \frac{1+b_1s+b_2s^2+\dots}{1+a_1s+a_2s^2+\dots}$$