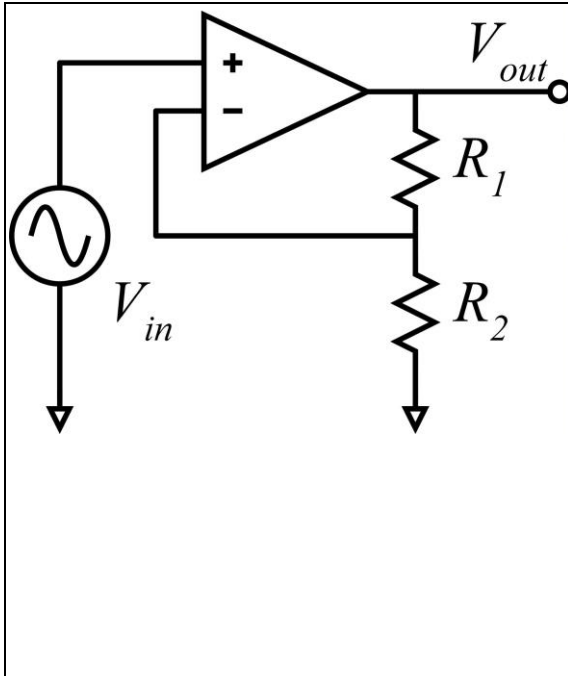


	<p>Problem 1</p> <p>a) The operational amplifier has infinite input impedance, zero output impedance, infinite common-mode rejection ratio, and a differential gain of $A_{diff}=10,000$. $R_1=9k\Omega$, $R_2=1k\Omega$. Find the gain V_{out}/V_{in}. (b) Now suppose that the op-amp has a differential input impedance of $100 k\Omega$. Find the closed-loop input impedance</p> <p>c) The differential amplifier has an output impedance of 10Ω (but infinite input impedance). Find the closed-loop output impedance.</p>
	<p>Problem 2</p> <p>The operational amplifier has zero output impedance, infinite common-mode rejection ratio, and a differential gain of $A_{diff}=10,000$. $R_1=9k\Omega$, $R_2=1k\Omega$. The amplifier's differential input is only 90Ω. Find the gain V_{out}/V_{in}. Hint: this requires use of the relationship $A_{cl} = A_{\infty} \frac{T}{1+T}$</p>
	<p>Problem 3. Feedback amplifier stability analysis by the Bode method. The operational amplifier has a differential gain of 10^6 at DC. Its differential gain has three poles, one at 10 Hz, and two at 5 MHz. The amplifier is otherwise ideal (infinite input impedance, zero output impedance, infinite CMRR). We will consider 2 cases: a) $R_1=0$ and $R_2=1k\Omega$ b) $R_1=9k\Omega$ and $R_2=1k\Omega$.</p> <p>In each of cases a), and b) do the following:</p> <ul style="list-style-type: none"> • Draw Bode plots (Magnitude and phase) of $A_d(f)$ and $\beta(f)$ • Find the loop bandwidth and estimate from this the bandwidth of V_{out}/V_{in}. • Find the gain margin and the phase margin of the feedback loop. Is the amplifier stable?



Problem 4
 Stability analysis: the Root Locus
 The operational amplifier has a differential gain of 10^6 at DC. Its differential gain has **two** significant poles, one at 10 Hz, and one at 1 MHz. The amplifier is otherwise ideal (zero output impedance, infinite input impedance, infinite CMRR). Consider 2 cases: a) $R_1=0$ and $R_2=1\text{k}\Omega$ b) $R_1=9\text{k}\Omega$ and $R_2=1\text{k}\Omega$. In each of cases a), and b) do the following:
 Solve mathematically for $V_{out}(s)/V_{gen}(s)$
 Find the natural frequency, the damped frequency, and the damping factor
 Draw to scale the location of the poles of $V_{out}(s)/V_{gen}(s)$ on the S-plane.
 Graph the (amplitude) of $V_{out}(j\omega)/V_{gen}(j\omega)$
 Graph the step response of the amplifier $V_{out}(t)$ given $V_{in}(t)=1\text{V}\cdot U(t)$