

Transistor small-signal high-frequency models: Hybrid-pi model (simplified)		
	$f_\tau = g_m / (2\pi(C_{gs} + C_{gd}))$ Expressions for $g_m$ , $C_{gs}$ etc depend on whether velocity-limited or mobility-limited. $R_{DS} = (1/\lambda + V_{DS})/I_D$	
	$C_{be} = C_{je} + g_m \tau_f$ $C_{je}$ = base-emitter depletion capacitance $\tau_f$ = forward (base+collector) transit time $g_m = qI_E/kT$ $R_{be} = (1+\beta)/g_m$ $\alpha = \beta/(\beta+1)$ $R_{ce} = (V_A + V_{CE})/I_C$ $f_\tau = g_m / (2\pi(C_{be} + C_{cb}))$	
Common-gate/base T-models (easier common base/gate analysis if $R_{CE}/R_{DS} \rightarrow \infty$ )		
Simplification of source and emitter degeneration		
		Note: $C_{cb}$ , not $C'_{cb}$
		Note: $C_{gd}$ , not $C'_{gd}$
$C_{gs}/C'_{gs} = g_m / g'_m = R'_DS / R_{DS} = (1 + g_m R_{SS})$ $C_{be}/C'_{be} = g_m / g'_m = R'_{ce} / R_{ce} = R'_{be} / R_{be} = (1 + g_m R_{EE})$		

Exact iff  $R_{SS}C_{SS} = C_{gs}/g_m$  or  $R_{EE}C_{EE} = C_{be}/g_m$ ; approximate if  $C_{SS}, C_{EE} = 0$

### Common-source and common-emitter

	$V_{out}/V_{gen} = \left( V_{out}/V_{gen} \right)_{MB} \frac{1+b_1s}{1+a_1s+a_2s^2}$ $b_1 = -C_{gd/cb}/g_m$ $a_1 = C_{gs/be}R_i + C_{gd/cb}(R_i(1+g_mR_{Leq}) + R_{Leq}) + C_L R_{Leq}$ $a_2 = R_i R_{Leq} (C_{gs/be} C_{gd/cb} + C_{gs/be} C_L + C_{gd/cb} C_L)$
--	---

### Source-follower

	$V_{out}/V_{gen} = \left( V_{out}/V_{gen} \right)_{MB} \frac{1+b_1s}{1+a_1s+a_2s^2}$ <p>given that <math>A_{V,mb} = R_{Leq}/(R_{Leq} + 1/g_m)</math>:</p> $b_1 = C_{gs}/g_m$ $a_1 = C_{gd}R_i + C_{gs}(R_i(1-A_{V,mb}) + R_{Leq} \parallel g_m^{-1}) + C_L(R_{Leq} \parallel g_m^{-1})$ $a_2 = R_i(R_{Leq} \parallel g_m^{-1})(C_{gd}C_{gs} + C_{gd}C_L + C_{gs}C_L)$
--	---

### Emitter-follower

	$V_{out}/V_{gen} = \left( V_{out}/V_{gen} \right)_{MB} \frac{1+b_1s}{1+a_1s+a_2s^2}$ <p>given that <math>A_{V,mb} = R_{Leq}/(R_{Leq} + 1/g_m)</math>:</p> $b_1 = C_{be}/g_m$ $a_1 = C_{cb}(R_i \parallel R_{in,t}) + C_{be}\{(R_i(1-A_{V,mb}) + R_{Leq} \parallel g_m^{-1}) \parallel R_{be}\} + C_L(R_{Leq} \parallel R_{out,t})$ $a_2 = (R_i \parallel R_{in,t})(R_{Leq} \parallel g_m^{-1})(C_{be}C_{cb} + C_{be}C_L + C_{cb}C_L)$ <p>where <math>R_{in,t} = \beta(R_{Leq} + g_m^{-1})</math> and <math>R_{out,t} = g_m^{-1} + R_i/\beta</math></p>
--	--

**General Solutions of Problems: Nodal analysis (Know how to do this!)**

1) Write the nodal equations (sum of the currents=0) at each circuit node, and put the resulting equations in matrix form (the Y's being various combinations of gm's, 1/R's, 1/sL's, and sC's):

$$\begin{bmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} \end{bmatrix} \begin{bmatrix} V_{in} = V_1 \\ V_2 \\ V_3 \\ V_{out} = V_4 \end{bmatrix} = \begin{bmatrix} I_{in} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

2) Use Cramer's rule to solve

$$V_{out} = \frac{\begin{vmatrix} Y_{11} & Y_{12} & Y_{13} & I_{in} \\ Y_{21} & Y_{22} & Y_{23} & 0 \\ Y_{31} & Y_{32} & Y_{33} & 0 \\ Y_{41} & Y_{42} & Y_{43} & 0 \end{vmatrix}}{\begin{vmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} \end{vmatrix}}$$

3) This comes out as:

$$\frac{V_{out}}{I_{in}} = ks^m \frac{c_0 + c_1s + c_2s^2 + \dots}{d_0 + d_1s + d_2s^2 + \dots}$$

, which is divided through to get:

(if present, m is the number of zeros minus the number of poles, in the transfer function)




5) To find the impulse response, do a partial-fraction expansion and then take the inverse LaPlace transform

4)

$$\frac{V_{out}}{V_{gen}} = \left( \frac{V_{out}}{V_{gen}} \right)_{MB} \frac{1 + b_1s}{1 + a_1s + a_2s^2}$$

...and the poles and zeroes are found by factoring the numerator and denominator. The separated-pole approximation, if applicable, makes this factoring easy

6) To find the sinusoidal frequency response, set  $s = j\omega$

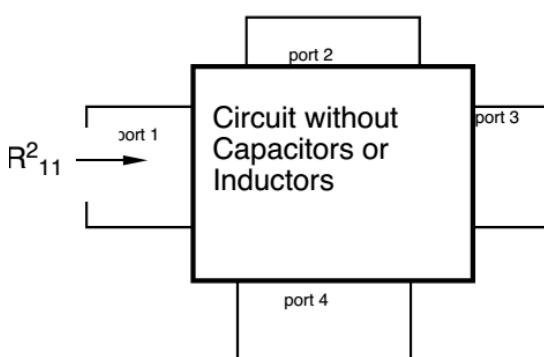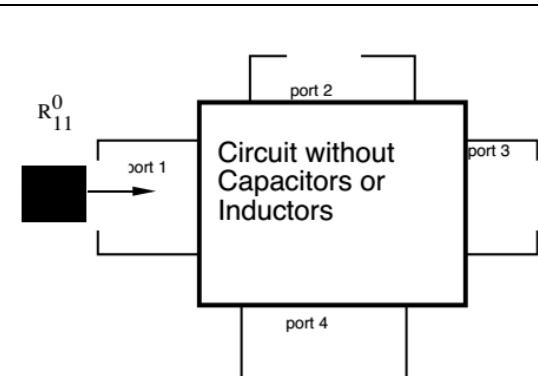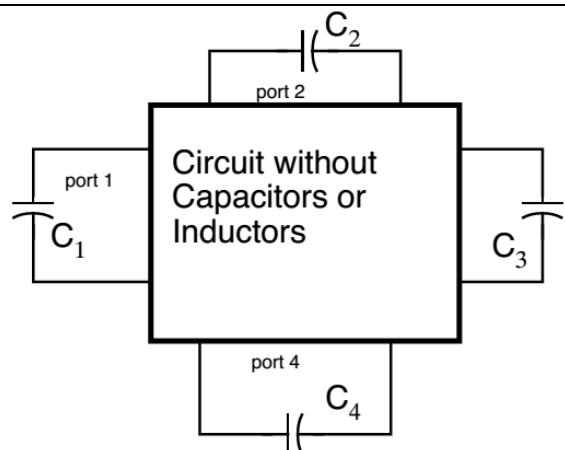**General Solutions of Problems: Method of Time Constants**


$$\frac{V_{out}}{V_{gen}} = \left( \frac{V_{out}}{V_{gen}} \right)_{MB} \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$$

$$a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 + R_{33}^0 C_3 + R_{44}^0 C_4$$

$$a_2 = R_{11}^0 C_1 C_2 R_{22}^1 + R_{11}^0 C_1 C_3 R_{33}^1 + R_{11}^0 C_1 C_4 R_{44}^1$$

$$+ R_{22}^0 C_2 C_3 R_{33}^2 + R_{22}^0 C_2 C_4 R_{44}^2 + R_{33}^0 C_3 C_4 R_{44}^3$$

note that  $R_{xx}^0 R_{yy}^x = R_{xx}^y R_{yy}^0$

	$R_{xx}^0 = R_i(1 - A_{vmb}) + R_{Leq} \parallel R_{out,t}$ <p>where</p> $A_{vmb} = R_{Leq} / (R_{Leq} + g_m^{-1})$ $R_{out,T} = g_m^{-1}$
	$R_{xx}^0 = \{R_i(1 - A_{vmb}) + R_{Leq} \parallel g_m^{-1}\} \parallel R_{be}$ <p>where</p> $A_{vmb} = R_{Leq} / (R_{Leq} + g_m^{-1})$
	$R_{xx}^0 = R_i(1 - A_{vmb}) + R_{Leq}$ <p>where</p> $A_{vmb} = -g_m R_{Leq}$
	$R_{xx}^0 = (R_i \parallel R_{in,t})(1 - A_{vmb}) + R_{Leq}$ <p>where</p> $A_{vmb} = -g_m R_{Leq}$ $R_{in,t} = \beta / g_m$