

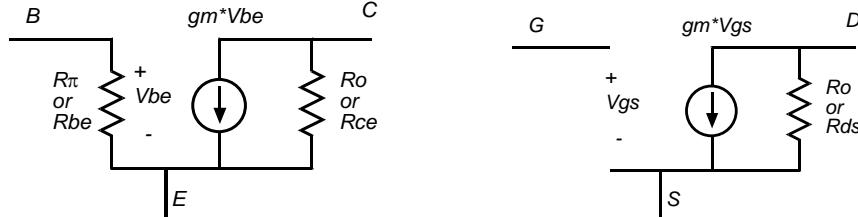

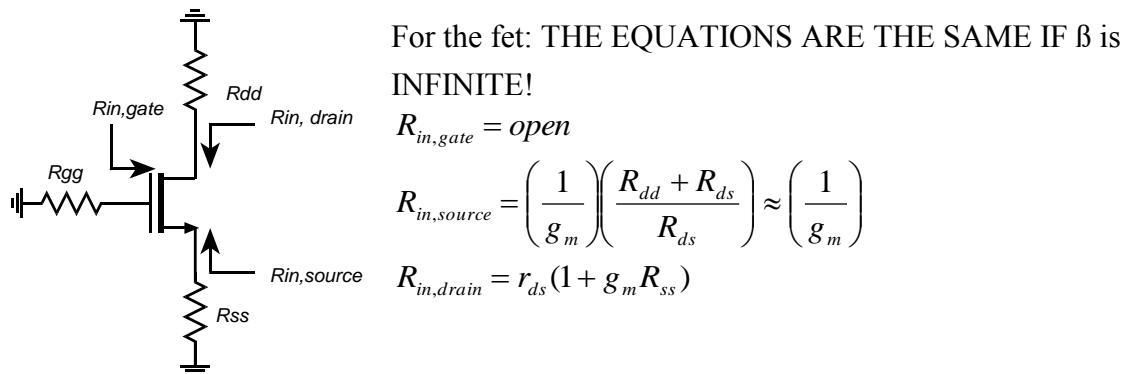
### Basics: Amplifiers at Low Frequencies




Left is the equivalent circuit of a bipolar transistor;  $g_m = I_E / V_T = 1/r_e$ ,  $V_T = kT/q$ ,  $r_\pi = r_{be} = \beta / g_m$ .  $R_{ce} = (V_A + V_{CE}) / I_C$ . On the right is the FET model.  $g_m = v_{sat} C_{ox} W_g$  (short-gate / velocity saturation model) or  $g_m = (\mu c_{ox} W_g / L_g)(V_{gs} - V_{th})$  (long-gate / mobility limited model)  $R_{ds} = [(1/\lambda) + V_{DS}] / I_D$

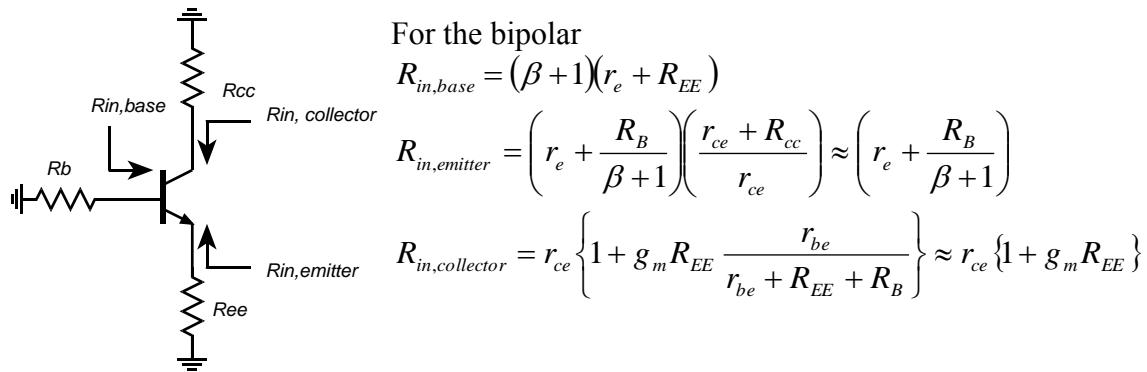

Be warned that in the equations above  $R_{cc}$ ,  $REE$  and  $RB$  are the equivalent resistances seen by the transistor. So in, the amplifier circuits below, THINK: "what is the effective resistance seen by the transistor?", before plugging into the equations.

## Amplifier Stages

### Common Emitter and Common Source

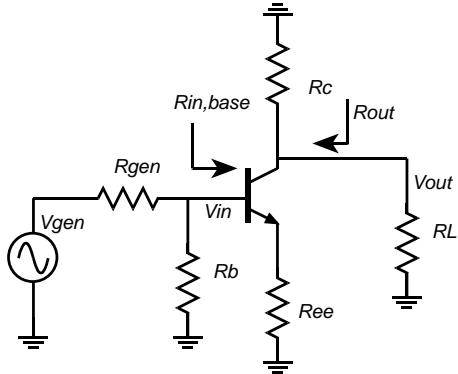


Common emitter:

$$R_{in} = R_B \parallel R_{in,base} = R_B \parallel (\beta + 1)(R_{EE} + r_e)$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{-R_{Leq}}{r_e + R_{ee}} = \frac{-(R_c \parallel R_L \parallel R_{out,collector})}{r_e + R_{ee}}$$
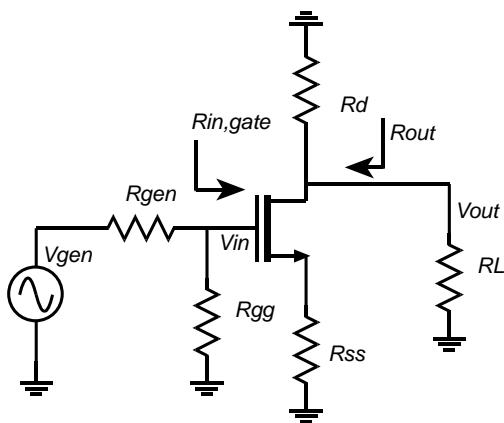
$$R_{out} = R_c \parallel R_{out,collector}$$



Common source:


$$R_{in} = R_{gg}$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{-R_{Leq}}{R_{ss} + 1/g_m} = \frac{-(R_d \parallel R_L \parallel R_{out,drain})}{R_{ss} + 1/g_m}$$

$$R_{out} = R_d \parallel R_{out,drain}$$
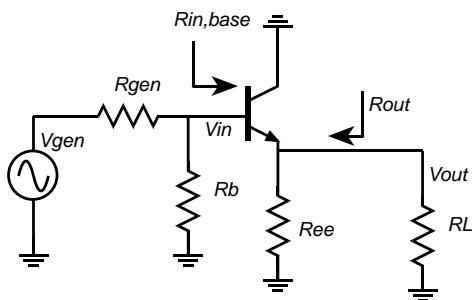
### Common Collector (emitter follower) and common drain (source follower)



for the emitter follower:


$$R_{in} = R_B \parallel R_{in,base} = R_B \parallel (\beta + 1)(R_{EE} \parallel R_L + r_e)$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_{Leq}}{R_{Leq} + r_e} = \frac{R_{ee} \parallel R_L}{R_{Leq} + r_e}$$

$$R_{out} = R_{ee} \parallel R_{in,emitter} = R_{ee} \left\| \left( r_e + \frac{R_B}{1 + \beta} \right) \right\|$$

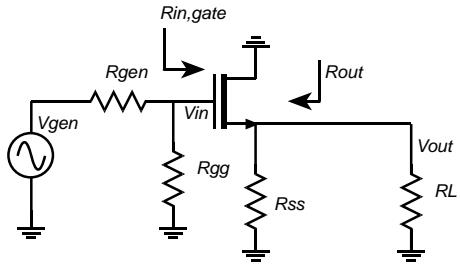Single stage amplifier crib sheet, page 3



For the source follower:


$$R_{in} = R_g$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_{Leq}}{R_{in} + 1/g_m} = \frac{R_{ss} \| R_L \| R_{ds}}{R_{ss} \| R_L \| R_{ds} + 1/g_m}$$

$$R_{out} = R_{ss} \| R_{in,source} = R_{ss} \| (1/g_m)$$

Common Base and common gate

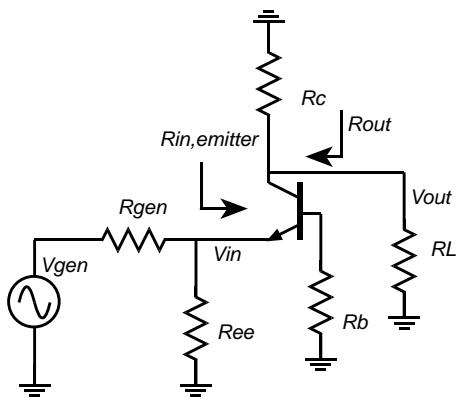

For the common base:

$$R_{in} = R_{EE} \| R_{in,emitter}$$

$$R_{in,emitter} = \left( r_e + \frac{R_B}{\beta + 1} \right) \left( \frac{r_{ce} + R_c \| R_L}{r_{ce}} \right) \approx \left( r_e + \frac{R_B}{\beta + 1} \right)$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_{Leq}}{R_{in,emitter}} = \frac{R_C \| R_L}{R_{in,emitter}}$$

$$R_{out} = R_c \| R_{out,collector}$$

For the common gate

$$R_{in} = R_{SS} \| R_{in,source}$$

$$R_{in,source} = \left( \frac{1}{g_m} \right) \left( \frac{r_{ds} + R_d \| R_L}{r_{ds}} \right) \approx \left( \frac{1}{g_m} \right)$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_{Leq}}{R_{in,source}} = \frac{R_D \| R_L}{R_{in,source}}$$

$$R_{out} = R_D \| R_{out,drain}$$

