

**ECE ECE145A (undergrad) and ECE218A (graduate)**

**Mid-Term Exam. November 12, 2014**

Do not open exam until instructed to.

Open notes, open books, etc

You have 1 hr and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine. ), ***AFTER STATING THEM.***


Problem	Points Received	Points Possible
1		15
2a		10
2b		15
3a		10
3b		10
3c		10
4		15
5		15
total		100


Name: Schuman

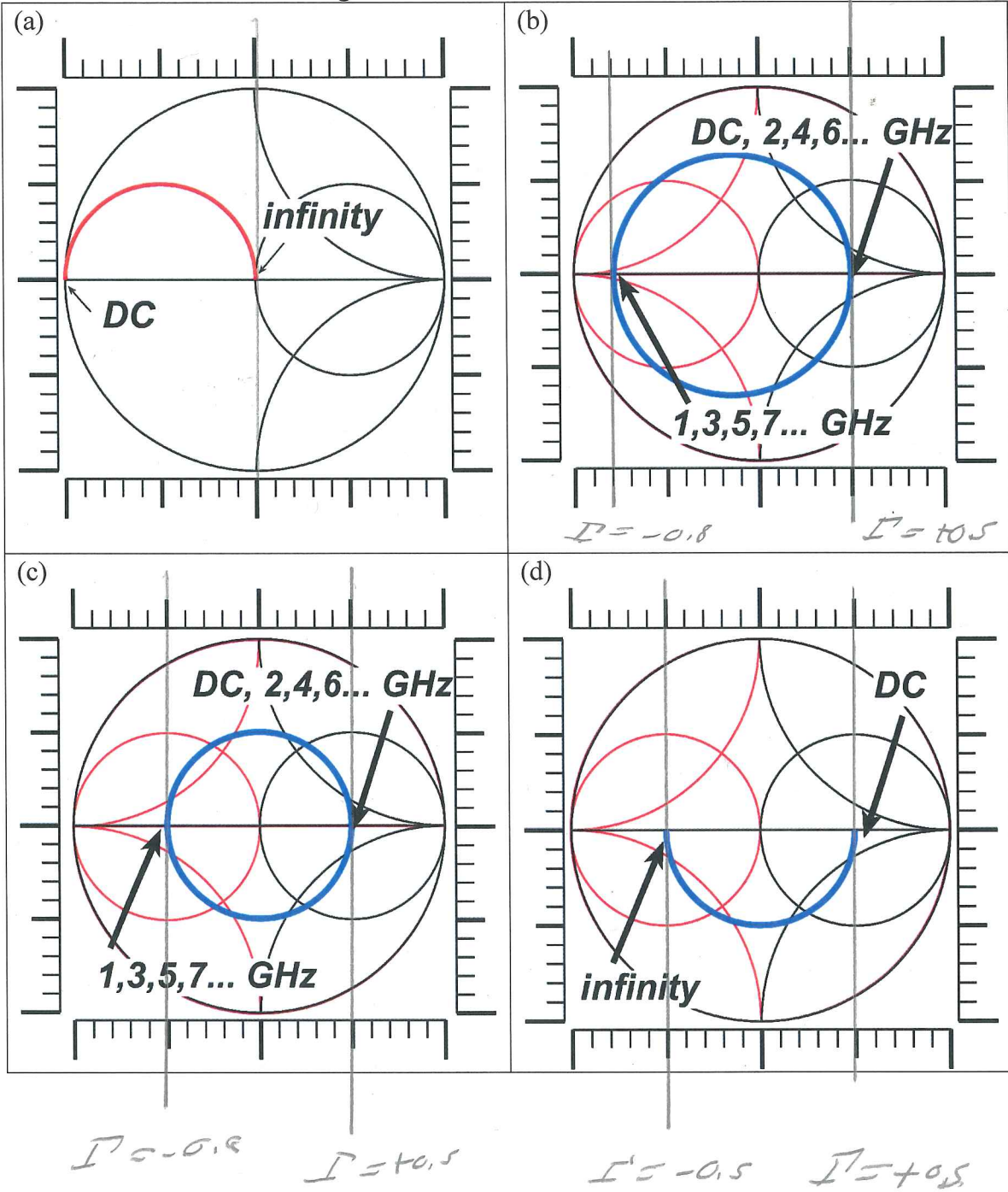**Problem 1, 15 points**

*The Smith Chart and Frequency-Dependent Impedances.*

HINT: use the scales on the figures to measure distances as needed.



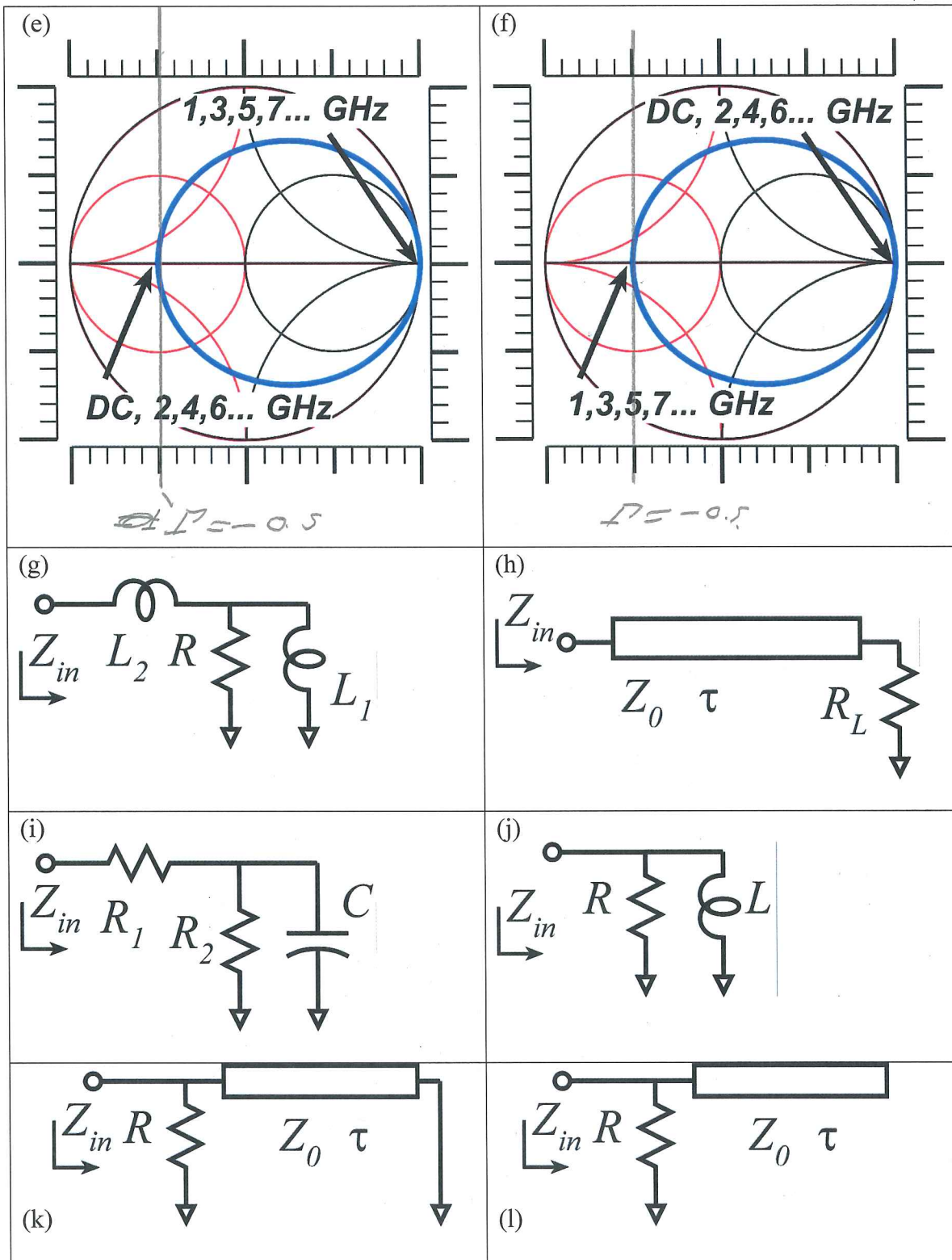

First match each Smith Chart with each circuit. **Then determine as many component values as is possible** (RLC values, transmission line delays and characteristic impedances)...note that some values cannot be determined with the information given. The charts all use 50 Ohm normalization:

- Smith chart (a). Circuit= j. Component values=  $R = 50 \Omega$ .  
 Smith chart (b). Circuit= h. Component values=  $150 \Omega = R_L, Z_0 = 29 \Omega, T = 25 \mu s$   
 Smith chart (c). Circuit= h. Component values=  $150 \Omega = R_L, Z_0 = 50 \Omega, T = 25 \mu s$   
 Smith chart (d). Circuit= L. Component values=  $R_1 = 16.6 \Omega, R_2 = 143.3 \Omega$   
 Smith chart (e). Circuit= L. Component values=  $R = 16.6 \Omega, T = 25 \mu s$   
 Smith chart (f). Circuit= K. Component values=  $R = 16.6 \Omega, T = 25 \mu s$

smith chart a  $S_{11} \rightarrow 0$  as  $f \rightarrow \infty$ , so  $R = 50 \Omega$

chart b:  $\Gamma$  varies from  $0.5 @ DC, 2, 4, 6 \dots GHz$   
to  $-0.8 @ 1, 3, 5, GHz$

this is chart h, a ~~1/4~~ line with  $R_L$ .

$$@ DC \Gamma = 0.5 \rightarrow R_L = Z_0 \frac{1+0.5}{1-0.5} = 50 \Omega \cdot 3 = 150 \Omega$$

$$@ 1 GHz, \Gamma = -0.8 \Rightarrow Z_L = Z_0 \frac{1-0.8}{1+0.8} = 5.555 \Omega$$

at  $1 GHz$ , we have a  $1/4$  line,

$$\text{and } \frac{Z_{in}}{Z_0} = \frac{Z_0}{Z_L} \Rightarrow Z_0 = \sqrt{Z_L Z_{in}} = \sqrt{150 \Omega \cdot 5.555 \Omega} = 29 \Omega$$

$$\text{line is } 1/4 @ 1 GHz, \text{ so } T = 1/4 \cdot 195 = 25 \mu s$$

chart c  $\Gamma$  varies from  $+0.5 @ 0, 2, 4 \dots GHz$   
to  $-0.5 @ 1, 3, 5 \dots GHz$

same procedure as above

$$@ DC \Gamma = 0.5 \rightarrow R_L = 150 \Omega$$

$$@ 1 GHz, \Gamma = -0.5 \rightarrow Z_L = 16.6 \Omega$$

$$\Rightarrow Z_0 = \sqrt{Z_L Z_{in}} = \sqrt{150 \Omega \cdot 16.6 \Omega} = 50 \Omega$$

chart D

@ DC,  $I = 0.5 \rightarrow R_{i2} = 150\Omega = R_1 + R_2$

@  $\infty$  f,  $I = -0.5 \rightarrow R_{i2} = 16.7\Omega = R_1$

$R_2 = 150\Omega - 16.66\Omega = 143.33\Omega$

---

chart E

@ DC,  $I = -0.5 \Rightarrow R_{i2} = 16.66\Omega = R$

@  $1\text{GHz}$ ,  $R_{i2} = 0$ , so line is  $\lambda/4$

$T = 1\text{ns}/4 = 250\text{ps}$

---

chart F

@ DC,  $I = 0.5 \Rightarrow R_{i2} = 166\Omega = R$

@  $1\text{GHz}$ ,  $R_{i2} = \infty$ , so line is  $\lambda/4$


$T = 1\text{ns}/4 = 250\text{ps}$

**Problem 2, 25 points**



*2-port parameters and Transistor models*

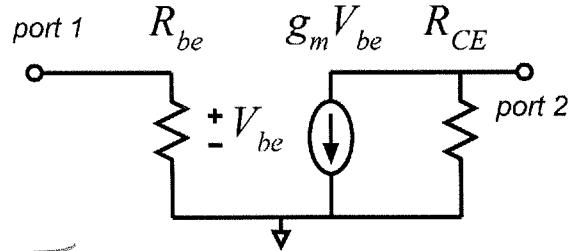Part a, 10 points

For the network at the right, give algebraic expressions for the four Y-parameters and for the four S-parameters.



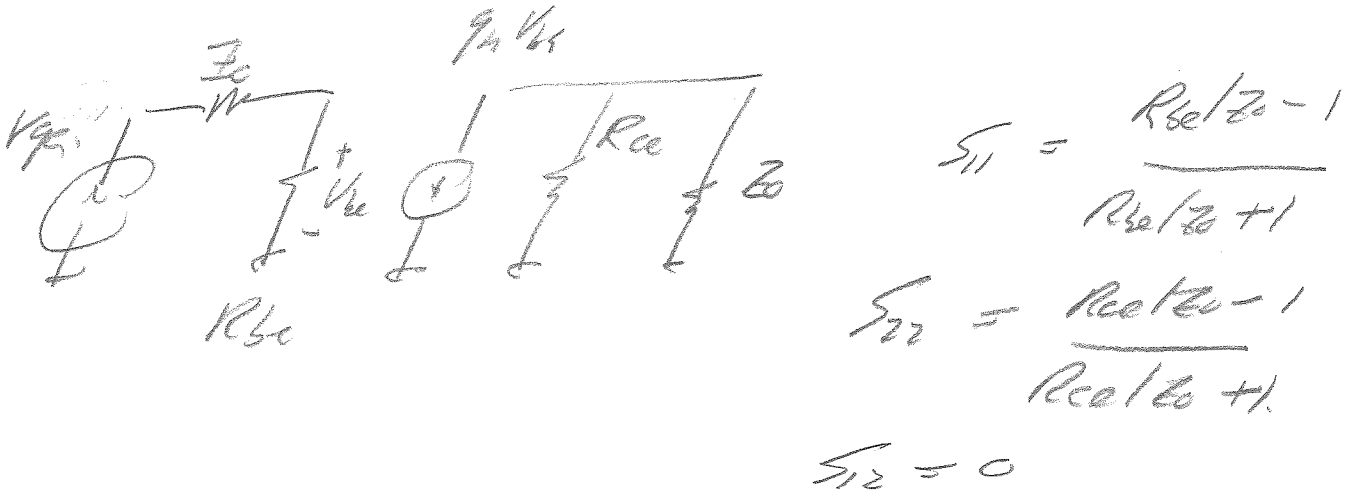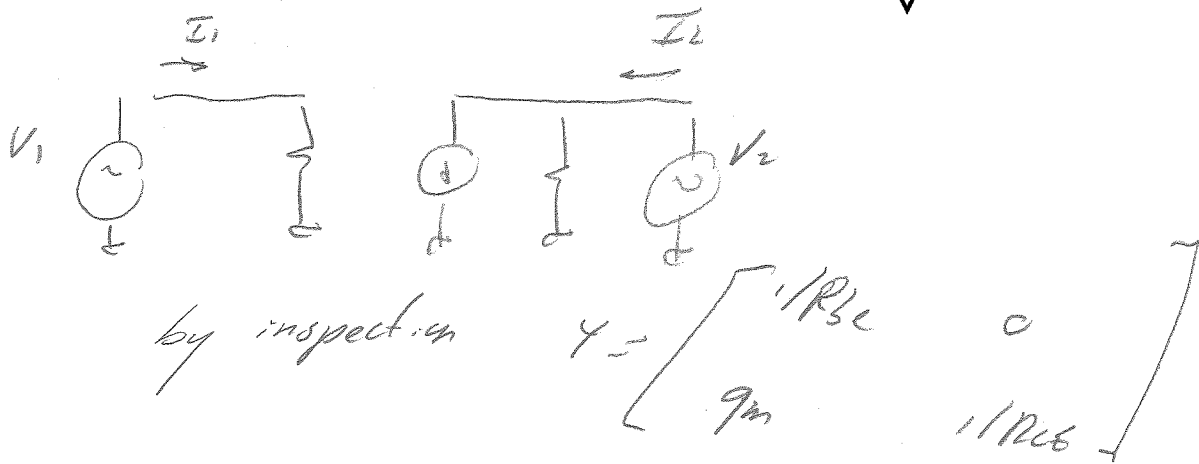Assume a normalization to impedance  $Z_0$  for the S parameters.





$$S_{21} = 2 \cdot \frac{R_{be}}{R_{be} + Z_0} \cdot (-g_m)(R_{ce} \parallel Z_0)$$

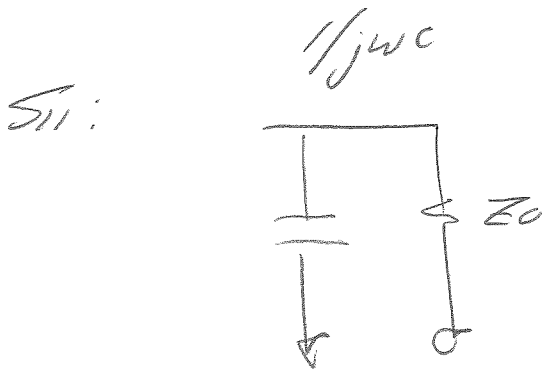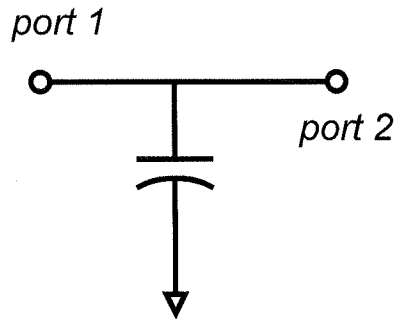Part b, 15 points

First, compute  $S_{11}$  and  $S_{21}$ , both as a function of frequency, for this network.


Second, find the frequency at which  $S_{21}$  has a magnitude of 0.7071, i.e. is down 3dB from the DC value.



$$S_{11} = \frac{Y_{in}/Y_0 - 1}{Y_{in}/Y_0 + 1}$$

$$= \frac{1 + j\omega C Z_0 - 1}{1 + j\omega C Z_0 + 1}$$
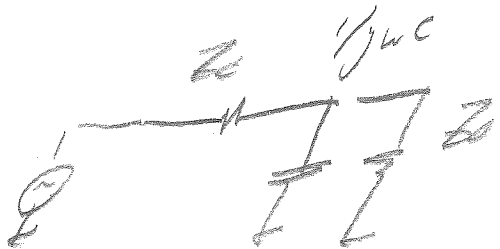
$$S_{11} = \frac{j\omega C Z_0 / 2}{1 + j\omega C Z_0 / 2} = S_{12}$$



$$S_{21} = S_{12} = 2 \cdot \left[ \frac{1}{2} \cdot \frac{1}{1 + j\omega C Z_0 / 2} \right]$$

$$S_{12} = S_{21} = \frac{1}{1 + j\omega C Z_0 / 2}$$

Down 3dB when  $f = \frac{1}{2\pi(C)(Z_0/2)}$

### Problem 3, 30 points


#### Transmission-line theory

Hint: we are testing here your understanding of transmission-lines and their relationships to lumped elements. If the calculation appears to be extremely difficult, you may possibly be missing some key insight.
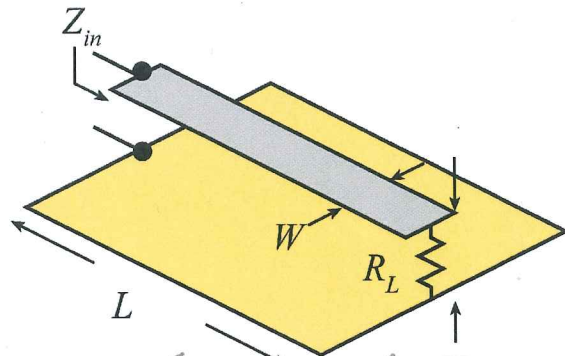
#### Part a, 10 points

Ignoring fringing fields, you have a microstrip line of 3cm length, 5mm width and 1 mm height above a ground plane. The dielectric constant is 1.0.

Find the characteristic impedance of the line, the velocity, the total line inductance, and the total line capacitance.



$$Z_0 = \sqrt{\frac{\mu_0}{\epsilon_0}} \frac{H}{W} \text{ ignoring Fringing fields}$$
$$= 377 \Omega \cdot \frac{1}{5} = \underline{75.4 \Omega}$$

$$\epsilon_r = 1 \quad \epsilon_0 = 8.85 \times 10^{-12} \text{ F/m} \quad v = c = 3 \cdot 10^8 \text{ m/s}$$
$$\text{delay} = \tau = \frac{3 \cdot 10^{-2} \text{ m}}{3 \cdot 10^8 \text{ m/s}} = 10^{-10} \text{ sec} = \underline{0.1 \text{ ns}}$$


$$C = \frac{\tau}{Z_0} = \frac{100 \text{ ps}}{75 \Omega} = \underline{1.333 \text{ pF}}$$

$$L = \tau Z_0 = \underline{7.54 \text{ nH}}$$




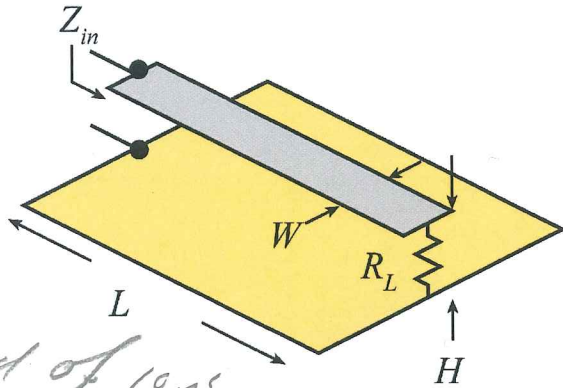Part b, 10 points

If the line is loaded by  $R_L=1$  Ohms, find an approximate value for  $Z_{in}$  at 100MHz signal frequency. Hint: wise use of approximations will make this calculation easy.




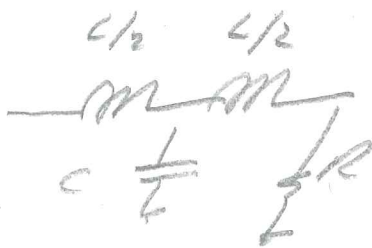100 MHz has a period of 10 ns.  
 line delay is 100 ps, 1/100 of the signal period  
 $\Rightarrow$  line is 1/100 long  $\Rightarrow$  use lumped elements



Now:  $RC = 1.33 \text{ pF} \cdot 1 \Omega$   
 $= 1 \text{ ps}$   
 $\ll (1/2 \pi \cdot 100 \text{ MHz})$   
 $\rightarrow$  ignore C.

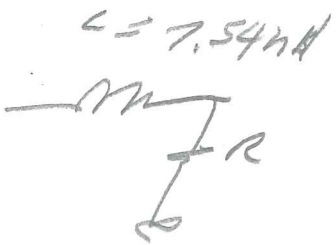
$L/R = \frac{7.54 \text{ nH}}{1 \Omega} = 7.54 \text{ ns}$ , comparable to  $\frac{1}{2 \pi \cdot 100 \text{ MHz}}$



$\Rightarrow Z_{in} \approx R + j\omega L$   
 $= 1 + j \cdot 2\pi (100 \text{ MHz}) \cdot 7.54 \text{ ns}$   
 $Z_{in} = 1 + j4.74 \Omega$

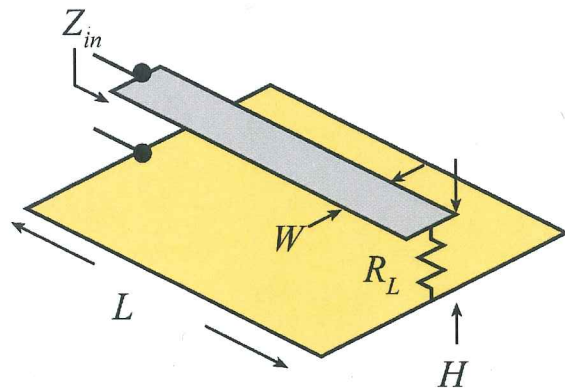Part c, 10 points

If the line is loaded by  $R_L = 1 \text{ Ohms}$ , find the value for  $Z_{in}$  at 2.5GHz signal frequency.



the line has 100ps delay.  
the frequency is  $2.5 \text{ GHz} = 400\text{ps}$ .

$\Rightarrow$  Line is  $\lambda/4$  Long.

$\Rightarrow$  quarter-wave transformer

$$Z_L = 1\Omega / 75.4\Omega = 1.33 \cdot 10^{-2}$$


at  $\lambda/4$  distance,  $Z_0 = 1/Z_L = 75.4$

$$Z_{in} = Z_0^2 Z_L = 75.4 \cdot (75.4\Omega) = 5.7 \text{ k}\Omega$$

(given finite conductor losses,  $Z_{in}$  would not reach such a high value)

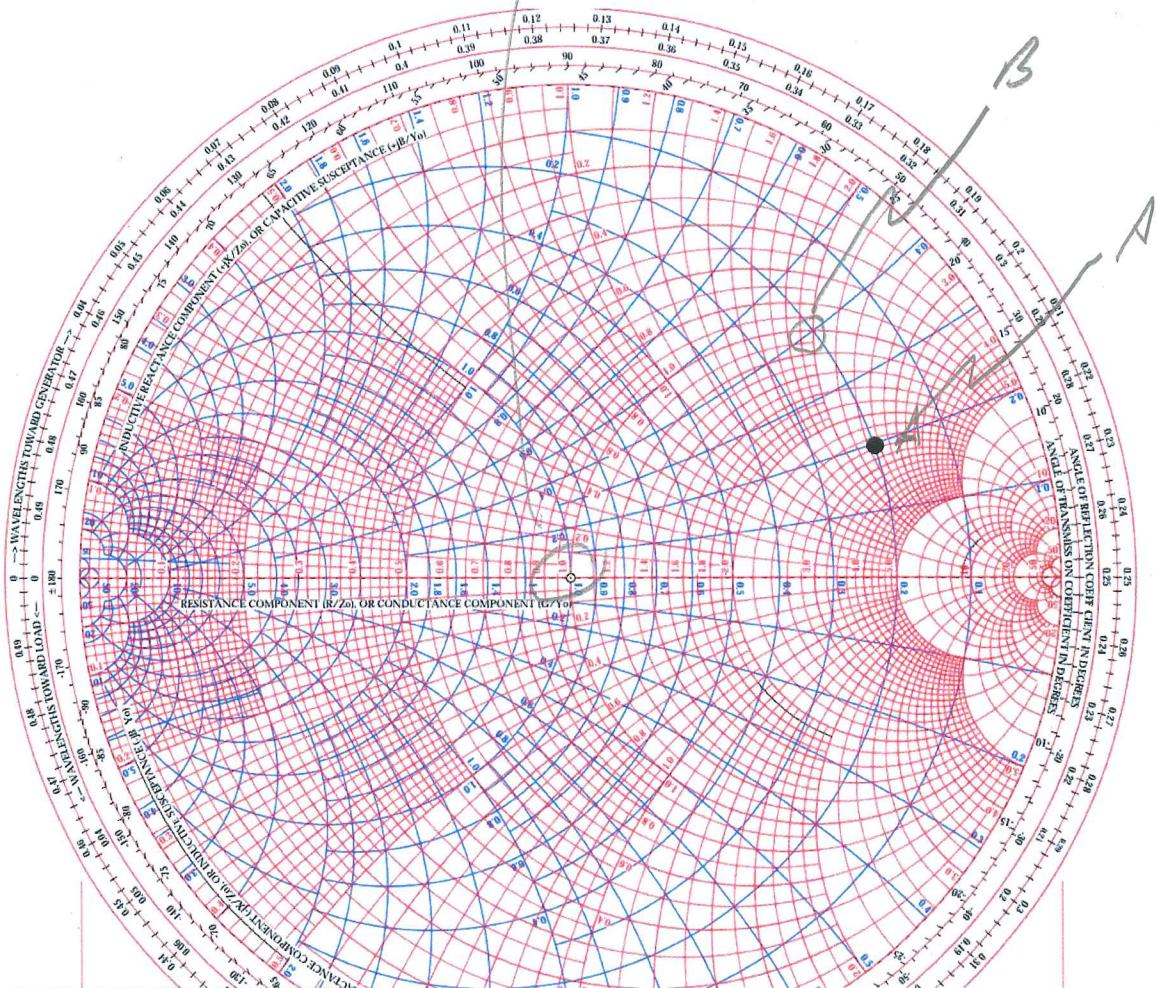**Problem 4, 15 points**  
*Impedance-matching exercise.*

The (50 Ohm normalization) Smith chart gives the input impedance of a circuit at 1 GHz signal frequency. Design a lumped-element matching network which converts this impedance to **50 Ohms** at 1 GHz. Give all element values.



*There are 2 easy solutions here - I show one*

Point a

$$Z_a = 2 + j2.3$$

$$Y_a = 0.2 - j0.2 = g + jb$$

Point B

$$Y_b = 0.2 - j0.4 = g + jb$$

$$\Delta b = -j0.6 = \frac{Z_0}{j\omega L_p}$$

$$\Rightarrow L_p = \frac{Z_0}{2\pi f (0.6)} = 13.3 \text{ nH}$$

$\uparrow$   
1 GHz

$$Z_b = 1.0 + j2.0$$

1 GHz


Point c

$$Z_c = 1.0 + j0.0$$

$$\Delta Y = -j2.0 = \frac{-1}{j\omega C_s} \frac{1}{Z_0}$$

$$\Rightarrow C_s = \frac{1}{2\pi f (2.0) Z_0} = 1.59 \text{ pF}$$

$\uparrow$   
1 GHz

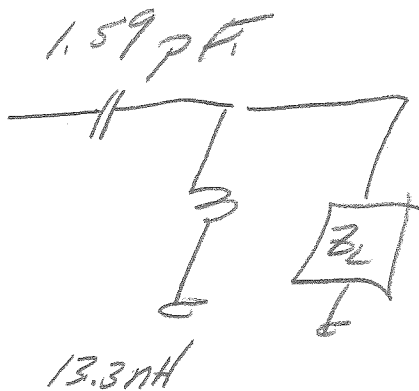


2nd solution

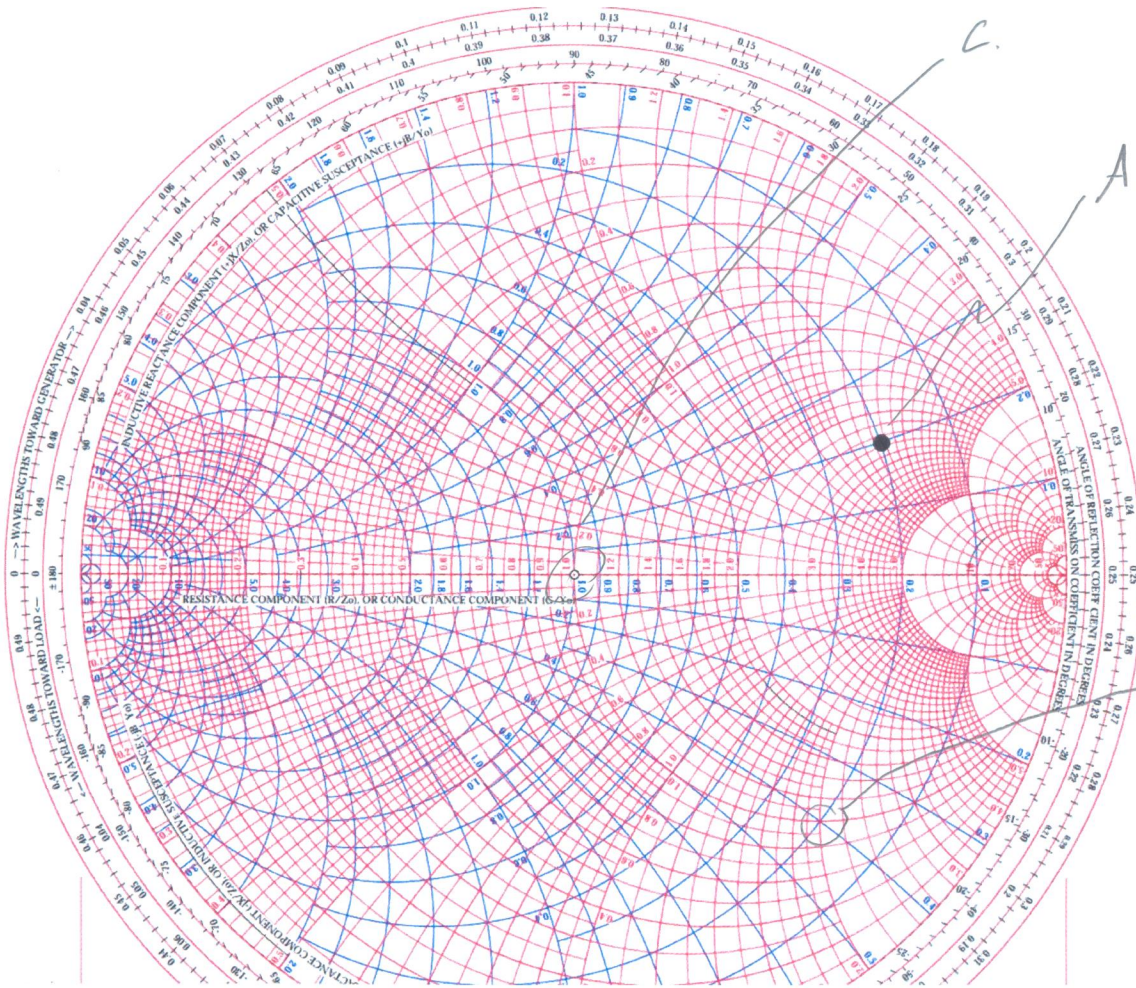**Problem 4, 15 points**

*Impedance-matching exercise.*

The (50 Ohm normalization) Smith chart gives the input impedance of a circuit at 1 GHz signal frequency. Design a lumped-element matching network which converts this impedance to **\*\*50 Ohms\*\*** at 1 GHz. Give all element values.



2nd solution.

Point A  $Z_A = 2 + j23$

$$Y_A = 0.2 - j0.2 = g + j\omega C \quad ] 1$$


---

Point B

$$Y_B = 0.2 + j0.4 = g + j\omega C \quad ] 1$$

$$\Delta Y = j0.6 = j\omega C p Z_0 \quad ] 2$$

$$\Rightarrow C_p = \frac{0.6}{2\pi f Z_0} = 1.9 \text{ pF} \quad ] 2$$


$$Z_B = 10 - j2.0 \quad ] 2$$


Point C

$$Z_C = 1.0 + j0.0 \quad ] 2$$

$$\Delta X = +j2.0 = \frac{j\omega L}{Z_0} \quad ] 2$$
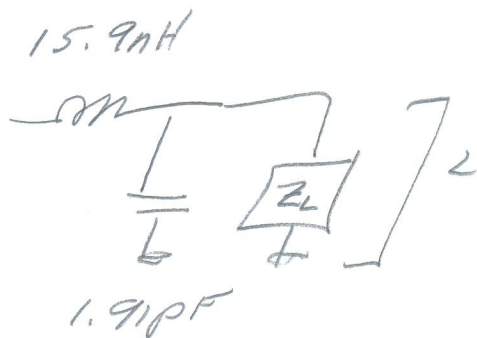
$$\Rightarrow L_s = \frac{2.0 \cdot Z_0}{2\pi f} = 15.9 \text{ nH} \quad ] 2$$




**Problem 5, 15 points**

Signal flow graphs

We have a cascade of two amplifiers, "x" and "y". The signal flow graph is also shown.

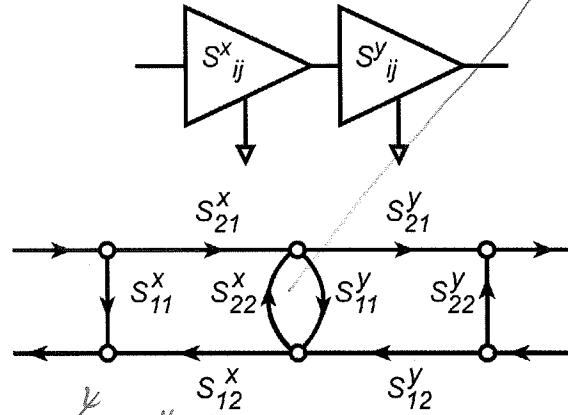Find S11 and S21 of the resulting combination.



$$S_{11} = \frac{S_{11}^x (1 - S_{22}^x S_{11}^y) + S_{21}^y S_{11}^y S_{12}^x}{1 - S_{22}^x S_{11}^y}$$

$$= S_{11}^x + \frac{S_{21}^x S_{11}^y S_{12}^x}{1 - S_{22}^x S_{11}^y}$$

$$S_{21} = \frac{S_{21}^x S_{21}^y}{1 - S_{22}^y S_{11}^y}$$