

## ECE ECE145A (undergrad) and ECE218A (graduate)

**Final Exam. Tuesday, December 8, 12-3 p.m.**

Do not open exam until instructed to.

Open notes, open books, etc. You have 3 hrs.

Use all reasonable approximations (5% accuracy is fine.) ,

**AFTER STATING and justifying THEM.**

Think before doing complex calculations. Sometimes there is an easier way.

Problem	Points Received	Points Possible
1a		5
1b		7
2a		7
2b		5
3a		5
3b		7
3c		8
3d		5
3e		5
3f		5
4a		5
4b		7
4c		5
4d		5
5a		6
5b		5
5c		8
total		100

Name: Selafiz

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)(1 - |\Gamma_L|^2)}{|(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - S_{21} S_{12} \Gamma_s \Gamma_L|^2} \quad G_P = \frac{1}{1 - \|\Gamma_{in}\|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2}$$

$$G_a = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - \|\Gamma_{out}\|^2} \quad G_{\max} = \frac{|S_{21}|}{|S_{12}|} \cdot [K - \sqrt{K^2 - 1}] \text{ if } K > 1$$

$$G_{MS} = \frac{|S_{21}|}{|S_{12}|} \cdot \text{if } K < 1 \quad K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{21} S_{12}|} \quad \text{where } \Delta = \det[S]$$

Unconditionally stable if : (1)  $K > 1$  and (2)  $\|\det[S]\| < 1$

**Problem 1, 12 points**

*Two-port properties, Gain relationships*


part a, 5 points

Transistor cutoff frequencies

$$C_{gs} = 100 \text{ fF}, g_m = 100 \text{ mS.}$$


$$R_{ds} = 100 \text{ Ohms}, R_i = 10 \text{ Ohms},$$

Find  $f_\tau$  and  $f_{\max}$ .

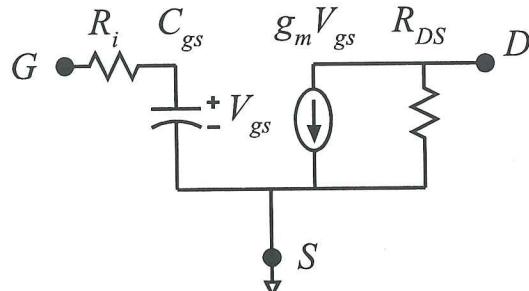

can work either by formula or by derivation.

by derivation:

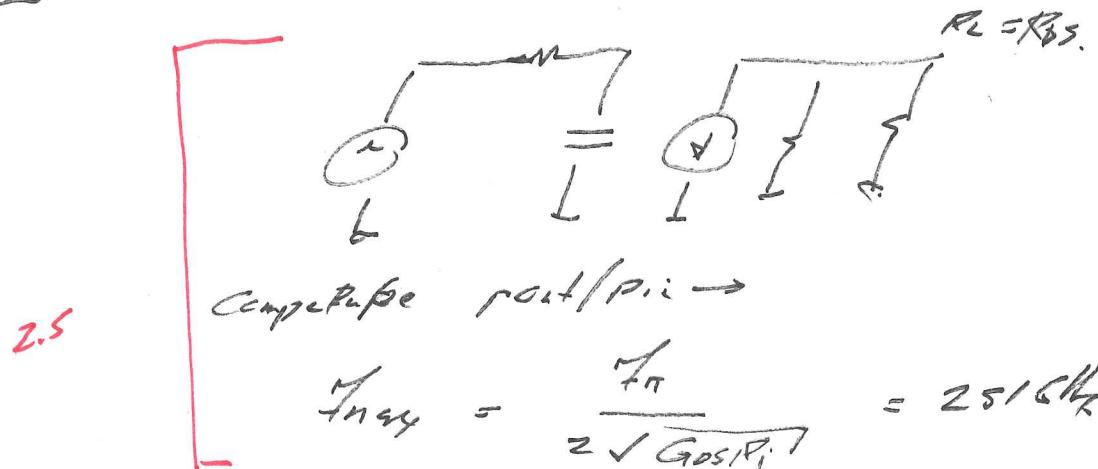

2.5

*simplifying:*

$$f_\pi = \frac{g_m}{2\pi C_{gs}} = 159 \text{ GHz}$$

part b, 7 points

Find the short-circuit current gain and the maximum available power gain at 60 GHz

3.5 [ 
$$h_{21} = \frac{159 \text{ GHz}}{68 \text{ GHz}} = 2.25 \rightarrow 8.5 \text{ dB.}$$
  
$$(20 \log_{10})$$
 ]


3.5. [ 
$$\text{un. lateral - so mag } = a = \left( \frac{251 \text{ GHz}}{60 \text{ GHz}} \right)^2 = \underline{\underline{17.5}}$$
  
$$\rightarrow \cancel{12.4} \text{ dB.}$$
  
$$(10 \log_{10}).$$
 ]

**Problem 2, 12 points**

Potentially unstable amplifier design

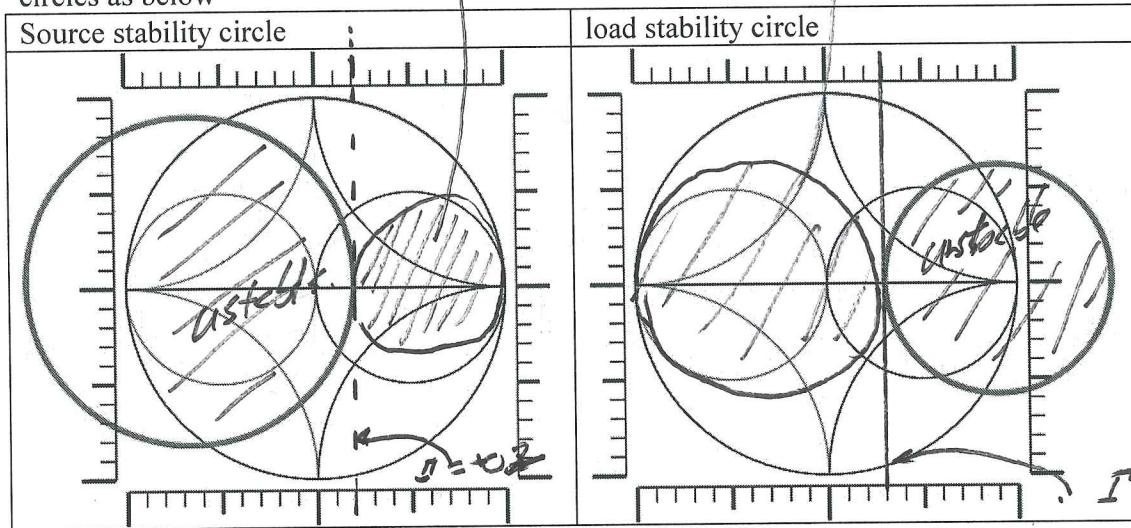
part a. 7 points

At a design frequency of 1 GHz, a common-source FET has source and load stability circles as below



$I = 10^3$

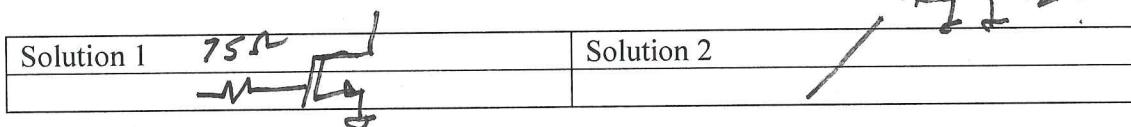Given that  $S_{11}=0.5$  and  $S_{22}=1.1$  at 1GHz, draw two stabilization circuits in the boxes below, giving element values



$$Z_{in} = S_{11} + \frac{S_{21} S_{12} Z_0}{1 - S_{22} Z_0} ; \quad I_{out} = S_{21} + \frac{S_{11} S_{12} Z_0}{1 - S_{22} Z_0}$$

[source stab. C61.  $Z_0 = 50\Omega$ . gives  $I_{out} = S_{21} = 1.1 > 1$ , so center of Smith chart is unstable] 2

must add series resistance on input of  $50\Omega \cdot \frac{1+0.2}{1-0.2} = 75\Omega$ ] 1.5

load stability circle.  $Z_0 = 0$  gives  $I_{out} = S_{11} = 0.5 < 1$   
so center of Smith chart is stable]


must add parallel resistance on output of

$$50\Omega \cdot \frac{1+0.5}{1-0.3} = 92.8\Omega$$

] 1.5.

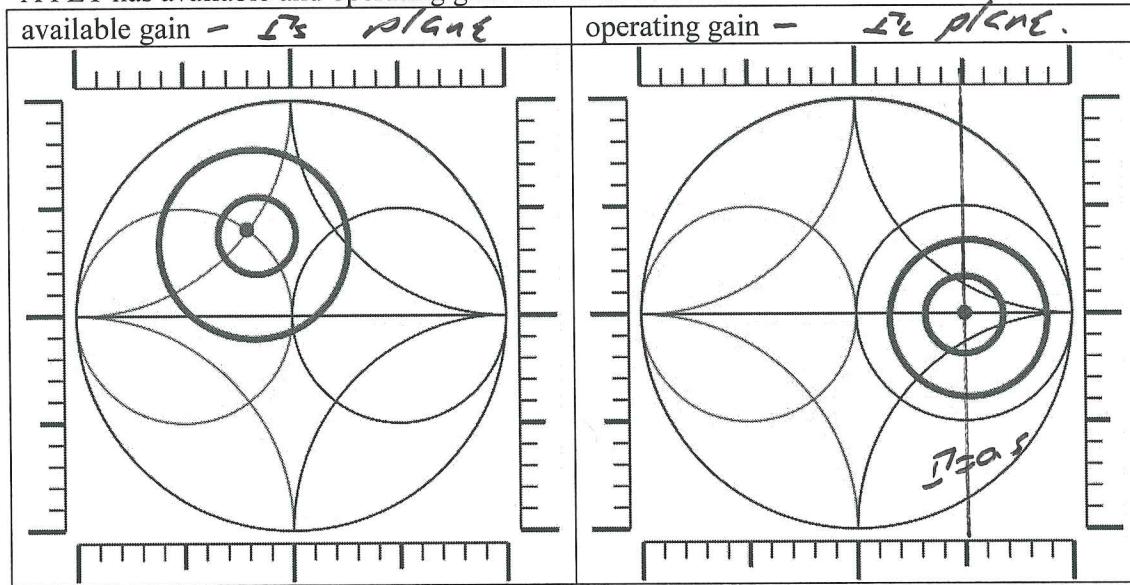part b, 5 points

A FET has available and operating gain circles as below at 1 GHz.



Assuming a 50Ω impedance normalization, what are the optimum generator and load impedances?

$$Z_{gen,opt} = \cancel{\frac{15}{(1+j)}} \Omega \quad Z_{L,opt} = \frac{150 + j0 \Omega}{}$$

$$G_A = \frac{P_{AVA}}{P_{AVG}} \stackrel{\text{iff } \text{IP matched}}{=} \frac{P_L}{P_{AVC}} = G_T \quad \left| \begin{array}{l} \text{optimum } Z_s \text{ if } s = 1-j1 \\ Y_{s,opt} = \frac{1-j1}{50 \Omega} \\ Z_{s,opt} = \frac{50 \Omega}{1-j1} = \frac{50}{\sqrt{2}} \Omega (1+j) \end{array} \right.$$

2s - ~~Z<sub>s,opt</sub>~~

2.  $G_P = \frac{P_L}{P_{in}} \stackrel{\text{iff IP matched}}{=} \frac{P_L}{P_{AVC}} = G_T$

so  $G_P = G_P(\text{Z}_L)$  2.5


optimum  $\text{Z}_L = 0.5$

3. optimum  $Z_L = 50 \Omega \frac{1+0.5}{1-0.5} = 50 \Omega \frac{1.5}{0.5} = 150 \Omega$

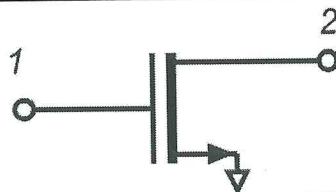**Problem 3, 35 points**

*Power gains and stability*

The transistor has  $S_{11}=0$ ,  $S_{12}=0.1$ ,  $S_{21}=8$ ,  $S_{22}=0.5$



part a, 5 points

If the load impedance is an open-circuit, what is the input reflection coefficient?

$$\Gamma_{in} = \frac{1.6}{3}$$

5.

$$\begin{aligned}\Gamma_{in} &= S_{11} + \frac{S_{12} S_{21} Z_L}{1 - S_{22} Z_L} \stackrel{3}{=} S_{11} + \frac{S_{12} S_{21}}{1 - S_{22}} \\ &= 0 + \frac{0.1 \cdot 8}{1 - 0.5} = \frac{0.8}{0.5} = 1.6, \text{ which is greater than } \underline{\underline{\underline{\underline{\underline{1}}}}} \end{aligned}$$

z for an amplifier

so, without having to compute  $G_1$ ,  $B_1$ ,

we can see that this circuit

is potentially unstable

part b. 7 points

Is it necessary to stabilize the device before simultaneous input and output matching to it ? Assuming that you have stabilized, if necessary, or have not stabilized (if not necessary), what power gain will you obtain after matching on both input and output ?

Unconditionally Stable ? NO.

Power gain after simultaneous matching = 80.1.

3 From part a, with  $|S_2| \leq 1$ , we have  $|T_2| > 1$ , so potentially unstable.

Since it is potentially unstable,

the power gain after stabilizing & matching

$$\text{is the M.G. } \frac{|S_2|}{|S_{12}|} = \frac{1.81}{10.11} = 80. \quad (19.0 \text{ dB})$$

2

part c, 8 points


(hard thinking, ok math): Can you determine from the S-parameters above what values of source reflection coefficient would lead to potential instability? Can you determine the necessary value of parallel input stabilization resistance?

$$P_{out} = S_{22} + \frac{S_{12} S_{21} L_5}{1 - S_{11} L_5} = 0.5 + 0.8 L_5$$

set  $|P_{out}| = 1$ , so  $[P_{out} = e^{j\theta_0}] \text{ or } [e^{j\theta_0} = 0.5 + 0.8 L_5]$



$$[e^{j\theta_0} = 0.5 + 0.8 L_5] \rightarrow [L_5 = 1.25 \cdot e^{j\theta_0} - 0.625]$$

$\theta_0 = -1.875$ ,  $-0.625$

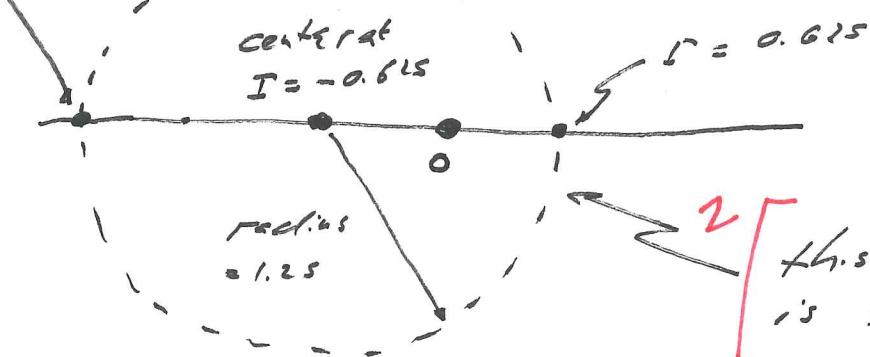

so, we need to keep  $L_5$  below  $-0.625$
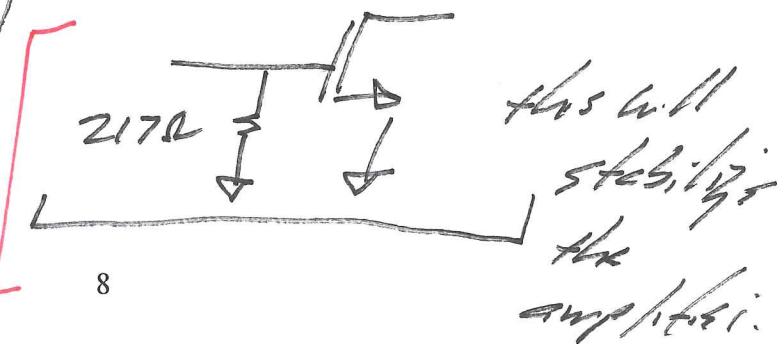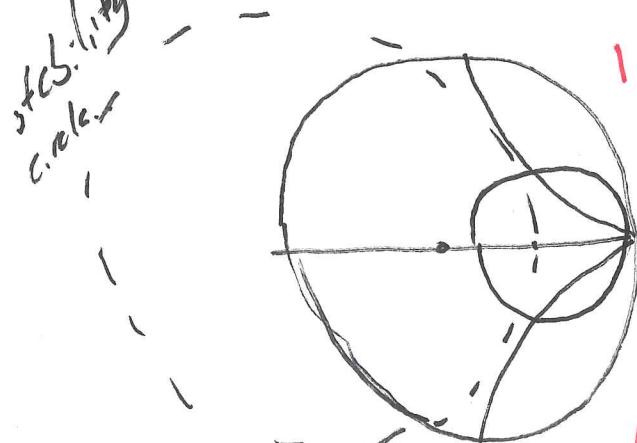
$$\text{so } R \frac{1+0.625}{1-0.625} = 217\Omega.$$



$$S_{11} = 0, \quad S_{12} = Q_1, \quad S_{21} = \delta, \quad S_{22} = 0.5$$

part d, 5 points

Without stabilizing the FET, the FET is connected to a 100 Ohm generator, with 1mW available power, and a 100 Ohm load. Find the power in the load

$$P_L = \underline{91 \text{ mW.}}$$

2. [we are being asked for the transducer gain, since  $G_T = \frac{P_L}{P_{AVG}}$ .]

$$1. \quad G_T = \frac{(S_{21})^2 (1 - (R_L)^2 K_1 - (R_S)^2)}{1 - R_S S_{11} (K_1 - R_L S_{21}) - S_{21} S_{12} R_S R_L}$$

$$R_S = R_L = \frac{100 - 50}{100 + 50} = \frac{1}{3}$$

$$1. \quad = \frac{\delta^2 [1 - 1/9] [1 - 1/9]}{1(1)(1 - \frac{1}{3} \cdot \frac{1}{2}) - \frac{0.8}{9}} = \frac{1}{10.741^2}$$

$$= \frac{50.56}{10.741^2} = 91.23 = \frac{P_L}{P_{AVG}}$$

$$1. \quad P_L = 91.23 \cdot 1 \text{ mW} = 91.23 \text{ mW}$$

part e, 5 points

Without stabilizing the FET, the FET is connected to a 50 Ohm generator, with 1mW available power, and a 50 Ohm load. Find the power in the load

$$P_L = \underline{64 \text{ mW.}}$$

4. we are going to solve for the insertion gain, which is  $|S_{11}|^2$

$$\boxed{P_L = 1 \text{ mW} (8)^2 = 64 \text{ mW}}$$

$$S_{11} = 0$$

$$S_{12} = 0.1$$

$$S_{21} = 8$$

$$S_{22} = 0.5$$

part f, 5 points

Without stabilizing the device, the generator, with 1mW available power, is impedance-matched to the FET input, and is then connected directly to a 100 Ohm load. Find the power in the load

$$P_L = \underline{90.9 \text{ mW}}$$

$$\boxed{G_T = \frac{P_L}{P_{AVC}} \quad \frac{P_L}{P_{in}} = G_D \quad | \quad \frac{P_L}{P_{in}} = \frac{100 \cdot 50}{100 + 50} = \frac{1}{3}}$$

Since the generator is (?) matched to the input, we have  $G_D = G_T$  and  $P_{out} = G_D \cdot P_{AVC}$ .

$$\boxed{P_{in} = S_{11} + \frac{S_{21} S_{12} I_L}{1 - S_{22} I_L} = \frac{0.8 \cdot \frac{1}{3}}{1 - 0.5 \cdot \frac{1}{3}} = \frac{0.2666}{0.5333} = 0.320}$$

note that  $|P_{in}| < 1$  with this particular  $I_L$ . In other words, though the FET is potentially unstable, the load we have been given lies within the stable region on the  $I_L$ -plane. Had this not been true, the solution would not have existed (!).

$$\boxed{G_D = \frac{1}{1 - |I_L|^2} \frac{|S_{11}|^2}{|1 - S_{22}|^2}}$$

$$\boxed{= \frac{1}{(1 - 0.32)^2} \frac{64}{(1 - \frac{1}{2} \cdot \frac{1}{3})^2} = 1.11 \cdot 64 \cdot \frac{819}{0.69} = 90.93}$$

$$\boxed{P_L = 90.93 \cdot 1 \text{ mW} = 90.93 \text{ mW}}$$

**Problem 4, 22 points**

*S parameters and Signal flow graphs*

A transistor has the following s-parameters:



$$S_{11}=0.5$$

$$S_{22}=0.25$$

$$S_{12}=0.5$$

$$S_{21}=5$$

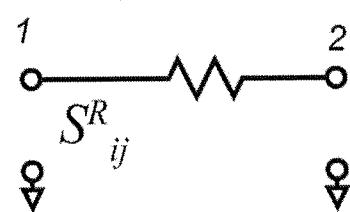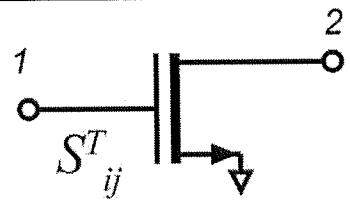A second two-port consists of a 25 Ohm resistor between its input and output ports




part a, 5 points

Using a 50 Ohm impedance standard, compute the four S-parameters of the resistor network.

$$S_{11} = \frac{1/5}{1/5} \quad S_{12} = \frac{4/5}{1/5} \quad S_{21} = \frac{4/5}{1/5}$$


2.5  $S_1$  (and  $S_{21}$ )  $25\Omega$

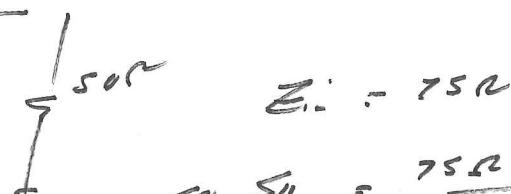

$$Z_i = 75\Omega$$

$$\text{so } S_{11} = \frac{75\Omega - 50\Omega}{75\Omega + 50\Omega} = \frac{25}{125} = 1/5.$$

2.5  $S_{21}$  (and  $S_{12}$ )

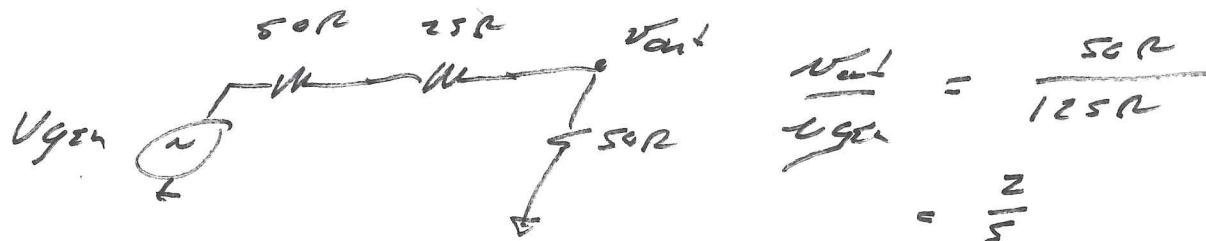

$$\frac{V_{out}}{V_{in}} = \frac{50\Omega}{125\Omega}$$

$$= \frac{2}{5}$$


$$\text{so } S_{21} = \frac{2/5}{1/5} = 4/5$$

$$\text{if } Z_i = Z_o = Z_s$$

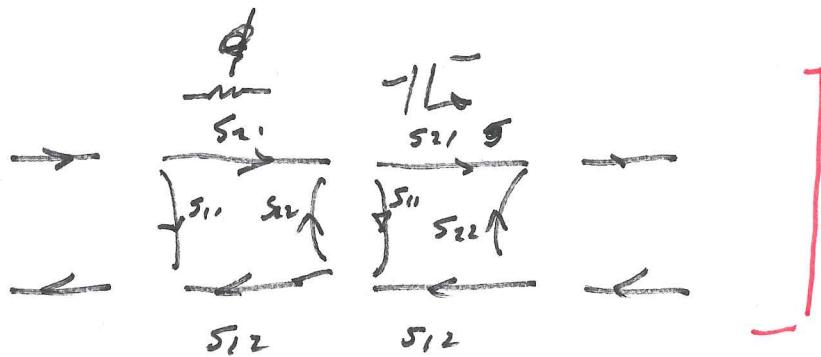part b, 7 points

The resistor network is connected between to the FET input. Compute the four S-parameters of the combined network.

$$S_{11} = \underline{0.555} \quad S_{12} = \underline{0.444} \quad S_{21} = \underline{4.44} \\ S_{22} = \underline{0.805}$$



$$2 \left[ S_{21}^{\text{overall}} = \frac{S_{21}^R S_{21}^{T^*}}{1 - S_{22}^R S_{11}^{T^*}} = \frac{(4/5)(5)}{1 - (1/5)(0.5)} \right. \\ \left. = \frac{4}{1 - 0.1} = 4.44 \quad \text{half for formula} \right. \\ \left. \text{half for meth.} \right]$$

$$2 \left[ S_{12}^{\text{overall}} = \frac{S_{12}^R S_{12}^{T^*}}{1 - S_{21}^R S_{11}^{T^*}} = \frac{(4/5)(0.5)}{1 - (1/5)(0.5)} = 0.444. \right]$$



$$2 \left[ S_{11}^{\text{overall}} = \frac{S_{11}^R (1 - S_{21}^R S_{11}^{T^*}) + S_{21}^R S_{11}^{T^*} S_{12}^R}{1 - S_{22}^R S_{11}^{T^*}} = S_{11}^R + \frac{S_{21}^R S_{11}^{T^*} S_{12}^R}{1 - S_{22}^R S_{11}^{T^*}} \right. \\ \left. = 1/5 + \frac{(4/5)(0.5)(4/5)}{1 - (1/5)(0.5)} = 1/5 + \frac{0.32}{0.9} = 0.555 \right]$$

$$1 \left[ S_{22}^{\text{overall}} = S_{22}^{T^*} + \frac{S_{12}^{T^*} S_{21}^{T^*} S_{22}^R}{1 - S_{22}^R S_{11}^{T^*}} = 0.25 + \frac{5(1/2)(1/5)}{1 - (1/5)(0.5)} = 0.25 + \frac{0.5}{0.9} = 0.805 \right]$$

part c, 5 points

Y-parameters

Compute the Y-parameters of this network

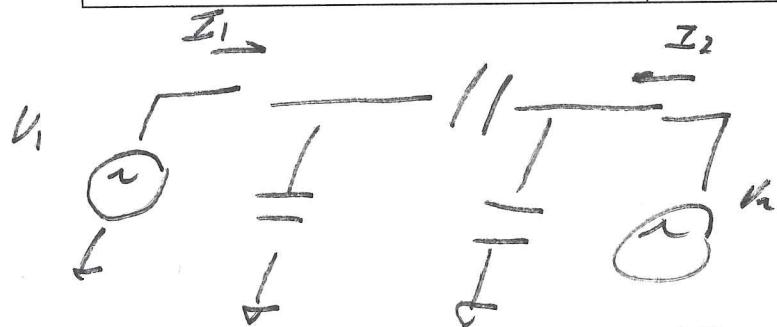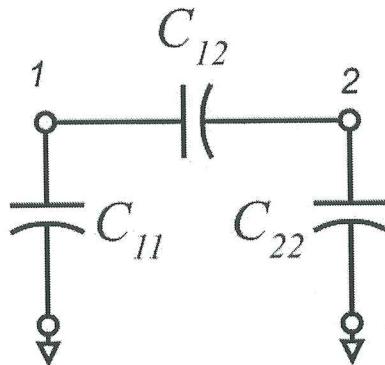



$$\Rightarrow \text{connection: } [Y_{ij}] = \begin{bmatrix} j\omega C_{11} + j\omega C_{12} & -j\omega C_{12} \\ -j\omega C_{12} & j\omega C_{22} + j\omega C_{12} \end{bmatrix}$$

1.25 % each parameter

part d, 5 points

Z-parameters

Compute the Z-parameters of this network

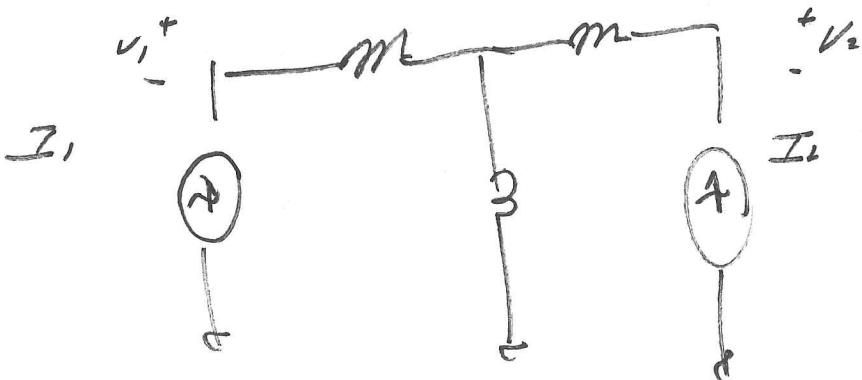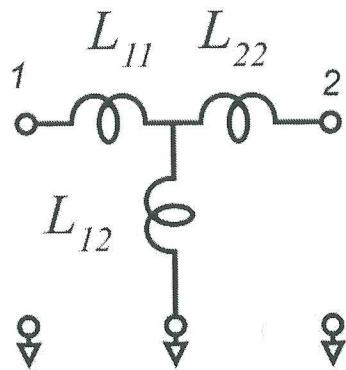

by inspection:

$$[Z_{ij}] =$$

$$j\omega L_{11} + j\omega L_{12}$$


$$j\omega L_{12}$$

$$-j\omega L_{12}$$

$$j\omega L_{22} - j\omega L_{12}$$

1.25 for each parameter.

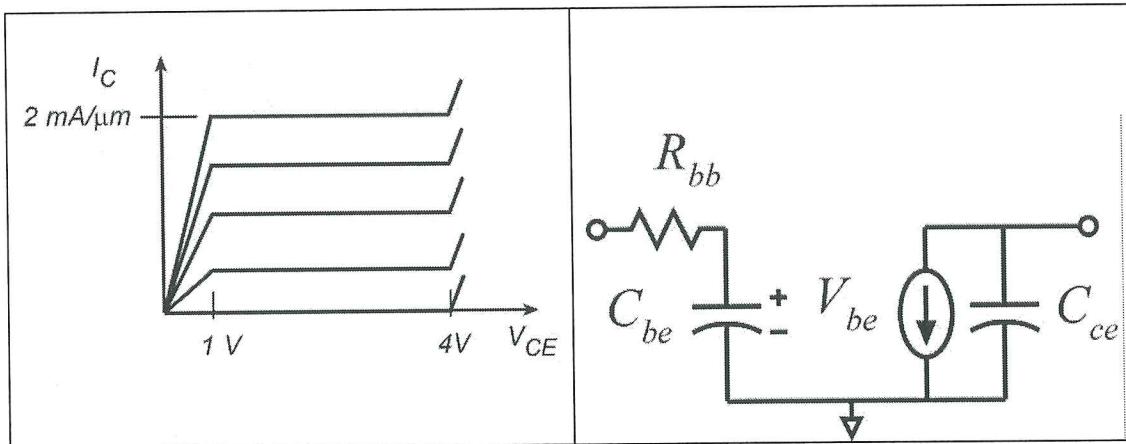**Problem 5, 19 points**  
*Power amplifier design*



An HBT has the output characteristics as shown, with a maximum 2mA/micron collector current. The (somewhat contrived) device model is to the right, with

$$g_m = 20.0 \text{ mS} / \mu\text{m} \cdot L_E \quad R_{bb} = 20\Omega - \mu\text{m} / L_E \quad C_{be} = g_m \tau_f, \text{ where } \tau_f = 0.5 \text{ ps},$$

$$C_{ce} = 2 \text{ fF} / \mu\text{m} \cdot L_E$$

part a, 6 points

The optimum load *admittance* is parallel combination of a conductance G and an inductive susceptance. Setting G to 40 millisiemens, and setting the signal frequency to 100GHz, find (1) the appropriate HBT emitter length  $L_E$  and (2) the required parallel load inductance L.

1 [optimum load impedance for  $C_E = 1 \mu\text{m}$  ::

$\rightarrow Z_{load} = \frac{3V}{2 \text{ mS}} = 1.5 \text{ k}\Omega$  with parallel inductive load.

so... we have a local of  $40 \text{ mS} = 1/25 \Omega$

2  $\rightarrow L_E = \frac{1500 \Omega}{25 \Omega} = \frac{6000 \Omega}{100 \Omega} = 60 \mu\text{m}$

1  $\Rightarrow C_{CE} = 2.67 \text{ fF}/\mu\text{m} \cdot 60 \mu\text{m} = 120 \text{ fF}$

2 need  $2\pi f = 1/(LC) \rightarrow L = \frac{1}{C(2\pi f)^2} = 21.1 \text{ pH}$

part b, 5 points

What is the maximum saturated output power ? What is the correct collector bias voltage and collector bias current ?

3

$$\boxed{P_{max} = \frac{1}{8} \Delta V \cdot \Delta I = \frac{1}{8} \cdot 3V \cdot \left( \frac{2 \mu A}{\mu A} \cdot 60 \mu A \right)}$$
$$= \frac{1}{8} \cdot 3V \cdot 120mA = \underline{\underline{4.5mW}}$$

1  $\boxed{V_{B_{sat}} = \frac{1V + 4V}{2} = 2.5V}$

1  $\boxed{I_{S_{sat}} = 60mA}$

part c, 8 points

After impedance-matching on the amplifier input and output, what is the amplifier power gain?

clt  
and  
parameters.

$R_{SS} = \frac{2\alpha R}{60} = 1/3 \Omega$

$\boxed{2}$

$I_{out} = I_{in} \cdot 25\Omega = (\mu_m V_{be})^2 25\Omega$

$C_{oe} = g_m T_f \quad g_m = \frac{2emS}{\mu_m} \cdot 60 \mu m = 120 mS$

$= 60 pF$

$\boxed{2} P_{out} = I_{out}^2 \cdot 25\Omega = (\mu_m V_{be})^2 25\Omega$

$\boxed{2} P_{in} = I_{in}^2 \cdot (1/3 \Omega) = (\omega C_{oe} V_{be})^2 (1/3)$

$\boxed{1} \frac{P_o}{P_i} = \left( \frac{\mu_m}{\omega C_{oe}} \right)^2 \frac{25\Omega}{1/3 \Omega}$

but  $C_{oe} = g_m T_f$

so  $\frac{\mu_m}{\omega C_{oe}} = \frac{\mu_m}{\omega g_m T_f} = \frac{1}{\omega T_f}$

$\frac{P_o}{P_i} = \left( \frac{1}{2\pi f T_f} \right)^2 \frac{25\Omega}{1/3 \Omega} = 10 \cdot 1 \cdot \frac{25\Omega}{1/3 \Omega} = 760$

$100 \text{ dB} \quad 42 \text{ dB}$

$\boxed{1} \frac{P_o}{P_i} = 760 \quad \text{quite unrestrictive (5.1V transistor bias).}$

(29dB)