

ECE ECE145A (undergrad) and ECE218A (graduate)

Mid-Term Exam. October 26, 2016

Do not open exam until instructed to.

Open notes, open books, etc.

You have 1 hr and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.) , **AFTER STATING THEM.**


Problem	Points Received	Points Possible
1		15
2a		10
2b		15
2c (218 only)		15 (218)
3a		10
3b		10
3c		10
4		15
5a		7.5 (145) or 12.5 (218)
5b		7.5
total		85 (145) or 105 (218)

Name: *Solution.*

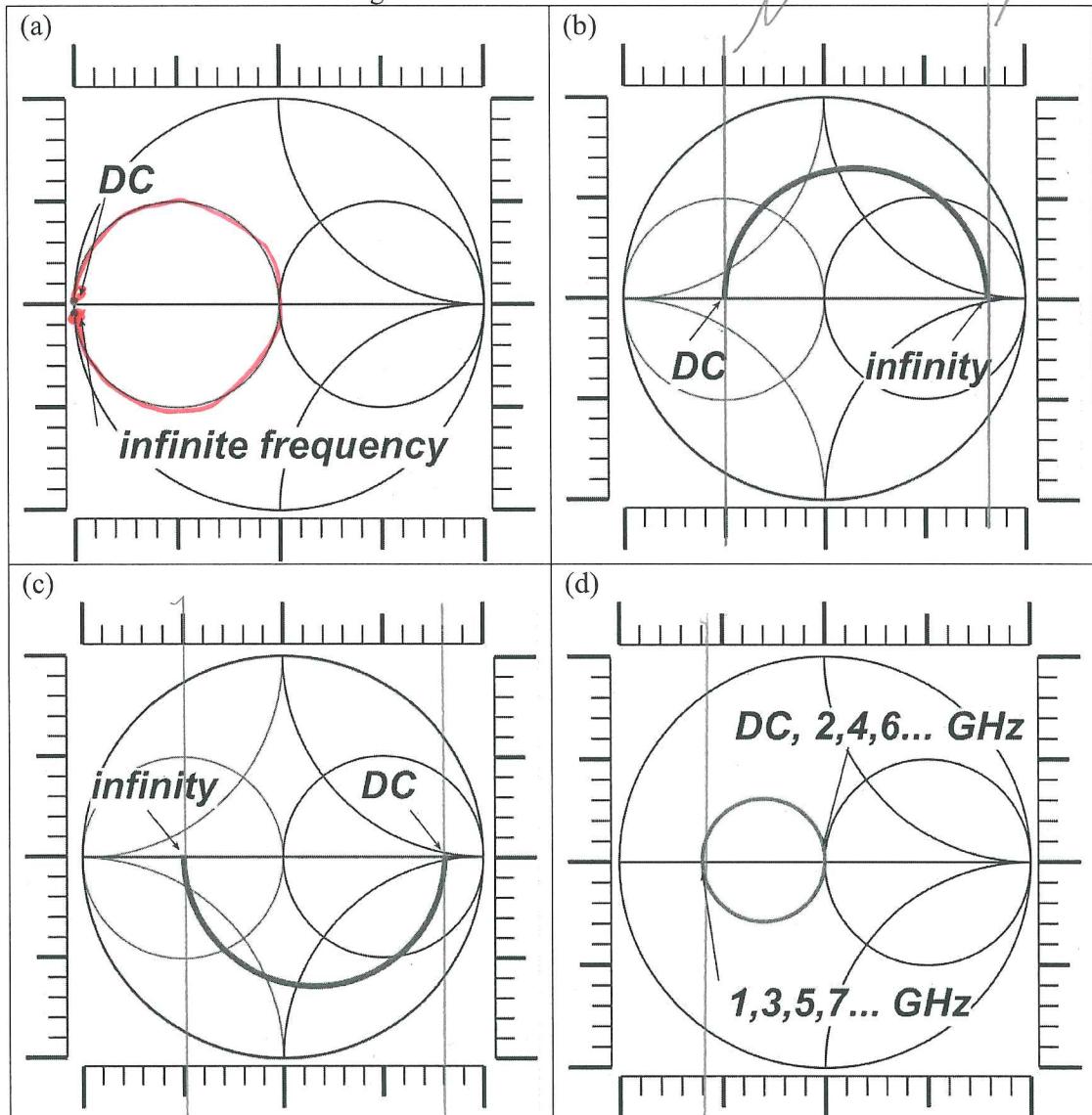Problem 1, 15 points

The Smith Chart and Frequency-Dependent Impedances.

HINT: use the scales on the figures to measure distances as needed.



$$1 \quad Y = -0.5 \quad Z = \frac{50}{3} \Omega$$


$$2 \quad Y = +0.8 \quad Z = 45\Omega$$


$$3 \quad Y = -0.6 \quad Z = \frac{0.4}{1.6} = \frac{1}{4}$$

$$2 \quad Y = 1.8 \quad Z = 0.2 \Omega$$

$$Z = 45\Omega$$

$$Z = 50 \Omega$$

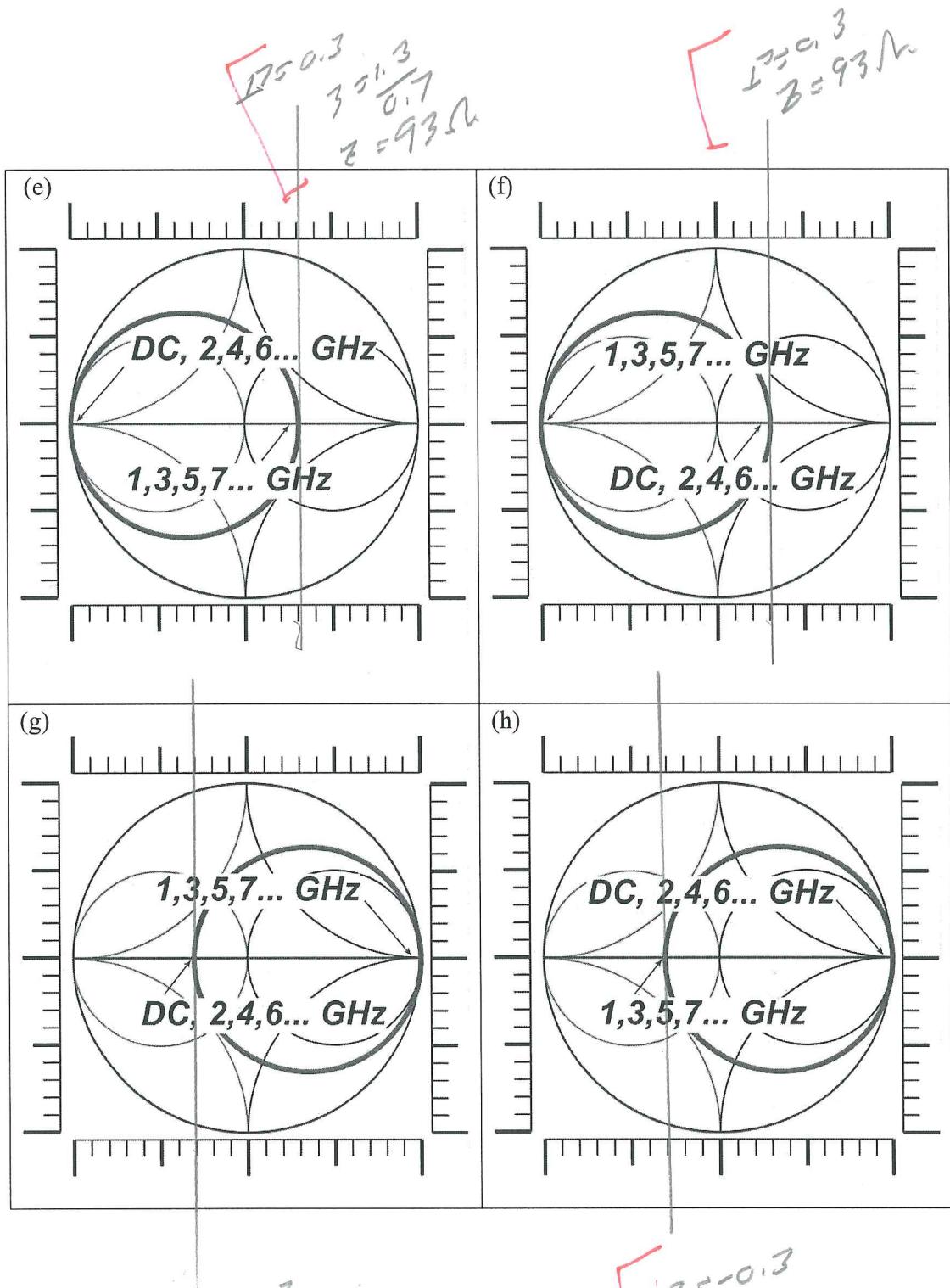

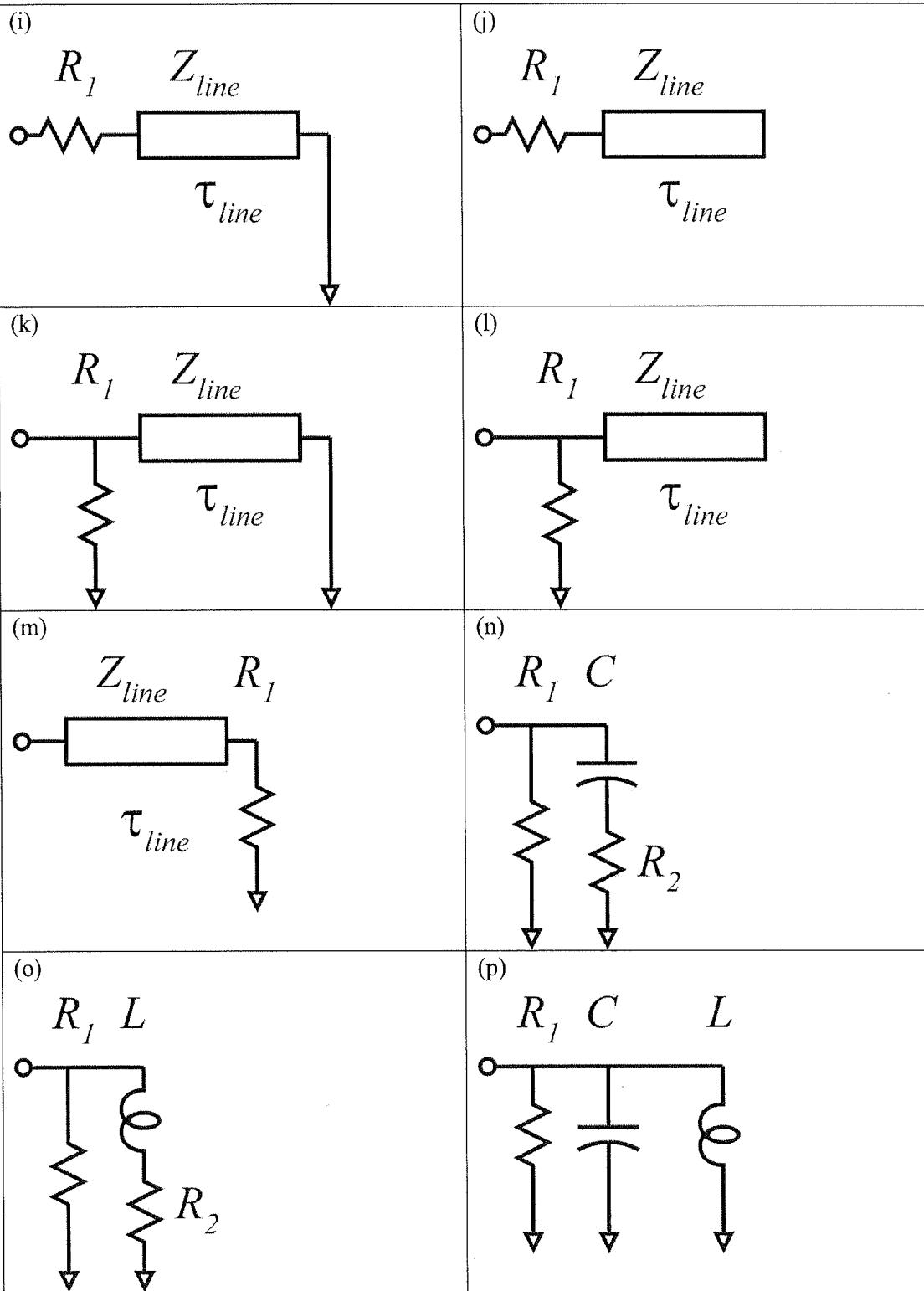

First match each Smith Chart with each circuit. ***Then determine as many component values as is possible*** (RLC values, transmission line delays and characteristic impedances)...note that some values cannot be determined with the information given. The charts all use 50 Ohm normalization:

- 2 Smith chart (a). Circuit= P.
 Component values: R = 50Ω, _____, _____,
- 2 Smith chart (b). Circuit= O.
 Component values: R₁ = 450Ω, R₂ = 17.3Ω, _____,
- 2 Smith chart (c). Circuit= N.
 Component values: R₁ = 450Ω, R₂ = 17.3Ω, _____,
- 2 Smith chart (d). Circuit= M.
 Component values: R = 50Ω, Z₀ = 25Ω, T = 1/4 ns.,
- 2 Smith chart (e). Circuit= K.
 Component values: R = 93Ω, T = 1/4 ns.,
- 2 Smith chart (f). Circuit= L.
 Component values: R = 93Ω, T = 1/4 ns.,
- 2 Smith chart (g). Circuit= i.
 Component values: R₁ = 27Ω, T = 1/4 ns.,
- 1 Smith chart (h). Circuit= j.
 Component values: R = 27Ω, T = 1/4 ns.,

Smith Chart D

Impedance is 50Ω @ DC, 2, 4, 6, ... GHz
is $50/\sqrt{2}$ @ 1, 3, 5, 7, ... GHz

2 \Rightarrow  This is a T-line with $R_L = 50\Omega$.
 $Z_0 = \sqrt{50 \cdot \frac{50}{4\pi^2}} = \frac{50}{\pi} \Omega = 25\Omega$.
 $\ell = 1/4 @ 16\text{GHz}$ so $\tau = \frac{4}{16\text{GHz}} \frac{1}{4} = \frac{1}{4\text{n}s}$.

Smith Chart E

or @ DC, 2, 4, 6 GHz,
 93Ω at 1, 3, 5, 7, 9 GHz

2 \Rightarrow  $R_L = 93\Omega$, Z_0 unknown.
line is $1/4 @ 16\text{GHz}$.
 $\tau = (1/4)/16\text{GHz} = 4\text{n}s$.

Smith Chart F

or @ 1, 3, 5, 7, ... GHz
 93Ω @ DC, 2, 4, ... GHz

2 \Rightarrow  $R_L = 93\Omega$, Z_0 unknown. line is $1/4 @ 16\text{GHz}$.
 $T = 4\text{n}s$.

Smith Chart G

27Ω @ DC, 2, 4, 6 GHz
DC @ 1, 3, 5, 7, 9 GHz

2 \Rightarrow  $R_L = 27\Omega$, $\tau = (1/4)/16\text{GHz} = 4\text{n}s$.

Smith Chart H


22Ω @ 1, 3, 5, 7, 9 ... GHz
DC @ 2, 4, 6 GHz

1 \Rightarrow  $R_L = 22\Omega$
 $\tau = (1/4)/(16\text{GHz}) = 1/4\text{n}s$.

Smith Chart A

2

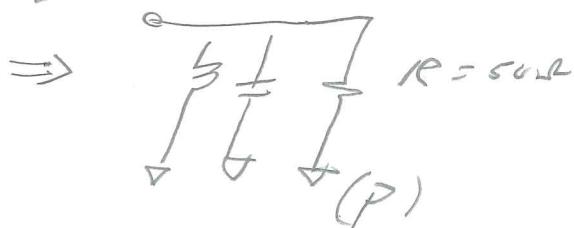This goes from $\infty \Omega$ at DC to 50Ω at some frequency to $\infty \Omega$ at $f = \infty$ Hz.




without more information,
we can't compute
 L or C .

Smith Chart B

2

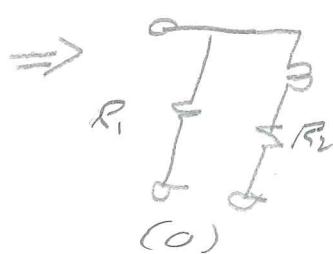goes from 16.66Ω (DC) to 450Ω ($f = \infty$) and is inductive



$$R_1 \parallel R_2 = \frac{17}{450}\Omega \rightarrow G_1 + G_L = 0.065,$$

$$R_1 = 450\Omega \rightarrow G_1 = 2.22mS,$$

$$G_L = 60mS - 2.22mS = 57.77mS$$


$$R_2 = 17.3\Omega.$$

Can't compute G

Smith Chart C

2

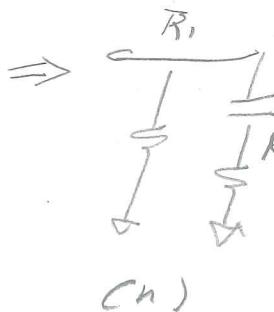goes from 450Ω (DC) to 16.66Ω ($f = \infty$)
and is capacitive



calculations for R_1 & R_2 are
the same as above.


$$R_2 = 17.3\Omega, R_1 = 450\Omega$$

Part c, ECE218A students only 15 points

For the network at the right, give algebraic expressions for the four S-parameters.


$$R_{be} \quad C_{be} \quad g_m V_{be}$$

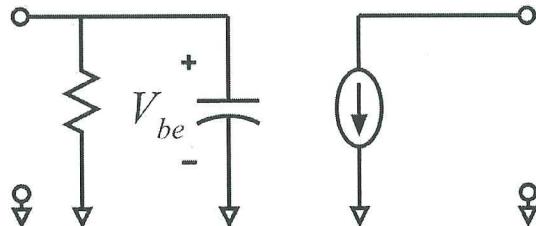Assume a normalization to impedance Z_0 for the S parameters.



$$1 [S_{12} = 0 \text{ (no connection)}]$$
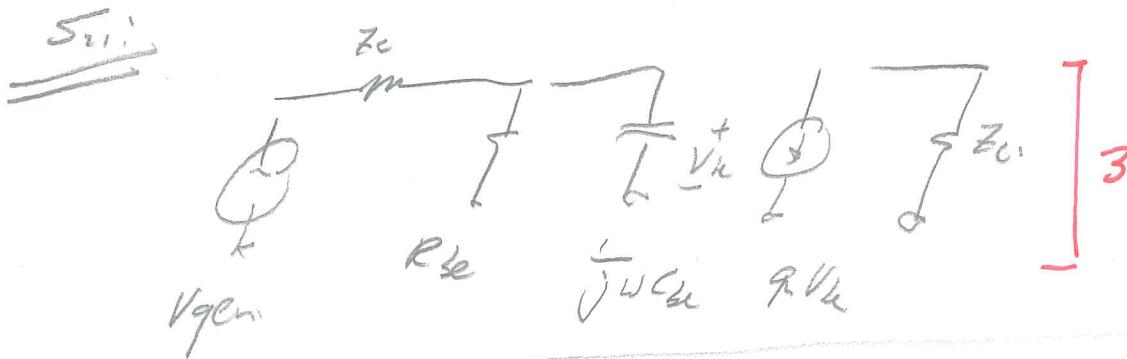
$$1 [S_{22} = 1 \text{ (} Z_{out} = \infty \text{)}]$$



$$3 \boxed{S_{21} = 2 \frac{V_o}{V_{be}} \Big|_{Z_0 = Z_L = Z_{be}} = -2g_m Z_0 \cdot \frac{R_{be}}{R_{be} + Z_0} \cdot \frac{1}{1 + jwC_{be}(R_L/Z_0)}}$$

$$3 \boxed{S_{11} = \frac{Z_{in}/Z_0 - 1}{Z_{in}/Z_0 + 1} = \frac{1 - Z_0/Z_L}{1 + Z_0/Z_L} = \frac{1 - Z_0 Y_{ii}}{1 + Z_0 Y_{ii}}}$$

$$Y_{ii} = G_{be} + j w C_{be}$$



$$\boxed{S_{11} = \frac{1 - G_{be} Z_0 - j w C_{be} Z_0}{1 + G_{be} Z_0 + j w C_{be} Z_0}}$$

$$3 \boxed{= \frac{1 - G_{be} Z_0}{1 + G_{be} Z_0} - X^{12} \frac{1 - j w C_{be} Z_0 / (1 - G_{be} Z_0)}{1 + j w C_{be} Z_0 / (1 + G_{be} Z_0)}}$$

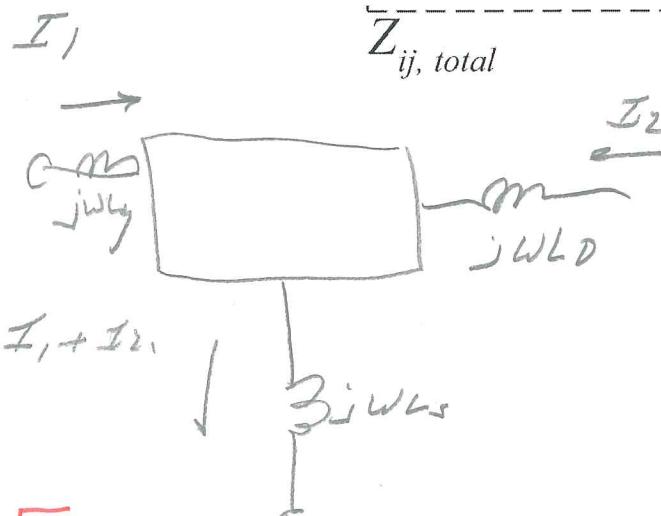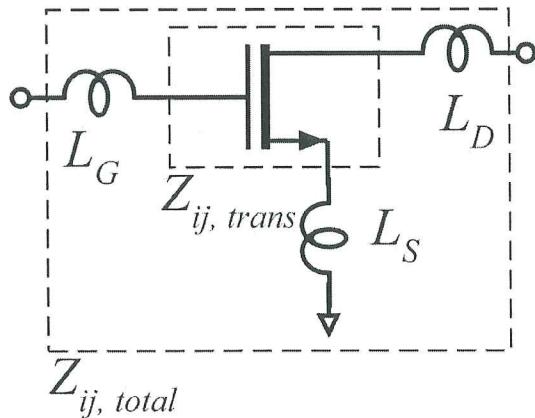Part b, 15 points

A transistor has four Z-parameters $Z_{ij,trans}$.

Derive algebraic expressions for the four Z-parameters of the overall network $Z_{ij,total}$



before

$$s \begin{bmatrix} V_1^{TRANS} = Z_{11}^T I_1 + Z_{12}^T I_2 \\ V_2^{TRANS} = Z_{21}^T I_1 + Z_{22}^T I_2 \end{bmatrix}$$

but

$$s \begin{bmatrix} V_1^{total} = (j\omega L_g + j\omega L_s) I_1 + j\omega L_s I_2 + V_1^{TRANS} \\ V_2^{total} = j\omega L_s I_1 + (j\omega L_d + j\omega L_s) I_2 + V_2^{TRANS} \end{bmatrix}$$

5.



$$\boxed{\begin{bmatrix} Z_{ij}^{total} = \begin{bmatrix} Z_{11}^{TRANS} + j\omega L_g + j\omega L_s & Z_{12}^{TRANS} + j\omega L_s \\ Z_{21}^{TRANS} + j\omega L_s & Z_{22}^{TRANS} + j\omega L_g + j\omega L_d \end{bmatrix} \end{bmatrix}}$$

Problem 2, 25 points (ece145A), 40 points (ece218A)
2-port parameters and Transistor models

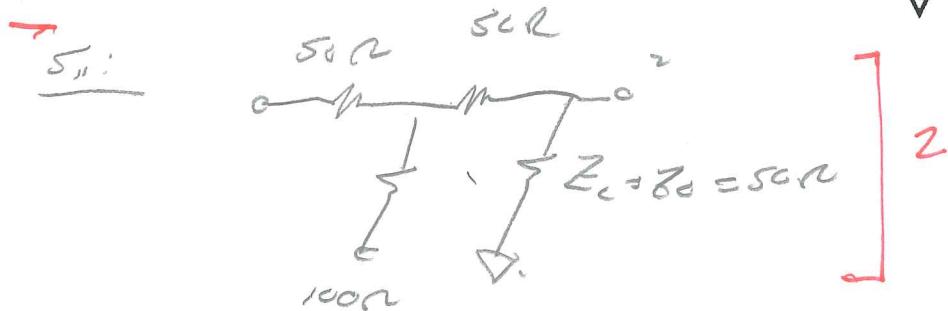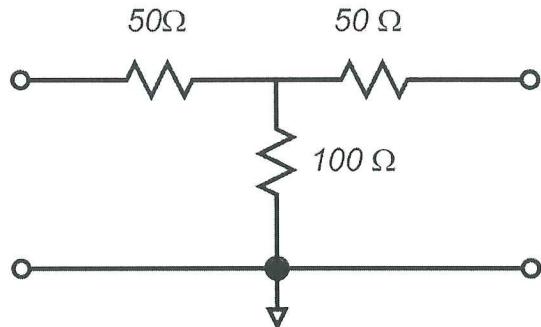Part a, 10 points


For the network at the right, give numerical values for the four S-parameters. Assume that the reference Z_0 is 50 Ohms.

$$S = \begin{bmatrix} 1/3 & 1/3 \\ 1/3 & 1/3 \end{bmatrix}$$



$$1 \left[\frac{Z_L}{Z_L + Z_0} = 50\Omega + 100\Omega // (50\Omega + 50\Omega) \right] \Rightarrow S_{11} = 1/3$$
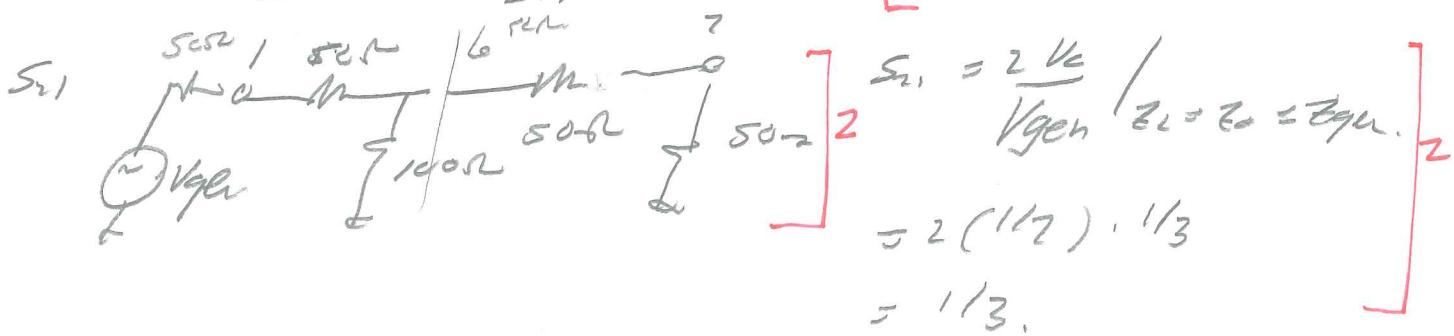
$$1 \left[S_{11} = \frac{2-1}{2+1} = 1/3 \right] \quad 1 \left[S_{22} = 1/3 \text{ by symmetry} \right]$$



$$1 \left[S_{12} = 1/3 \text{ by symmetry} \right]$$

$$\frac{1}{2} \left[\frac{1}{Z_0} = 1 \right]$$

$$\frac{1}{2} \left[\frac{1}{Z_0} = \frac{50}{50 + 50/3} = \frac{50}{40/3} = \frac{3/4}{1/3} = \frac{3}{4} \right]$$




$$\frac{1}{2} \left[Z_S = \frac{1/3 - 1}{1/3 + 1} = \frac{-2/3}{4/3} = -\frac{1}{2} \right]$$

Part b, 7.5 points

RL is infinite. Rgen is $(50/3)$ Ohms.

Plot $V_{out}(t)$ on the graph below.

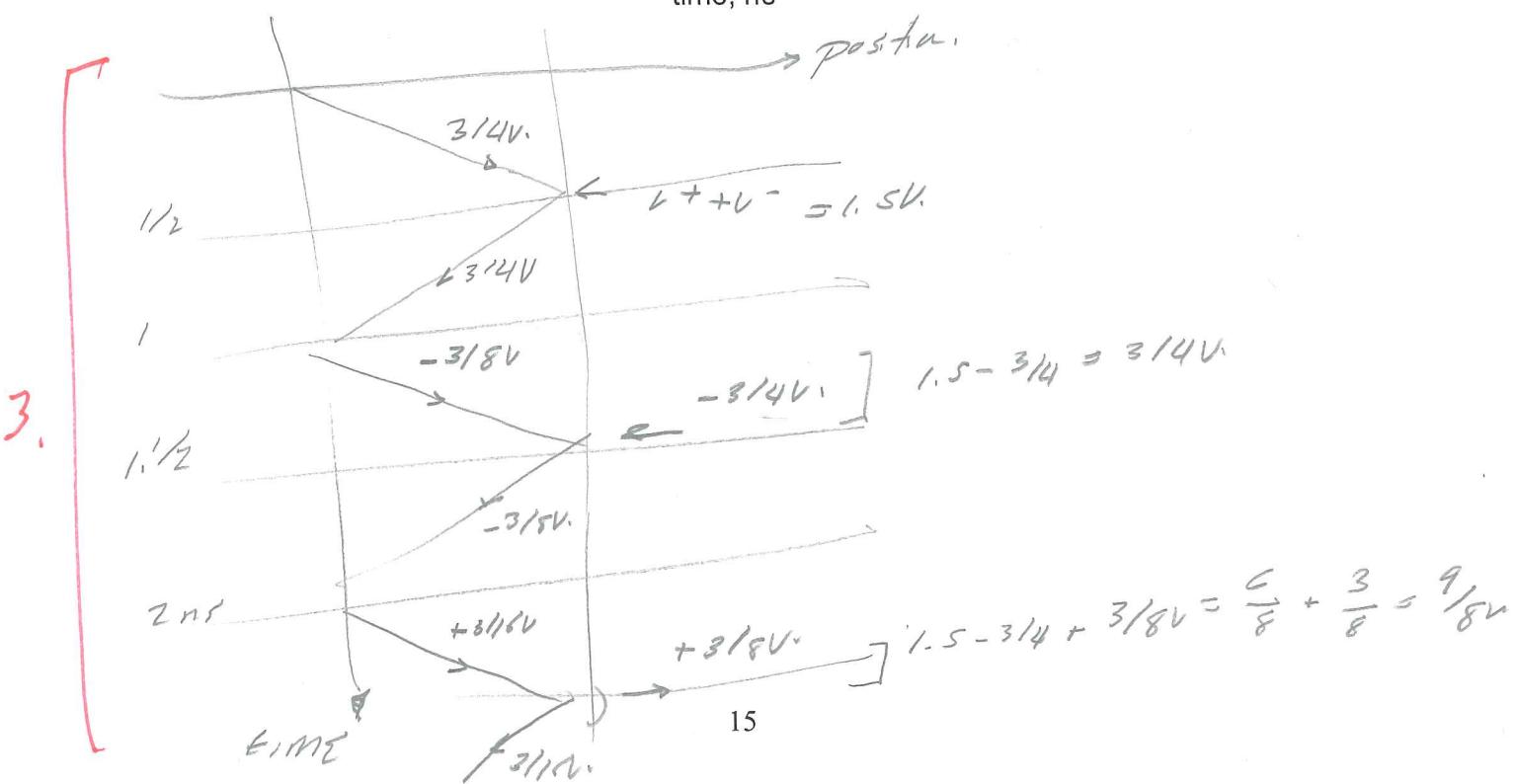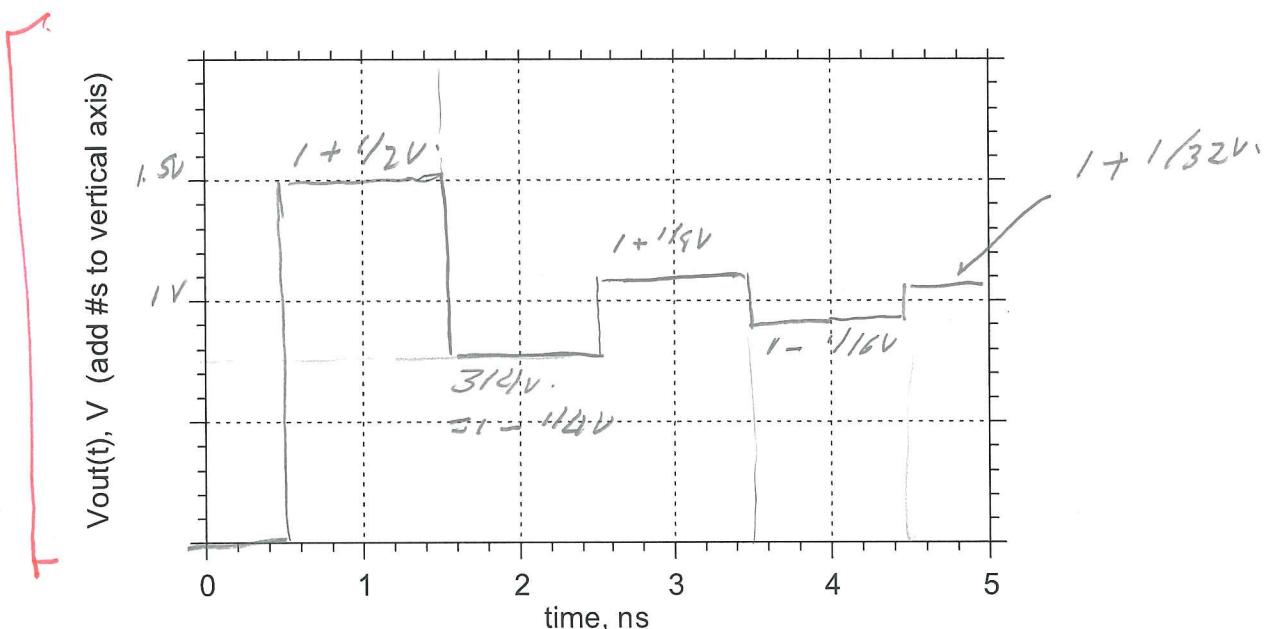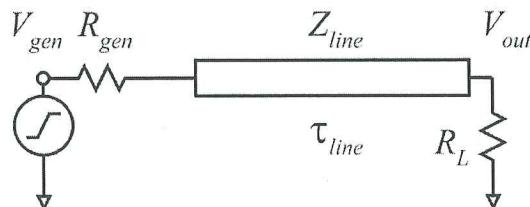Does the step response of the line appear inductive, capacitive, both, or neither?



$$1/2 [L_2] = 1$$

$$1/2 \left[T_S = \frac{50\Omega}{150\Omega + 50\Omega} = 1/4 \right]$$

$$1/2 \left[L_S = \frac{3-1}{3+1} = 1/2 \right]$$

Problem 3, 15 points

Transmission lines in the time domain.




Part a, 7.5 points

V_{gen} is a 1V step-function occurring at $t=0$ seconds. Z_{line} is 50 Ohms. τ_{line} is $1/2$ ns.

R_L is infinite. R_{gen} is 150 Ohms.

Plot $V_{out}(t)$ on the graph below.

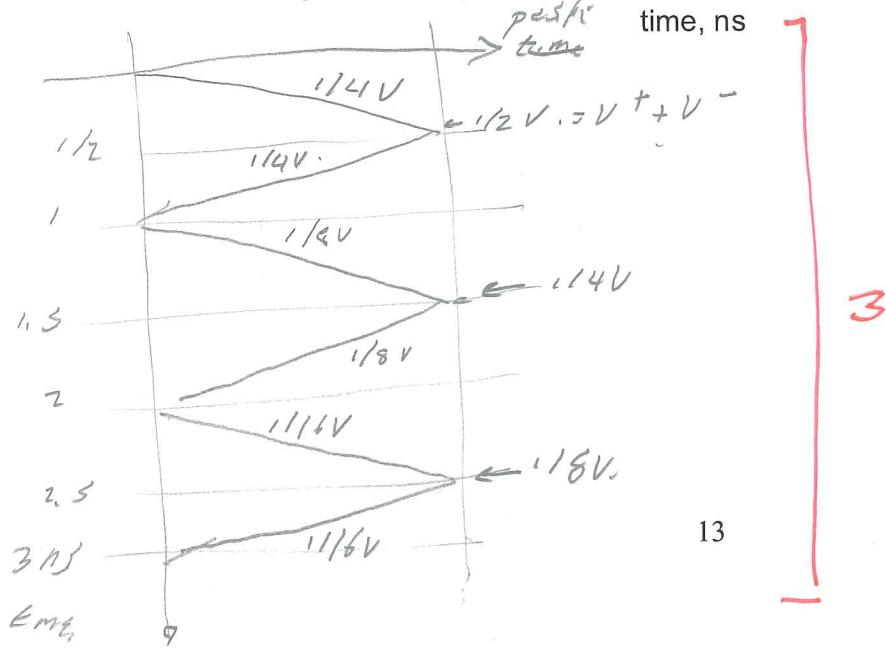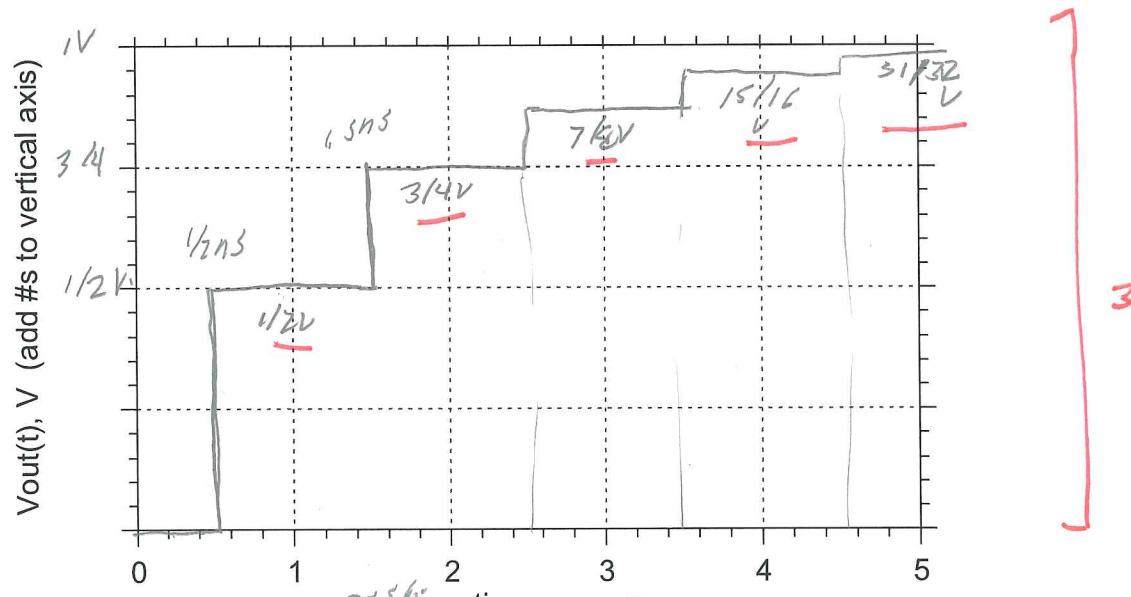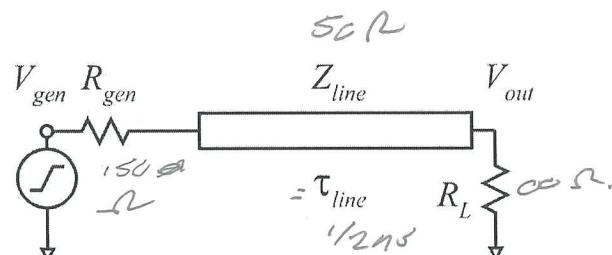
Does the step response of the line appear inductive, capacitive, both, or neither?




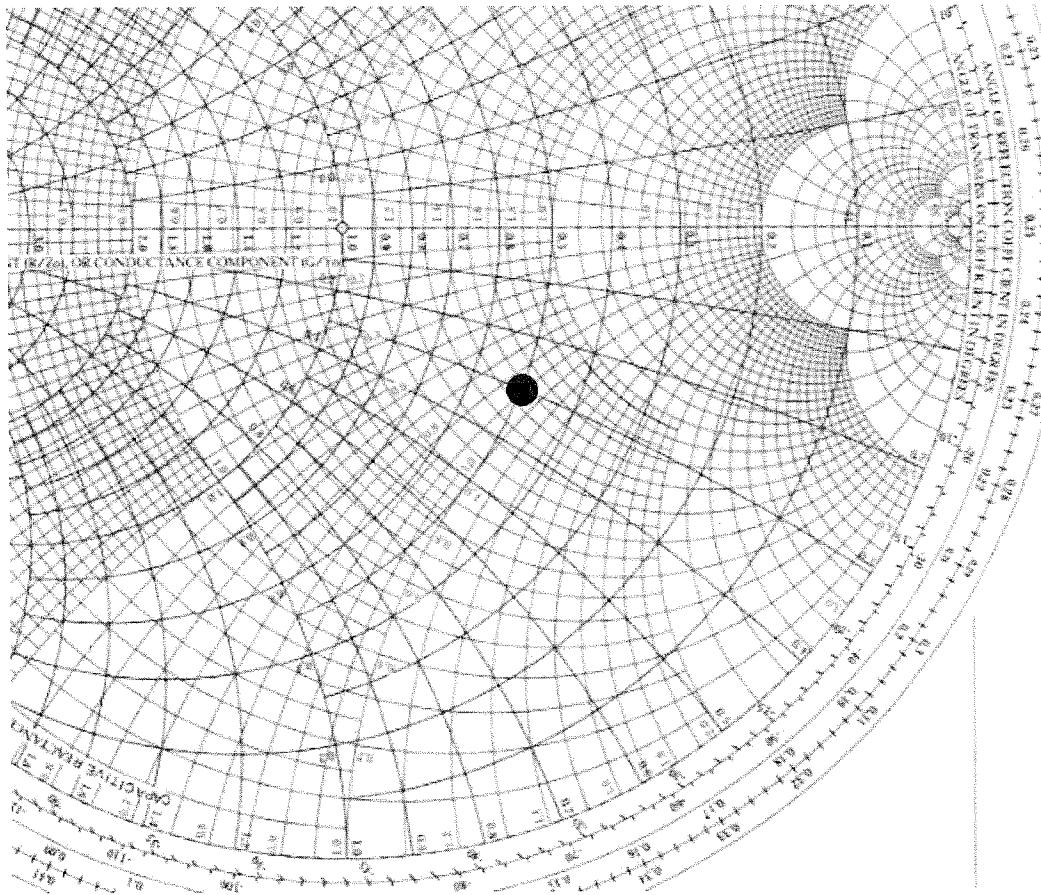Problem 4, 15 points

Impedance-matching exercise.

The (50 Ohm normalization) Smith chart gives the input impedance of a circuit at 10 GHz signal frequency. Design a lumped-element matching network which converts this impedance to **50Ohms** at 10 GHz. Give all element values. Use the full impedance-admittance chart which has been provided to you.



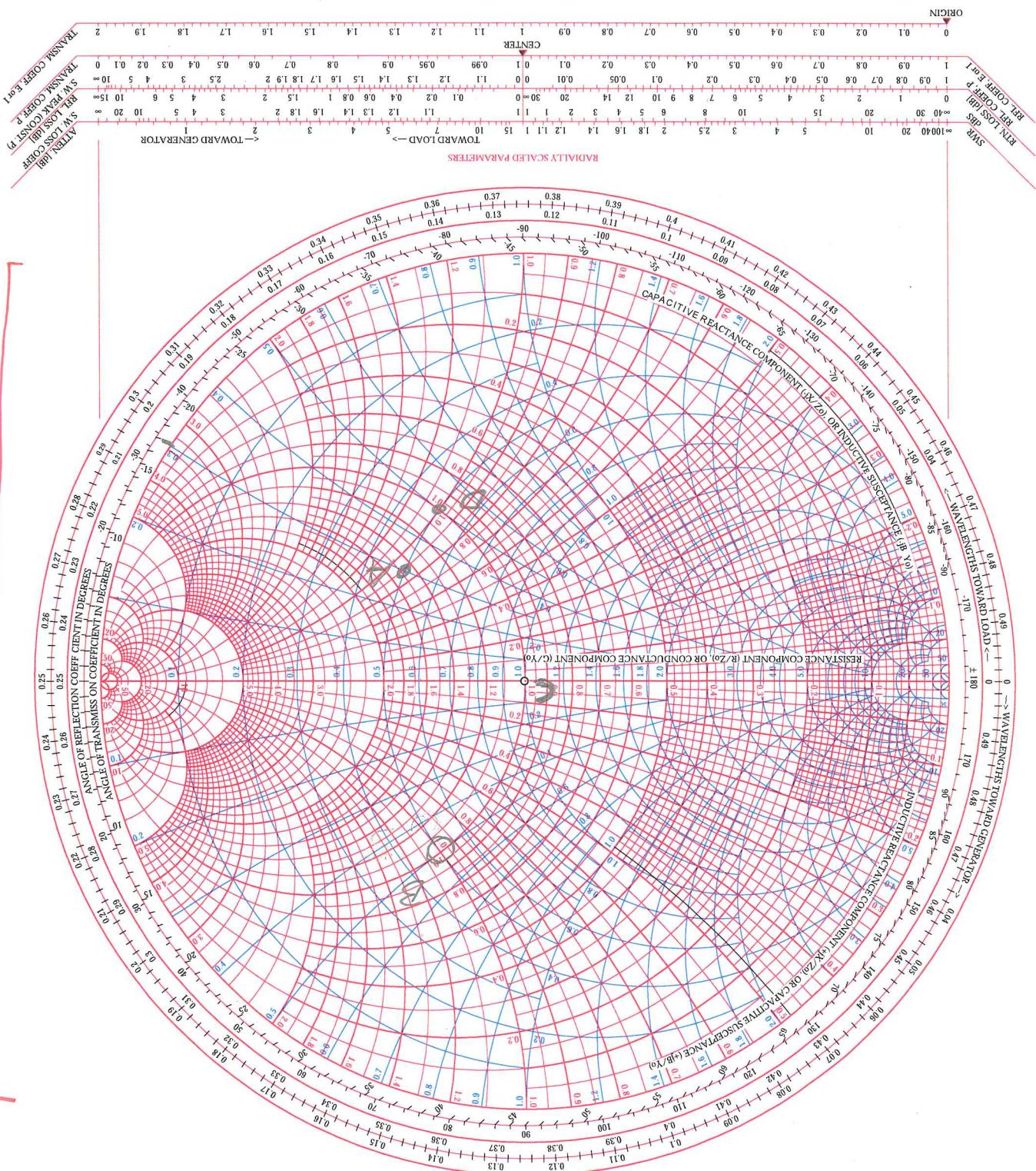

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES

NAME	TITLE	DATE	SMITH CHART FORM ZY-01-N	
			DWG. NO.	MICROWAVE CIRCUIT DESIGN - EEE523 - FALL 2000

There are two solutions. A-B-C & A-D-C

A-B-C

point A: $\underline{y} = 0.5 + j0.3 \quad]'$

point B: $\underline{y} = 0.5 - j0.5 \quad]'$

$$\Delta y = -j0.8 \quad]'$$

$$\Delta Y = \Delta y \cdot Z_0 = -j \cdot 16 \text{ mS} = \frac{1}{j\omega L} \quad]'$$

$$\Rightarrow L = \frac{1}{16 \text{ mS} (2\pi \cdot 106 \text{ Hz})} = 0.99 \text{ nH.} \approx 1 \text{ nH.} \quad]'$$

point B $\underline{z} = 1 + j1 \quad]'$

point C $\underline{z} = 1 + j0. \quad]'$

$$\Delta z = -j1 \quad]'$$

$$\Delta Z = \Delta z \cdot Z_0 = -j \cdot 50 \Omega = \frac{1}{j\omega C} \quad]'$$

$$\Rightarrow C = \frac{1}{50 \Omega} \frac{1}{2\pi(106 \text{ Hz})} = 0.32 \text{ pF} \quad]'$$

~~32 pF~~



ADC

Point A: $\underline{Y} = 0.5 + j0.3 \quad]'$

Point D: $\underline{Y} = 0.5 + j0.5 \quad]'$

$\Delta Y = +j0.2 \quad]'$

$$\Delta Y = \Delta Y / Z_0 = \frac{j0.2}{50\Omega} = +j \cdot 4 \text{ mS.} = j \omega C \quad]'$$

$$\Rightarrow C = \frac{4 \text{ mS}}{2\pi(10 \text{ MHz})} = 64 \text{ fF} \quad]'$$


Point D $\Rightarrow \underline{Z} = 1 - j1 \quad]'$

Point C $\Rightarrow \underline{Z} = d + j0 \quad]'$

$\Delta Z = +j1 \quad]'$

$$\Delta L = \sqrt{50\Omega} = j \omega L \quad]'$$
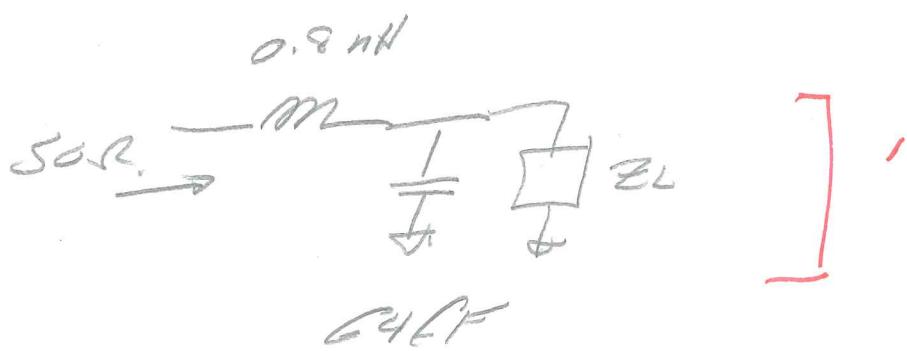
$$L = \frac{50\Omega}{2\pi(10 \text{ MHz})} = 0.8 \text{ nH.} \quad]'$$




Problem 5, 15 points (ece145A), 20 points (218A)
Transmission-line parasitics.

Part a, 7.5 points (145A), 12.5 points (218A)

We are designing a microstrip line and calculating its properties. We will assume dimensions typical of a dielectric stack on an IC: the signal and ground planes are separated vertically by $5 \mu\text{m}$, and the dielectric constant is 3.8.

If we approximate the effective conductor width as being the physical conductor width plus the dielectric thickness then (1) what width is required for a 50 Ohm characteristic impedance ?

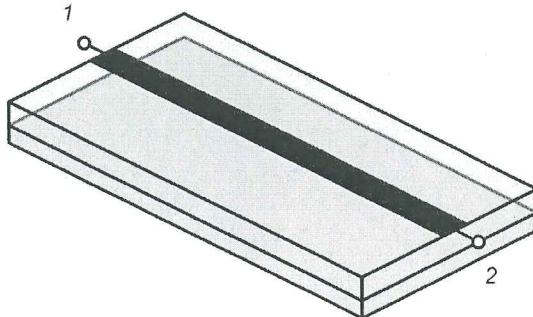If the line were 300 microns length, what is the total wiring inductance and total wiring capacitance in that length ?



$$W = 14.33 \mu\text{m}$$

$$L = 97.5 \mu\text{H}$$

$$C = 38.9 \text{ fF}$$

ECE 218 students only (5 more points)

The conductivity of copper is

59.6×10^6 Siemens/meter and

$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$. Find the skin depth, the attenuation constant α , and the total line attenuation at 60GHz signal frequency.

Hint----the skin depth is $\delta = \sqrt{2/\alpha\mu_0\sigma}$

line width required for $Z_0=50$ Ohms; $W = 14 \mu\text{m}$

total inductance in 100 microns $L = 97.5 \mu\text{H}$

total capacitance in 100 microns $C = 38.9 \text{ fF}$

skin depth $\delta = 0.266 \mu\text{m}$

attenuation constant alpha = 160 (nepers/meter)

total attenuation, $S_{21} =$ _____ (dB)

$1384 \text{ dB/m or } 1.38 \text{ dB/m}$

Part b, 7.5 points

Using the very crude approximation that the effective conductor width is the physical conductor width plus the substrate thickness, what is the highest characteristic impedance which we can obtain ?

Assuming a signal frequency of 60 GHz, what is the maximum conductor width allowable to suppress propagation of parasitic *transverse* modes on the conductor ?


Setting a practical limit of width 2:1 smaller than that, what would be the resulting Z_0 .

Maximum feasible $Z_0 = \underline{193 \Omega}$.

Minimum feasible $Z_0 = \underline{\quad}$

Maximum width to prevent transverse modes at 60 GHz $W = \underline{1.3 \text{ mm}}$.

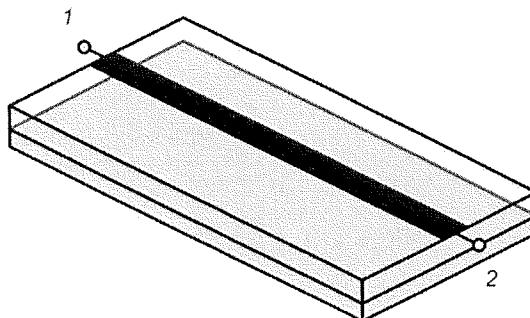Characteristic impedance with width set to 1/2 of the above, $Z_0 = \underline{1.5 \Omega}$



$$\sqrt{\frac{M_0}{\epsilon_0}}$$

very approx. method

$$2 \left[Z_0 = \frac{377 \Omega}{\sqrt{\epsilon_r}} \cdot \frac{H}{H+w} = 193.4 \Omega \cdot \frac{1}{1+w/H} = 50 \Omega \right]$$

$$1+w/H = \frac{193.4 \Omega}{50 \Omega} = w/N = 2.87 \rightarrow w = \underline{14.33 \mu m}$$

$$\text{velocity} = \frac{c}{\sqrt{\epsilon_r}} \Rightarrow \text{delay} = \tau = \frac{l}{c} \cdot \sqrt{\epsilon_r} = 1.95 \mu s.$$

$$2 \left[c = Z_0 \cdot \tau = 50 \Omega \cdot 1.95 \mu s = 97.5 \mu m \right]$$

$$2 \left[c = \tau / \tau_0 = 38.9 \text{ ft} \right]$$

$$1 \left[\delta = \sqrt{2 / \omega_{pe}} = 0.266 \mu m @ 60.6 \text{ kHz} \right]$$

$$1 \left[R_{series/lc} = \frac{1}{\delta \sigma} \cdot \left[\frac{1}{\omega} + \frac{1}{\omega + N} \right] \right. \\ \left. = 15.9 \frac{14 \mu m}{12 \mu m} \text{ kohm/meter} \right]$$

$$1 \left[\alpha = \frac{R_{series}}{L} = \frac{\sigma l}{2 Z_0} = 78.2 \text{ 1/m} \right]$$

$$2 \left[\text{attenuation} = 300 \mu m \quad S_{21} = e^{-\alpha l} \right]$$

$$dB S_{21} = 20 \log_{10}(0.977) \\ = -0.20 dB$$

ok for the short line..

2.5

$$Z_0 = 193\Omega \cdot \frac{1}{1 + w/H} \rightarrow \text{approx., mdy } 193\Omega \text{ when } w \rightarrow 0$$

(actual variation of Z_0 with $w/H \ll 1$ is \approx logarithmic in w/H)

2.5

$$\begin{aligned} \text{max. man width: } \quad g_{1/2} &= \frac{1}{2} \frac{c}{60918 \sqrt{\epsilon_r}} = 1.3 \text{ mm.} \\ \text{pract. width: } &640 \mu\text{m} \end{aligned}$$

2.5.

$$Z_0 = 193\Omega \cdot \frac{H}{w} = 193\Omega \cdot \frac{\frac{5 \mu\text{m}}{150 \mu\text{m}}}{\frac{640 \mu\text{m}}{640 \mu\text{m}}} = 1.5\Omega$$

this has turned out to be a bad example
 - we would never make a line this wide with
 5 μm thickness