

ECE ECE145A (undergrad) and ECE218A (graduate)

Mid-Term Exam. November 2, 2017

Do not open exam until instructed to.

Open notes, open books, etc.

You have 1 hr and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.) , ***AFTER STATING THEM.***


Problem	Points Received	Points Possible
1		15
2a		10
2b		15
2c (218 only)		15 (218)
3a		10
3b		10
3c		10
4		15
5a		7.5 (145) or 12.5 (218)
5b		7.5 (145) or 10(218)
total		85 (145) or 107.5 (218)


Name: _____

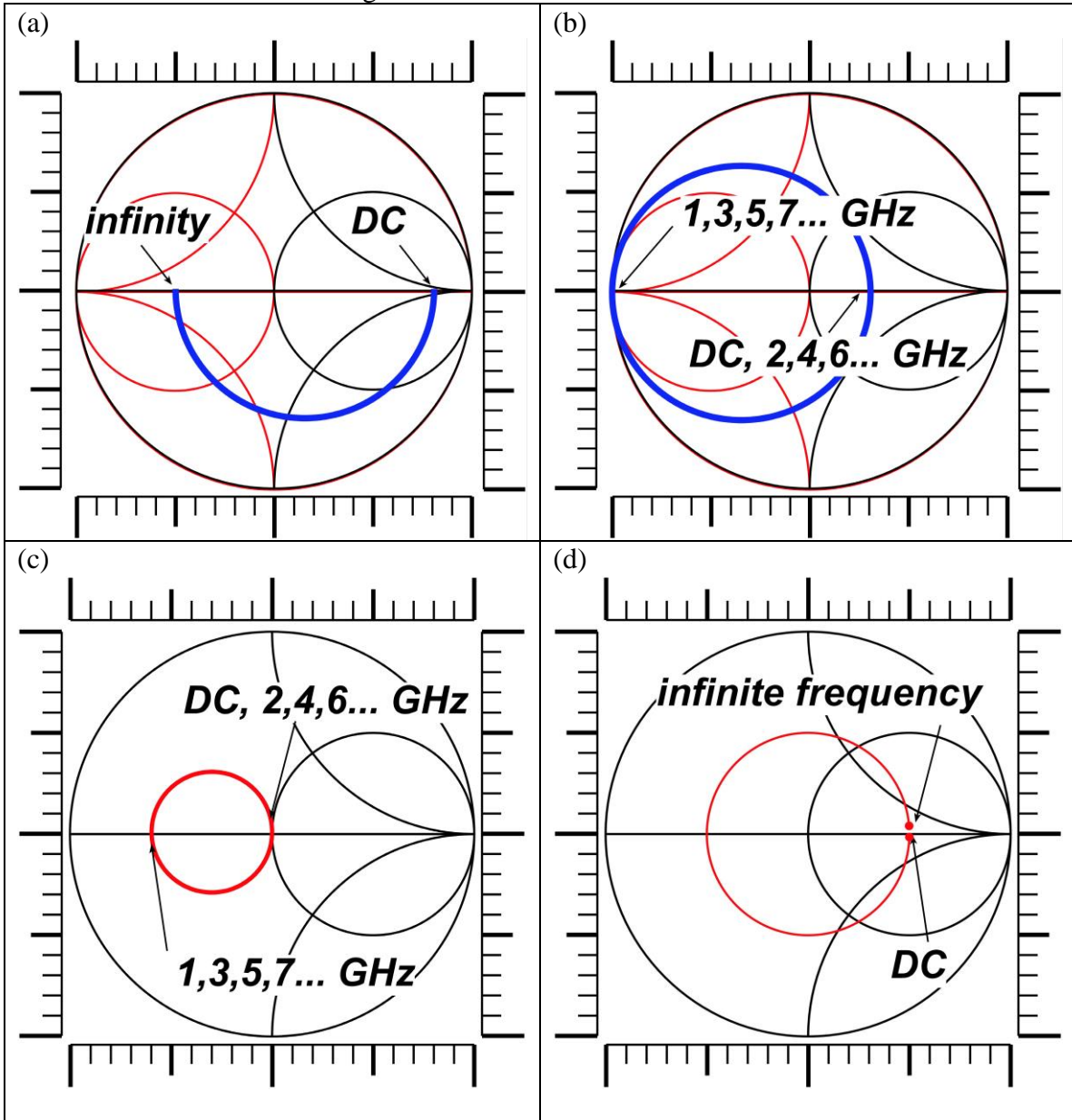
Problem 1, 15 points

The Smith Chart and Frequency-Dependent Impedances.

HINT: use the scales on the figures to measure distances as needed.



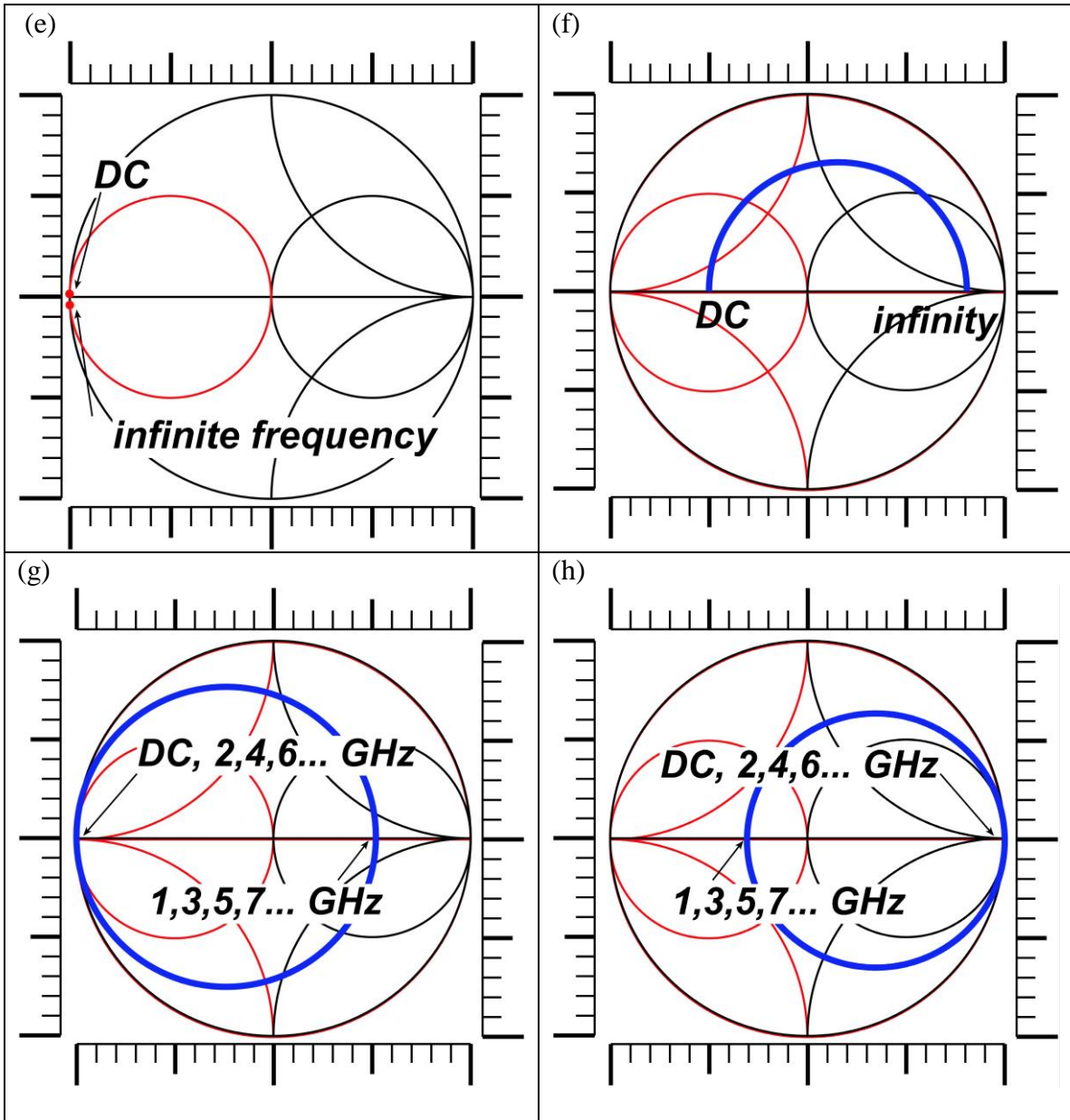

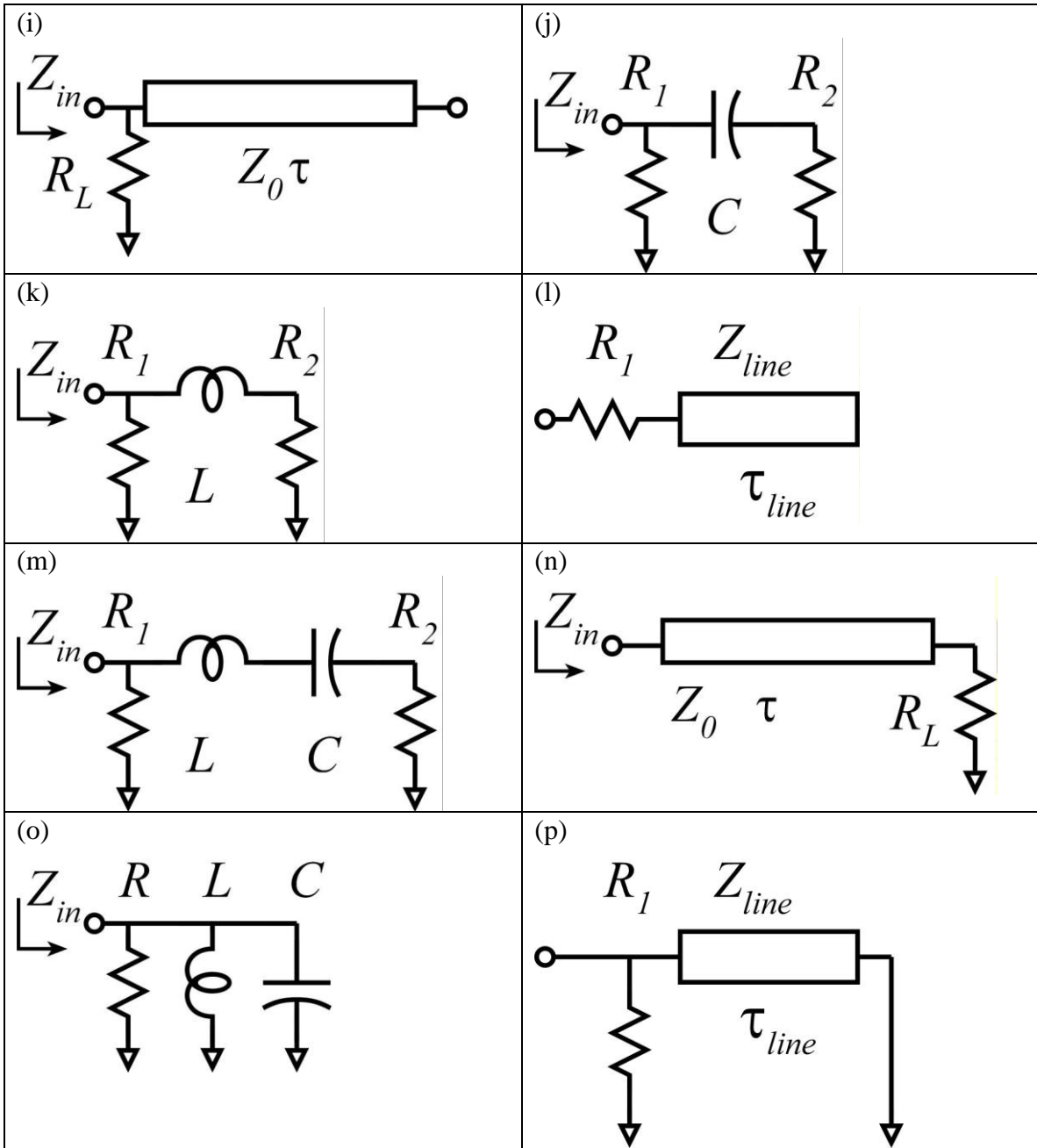


First match each Smith Chart with each circuit. ***Then determine as many component values as is possible*** (RLC values, transmission line delays and characteristic impedances)...note that some values cannot be determined with the information given. The charts all use 50 Ohm normalization:

- Smith chart (a). Circuit=_____.
Component values: _____, _____, _____,
- Smith chart (b). Circuit=_____.
Component values: _____, _____, _____,
- Smith chart (c). Circuit=_____.
Component values: _____, _____, _____,
- Smith chart (d). Circuit=_____.
Component values: _____, _____, _____,
- Smith chart (e). Circuit=_____.
Component values: _____, _____, _____,
- Smith chart (f). Circuit=_____.
Component values: _____, _____, _____,
- Smith chart (g). Circuit=_____.
Component values: _____, _____, _____,
- Smith chart (h). Circuit=_____.
Component values: _____, _____, _____,

Problem 2, 25 points (ece145A), 40 points (ece218A)
2-port parameters and Transistor models

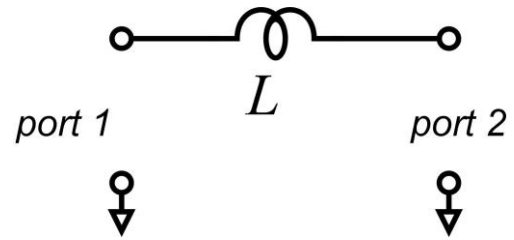Part a, 10 points


For the network at the right, give numerical values for the four S-parameters. Assume that the reference Z_0 is 50 Ohms.



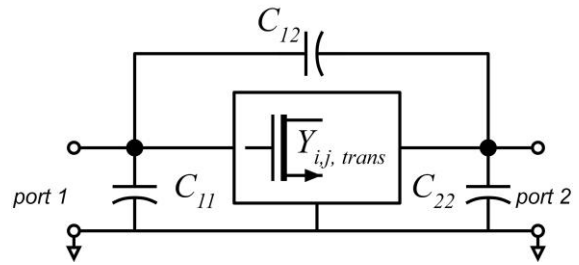Part b, 15 points

A transistor has four Y-parameters $Y_{ij,trans}$.


Derive algebraic expressions for the four Y-parameters of the overall network $Y_{ij,total}$



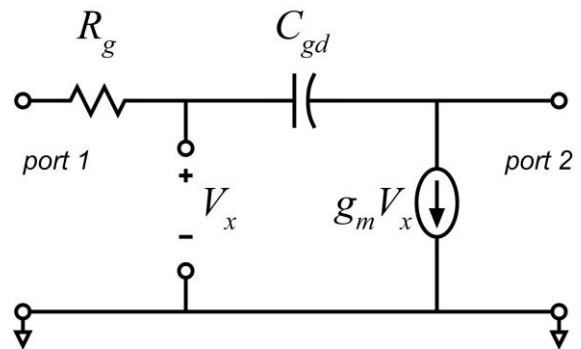Part c. ECE218A students only 15 points

For the network at the right, give an algebraic expressions for Y_{12} and Y_{22} . Please write as a Taylor series in $j\omega$, omitting terms of power $(j\omega)^3$ and higher.

This is an exercise in device model extraction from measured S/Y/Z parameters.



Problem 3, 15 points


Transmission lines in the time domain.

Part a, 7.5 points


V_{gen} is a 1V step-function occurring at $t=0$ seconds. Z_{line} is 50 Ohms. τ_{line} is 1 ns.

R_L is 5 Ohms. R_{gen} is 5 Ohms.

Plot $V_{out}(t)$ on the graph below.

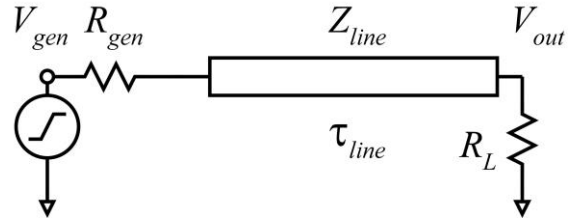

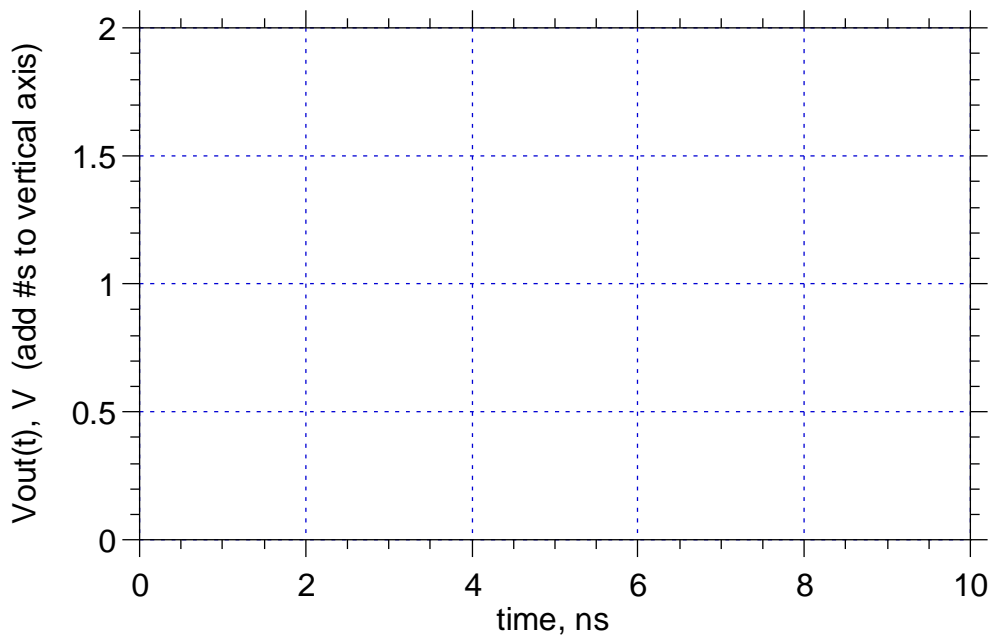Does the step response of the line appear inductive, capacitive, both, or neither ?





Part b, 7.5 points

V_{gen} is, again, a 1 V step-function.

R_{gen} is 50 Ohms and R_L is 100 Ohms.

τ_1 and τ_2 are both 1/2 ns


Plot below $V_{out}(t)$ and $V_1(t)$

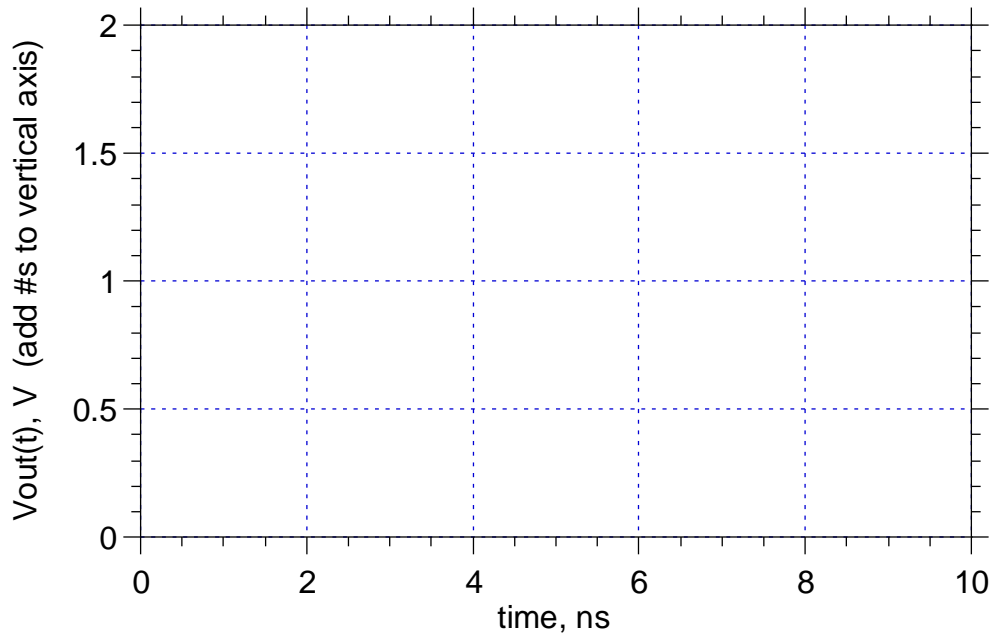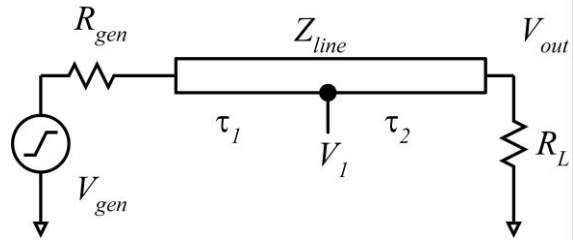

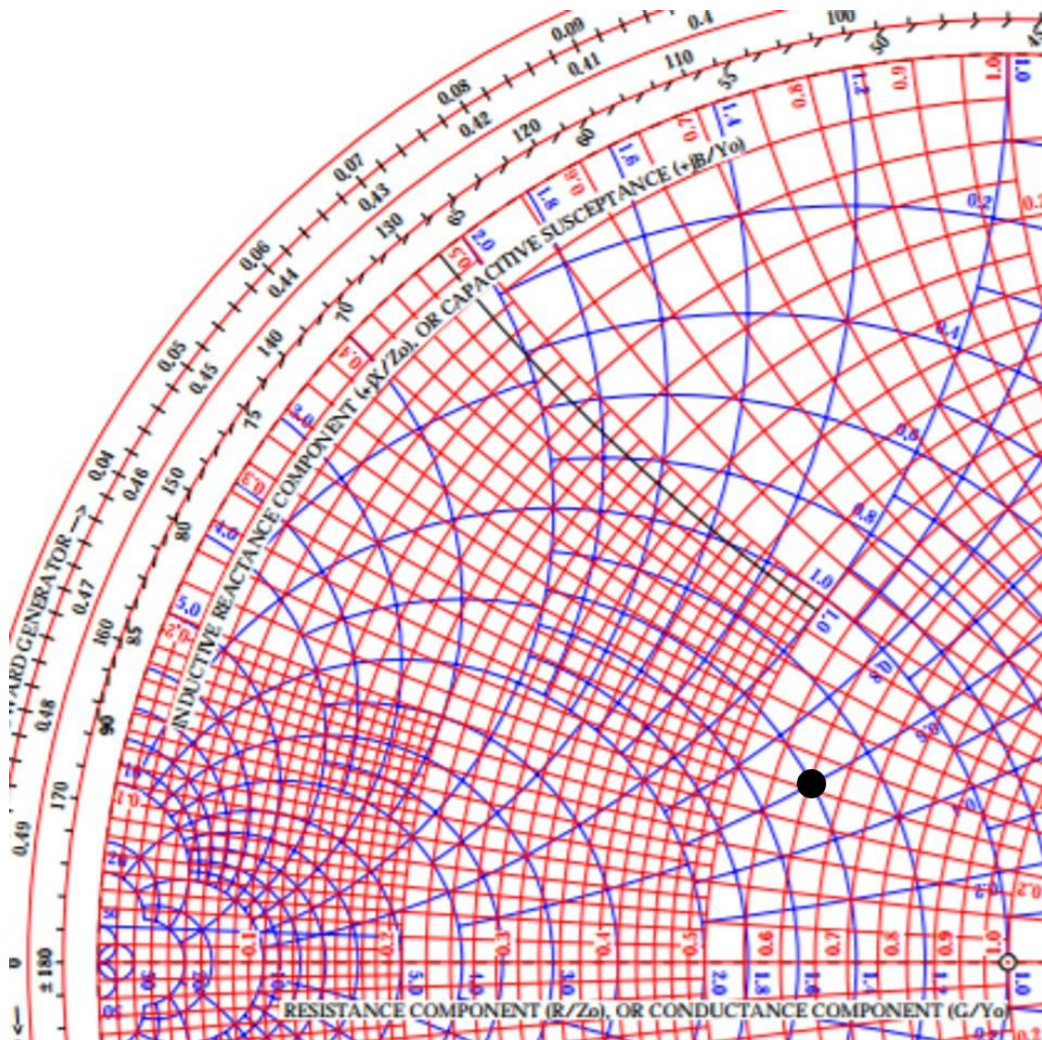Problem 4, 15 points

Impedance-matching exercise.

The (50 Ohm normalization) Smith chart gives the input impedance of a circuit at 10 GHz signal frequency. Design a lumped-element matching network which converts this impedance to **50 Ohms** at 3 GHz. Give all element values. Use the full impedance-admittance chart which has been provided to you.



Problem 5, 15 points (ece145A), 20 points (218A)

Transmission-line properties.

Part a, 7.5 points (145A), 12.5 points (218A)

We have designed a transmission-line impedance-matching network, as shown on the right.

$Z_{o2}=75$ Ohms, $\tau_2=100$ ps

$Z_{o1}=25$ Ohms, $\tau_1=75$ ps


This is constructed on a circuit board whose dielectric constant is 3.8 and whose thickness is 1mm. Neglecting fringing fields, determine the length and width of both lines.

line 1 length=_____

line 1 width=_____

line 2 length=_____

line 2 width=_____

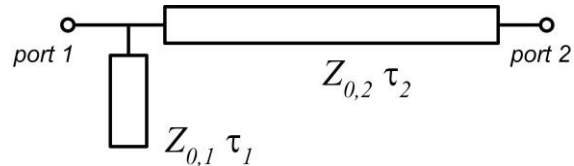

ECE 218 students only (5 more points)

The conductivity of copper is

$59.6 \cdot 10^6$ Siemens/meter and

$\mu_0 = 4\pi \cdot 10^{-7}$ H / m . For line 2, Find the total line attenuation at 1.25GHz signal frequency.

Hint----the skin depth is $\delta = \sqrt{2 / \omega \mu_0 \sigma}$

line 2 attenuation, dB = _____

Part b, 7.5 points

We are using these transmission-lines at 1.25GHz. Representing line 2 as a Pi network and line 1 as a T network, draw an approximate lumped-element equivalent circuit for the matching network, giving element values. **ECE 218 students only (2.5 more points)** please be sure to include the equivalent skin-effect resistance for both line sections.

