

**ECE ECE145A (undergrad) and ECE218A (graduate)**  
**Final Exam. Monday December 9, 2019, noon - 3 p.m**

Open book. You have 3 hrs.

Use all reasonable approximations (5% accuracy is fine.) ,

**AFTER STATING and justifying THEM.**

**Think before doing complex calculations. Sometimes there is an easier way.**

Problem	Points Received	Points Possible
1A		5
1B		5
1C		7 (218A only)
2A		5
2B		10
3A		5
3B		10 (218A only)
3C		5
3D		10
4A		5
4B		5
4C		5
4D		10
5A		7
5B		5
5C		10 (218A only)
total		87(145A), 114 (218A)

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)(1 - |\Gamma_L|^2)}{|(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - S_{21} S_{12} \Gamma_s \Gamma_L|^2} \quad G_P = \frac{1}{1 - \|\Gamma_{in}\|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2}$$

$$G_a = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - \|\Gamma_{out}\|^2} \quad G_{\max} = \frac{|S_{21}|}{|S_{12}|} \cdot [K - \sqrt{K^2 - 1}] \text{ if } K > 1$$

$$G_{MS} = \frac{|S_{21}|}{|S_{12}|} \cdot \text{if } K < 1 \quad K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{21} S_{12}|} \quad \text{where } \Delta = \det[S]$$

Unconditionally stable if : (1)  $K > 1$  and (2)  $\|\det[S]\| < 1$



**Problem 1, 10 points (145A), 17 points (218A)**  
*Transistor two-port properties, Gain relationships*

Device model:


$$g_m = 2mS / \mu m \cdot W_g \quad R_i = 1/g_m$$

$$C_{gd} = 0.0 fF / \mu m \cdot W_g$$

$$C_{gs} = 0.5 fF / \mu m \cdot W_g$$

$$G_{ds} = 0.2mS / \mu m \cdot W_g$$

$$W_g = 20 \mu m$$

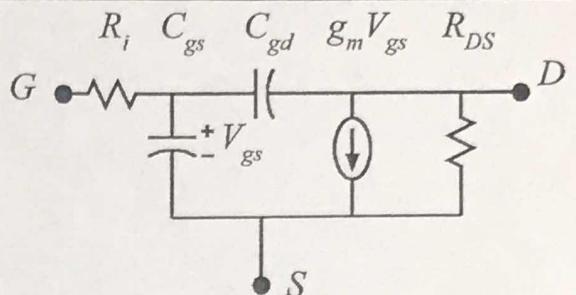

part a, 5 points

What are  $f_\tau$  and  $f_{\max}$  for this transistor?

$$f_\tau = \frac{636}{1010} \text{ GHz}$$

$$f_{\max} = \frac{1010}{1010} \text{ GHz}$$

$$\boxed{g_m = 2mS/\mu m \cdot 20\mu m = 40mS = 1/25\Omega}$$

$$R_i = 1/g_m = 25\Omega$$

$$C_{gs} = 0.5 fF/\mu m \cdot 20\mu m = 10 fF$$

$$C_{gd} = 0.0 fF$$

$$G_{ds} = 0.2 mS/\mu m \cdot 20\mu m = 4 mS = 1/250\Omega$$

2.5

$$\boxed{f_\tau = \frac{g_m}{2\pi(G_{gs} + g_d)} = 0.1164 \cdot \frac{40mS}{10 fF} = 636 \text{ GHz}}$$

2.5

$$\boxed{f_{\max} = \frac{f_\tau}{2\sqrt{R_i G_{ds}}} = \frac{636}{0.632} = 1.017 \text{ GHz}}$$

For this device model only.

part b, 5 points

You are going to use the transistors at 60 GHz signal frequency.

What power gain would you expect to get after impedance matching?

What would be the correct generator impedance and load impedance to obtain this power gain?


$$\text{Gain} = \frac{24.5}{\text{dB}}$$

$$\text{Source impedance} = \frac{25 + j265}{\text{Ohms}}$$

$$\text{Load impedance} = \frac{250}{\text{Ohms}}$$

we can use  $\text{mocf} = (\text{fmax}) = \frac{1.01 \text{ THz}}{60 \text{ GHz}} = 283$ .

or from first principles:

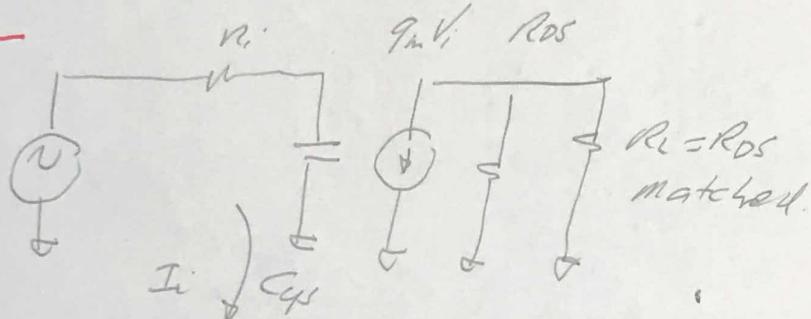

$$R_L = R_{DS}$$

matched

$$P_{in} = I_{in}^2 R_i; \quad g_m V_i = \frac{g_m}{\omega C_{GS}} \cdot I_{in}$$

$$P_{out} = 1/4 (g_m V_i)^2 R_{DS} = I_{in}^2 \left( \frac{g_m}{\omega C_{GS}} \right)^2 \frac{R_{DS}}{4}$$

$$\frac{P_o}{P_i} = \frac{R_{DS}}{4R_i} \left( \frac{g_m}{\omega C_{GS}} \right)^2 = \left( \frac{f_{max}}{f} \right)^2 = \left( \frac{1.01 \text{ THz}}{60 \text{ GHz}} \right)^2$$

$$= 283.1 \quad \text{or} \quad 10 \log_{10}(283) = 24.5 \text{ dB}$$

optimum load impedance is  $R_L = R_{DS} = 250\Omega$ .



2. 
$$\begin{aligned} Z_i &= R_i + \frac{1}{j\omega C_{DS}} = 25\Omega + \frac{0.159}{j60G\text{Hz} \cdot 10^6} \\ &= 25\Omega - j265\Omega. \end{aligned}$$

$$Z_{out,opt} = Z_i^* = 25\Omega + j265\Omega.$$

1.  $Z_{L,opt} = R_{DS} = 250\Omega.$

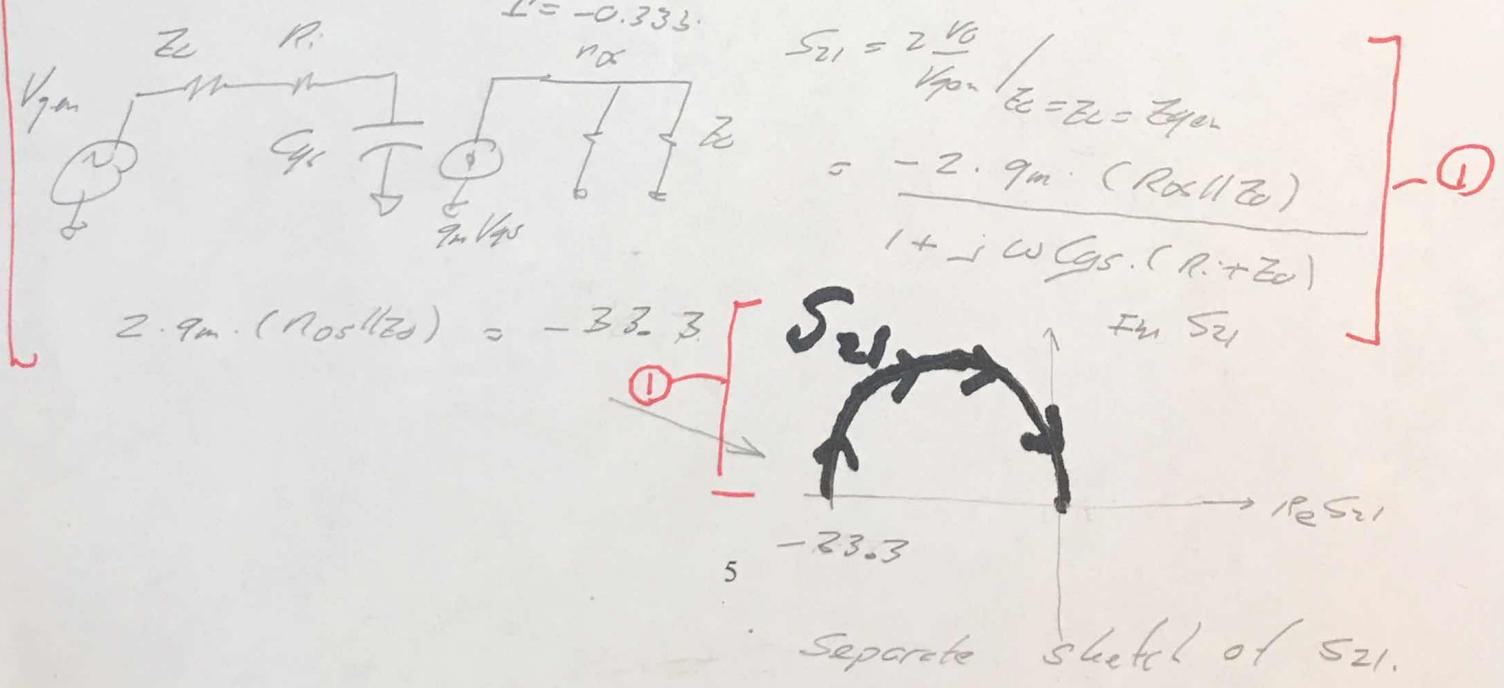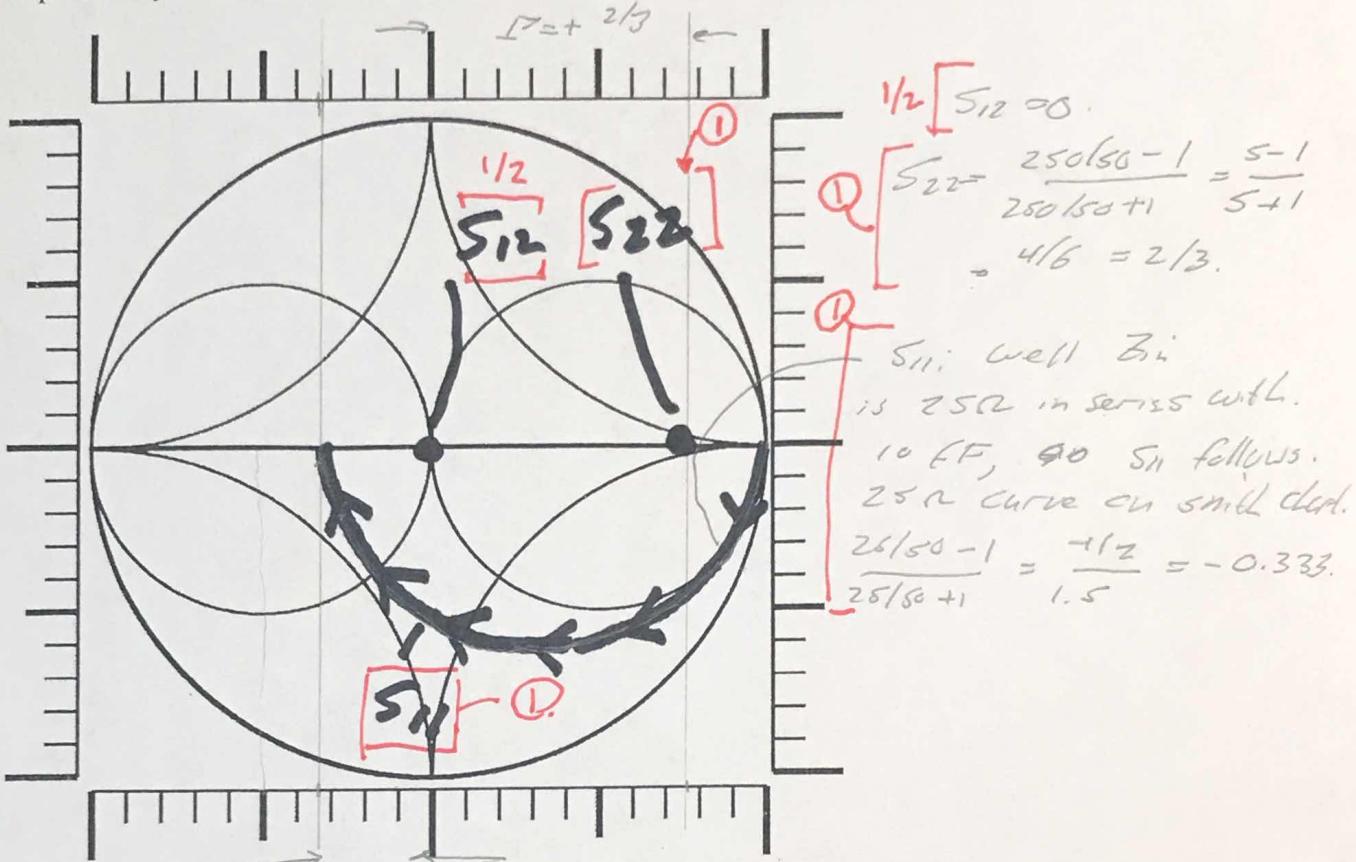part c, 7 points (218A students only)

With the numerical values given in the equivalent circuit, make clear sketches of S11, S22, S12, and S21, from DC to infinite frequency, on the Smith chart below. This may require that you calculate the S parameters first.



**Problem 2, 15 points**

*Two-port properties*


part a, 5 points

*Properties of Y-parameters*

$$C_{gs} = 63.6 \text{ fF}, g_m = 50 \text{ mS.}$$

$$R_{ds} = 100 \text{ Ohms}, R_i = 50 \text{ Ohms,}$$

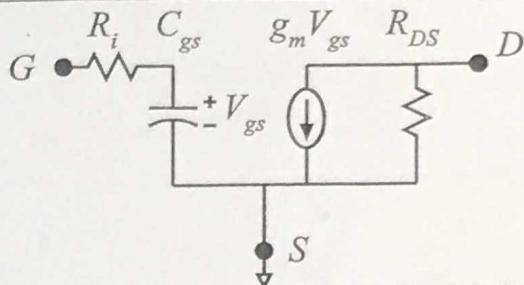Find  $Y_{11}, Y_{12}, Y_{21}, Y_{22}$  at 50 GHz.



$$Y_{11} = \frac{1}{R_i + j\omega C_{gs}} = \frac{1}{50\Omega - j50\Omega}$$

$$Y_{12} = 0 \text{ ms.}$$

$$Y_{21} = \frac{g_m}{1 + j\omega R_i C_{gs}} = \frac{50 \text{ ms}}{1 + j50 \text{ ms}}$$

$$Y_{22} = 10 \text{ ms.}$$

$$\boxed{2.} \quad Y_{11} = \frac{1}{R_i + j\omega C_{gs}} = \frac{1}{50\Omega - j50\Omega}$$

$$= \frac{1}{50\Omega} \cdot \frac{1}{1 - j1} \cdot \frac{1 + j1}{1 + j1} = \frac{1}{50\Omega} \cdot \frac{1 + j1}{2} = 10 \text{ ms} + j10 \text{ ms.}$$

$$\boxed{2} \quad Y_{21} = \frac{g_m}{1 + j\omega R_i C_{gs}} = \frac{50 \text{ ms}}{1 + j50 \text{ ms}} \cdot \frac{1 - j}{1 - j} = \frac{50 \text{ ms}}{2} (1 - j)$$

$$= 25 \text{ ms} - j25 \text{ ms.}$$

$$\boxed{1/2} \quad Y_{12} = 0 \text{ ms}$$

$$\boxed{1/2} \quad Y_{22} = 1/R_{DS} = 1/100\Omega = 10 \text{ ms.}$$

part b, 10 points


*Properties of S-parameters*

The network at the right is for a DC bias feed.

If we want  $|S_{21}| > -3 \text{ dB}$  at 1GHz, what is the minimum value of the inductor?

If we want  $|S_{11}| < -40 \text{ dB}$  at 1GHz, what is the minimum value of the inductor?

Assume a 50 Ohm impedance standard.

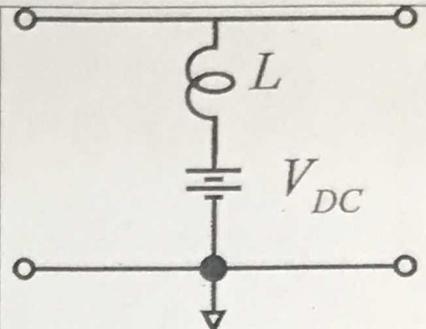

$$\text{Minimum value of } L \text{ to meet } S_{21} \text{ specification} = \frac{4 \text{ nH}}{400 \text{ nA}}$$

$$\text{Minimum value of } L \text{ to meet } S_{11} \text{ specification} = \underline{\quad}$$

$S_{21}$

$$S_{21} = \frac{V_o}{V_{gen}} / \frac{Z_0}{Z_0 + Z_L + \frac{1}{jwL}}$$

Nodal analysis:

$$V_o \left( Y_0 + Y_0 + \frac{1}{jwL} \right) = V_{gen} Y_0$$

$$S_{21} = \frac{Z Y_0}{Z Y_0 + \frac{1}{jwL}} = \frac{jwL \cdot 2Y_0}{1 + j w L \cdot 2Y_0} = \frac{j w L / (Z_0/2)}{1 + j w L / (Z_0/2)}$$

$\rightarrow -3 \text{ dB}$  when  $\omega = \frac{Z_0/2}{L} \rightarrow f = \frac{1}{2\pi} \frac{Z_0/2}{L} \Rightarrow L = \frac{Z_0/2}{2\pi f} = 4 \text{ nH}$

$S_{11}$

$$S_{11} = \frac{Z_0 / (Z_0 - Z_0) - Z_0}{Z_0 / (Z_0 - Z_0) + Z_0} = \frac{Y_0 - Y_{in} / Y_0 = Z_0}{Y_0 + Y_{in} / Y_0 = Z_0}$$

$$S_{11} = \frac{Y_0 - (Y_0 + \frac{1}{jwL})}{Y_0 + (Y_0 + \frac{1}{jwL})} = \frac{1 / j w L}{2 Y_0 + 1 / j w L}$$

$$S_{11} = \frac{1}{1 + j w L \cdot 2 Y_0} = \frac{1}{1 + j w L / (Z_0/2)} = \frac{1}{1 + j w \tau} \text{ where } \tau = \frac{L}{Z_0/2}$$

$$\text{If } S_{11} = -40 \text{ dB} \rightarrow |S_{11}| = \frac{1}{100} \rightarrow w \tau \leq \frac{1}{100}$$


8  $\rightarrow \omega = 100/\tau = 100 \cdot \frac{Z_0/2}{L}$

$$L = \frac{100 \cdot Z_0/2}{2\pi f} = 400 \text{ nH.}$$

**Problem 3, 20 points (145A), 30 points (218A)**  
 2-port parameters and signal flow graphs

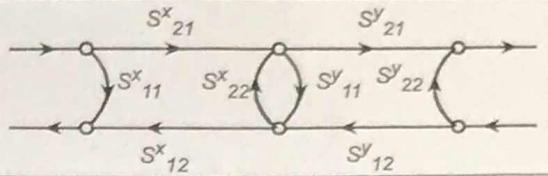**Part a, 5 points**

The signal flow graph to the right represents the cascade of two-ports "x" and "y". If we call the combined network "z", find  $S_{21}^Z$ ,  $S_{12}^Z$ ,  $S_{21}^Z / S_{12}^Z$  and  $S_{11}^Z$



$$S_{21}^Z = \frac{S_{21}^X S_{21}^Y}{1 - S_{22}^X S_{11}^Y}, \quad S_{12}^Z = \underline{\hspace{10em}}$$

$$S_{21}^Z / S_{12}^Z = \underline{\hspace{10em}}, \quad S_{11}^Z = \underline{\hspace{10em}}$$

(1)  $S_{21}^Z$ : there is one path  $S_{21}^X \cdot S_{21}^Y$   
 there is one loop  $S_{22}^X S_{11}^Y$  -- and it touches the path.

$$\hookrightarrow S_{21}^Z = \frac{S_{21}^X S_{21}^Y}{1 - S_{22}^X S_{11}^Y}$$

(1/2)  $S_{12}^Z$ : by symmetry:  $S_{12}^Z = \frac{S_{12}^X S_{12}^Y}{1 - S_{22}^X S_{11}^Y}$

(1/2)  $S_{12}^Z$ :  $\frac{S_{21}^Z}{S_{12}^Z} = \frac{S_{21}^X S_{21}^Y}{S_{12}^X S_{12}^Y}$

(2)  $S_{11}^Z$ : the first path is  $S_{11}^X$ .  
 this does not touch the loop  $S_{22}^X S_{11}^Y$ .


the second path is  $S_{21}^X S_{11}^Y S_{12}^X$   
 this does touch the only loop.

$$S_{11}^Z = \frac{S_{11}^X (1 - S_{22}^X S_{11}^Y) + S_{21}^X S_{11}^Y S_{12}^X}{1 - S_{22}^X S_{11}^Y}$$

$$= S_{11}^X + \frac{S_{21}^X S_{11}^Y S_{12}^X}{1 - S_{22}^X S_{11}^Y}$$

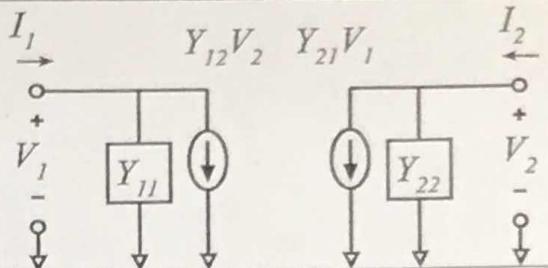part b, 10 points (218A only)

We can represent a 2-port network having Y-parameters  $Y_y$  by the circuit to the right




Given that

$$S_{21} = 2(V_o / V_{gen}) \Big|_{Z_L = Z_{gen} = Z_0}$$

, we have

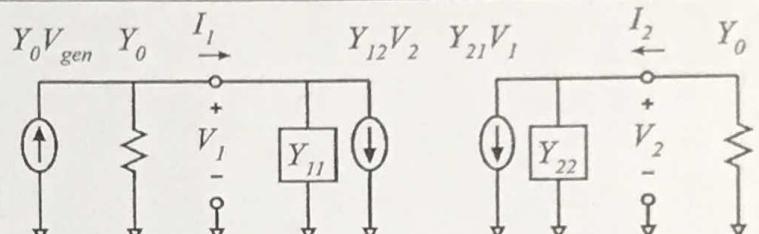$S_{21} = 2V_{out} / V_{gen}$  in the circuit to the right, where  $Y_0 = 1/Z_0$



Prove that  $S_{21} / S_{12} = Y_{21} / Y_{12}$ . This involves nodal analysis of the above circuit.

$$\sum I = 0 \text{ at } V_1 \quad V_1(Y_{11} + Y_0) + V_2(Y_{12}) = Y_0 V_{gen} \quad (3)$$

$$\sum I = 0 \text{ at } V_2 \quad V_1(Y_{21}) + V_2(Y_{22} + Y_0) = 0 \quad (4)$$

In matrix form:

$$\begin{bmatrix} Y_{11} + Y_0 & Y_{12} \\ Y_{21} & Y_{22} + Y_0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Y_0 \\ 0 \end{bmatrix} V_{gen} \quad (2)$$

$$\text{so } S_{21} = \frac{V_0}{V_{gen}} = \frac{2 \cdot N_{21}}{D} \text{ where } N_{21} = \begin{vmatrix} Y_{11} + Y_0 & Y_0 \\ Y_{21} & 0 \end{vmatrix} = -Y_0 Y_{21} \quad (2)$$

$$D = \begin{vmatrix} Y_{11} + Y_0 & Y_{12} \\ Y_{21} & Y_{22} + Y_0 \end{vmatrix}$$


by symmetry,

$$S_{12} = \frac{2 \cdot N_{12}}{D} \text{ where } N_{12} = -Y_0 Y_{12} \quad (2)$$

(1)  $\frac{S_{21}}{S_{12}} = \frac{N_{21}}{N_{12}} = \frac{Y_{21}}{Y_{12}}$

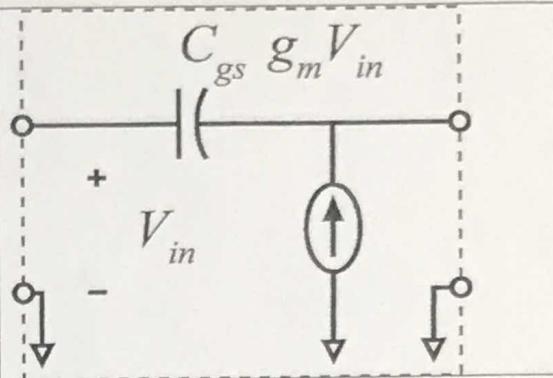part c, 5 points (BOTH 218A and 145A)

Given that  $S_{21}/S_{12} = Y_{21}/Y_{12}$ , for the circuit to the right, find  $Y_{21}/Y_{12}$ . After finding an exact answer, assume that  $g_m \gg \omega C_{gs}$  to find a simpler answer applicable at lower frequencies.



$$Y_{21}/Y_{12} = \underline{\hspace{2cm}}$$

$$Y_{21}/Y_{12} \approx \underline{\hspace{2cm}}$$

by inspection:



$$\begin{aligned} Y_{21} &= -g_m - j\omega C_{gs} \\ Y_{12} &= -j\omega C_{gs} \end{aligned} \quad \left. \begin{array}{l} \text{1.5} \\ \text{1.5} \end{array} \right]$$

$$Y_{21}/Y_{12} = \frac{g_m + j\omega C_{gs}}{j\omega C_{gs}} = \frac{g_m}{j\omega C_{gs}} + 1 \quad \textcircled{1}$$

at low frequencies, this is approximately:

$$Y_{21}/Y_{12} \approx \frac{g_m}{j\omega C_{gs}} \quad \textcircled{1}$$

part d, 10 points

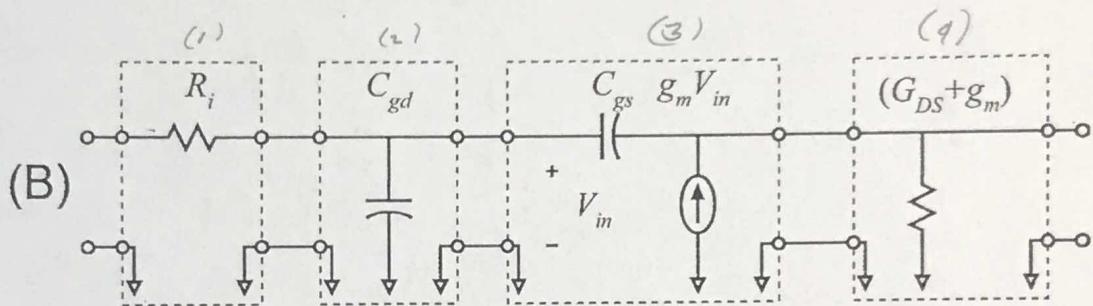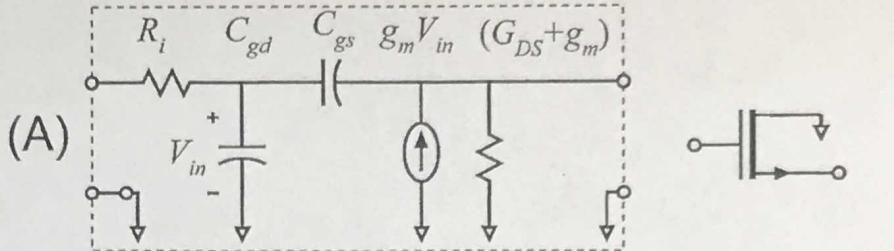

The network (A), which represents the hybrid-pi FET model in source-follower operation, can be represented as the cascaded network (B) below.

If we assume that the network is potentially unstable (it will be at lower frequencies), find an expression for the maximum stable gain. This derivation shows why source followers have difficulties with stability.

$$MSG = \frac{g_m}{\omega C_{gs}} \text{ or } \sqrt{1 + \left(\frac{g_m}{\omega C_{gs}}\right)^2}$$

③ [ "networks (1), (2), (4) are symmetric and have  $Y_{11} = Y_{12}$   
(we can also invoke reciprocity for these) ]

so, from part a of the problem set:

$$\boxed{\textcircled{3}} \quad \left[ \frac{Y_{21}}{Y_{12}} \text{ overall} = \frac{Y_{21}}{Y_{12}} \text{ / part 3.} \right] = 1 + \frac{g_m}{j\omega C_{gs}} \approx \frac{g_m}{\omega C_{gs}}$$

$$\boxed{\textcircled{2}} \quad \left[ \text{but } MSG = \frac{|S_{21}|}{|S_{12}|} = \left| \frac{Y_{21}}{Y_{12}} \right| \text{ if } \omega \ll 1 \right]$$

$$= \begin{cases} \frac{g_m}{\omega C_{gs}} & \text{approximate} \\ \sqrt{1 + \left(\frac{g_m}{\omega C_{gs}}\right)^2} & \text{exact} \end{cases} \quad \boxed{\textcircled{1}}$$

## Comment

Here we encounter a common silly error.


$h_{21}$  is current gain, so

$$dB(h_{21}) = 20 \cdot \log_{10} \left( \frac{g_m}{\omega C_{GS}} \right)$$

$MSC$  is power gain, so

$$dB(MSC) = 10 \cdot \log_{10} \left( \frac{g_m}{\omega C_{GS}} \right)$$

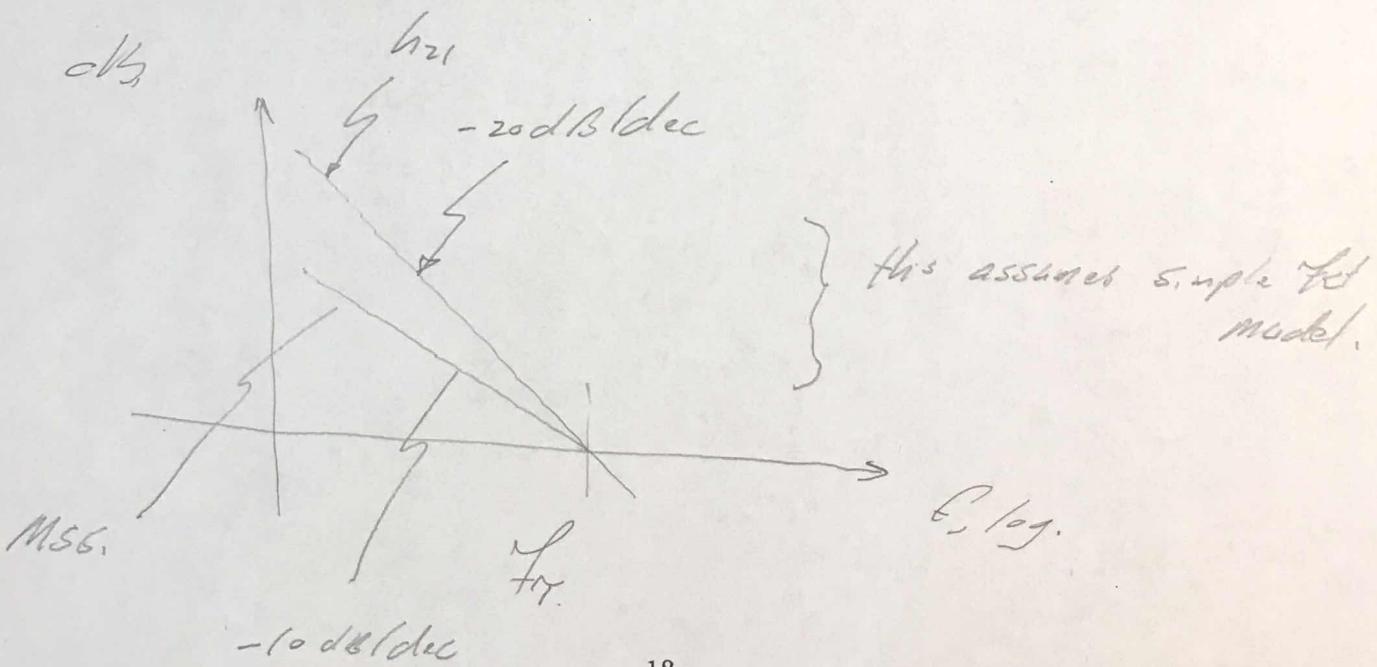
If  $h_{21}$  is 20 dB, then  $MSC$  is only 10 dB!!



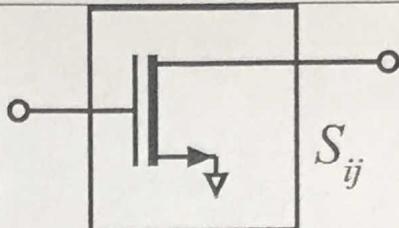**Problem 4, 25 points**

*gain definitions*

At a signal frequency of 10 GHz, a two-port has  $S_{11} = 0.7071$ ,  $S_{12} = 0$ ,  $S_{21} = 5$  and  $S_{22} = 0.5$ , as defined with a 50 Ohm impedance reference.



part a, 5 points

The device is connected to a 50 Ohm generator with 1 microwatt available power, and is connected via a conjugate impedance-matching network to a 50 Ohm load. Find the power in the load.

$$P_{\text{Load}} = \underline{33 \mu\text{W}}$$

2 [The output is matched  
The input is not  
This is the AVAILABLE GAIN.]

2  $G_a = \frac{1 - |S_{21}|^2}{|1 - S_{21}S_{11}|^2} \cdot \frac{|S_{21}|^2}{1 - |1 - P_{\text{av}}|H|^2}$  where  $P_{\text{av}} = S_{22} + \frac{S_{12}S_{21}H^2}{1 - S_{11}H^2}$   
but  $Z_{\text{gen}} = 50\Omega = Z_0$  so  $H = 0$

$G_a = |S_{21}|^2 \cdot \frac{1}{1 - |1 - P_{\text{av}}|H|^2}$  where  $P_{\text{av}} = S_{22} +$

1/2  $= \frac{|S_{21}|^2}{1 - |1 - S_{22}|H|^2} - \frac{|S_{21}|^2}{1 - |1 - 0.5|H|^2} = \frac{\frac{25}{14}}{1 - \frac{25}{14}} = \frac{25}{314} = 25 \cdot \frac{4}{3}$   
 $\frac{1}{3} = \frac{100}{3} = \underline{33.333}$

1/2  $P_{\text{load}} = 33.3 \cdot 1 \mu\text{W}$   
 $= 33 \mu\text{W}$

part b, 5 points

The device is directly connected to a 50 Ohm generator with 1 microwatt available power, and is directly connected to a 50 Ohm load. Find the RF power in the load.

$$P_{Load} = \underline{25 \mu W.}$$

4

$R_s$  &  $\pi_L$  are both zero.

$$\text{Power gain} = |S_{21}|^2$$

$$\begin{aligned} P_{Load} &= 1 \mu W \cdot |S_{21}|^2 = 1 \mu W \cdot 25 \\ &= 25 \mu W \end{aligned}$$

part c, 5 points

The device is connected via a conjugate impedance-matching network to a 50 Ohm generator with 1 microwatt available power, and is connected via a conjugate impedance-matching network to a 50 Ohm load. Find the power in the load. Find the source and load impedances presented to the transistor.

$$P_{Load} = \frac{66.6 \mu\text{W}}{Z_{source} 291\Omega} \quad Z_{Load} = \frac{150\Omega}{Z_{source}}$$

[This is the M<sub>1G</sub>]

$$\text{Because } S_{11} = 0, \quad M_{1G} = \frac{1}{1 - \|S_11\|^2} \quad \frac{\|S_{21}\|^2}{1 - \|S_{22}\|^2}$$

$$M_{1G} = \frac{1}{1 - \left(\frac{1}{27}\right)^2} \quad \frac{\|S\|^2}{1 - \|S_22\|^2}$$

$$= 2 \cdot 25 : 4/3 = 100 \cdot 2/3 = 66.66$$

$$P_{load} = 1 \mu\text{W} \cdot 66.66 = 66.66 \mu\text{W}$$

$$\text{Because } S_{12}S_{21} = 0, \quad S_{11} = 17, \quad S_{22} = 12$$

$$\text{so } Z_{source} = 50\Omega \cdot \frac{1 + S_{11}}{1 - S_{11}} = 50\Omega \cdot \frac{1 + 1/27}{1 - 1/27}$$

$$= 50\Omega \cdot 5.83 = 291\Omega$$

$$\text{and } Z_{load} = 50\Omega \cdot \frac{1 + S_{22}}{1 - S_{22}} = 50\Omega \cdot \frac{1 + 1/2}{1 - 1/2}$$

$$= 50\Omega \cdot 3 = 150\Omega$$

part d, 10 points

Using the impedance-matching networks of part C (they are NOT CHANGED for part d), the device is now connected to a 100 Ohm generator with 1 microwatt available power, and is directly connected to a 25 Ohm load. Find the RF power in the load.

$$P_{Load} = \underline{\hspace{2cm}}$$

this amplifier matched to 50Ω has, from part c:

1.5

$$|S_{21}| = \sqrt{66.66^2} \quad S_{12} = 0.$$

$$S_{11} = 0, \quad S_{22} = 0.$$

this is a now z-port

we are now calculating the transducer gain of this new z-port with

$$A_s = \frac{100\Omega/50\Omega - 1}{100\Omega/50\Omega + 1} = \frac{2-1}{2+1} = \frac{1}{3}$$

$$\text{and } A_L = \frac{25\Omega/50\Omega - 1}{25\Omega/50\Omega + 1} = \frac{4-1}{4+1} = -\frac{1}{3}.$$

given that  $S_{12} = 0$ :

$$G_T = \frac{1 - \|L_s\|^2}{\|(1 - A_s S_{11})\|^2} \frac{\|S_{21}\|^2}{\|(1 - A_L S_{22})\|^2}$$

$$\text{but } S_{11} = S_{22} = 0$$

$$\begin{aligned} G_T &= [1 - \|L_s\|^2] [\|S_{21}\|^2] [1 - \|L_s\|^2] \\ &= (1 - \frac{1}{9}) \cdot 66.66 \cdot (1 - \frac{1}{9}) \\ &= (\frac{8}{9})^2 \cdot 66.6 = \underline{\underline{52.7}} \end{aligned}$$


1/2  $P_{Load} = 52.7 \cdot 1\mu\text{W} = \underline{\underline{52.7\mu\text{W}}}$

potentially unstable



**Problem 5, 15 points (145A), 25 points (218A)**  
**Potentially unstable amplifier design**

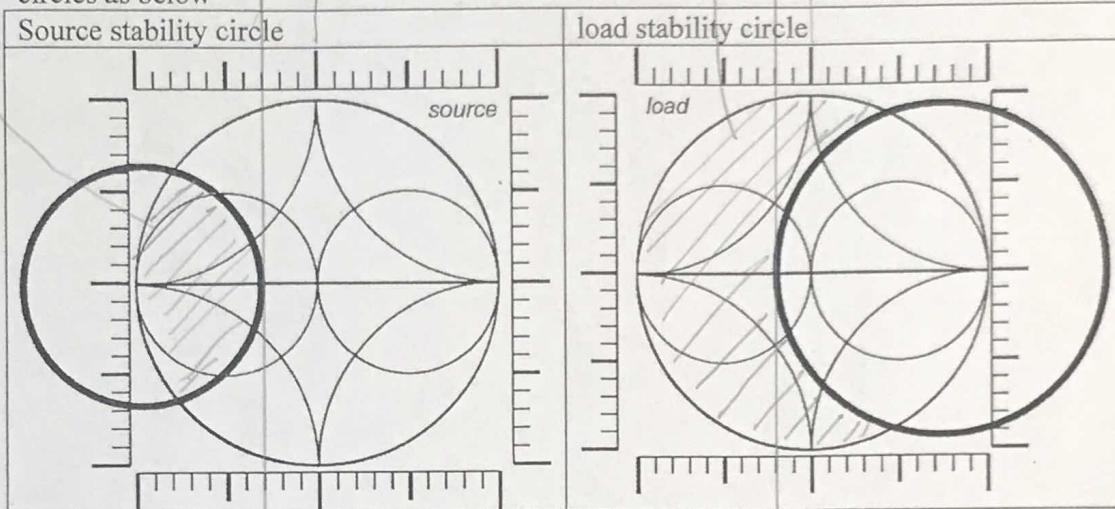part a, 7 points

At a design frequency of 10 GHz, a common-source FET has source and load stability circles as below




Given that  $S_{11}=0.5$  and  $S_{22}=0.9$  at 10 GHz, draw two stabilization circuits in the boxes below, giving element values

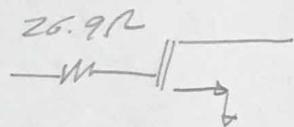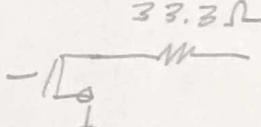Solution 1	Solution 2
 $26.9 \Omega$	 $33.3 \Omega$

- 1 [ Because  $|Hs_1|, |Hs_2| < 1$  the centers of the Smith charts are stable.
- 2 [ Unstable regions are shaded on diagrams.
- 2 [ On the input, we can force  $L_s$  to be more positive than -0.3.  
 → Series resistor of  $R = Z_0 \frac{1+L}{1-L} = 50\Omega \frac{1-0.3}{1+0.3} = 50\Omega \frac{0.7}{1.3} = 26.9\Omega$ .
- 2 [ On the output, we can force  $L_o$  to be more positive than -0.2  
 → Series resistor of  $R = Z_0 \frac{1+L}{1-L} = 50\Omega \frac{1-0.2}{1+0.2} = 50\Omega \frac{0.8}{1.2} = 50\Omega \frac{8}{12} = 50\Omega \cdot \frac{2}{3} = 33.33\Omega$

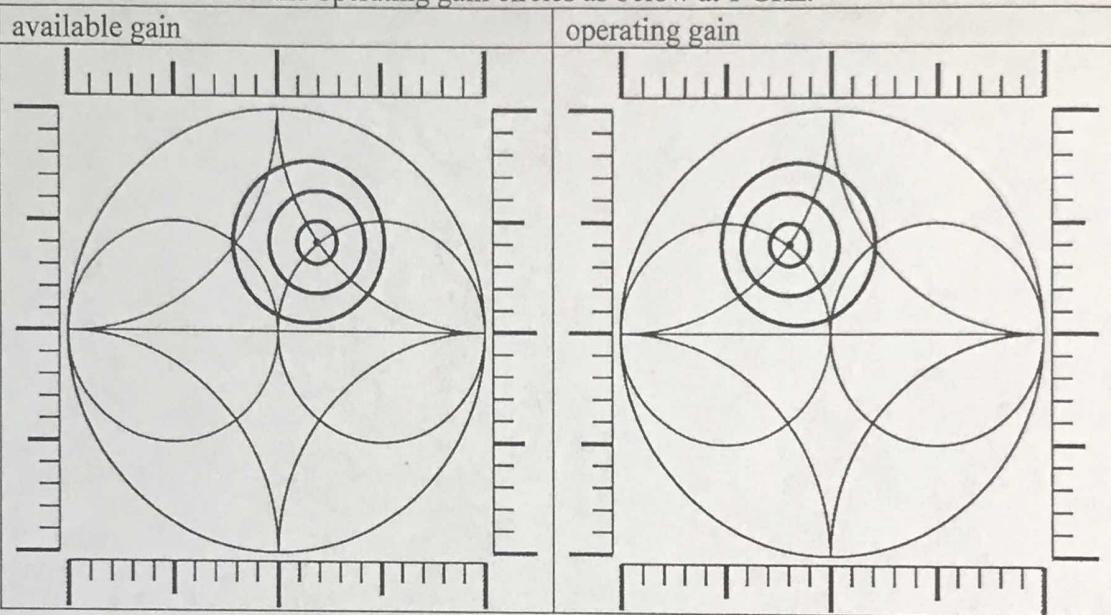part b, 5 points

A FET has available and operating gain circles as below at 1 GHz.



Assuming a 50Ω impedance normalization, what are the optimum generator and load impedances?

$$Z_{gen,opt} = \underline{\hspace{2cm}} \quad Z_{l,opt} = \underline{\hspace{2cm}}$$

1 [  $G_a$  is a function of  $Z_s \rightarrow$  optimum source impedance

From  $G_a$  circles above,  $\gamma_{s,opt} = 1 + j1$

$$\frac{1}{2} [ Z_{gen,opt} = 50\Omega + j50\Omega ]$$

1 [  $G_p$  is a function of  $Z_L \rightarrow$  optimum load impedance.

From  $G_p$  circles above:

$$G_p,opt = 1 - j1$$


$$\gamma_{L,opt} = \frac{1}{1-j1} \cdot \frac{1+j1}{1+j1} = \frac{1+j1}{2} = \frac{1}{2} + j\frac{1}{2}$$

$$\frac{1}{2} [ Z_{L,opt} = 25\Omega + j25\Omega ]$$

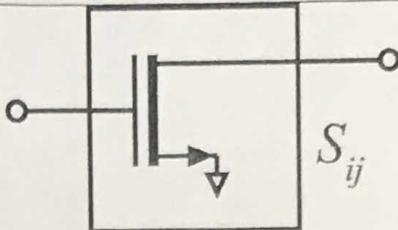part c, 10 points (218A only)


At 10GHz, a transistor has  
 $S_{11}=0$ ,  $S_{12}=0.1$ ,  
 $S_{21}=20$ ,  $S_{22}=-0.5$ .

These S-parameters are normalized to a 50 Ohm reference impedance



Draw the \*source\* stability circle on the graph below:

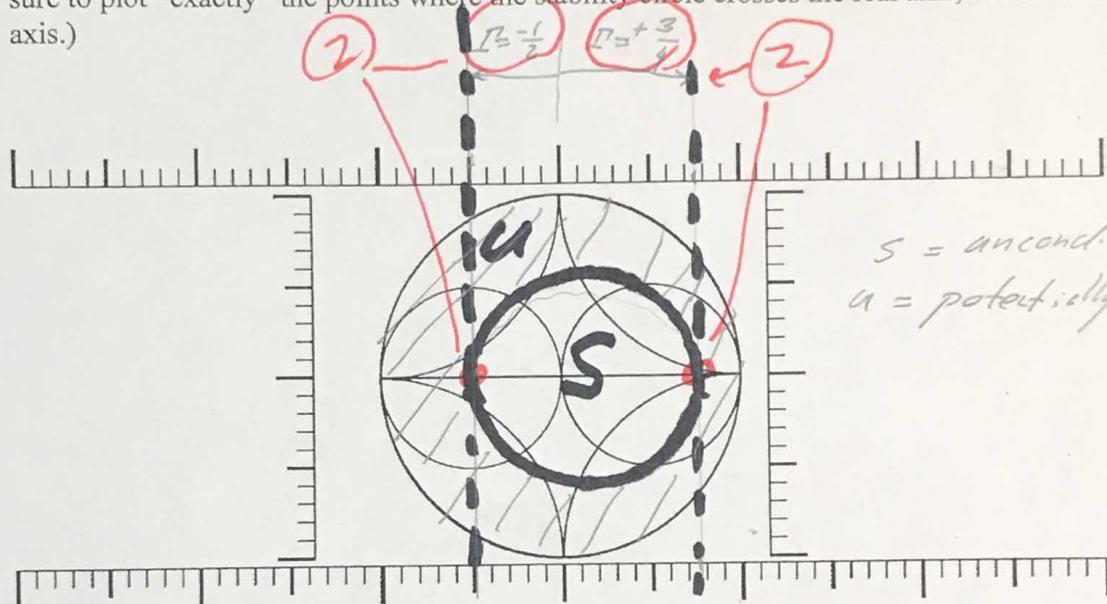(to do this perfectly, you would need a compass: you can sketch most of the curve, but be sure to plot \*exactly\* the points where the stability circle crosses the real axis, i.e. the x-axis.)



$$2 \left[ \text{The real axis intercepts are when } e^{j\theta} = \pm 1, \text{ so } L_s = \begin{cases} 0.25 + 0.5 = 0.75 \\ 0.25 - 0.5 = -0.25 \end{cases} \right]$$