

ECE ECE145A (undergrad) and ECE218A (graduate)

Mid-Term Exam. November 8, 2022

Do not open exam until instructed to.

Open notes, open books, etc.

You have 1 hour and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.), ***AFTER STATING THEM.***


Problem	Points Received	Points Possible
1		15
2a		10
2b		7
2c		8
2d (218 only)		10 (218A only)
3a		5
3b		5
3c		7.5
3d		7.5
4		15
5a		10
5b (218 only)		15 (218A only)
6		10
total		100 (145), 125 (218A)


Name: _____

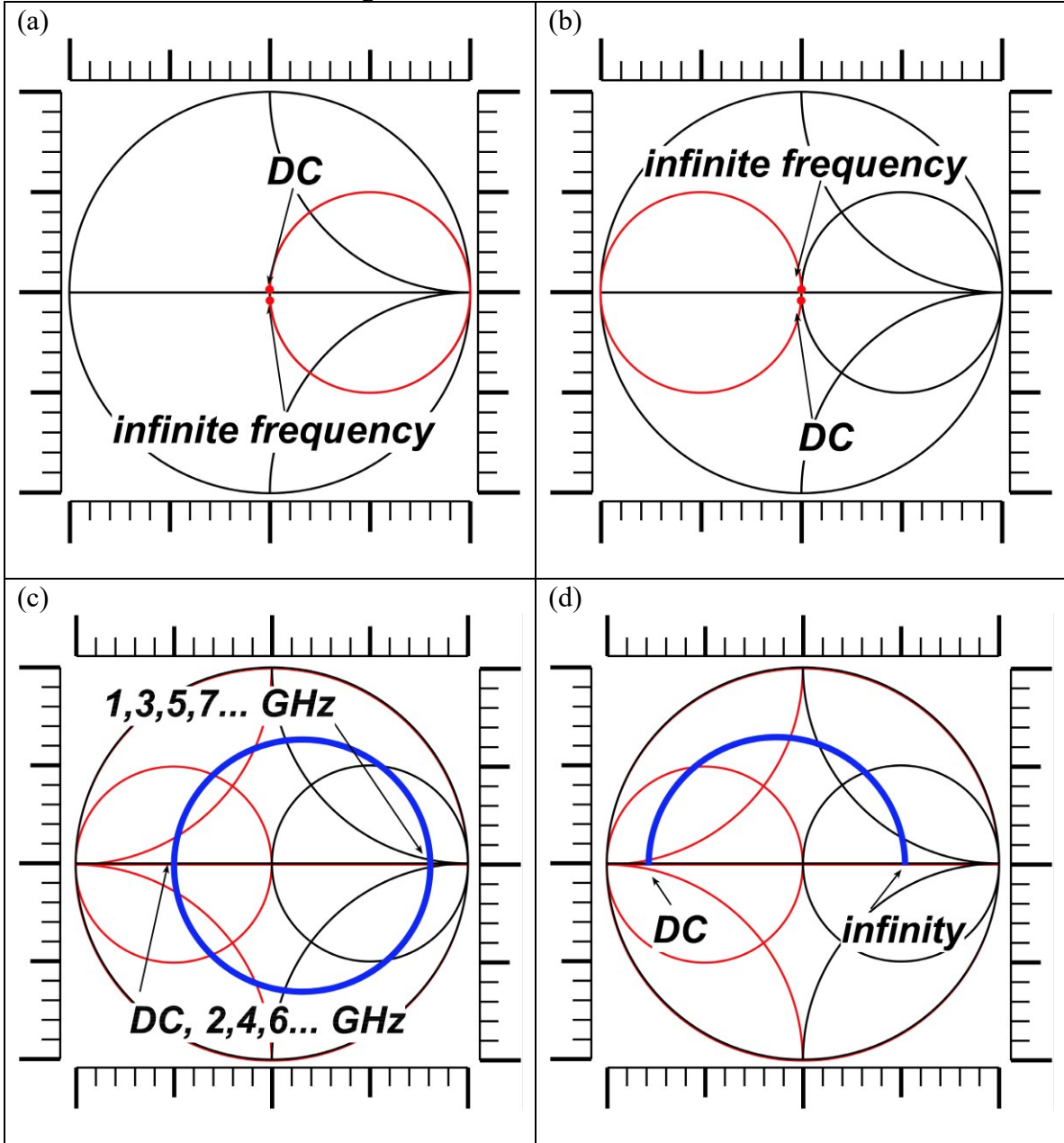Problem 1, 15 points

The Smith Chart and Frequency-Dependent Impedances.

HINT: use the scales on the figures to measure distances as needed.



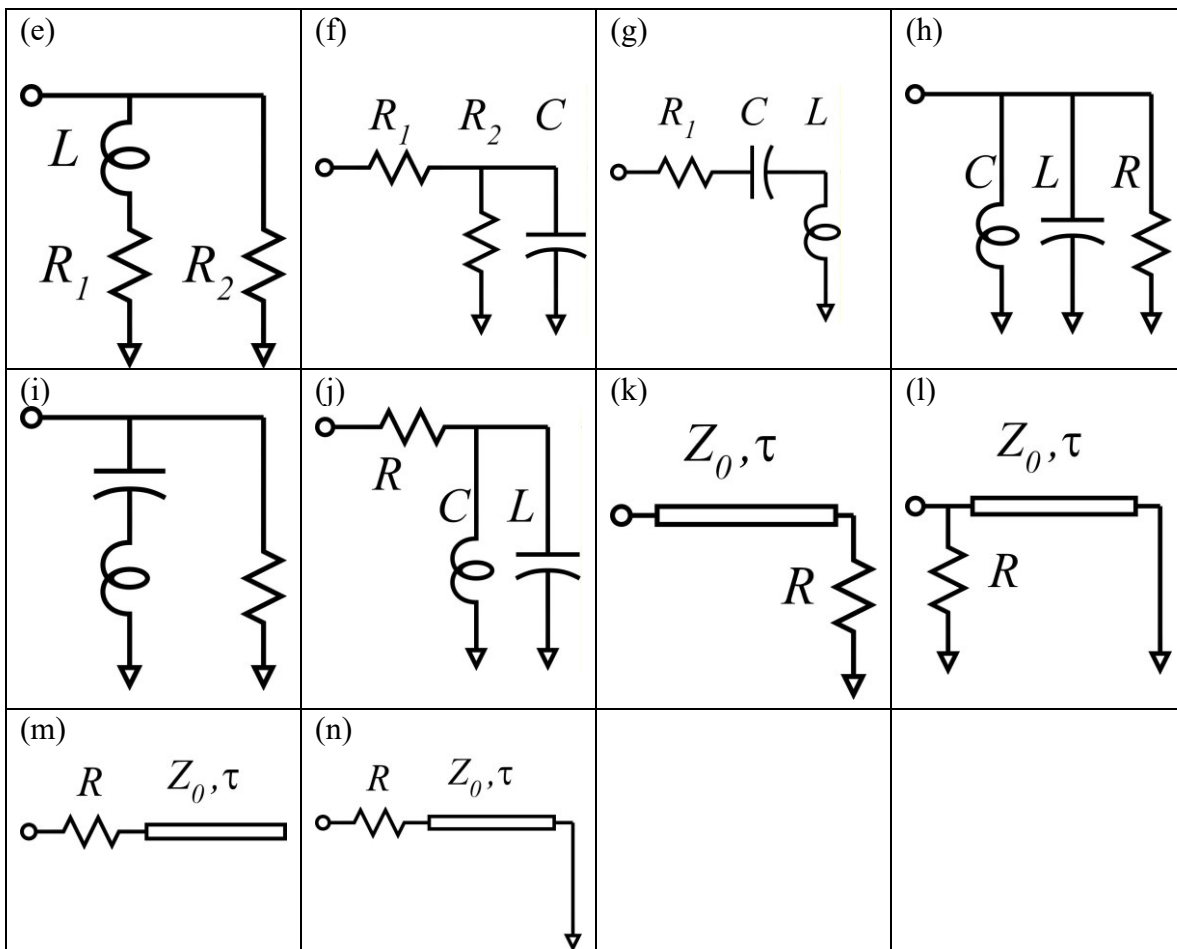

First match each Smith Chart with each circuit. ***Then determine as many component values as is possible*** (RLC values, transmission line delays and characteristic impedances)...note that some values cannot be determined with the information given. The charts all use 50 Ohm normalization:

Smith chart (a). Circuit=_____.
Component values: _____, _____, _____,

Smith chart (b). Circuit=_____.
Component values: _____, _____, _____,


Smith chart (c). Circuit=_____.
Component values: _____, _____, _____,

Smith chart (d). Circuit=_____.
Component values: _____, _____, _____,


Problem 2, 25 points (ece145A), 35 points (ece218A)
2-port parameters and Transistor models

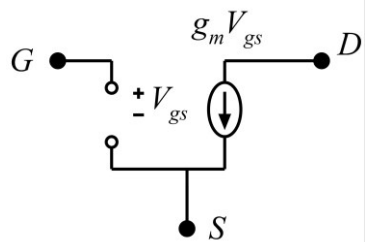Part a, 10 points

At the right is the equivalent circuit for a FET. The transconductance g_m is 1 mS.




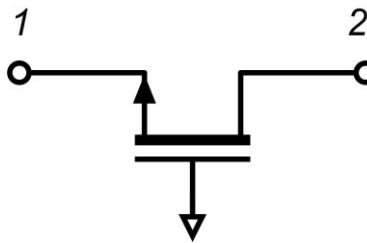Now, given this model, for the network at the right, give the numerical values of S21 and S11. The reference Z_0 is 50 Ohms. .



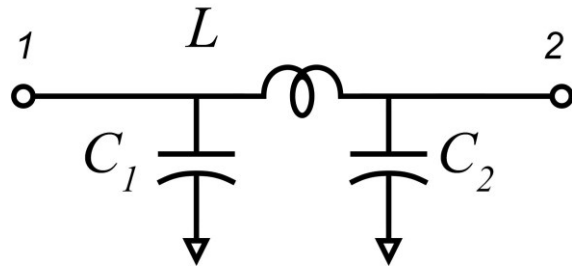
Part b, 7 points

Derive algebraic expressions for the four Y parameters for this network



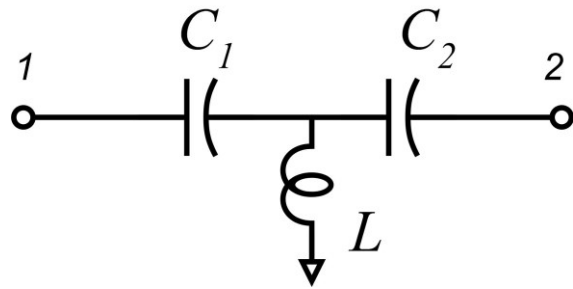Part c, 8 points

Derive algebraic expressions for the four Z parameters for this network




Part d, ***ECE218A students only*** 10 points

Compute the Y parameters for network, to second order in $j\omega C_{gd}R_i$. The Taylor

series expansion

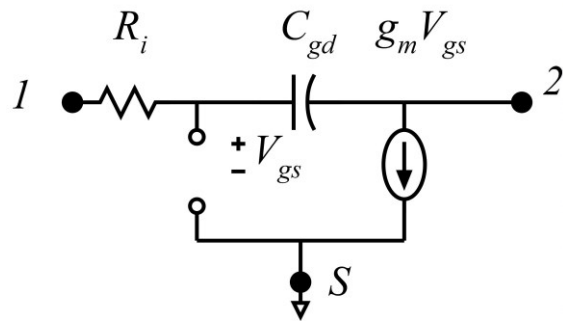$(1 + \varepsilon)^{-1} = 1 - \varepsilon + \varepsilon^2 + O(\varepsilon^3)$ may be useful




Problem 3, 25 points (ECE145A), 25 points (ECE 218A)

Available source power relationships, lumped/distributed relationships.

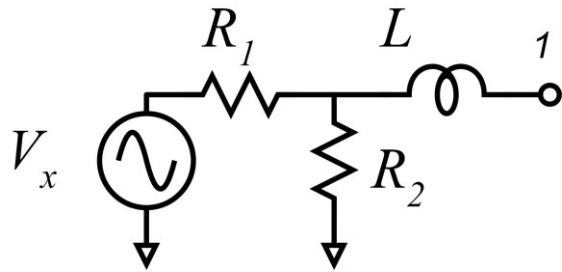Part a, 5 points

V_s is 2V RMS at 10GHz. R_1 and R_2 are both 50 Ohms, L is 0.795 nH.

At 10GHz, what is the available signal power? Draw the circuit diagram of a load network, with element values specified, that would, when connected to the source, absorb this amount of power from the generator.



Part b, 5 points


A coaxial cable has 50 Ohms characteristic impedance, is 10 meters long, and the insulating dielectric has a dielectric constant of 2.0.

- a) What is the total capacitance of the cable ?
- b) What is the total inductance of the cable ?

Part c, 7.5 points

A capacitor has round plates of radius $R=1$ cm, and separation $H = 0.1$ mm. Between the plates is an insulator whose dielectric constant is 100.

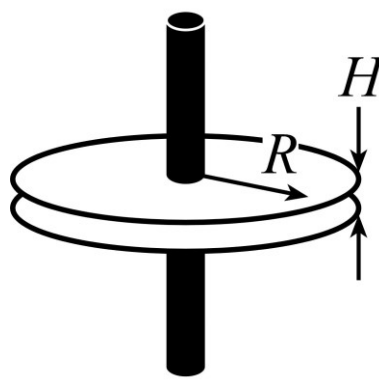- a) What is the capacitor's impedance at 1 kHz ?
- b) At what frequencies is the impedance infinity Ohms ?
- c) At what frequencies is the impedance zero Ohms ?




Part d, 7.5 points

Using the approximate formula for transmission-line characteristic impedance,

$$Z_0 \approx \sqrt{\epsilon_r} \frac{H}{H+W}, \text{ if } H=1 \text{ mm, } W=5$$

mm, and $L=10$ cm, we have two metal plates that are short-circuited at a distance L from the drive point.

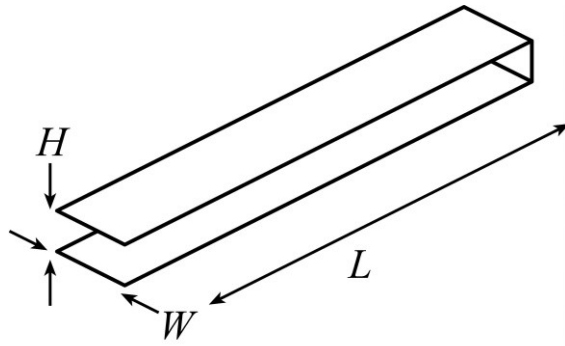- what is the approximate inductance between the two ends of the wire ?
- At what frequencies is the impedance infinity Ohms ?
- At what frequencies is the impedance zero Ohms ?




Problem 4, 15 points

Impedance-matching exercise.

At 10GHz signal frequency, an antenna has an input impedance of $100+j0$ Ohms. Design a matching network, using a series inductor and a shunt capacitor, which matches this impedance to 25 Ohms. Use a Smith chart with 50 Ohms impedance normalization

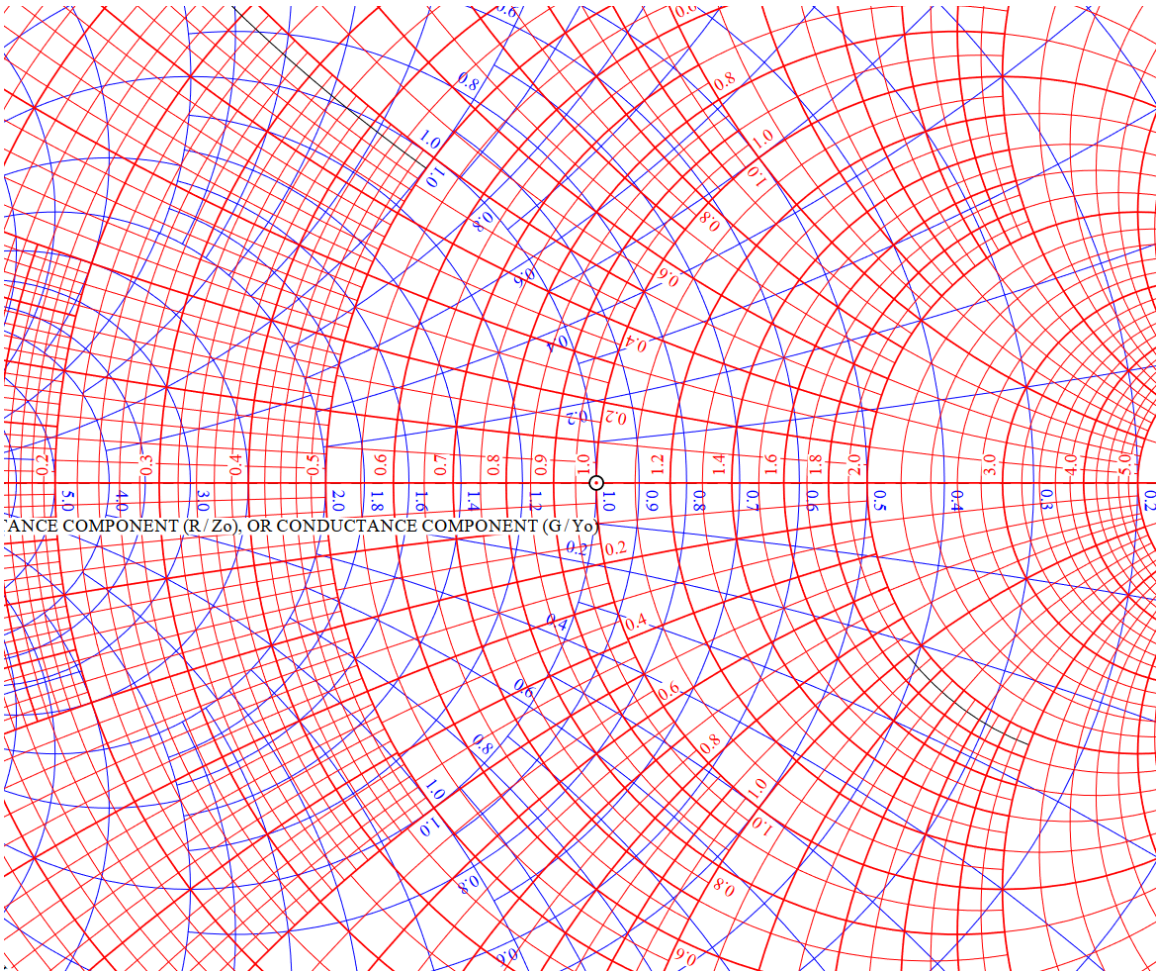
Give all element values. Either use a separate impedance-admittance chart , or use the attached one below..




Problem 5, 10 points (ece145A), 25 points (218A)
Signal flow graphs

Part a, 10 points

Find b_{out}/a_{gen} for this network.

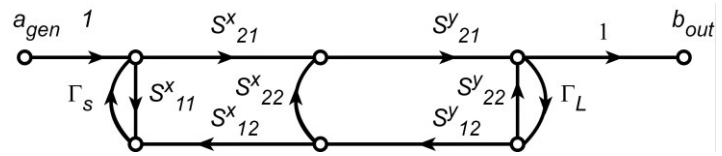

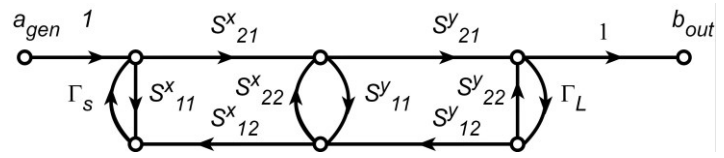Part b, (218A only) 15 points
 Find b_{out}/a_{gen} for this network.




Problem 6, 10 points

Transmission lines in the time domain.

V_{gen} is a 1V step-function occurring at $t=0$ seconds. Zline is 50 Ohms. The line is 2 meters long and has a dielectric constant of 4.0.

R_2 is zero Ohms

R_1 is 50 Ohms.

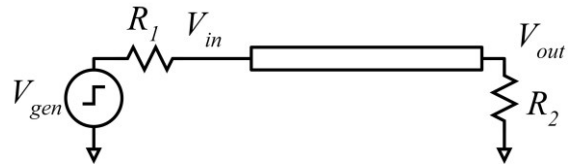

Plot $V_{in}(t)$ on the graph below.

