

**ECE ECE145A (undergrad) and ECE218A (graduate)  
Final Exam. Monday December 5, 2021, noon - 3 p.m.**

Open book. You have 3 hrs.

Use all reasonable approximations (5% accuracy is fine. ),

***AFTER STATING and justifying THEM.***

***Think before doing complex calculations. Sometimes there is an easier way.***

Problem	Points Received	Points Possible
1A		5
1B		5
1C		5
1D		5
1D		5
1F		10
1G		10 (218A only)
2		10
3		10
4A		10
4B		10 (218A only)
5A		5
5B		10 (218A only)
total		70 (145A), 100 (218A)

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)(1 - |\Gamma_L|^2)}{|(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - S_{21} S_{12} \Gamma_s \Gamma_L|^2} \quad G_P = \frac{1}{1 - \|\Gamma_{in}\|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2}$$

$$G_a = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - \|\Gamma_{out}\|^2} \quad G_{max} = \frac{|S_{21}|}{|S_{12}|} \cdot \left[ K - \sqrt{K^2 - 1} \right] \text{ if } K > 1$$

$$G_{MS} = \frac{|S_{21}|}{|S_{12}|} \cdot \text{if } K < 1 \quad K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{21} S_{12}|} \quad \text{where } \Delta = \det[S]$$

Unconditionally stable if : (1)  $K > 1$  and (2)  $\|\det[S]\| < 1$

*Solution.*


**Problem 1, 30 points (145A), 40 points (218A)**

*Power Gain Definitions*

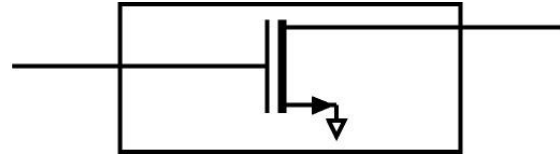part a, 5 points

At 100 GHz, the transistor has  
 $S_{11} = -1/2$ ,  $S_{21} = -4$ ,  $S_{12} = 0$ ,  $S_{22} = +1/3$ ,  
 (S-parameters using  $50\Omega$  normalization)

The generator has  $(250/3)$  Ohms source impedance and 1 mW available power. The load is  $(50/3)$  Ohms.



If we directly connect the generator to the transistor input, but impedance-match the load to the transistor output, what RF power will be delivered to the load ?

RF power delivered to the load = 11.25 mW

Load is matched, source is not → GA ]'

$$\Gamma_s = \frac{Z_L / Z_0 - 1}{Z_L / Z_0 + 1} = \frac{5/3 - 1}{5/3 + 1} = \frac{5 - 3}{5 + 3} = \frac{2}{8} = 1/4. ]'$$

$$\Gamma_{out} = S_{22} + \frac{S_{21} S_{12} \Gamma_s}{1 - S_{11} \Gamma_s} = \frac{1}{3} + 0 = \frac{1}{3} ]'$$

$$G_a = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |\Gamma_{out}|^2} = \frac{1 - \|1/4\|^2}{|1 - \frac{1}{4}(-\frac{1}{2})|^2} \cdot \|4\|^2 \cdot \frac{1}{1 - \|1/3\|^2}$$

$$= \frac{15/16}{1 + 1/8} \cdot 16 \cdot \frac{1}{1 - 1/9}$$


$$= \frac{15}{16 + 2} \cdot 16 \cdot \frac{9}{8} = \frac{15}{18} \cdot 16 \cdot \frac{9}{8}$$

$$P_L = 1 \text{ mW} \cdot \frac{5}{8} \cdot 2 \cdot \frac{9}{8} = 1 \text{ mW} \cdot \frac{45}{4} = 11.25 \text{ mW} ]'$$

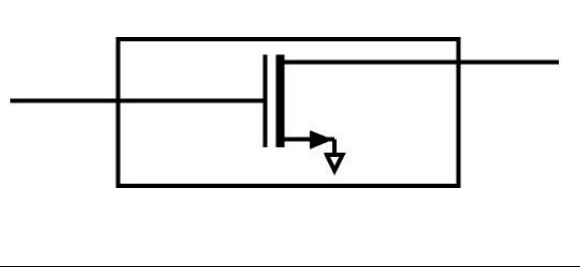part b, 5 points

At 100 GHz, the transistor has  
 $S_{11} = -1/2$ ,  $S_{21} = -4$ ,  $S_{12} = 0$ ,  $S_{22} = +1/3$ ,  
 (S-parameters using  $50\Omega$  normalization)

The generator has 50 Ohms source impedance and 1 mW available power. The load is 50 Ohms.



If we directly connect the generator and load to the transistor, what RF power will be delivered to the load?

← This is  $\|S_{21}\|^2$  the insertion gain. ]<sup>2</sup>

RF power delivered to the load = 16 mW

$$P_L = \|S_{21}\|^2 \cdot P_{AVG}$$


$$= 16 \cdot 1 \text{ mW}$$

$$= 16 \text{ mW. ]}$$

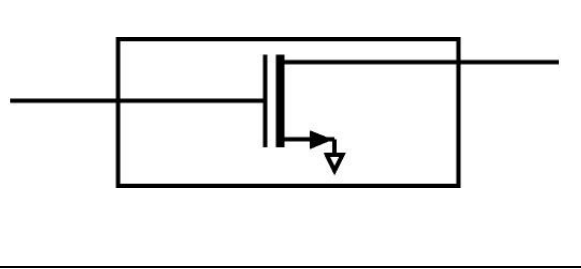part c, 5 points

At 100 GHz, the transistor has  
 $S_{11} = -1/2$ ,  $S_{21} = -4$ ,  $S_{12} = 0$ ,  $S_{22} = +1/3$ ,  
 (S-parameters using  $50\Omega$  normalization)

The generator has  $(250/3)$  Ohms source impedance and 1 mW available power. The load is  $(50/3)$  Ohms.



If we impedance-match the generator to the transistor input, but directly connect the load to the transistor output, what RF power will be delivered to the load?

input matched  $\rightarrow G_p$

RF power delivered to the load =  $11.75 \text{ mW}$

$$1 \left[ \Gamma_L = \frac{Z_L / Z_0 - 1}{Z_L / Z_0 + 1} = \frac{1/3 - 1}{1/3 + 1} = \frac{1 - 3}{1 + 3} = \frac{-2}{4} = -1/2 \right]$$

$$2 \left[ \Gamma_{in} = S_{11} \text{ because } S_{12} S_{21} = 0. \right]$$

$$G_p = \frac{1}{1 - \|\Gamma_{in}\|^2} \cdot |S_{21}|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{|1 - \Gamma_L S_{22}|^2} = \frac{1}{1 - \|\Gamma_L\|^2} \cdot \|4\|^2 \cdot \frac{1 - (-1/2)^2}{|1 - (-1/2)(1/3)|^2}$$


$$= \frac{1}{1 - 1/4} \cdot 16 \cdot \frac{1 - 1/4}{\|1 + 1/6\|^2} = \frac{16}{(7/6)^2} = \frac{36}{49} \cdot 16$$

$$1 \left[ P_L = 1 \text{ mW} \cdot \frac{36}{49} \cdot 16 = 11.7551 \text{ mW} \right]$$

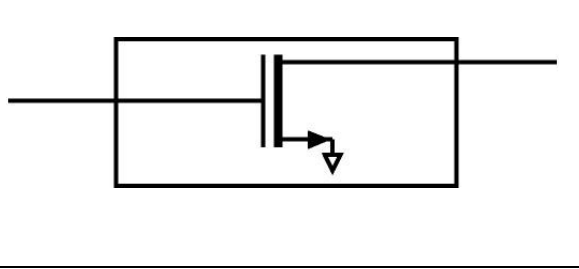part d, 5 points

At 100 GHz, the transistor has  
 $S_{11} = -1/2$ ,  $S_{21} = -4$ ,  $S_{12} = 0$ ,  $S_{22} = +1/3$ ,  
 (S-parameters using  $50\Omega$  normalization)

The generator has  $(250/3)$  Ohms source impedance and 1 mW available power. The load is  $(50/3)$  Ohms.



If we place impedance-matching networks between the generator and the transistor, and between the transistor and the load, what RF power will be delivered to the load?  $\rightarrow$  24 mW

1) [1] because  $S_{12} = S_{21} = 0$ ;  $\Gamma_{in} = S_{11}$  &  $\Gamma_{out} = S_{22}$

1) [2] because  $S_{21} = S_{12} = 0$

$$1) [G_{max} = \frac{1}{1 - \|S_{11}\|^2} \|S_{21}\|^2 \frac{1}{1 - \|S_{22}\|^2}$$

$$= \frac{1}{1 - \|1/2\|^2} \cdot 16 \cdot \frac{1}{1 - \|1/3\|^2}$$

$$= \frac{1}{1 - 1/4} \cdot 16 \cdot \frac{1}{1 - 1/9}$$


$$= \frac{4}{3} \cdot 16 \cdot \frac{9}{8} = 4 \cdot 2 \cdot 3 = 24$$

$$1) [P_{load} = 24 \text{ mW}]$$

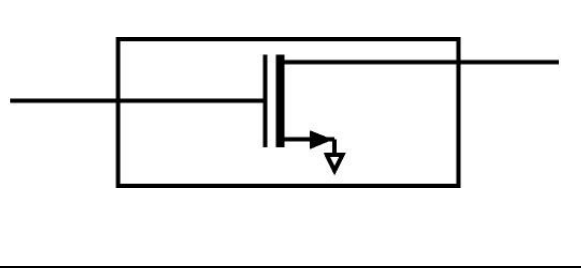part e, 5 points

At 100 GHz, the transistor has  
 $S_{11} = -1/2$ ,  $S_{21} = -4$ ,  $S_{12} = 0$ ,  $S_{22} = +1/3$ ,  
 (S-parameters using  $50\Omega$  normalization)

The generator has  $(250/3)$  Ohms source impedance and 1 mW available power. The load is  $(50/3)$  Ohms.



If we directly connect the generator and load to the transistor, what RF power will be delivered to the load?

*This is  $G_T$*

RF power delivered to the load = 6.53 mW

$$\Gamma_{in} = S_{11}, \quad \Gamma_{out} = S_{22} \quad \text{because } S_{12}S_{21} = 0.$$

$$= -1/2 \qquad = 1/3$$

$$\Gamma_s = \frac{Z_0/Z_G - 1}{Z_0/Z_G + 1} = \frac{5/3 - 1}{5/3 + 1} = \frac{5-3}{5+3} = \frac{2}{8} = 1/4.$$

$$\Gamma_L = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} = \frac{1/3 - 1}{1/3 + 1} = \frac{1-3}{1+3} = \frac{-2}{4} = -1/2$$

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)(1 - |\Gamma_L|^2)}{|(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - S_{21} S_{12} \Gamma_s \Gamma_L|^2}$$

$$= \frac{16 \cdot (1 - \frac{1}{16}) (1 - \frac{1}{4})}{\left[ \left(1 + \frac{1}{4} \cdot \frac{1}{2}\right) \left(1 + \frac{1}{2} \cdot \frac{1}{3}\right) \right]^2}$$

$$= \frac{16 \cdot \left(\frac{15}{16}\right) \left(\frac{3}{4}\right)}{\left(1 + \frac{1}{8}\right)^2 \left(1 + \frac{1}{6}\right)^2} = \frac{15 \cdot \frac{3}{4}}{\left(\frac{9}{8}\right)^2 \left(\frac{7}{6}\right)^2}$$


$$= 15 \cdot \frac{3}{4} \cdot \frac{64}{81} \cdot \frac{36}{49}$$

$$P_L = 1 \text{ mW} \cdot 15 \cdot \frac{3}{4} \cdot \frac{64}{81} \cdot \frac{36}{49} = 6.53 \text{ mW}$$

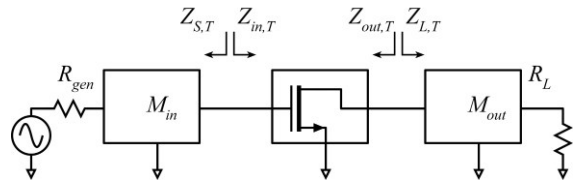part f, 10 points

At 100 GHz, the transistor has  
 $S_{11} = (1/2 + j/2)$  ← **note the change!**  
 $S_{21} = -4$ ,  $S_{12} = 0$ ,  $S_{22} = +1/3$ , (S-parameters using  $50\Omega$  normalization)

The generator has 50 Ohms source impedance and 1 mW available power. The load is 50 Ohms.



We impedance-match the generator to the transistor input and impedance-match the load to the transistor output .

Please find the following:

Input impedance of the transistor  $Z_{in,T} = 50 + j100 \Omega$

Source impedance presented to the transistor  $Z_{S,T} = 50 - j100 \Omega$ .

Output impedance of the transistor  $Z_{out,T} = 100 \Omega$

Load impedance presented to the transistor  $Z_{L,T} = 100 \Omega$

$S_{21}, S_{12} = 0$  so  $\Gamma_{in} = S_{11} = 1/2 + j/2$  &  $\Gamma_{out} = S_{22} = 1/3$

$Z_{in} = Z_0 \cdot \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 50 \Omega \cdot \frac{1 + 1/2 + j/2}{1 - 1/2 - j/2} = 50 \Omega \cdot \frac{3 + j}{1 - j}$   
 $= 50 \Omega \cdot \frac{3 + j}{1 - j} \cdot \frac{1 + j}{1 + j} = 50 \Omega \cdot \frac{3 + j + 3j - 1}{2}$   
 $\Rightarrow 50 \Omega \cdot \frac{2 + 4j}{2} = 50 \Omega (1 + 2j) = 50 \Omega + j100 \Omega$

$Z_{S,opt} = Z_{in}^* = 50 - j100 \Omega$

$Z_{out} = Z_0 \cdot \frac{1 + \Gamma_{out}}{1 - \Gamma_{out}} = 50 \Omega \cdot \frac{1 + 1/3}{1 - 1/3} = 50 \Omega \cdot \frac{3 + 1}{3 - 1}$   
 $\Rightarrow 50 \Omega \cdot 4/2 = 100 \Omega$

$Z_{L,T,opt} = Z_{out}^* = 100 \Omega$






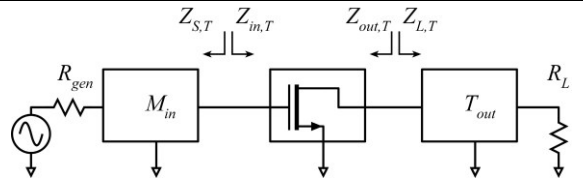part g. 10 points (218A only)

At 100 GHz, the transistor has  $S_{11}=0$ ,  $S_{21}=4$ ,  $S_{12}=1/8$ ,  $S_{22}=1/3$ ; ← **note the changes!** (S-parameters using  $50\Omega$  normalization)

The generator has  $R_{gen} = 50$  Ohms source impedance. The load is  $R_L = 50$  Ohms.



We are designing a \*power amplifier\*. We have independently determined from  $V_{max}$ ,  $V_{min}$ ,  $I_{max}$ , etc., that the optimum large-signal transistor load impedance is  $Z_{L,T}=200\Omega$  and that the maximum output power, at clipping, is 100 mW. We impedance-match on the input.

*note  $S_{12}S_{21} \neq 0$*  *match on input* *not match on output* }  $G_p$  <sup>2</sup>

Please find the following:

Available generator power at which the amplifier reaches clipping = \_\_\_\_\_

\*\*This will required some hard thinking\*\*

$$\Gamma_{L,T} = \frac{200/50 - 1}{200/50 + 1} = \frac{4-1}{4+1} = 3/5$$

$$\Gamma_{in,T} = S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L} = 0 + \frac{4 \cdot \frac{1}{8} \cdot \frac{3}{5}}{1 - \frac{1}{3} \cdot \frac{3}{5}}$$

$$= \frac{3/10}{1 - 1/5} = \frac{3}{10 - 2} = \frac{3}{8}$$

$$G_p = \frac{1}{1 - \|\Gamma_{in}\|^2} \cdot |S_{21}|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{|1 - \Gamma_L S_{22}|^2} = \frac{1}{1 - (3/8)^2} \cdot 16 \cdot \frac{1 - (3/5)^2}{|1 - \frac{3}{5} \cdot \frac{1}{3}|^2}$$

$$= \frac{1}{1 - \frac{9}{64}} \cdot 16 \cdot \frac{1 - \frac{9}{25}}{(1 - \frac{1}{5})^2}$$

$$\rightarrow \frac{64}{55} \cdot 16 \frac{1 - 9/25}{\left(\frac{4}{5}\right)^2}$$


$$= \frac{64}{55} \cdot 16 \cdot \frac{16}{25} \cdot \frac{25}{16} = \frac{64}{55} \cdot 16$$

$$P_{in} = \frac{\text{max output power}}{\text{gain}} = \frac{100 \text{ mW}}{\left(\frac{64}{55} \cdot 16\right)}$$

$$= \frac{100 \text{ mW}}{64 \cdot 16} \cdot 55 = 5.47 \text{ mW}$$

**Problem 2, 10 points**

*Stabilization*

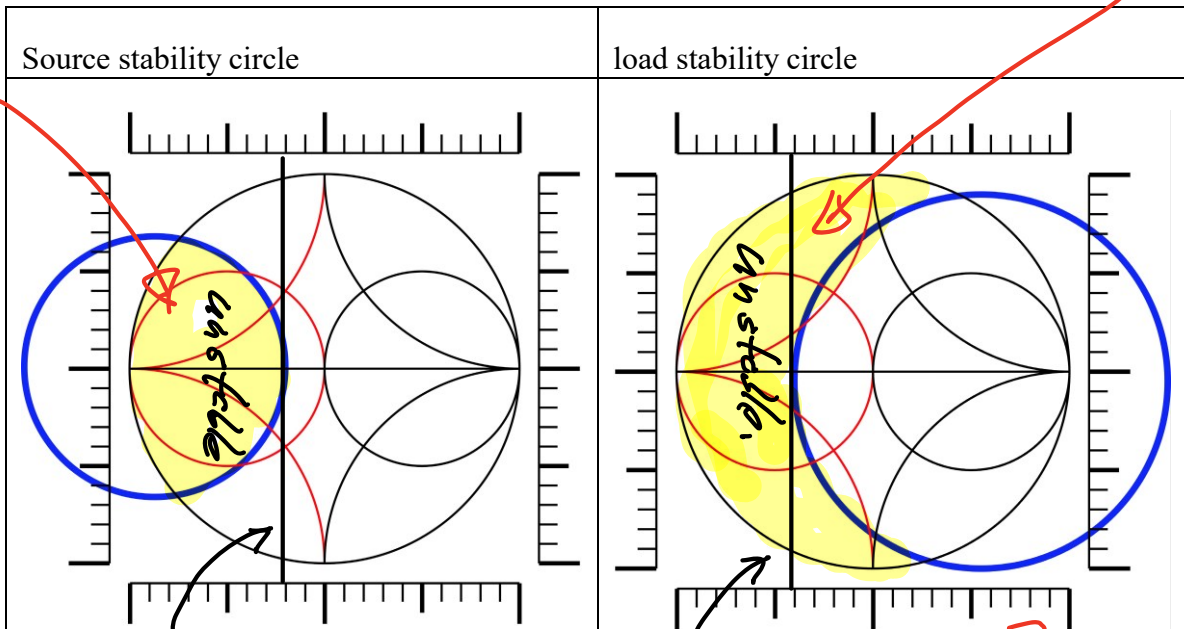


$\Gamma_s = -0.2$


$\Gamma_L = -0.4$

A MOSFET in common-source mode has  $\|S_{11}\| < 1$  and  $\|S_{22}\| < 1$ . Source and load stability circles are as shown. The Smith charts use 50 Ohms impedance normalization. Draw **\*\*2\*\*** circuit diagrams, giving resistor values, of methods of stabilizing the transistor. *Please draw your answers in the 2 boxes below*

circuit #1

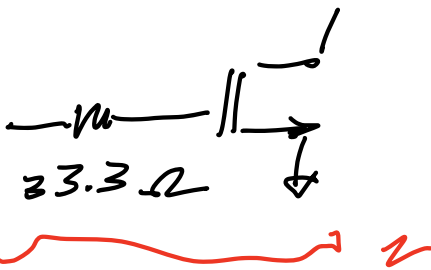

circuit #2

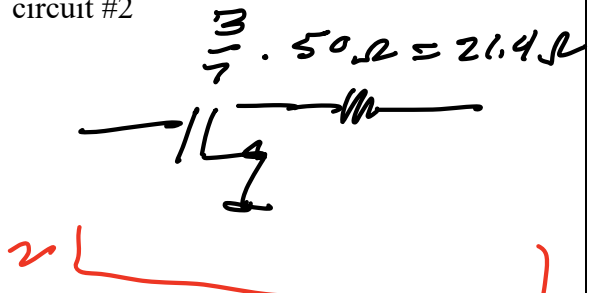

$$R_s / Z_0 = \frac{1 + \Gamma_s}{1 - \Gamma_s} = \frac{1 - 0.2}{1 + 0.2} = \frac{0.8}{1.2} = \frac{8}{12} = \frac{4}{6} = \frac{2}{3}$$

$$R_s = \frac{2}{3} \cdot 50 \Omega = 33.33 \Omega$$


$$R_s / Z_0 = \frac{1 + \Gamma_L}{1 - \Gamma_L} = \frac{1 - 0.4}{1 + 0.4} = \frac{0.6}{1.4} = \frac{6}{14} = \frac{3}{7}$$

$$R_s = \frac{3}{7} \cdot 50 \Omega = 21.4 \Omega$$



**Problem 3, 10 points**

Gain circles

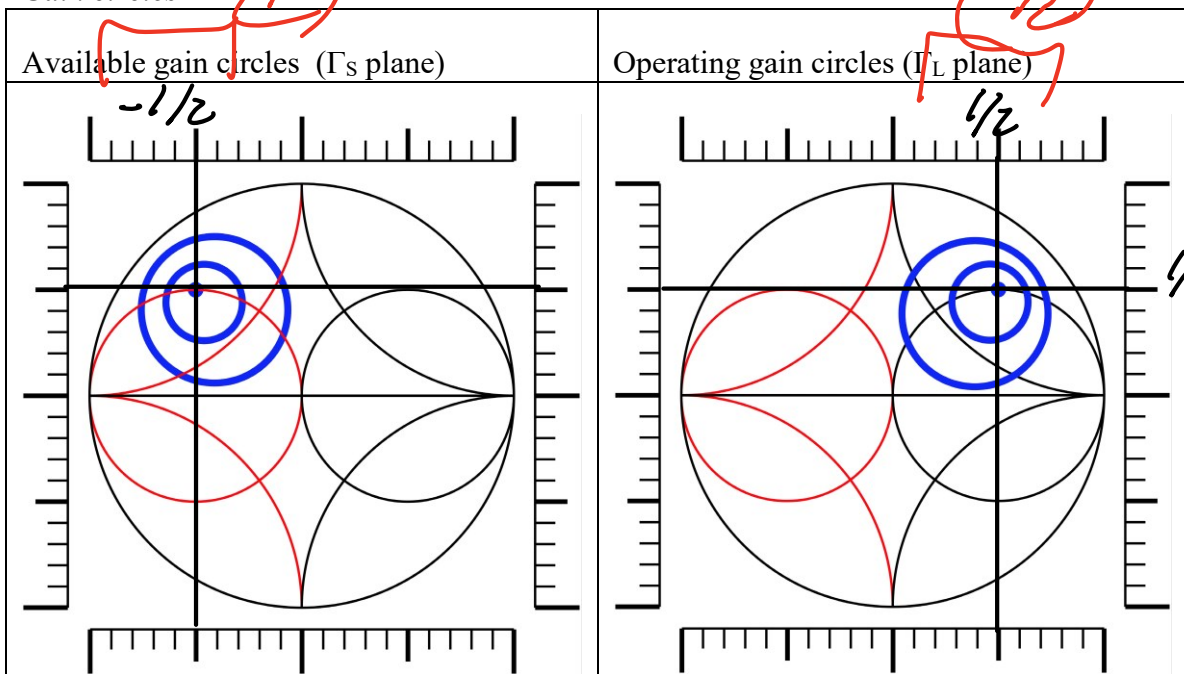

A FET in common-source mode has operating and available gain circles as shown (50 Ohm impedance normalization). Find the optimum generator and load impedances (in complex Ohms).

optimum source impedance =  $10\Omega + j20\Omega$

optimum load impedance =  $50\Omega + j100\Omega$

$\Gamma_{s,opt} = -1/2 + j/2$

$\frac{Z_{s,opt}}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 - 1/2 + j/2}{1 + 1/2 - j/2} = \frac{1 + j}{3 - j}$

$= \frac{1 + j}{3 - j} \cdot \frac{3 + j}{3 + j} = \frac{3 + j3 + j - 1}{10} = \frac{2 + 4j}{10}$

$= \frac{1 + 2j}{5}$

$Z_{s,opt} = 50\Omega \cdot \left( \frac{1 + 2j}{5} \right) = 10\Omega + j20\Omega$

$$n \left[ \Gamma_{2,opt} = 1/2 + j/2 \right]$$

$$Z_{L,opt} = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + 1/2 + j/2}{1 - 1/2 - j/2} = \frac{3 + j}{1 - j}$$

$$= \frac{3 + j}{1 - j} \frac{1 + j}{1 + j} = \frac{3 + j + 3j - 1}{2} = \frac{2 + 4j}{2}$$

$$= 1 + 2j$$

$$Z_{L,opt} = 50 \Omega + j 100 \Omega$$

**Problem 4, 10 points (145A), 20 points (218A)**

2-port parameters and signal flow graphs


Part a, 10 points

Amplifiers A and B have S-parameters

$$S_{ij}^A = \begin{bmatrix} 0 & 0 \\ 2 & 1/2 \end{bmatrix} \text{ and } S_{ij}^B = \begin{bmatrix} 1/2 & 0 \\ 2 & 0 \end{bmatrix}$$



(S-parameters using 50Ω normalization).
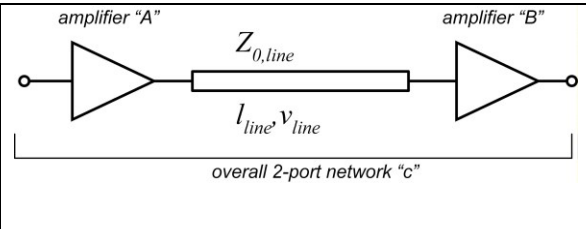
$$Z_{o,line} = 50 \Omega, l_{line} / v_{line} = \tau_{line} = 1 \text{ nS.}$$



Compute  $S_{21}^c$  as a function of frequency. (hint: first draw a signal flow graph)

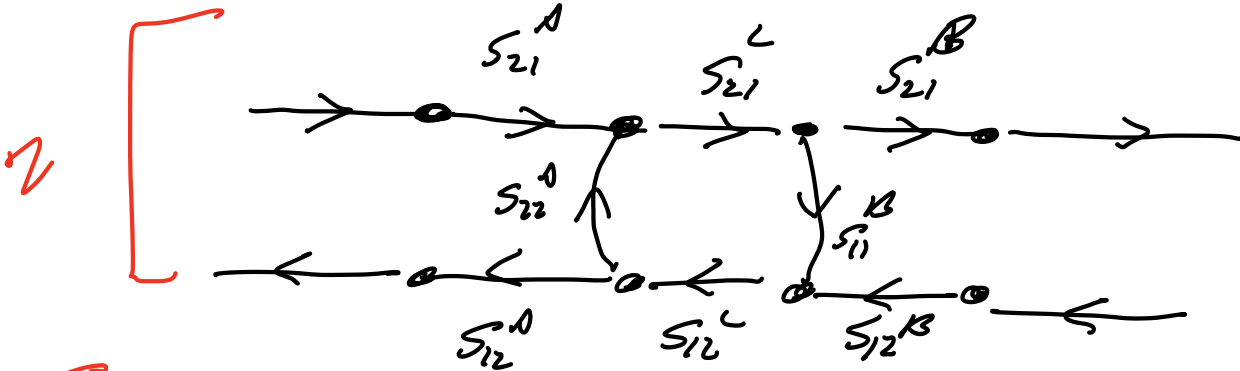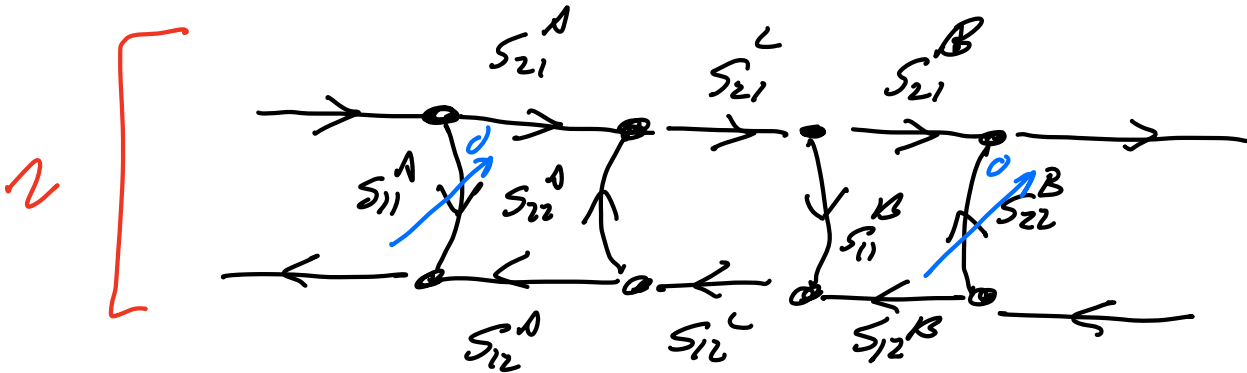2 [ Key: the line has  $S_{11}^L \approx S_{22}^L = 0$   
 &  $S_{21}^L = S_{12}^L = \exp(-j\omega\tau_{line})$



2 [

$$S_{21}^c = \frac{S_{21}^A S_{21}^L S_{21}^B}{1 - S_{22}^A S_{11}^B S_{21}^L S_{12}^L}$$

$$2 \left[ S_{21}^c = \frac{4 \cdot e^{-j\omega T}}{1 - \frac{1}{4} e^{-2j\omega T}} \right] \quad \text{where } T = 1 \text{ ns}$$




Part b, 10 points (218a only)

Amplifier A has S-parameters

$$S_{ij}^A = \begin{bmatrix} 0 & 1/4 \\ 2 & 1/2 \end{bmatrix}$$


(S-parameters using  $50\Omega$  normalization).

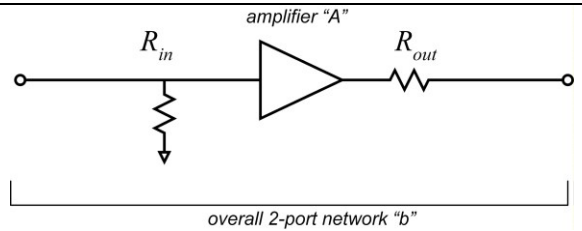Resistors  $R_{in} = 50\Omega$  and  $R_{out} = 50\Omega$  are added in parallel to the input and in series to the output.




Compute  $S_{21}^B$  (hint: first draw a signal flow graph)

$$Z_{in} |_{Z_L = Z_0} = Z_0/2 \rightarrow S_{11} = \frac{1/2 - 1}{1/2 + 1} = -1/3 = S_{22}$$

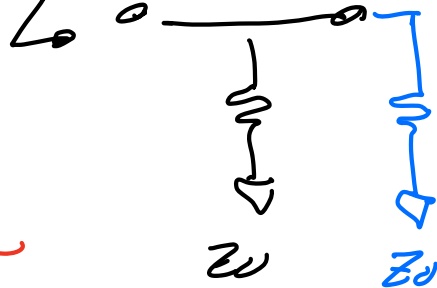


$$\frac{V_0}{V_{gen}} = \frac{1/2}{1/2 + 1} = \frac{1}{2}$$

$$\Rightarrow S_{21} = \frac{2V_0}{V_{gen}} |_{Z_L = Z_0 = Z_0} = 2/3 = S_{12}$$

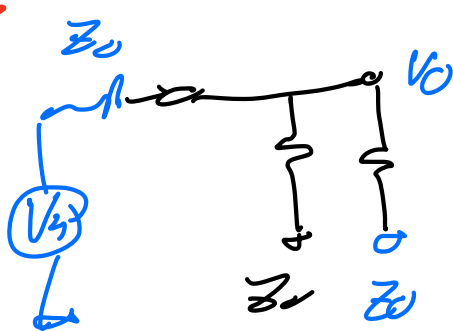




$$Z_{in} |_{Z_L = Z_0} = 2Z_0 \rightarrow S_{11} = \frac{2 - 1}{2 + 1} = +1/3 = S_{22}$$

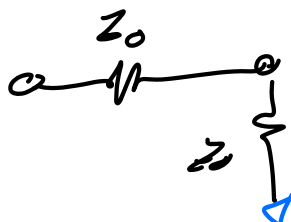

$$V_0/V_{gen} = 1/3$$

$$\rightarrow S_{21} = 2/3 = S_{12}$$

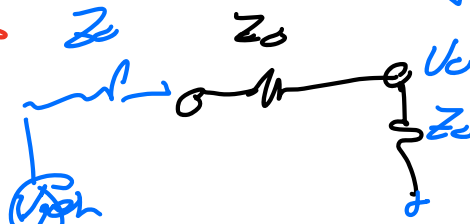

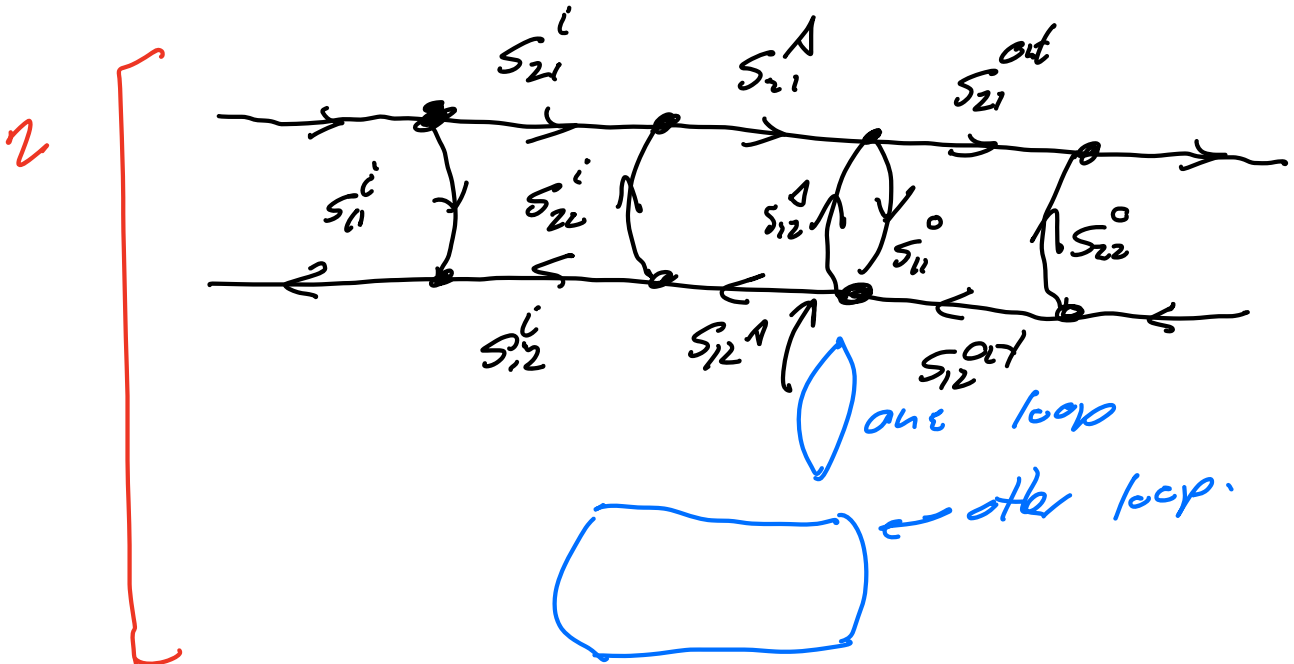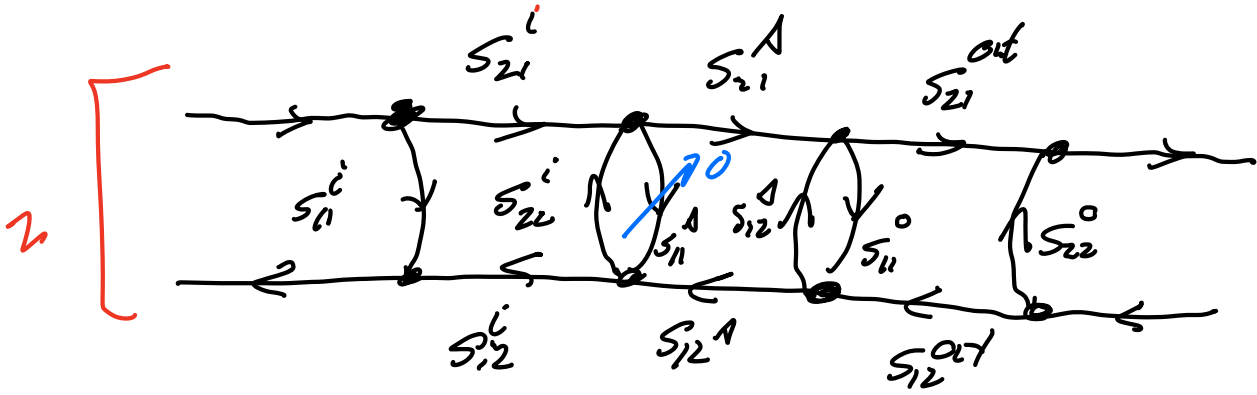

2

$$S_{21}^B =$$

$$S_{21}^{in} S_{21}^A S_{21}^{out}$$

$$1 - S_{22}^A S_{11}^o - S_{22}^i S_{21}^A S_{11}^o S_{12}^A$$

$$= \frac{(2/3) \cdot 2 \cdot (2/3)}{1 - (1/2)(1/3) - (-1/3)(2)(1/3)(1/4)}$$

$$= \frac{8/9}{1 - 1/6 + 1/18}$$

$$= \frac{8/9}{1 - 1/6 + 1/18}$$

$$= \frac{16}{18 - 3 + 1} = \frac{16}{16} = 1$$

**Problem 5, 5 points (145A), 15 point (218A)**  
 Power amplifier design

(Note actual Teledyne value is 2 mA/μm)

part a, 5 points

Teledyne's 250nm node InP HBT (heterojunction bipolar transistor) technology has a maximum safe current of 1 mA per micrometer of emitter finger length. For wide bandwidth (high fmax), the maximum emitter finger length is 5.0 micrometers; set the emitter length at this value, but use multiple emitter to further increase maximum output current to some desired value. The maximum safe collector-emitter voltage is 4.5 V, and the minimum (knee) voltage is 0.5 Volts.

What is the maximum RF power per 1 micron of emitter finger length ?

Power (1 micron) = 1/2 mW

We seek to design a multi-finger HBT cell layout that interfaces to 50 Ohms, with some parallel inductance to tune out the HBT output capacitance.

How many 5 micrometer length emitter fingers would that cell use ? 16

What is the maximum output power of that cell ? 40 mW

What would be the collector efficiency ? 40 %

1 [ 1 μm finger → 1 mA,  $V_{max} - V_{min} = 4V$   
 $P_{max} = 1 mA \cdot 4V / 2 = 0.5 mW$

2 [ want 50Ω load  
 $R_L = 50Ω \Rightarrow \frac{V_{max} - V_{min}}{I_{MAX}} = \frac{4V}{I_{MAX}}$   
 $I_{max} = \frac{4V}{50Ω} = \frac{8V}{100Ω} = 80 mA$   
 $\Rightarrow 80 μm$  length →  $\frac{80 μm}{5 μm / finger} \rightarrow 16$  fingers

$$1] P_{max} = 80 \mu m \cdot 0.5 \text{ mW}/\mu m = 40 \text{ mW}.$$

$$1] \eta_c = \frac{1}{2} \frac{V_{max} - V_{min}}{V_{max} + V_{min}} = \frac{1}{2} \cdot \frac{4.5V - 0.5V}{4.5V + 0.5V}$$
$$= \frac{1}{2} \cdot \frac{4}{5} = \frac{2}{5} = 40\%.$$

0.5  
x


part b, 10 points (218A only)

The transistor is now modelled by the equivalent circuit to the right.

$$g_m = (1 \text{ mA}/\mu\text{m} \cdot q / kT) \cdot (\text{emitter length}) \cdot (\text{number emitter fingers})$$

$$\beta = 25$$

$$R_{bb} = 10 / g_m$$

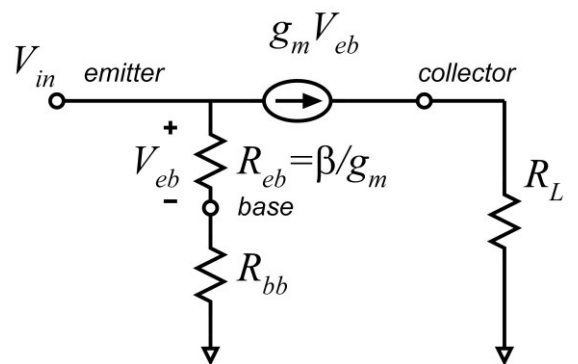


Given the 50 Ohm load, the 5 micron emitter length, and the number of emitter fingers you have found earlier, what input power is necessary to produce this maximum output power ?

$$g_m = \frac{0.5 \text{ mA}}{1 \mu\text{m}} \cdot \frac{q}{kT} \cdot 80 \mu\text{m} = \frac{40 \text{ mA}}{26 \text{ mV}}$$

$$1/g_m = \frac{26 \text{ mV}}{40 \text{ mA}} = \frac{2.6 \Omega}{4} = \frac{1.3 \Omega}{2} = \underline{\underline{0.65 \Omega}}$$

$$R_{eb} = \beta / g_m = 25 \cdot 0.65 \Omega$$

$$R_{bb} = 10 / g_m = 6.5 \Omega$$

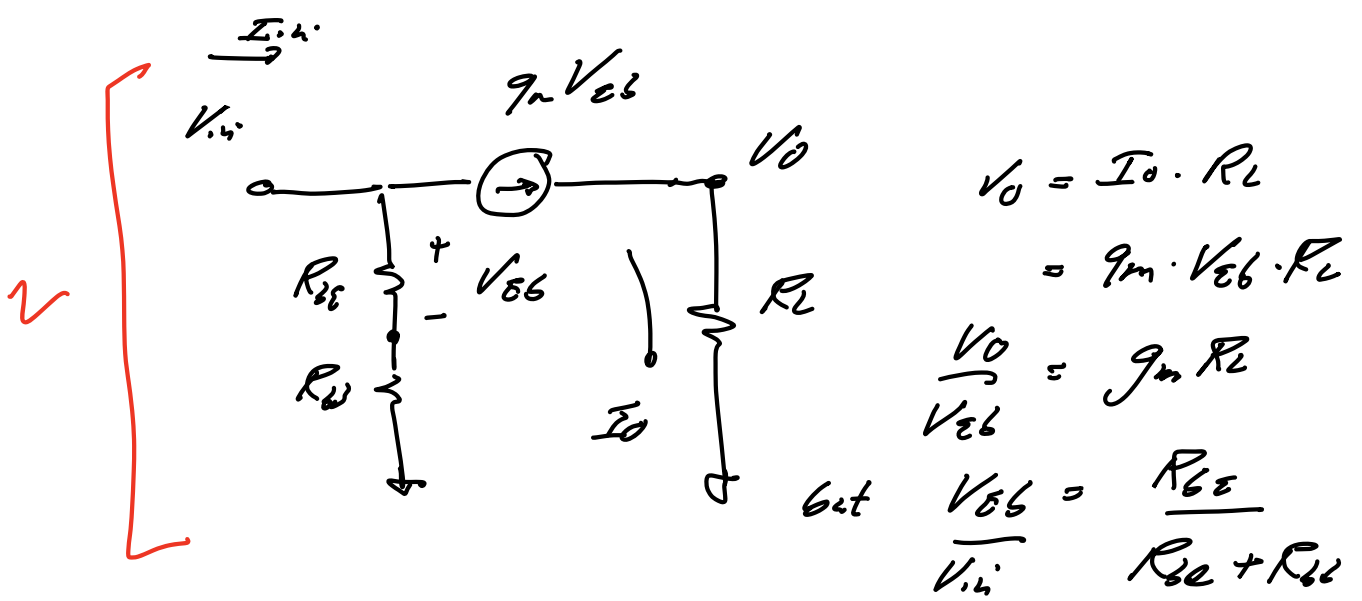

$$\frac{V_o}{V_{in} \cdot \frac{R_{be}}{R_{be} + R_L}} = g_m R_L \rightarrow \left[ \frac{V_{out}}{V_{in}} = \frac{R_{be}}{R_{be} + R_L} \cdot g_m R_L \right]^2$$

$$\left[ \frac{I_{out}}{I_{in}} = \frac{1}{1 + \frac{1}{\beta}} = \frac{\beta}{\beta + 1} \right]^2$$

$$\left[ \frac{P_{out}}{P_{in}} = \frac{V_o}{V_{in}} \cdot \frac{I_o}{I_{in}} = \frac{\beta}{\beta + 1} \cdot g_m \cdot R_L \cdot \frac{R_{be}}{R_{be} + R_L} \right]^2$$

$$= \frac{25}{26} \cdot \frac{50 \Omega}{0.65 \Omega} \cdot \frac{\beta / g_m}{\beta / g_m + 10 / g_m}$$


$$= \frac{25}{26} \cdot \frac{50 \Omega}{0.65 \Omega} \cdot \frac{25}{25 + 10} =$$

$$= \frac{25}{26} \cdot \frac{50}{0.65} \cdot \frac{25}{35} = \underline{\underline{52.8}}$$



$$P_{in} = \frac{P_o}{P_o/P_{in}} = \frac{40mW}{P_o/P_{in}} = \underline{0.757mW}$$

alternate method:

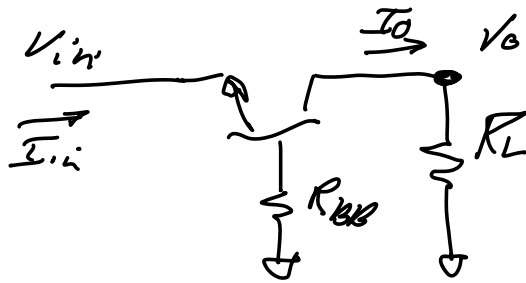

From basic  
transistor  
circuit design  
(ECE137A)

$$\frac{V_o}{V_{in}} = \frac{R_L}{R_{inT}} = \frac{R_L}{1/g_m + R_{BE}/\beta}$$

$$\frac{I_o}{I_{in}} = \frac{\beta}{\beta+1} \quad \text{so}$$

$$\frac{P_o}{P_{in}} = \frac{\beta}{\beta+1} \frac{R_L}{1/g_m + R_{BE}/\beta}$$

$$= \frac{\beta}{\beta+1} \frac{g_m R_L}{1 + g_m R_{BE}/\beta}$$

$$= \frac{\beta}{\beta+1} \cdot g_m R_L \frac{1}{1 + g_m R_{BE}/\beta}$$

$$= \frac{\beta}{\beta+1} g_m R_L \frac{\beta/g_m}{\beta/g_m + R_{BE}}$$

$$= \frac{\beta}{\beta + 1} \cdot g_m R_L \cdot \frac{R_{be}}{R_{be} + R_{b2}}$$

= Same answer as above