


ECE 145A / 218 C, notes set xx: Class A power amplifiers

Mark Rodwell


University of California, Santa Barbara

Class A power amplifier: what do we mean ?

PA has input, output tuning

 


loadline would be as so

 


Transistor Output Characteristics: Real


250nm InP HBT

 

500nm InP HBT

 

 Transistor Output Characteristics: Idealized



Minimum voltage: V_{sat}


Maximum voltage: V_{br}

Maximum current: I_{max}

FETs: $I_{max} \propto W_g$, # gate fingers

bipolars: $I_{max} \propto L_e$, # emitter fingers

Transistor Output Characteristics: Real

 

V_{br} varies with current


V_{sat} varies with current

Subsequent lecture notes are therefore somewhat idealized

Transistor Output Characteristics: Power

Transistor power = $V_{ce} I_c$ or $V_{DS} I_D$

Constant power : hyperbola on I_{out}, V_{out} plane

 

Case 1 : low - frequency power amp

frequency \ll (thermal time constant) $^{-1}$

→ loadline must lie below maximum power density curve


Case 2 : high - frequency power amp

frequency \gg (thermal time constant) $^{-1}$

→ *bias point* must lie below maximum power density curve

Device Bandwidth vs Operating Point

bipolar transistors :

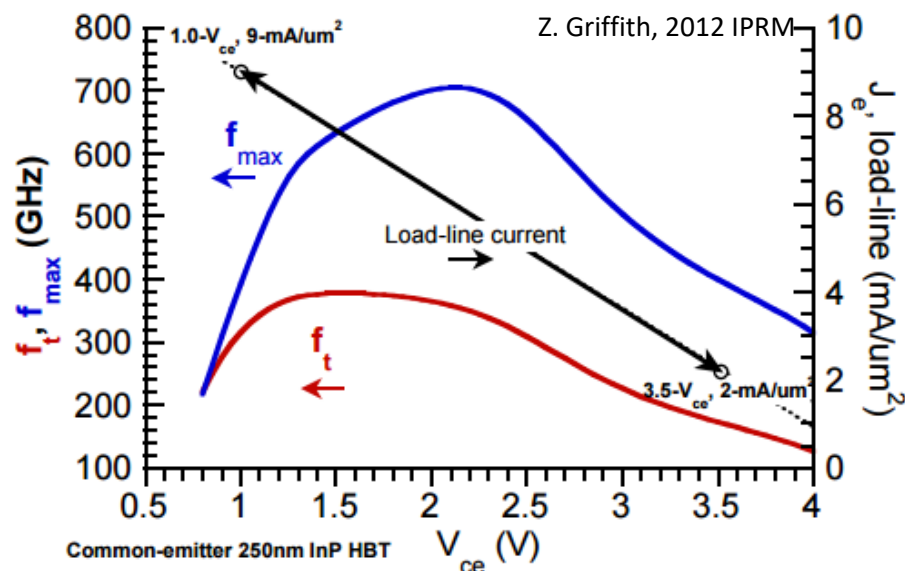

Low voltage, high current :

"Kirk effect" = space - charge - limited current

reduction in f_t , increase in C_{cb} → reduced bandwidth

High voltage :


all semiconductors : push - out of collector depletion region

III- V semiconductors : reduction of electron velocity in collector


reduction in f_t , * de * crease in C_{cb} → reduced bandwidth

Device Bandwidth vs Operating Point: FETs

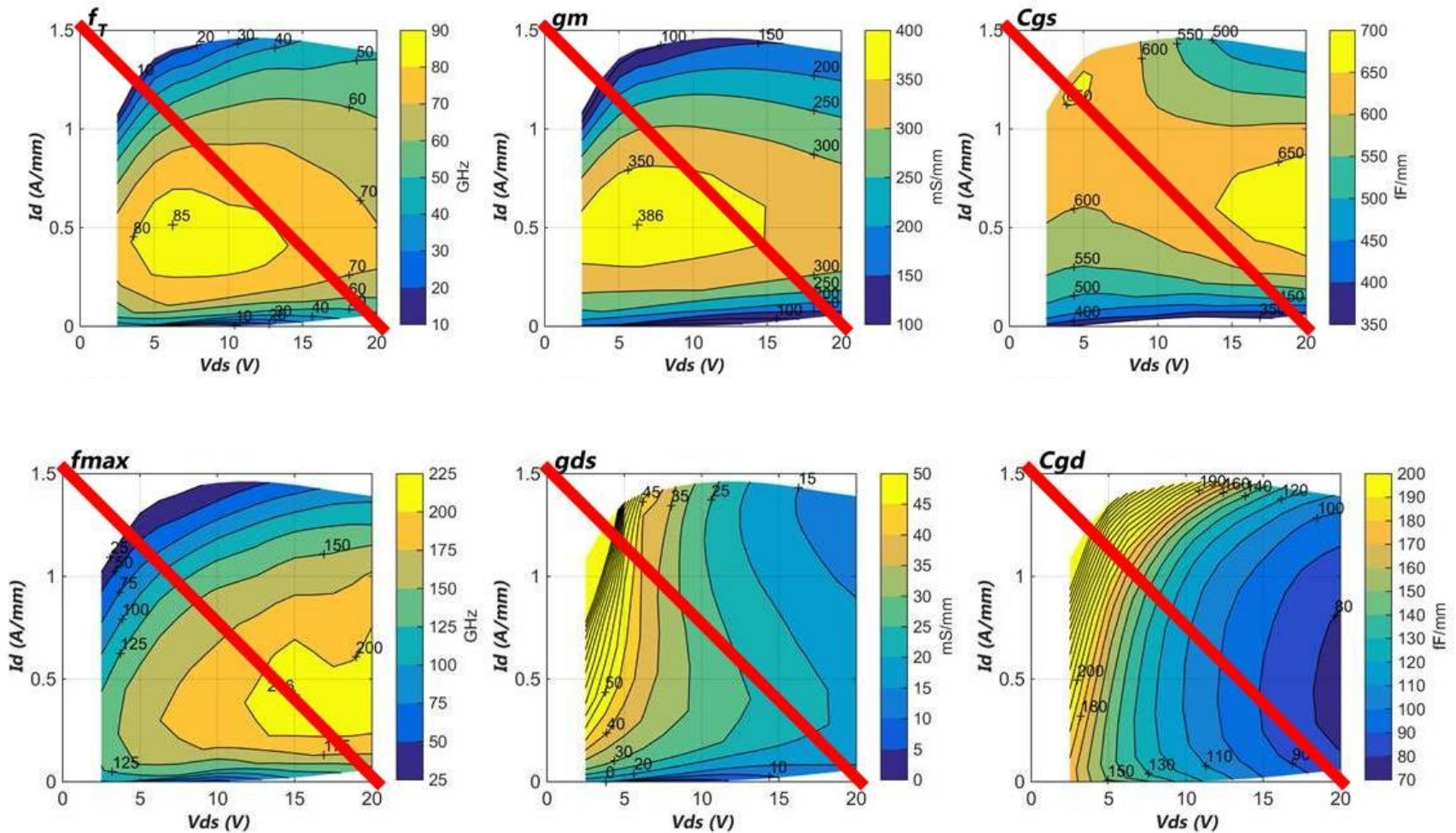Variations of g_m , C_{gs} , f_T , over loadline.



 
Device Bandwidth vs Operating Point: FETs



Increased drain bias \rightarrow increased drain depletion
 \rightarrow increased transit time, decreased C_{gd} , decreased G_{ds}

Also: variation of g_m with current.

 Low at both low currents and high currents



Operating areas

Safe operating area

standard terminology




region bounded by power, V_{br} , I_{max}

fast operating area

not standard terminology

region with adequately high f_t , f_{max}

Loadline must lie within both

  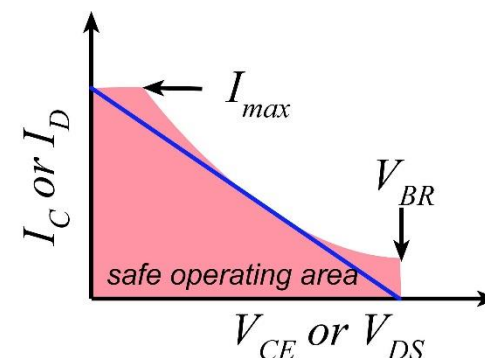


safe operating area
 fast operating area
 loadline


Oversimplified SOA/FOA; for class

Maximum, minimum voltages

Maximum current $\propto W_g$ or L_E

 

Simple class A power analysis

 

Bias point in center of rectangle.

Loadline reaches corners of rectangle

$$Z_L = (V_{\max} - V_{\min}) / I_{\max}$$


$$P_{DC} = V_{DC} I_{DC} = (V_{\max} + V_{\min}) I_{\max} / 4$$

$$P_{RF, \max} = (V_{\max} - V_{\min}) I_{\max} / 8$$

$$\text{maximum drain/collector efficiency} = \eta_{\text{drain/collector}} = P_{RF, \max} / P_{DC} = 1/2$$


Power-added efficiency
 
$$\begin{aligned}
 \text{P.A.E.} &\equiv (P_{out} - P_{in}) / P_{DC} \\
 &= \frac{P_{out}}{P_{DC}} \left[1 - \frac{P_{in}}{P_{out}} \right] = \eta_{\text{drain/collector}} \cdot \left[1 - \frac{1}{\text{gain}} \right]
 \end{aligned}$$



Noting that P_{out} for one stage is P_{in} for the next,
 if we have a chain of PAs with identical PAE,
 at that specific operating RF power, then
 the PAE of the cascade will be that of the individual PAs.

Power Amplifier Design

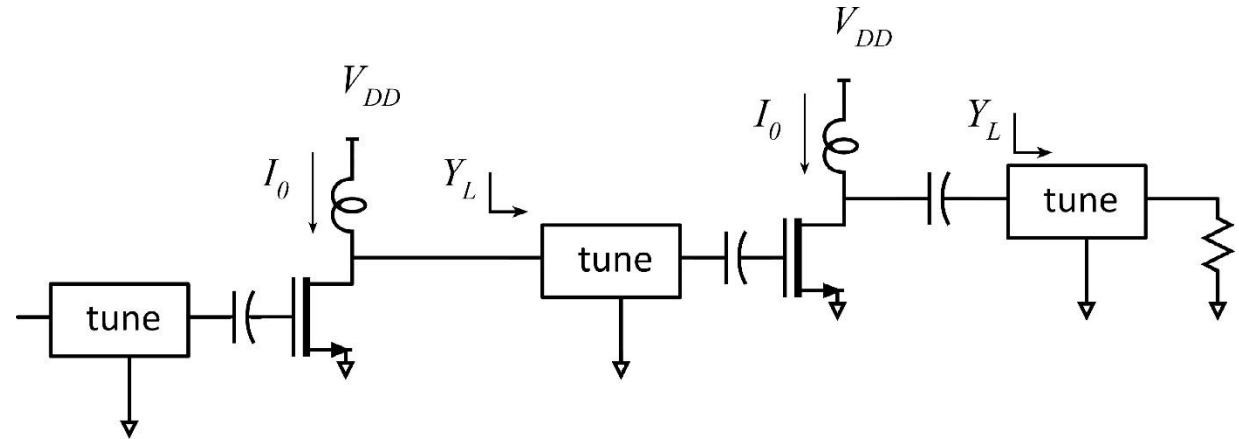




For highest efficiency, each stage should be loaded with

$$Z_{L,opt} = (V_{\max} - V_{\min}) / I_{\max}$$

The interstage networks are tuning networks,
not matching networks.

Thus far, we have neglected transistor parasitics.

  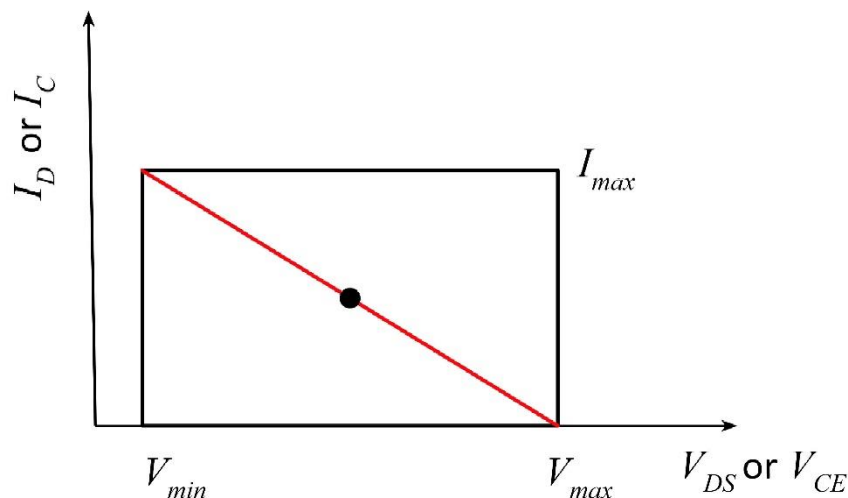Loadline: inclusive of transistor parasitics



Transistors have resistive, capacitive parasitics.


It is the *internal* (I_C, V_{CE}) or (I_D, V_{DS}) which must follow the above loadline.

Loadline current must be electron current, not $C \cdot dV / dt$ displacement current.

Current meters must be placed inside the capacitive parasitics.

How do we do this ?

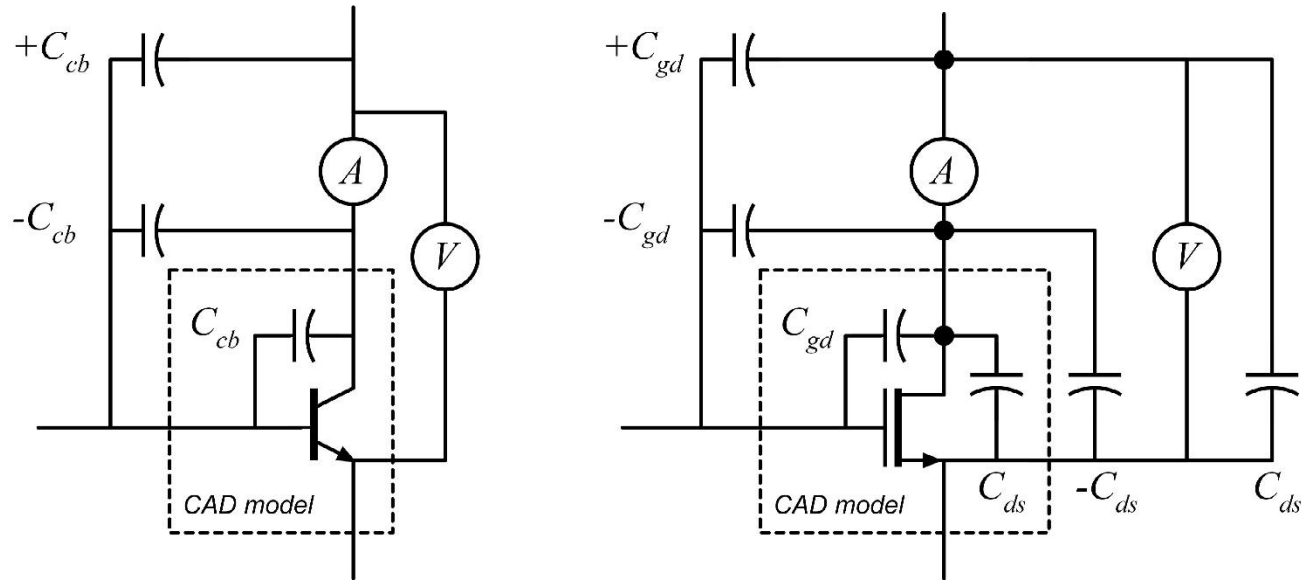Loadline: inclusive of transistor parasitics



Read the CAD device model → determine transistor capacitances.

Add external negative capacitances to cancel these.

Add voltmeter and current meter.

These correctly measure the loadline



Then add external positive capacitances.

Example of ammeter, voltmeter placement

Here I took the CAD model and

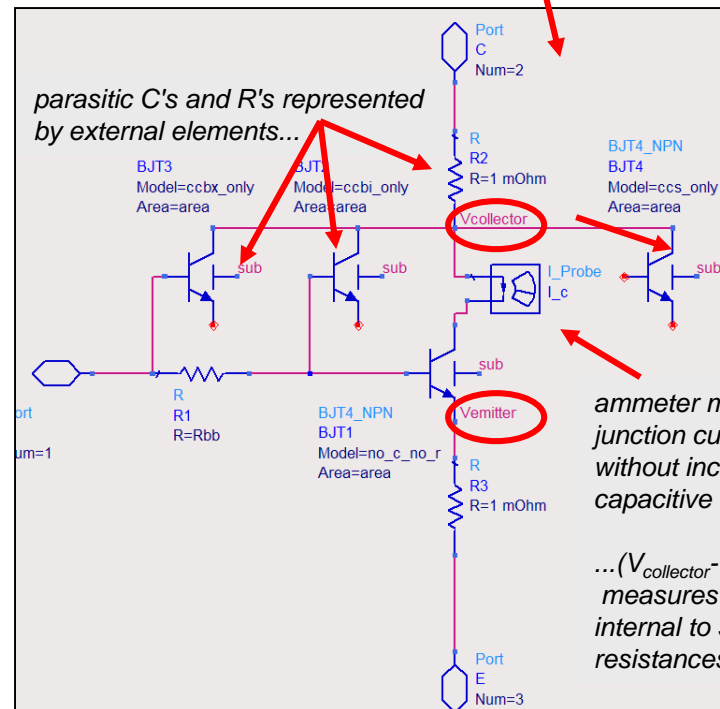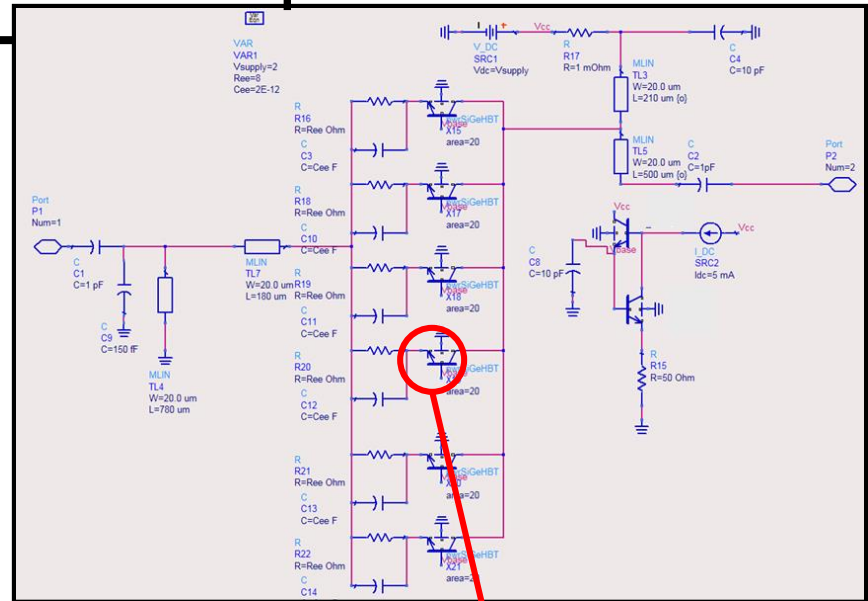- 1) created a variant with zero C_{cb} , zero $C_{c,sub}$
- 2) used this for the active transistor model.
- 3) created a second variant with C_{cbi} only
- 4) created a third variant with C_{cbx} only.

In this manner, voltage variation of the capacitances is correctly accounted for.



Power Amplifier Methodology


The above technique, direct loadline method
known as the Cripps technique
requires that you know, add, subtract capacitances.

Alternate technique : load pull contours
Empirical, not analytical
will cover in a few slides



Power Amplifier Design (Cripps Method)

Design steps are

 - 1) input stabilization (in-band)
- 2) output tuning for correct load-line
- 3) input tuning (match)
- 4) out-of-band stabilization




Example: 60 GHz, 30 mW PA, 130 nm BiCMOS

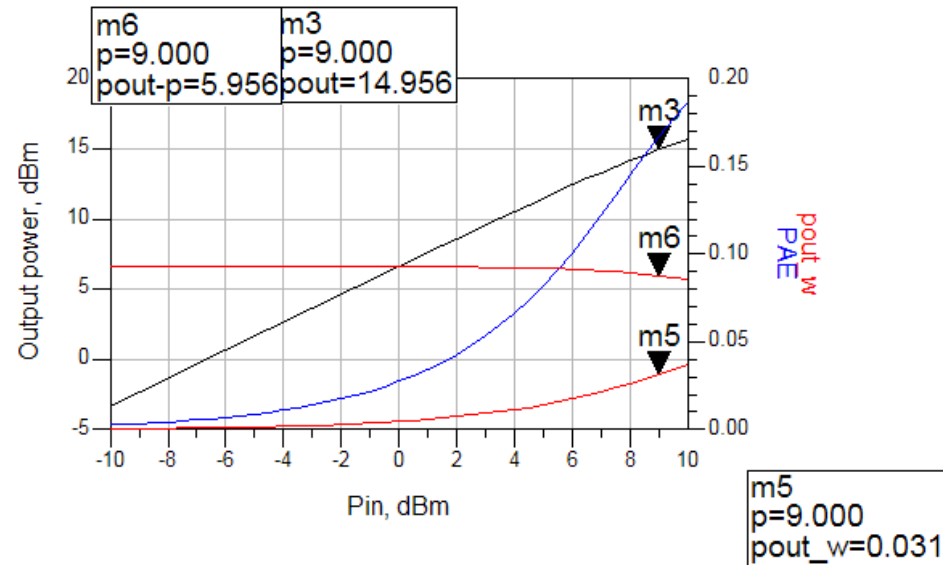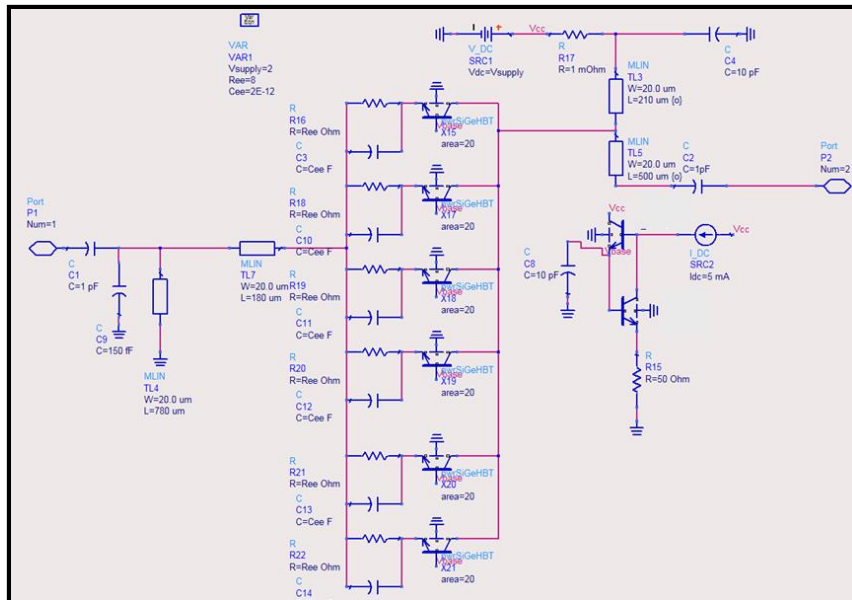

Power Amplifier Design Example

Power amplifier *cell*. 20 micron emitter finger.

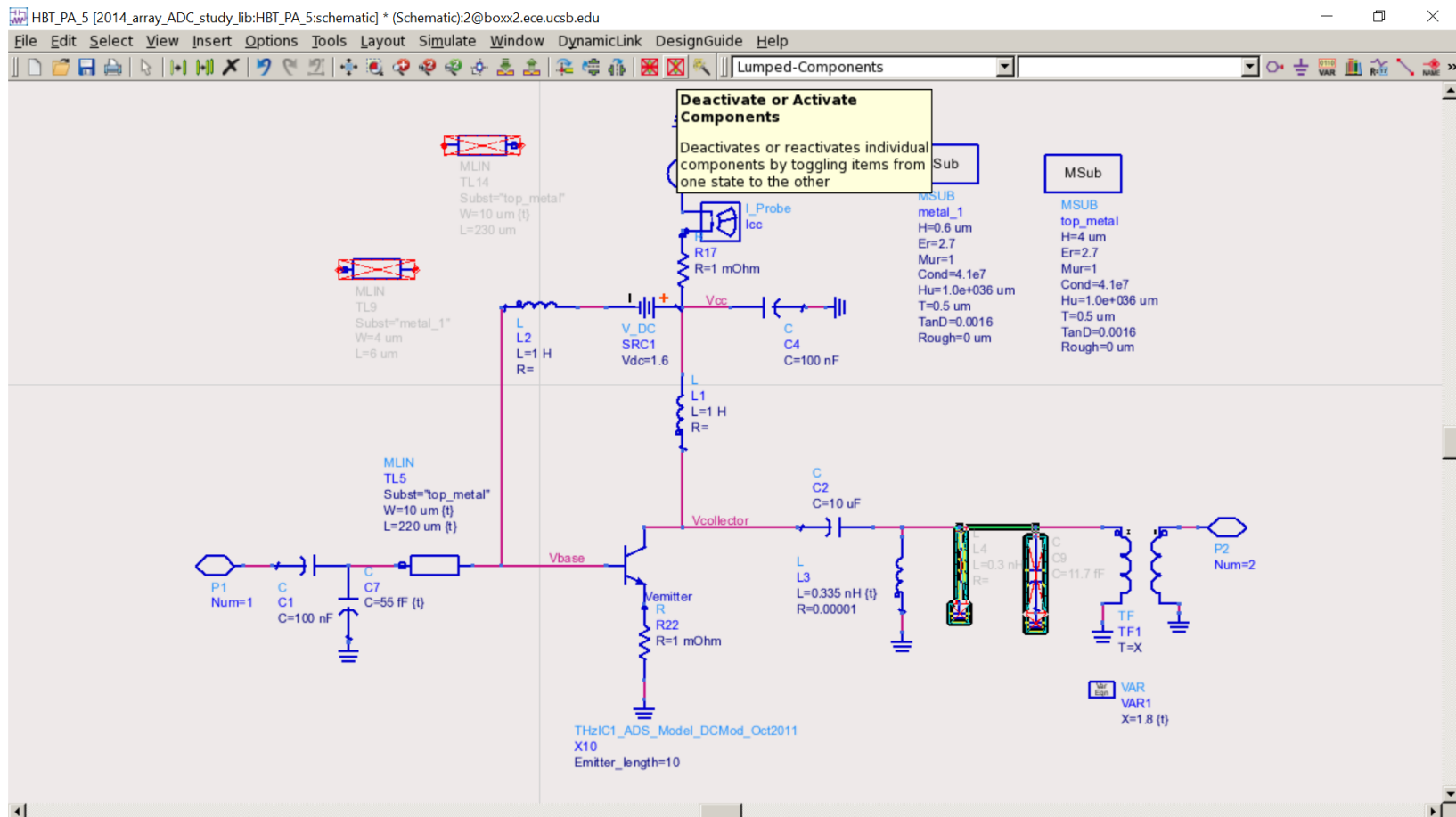bias : $I_c = 10\text{mA}$, $V_{cb} = 1.86\text{ Volts} \rightarrow V_{CE} = 2.5\text{V}$.




The biasing technique used is just for CAD experimentation; not practical

The inactivated output LC network is a bandpass filter

Power Amplifier Design Example

First, simulate the transistor vs frequency at the bias point,
determine f_{max} , MAG/MSG at the design frequency.
determine the stability factor at the design frequency
if unstable, stabilize (input network) at the design frequency

PA example: output network

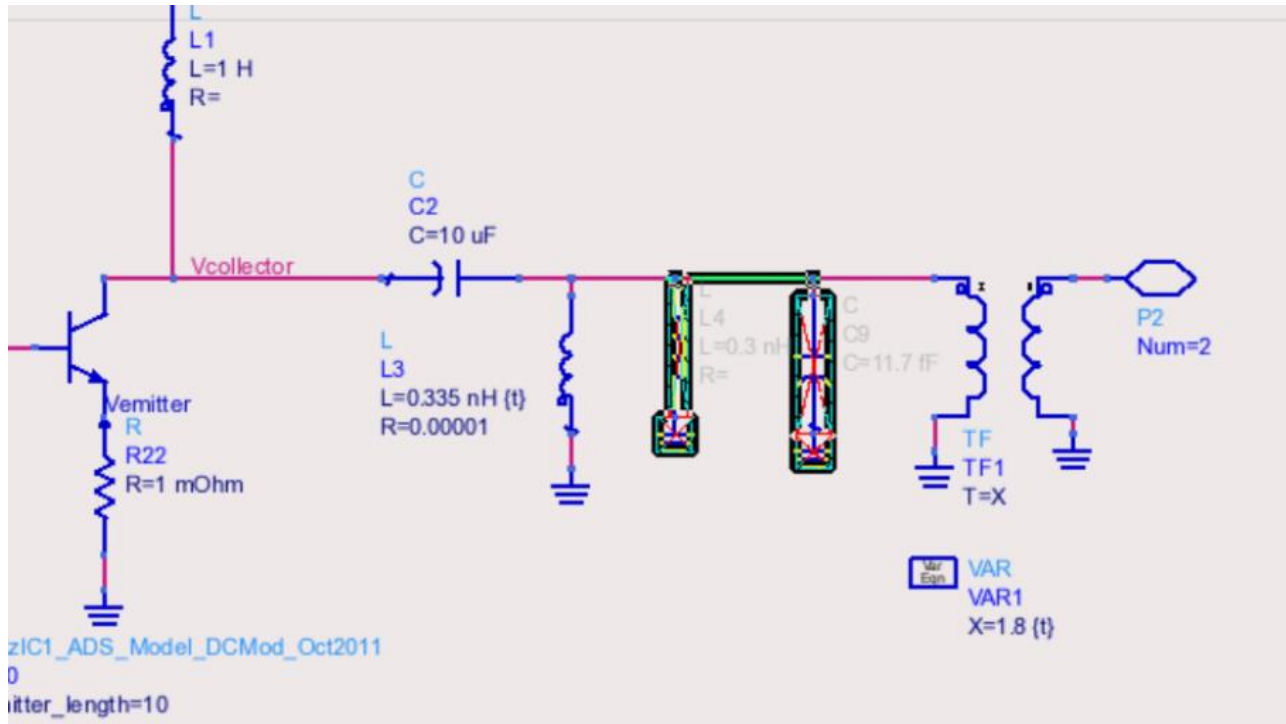

Note the output network : ideal transformer plus parallel inductance.


This is not the final output network : it is used to quickly find $Y_{L,opt}$.

PA example: measuring the loadline

THzIC1_ADS_Model_DCMod_Oct2011 [2014_array_ADC_study_lib:THzIC1_ADS_Model_DCMod_Oct2011:schematic] (Schematic):2@boxx2.ece.ucsb.edu

File Edit Select View Insert Options Tools Layout Simulate Window DynamicLink DesignGuide Help

Lumped-Components

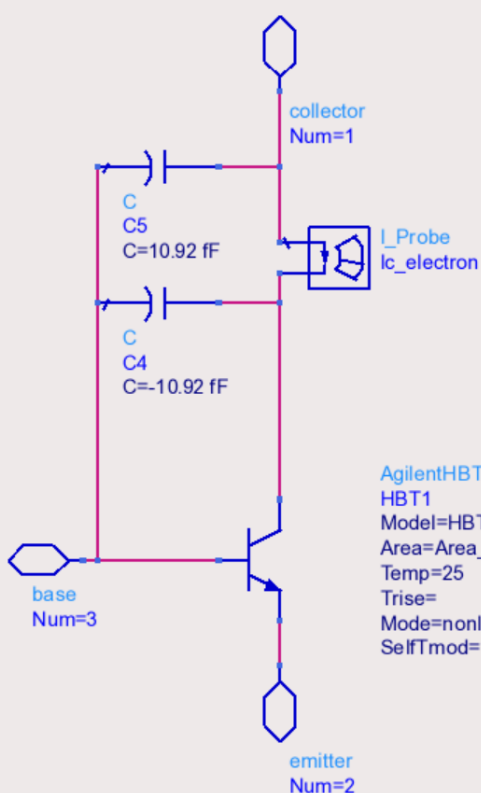

collector
Num=1

C
C5
C=10.92 fF

I_Probe
Ic_electron

C
C4
C=-10.92 fF

base
Num=3

emitter
Num=2


AgilentHBT_NPN
HBT1
Model=HBTM1
Area=Area_physical
Temp=25
Trise=
Mode=nonlinear
SelfTmod=1

AgilentHBT_Model
HBTM1
Tnom=25.0
Re=(Rex*Area_physical) Ohm
Rci=0 Ohm
Rcx=(Rc*Area_physical) Ohm
Rbi=(Rbb*Area_physical) Ohm
Rbx=0 Ohm
Is=369a
Nf=1.016
Isr=369a
Nr=1.016
Ish=135a
Nh=1.104
Ise=.736 pA
Ne=1.834
Isrh=.989a

Nrh=736m	Gkdc=0.0
Isc=66.8 pA	Ik=1.0 A
Nc=1.772	Cje=(Cje/Area_pf
Abel=0.0	Vje=4 V
Vaf=32 V	Mje=0.0001
Var=20 V	Cemax=10*(Cje/A
Isa=1.0e+10 A	Vpte=1.0 V
Na=1.0	Mjer=0.05
Isb=1.0e+10 A	Abex=0.0
Nb=1.0	Cjc=(1.64*Ccb/Ar
Ikdc1=10 A	Vjc=0.5 V
Ikdc2Inv=0.0	Mjc=.9
Ikdc3=10.0 A	Ccmax=50 fF
VkdcInv=0.1	Vptc=0.85 V
Nkdc=3.0	Mjcr=0.01

Dropping down in the hierarchy into the device model, we see the monitoring ammeter plus negative and positive Ccb.

PA example: finding the optimum load


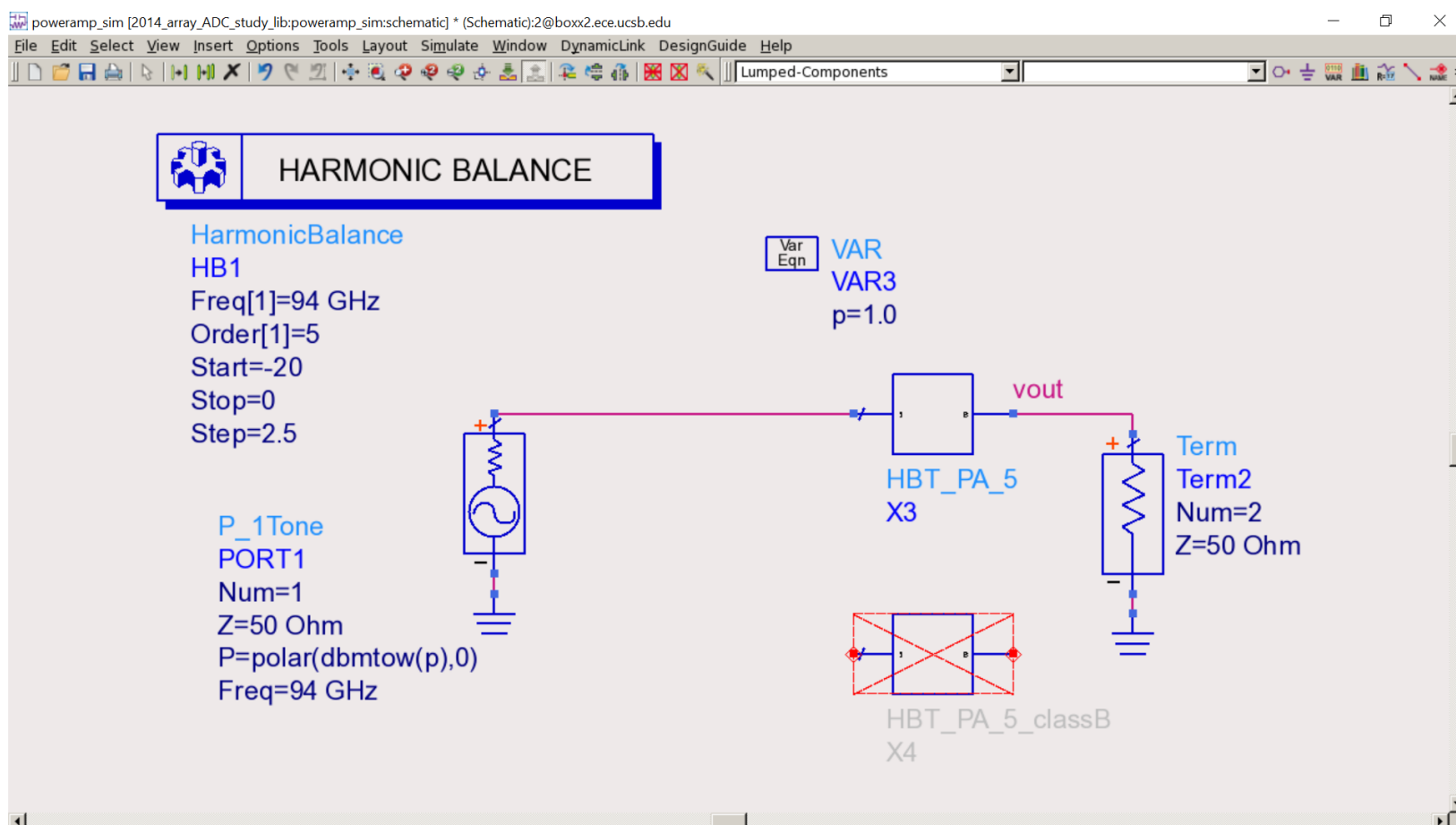


The input is not yet matched, and the load is not yet tuned.

We drive the transistor with a large drive signal and observe the loadline



Power Amplifier Design Example

 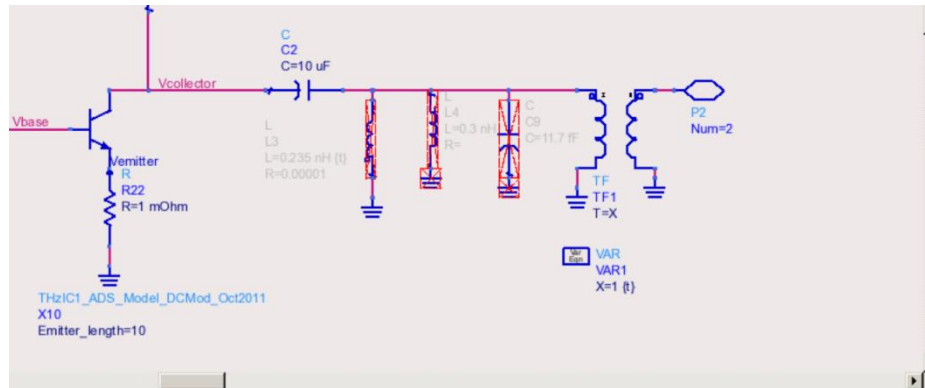With no inductive tuning, and with a 1:1 transformer ratio,
The loadline initially looks like this :





Power Amplifier Design Example

 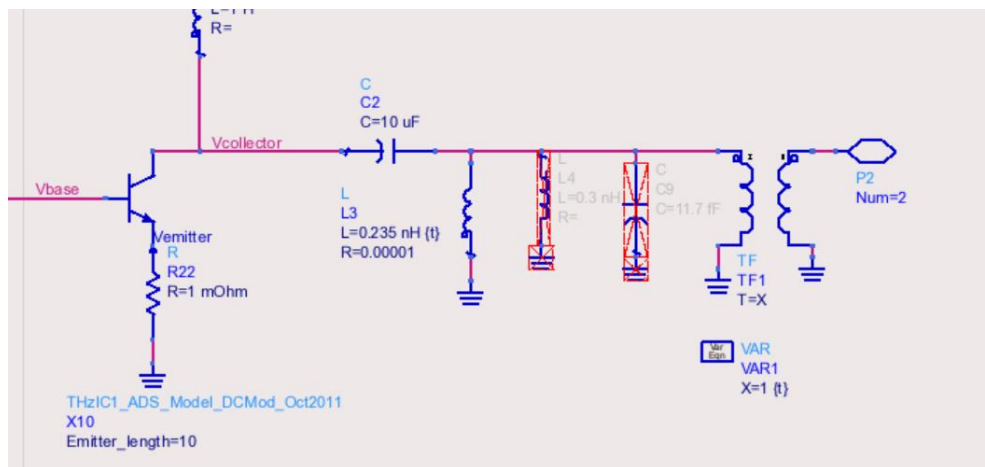First add the inductive tuning, adjusting the shunt L to eliminate loadline looping



Power Amplifier Design Example

 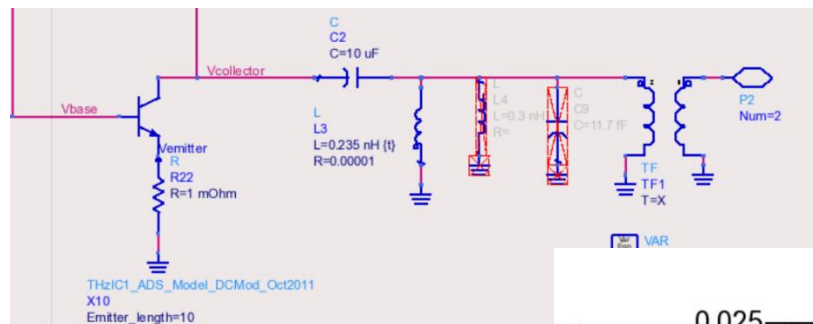Then adjust the transformer ratio to obtain a loadline passing through the target endpoints (V_{\min}, I_{\max}) and ($V_{\max}, I_{\min} = 0A$)



We had expected a straight line.


The looping (3 per cycle) is 3rd harmonic generation

Power Amplifier Design Example

We have now determined Y_{opt} .

We then (not shown), in a separate circuit simulation file, design a practical output network which provides Y_{opt} .

We then add this to the PA.

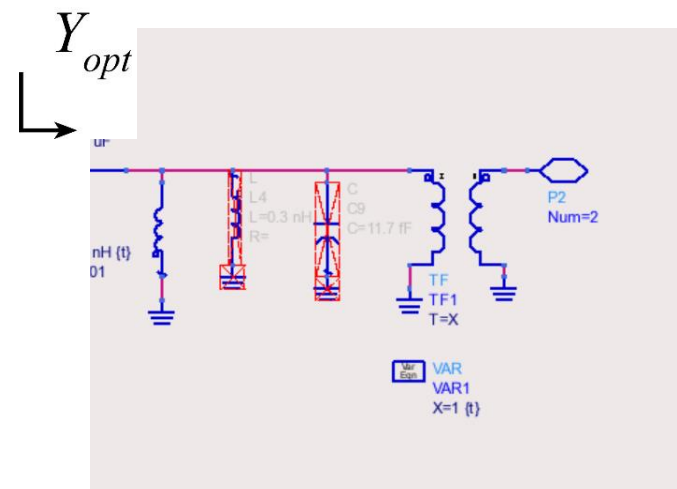

Power Amplifier Design Example

Remaining steps :

Input matching network

Out - of - band stabilization


(ece145a)

Often : filters

to suppress 2nd, 3rd harmonics.


Power Amplifier Design Example

Here is our final simulated performance

 


Load pull method

 We can also empirically determine (in CAD, or with instruments) the load impedance giving the largest saturated P_{out} . We then use this impedance for our PA design



Load pull method

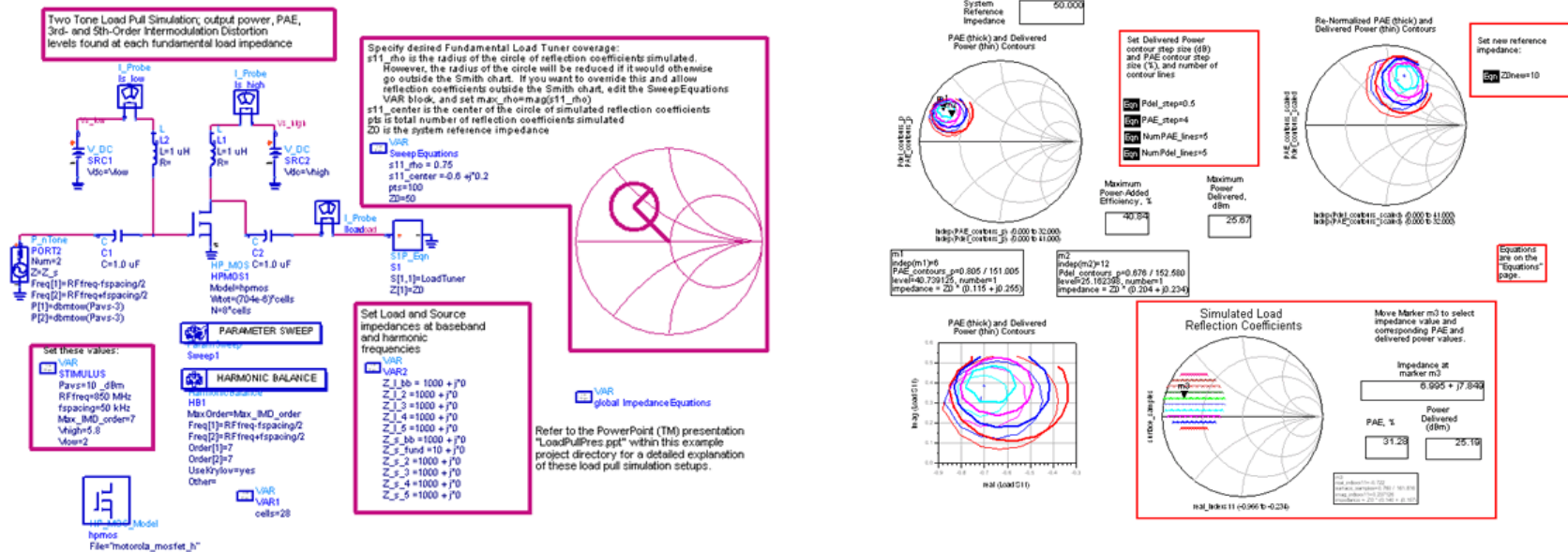We can also empirically determine (in CAD, or with instruments) the load impedance giving the largest saturated Pout. We then use this impedance for our PA design



Keysight ADS has pre - configured test benches to do this.

I suspect that other CAD packages do, too.

I prefer the Cripps method.

The power-combiner problem

Output power : $P_{out} = (V_{max} - V_{min}) I_{max} / 8$

Necessary load impedance : $R_L = (V_{max} - V_{min}) / I_{max}$

So, output power $P_{out} = (V_{max} - V_{min})^2 / 8R_L$

High - frequency transistors have low V_{max} .

High P_{out} requires very low R_L ,

or

High P_{out} requires * power - combining *

Minimum load impedance

Transmission lines have some minimum $Z_{line,min}$.

See ECE145A notes :


width, lateral modes, junction parasitics, high skin loss.

Impedance transformation permits $Z_{load} < Z_{line,min}$


But high $Z_{load} : Z_{line,min}$ ratios increase the line's VSWR

→ increased line losses.

 Z_{load} much below 10Ω will incur high losses



Parallel Power-Combining

 


Output power: $P_{OUT} = N \times V \times I$

Parallel connection increases P_{OUT} ✓

Load Impedance: $Z_{OPT} = V / (N \times I)$

Parallel connection decreases Z_{opt} ✗

 

High $P_{OUT} \rightarrow$ Low Z_{opt}

Needs impedance transformation:


lumped lines, Wilkinson, ...

High insertion loss ✗

Small bandwidth ✗

Large die area ✗

Wilkinson Power-Combiner

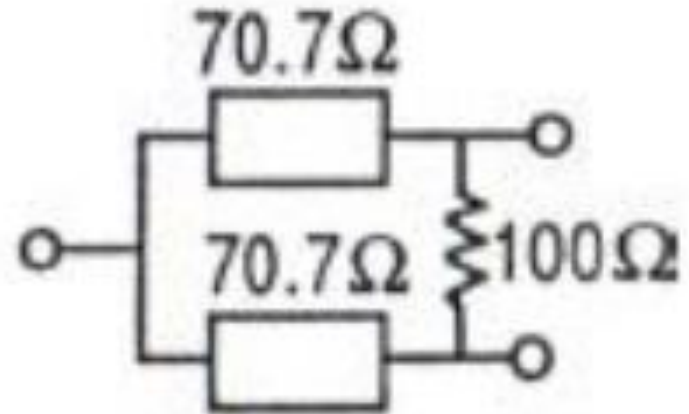

Lines are one quarter - wavelength


Does provide 2 : 1 combining, 50 Ohm ports.

But :

Lines are long : large die area

Lines are long, hence lossy : loss in power, efficiency

Corporate Wilkinson Power-combiner

 


Assume : all these lines are $\sqrt{2} \times 50\Omega$ impedance

Assume : all these lines are quarter - wavelenght.

Then : this is a 3 - stage Wilkinson power - combiner

Then : we have 8 : 1 power - combining

Corporate Wilkinson Power-combiner

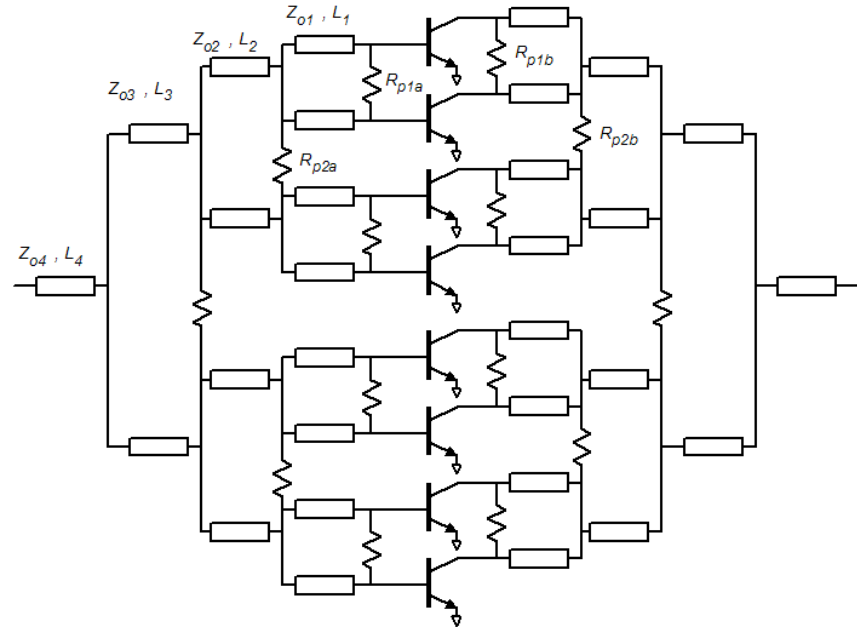



Corporate Wilkinson combiners are common in textbooks.

Corporate Wilkinson combiners are *rare* in ICs.

Why ?

Very long lines. Large die area. High losses

Corporate Power-combiners: Non-Wilkinson

  

Real IC power - combiners look like this.


The structure is corporate.

But, the lines are not 71 Ohms

And, the lines are much shorter than $\lambda_{\text{guide}} / 4$.

Shorter lines : less loss, smaller IC.

Design of Non-Wilkinson Combiners

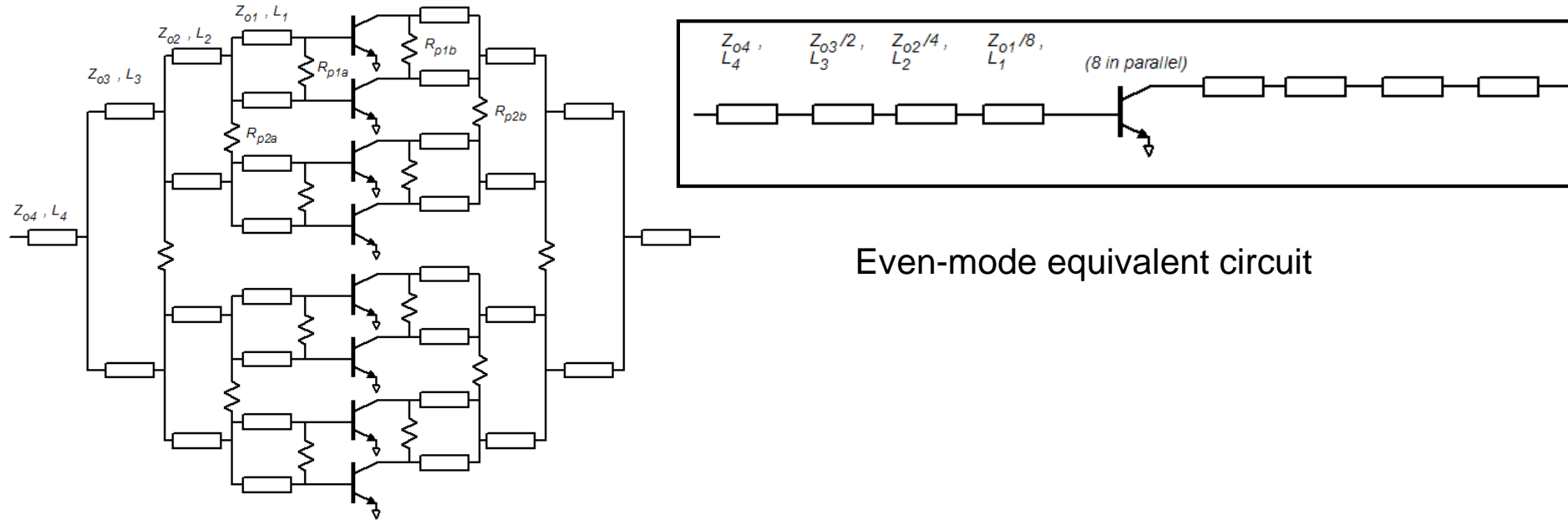

Even-mode equivalent circuit

The equivalent circuit : a multi - section transmission - line transformer.





Shunt elements (inductors, capacitors) can also be added.

Line parameters are adjusted to reach $Z_{l,opt}$ and to match input.

CAD approach :

all similar lines defined by shared variables, simultaneously adjusted

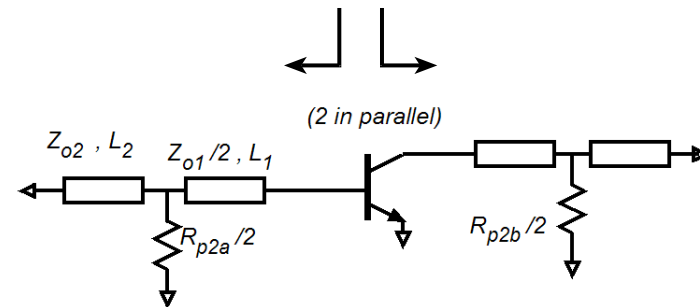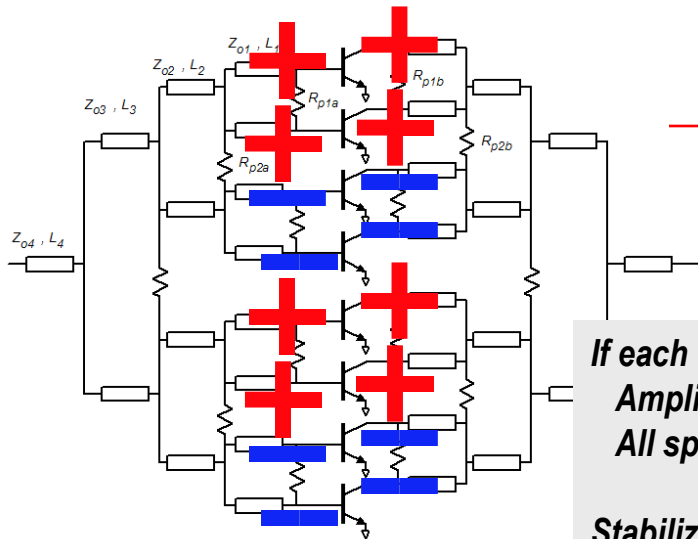 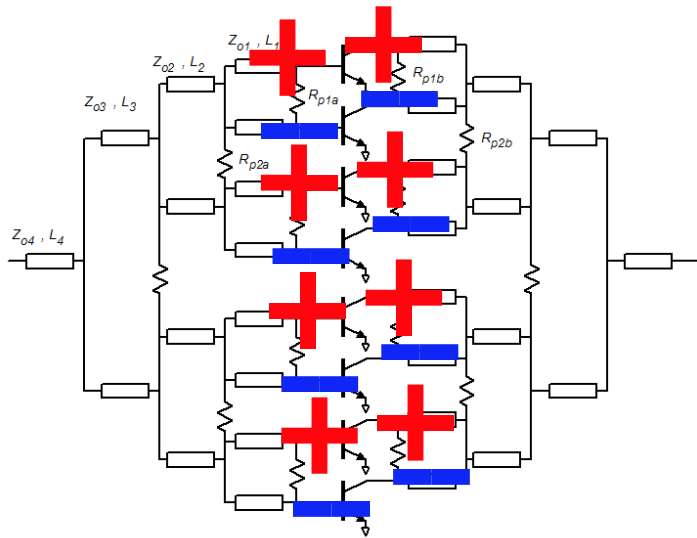Design: Multi-Finger Amplifiers: spatial mode instabilities




If each transistor finger is individually stabilized, high-order modes are stable. Amplifier layout usually does not allow sufficient space for this. All spatial modes must then be stabilized.


**Stabilization method: bridging resistors → parallel loading to higher-order modes
Select so that (Z_S, Z_L) presented to device lie in the stable regions**

etc...


Examples: PAs with corporate combining

 

 34 GHz InP HBT power amplifier - Rockwell




W-band InP HBT power amplifier - UCSB

 



mm-wave InP HBT power amplifier - Rockwell

 220 GHz 180mW Power Amplifier (330 mW design)



  2.3 mm x 2.5 mm


T. Reed, Z. Griffith et al
2013 CSIC symposium




Transformers for impedance transformation

Here the transformer changes
(decreases) the real part
of the load admittance.

 Additional tuning elements used
to adjust $\text{Im}(Y_L)$



 
Transformers have extensive parasitics
and require careful electromagnetic
modeling




Transformers for power combining

Here the transformers combine power from 2 cells.


Each cell sees $1/2$ the load impedance

 

 The transformer primary can be segmented to extend to N - way combining



Parallel Power-Combining

 


Output power: $P_{OUT} = N \times V \times I$

Parallel connection increases P_{OUT} ✓

Load Impedance: $Z_{OPT} = V / (N \times I)$

Parallel connection decreases Z_{opt} ✗

 

High $P_{OUT} \rightarrow$ Low Z_{opt}

Needs impedance transformation:


lumped lines, Wilkinson, ...

High insertion loss ✗

Small bandwidth ✗

Large die area ✗

Series Power-Combining & Stacks

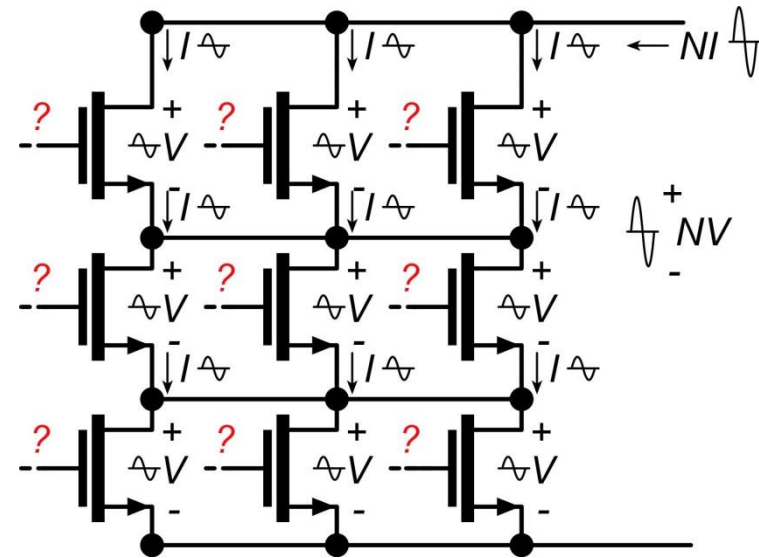

Parallel connections: $I_{out} = N \times I$

Series connections: $V_{out} = N \times V$


Output power: $P_{out} = N^2 \times V \times I$

Load impedance: $Z_{opt} = V/I$

Small or zero power-combining losses

Small die area

How do we drive the gates ?

 

Local voltage feedback:

drives gates, sets voltage distribution


Design challenge:

need uniform RF voltage distribution

need ~unity RF current gain per element


...needed for simultaneous compression of all FETs.

3-conductor transmission Lines

 

Two separate transmission lines (m_3 - m_2 , m_2 - m_1)
 → E, H fields between m_3 and m_1 perfectly shielded

 Standard $\lambda/4$ Baluns: Series Combining




Balun combiner:
voltages add

2:1 series connection

each source sees 25Ω

→ double I_{\max} for each source

4:1 increased P_{out}

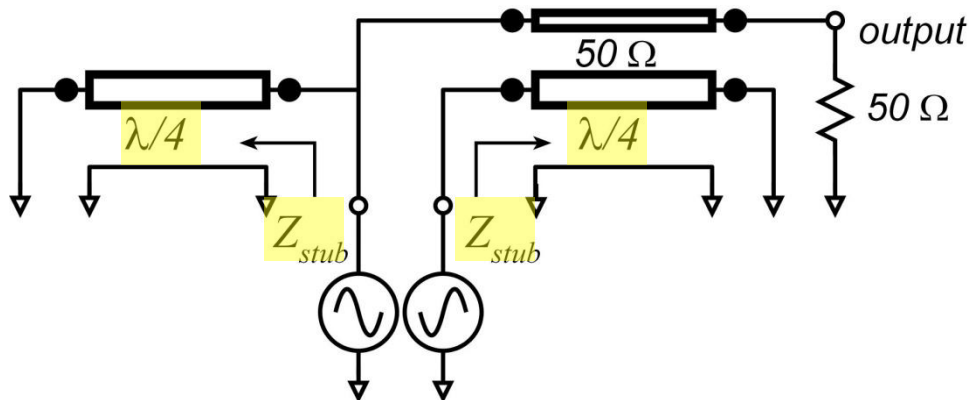

Standard $\lambda/4$ balun :

$\lambda/4$ stub → open circuit




long lines → high losses

long lines → large die


Sub- $\lambda/4$ Baluns for Series Combining

What if balun length is $\ll \lambda/4$?
Stub becomes inductive

 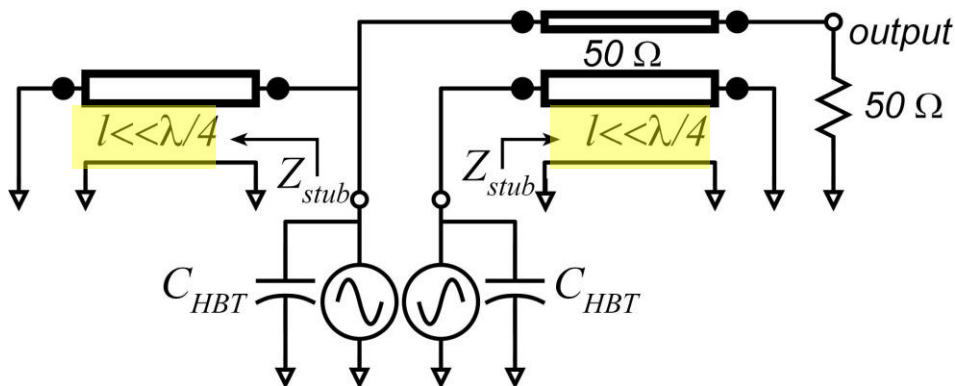 Sub- $\lambda/4$ balun :
stub \rightarrow inductive
tunes transistor C_{out}
short lines \rightarrow low losses
short lines \rightarrow small die



 Sub- $\lambda/4$ Baluns for **Series** Combining



2:1 baluns:


2:1 series connection

Each device loaded by 25Ω
 \rightarrow HBTs are 2:1 larger
 than needed for 50Ω load.
 \rightarrow 4:1 increased P_{out} .

Sub $\lambda/4$ balun: inductive stub
 balun inductive stub
 tunes HBT C_{out} .

Similar network on input.

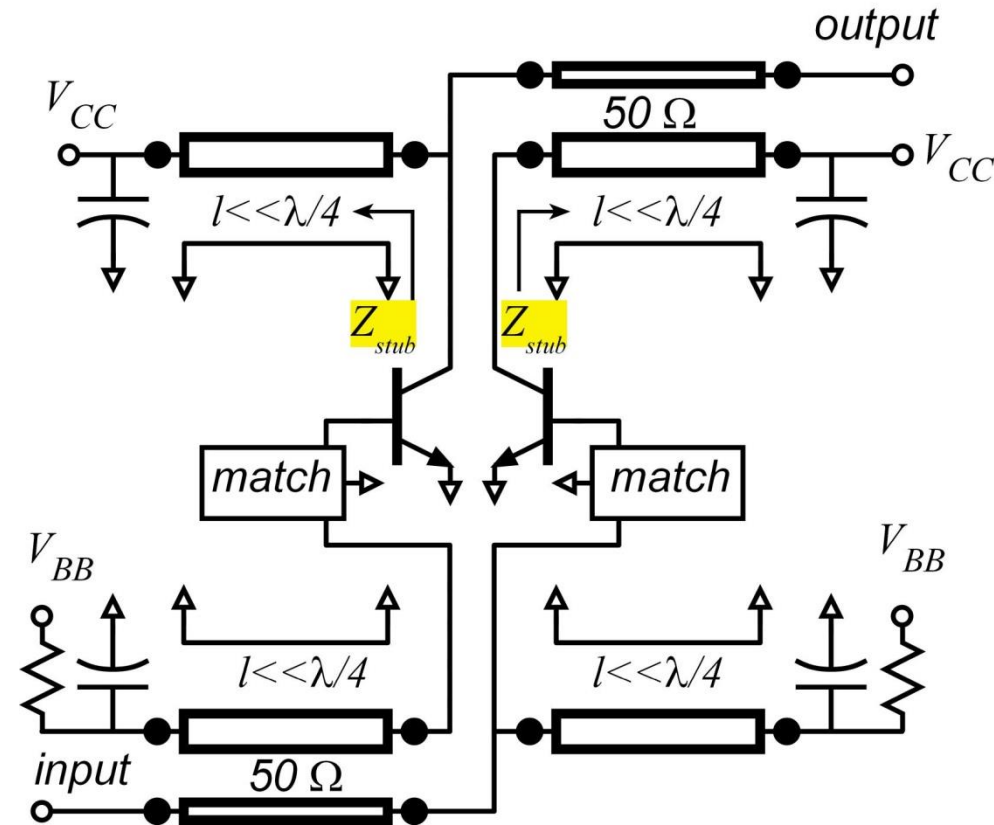Sub- $\lambda/4$ Balun Series-Combiner: Design



Each HBT loaded by 25Ω

HBT junction area selected

so that $I_{\max} = V_{\max} / 25\Omega$

Each HBT has some C_{out} .

Stub length picked so that





$Z_{\text{stub}} = -1/j\omega C_{\text{out}} \rightarrow$ tunes HBT

$$P_{\text{out}} = 4 \times \left(\frac{V_{\text{max}}^2}{8 \cdot 50\Omega} \right)$$

4:1 more power

than without combiner.

Baluns in Real ICs

    



1) M_1 as a GND

2) Slot-type transmission lines (M_1 - M_2), AC short (2 pF MIM)

3) Microstrip line (M_2 - M_3), E-field shielding NOT negligible


4) Sidewalls between M_3 - M_1 (Faraday cages), $\lambda/16$ length

PA Designs Using 2:1 Balun

 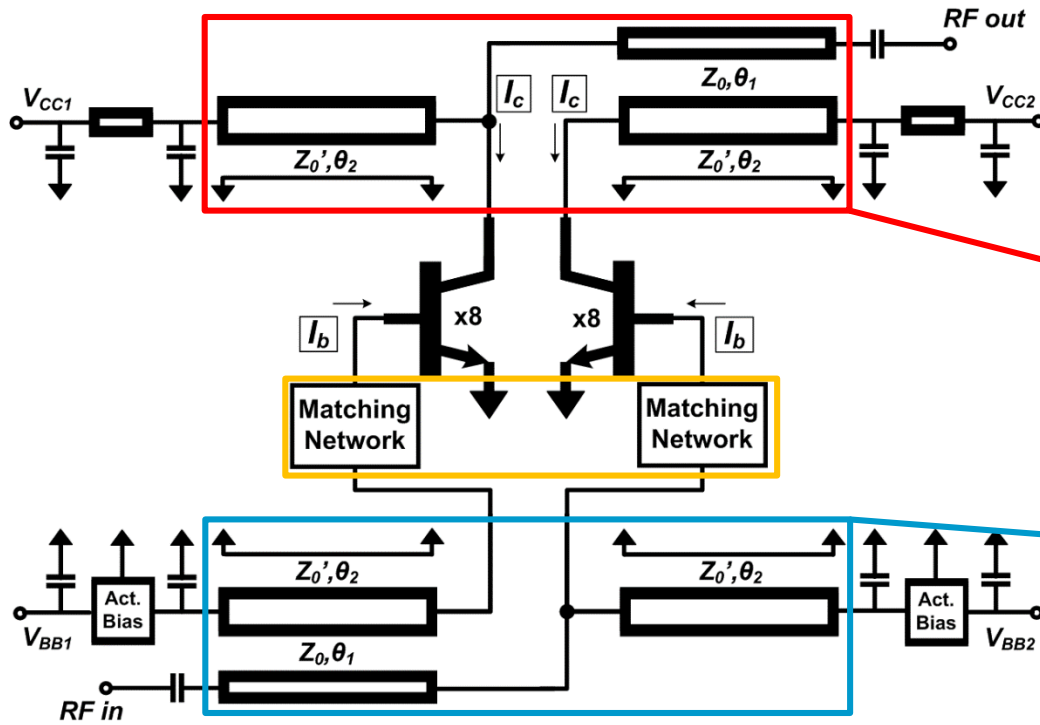

16:1 PA Using 4:1 Baluns

4:1 series-connected power-combining

 

Each HBT loaded by 12.5Ω
 HBT junction area selected
 so that $I_{max} = V_{max} / 12.5\Omega$

$$P_{out} = 16 \times \left(\frac{V_{max}^2}{8 \cdot 50\Omega} \right)$$

Each HBT has some C_{OUT}
 Stub length picked so that
 $Z_{stub} = -1/j\omega C_{out} \rightarrow$ tunes HBT



16:1 more power
 than without combiner.

PA IC Schematic (2-stages)

2-stage PA using 2:1 and 4:1 baluns


1st stage

2nd stage

 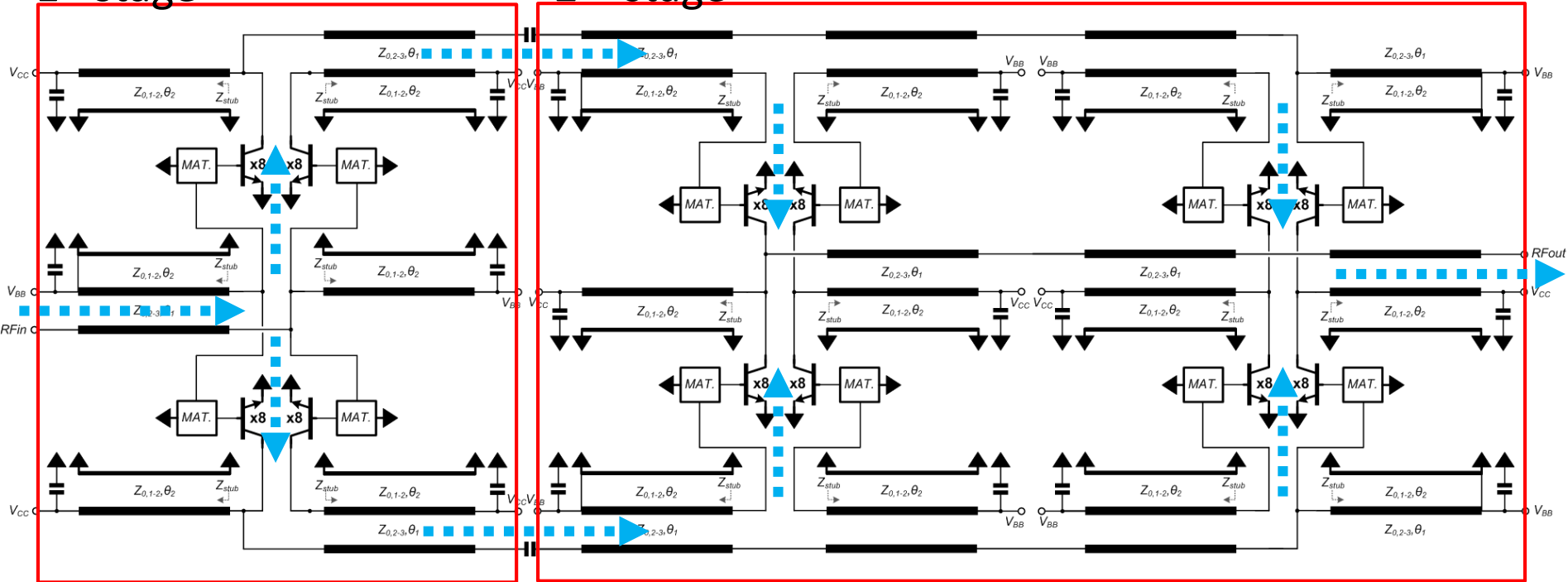

Long lead lines

$$Z_{load} \neq Z'_{load}$$

 

PA IC Die Image (2-stages)

IC Size: 1.08 x 0.98 mm²

