

# ***ECE145a / 218a: Notes Set 5 device models & device characteristics:***

***Mark Rodwell***

***University of California, Santa Barbara***

rodwell@ece.ucsb.edu 805-893-3244, 805-893-3262 fax

# Content:

---

Bipolar Transistor Models





MOSFET Models

HEMT(JFET) models



Cutoff frequencies.

# **Active Devices: Bipolar Transistors**

# HBT Physical Structure

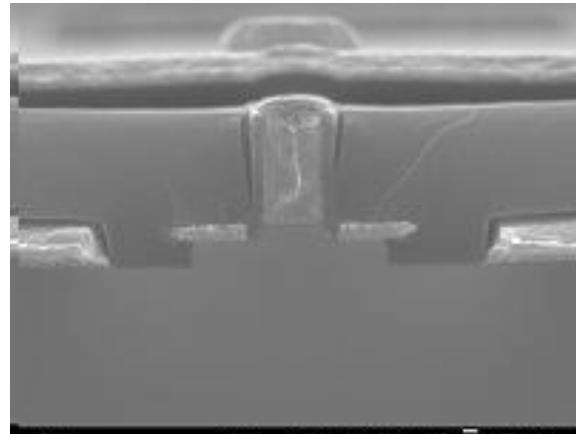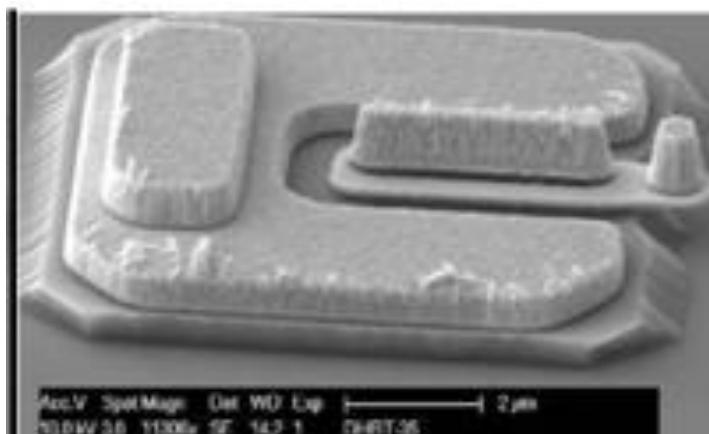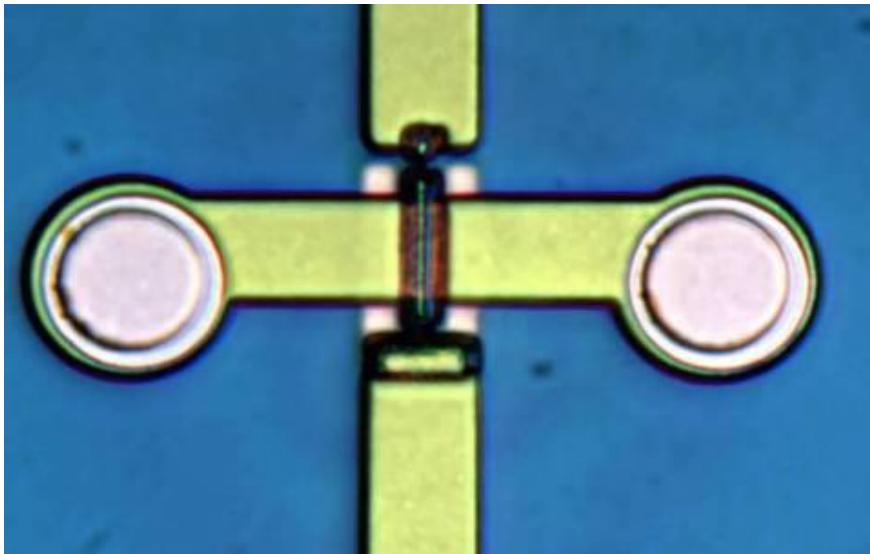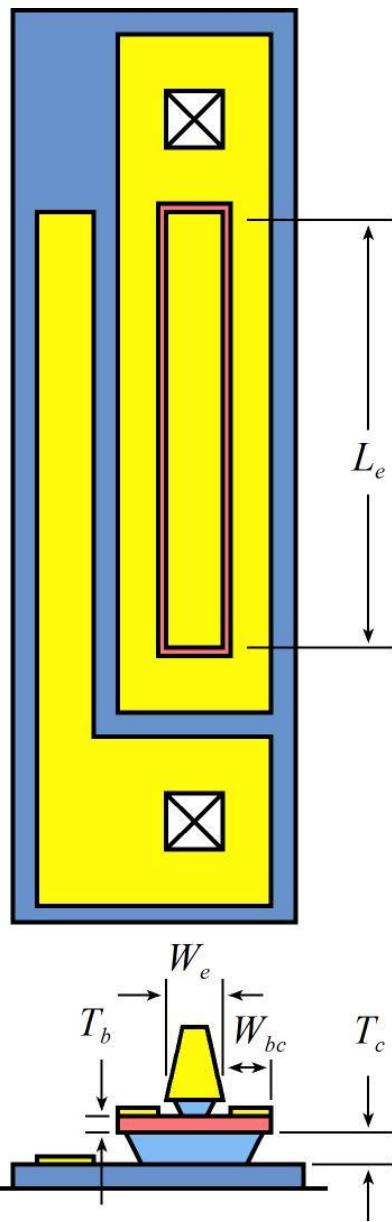

# Increasing total emitter area

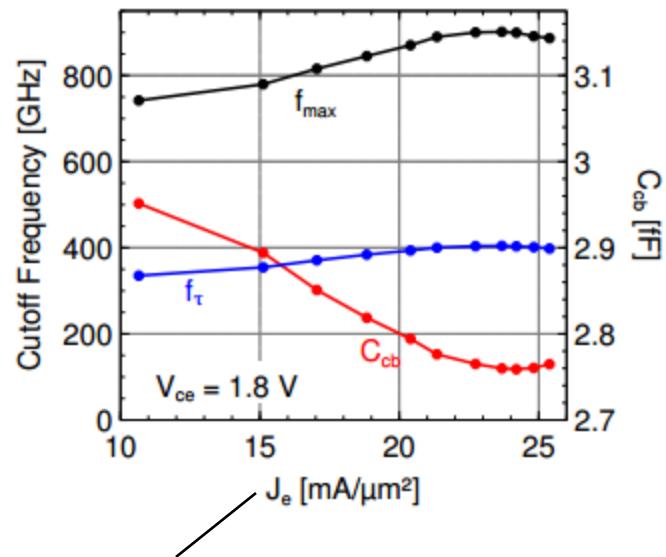
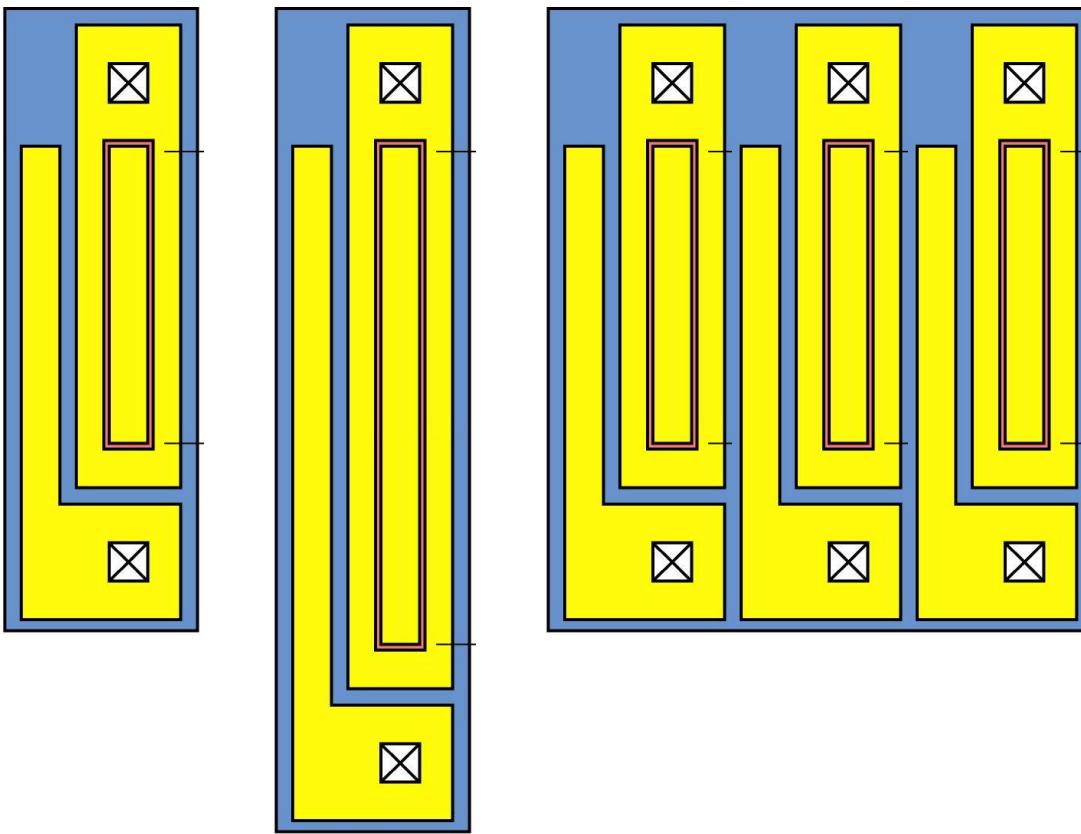


$$J_E = I_E / (\text{total emitter area})$$

Increasing the emitter area (increasing  $L_E$ , or multiple fingers) increases the maximum current.

Emitter area generally selected to reach peak bandwidth at some specified current.
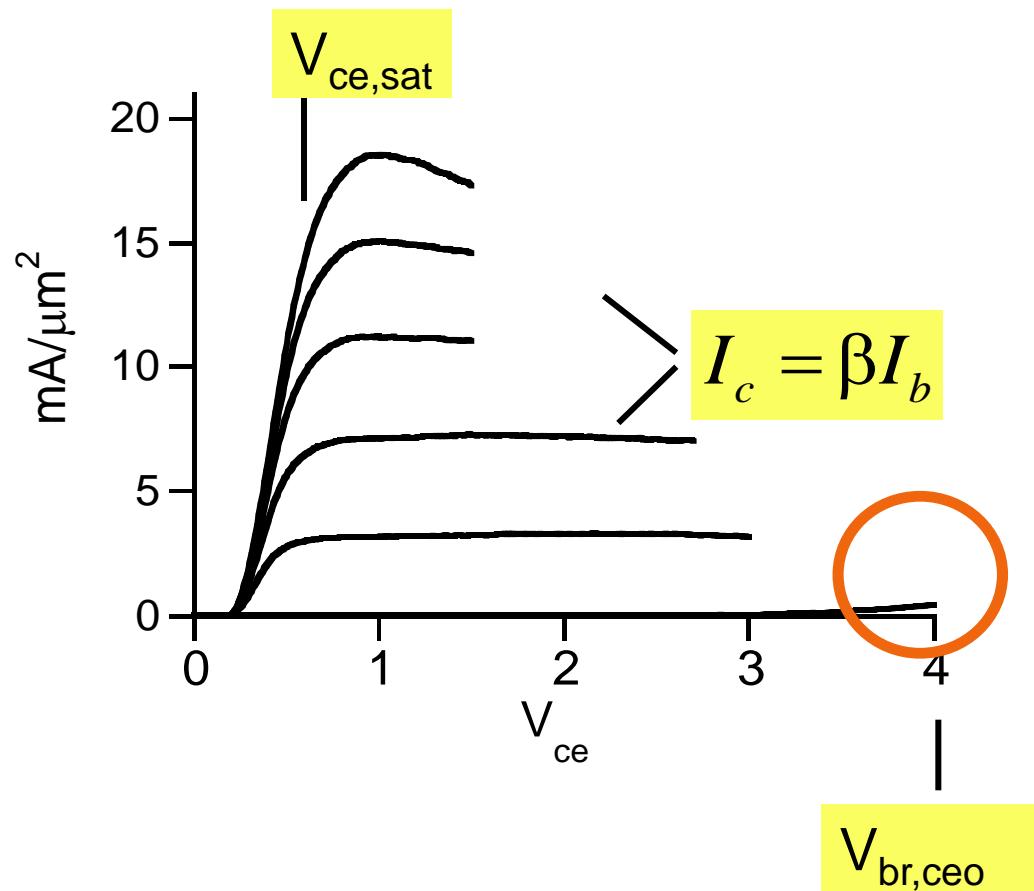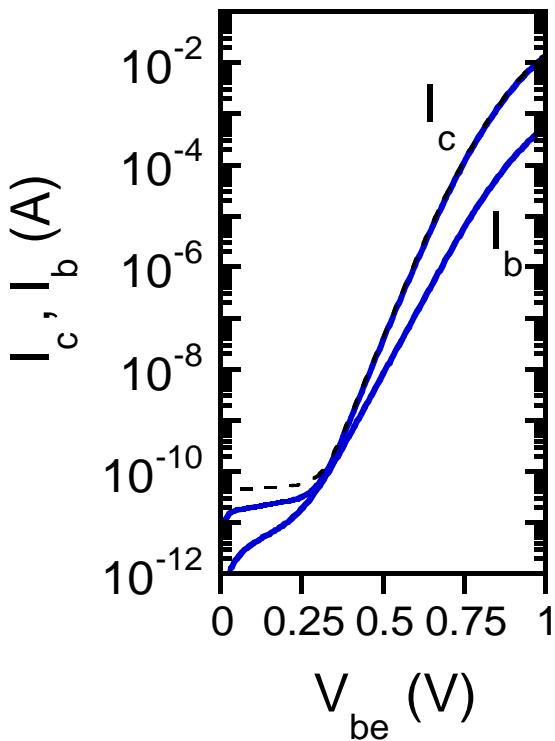
# Bipolar Transistor: DC characteristics: common-emitter



Approximately :

$$I_c = I_s e^{qV_{be}/nkT} \quad \text{and} \quad I_b = I_c / \beta$$

These relationships are approximate,  
and fail at higher current densities

# HBT hybrid-Pi equivalent-circuit model

$$R_{be} = \beta / g_m$$

$$\tau_f = \tau_b + \tau_c$$

$$\tau_f = \tau_{base} + \tau_{collector}$$

$$g_{mo} \equiv \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{(nkT/q)}$$


$$g_m = g_{mo} e^{-j\omega\gamma\tau_c} \quad 0 < \gamma < 1 \text{ (typically } \sim 0.8)$$

$C_{je}, C_{cbi}, C_{cbx}$  : depletion capacitances

$C_{be,diff}$  : diffusion capacitance

$\tau_b, \tau_c$  : carrier transit times in base and collector


$R_b, R_e, R_c$  : parasitic resistances

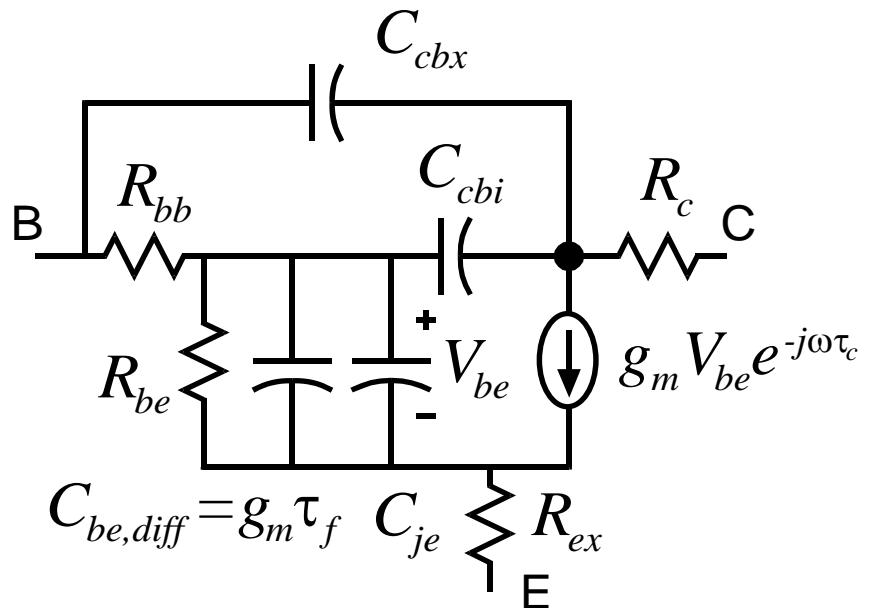

The term  $e^{-j\omega\gamma\tau_c}$ , though often neglected, can be significant in some circuits.

# Bipolar Transistor T-model

---


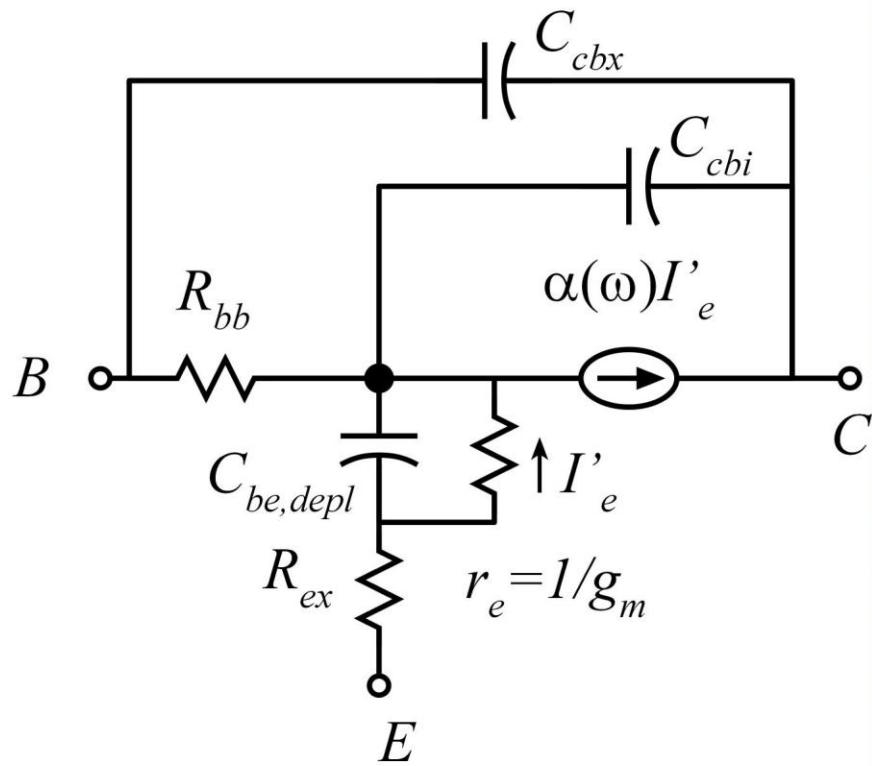


$$\begin{aligned}\alpha(\omega) &\cong \alpha_0 \left( \frac{1}{1 + j\omega\tau_b} \right) \exp(-j\omega\tau_c) \\ &\cong \alpha_0 \left( \frac{1}{1 + j\omega\tau_b} \right) \left( \frac{1}{1 + j\omega\tau_c} \right) \\ &\cong \alpha_0 \left( \frac{1}{1 + j\omega(\tau_b + \tau_c)} \right)\end{aligned}$$

The approximations above, if taken to first order in  $\omega$ , produce the hybrid pi model.

The T model is more convenient for common-base amplifier analysis.
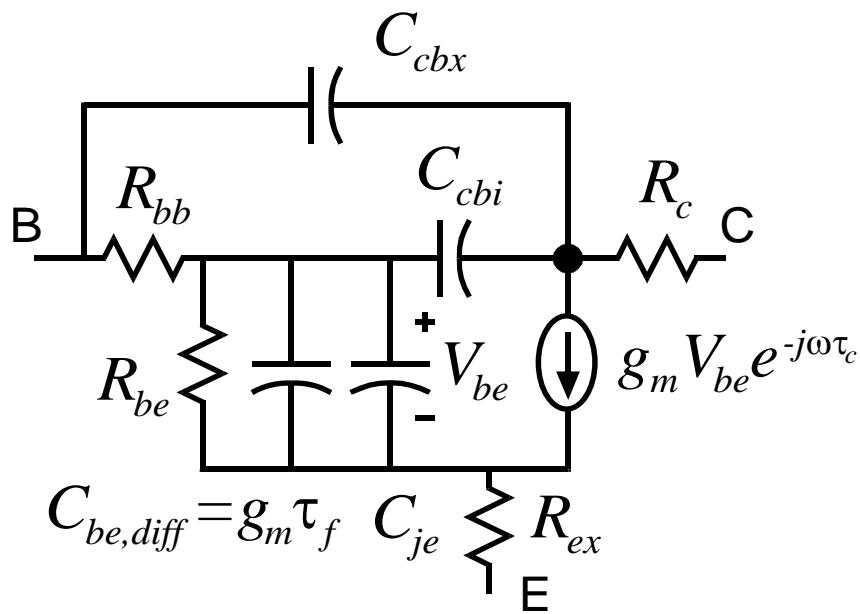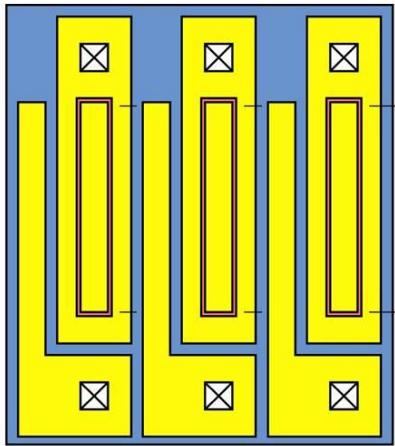
# How model varies as emitter area is increased



Increasing the emitter area by N : 1 → same as wiring N HBTs in parallel.


All capacitances increase N : 1, all resistances decrease 1 : N.

$C_{be}$ ,  $R_{be}$  and  $g_m$  are given by the formulas on the previous pages.



# **Active Devices: Silicon MOSFETs**

# Planar Bulk MOSFET



Cross-Section

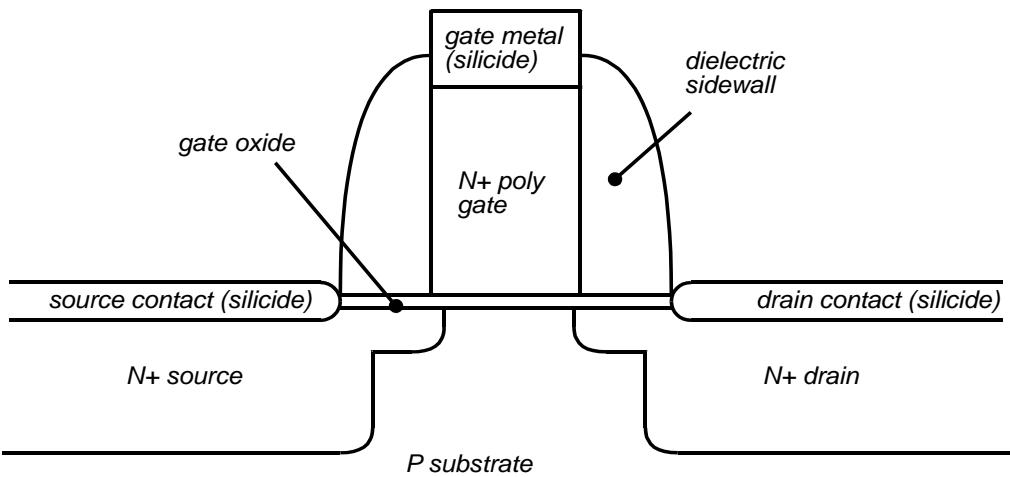

Layout (multi-finger)

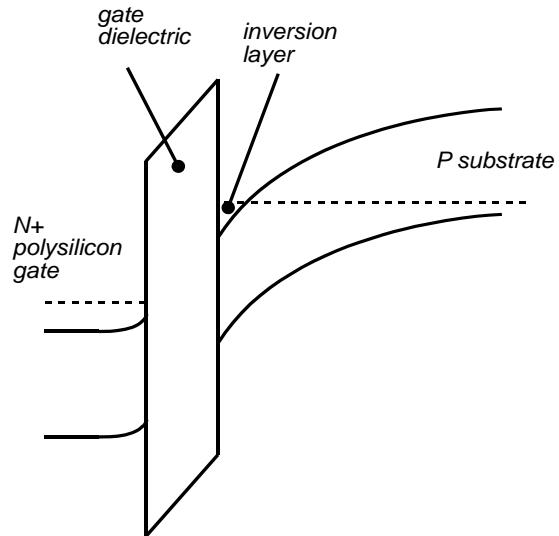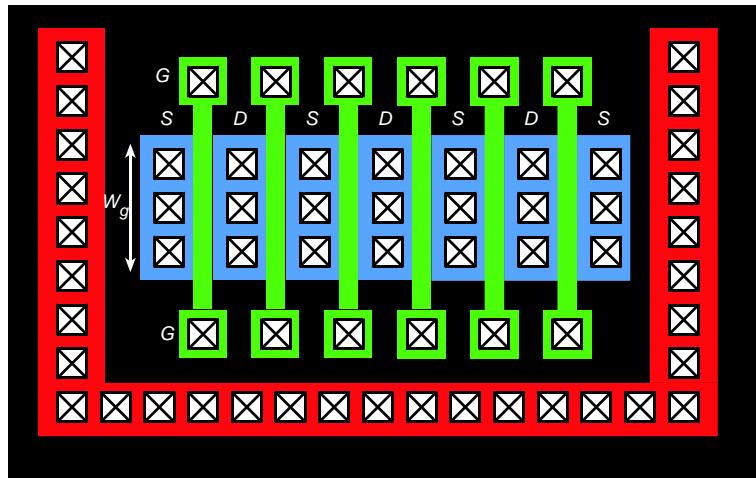

# MOSFET DC Characteristics

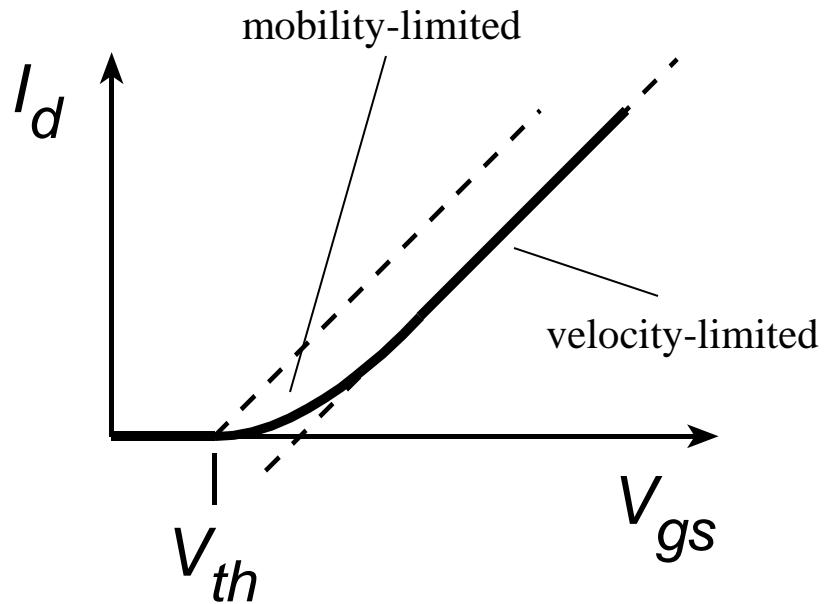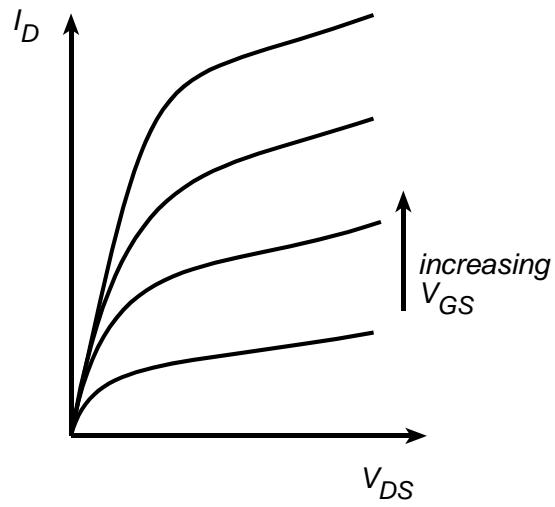

For drain voltages larger than the knee voltage :

mobility – limited current

$$I_{D,\mu} = \mu c_{ox} W_g (V_{gs} - V_{th})^2 / 2 L_g$$

velocity – limited current


$$I_{D,v} = c_{ox} W_g v_{sat} (V_{gs} - V_{th})$$

Generalized Expression


$$\left( \frac{I_D}{I_{D,v}} \right)^2 + \left( \frac{I_D}{I_{D,\mu}} \right) = 1$$
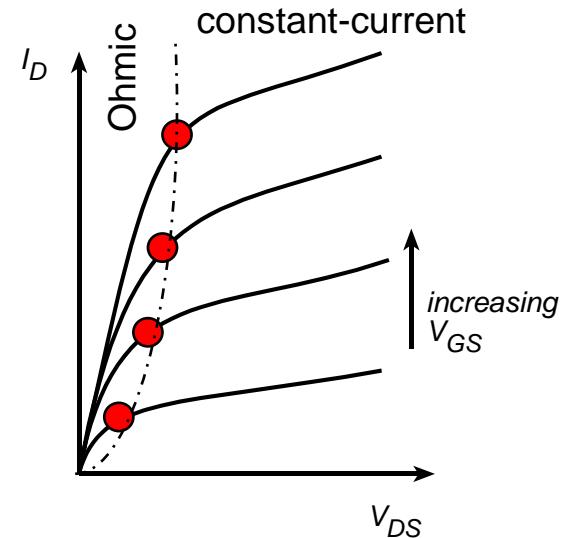
# Knee Voltage: Mobility-Limited Case


The knee voltage defines the boundary between the Ohmic and constant - current regions



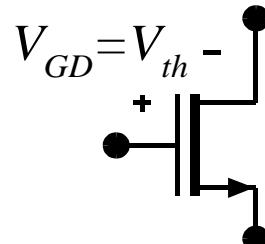In the mobility - limited regime,  
the knee in curve occurs when  
 $V_{dg} = V_{ds} - V_{gs} = -V_{th}$



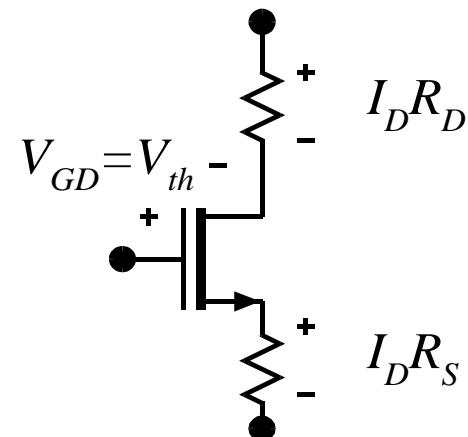
The Knee Voltage is further increased by voltage drops across the parasitic source & drain resistances.



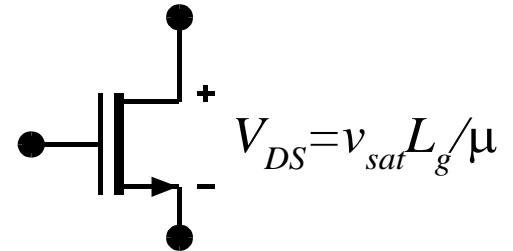
# Knee Voltage: Velocity-Limited Case

---


In the velocity - limited regime, the knee in curve occurs when  $V_{ds} = v_{sat}L_g / \mu$



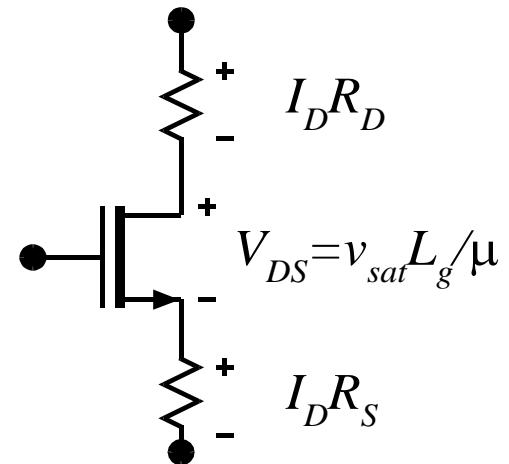Again, the Knee Voltage is further increased by voltage drops across the parasitic source & drain resistances.


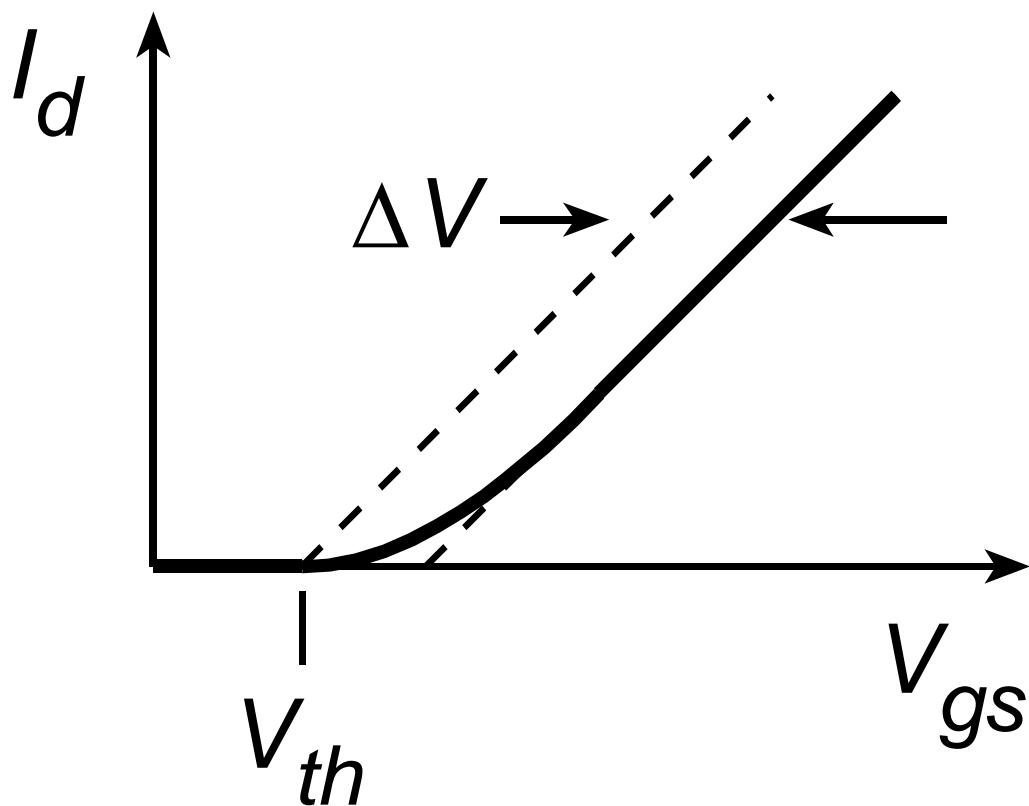
# DC Characteristics---Far Above Threshold



$$I_D \approx c_{ox} W_g v_{sat} (V_{gs} - V_{th} - \Delta V) \text{ for } (V_{gs} - V_{th}) / \Delta V \gg 1$$


$$\text{where } \Delta V = v_{sat} L_g / \mu$$

# MOSFET Transconductance

mobility – limited

$$I_{D,\mu} = \mu c_{ox} W_g (V_{gs} - V_{th})^2 / 2L_g$$

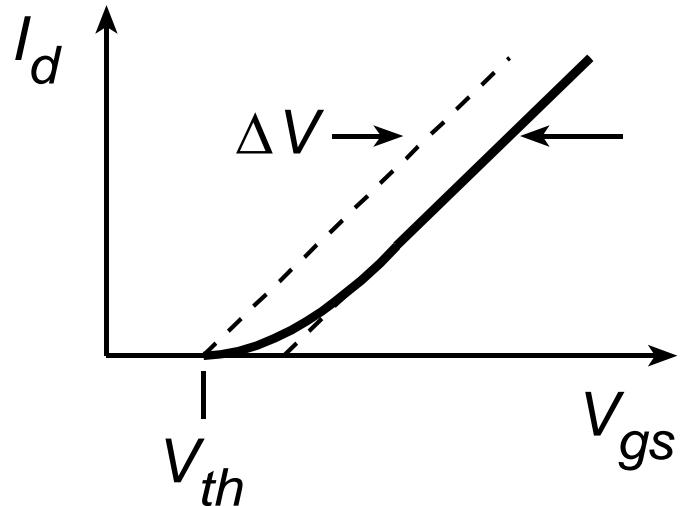
$$\rightarrow g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu c_{ox} W_g (V_{gs} - V_{th}) / L_g$$




velocity – limited

$$I_{D,v} = c_{ox} W_g v_{sat} (V_{gs} - V_{th})$$

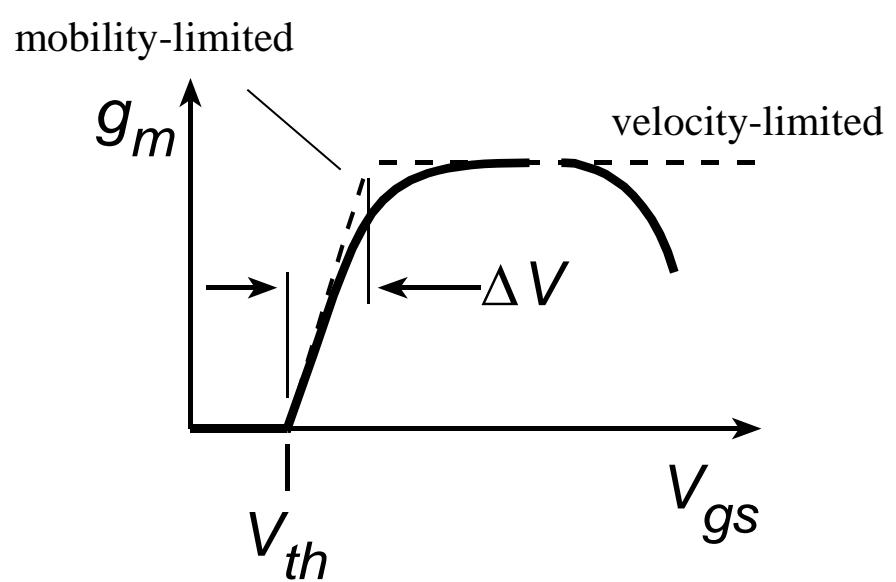
$$\rightarrow g_m = \frac{\partial I_D}{\partial V_{GS}} = c_{ox} W_g v_{sat}$$


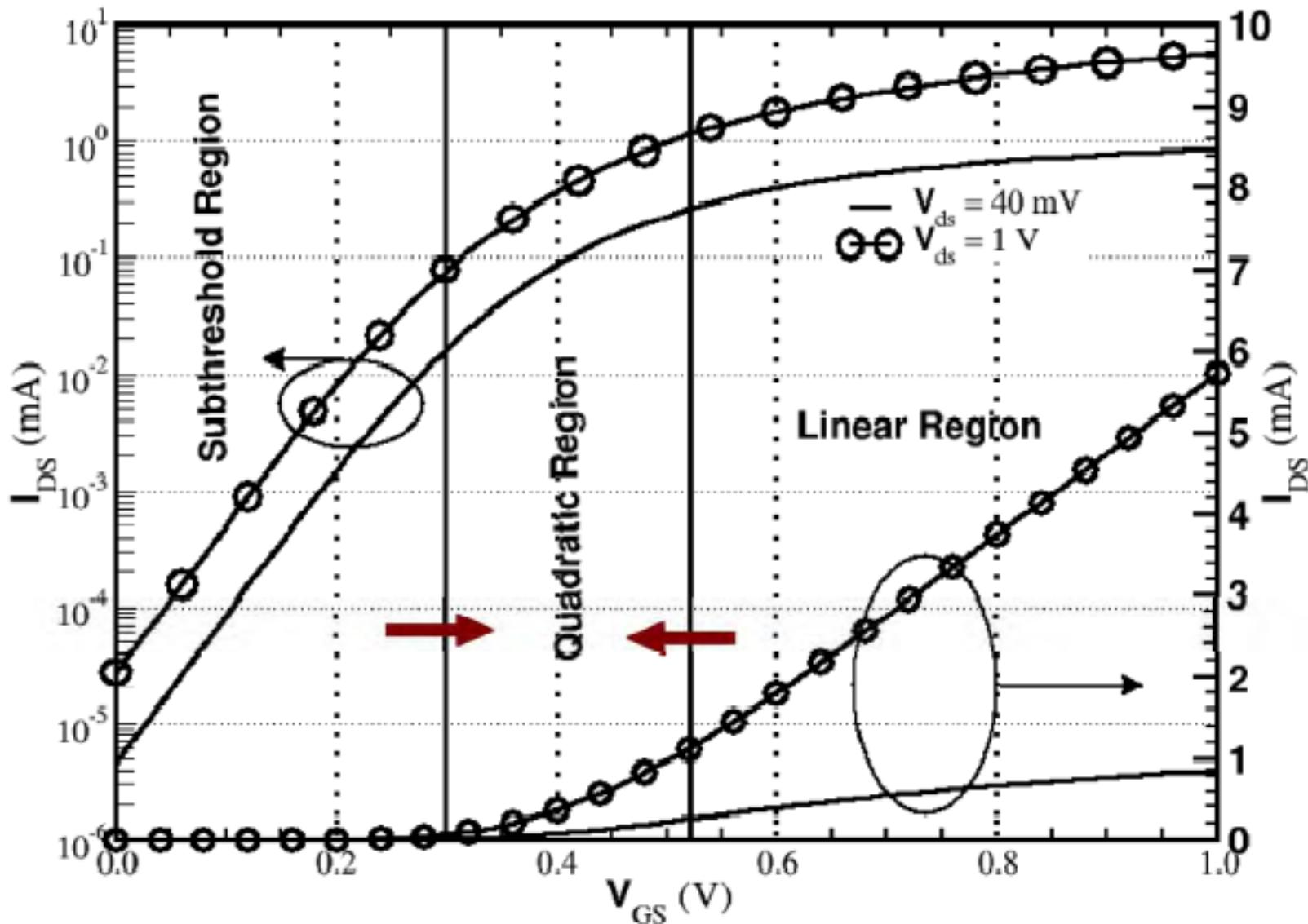
# Linear vs. Square-Law Characteristics: 90 nm



# 90 nm MOSFET DC Characteristics

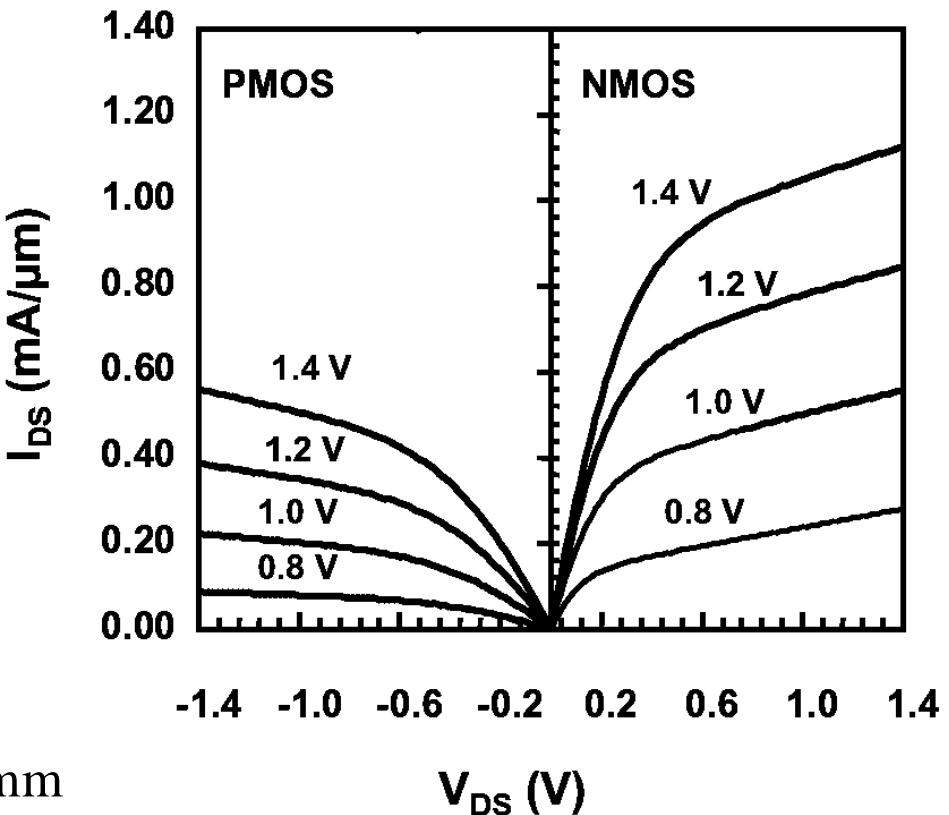

N - channel

$$g_m/W_g = c_{ox}v_{sat} = 1.4 \text{ mS}/\mu\text{m} = 1.4 \text{ S/mm}$$



$$V_{th} = 0.6 \text{ V} \quad 1/\lambda \sim 3 \text{ V}$$

P - channel

$$g_m/W_g = c_{ox}v_{sat} = 0.7 \text{ mS}/\mu\text{m} = 0.7 \text{ S/mm}$$

$$|V_{th}| = 0.6 \text{ V} \quad 1/\lambda \sim 3 \text{ V}$$
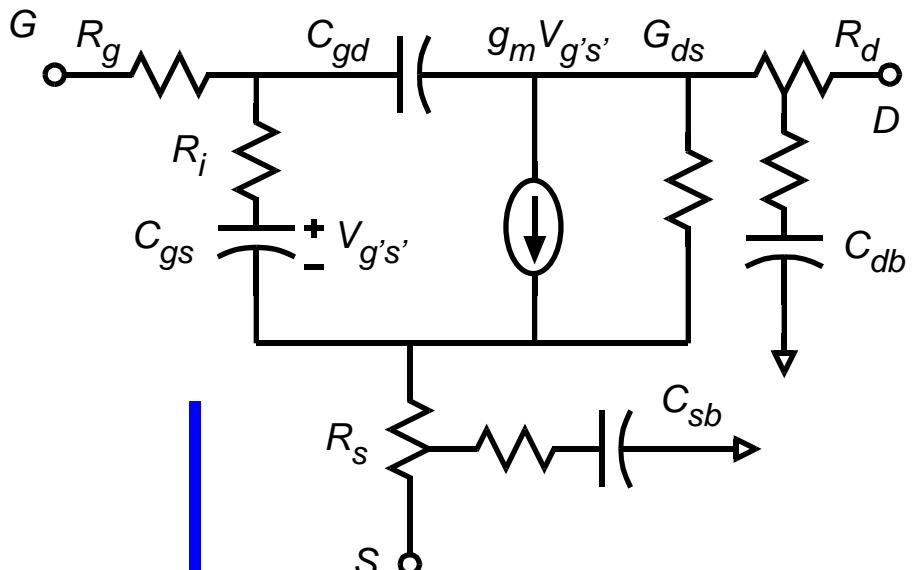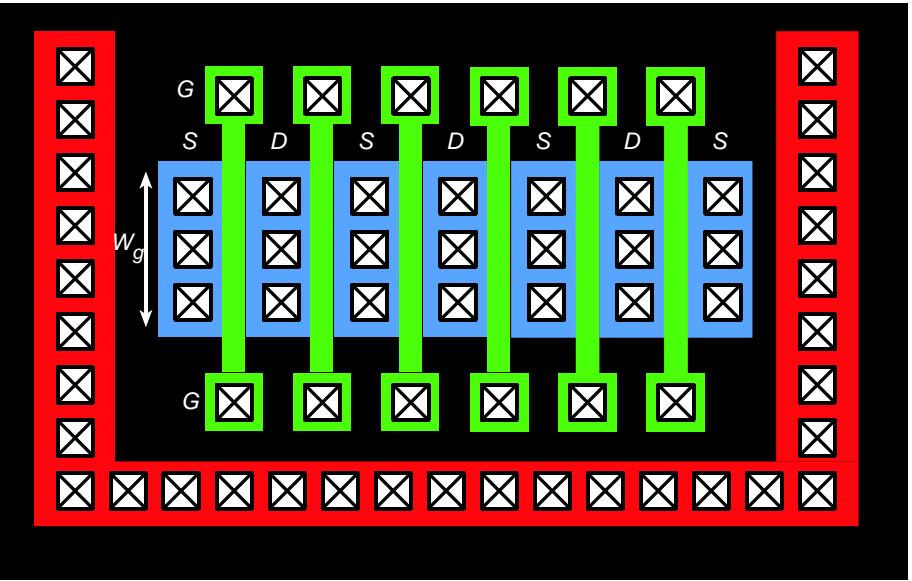
# Device Structure and Model: multi-finger device



$$g_m \equiv \frac{\varepsilon}{T_{eq}} v_{eff} (N W_g) \text{ or } \frac{\varepsilon}{T_{eq}} \mu (N W_g) (V_{gs} - V_{th})$$

$$C_{gd} \equiv k_o W_g$$

$$k_o \approx (0.3 - 0.5) \text{ fF}/\mu\text{m}$$

$$C_{gs} \equiv \frac{\varepsilon}{T_{eq}} L_g (N W_g) + k_o W_g$$

$$G_{ds} \propto N W_g$$

$$R_i \sim 1/g_m$$

$$R_g \sim \frac{\rho_s}{12L_g} \left( \frac{W_g}{N} \right) + \frac{R_{end}}{2N}$$

$$R_d \propto 1/N W_g$$

$$R_s \propto 1/N W_g$$

$$C_{sb} \propto N W_g$$

$$C_{db} \propto N W_g$$

Increase  $f_{max}$  using  
 - short gate fingers  
 - ample substrate contacts

# Oversimplified Model

For rough hand analysis, etc

$$g_{mx} \sim \frac{g_m}{1 + g_m R_s}$$

$$C_{gsx} \sim \frac{C_{gs}}{1 + g_m R_s}$$


$$G_{dsx} \sim \frac{G_{ds}}{1 + g_m R_s}$$

$$R_{in} \sim R_s + R_g + R_i$$

Approximate cutoff frequencies



$$1/2\pi f_\tau \sim C_{gs}/g_m + C_{gd}/g_m + (R_s + R_d)C_{gd}$$
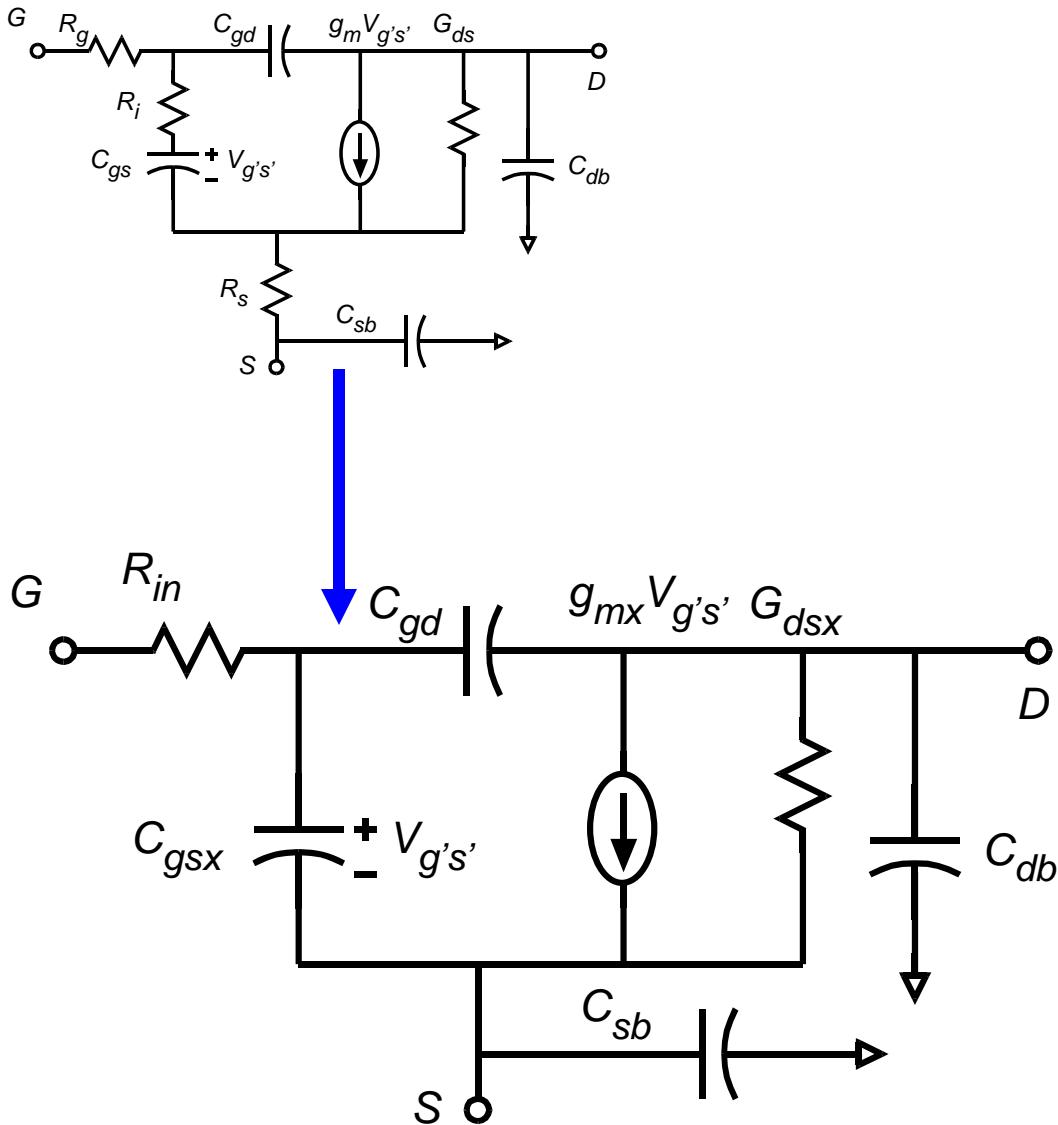
$$f_{\max} \sim \frac{f_\tau}{2\sqrt{(R_s + R_g + R_i)G_{ds} + 2\pi R_g C_{gd}}}$$




# **Active Devices: III-V Field-Effect Transistors**
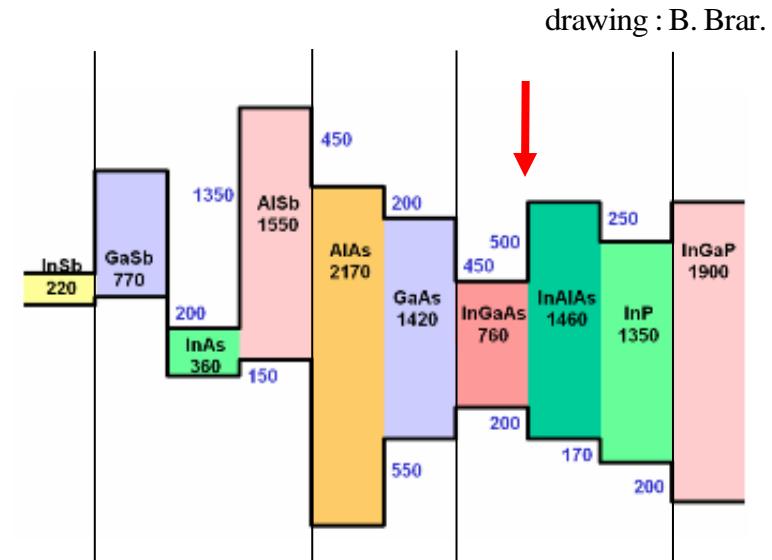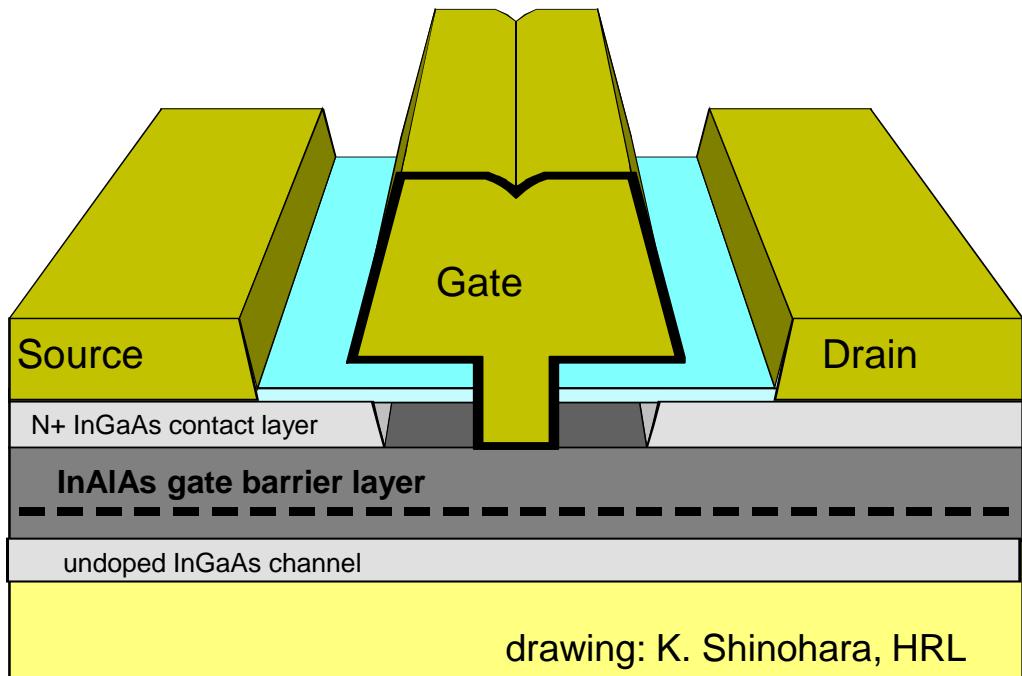
# FET with Heterojunction for Gate Barrier → HEMT



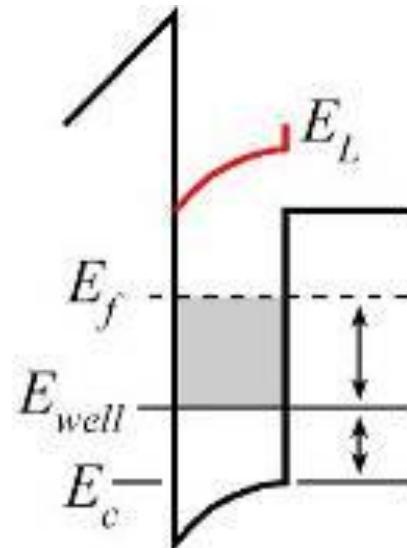
**HEMT:**

FET with semiconductor heterojunction  
for barrier between channel and gate.




# HEMTs: Typical interdigitated structure

---

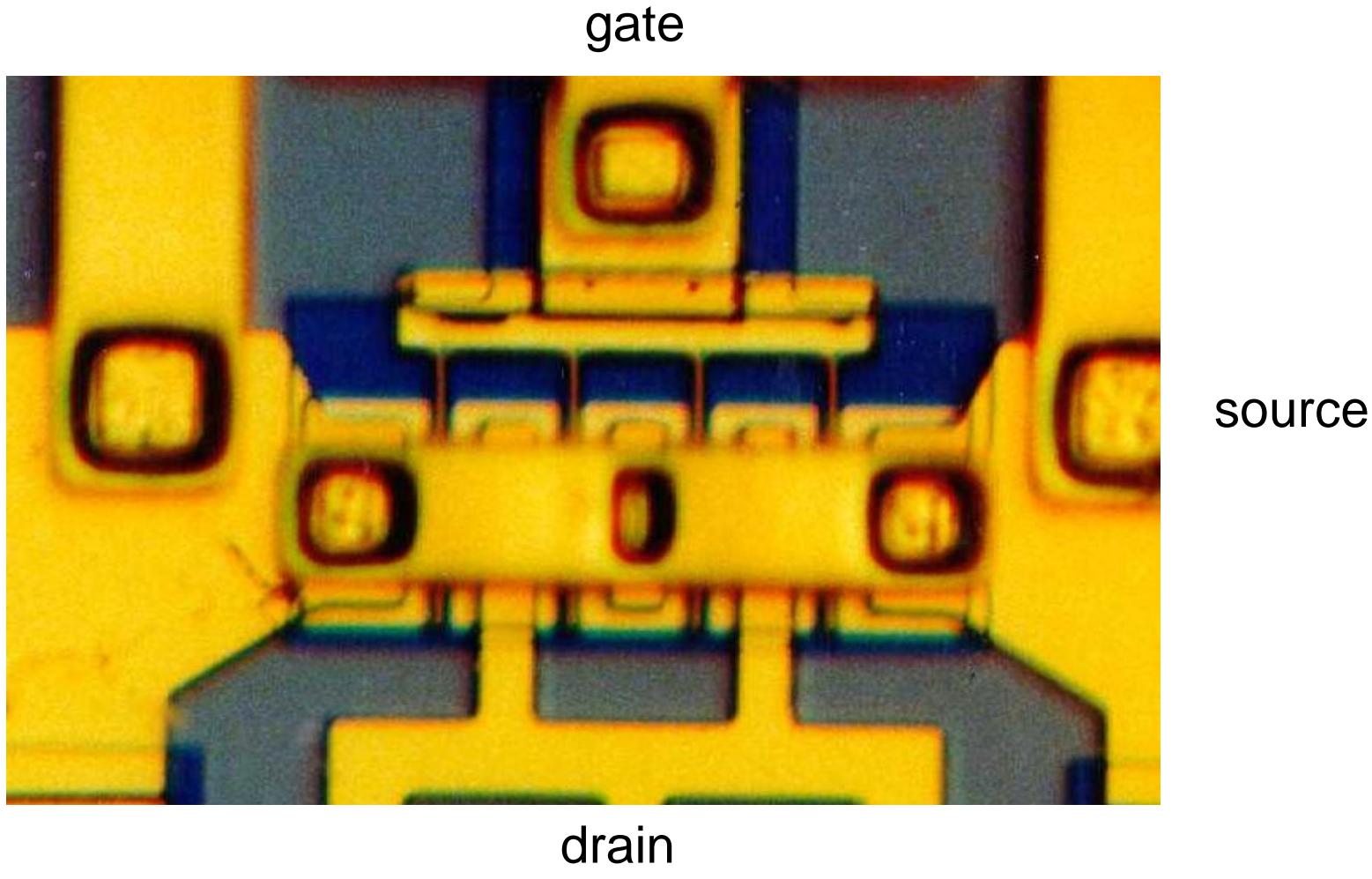

Note multiple gate fingers.
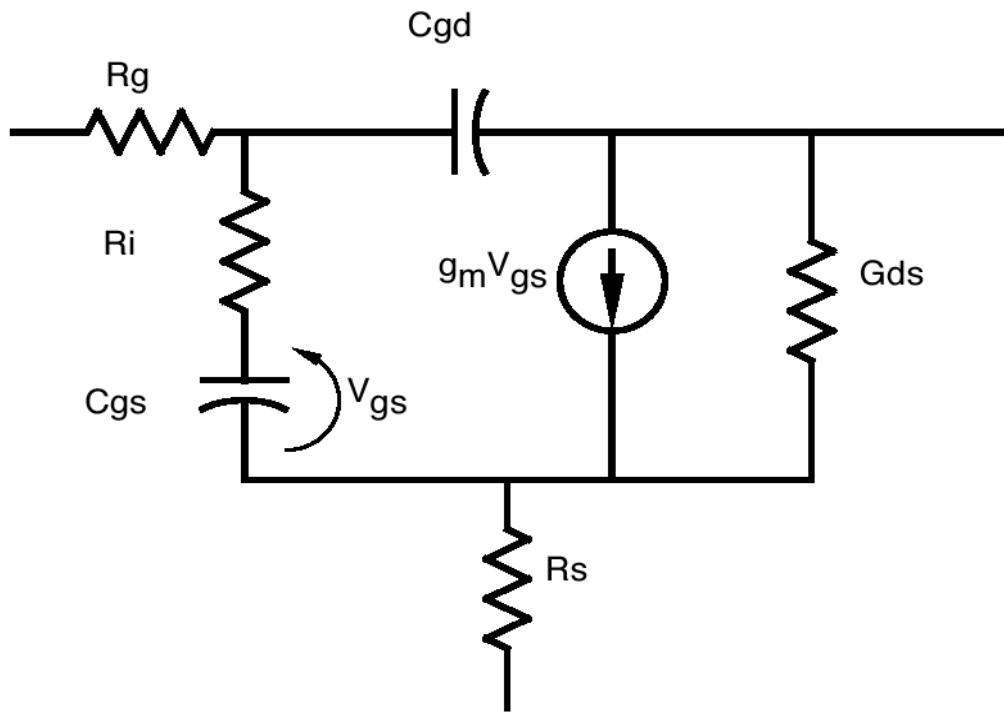
# HEMT: approximate equivalent circuit model





$I_{dss}$ ,  $C_{gs}$ ,  $C_{gd}$ ,  $g_m$ ,  $G_{ds}$  all scale proportionally with gate periphery

$R_i$ ,  $R_s$  scale proportionally with (1/ gate periphery)

$R_g$  scales proportionally to (gate finger length)/(number fingers)

# HEMT DC-IV characteristics

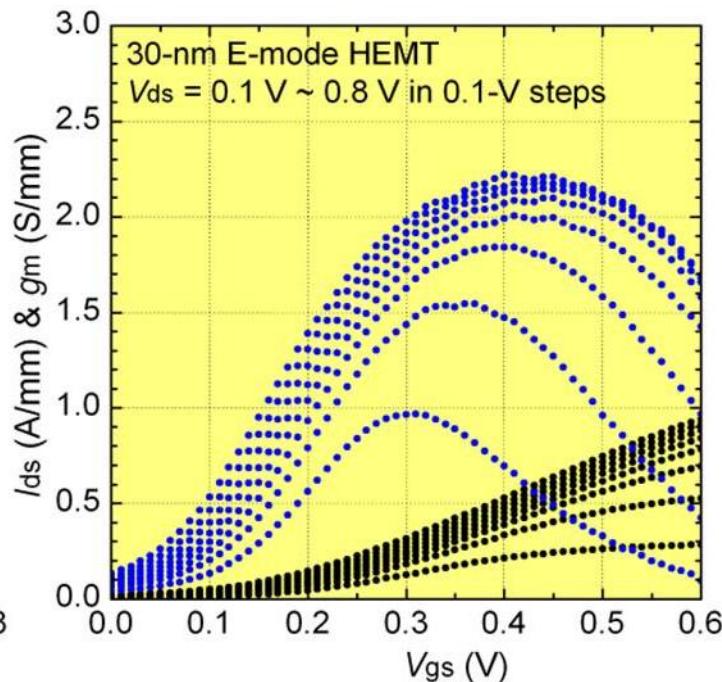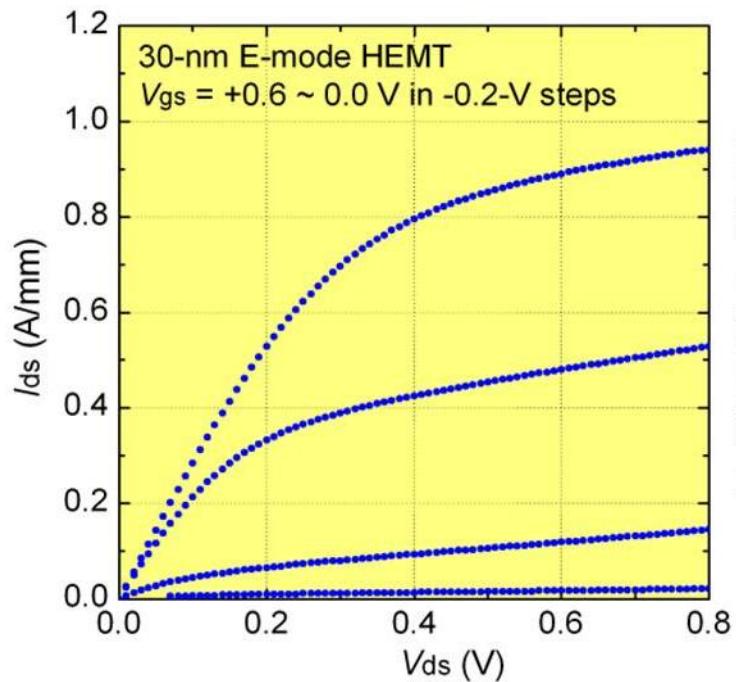

Data : K. Shinohara, Teledyne Scientific

Schottky diode between gate and channel;  
 gate will draw current for  $V_{gs}$  more positive than c.a. 0.6 V

# **Figures of Merit**

# Transistor figures of Merit

---


Transistor small-signal bandwidth is typically stated in terms of the figures of merit  $f_\tau$  and  $f_{\max}$

In order to understand these figures of merit, we must introduce device power gain.


These power gains will be studied in more detail later in the course.

# Definition of short-circuit current gain

---

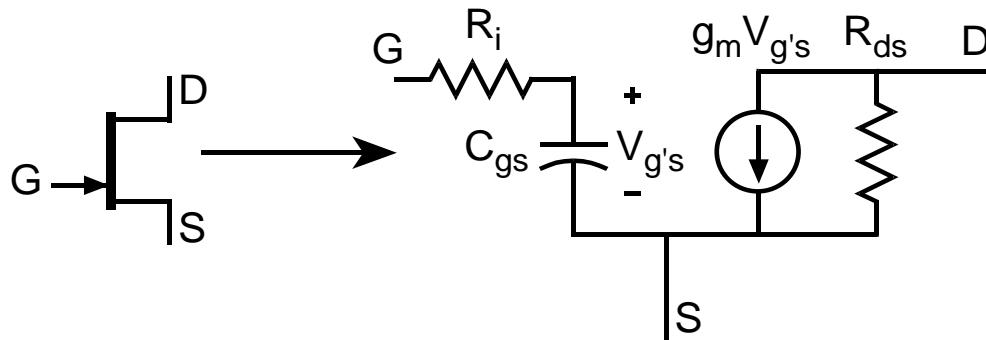


example: FET  
small-signal model

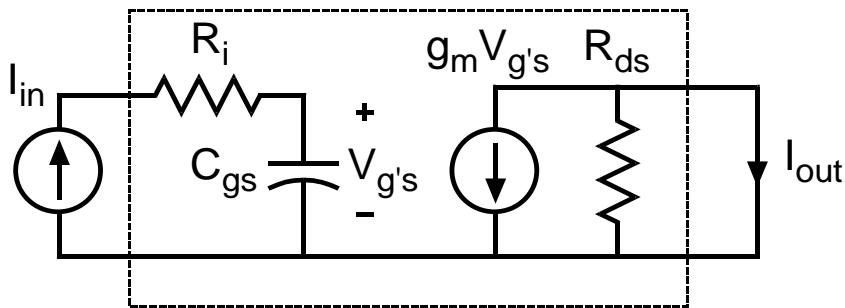

short-circuit current gain:  
drive input with AC current,  
short output, measure  
 $I_{out}/I_{in}$


$$V_{gs} = I_{in} / j\omega C_{gs} \quad \frac{I_{out}}{I_{in}} = \frac{g_m V_{gs}}{I_{in}} = \left( \frac{g_m}{j\omega C_{gs}} \right) = \left( \frac{f_\tau}{jf} \right)$$
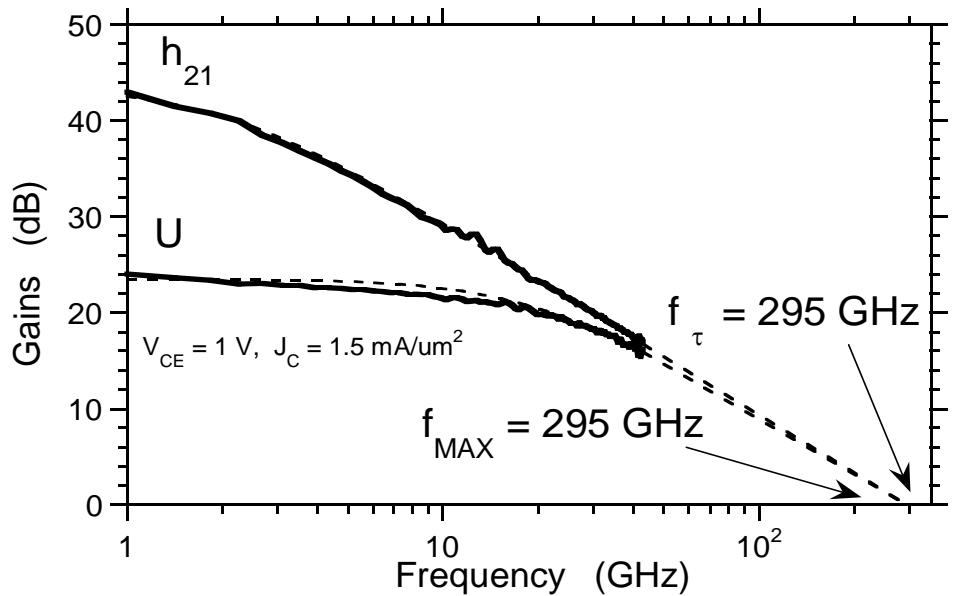
# Variation of H21 with frequency: Bipolar Transistors



H21 is plotted in dB.  
because H21 is a  
current gain:

$$dB(H_{21}) = 20 * \log_{10}(H_{21})$$

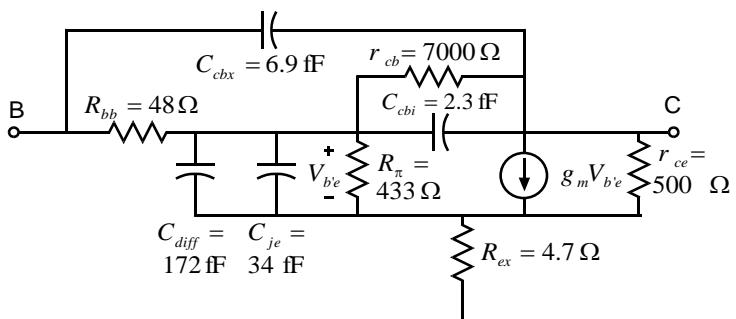

$$g_m = g_{mo} \exp(-j\omega\tau_c)$$



$$C_{diff} = g_{mo} \tau_f$$

$$R_\pi = \beta / g_m$$

Because of effect of  $R_\pi = \beta / g_m$ :

$$H_{21}(f) = \frac{1}{(1/\beta) + (f_\tau / jf)}$$
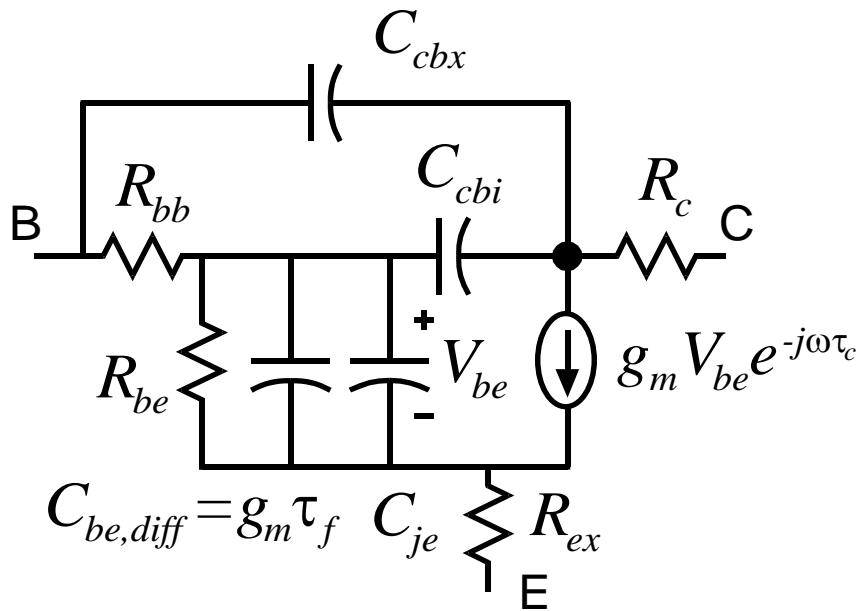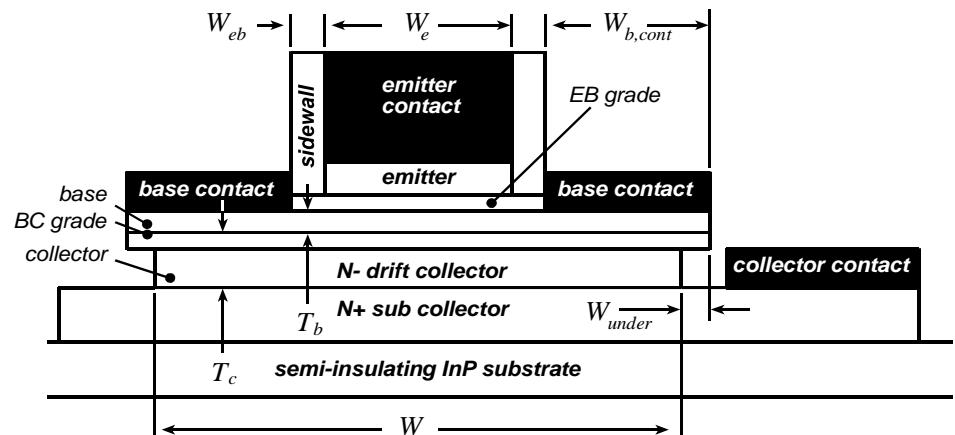
# Current-gain cutoff frequency: Bipolar Transistors





$$\frac{1}{2\pi f_\tau} = \tau_{base} + \tau_{collector} + C_{je} \frac{kT}{qI_E} + C_{bc} \left( \frac{kT}{qI_E} + R_{ex} + R_{coll} \right)$$

$$\tau_{base} \approx T_b^2 / 2D_n \quad \tau_{collector} \approx T_c / 2v_{sat}$$

# Current-gain cutoff frequency: Field-Effect Transistors


---

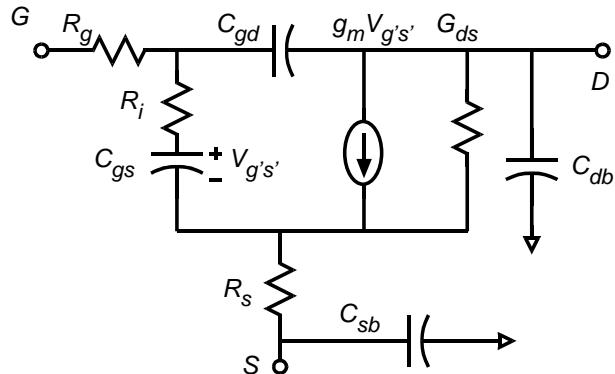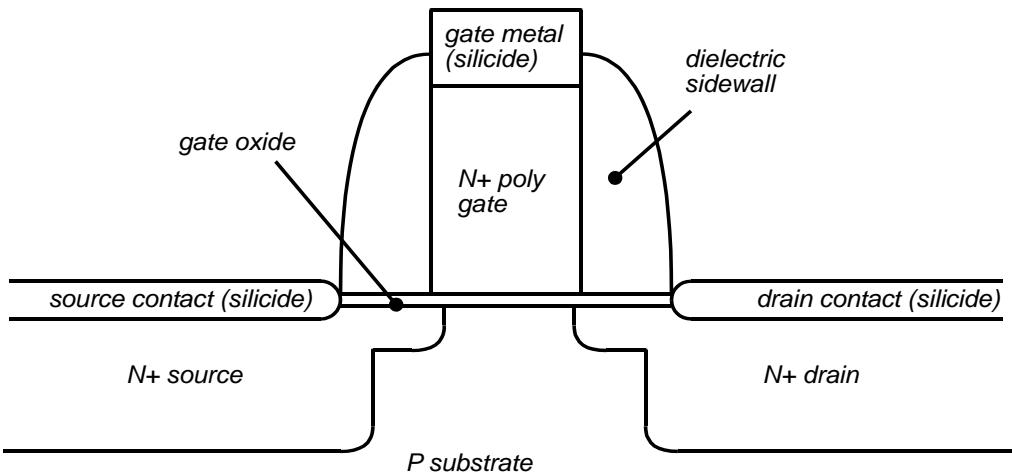

$$f_\tau \cong \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

# Maximum Power Transfer Theorem

---

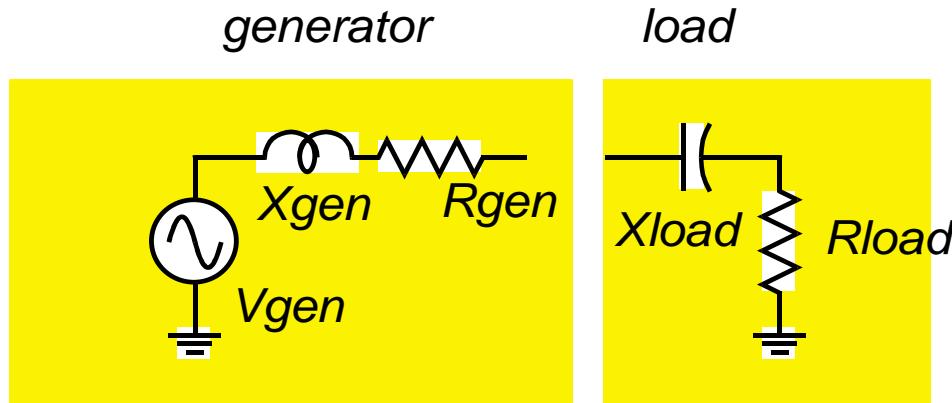

Maximum power is transferred from generator to load if

$$X_{load} = -X_{gen} \quad \text{and} \quad R_{load} = R_{gen}$$


this is called \*\*\*conjugate impedance matching\*\*\*

The power delivered, called the available generator power is

$$P_{avg} = \frac{V_{gen,(RMS)}^2}{4R_{gen}}$$

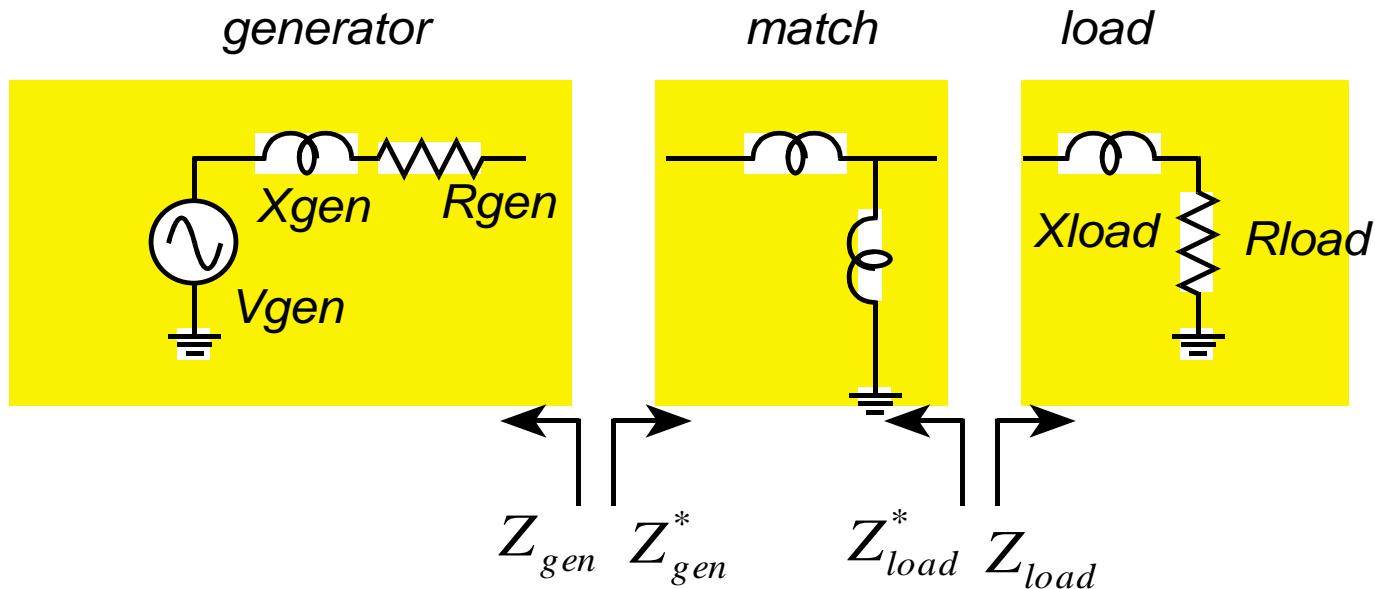
# Impedance Matching

Maximum power transfer can be obtained by adding a \*\*\*lossless\*\*\* (no resistances) impedance matching network between the generator and the load:



# Maximum Available Power Gain (if it exists)


---

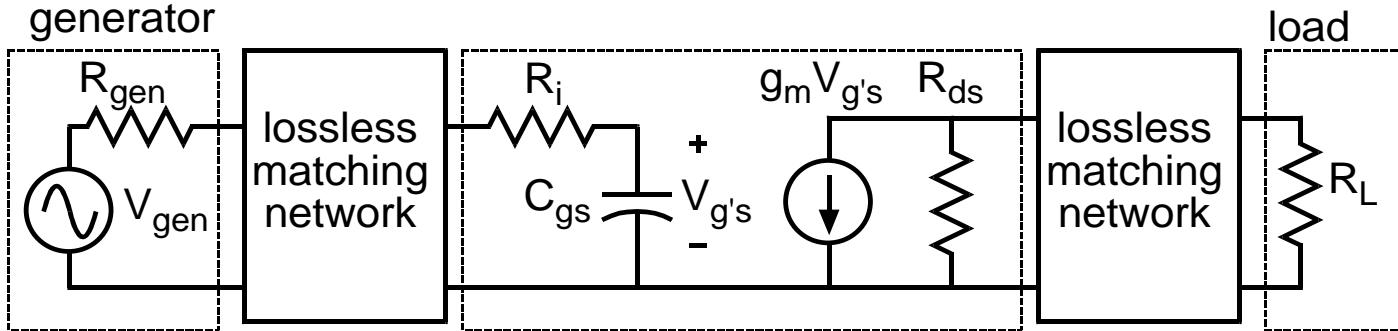

The transistor or amplifier is connected to generator and load via lossless matching networks. If it is possible to match at both input and output, then the power gain is called the \*maximum available gain\* (MAG)

Detailed microwave circuit theory (see later notes) indicates that this procedure often produces an oscillator (if the device is “potentially unstable”). In that case we must define **Maximum stable gain**

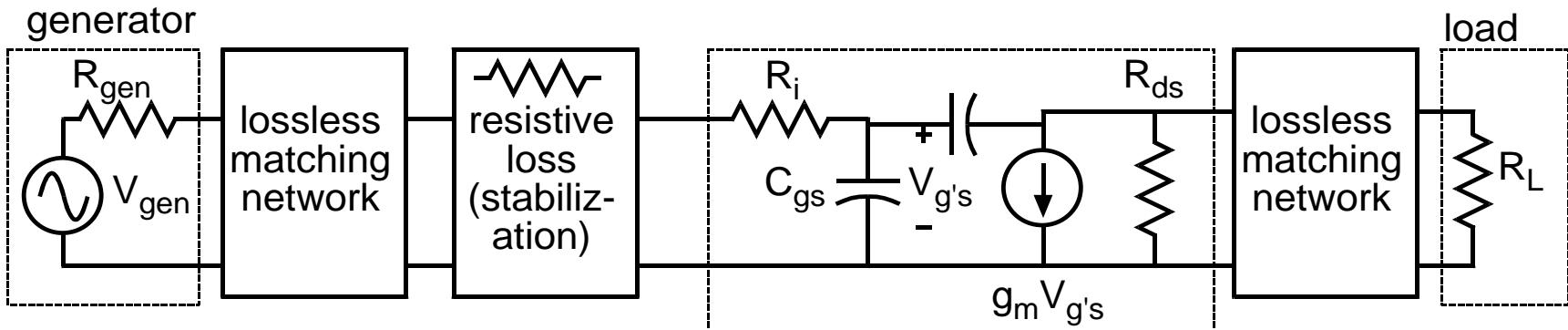
# Maximum Stable Power Gain (if MAG does not exist)



If the device is potentially unstable (usually due to strong feedback through  $C_{gd}$  as indicated), addition of a minimum amount of series/shunt resistance to the device input/output will prevent oscillation, and the device can then be matched. The resulting power gain is called the ***Maximum stable power gain***.

# Unilateral power gain

---

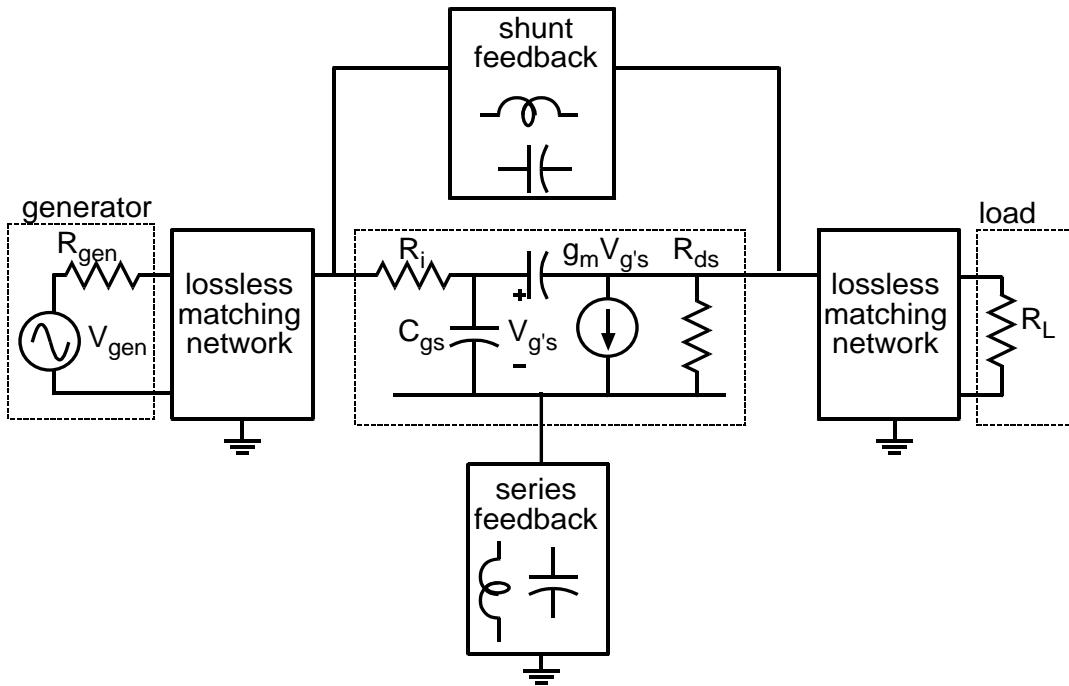

If the device is potentially unstable (due to strong feedback), addition of lossless reactive feedback as indicated can cancel the feedback and prevent oscillation. The device can then be matched. The resulting power gain is called ***Mason's invariant power gain*** \*\*or\*\* ***the Unilateral power gain***,  $U$ .

# Power-Gain Cutoff Frequency (Fmax)

This is the frequency at which the device Unilateral power gain reaches unity.



The maximum available gain (either in the forward or reverse direction) also reaches unity at the same frequency

For Field - Effect Transistors :


$$f_{\max} \cong \frac{f_\tau}{2\sqrt{(R_i + R_s + R_g)G_{ds} + 2\pi f_\tau R_g C_{dg}}}$$

For Bipolar Transistors ( $R_{ce}$  being large) :
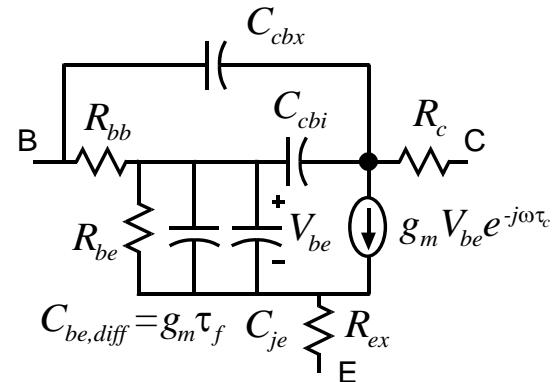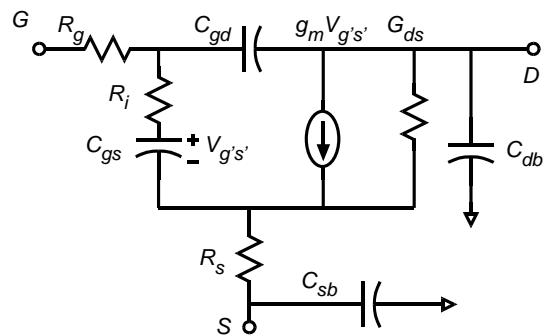
$$f_{\max} \cong \frac{f_\tau}{2\sqrt{R_{bb}/R_{ce} + 2\pi f_\tau R_{bb} C_{cbi}}} \rightarrow \sqrt{\frac{f_\tau}{8\pi R_{bb} C_{cbi}}}$$



# Power gains of a typical transistor

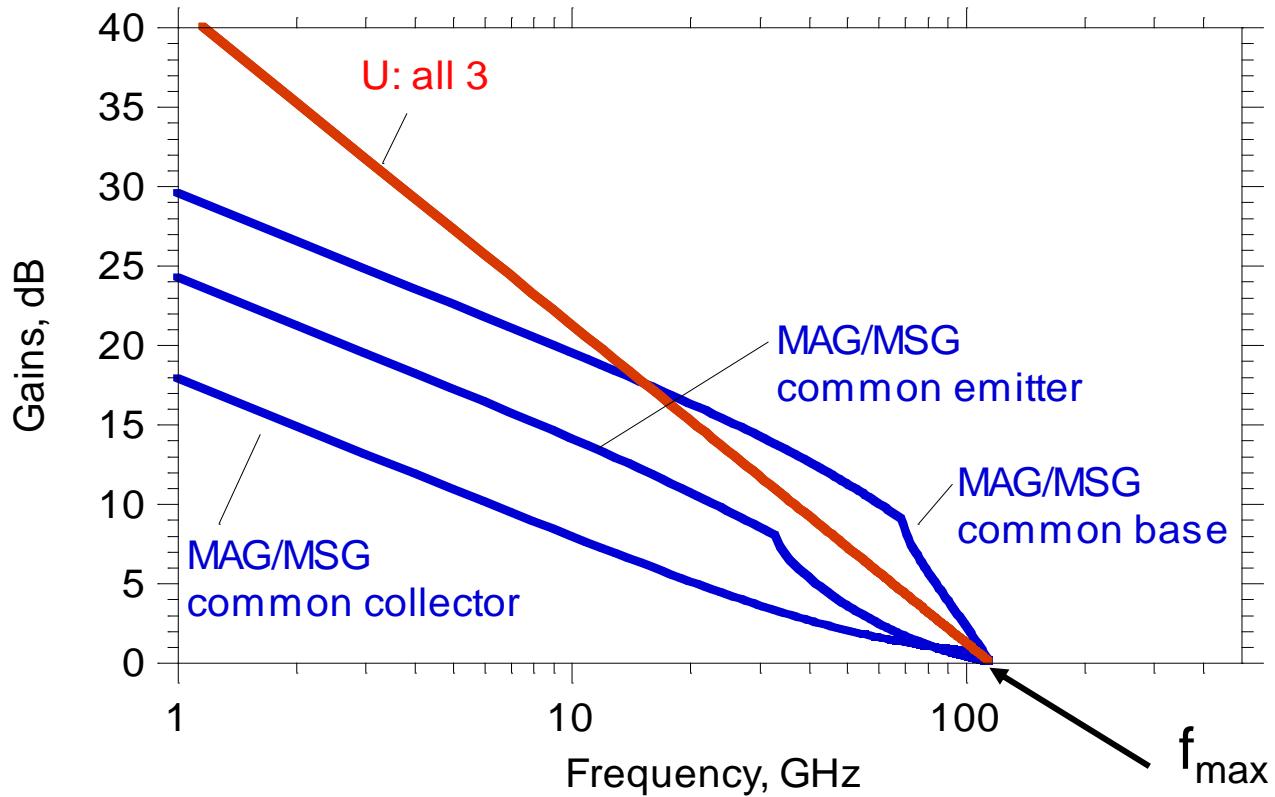

The inflection in the curves is the break between unstable (MSG) at lower frequencies and stable (MAG) at higher frequencies.

MAG/MSG is directly relevant for RF/microwave/mm-wave IC design.


Because U has -20 dB/decade slope, it is used to extrapolate measurements to determine  $f_{\max}$

# End

# **Appendix (optional)**

# Bipolar Transistor Operation
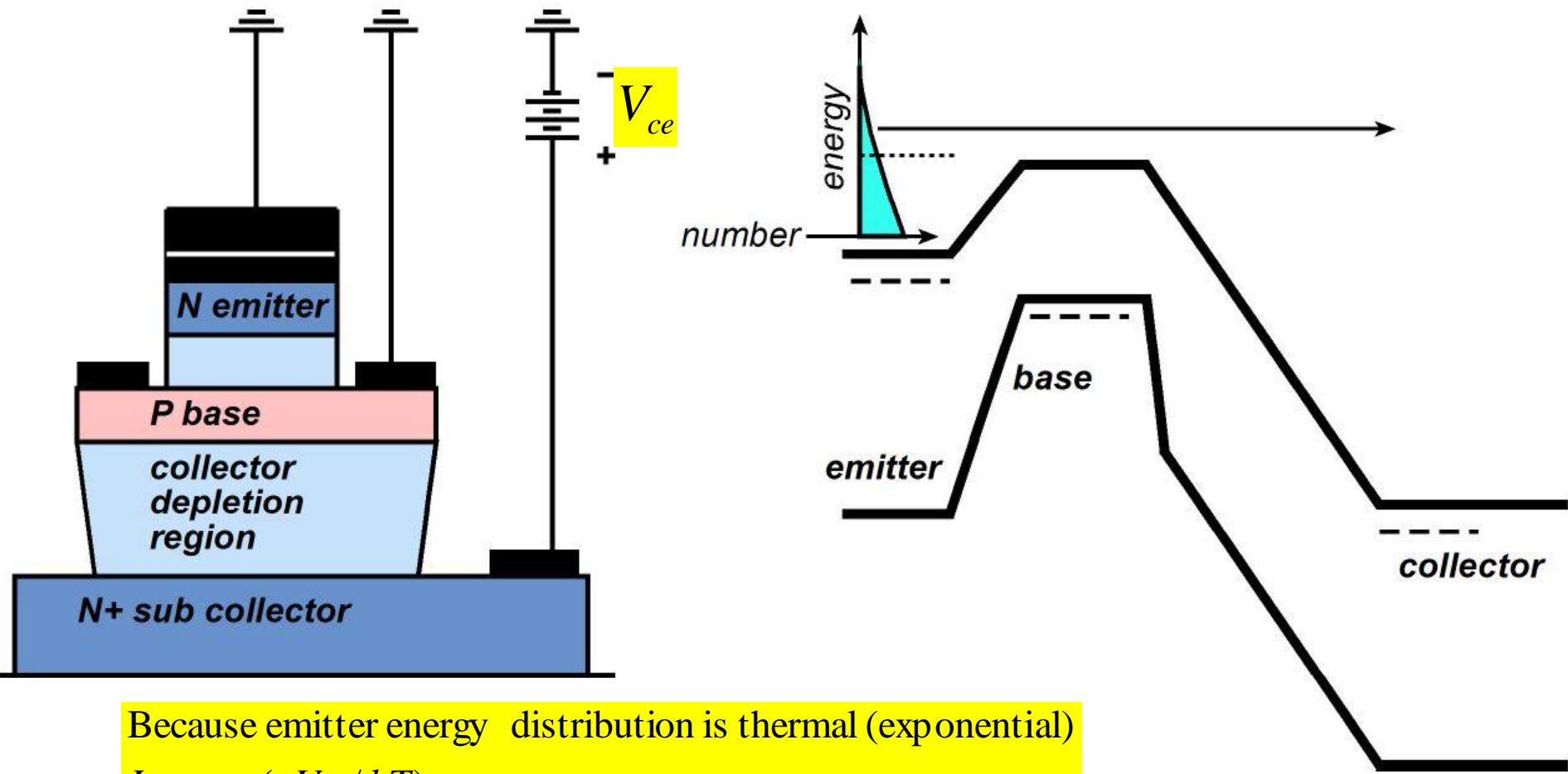
# Bipolar Transistor ~ MOSFET Below Threshold





Because emitter energy distribution is thermal (exponential)

$$I_c \propto \exp(qV_{be} / kT)$$

Almost all electrons reaching base pass through it

$\rightarrow I_c$  varies little with collector voltage
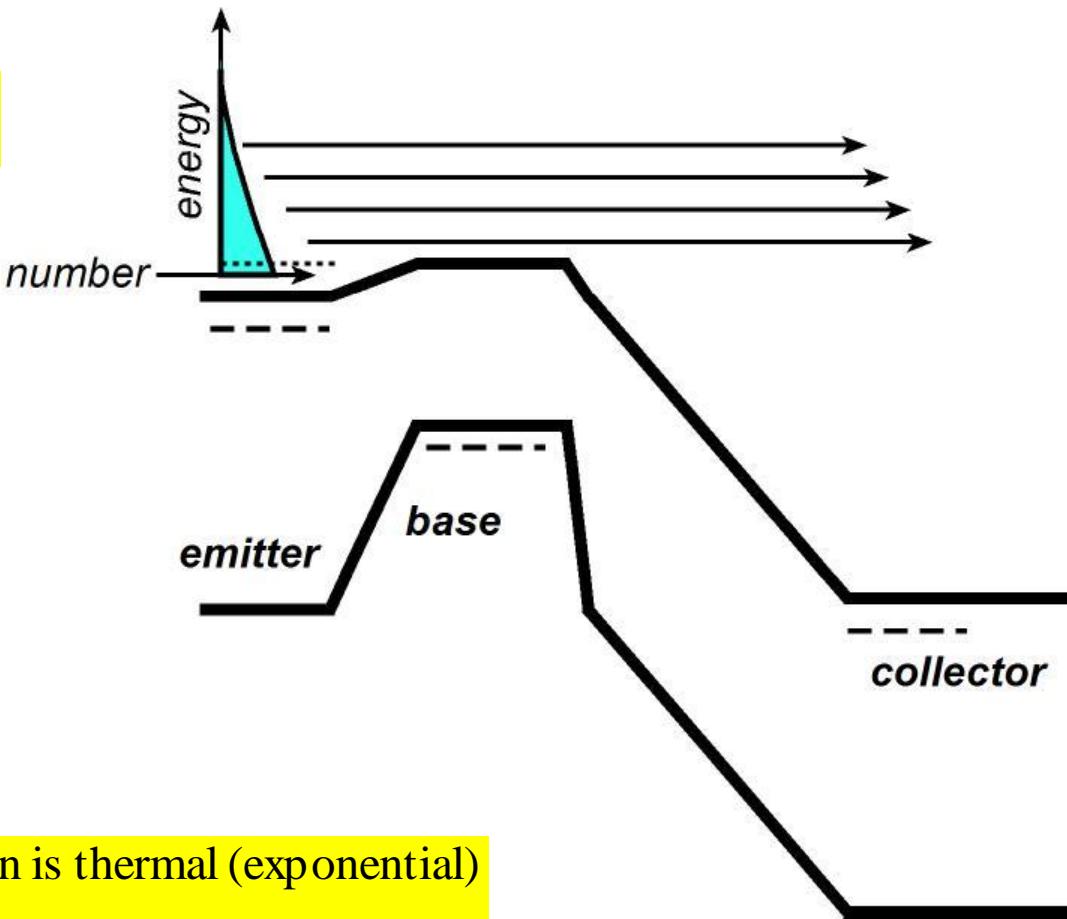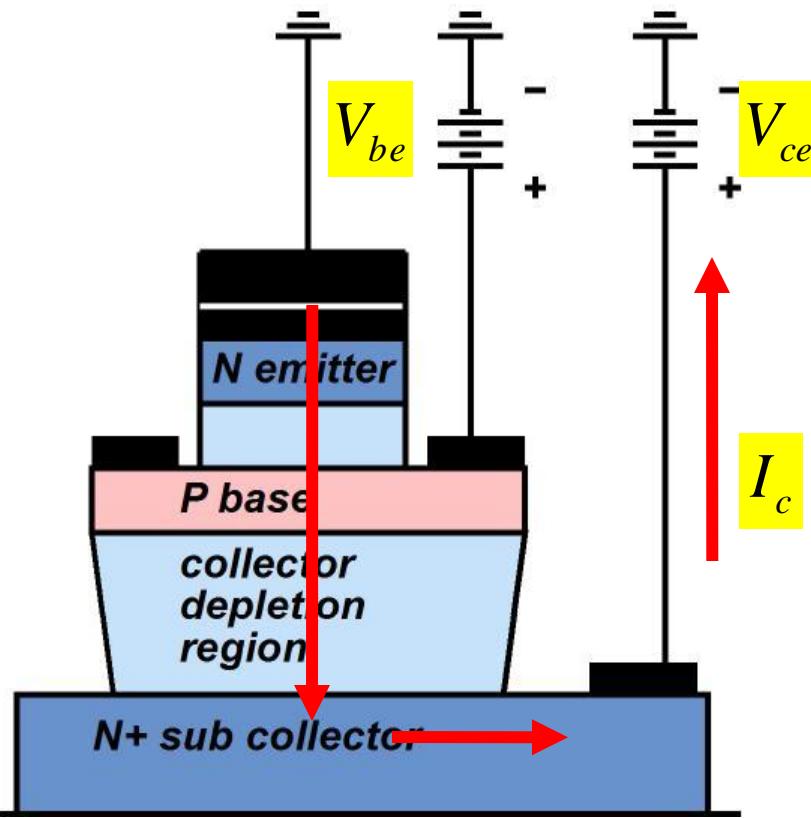
# Bipolar Transistor ~ MOSFET Below Threshold



Because emitter energy distribution is thermal (exponential)

$$I_c \propto \exp(qV_{be} / kT)$$

Almost all electrons reaching base pass through it


$\rightarrow I_c$  varies little with collector voltage

# **HBT Equivalent Circuit Model**



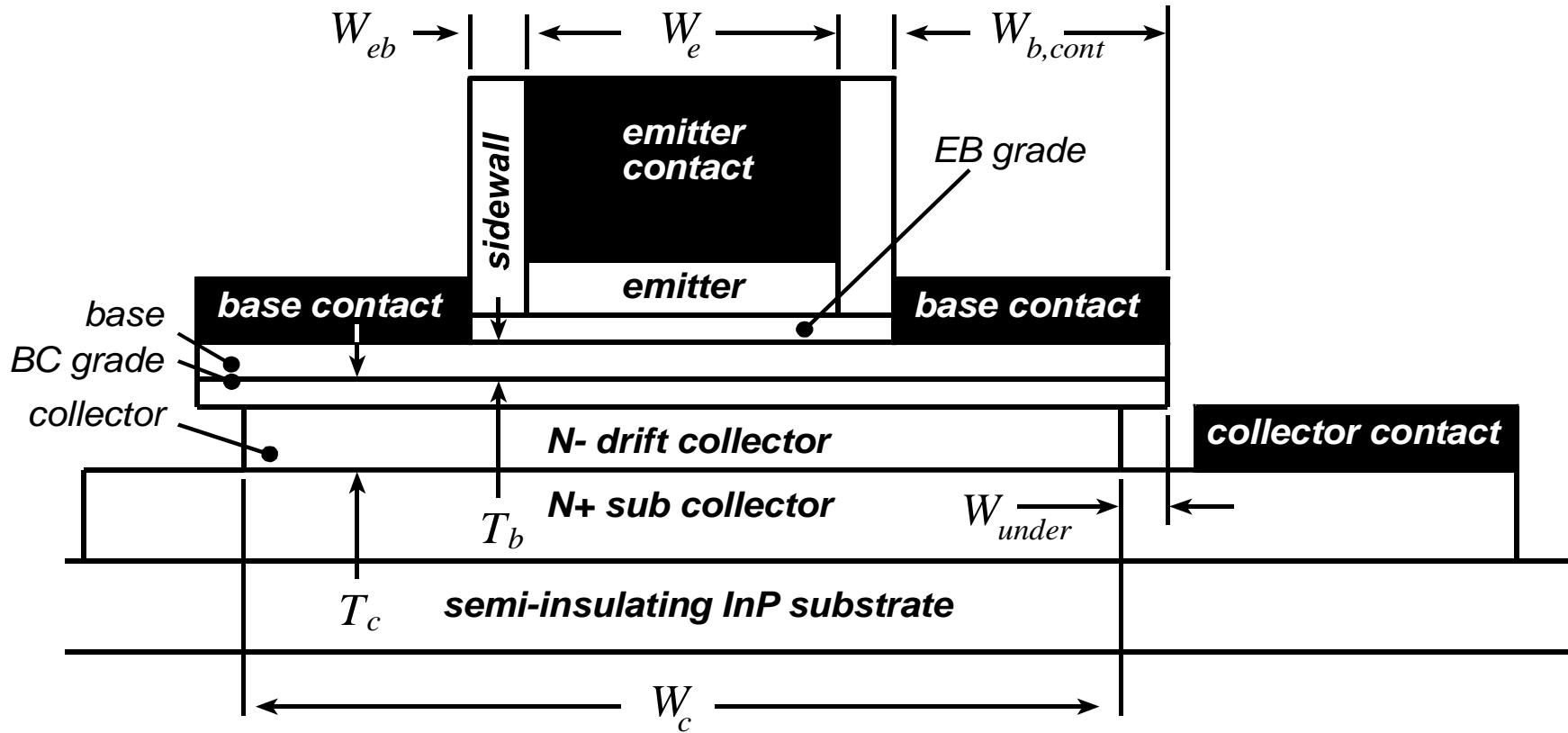
# Physical structure, symbolic

---

Device Stripe Length =  $L_E$   
perpendicular to drawing


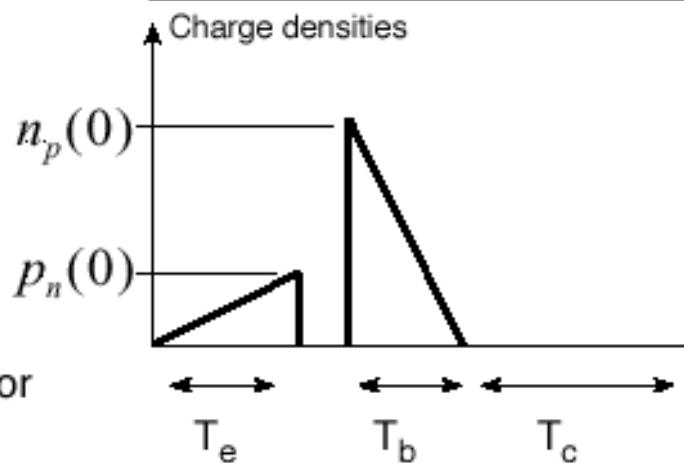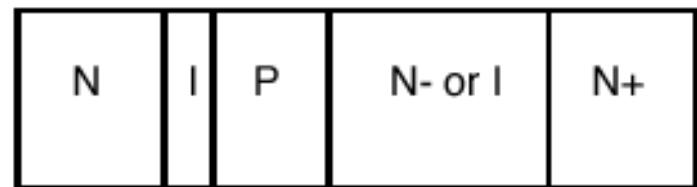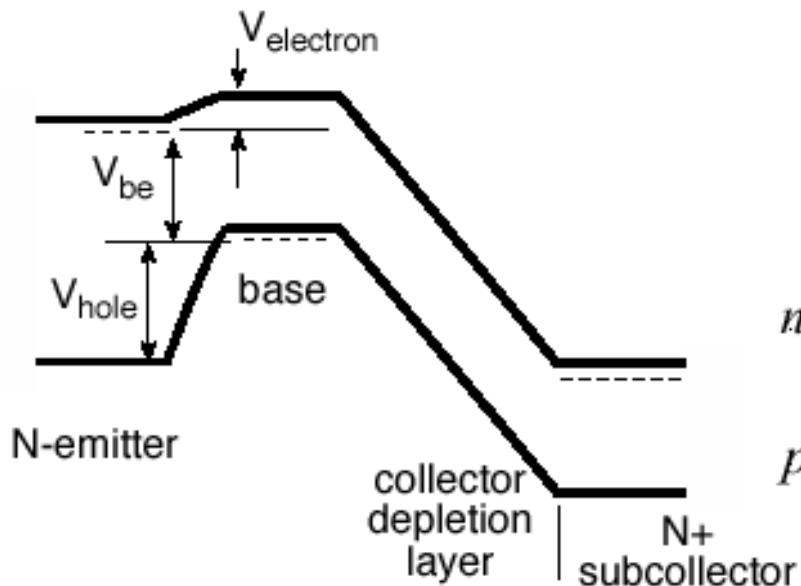
# Bipolar Transistor DC-IV Characteristics



$$n_p(0) = qN_c e^{-qV_{electron}/kT} \propto e^{+qV_{be}/kT}$$

electron concentration at emitter edge of base

$$p_n(0) = qN_v e^{-qV_{hole}/kT} \propto e^{+qV_{be}/kT}$$

hole concentration at base edge of emitter  
heterojunction makes this small

$$I_{electron} = \frac{D_n q A_e N_c}{T_b} e^{-qV_{electron}/kT} \propto e^{+qV_{be}/kT}$$



electron current from emitter to collector

$$g_m \equiv \frac{dI_c}{dV_{be}} = \frac{qI_c}{kT}$$

transconductance

# Bipolar Transistor: Carrier Transit Times

## Base Transit Time

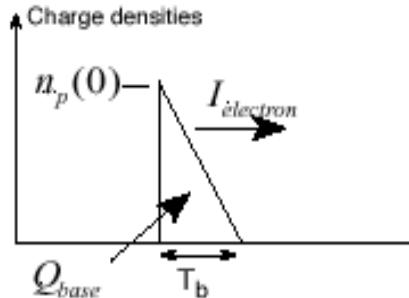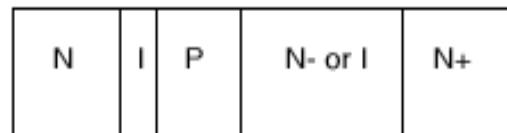

electron concentration at emitter edge of base

$$n_p(0) = qN_c e^{-qV_{electron}/kT} \propto e^{+qV_{be}/kT}$$

electron current from emitter to collector

$$I_{electron} = qn_p(0)D_n / T_b$$

stored base charge

$$\begin{aligned} Q_{base} &= qA_e n_p(0)T_b / 2 \\ &\dots = I_{electron} T_b^2 / 2D_n = \tau_b I_{electron} \end{aligned}$$



"Diffusion Capacitance"

$$C_{diffusion} \equiv \frac{dQ_{base}}{dV_{be}} = \frac{dQ_{base}}{dI_c} \frac{dI_c}{dV_{be}} = (\tau_b + \tau_c)g_m$$

$$C_{be, \text{ diffusion}} = g_m (\tau_b + \tau_c)$$

fictitious capacitance between base & emitter  
modelling charge storage

## Collector Transit Time

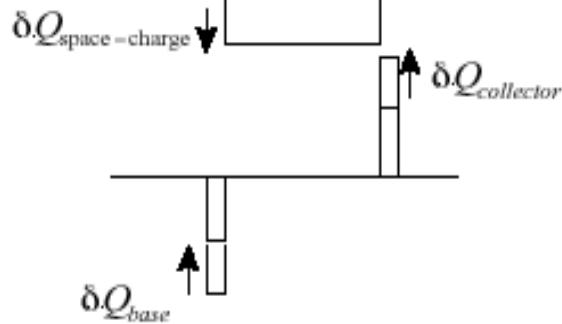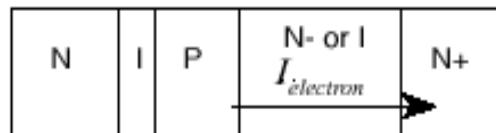


depletion-layer space-charge

$$\delta Q_{space-charge} = \frac{T_c}{v_{sat}} \delta I_{collector}$$

change in base stored charge

$$\begin{aligned} \delta Q_{base} &= \delta Q_{collector} = \delta Q_{space-charge} / 2 \\ &\dots = \delta I_{collector} (T_c / 2v_{sat}) = \tau_c \delta I_{collector} \end{aligned}$$
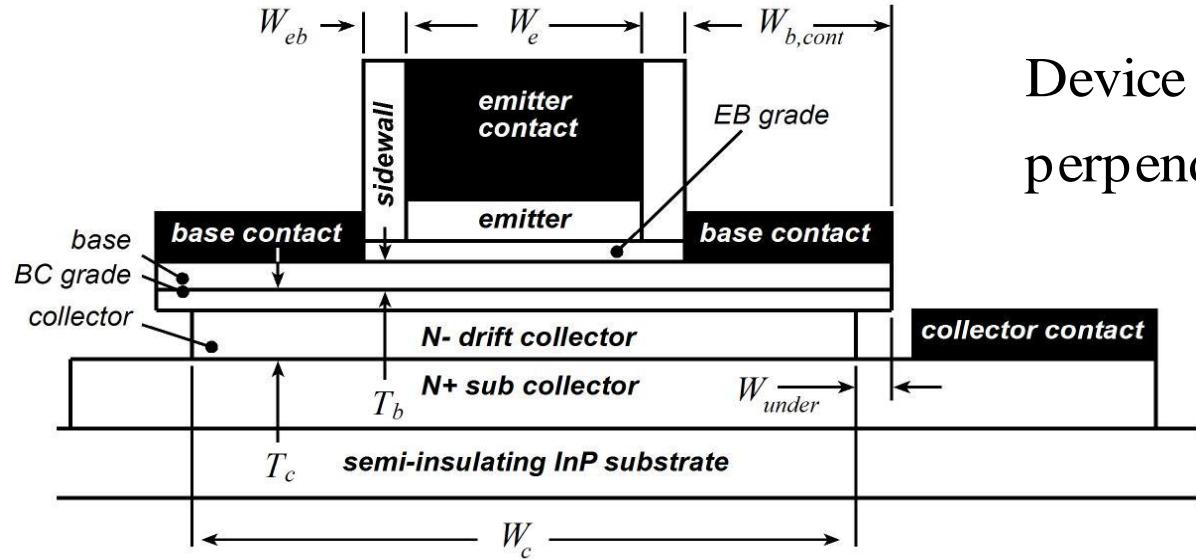
# Base resistance & collector-base capacitance



Device Stripe Length =  $L_E$   
perpendicular to drawing

$R_{bb} \approx$  contact term + spreading under contact + spreading under emitter



$$R_{bb} \approx \frac{\rho_{contact}}{2 \cdot L_E \cdot W_{b,cont}} + \frac{1}{6} \frac{W_{b,cont}}{L_E} \rho_{base\_sheet} + \frac{1}{12} \frac{W_E}{L_E} \rho_{base\_sheet}$$

$$C_{cb} \approx \frac{\epsilon_{semiconductor} W_c L_e}{T_c}$$

$R_{bb}$  and  $C_{cb}$  are distributed  $\rightarrow$  splitting of  $C_{cb}$  into  $C_{cbx}$  and  $C_{cbi}$

Details beyond scope of class (see Rodwell IEEE EDL Nov. 2001, Proc. IEEE Feb. 2008)



# HBT RC Parasitics

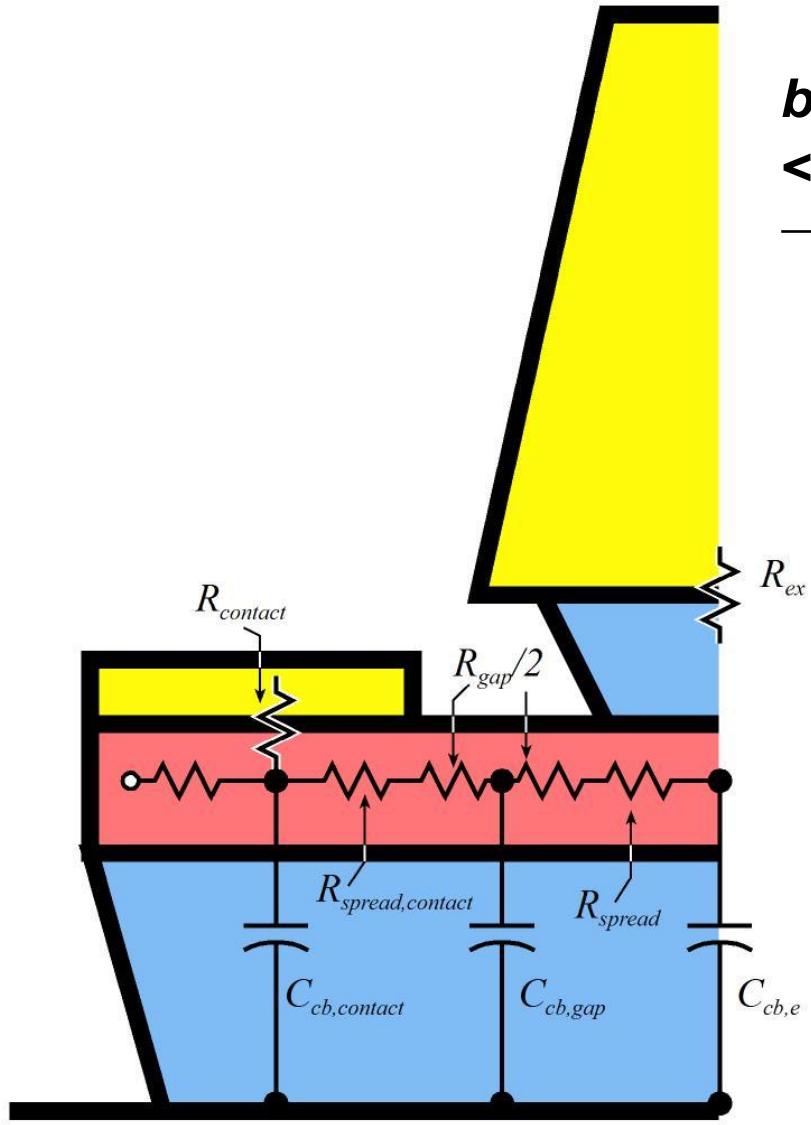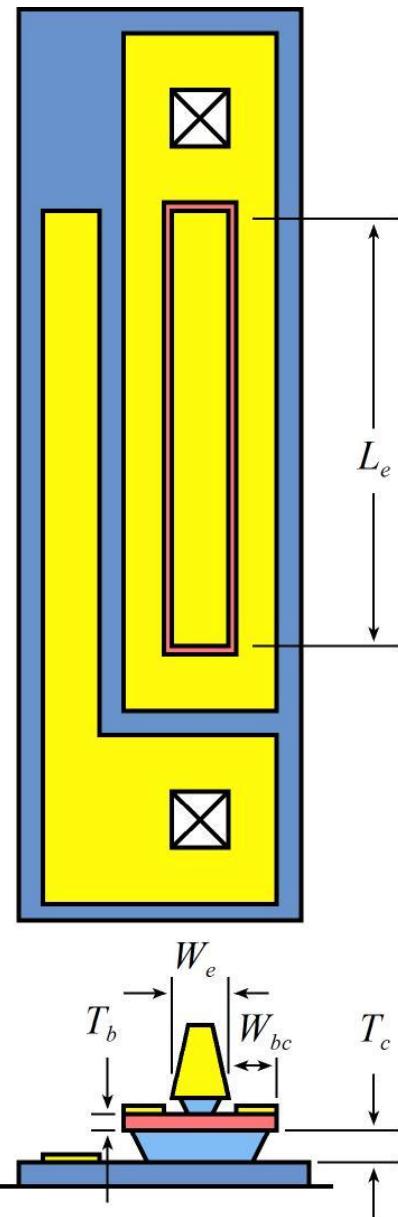

**base contact width  
< 2 transfer lengths  
→ simple analysis**

**Limiting case of  
Pulfrey / Vaidyanathan  
 $f_{max}$  model.**

# HBT RC Parasitics

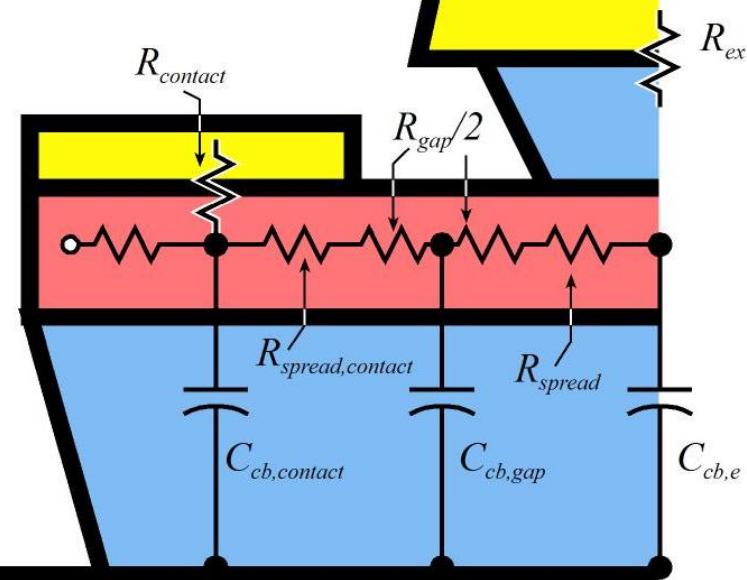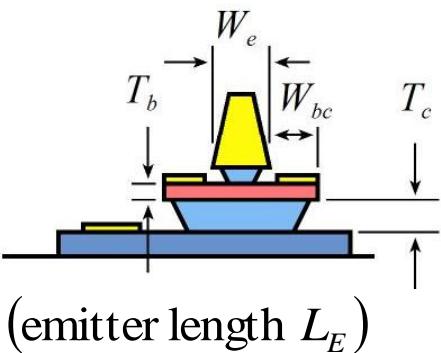

$$R_{ex} = \rho_{contact,emitter} / A_{emitter}$$

$$R_{spread} = \rho_s W_e / 12 L_E$$

$$R_{gap} = \rho_s W_{gap} / 4 L_E$$

$$R_{spread,contact} = \rho_s W_{bc} / 6 L_E$$

$$R_{contact} = \rho_{contact,base} W_{bc} / A_{base\_contacts}$$

$$C_{cb,e} = \epsilon A_{emitter} / T_c$$

$$C_{cb,gap} = \epsilon A_{gap} / T_c$$


$$C_{cb,contact} = \epsilon A_{base\_contacts} / T_c$$

# Base-Collector Time Constant & Fmax.

---

$$f_{\max} \cong \sqrt{\frac{f_\tau}{8\pi R_{bb} C_{cbi}}} \text{ where}$$


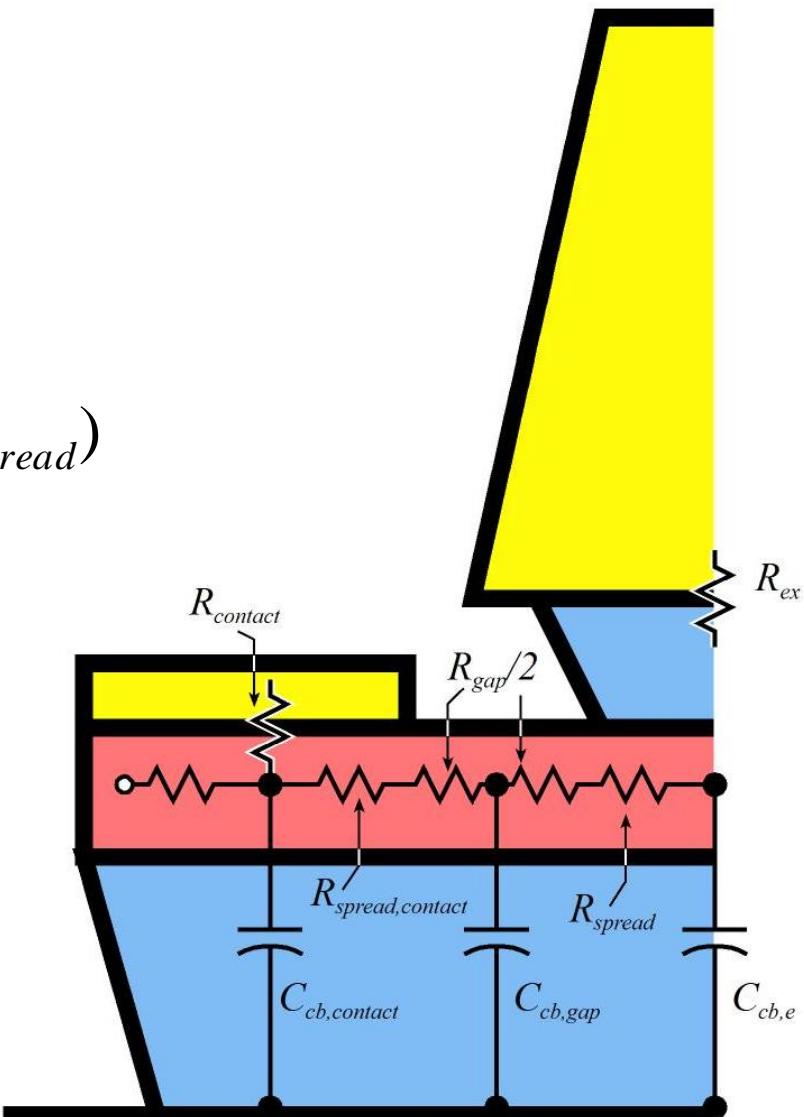
$$\begin{aligned}\tau_{cb} &= R_{bb} C_{cbi} = C_{cb,contact} R_{contact} \\ &+ C_{cb,gap} (R_{contact} + R_{spread,contact} + R_{gap}/2) \\ &+ C_{cb,e} (R_{contact} + R_{spread,contact} + R_{gap} + R_{spread})\end{aligned}$$


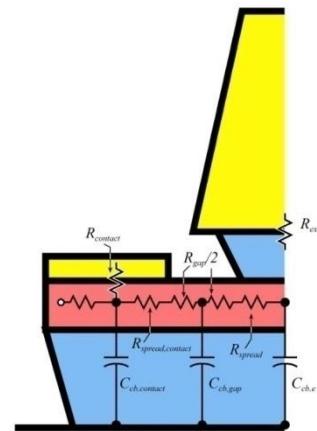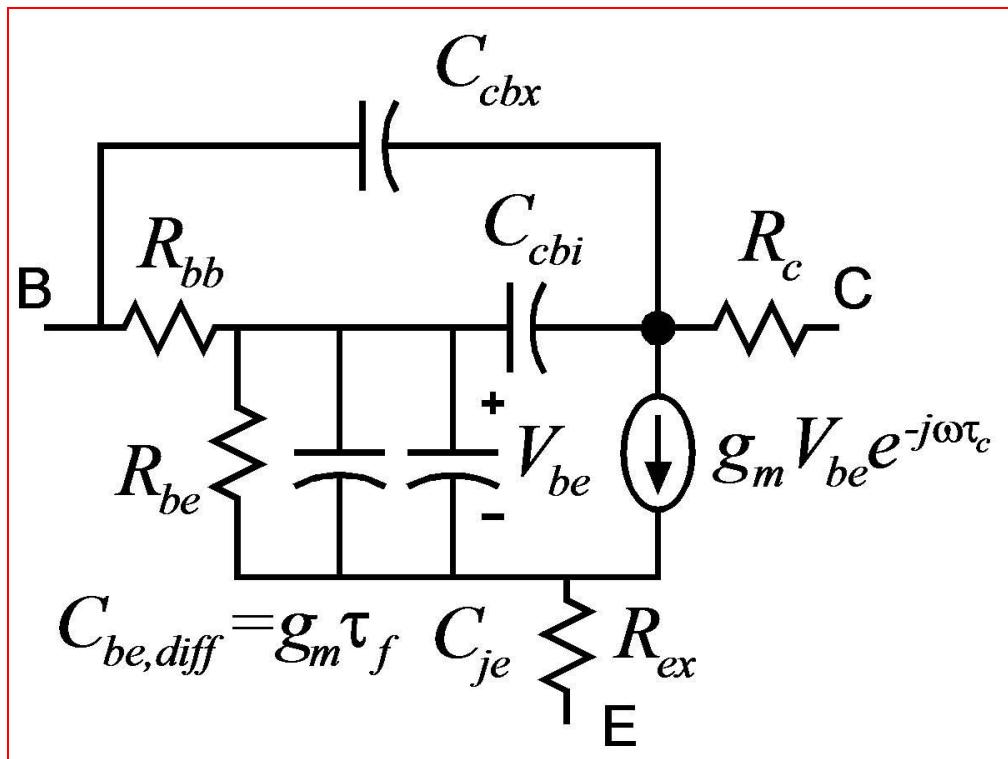
# Relationship to HBT Equivalent Circuit Model

$$C_{cbx} + C_{cbi} = C_{cb,e} + C_{cb,gap} + C_{cb,contact}$$



$$R_{bb} = R_{spread} + R_{gap} + R_{contact,spread} + R_{contact}$$



$$\begin{aligned} R_{bb} C_{cbi} &= C_{cb,contact} R_{contact} + C_{cb,gap} (R_{contact} + R_{spread,contact} + R_{gap}/2) \\ &\quad + C_{cb,e} (R_{contact} + R_{spread,contact} + R_{gap} + R_{spread}) \end{aligned}$$



# **Field-Effect Transistor Operation (Approximate)**

# Field-Effect Transistor Operation

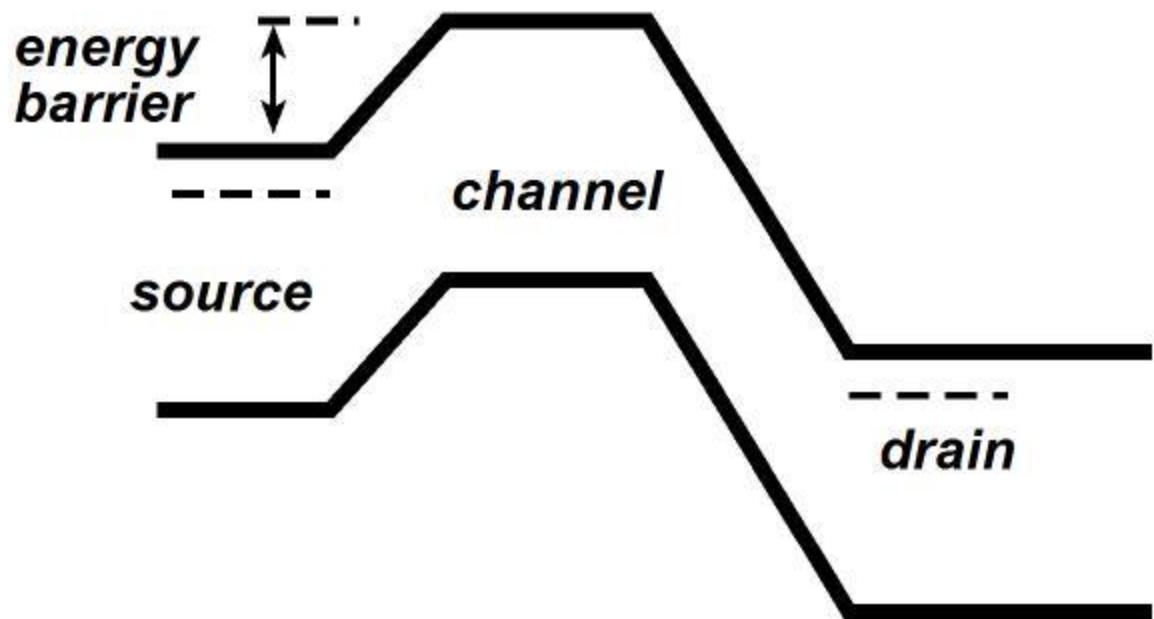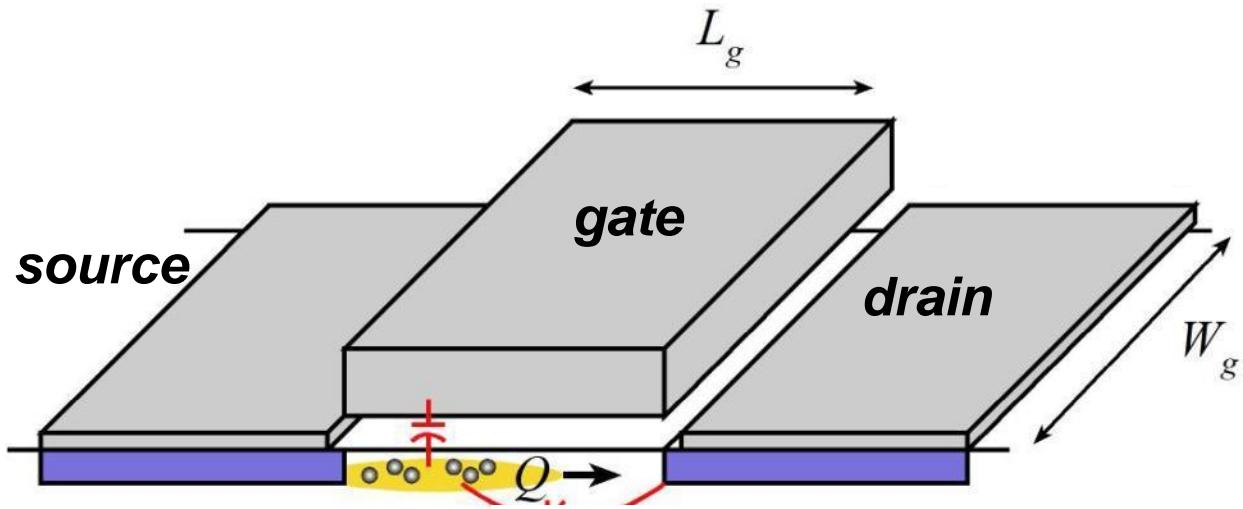


**Positive Gate Voltage**  
→ reduced energy barrier  
→ increased drain current

# Field-Effect Transistor Operation

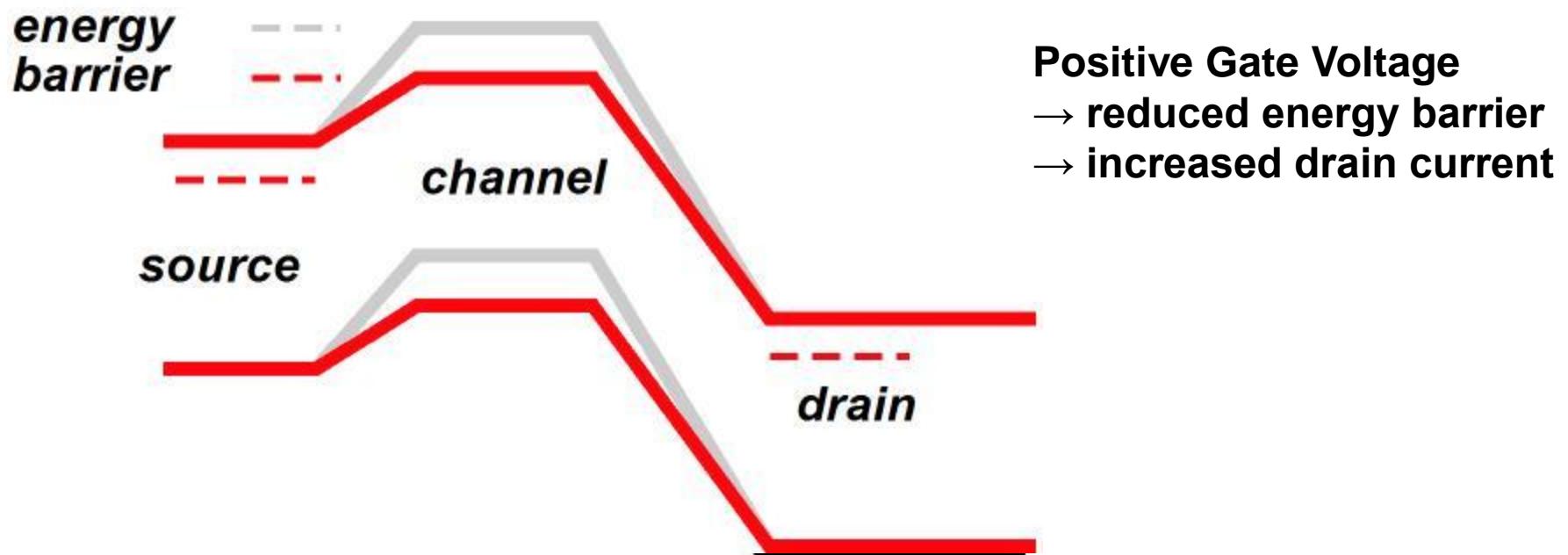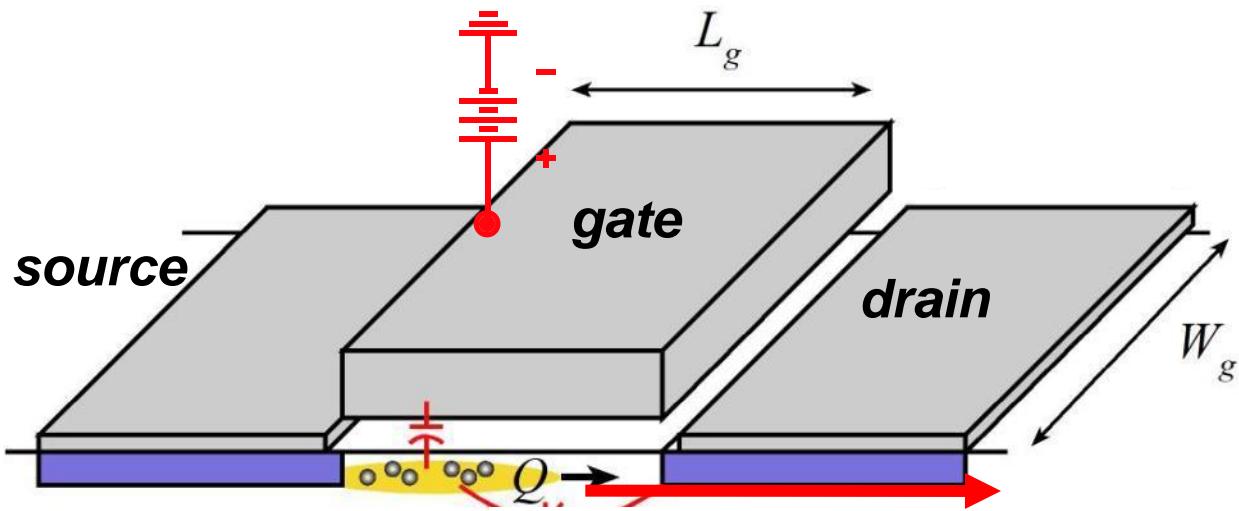

# FETs: Basic Operation

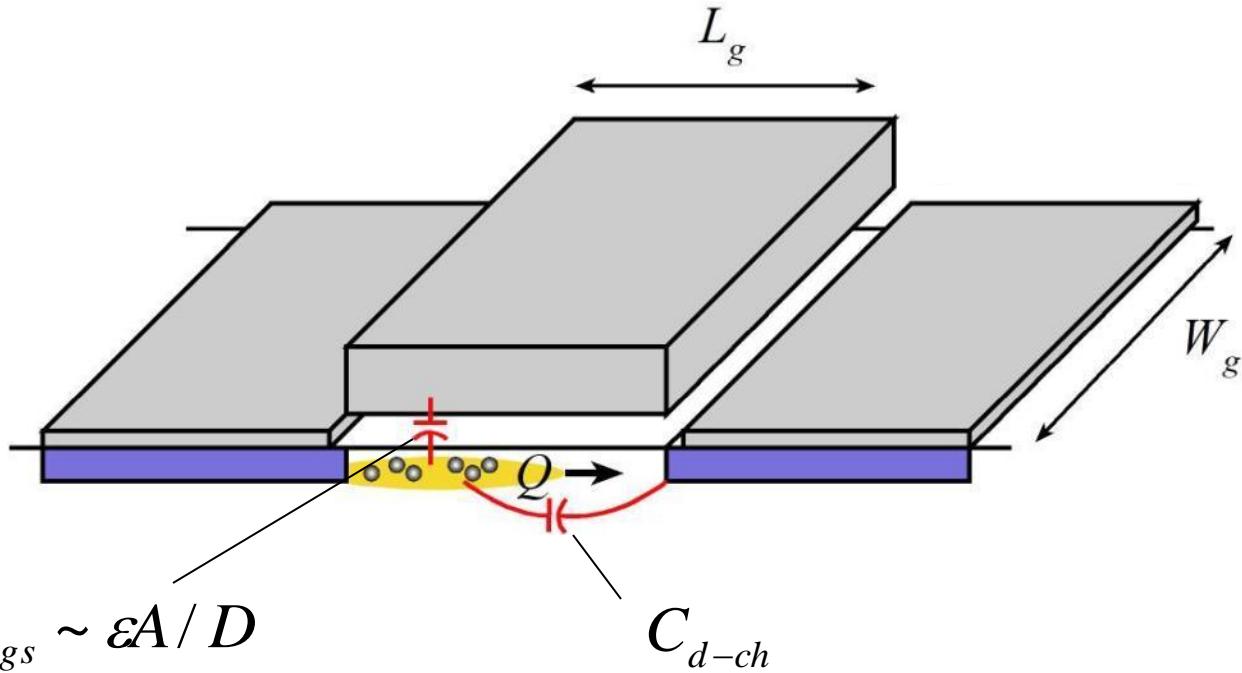


$$I_d = Q / \tau \quad \text{where} \quad \tau = L_g / v_{electron}$$

$$\delta Q = C_{gs} \delta V_{gs} + C_{d-ch} \delta V_{ds}$$

$$\delta I_d = g_m \cdot \delta V_{gs} + G_{ds} \cdot \delta V_{ds} \quad \text{where} \quad g_m = C_{gs} / \tau \text{ and } G_{gd} = C_{d-ch} / \tau$$

# FET Characteristics

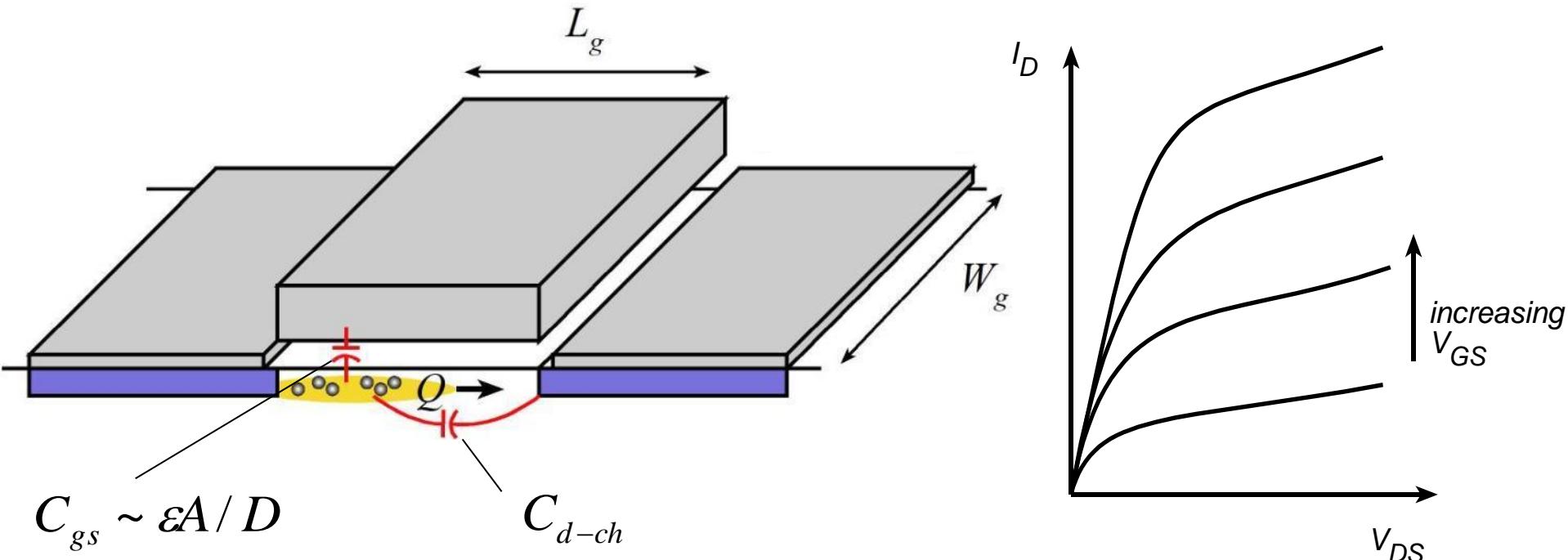

$$\delta I_d = g_m \cdot \delta V_{gs} + G_{ds} \cdot \delta V_{ds}$$



$$g_m = C_{gs} / \tau \quad G_{gd} = C_{d-ch} / \tau \quad \tau = L_g / v_{electron}$$

# FET Parasitic Capacitances (Estimate)

