

ECE ECE145B (undergrad) and ECE218B (graduate)

Mid-Term Exam. February 15, 2012

Do not open exam until instructed to.

Open notes, open books, etc

You have 1 hr and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.), ***AFTER STATING THEM.***

Problem	Points Received	Points Possible
1a		7
1b		7
1c		8
1d		8
2a		10
2b		10
3a		15
3b		25
total (145b)		100

ECE 218b students ONLY will be working problem 4

4		40
total (218b)		140


Name: _____

Problem 1, 30 points

Signal/noise ratios and noise figure

$R_{gen} = 50 \Omega$. The amplifier has a total input-referred noise voltage $E_{n,t,amp}$ whose spectral density is $3.31 \cdot 10^{-18} \text{ V}^2/\text{Hz}$.

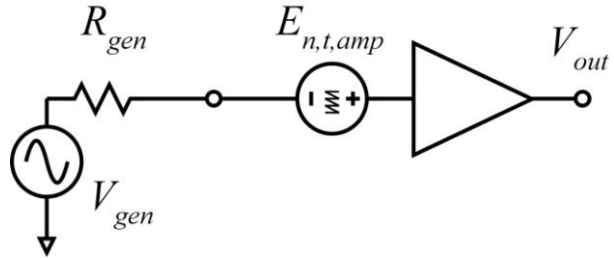The generator is at 300 Kelvin, i.e. the thermal voltage noise of R_{gen} has a spectral density of $4kTR_{gen}$.



Part a, 7 points

Find the spectral density, in V^2/Hz , of the **total** input-referred noise.

$E_{n,t} =$ _____

Part b, 7 points

Find amplifier noise figure. Please state in linear and in dB units.

Noise figure _____(linear) _____(dB)

Part c, 8 points

If we filter V_{out} with a 1 Hz bandwidth*, what RMS value of V_{gen} would result in a 0 dB signal/noise ratio ?

*One can relate integration time or averaging time in an experiment with an equivalent filter bandwidth. 1 Hz filter bandwidth is roughly equivalent to observing a signal for 1 second. So the analysis is, in effect, determining the minimum observable signal in a one-second observation time.

RMS value of V_{gen} _____

Part d, 8 points

If we filter V_{out} with a 10 kHz bandwidth, about that required for an AM radio, what RMS value of V_{gen} would result in a 20 dB signal/noise ratio ? What is the available generator signal power in this case ?

RMS value of V_{gen} _____

available generator signal power _____


Problem 2, 20 points

2-port noise descriptions and signal/noise ratios.

$R_{gen} = 100 \Omega$.

$E_{n,amp}$ has a spectral density is $1.0 \cdot 10^{-18} \text{ V}^2/\text{Hz}$.

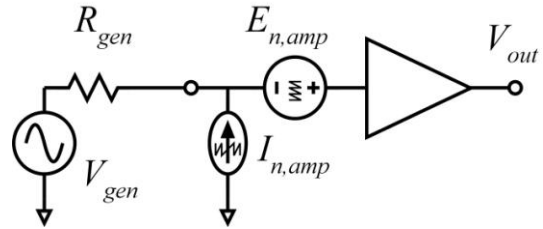$I_{n,amp}$ has a spectral density is $1.0 \cdot 10^{-22} \text{ A}^2/\text{Hz}$.



The cross spectral density of $E_{n,amp}$ and $I_{n,amp}$ is $5.0 \cdot 10^{-21} \text{ V} \cdot \text{A}/\text{Hz}$, and is purely real.

The generator is at 300 Kelvin, i.e. the thermal voltage noise of R_{gen} has a spectral density of $4kTR_{gen}$.

Part a, 10 points

Find the spectral density, in V^2/Hz ,of the **total** input-referred noise.

$E_{n,t} =$ _____

Part b, 10 points

Find amplifier noise figure. Please state in linear and in dB units.

Noise figure _____(linear) _____(dB)



Problem 3, 50 points

Low-Frequency Circuit Noise Analysis.

We are analyzing the FET amplifier to the right, with the FET small-signal model shown below. $R_D = 1 \text{ k}\Omega$ $R_L = 2 \text{ k}\Omega$, $R_G = 10 \text{ M}\Omega$ (please take this as infinity to simplify the math), $R_{gen} = 1 \text{ k}\Omega$.

The FET has $g_m = 100 \text{ mS}$, $R_g = 100 \text{ }\Omega$, $R_D = R_S = R_i = 0 \text{ }\Omega$, $C_{gs} = C_{gd} = 0 \text{ fF}$, $G_{ds} = 0 \text{ S}$, $\Gamma = 2/3$.

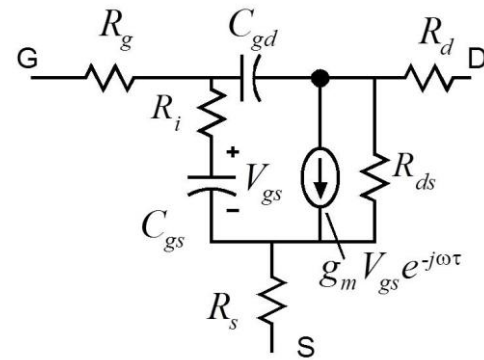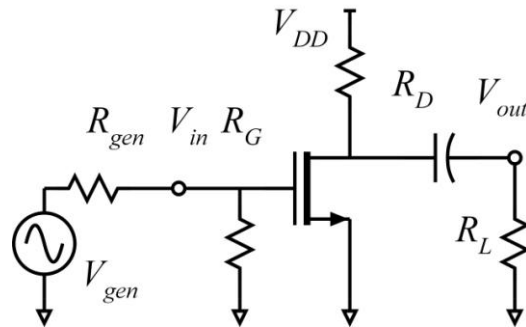The generator is at 300 Kelvin, i.e. the thermal voltage noise of R_{gen} has a spectral density of $4kTR_{gen}$.



Part a, 15 points

Draw an equivalent circuit diagram with all random voltage and current generators indicated. Assign a name/symbol to each. Give (1) algebraic expressions and (2) numerical values in A^2/Hz or V^2/Hz for the spectral density of each noise generator.

Part b, 25 points

Compute the total input-referred noise voltage spectral density of the circuit, including the noise contributions of the generator, of the amplifier, and of the load resistor.

Give both an algebraic expression and a numerical value in V^2/Hz .

Hint: You might either use the source transposition method, or might choose to compute the output noise and subsequently divide by the circuit gain.

expression for $S_{En,t} =$

$S_{En,t} =$

(V^2/Hz)

Problem 4, 40 points

****ECE 218B students only****

High-Frequency Circuit Noise Analysis.

We are analyzing the FET amplifier to the right, with the FET small-signal model shown below. $R_D = 1 \text{ k}\Omega$ $R_L = 2 \text{ k}\Omega$, $R_G = 10 \text{ M}\Omega$ (please take this as infinity to simplify the math), **$R_{gen} = 50 \text{ }\Omega$** .

The FET has $g_m = 100 \text{ mS}$, **$R_g = 10 \text{ }\Omega$** , $R_D = R_S = R_i = 0 \text{ }\Omega$, $C_{gd} = 0 \text{ fF}$, $G_{ds} = 0 \text{ S}$, $\Gamma = 2/3$.

The generator is at 300 Kelvin, i.e. the thermal voltage noise of R_{gen} has a spectral density of $4kTR_{gen}$.

We now set **$C_{gs} = 100 \text{ fF}$** This gives $f_\tau = 100 \text{ GHz}$.

Compute the noise figure at 10 GHz.

