

ECE ECE145B (undergrad) and ECE218B (graduate)

Mid-Term Exam. February 20, 2013

Do not open exam until instructed to.

Open notes, open books, etc

You have 1 hr and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.) , ***AFTER STATING THEM.***

Problem	Points Received	Points Possible
1a		20
1b		10
2		20
3a		10
3b		10
3c		10
4a		10
4b		10
total (145b)		100

Name: *Solution*


mark rodwell

rodwell@ece.ucsb.edu

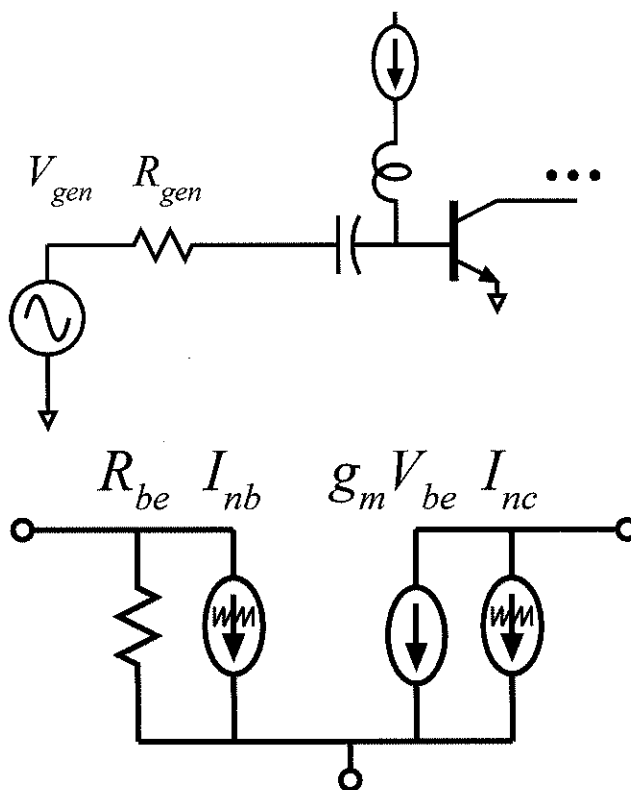Problem 1, 30 points

Circuit Noise calculations

To the left is shown a representation of a bipolar transistor amplifier, and below it the BJT small signal noise model.



Note that the only transistor parasitic element is the finite current gain β and hence the presence of the small signal resistance R_{be}

The base is biased at current I_{bo} , producing DC collector current $I_{co} = \beta I_{bo}$. The inductor and capacitor are both very large (infinite inductive reactance, infinite capacitive susceptance).




Part a, 20 points

We will assume that the generator (V_{gen}, R_{gen}) has thermal noise at an associated temperature of 300 Kelvin. Device by source transposition the spectral density of the total input-referred noise voltage, including the contributions of the amplifier and of the generator. Please reduce your answer to an algebraic expression involving *only* the following terms: $kT, q, I_{co}, \beta, R_{gen}$.

expression for $S_{En,i} =$

$$4kT R_{gen} + \frac{2q I_{co}}{\beta} R_{gen}^2 + 2kT \frac{kT}{q I_{co}} \left[1 + \frac{R_{gen} \cdot \frac{q I_{co}}{\beta kT}}{1} \right]^2$$

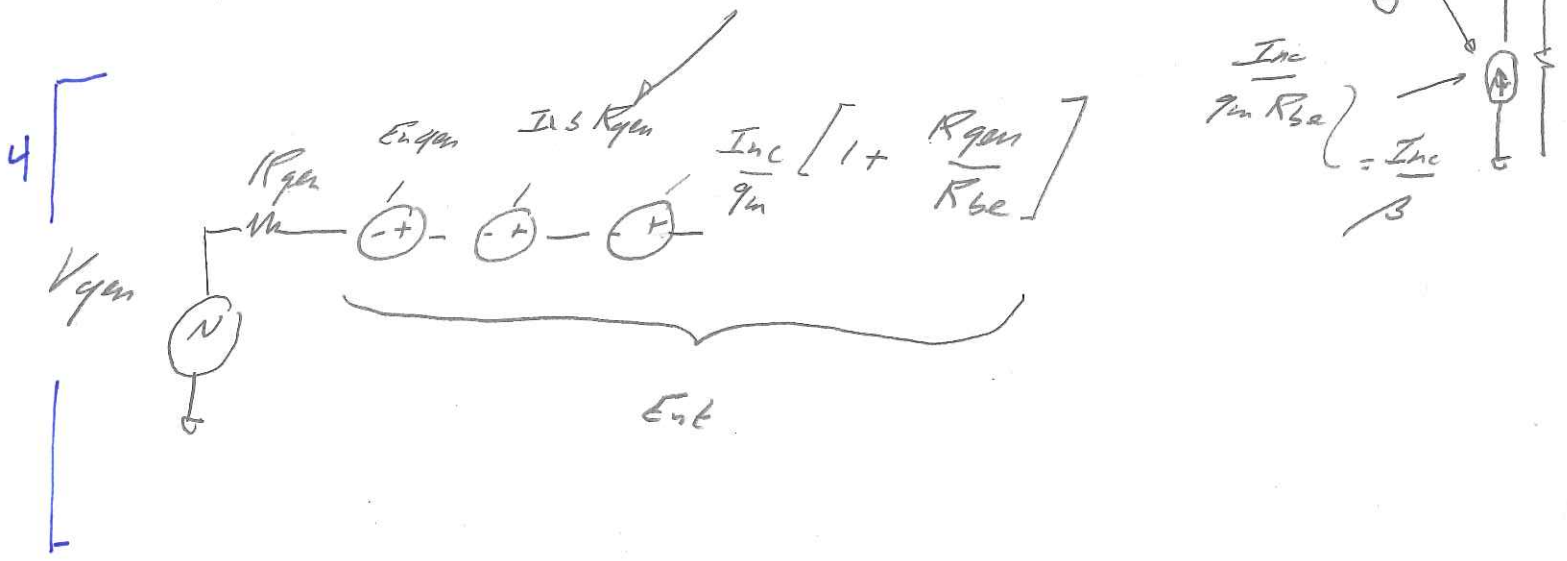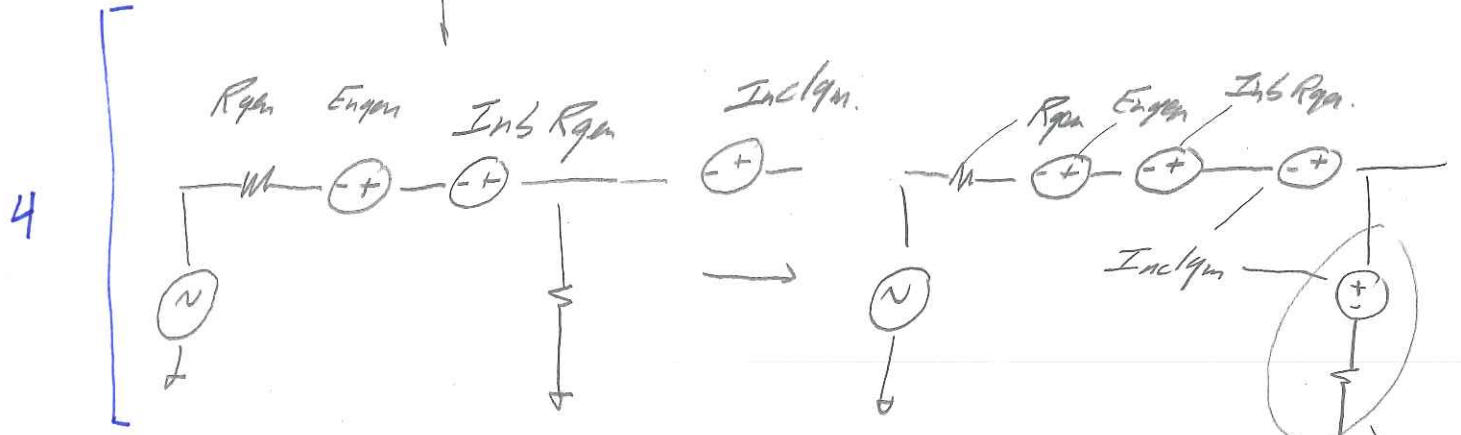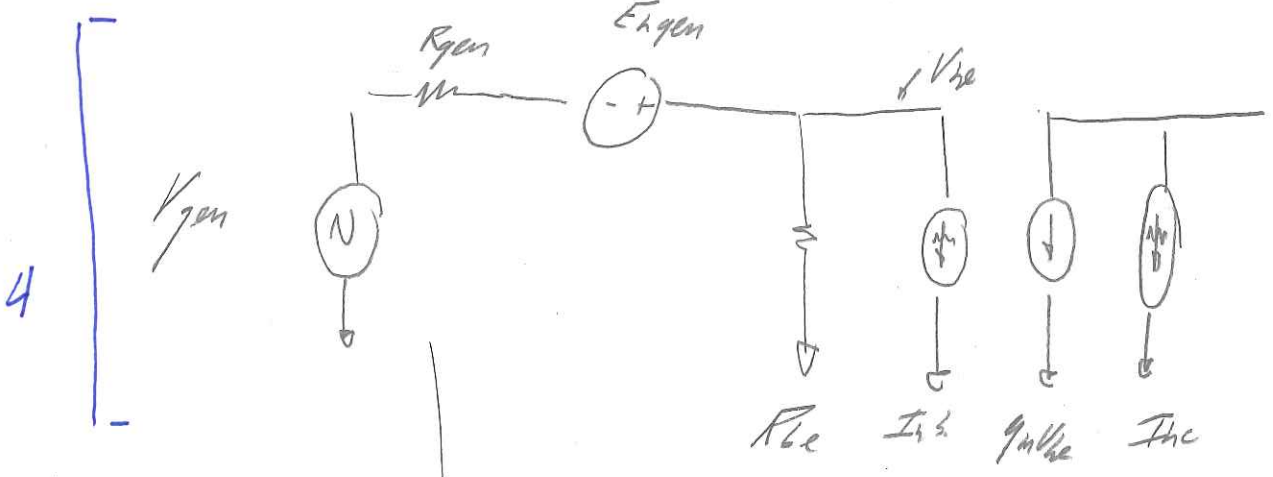$\underbrace{\hspace{10em}}_{\text{generator thermal noise}}$
 $\underbrace{\hspace{10em}}_{\text{base shot noise}}$
 $\underbrace{\hspace{10em}}_{\text{collector shot noise}}$



$$4 \left[\begin{aligned} E_{nt} &= E_{nqm} + I_{b3} R_{qm} + \frac{I_{nc}}{g_m} \left[1 + R_{qm}/R_{ce} \right] \\ \text{but } S_{E_{nqm}} &= 4kT R_{qm} & S_{I_{nc}} &= 2gI_c \\ S_{I_{b3}} &= 2gI_b & R_{ce} &= \frac{\beta}{g_m} = \frac{\beta kT}{gI_c} \end{aligned} \right]$$

$$4 \left[\begin{aligned} S_{ent} &= 4kT R_{qm} + 2gI_b R_{qm}^2 + \frac{2gI_c}{(gI_c + kT)^2} \left[1 + \frac{R_{qm}}{\beta kT/gI_c} \right]^2 \end{aligned} \right]$$

$$= 4kT R_{qm} + 2g \frac{I_{c0}}{\beta} R_{qm}^2 + \frac{2kT \cdot kT}{gI_{c0}} \left[1 + \frac{R_{qm} \cdot gI_{c0}}{\beta kT} \right]^2$$

Part b, 10 points

Adjusting the collector current (by adjusting the base bias current) will cause the total input-referred noise voltage to vary. What value of collector bias current gives the smallest input-referred noise ?

Hint: please simplify the calculus by assuming that R_{be} is much larger than R_{gen} .

expression for $I_{c,opt} =$

$$I_{c,opt} = \sqrt{\beta} \cdot \frac{kT}{g R_{gen}}$$

from which

$$g_m |_{opt} = R_{gen} / \sqrt{\beta}$$

this is a classic result.

we simplify by taking $R_{be} \gg R_{gen}$, which gives:

$$3 \quad S_{ent} = 4kT R_{gen} + 2g I_c \frac{R_{gen}^2}{\beta} + 2kT \frac{kT}{g I_0}$$

$$= a_1 + a_2 I_c + a_3 / I_c$$

$$4 \quad \left[\begin{array}{l} \text{from calculus, minimum is found when } a_2 I_c = a_3 / I_c \\ \rightarrow I_c = \sqrt{a_3 / a_2} \end{array} \right.$$

$$= \left(2kT \cdot \frac{kT}{g} \right)^{1/2} \left(\frac{\beta}{2g R_{gen}^2} \right)^{1/2} = \left(\frac{2 \cdot kT \cdot kT \cdot \beta}{2 \cdot g \cdot g \cdot R_{gen}^2} \right)^{1/2}$$

↳ easy!

$$5 \quad \left[\begin{array}{l} = \sqrt{\beta} \frac{kT}{g R_{gen}} \rightarrow \text{note this implies} \\ g_m = \frac{kT}{g I_0} = \frac{R_{gen}}{\sqrt{\beta}} \end{array} \right.$$


Problem 2, 20 points

More circuit noise calculations.

A two-stage FET amplifier is shown at the right.




Ignore DC bias considerations; you don't need these.

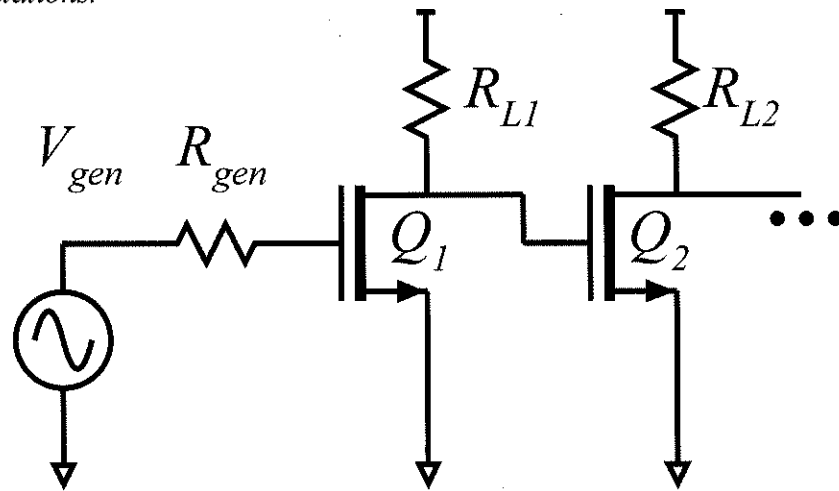The FETs have
 -zero parasitic capacitances,
 -zero parasitic gate, source, and drain resistances.



Both FETs have 10 mS transconductance and a channel noise parameter $\Gamma=1.5$. $R_{L1} = R_{L2} = 1\text{k}\Omega$, $R_{gen} = 100\text{ Ohms}$. Find the spectral density of the total (amplifier plus generator) input-referred noise voltage.

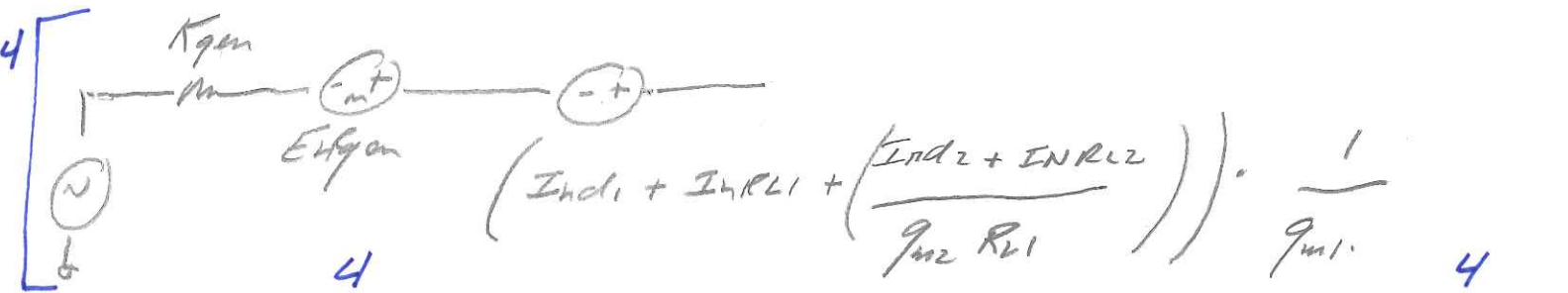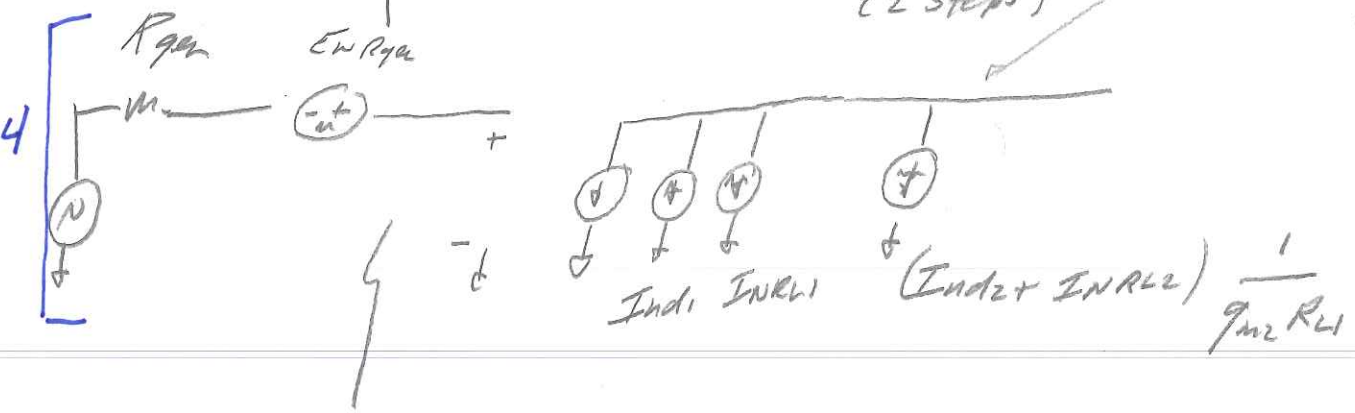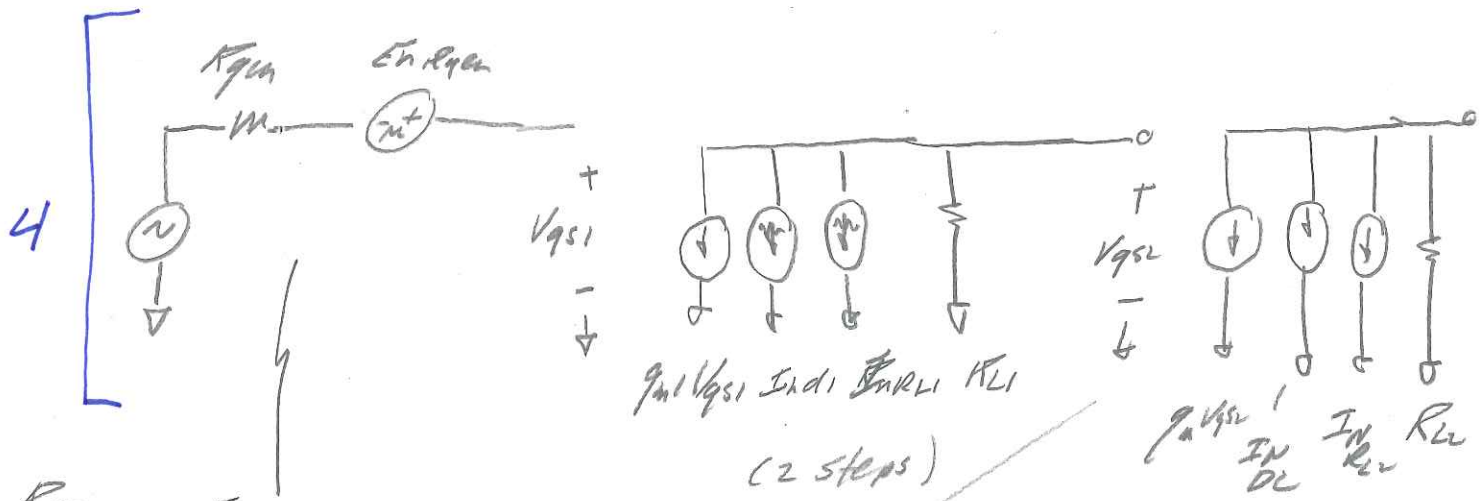$S_{En,t} = \underline{4.33 \cdot 10^{-18} \text{ V}^2/\text{Hz}}$ (give units)



$$S_{ENG} = 4kT R_{gen} + \frac{4kT I_1^2}{g_{m1}} + \frac{4kT}{R_{L1}} \cdot \frac{1}{g_{m1}^2} + \frac{4kT I_2^2}{g_{m2}} \cdot \frac{1}{g_{m1}^2 R_{L1}^2} + \frac{4kT}{R_{L2}} \cdot \frac{1}{g_{m2}^2 g_{m1}^2 R_{L1}^2}$$

generator	$1.66 \cdot 10^{-18} \text{ V}^2/\text{Hz}$	} $4.33 \cdot 10^{-18} \text{ V}^2/\text{Hz}$
Q1 thermal drain	$2.48 \cdot 10^{-18} \text{ V}^2/\text{Hz}$	
R_{L1}	$1.66 \cdot 10^{-19} \text{ V}^2/\text{Hz}$	
Q2 thermal drain	$2.48 \cdot 10^{-20} \text{ V}^2/\text{Hz}$	
R_{L2}	$1.66 \cdot 10^{-21} \text{ V}^2/\text{Hz}$	

10


Problem 3, 30 points

En-In models of circuits, noise figure

A FET is biased with an input resistor R_{gg} as shown.


The FET has

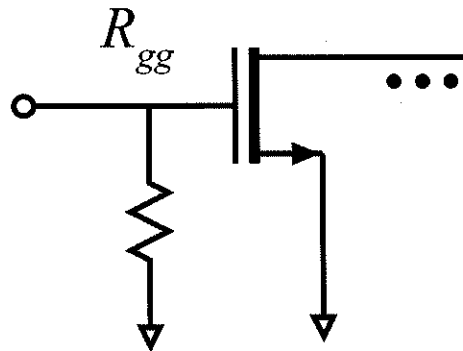- zero parasitic capacitances,
- zero parasitic gate, source, and drain resistances.
- a channel noise parameter of Γ



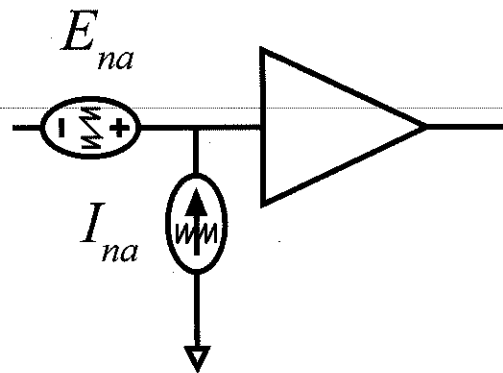Part a, 10 points



Calculate from the above the spectral density of E_{na} and of I_{na} , and their cross-spectral density



expression for $S_{E_{n,a}} = \frac{4kT}{9m}$

expression for $S_{I_{n,a}} = \frac{4kT}{R_{gg}} + \frac{4kT\Gamma}{9m R_{gg}^2}$

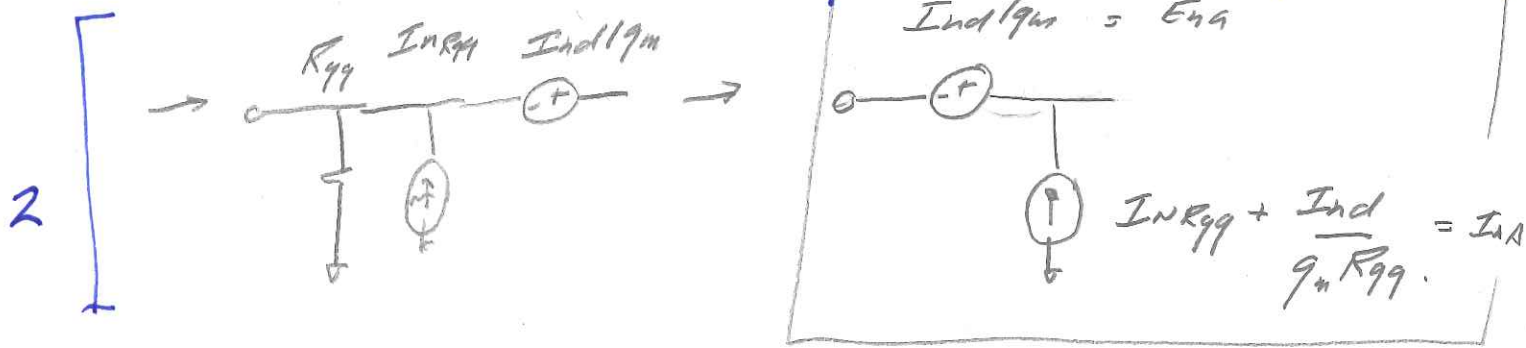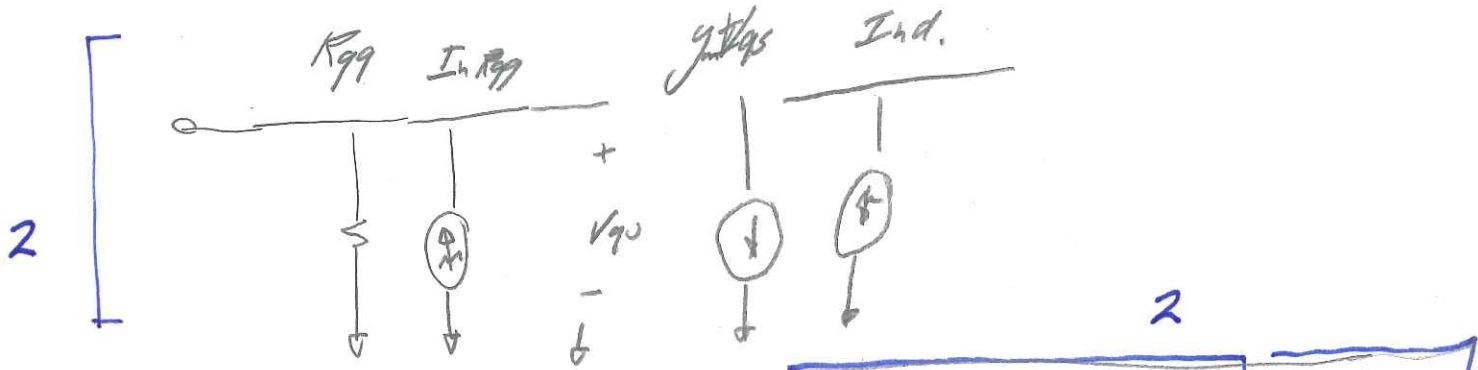expression for $S_{E_{n,a}I_{n,a}} = \frac{4kT\Gamma}{9m R_{gg}}$



1

$$S_{E_{na}} = \frac{4kT I^2 g_m}{g_m^2} = \frac{4kT I^2}{g_m}$$

1

$$S_{I_{nc}} = \frac{4kT}{R_{gg}} + \frac{4kT I^2 g_m}{g_m^2 R_{gg}^2} = \frac{4kT}{R_{gg}} + \frac{4kT I^2}{g_m R_{gg}^2}$$

2

$$S_{E_{I_{nc}}} = \frac{1}{g_m} S_{I_{nc}/I_n R_{gg}} + \frac{1}{g_m^2 R_{gg}} S_{I_{nc}}$$

$$= \frac{1}{g_m^2 R_{gg}} S_{I_{nc}} = \frac{1}{g_m^2 R_{gg}} \cdot 4kT I^2 g_m$$

$$= \frac{4kT I^2}{g_m R_{gg}}$$

Part b, 10 points

We now have a


different circuit with

$$S_{E_{na}} = 10^{-18} \text{ V}^2 / \text{Hz},$$


$$S_{I_{na}} = 10^{-22} \text{ A}^2 / \text{Hz},$$

$$\text{and } S_{E_{na}, I_{na}} = 10^{-21} \text{ W} / \text{Hz}.$$

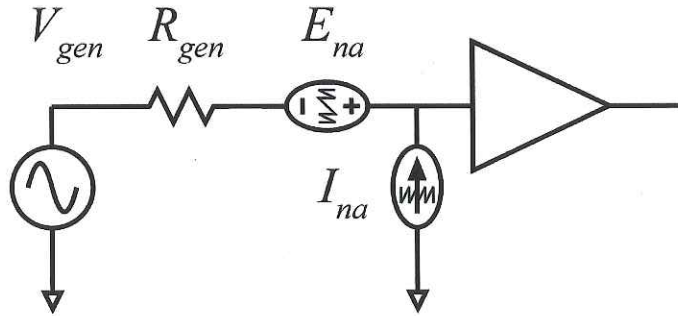If the generator resistance is 100 Ohms, find the spectral density of the total input-referred noise voltage (including that of the generator).


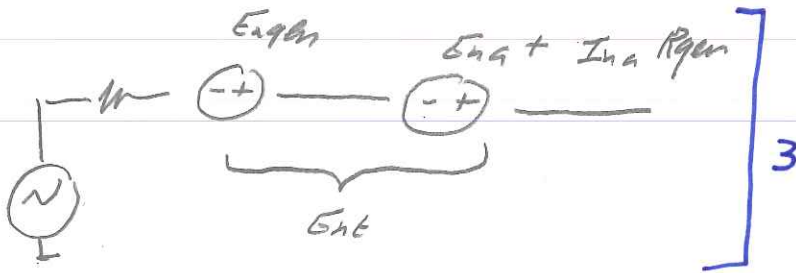
$$S_{E_{n,t}} = \underline{3.68 \cdot 10^{-18} \text{ V}^2/\text{Hz}} \quad (\text{give units})$$



$$\begin{aligned}
 S_{E_{nt}} &= 4kT R_{gen} + S_{E_{na}} + R_{gen}^2 S_{I_{na}} + 2 \cdot \text{Re} \{ S_{E_{na}, I_{na}} R_{gen} \} \\
 &= 4kT R_{gen} + S_{E_{na}} + R_{gen}^2 S_{I_{na}} + 2 R_{gen} \cdot S_{E_{na}, I_{na}} \\
 &= 1.66 \cdot 10^{-18} \text{ V}^2/\text{Hz} + 10^{-18} \text{ V}^2/\text{Hz} + 10^{-18} \text{ V}^2/\text{Hz} + 2 \cdot 10^{-19} \text{ V}^2/\text{Hz} \\
 &= 3.68 \cdot 10^{-18} \text{ V}^2/\text{Hz}
 \end{aligned}$$

Part c, 10 points


Continuing with the same circuit,
i.e.

$$S_{E_{na}} = 10^{-18} \text{ V}^2 / \text{Hz},$$

$$S_{I_{na}} = 10^{-22} \text{ A}^2 / \text{Hz},$$

and $S_{E_{na}, I_{na}} = 10^{-21} \text{ W} / \text{Hz}.$

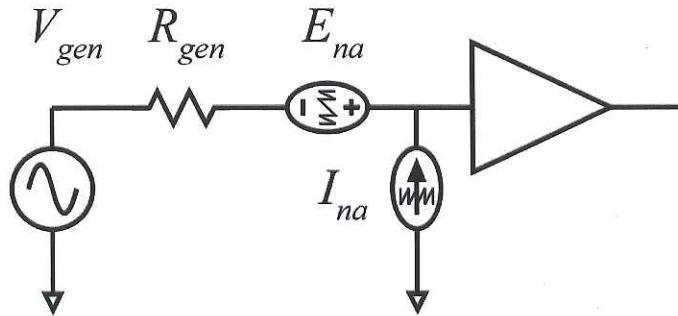If the generator resistance is 100 Ohms, find the noise figure.



noise figure = 2.33:1
(specify whether the answer is in linear units or dB)

5 [If the amplifier were not present, then

$$S_{E_{na}} = 4kTR_{gen} = 1.66 \cdot 10^{-18} \text{ V}^2 / \text{Hz}$$

5 [
$$F = \frac{3.68 \cdot 10^{-18} \text{ V}^2 / \text{Hz}}{1.66 \cdot 10^{-18} \text{ V}^2 / \text{Hz}} = \frac{3.68}{1.66}$$

$$= 2.22:1 \text{ in linear units}$$


$$= 3.47 \text{ dB}$$

Problem 4, 20 points

Signal/noise calculations

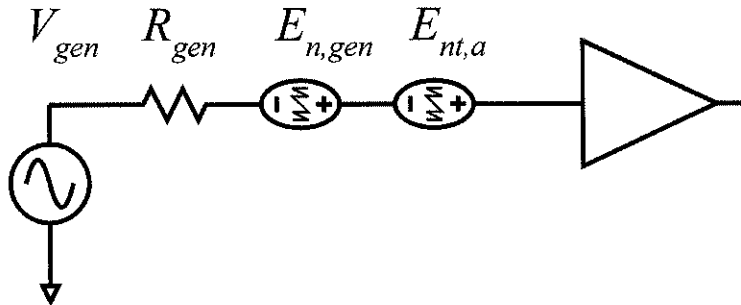Part a, 10 points


We are now analyzing a generator whose noise voltage is $E_{n,gen}$, connected to an amplifier whose total noise voltage is $E_{nt,a}$



We are working in a music recording studio, for which R_{gen} is standardized at 600 Ohms for microphones. The generator noise is thermal at 300K. $E_{nt,a}$ has a spectral density whose **square root** is 5 nV/Hz^{1/2}. Working with a standard audio system bandwidth of 20Hz-20kHz, what RMS voltage is required from V_{gen} to obtain a 30 dB signal/noise ratio? What available signal power does that correspond to?

RMS value of V_{gen} = 83.6 μ V (give units)

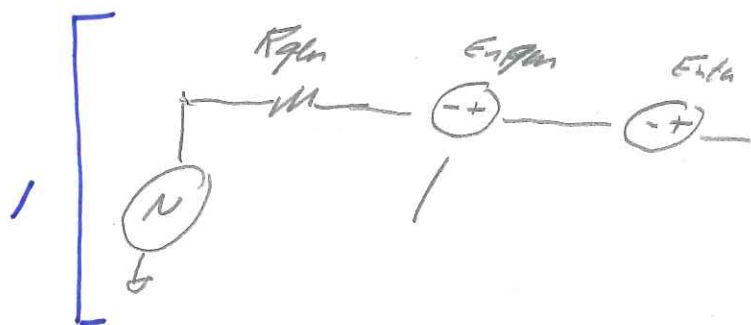Available signal power from the generator = 2.9 μ W
(give units)



$$S_{engm} = 4kTR_{gm} \stackrel{600\Omega}{=} 9.94 \cdot 10^{-18} \text{ V}^2/\text{Hz}$$

$$S_{entc} = (5 \text{ nV}/\sqrt{\text{Hz}})^2 = 25 \cdot 10^{-18} \text{ V}^2/\text{Hz}$$

$$S_{tot} = S_{engm} + S_{entc} = 3.5 \cdot 10^{-17} \text{ V}^2/\text{Hz}$$

Bandwidth = 20 kHz - 20 kHz \rightarrow approximately 20 kHz

$$E(V^2) = 3.5 \cdot 10^{-17} \text{ V}^2/\text{Hz} \cdot 2 \cdot 10^4 \text{ Hz} = 7.0 \cdot 10^{-12} \text{ V}^2$$

$$V_r = \sqrt{E(V^2)} = 2.64 \mu\text{V}$$

For 30dB SNR, we need V_{gm} 1000:1 bigger than this
 $\rightarrow V_{gm} = 83.6 \mu\text{V}$


$$\text{Power} = \frac{(83.6 \mu\text{V})^2}{4(600\Omega)} = 2.9 \cdot 10^{-12} \text{ W} = 2.9 \text{ pW}$$

Note $\frac{2.9 \text{ pW}}{20 \text{ kHz}} = 1.46 \cdot 10^{-16} \text{ W/Hz}$

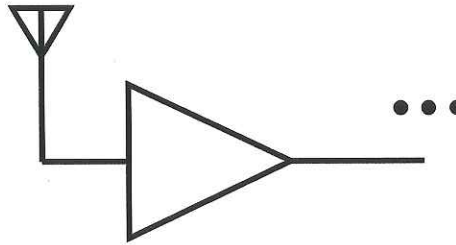Part b, 10 points

We are now analyzing a radio receiver.

The antenna radiation resistance is at 300K. The antenna has negligible conductor resistance. The amplifier has 3 dB noise figure.



The receiver is receiving QPSK data at 100 megabits/second data rate.

If we use ideal raised-cosine filters with zero excess bandwidth ($\beta=0$), what receiver bandwidth do we need?


receiver bandwidth = 100 MHz Hz

If no error-correcting code is used, we need a signal/noise ratio of 36:1 to obtain 10^{-9} bit error rate. What is the corresponding received signal power?

Signal power = -75.3 dBm (give units)
 or 30pW either answer fine.

5 [$P_s = Q^2 kT FNB$

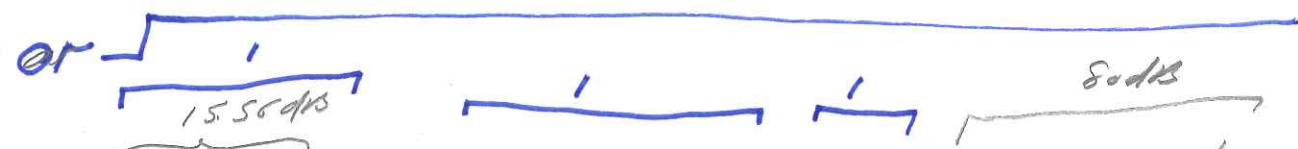5 [$= 36 \cdot kT \cdot (2) \cdot 10^6 = 3.0 \cdot 10^{-11} W = -75.3 dBm$



$P_s = 10 \log_{10}(36) - 173.8 \text{ dBm (1 Hz)} + 3 \text{ dB} + 10 \log_{10} \left(\frac{100 \text{ MHz}}{1 \text{ Hz}} \right)$

5 [$= 15.56 \text{ dB} - 173.8 \text{ dBm} + 3 \text{ dB} + 8 \text{ dB}$
 $= -75.2 \text{ dBm}$