

ECE145B (undergrad) and ECE218B (graduate)

Mid-Term Exam. February 20, 2013

Do not open exam until instructed to.

Open notes, open books, etc.

You have 1 hr. and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.), ***AFTER STATING THEM.***

Problem	Points received (145B)	Points received (218B)	Points Possible
1a			5
1b			5
1c			5
1d			5
2a			5
2b			5
2c			5
2d			5
3a		do not work	5
3b		do not work	15
3c		do not work	15
3d		do not work	5
4a	do not work		5
4b	do not work		15
4c	do not work		15
4d	do not work		5
total (145b)			80 (218 or 145)

Name: _____


Problem 1, 20 points

Radio link relationships.

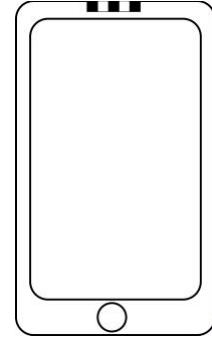Part a, 5 points


Antenna gains

Some new 5G cell phone handsets have 39 GHz transceivers. Assume a horizontal linear array, as shown, of 5 elements, each $\lambda/2$ by $\lambda/2$ (They are here drawn as alternating black & white squares).



For the overall 5 element array:

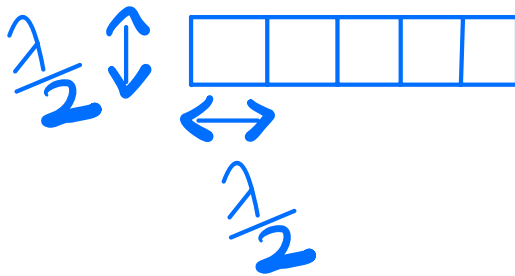What is the directivity in dB? 11.96 dB
The approximate vertical 3dB beamwidth in degrees 114.5°
The approximate horizontal 3dB beamwidth in degrees 22.9°



$$\begin{aligned} \text{Directivity} &= \frac{4\pi(\text{array area})}{\lambda^2} \\ &= \frac{4\pi(\lambda/2 \times \lambda/2 \times 5)}{\lambda^2} \\ &= 5\pi = 15.7 \\ &= \underline{11.96 \text{ dB}} \end{aligned}$$

$$\text{horizontal beamwidth} \cong \frac{\lambda}{\text{array width}} \text{ (radians)} = \frac{\lambda}{\lambda/2 \times 5} = 0.4 \text{ rad} = \underline{22.9^\circ}$$

$$\text{vertical beamwidth} \cong \frac{\lambda}{\text{array height}} = \frac{\lambda}{\lambda/2} = 2 \text{ rad} = \underline{114.5^\circ}$$

Part b, 5 points

Receiver sensitivity. Assume QPSK transmission, for which the minimum receiver power is $P_{\min} = kTFBQ^2$ where k is Boltzmann's constant, T is the absolute temperature, F is the receiver noise figure, B is the bit rate and Q^2 is the required signal/noise ratio. Simple QPSK without error-correcting codes requires $Q=3.1$ for 10^{-3} bit error rate (before error correction by coding). At the IEEE reference 290 K temperature, $kT \cdot (1\text{Hz}) = -174.0$ dBm.

Assuming 5 dB receiver noise figure, 10^{-3} bit error rate, and 1 Gb/s data transmission. What is the minimum receiver power in dBm ?

$P_{\text{received}} = \underline{-69.17}$ dBm

$$P_{\min} = kTFBQ^2$$

$$P_{\min}(\text{dBm}) = kT_{\text{dBm}} + F_{\text{dB}} + 10 \log B + 10 \log Q^2$$

$$= -174 + 5 + 90 + 9 \cdot 82$$

$$= \underline{-69.17 \text{ dBm}}$$

Part c, 5 points

Link propagation losses Assume that the transmitter is 1 km distant, and has a 64-element transmit antenna array, each being, each $\lambda/2$ by $\lambda/2$. Assume that the weather is giving 1 dB/km total atmospheric losses.

What is the transmitter directivity in dB? 23 dB
What is the required transmitter power, in dBm? 21.03 dBm

$$\begin{aligned} \text{total array area} &= \left(\frac{\lambda}{2}\right)^2 \times 64 \\ &= 16\lambda^2 \end{aligned}$$

$$\begin{aligned} \lambda &= c/f \\ &= \frac{c}{39\text{GHz}} = 7.68\text{mm} \end{aligned}$$

$$\begin{aligned} \text{Directivity} &= 4\pi \frac{(16\lambda^2)}{\lambda^2} \\ &= 64\pi \\ &= 201 \Rightarrow 23\text{dB} \end{aligned}$$

without atmospheric losses

$$\begin{aligned} \frac{P_R}{P_T} &= \frac{D_t D_r}{16\pi^2} \left(\frac{\lambda^2}{R^2}\right) \\ &= \frac{(64\pi)(5\pi)}{16\pi^2} \left(\frac{7.68 \times 10^{-3}}{10^3}\right)^2 \\ &= 20 (7.68 \times 10^{-6})^2 \\ &= 1.178 \times 10^{-9} \Rightarrow -89.2\text{dB} \end{aligned}$$

For 1km, atmospheric

attenuation is $\frac{1dB}{km} \times 1km$

$= 1dB.$

with atmospheric losses

$$\therefore P_{RdBm} - P_{TdBm}$$

$$= -89.2 - 1$$

$$= -90.2dB$$


$$P_{Tr} = P_{Rmin} + 90.2$$

$$= -69.17 + 90.2$$

$$= 21.03dBm$$

Part d, 5 points

Radio frequency plans:

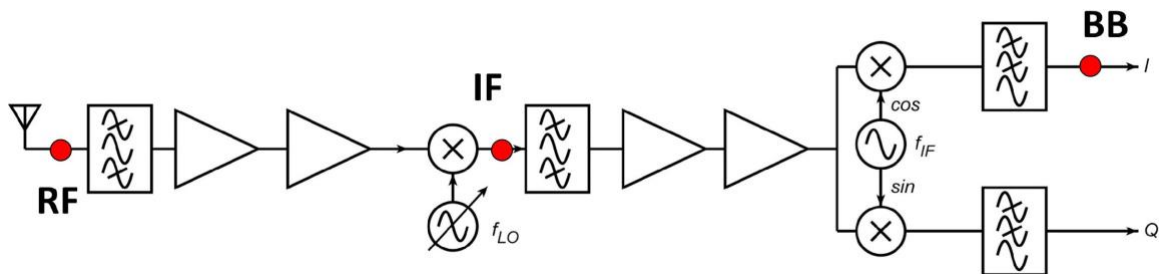

With the 39 GHz carrier, 1 Gb/s QPSK modulation, and the smallest possible bandwidth of the (root raised cosine) filter that still gives zero inter-symbol interference, make sketches below of the signal power spectral density, in W/Hz at the RF, IF, and baseband (BB) points indicated. You can use a relative scale for the vertical axis of the plots, i.e. there's no need to compute the absolute value of the spectrum in W/Hz.

$$\text{Bitrate} = 1\text{Gb/s}$$

$$\text{In QPSK 1 symbol} = 2\text{bits}$$


$$\begin{aligned}\text{Symbol rate} &= 1\text{G}/2 \\ &= 500\text{M} \frac{\text{symbols}}{\text{s}}\end{aligned}$$

Smallest possible bandwidth corresponds to beta=0 for the root raised cosine filter


$$\text{Assume } f_{LO} = 30\text{GHz}$$

$$\Rightarrow f_{IF} = 9\text{GHz}$$


RF

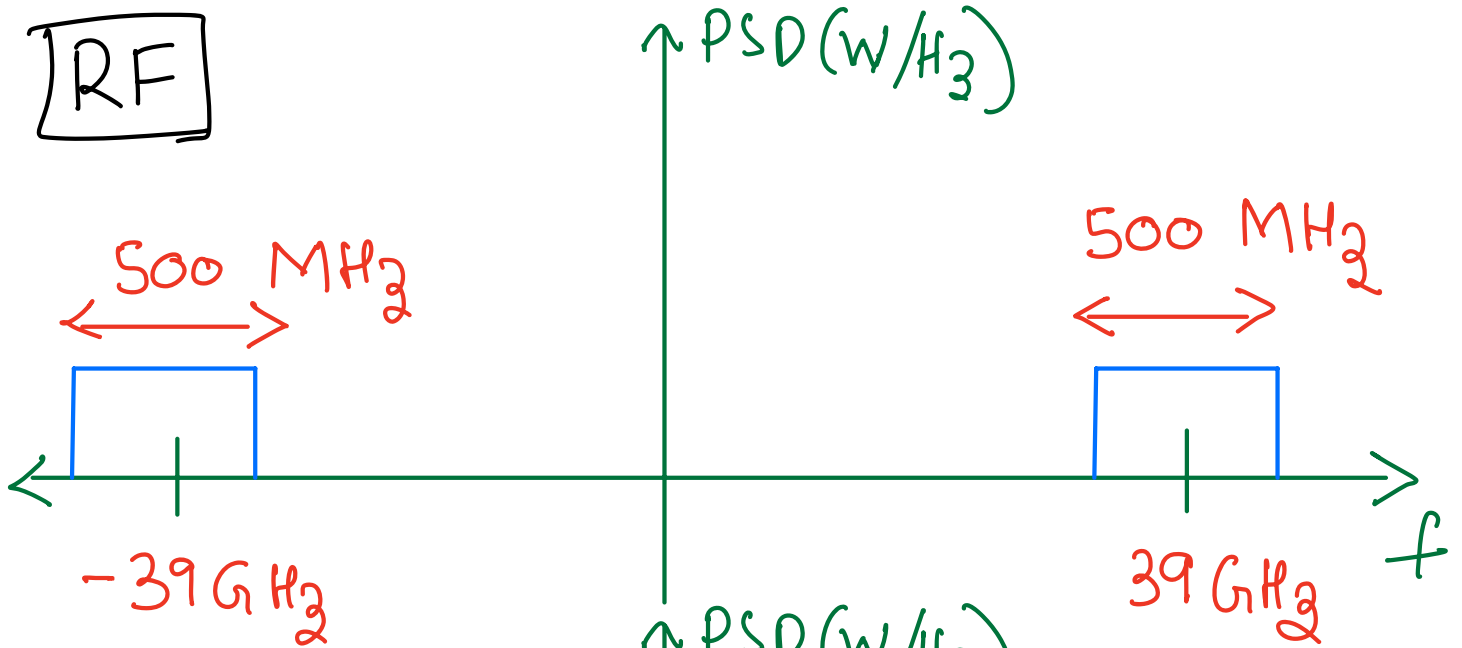

IF

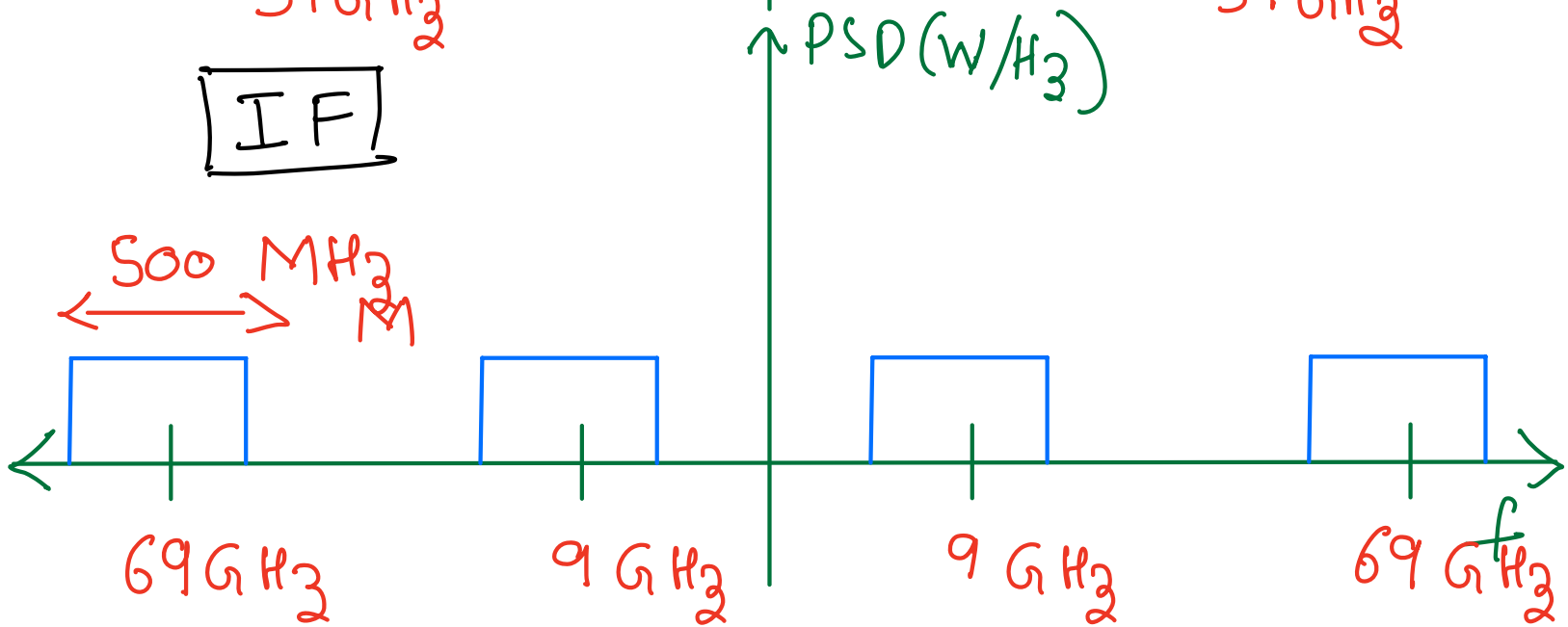

BB

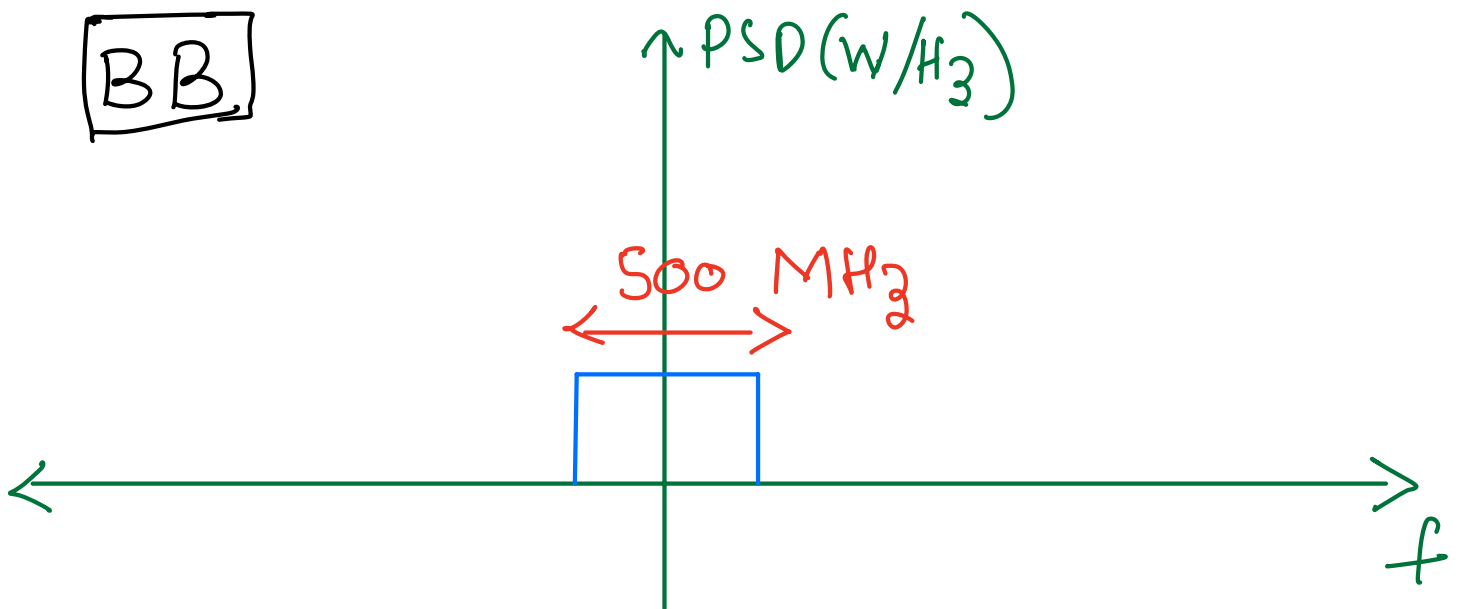

Problem 2, 20 points

basic noise math, simple circuit noise relationships


Part a, 5 points

V_{in} has a spectral density (in V^2/Hz) of

$$S_{V_{in}V_{in}} = 4kTR, \text{ where } R = 1 \text{ k}\Omega,$$

$$H_1(j2\pi f) = (1 + j2\pi f / 1\text{MHz}), \text{ and}$$
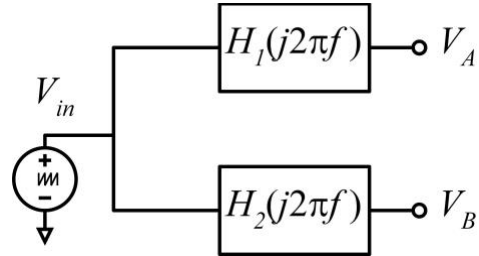
$$H_2(j2\pi f) = (1 + j2\pi f / 10\text{MHz}).$$



Write algebraic expressions for the spectral densities of V_A , V_B , and their cross spectral density

$$V_A(j2\pi f) = H_1(j2\pi f) V_{in}$$

$$V_B(j2\pi f) = H_2(j2\pi f) V_{in}$$

$$\begin{aligned} \tilde{S}_{V_A V_A} &= |H_1(j2\pi f)|^2 \tilde{S}_{V_{in} V_{in}} \\ &= \left(1 + \left(\frac{2\pi f}{1\text{MHz}} \right)^2 \right) 4kTR \end{aligned}$$

$$\begin{aligned} \tilde{S}_{V_B V_B} &= |H_2(j2\pi f)|^2 \tilde{S}_{V_{in} V_{in}} \\ &= \left(1 + \left(\frac{2\pi f}{10\text{MHz}} \right)^2 \right) 4kTR \end{aligned}$$

$$\begin{aligned}
\tilde{S}_{V_A V_B} &= V_A (j2\pi f) V_B^* (j2\pi f) \\
&= H_1 (j2\pi f) H_2^* (j2\pi f) V_{in} V_{in}^* \\
&= \left(1 + \frac{j2\pi f}{1\text{MHz}} \right) \left(1 - \frac{j2\pi f}{10\text{MHz}} \right) \tilde{S}_{V_{in} V_{in}} \\
&= \left(1 + \frac{(2\pi f)^2}{10 (1\text{MHz})^2} + j \frac{(18\pi f)}{10\text{MHz}} \right) 4kTR
\end{aligned}$$

part b, 5 points

A voltage $V_3 = V_1 + V_2$ is the sum of two voltages V_1 and V_2 , both of which are random processes. If V_1 has a power spectral density of $3 \cdot 10^{-16} \text{ V}^2/\text{Hz}$, V_2 has a power spectral density of $2 \cdot 10^{-16} \text{ V}^2/\text{Hz}$, and the cross spectral density of V_1 and V_2 is $10^{-16} \text{ V}^2/\text{Hz}$, what is the spectral density of V_3 ?

Spectral density of $V_3 = \underline{7 \times 10^{-16}} \text{ (V}^2/\text{Hz)}$

$$V_3 = V_1 + V_2$$



$$\begin{aligned}\tilde{S}_{V_3V_3} &= (V_1 + V_2)(V_1 + V_2)^* \\ &= V_1V_1^* + V_1V_2^* + V_2V_1^* + V_2V_2^* \\ &= \tilde{S}_{V_1V_1} + 2\text{Re}\left(\tilde{S}_{V_1V_2}\right) + \tilde{S}_{V_2V_2} \\ &= 3 \times 10^{-16} + 2 \times 10^{-16} + 2 \times 10^{-16} \\ &= 7 \times 10^{-16} \frac{\text{V}^2}{\text{Hz}}\end{aligned}$$

"

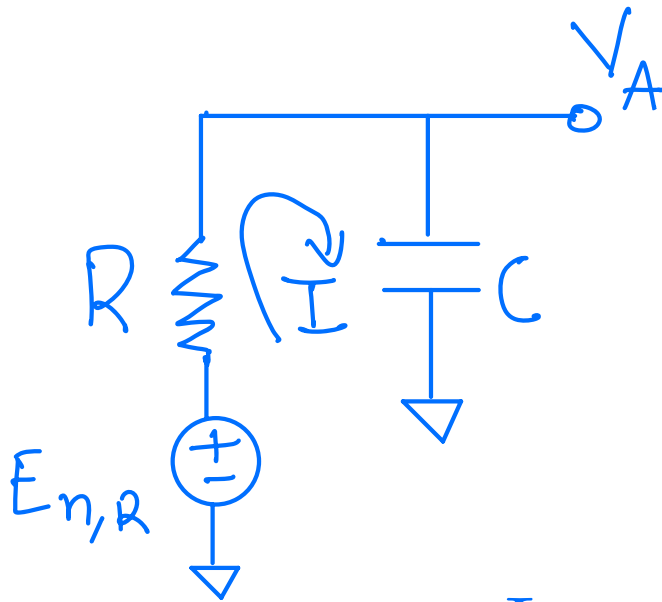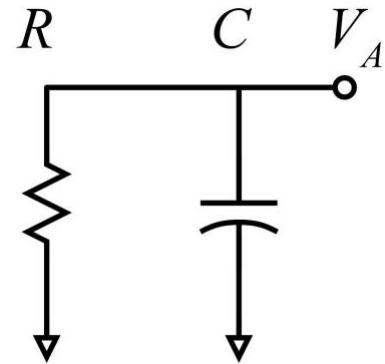Part c, 5 points

The resistor R has normal thermal noise. Calculate an expression for the spectral density of V_A in units of V^2/Hz .

$$S_{V_A, V_A} = \frac{4kTR}{1 + (2\pi fRC)^2} \quad (\text{V}^2/\text{Hz})$$



$$I = \frac{E_{n,R}}{R + \frac{1}{j2\pi fC}}$$

$$V_A = I \left(\frac{1}{j2\pi fC} \right)$$

$$= \frac{E_{n,R}}{1 + j2\pi fCR}$$

$$\begin{aligned}\tilde{S}_{V_A V_A} &= \frac{E_{n,R} E_{n,R}^*}{1 + (2\pi f C R)^2} \\ &= \frac{4kTR}{1 + (2\pi f RC)^2}\end{aligned}$$





Part d, 5 points

The current source I_0 is noiseless, and its current is much larger than that of the ideal PN junction diode having characteristics $I_{diode} = I_s (\exp(qV / kT) - 1)$.

Calculate an expression for the spectral density of V_A in units of V^2/Hz .
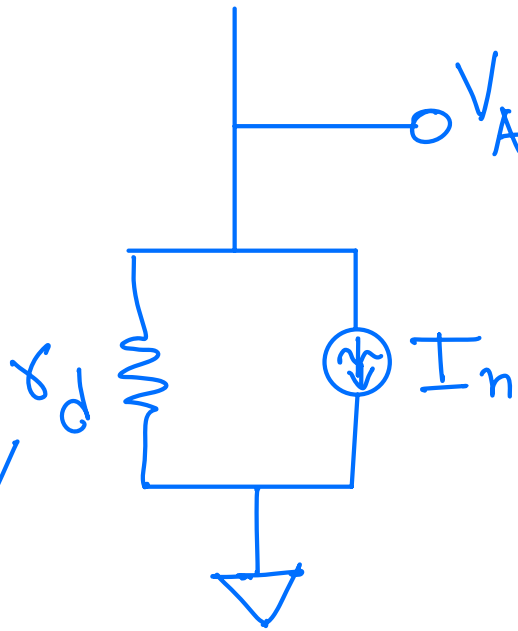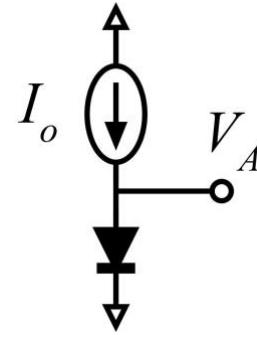
$$S_{V_A V_A} = \underline{2kTr_d} \quad (V^2/Hz)$$



$$\frac{\partial I_{diode}}{\partial V} = \frac{q}{kT} (I_s \exp\left(\frac{qV}{kT}\right))$$

$$\frac{1}{r_d} \simeq \frac{qI_0}{kT} \Rightarrow r_d = \frac{kT}{qI_0}$$

$$S_{I_n I_n} = 2qI_0$$

$$V_A = I_n r_d$$


$$S_{v_{AV_A}} = I_n I_n^* r_d^2$$

$$= 2qI_0 \left(\frac{kT}{qI_0}\right)^2 = \underline{\underline{2kTr_d}}$$

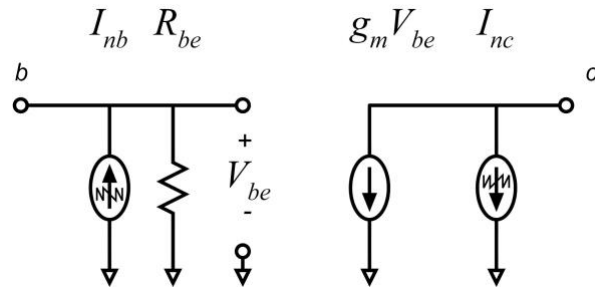Problem 3, 60 points: 145B only

Transistor noise derivation (145B only)

This is a low-frequency noise equivalent circuit model of a bipolar transistor with no parasitic resistances. I_{nb} and I_{nc} are the base and collector shot noise generators, and $R_{be} = \beta / g_m$, where $g_m = qI_{E,dc} / kT$. Note that R_{be} has no thermal noise.



Part a, 5 points (145B only)

Setting $\beta = 100$ and $I_{E,dc} = 1\text{mA}$, first determine the spectral densities below:

$$\text{base shot noise } S_{I_{nb}I_{nb}} = \frac{3.2 \cdot 10^{-24}}{\text{A}^2/\text{Hz}} \text{ (A}^2/\text{Hz)}$$

$$\text{collector shot noise } S_{I_{nc}I_{nc}} = \frac{3.2 \cdot 10^{-22}}{\text{A}^2/\text{Hz}} \text{ (A}^2/\text{Hz)}$$

Collector Shot noise

$$S_{I_c} = 2qI_c = 3.2 \cdot 10^{-22} \text{ A}^2/\text{Hz}$$


base shot noise

$$I_b = I_c / \beta = 10 \mu\text{A}$$

$$S_{I_b} = 2qI_b = 3.2 \cdot 10^{-24} \text{ A}^2/\text{Hz}$$

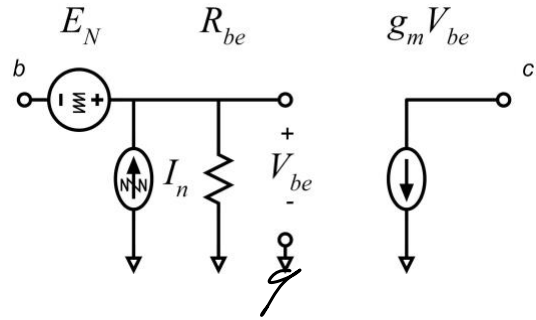Part b, 15 points (145B only)

The transistor's internal noise generators can be modelled by an external short-circuit noise voltage E_N and short-circuit noise current I_N





Determine the spectral densities below:

Short circuit input noise voltage spectral density $S_{E_N E_N} = 2 \cdot 10^{-19} \text{ (V}^2/\text{Hz)}$


Open circuit input noise current spectral density $S_{I_N I_N} = 3.24 \cdot 10^{-24} \text{ (A}^2/\text{Hz)}$

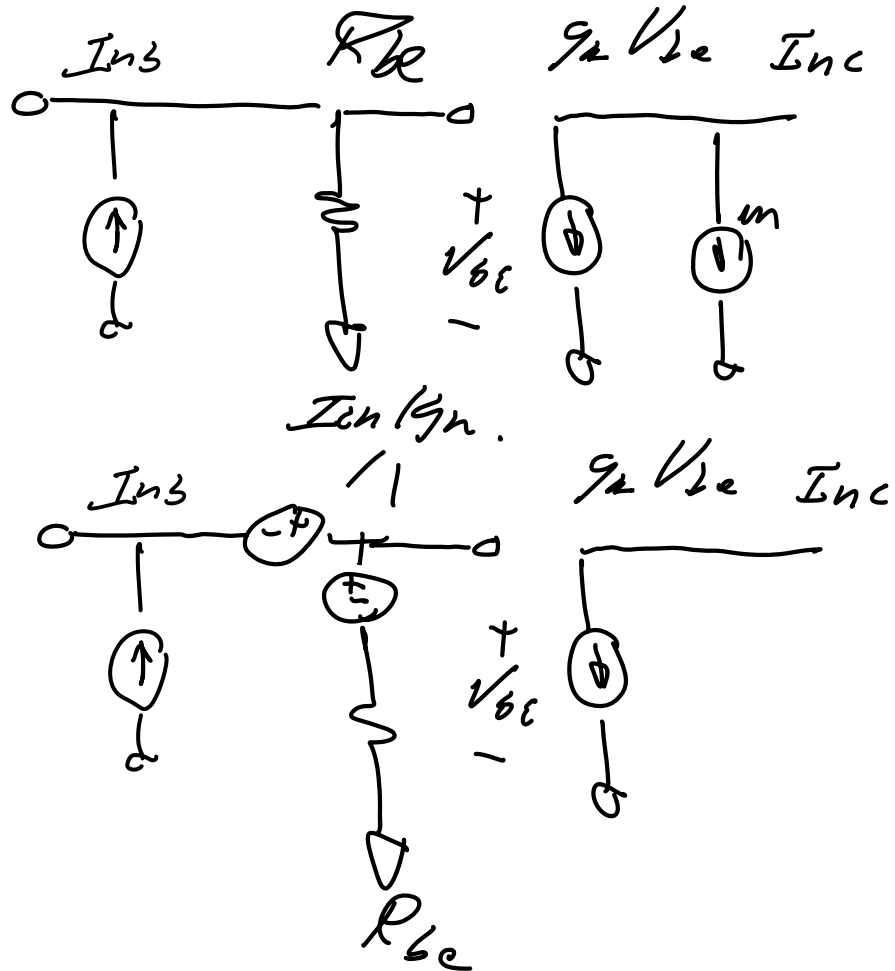Cross spectral density $S_{E_N I_N} = 8.0 \cdot 10^{-23} \text{ (V} \cdot \text{A}/\text{Hz)}$



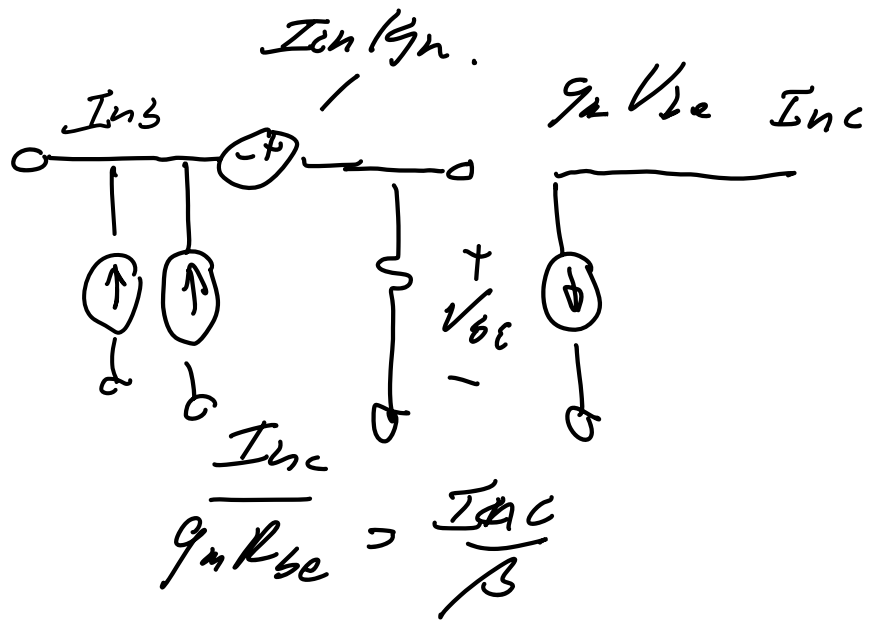

$$S_{I_n} = I_{in} I_{in}$$

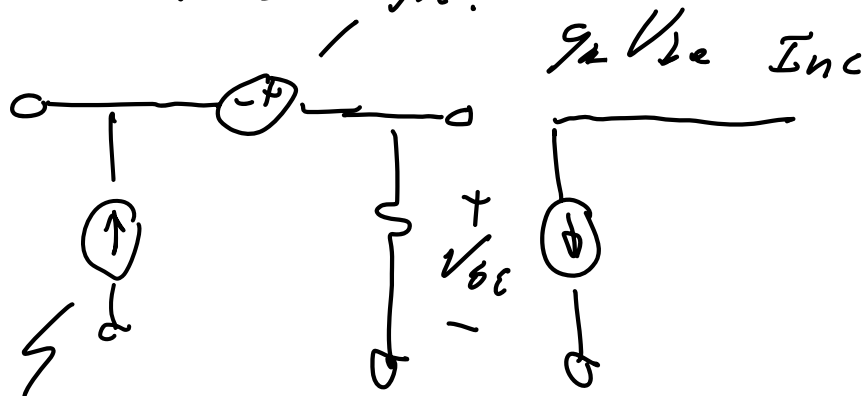

$$I_{in} = I_{nb} + I_{nc} / \beta$$

$$S_{I_n} = S_{I_{nc}} \frac{1}{\beta^2} = 2q I_c \frac{kT}{q I_c} \frac{kT}{q I_c}$$

$$= 2kT / q_m = 2kT (kT / q I_c)$$

$$= 2 \cdot 10^{-19} \text{ V}^2 / \text{Hz}$$

$$S_{I_n} = 2q I_b + 2q I_c / \beta^2$$

$$= 3.24 \cdot 10^{-24} \text{ A}^2 / \text{Hz}$$

$$E_n I_n^* = \frac{I_{nc}}{g_m} \left(I_{nb}^* + \frac{I_{nc}^*}{\beta} \right)$$

$$= \frac{I_{nc} I_{nb}^*}{g_m} + \frac{I_{nc} I_{nc}^*}{g_m \beta}$$


$$S_{bn I_n} = \frac{2g I_c}{g_m \beta} = 8.0 \cdot 10^{-23} \text{ W/Hz}$$

Part c, 15 points (145B only)

If we now connect the transistor to a generator of source impedance $Z_{gen} = R_{gen} + j0\Omega$, with

$R_{gen} = 100\Omega$, we have a generator noise $E_{N,gen}$ with spectral density $4kTR_{gen}$ and amplifier

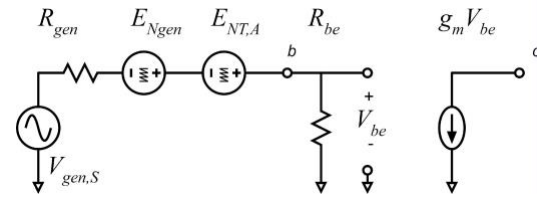total noise voltage $E_{NT,A} = E_N + I_N R_{gen}$



Determine the spectral densities below:

Spectral density of the generator noise voltage $S_{E_{N,gen}E_{N,gen}} = \frac{1.6 \cdot 10^{-18}}{1} \text{ (V}^2/\text{Hz)}$

Spectral density of the amplifier total noise voltage $S_{E_{NT,A}E_{NT,A}} = \frac{2.4 \cdot 10^{-19}}{1} \text{ (V}^2/\text{Hz)}$

$$E_{nta} = E_n + I_n R_{gen}$$

$$S_{ent, A} = S_{E_n} + S_{I_n} R_{gen}^2 + 2 \operatorname{Re} [S_{E_n I_n} R_{gen}]$$

$$= 2.0 \cdot 10^{-19} \text{ V}^2/\text{Hz}$$

$$+ 3.24 \cdot 10^{-24} \text{ A}^2/\text{Hz} \cdot (100\Omega)^2$$

$$+ 2 \cdot [8 \cdot 10^{-23} \text{ VA}/\text{Hz}] \cdot 100\Omega$$

$$= 2.4 \cdot 10^{-19} \text{ V}^2/\text{Hz}$$

$$S_{E_{n,gen}} = 4kT R_{gen} = 1.6 \cdot 10^{-18} \text{ V}^2/\text{Hz}$$

Part d, 5 points (145B only)

What is the resulting noise figure, F in linear units and dB?

F in linear units = 1.15

F in dB = 0.607


$$F = 1 + \frac{S_{\text{en, amp, total}}}{S_{\text{en, gen}}}$$
$$= 1 + \frac{2.4 \cdot 10^{-14} \text{ V}^2/\text{Hz}}{1.6 \cdot 10^{-15} \text{ V}^2/\text{Hz}}$$
$$= 1.15 \text{ (linear)}$$

$$F = 0.607 \text{ dB}$$

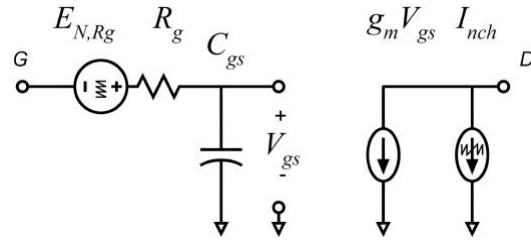Problem 4, 60 points: 218B only

Transistor noise derivation (218B only).

This is a simple high-frequency noise equivalent circuit model of a FET. E_{NRg} is the thermal noise of the gate (and other input resistances) and I_{nch} is the channel noise generator, having spectral density $4kT\Gamma g_m$, here taking $\Gamma = 2/3$.



Part a, 5 points (218B only)

Setting $g_m = 100 \text{ mS}$, $C_{gs} = g_m / 2\pi f_\tau$, where $f_\tau = 100 \text{ GHz}$ and $R_g = 10\Omega$ first determine the spectral densities below:

Gate resistance thermal noise voltage $S_{E_{NRg}E_{NRg}} = \frac{1.6 \cdot 10^{-19}}{\text{V}^2/\text{Hz}}$

channel thermal noise $S_{I_{nch}I_{nch}} = \frac{1.07 \cdot 10^{-21}}{\text{A}^2/\text{Hz}}$


$$S_{E_{NRg}} = 4kTR_g = 4kT \cdot 10\Omega$$

$$= 1.6 \cdot 10^{-19} \text{ V}^2/\text{Hz}$$

$$S_{I_{nch}} = 4kT\Gamma g_m = 1.07 \cdot 10^{-21} \text{ A}^2/\text{Hz}$$

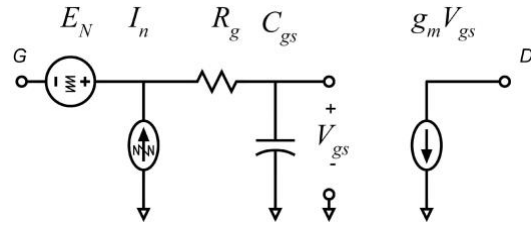Part b, 15 points (218B only)

The transistor's internal noise generators can be modelled by an external short-circuit noise voltage E_N and short-circuit noise current I_N




At a frequency of 10 GHz, determine the spectral densities below:


Short circuit input noise voltage spectral density $S_{E_N E_N} = 2.7 \cdot 10^{-19} \text{ (V}^2/\text{Hz)}$

Open circuit input noise current spectral density $S_{I_N I_N} = 1.07 \cdot 10^{-23} \text{ (A}^2/\text{Hz)}$

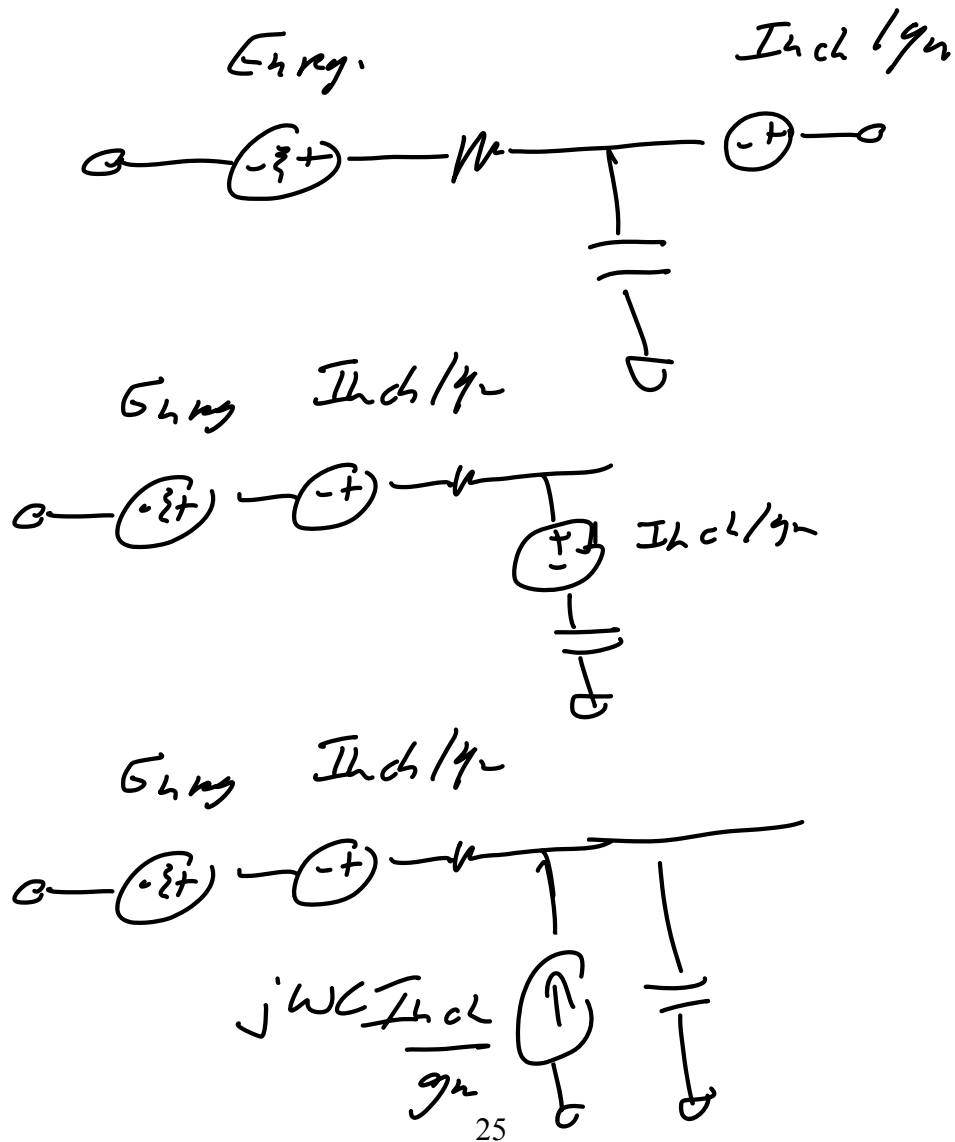
Cross spectral density $S_{E_N I_N} = \left(1.07 \cdot 10^{-22} - j 1.07 \cdot 10^{-21} \right) \text{ A}^2/\text{Hz}$




Без инд/к

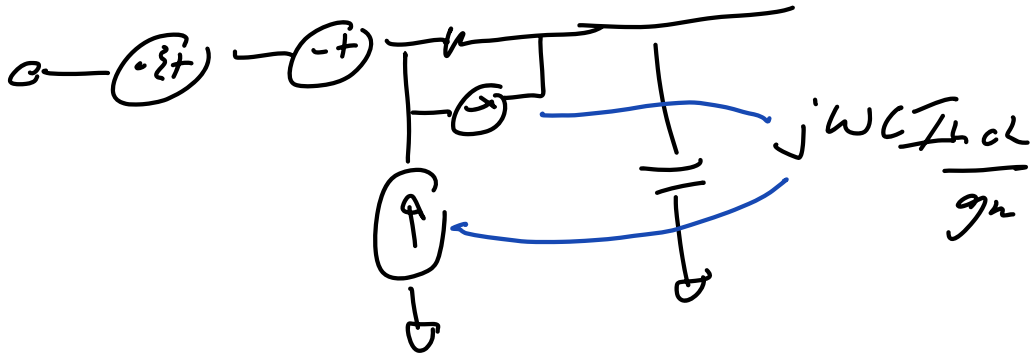

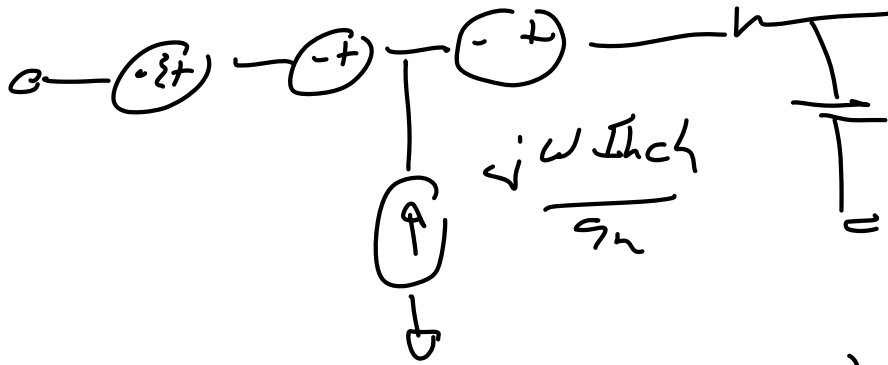Без инд/к / $\frac{j\omega R_g I_{nch}}{g_n}$


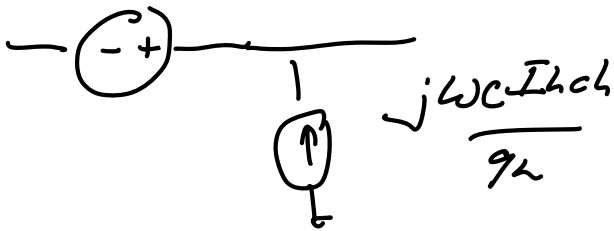
$$E_{nrg} + (I_{nch} / g_n) (1 + j\omega C R_g)$$



$$S_{G_n} = 4kT R_g + \frac{4kT I^2}{g_n} (1 + \omega^2 C^2 R_g^2)$$

$$= 2.68 \cdot 10^{-19} \text{ V}^2/\text{Гц}$$

$$S_{I_n} = \frac{4kT I^2}{g_n} (\omega C)^2 = 1.07 \cdot 10^{-23} \text{ A}^2/\text{Гц}$$

$$S_{G_n, I_n} = \frac{4kT I^2}{g_n} (1 + j\omega C R_g) (-j\omega C)$$


$$S_{\text{Gen}}^* = \frac{4kT\Gamma}{g_m} (\omega^2 C^2 R_g - j\omega C)$$
$$= 1.07 \cdot 10^{-22} - j \cdot 1.07 \cdot 10^{-21} \text{ A}\cdot\text{V}/\text{Hz}$$

Part c, 15 points (218B only)

If we now connect the transistor to a generator of source impedance $Z_{gen} = R_{gen} + j0\Omega$, with

$R_{gen} = 100\Omega$, we have a generator noise $E_{N,gen}$ with spectral density $4kTR_{gen}$ and amplifier

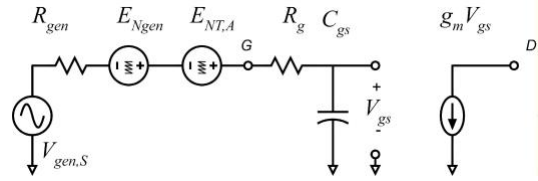total noise voltage $E_{NT,A} = E_N + I_N R_{gen}$



At a frequency of 10 GHz, determine the spectral densities below:

Spectral density of the generator noise voltage $S_{E_{N,gen}E_{N,gen}} = 1.6 \cdot 10^{-18} \text{ (V}^2/\text{Hz)}$

Spectral density of the amplifier total noise voltage $S_{E_{NT,A}E_{NT,A}} = 3.96 \cdot 10^{-19} \text{ (V}^2/\text{Hz)}$

$$S_{gen} = 4kTR_{gen} = 1.60 \cdot 10^{-18} \text{ V}^2/\text{Hz}$$

$$E_{nt,A} = E_{n,A} + I_{n,A} R_{gen}$$

$$\begin{aligned} S_{G_{nt,c}} &= S_{E_{n,A}} + S_{I_{n,A}} \cdot R_{gen}^2 + 2\text{Re}[S_{E_{n,A}I_{n,A}}] \cdot R_{gen} \\ &= 2.68 \cdot 10^{-19} \text{ V}^2/\text{Hz} \\ &\quad + 1.07 \cdot 10^{-19} \text{ V}^2/\text{Hz} \\ &\quad + 2.13 \cdot 10^{-20} \text{ V}^2/\text{Hz} = 3.96 \cdot 10^{-19} \text{ V}^2/\text{Hz} \end{aligned}$$

Part d, 5 points (218B only)

What is the resulting noise figure, F in linear units and dB?

F in linear units = 1.25

F in dB = 0.96

$$F = 1 + \frac{3.96 \cdot 10^{-19} \text{ V}^2/\text{Hz}}{1.6 \cdot 10^{-18} \text{ V}^2/\text{Hz}} = 1.25 \text{ or } \underline{\underline{0.96 \text{ dB}}}$$