

# ***ECE 145B / 218B, notes set 10: Oscillators, Part 2.***

***Mark Rodwell***

***University of California, Santa Barbara***

rodwell@ece.ucsb.edu 805-893-3244, 805-893-3262 fax

# Two-Port Oscillator Theory

---

Why ?

Selection of oscillator topology seems ad - hoc.

Is there any reason to pick a particular topology?

Many standard oscillators will not oscillate at  $f_{\max}$  !

Is "maximum frequency of oscillation" an oxymoron ?

Or are we not designing our oscillators well ?

Two - port theory will answer this.

# Two-Port Oscillator Theory


Take an active 2-port (transistor, etc)

It has power gain for  $0 < f < f_{\max}$ .

Now impedance-match on input and output.

If  $f < f_{\max}$ , then  $S_{11,\text{matched}} = S_{22,\text{matched}} = 0$  and


$S_{21,\text{matched}} = \|S_{21,\text{matched}}\| e^{j\phi}$  with  $\|S_{21,\text{matched}}\| > 1$

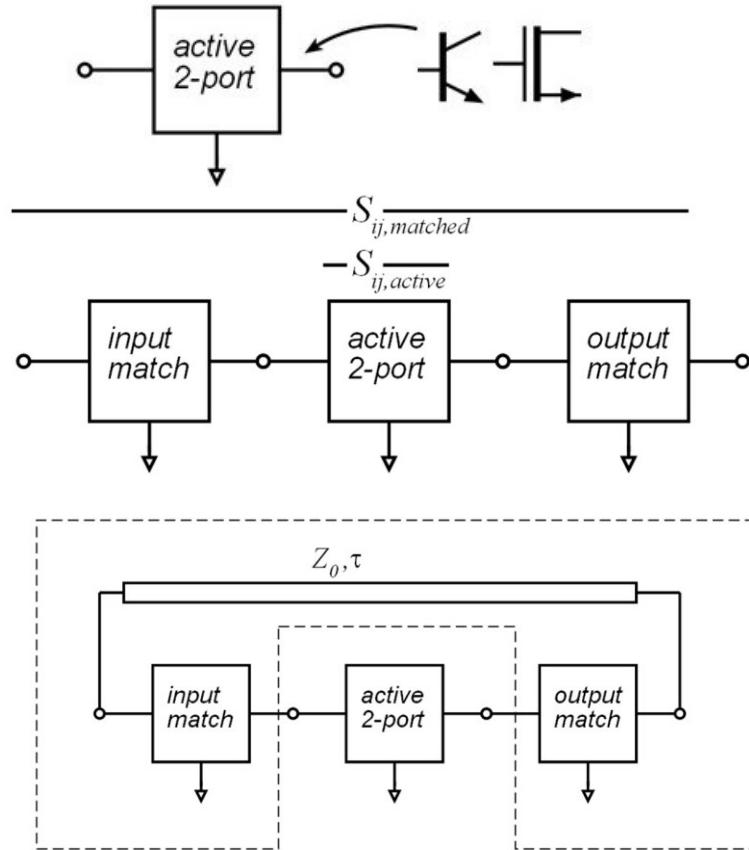

Add a transmission line of time delay  $\tau$  hence phase shift  $-j\omega\tau$ , such that  $\phi - j\omega\tau = n2\pi = n(360^\circ)$ .

The feedback loop has loop transmission  $T = \|T\| e^{j\theta_T}$  with  $\theta_T = 0$  and  $\|T\| > 1$ , hence the circuit will oscillate.

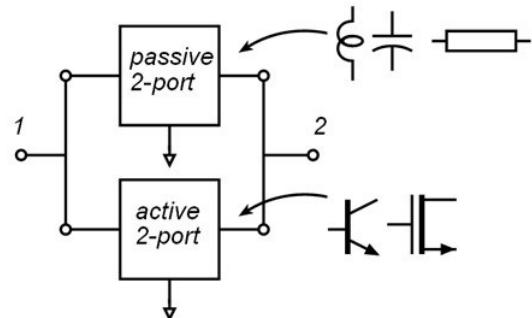
The combination of the 2 matching networks and the transmission-line is simply a 2-port network. Hence, for  $f < f_{\max}$ , a transistor will oscillate if connected to the appropriate 2-port network


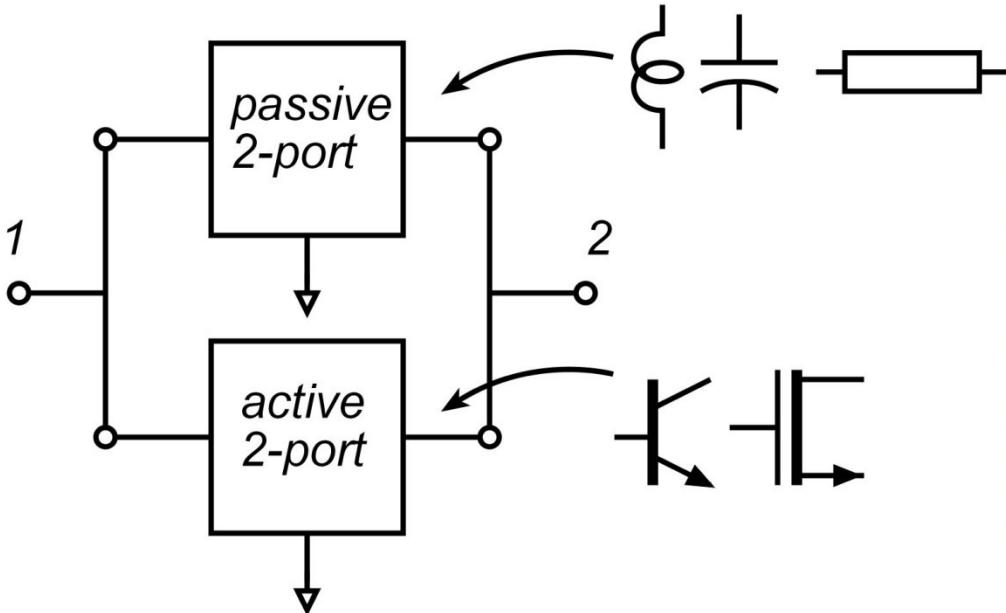
# Two-Port Oscillator Theory

Take an active 2 - port  
(transistor, etc)

..and add feedback with  
a passive 2 - port.



The passive 2 - port should clearly be lossless

The feedback is completely general.


We are analyzing all possible 1 - transistor oscillators

# Two-Port Oscillator Theory

---


Passive network :  $Y_{p,ij}$  ; this is reciprocal.

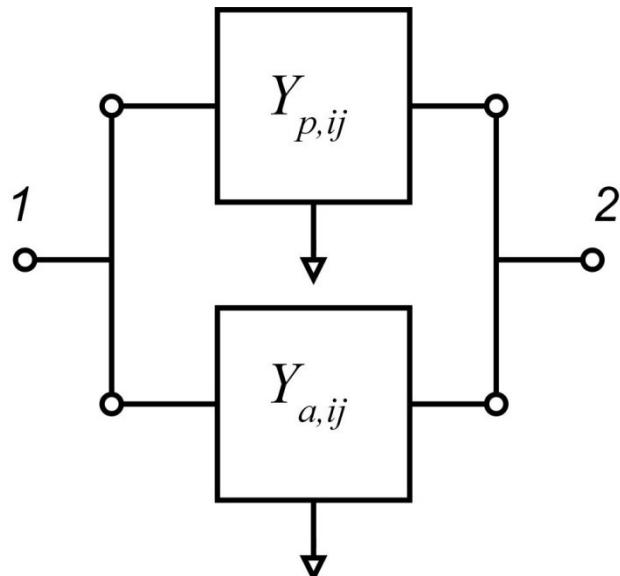Active network :  $Y_{a,ij}$  ; possibly not reciprocal



Note that the ground connection  
can be placed at nodes 1, 2, or 3.

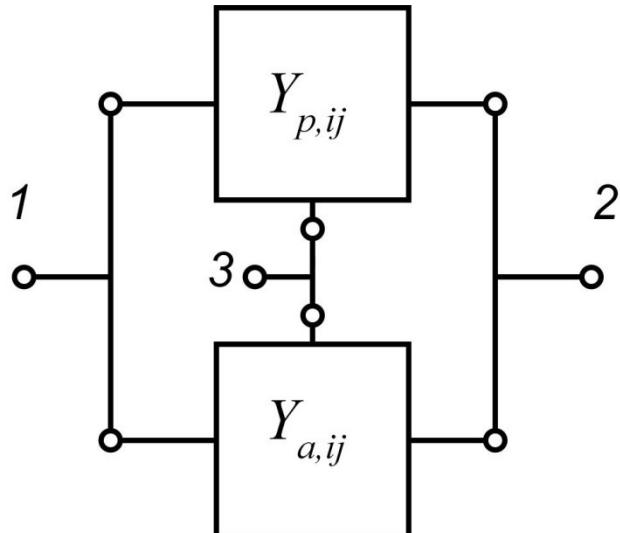This transforms oscillator from  
common - base to common - emitter,  
etc.



# The feedback network


The feedback network can be represented by either  $Y_{p,ij}$  or  $Z_{p,ij}$ .

It can be composed of either a T or a Pi network.

The Pi network is also known as a Delta network

More complex networks can be used, but are equivalent.

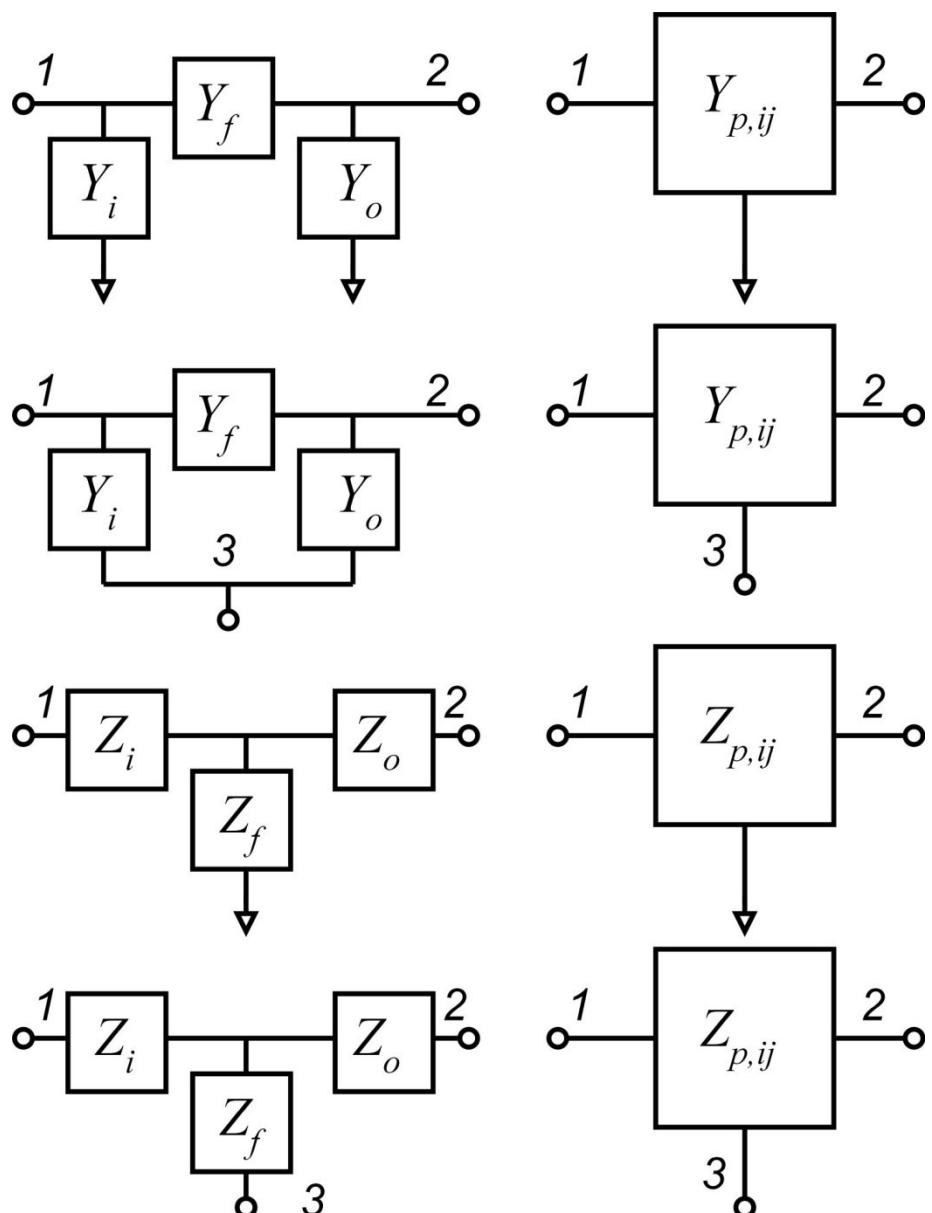Note that the feedback impedances and admittances are purely imaginary.



# The feedback network

$$\begin{bmatrix} Y_{ij,p} \\ Y_{ij,p} \end{bmatrix} = \begin{bmatrix} Y_i + Y_f & -Y_f \\ -Y_f & Y_o + Y_f \end{bmatrix}$$

$$Y_f = -Y_{p,12}$$

$$Y_i = Y_{p,11} - Y_{p,12}$$

$$Y_o = Y_{p,22} - Y_{p,12}$$


$$\begin{bmatrix} Z_{ij,p} \\ Z_{ij,p} \end{bmatrix} = \begin{bmatrix} Z_i + Z_f & -Z_f \\ -Z_f & Z_o + Z_f \end{bmatrix}$$

$$Z_f = -Z_{p,12}$$


$$Z_i = Z_{p,11} - Z_{p,12}$$

$$Z_o = Z_{p,22} - Z_{p,12}$$

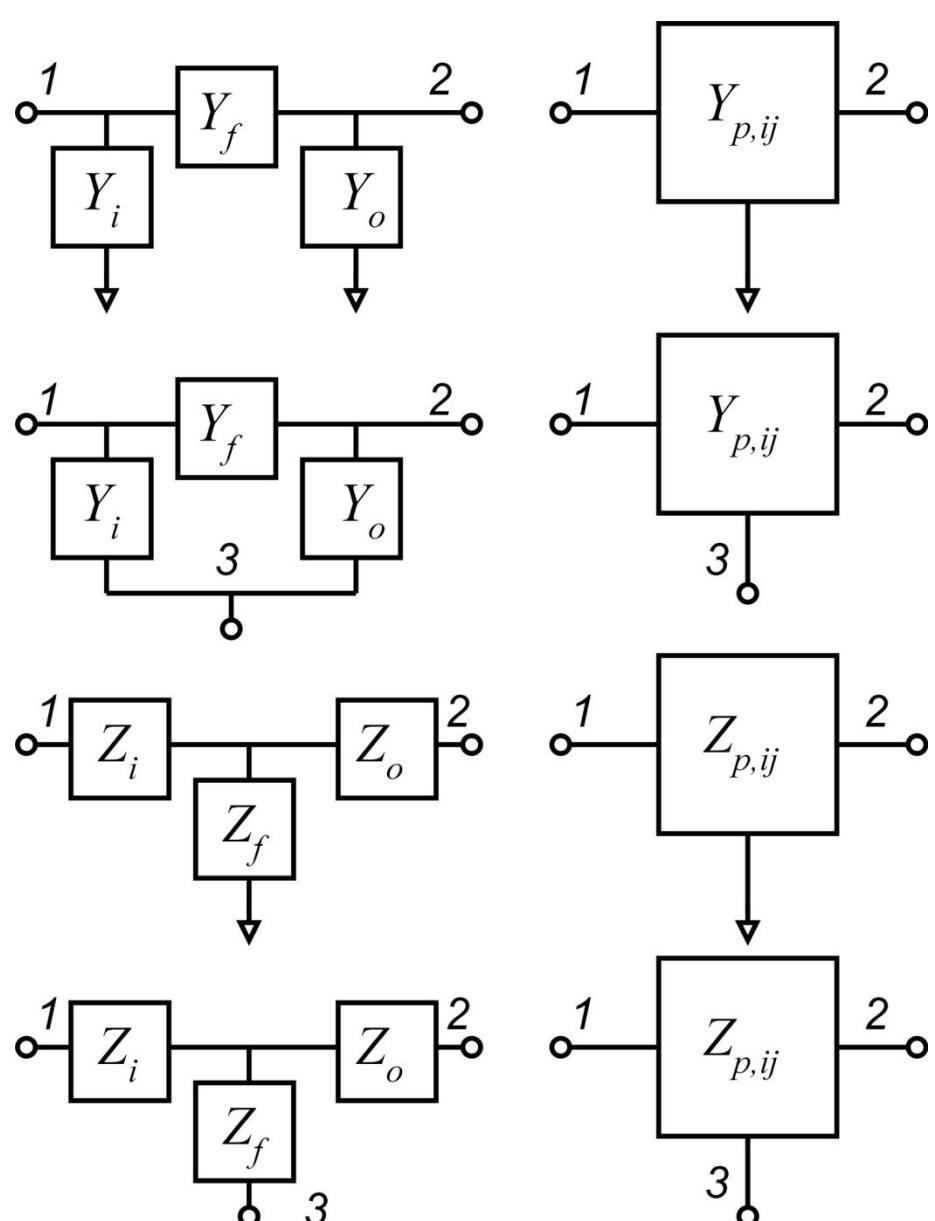
Note that the feedback impedances and admittances are purely imaginary.



# Series-Line-Tuned Oscillator

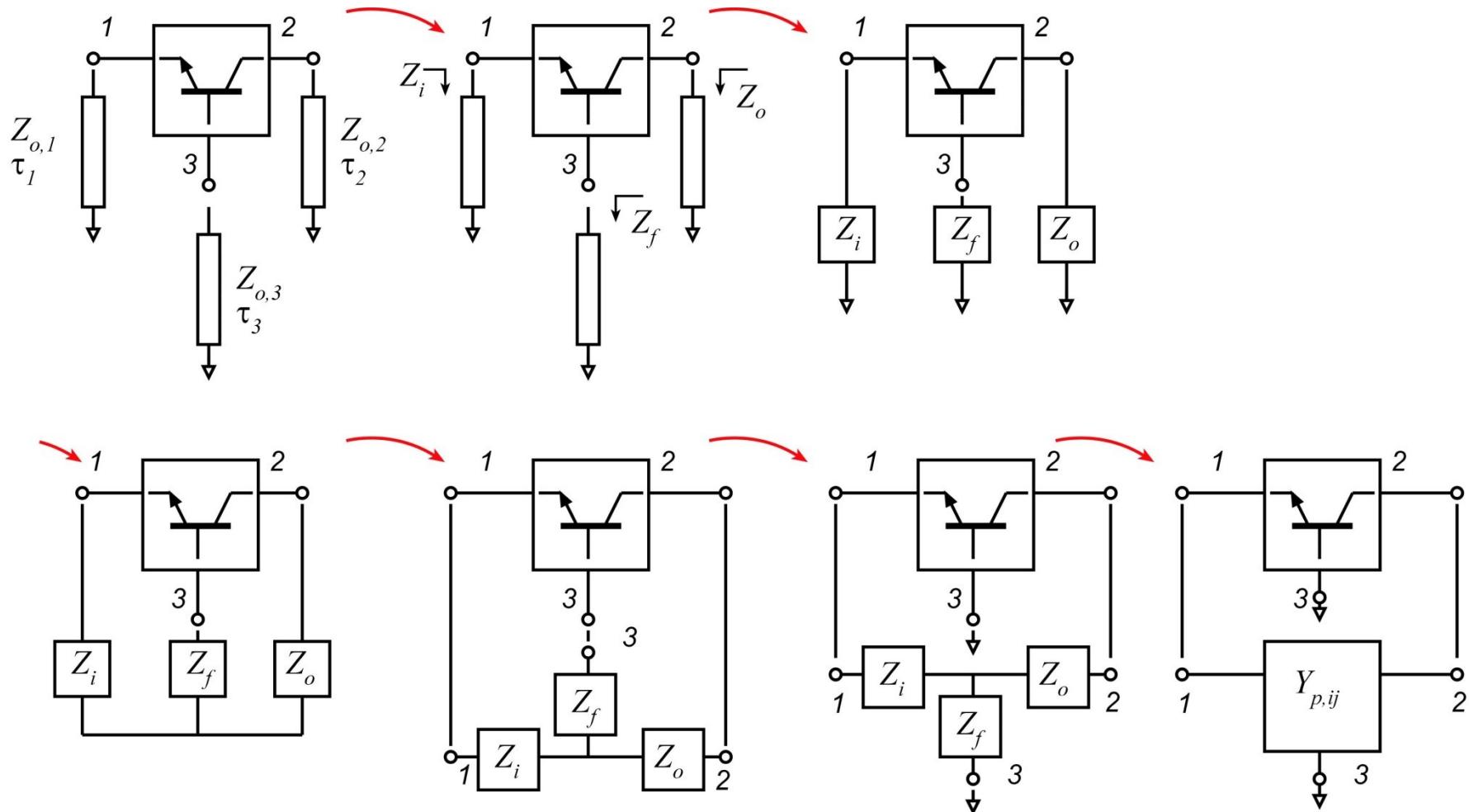


# Shunt-Line-Tuned Oscillator

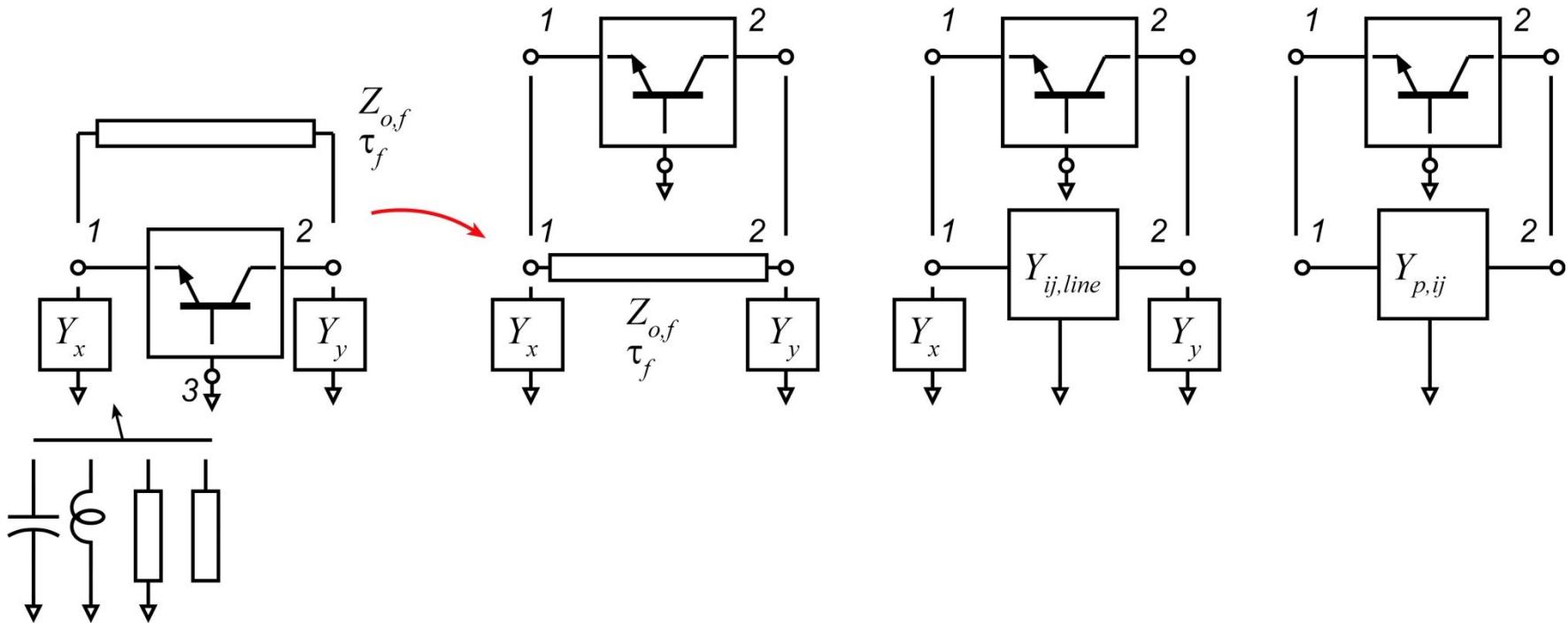
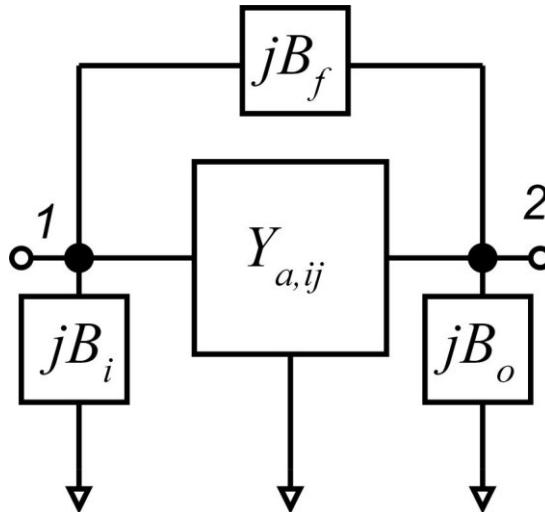
# The Oscillator

Active device

$$\begin{bmatrix} Y_{a,ij} \end{bmatrix} = \begin{bmatrix} G_{a,11} + jB_{a,11} & G_{a,12} + jB_{a,12} \\ G_{a,21} + jB_{a,21} & G_{a,22} + jB_{a,22} \end{bmatrix}$$



Oscillator

$$\begin{bmatrix} Y_{osc,ij} \end{bmatrix} = \begin{bmatrix} G_{a,11} + jB_{a,11} + jB_i + jB_f & G_{a,12} + jB_{a,12} - jB_f \\ G_{a,21} + jB_{a,21} - jB_f & G_{a,22} + jB_{a,22} + jB_o + jB_f \end{bmatrix} = \begin{bmatrix} Y_{osc,11} & Y_{osc,12} \\ Y_{osc,21} & Y_{osc,22} \end{bmatrix}$$

Simplify: write this as

$$\begin{bmatrix} Y_{osc,ij} \end{bmatrix} = \begin{bmatrix} G_{a,11} + jB_{11} & G_{a,12} + jB_{a,12} - jB_f \\ G_{a,21} + jB_{a,21} - jB_f & G_{a,22} + jB_{22} \end{bmatrix}$$

By adjusting the feedback network, we can set  $B_{11}$ ,  $B_{22}$ , and  $B_f$  to any value we desire.

# Oscillator Input Admittance


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{osc,11} & Y_{osc,12} \\ Y_{osc,21} & Y_{osc,22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_2 = 0 \rightarrow V_2 = -(Y_{osc,21} / Y_{osc,22})V_1$$

$$\rightarrow Y_{in} = Y_{osc,11} - (Y_{osc,12} Y_{osc,21} / Y_{osc,22})$$

$$\begin{bmatrix} Y_{osc,ij} \\ Y_{osc,ij} \end{bmatrix} = \begin{bmatrix} G_{a,11} + jB_{11} & G_{a,12} + jB_{a,12} - jB_f \\ G_{a,21} + jB_{a,21} - jB_f & G_{a,22} + jB_{22} \end{bmatrix}$$
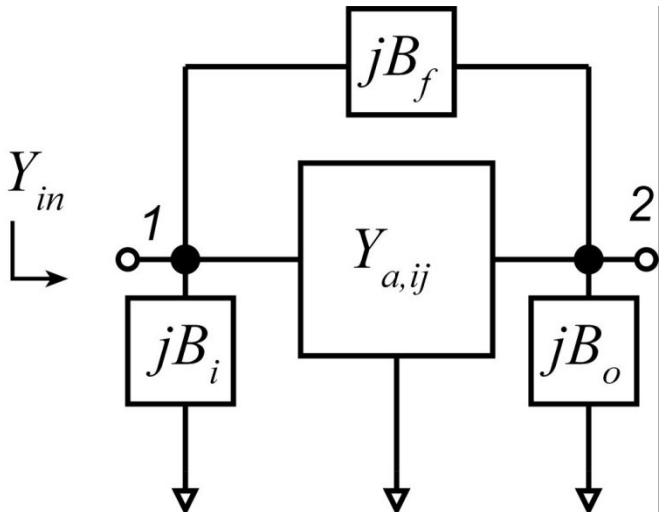
$$Y_{in} = G_{a,11} + jB_{11} - \frac{(G_{a,12} + jB_{a,12} - jB_f)(G_{a,21} + jB_{a,21} - jB_f)}{(G_{a,22} + jB_{22})} = G_{in} + jB_{in}$$



We want \$B\_{in} = 0\$, and to make \$G\_{in}\$ as negative as possible.

# Input Conductance

$$\begin{aligned}
 Y_{in} &= G_{a,11} + jB_{11} - \frac{(G_{a,12} + j(B_{a,12} - B_f))(G_{a,21} + j(B_{a,21} - B_f))}{(G_{a,22} + jB_{22})} \\
 Y_{in} &= G_{a,11} + jB_{11} - \frac{((G_{a,12}G_{a,21} - (B_{a,12} - B_f)(B_{a,21} - B_f)) + j(G_{a,21}(B_{a,12} - B_f) + G_{a,12}(B_{a,21} - B_f)))(G_{a,22} - jB_{22})}{(G_{a,22}^2 + B_{22}^2)} \\
 G_m &= G_{a,11} - \frac{(G_{a,12}G_{a,21} - (B_{a,12} - B_f)(B_{a,21} - B_f))G_{a,22} + (G_{a,21}(B_{a,12} - B_f) + G_{a,12}(B_{a,21} - B_f))B_{22}}{(G_{a,22}^2 + B_{22}^2)} \\
 B_m &= B_{11} + \frac{(G_{a,21}(B_{a,12} - B_f) + G_{a,12}(B_{a,21} - B_f))G_{a,22} - (G_{a,12}G_{a,21} - (B_{a,12} - B_f)(B_{a,21} - B_f))B_{22}}{(G_{a,22}^2 + B_{22}^2)}
 \end{aligned}$$

$$\begin{aligned}
 G_{in} &= G_{a,11} - \frac{(G_{a,12}G_{a,21} - (B_{a,12} - B_f)(B_{a,21} - B_f))G_{a,22}}{(G_{a,22}^2 + B_{22}^2)} \\
 &\quad - \frac{(G_{a,21}(B_{a,12} - B_f) + G_{a,12}(B_{a,21} - B_f))B_{22}}{(G_{a,22}^2 + B_{22}^2)}
 \end{aligned}$$

We should pick  $B_f$  and  $B_{22}$  and to obtain a large negative  $G_{in}$ .

Unfortunately, I've been unable to derive these\*.

$B_f$  and  $B_{22}$  can also be tuned manually to maximize the negative input conductance.

This is shown on the next slides.

\*Optimum feedback elements given in


D.F. Page, A.R. Boothroyd, "Instability in Two - Port Active Networks"

IRE Transactions on Circuit Theory, Vol. CT - 5, pp.133 - 139, June 1958.


# **Design Example (1): Topology, Negative G Tuning.**
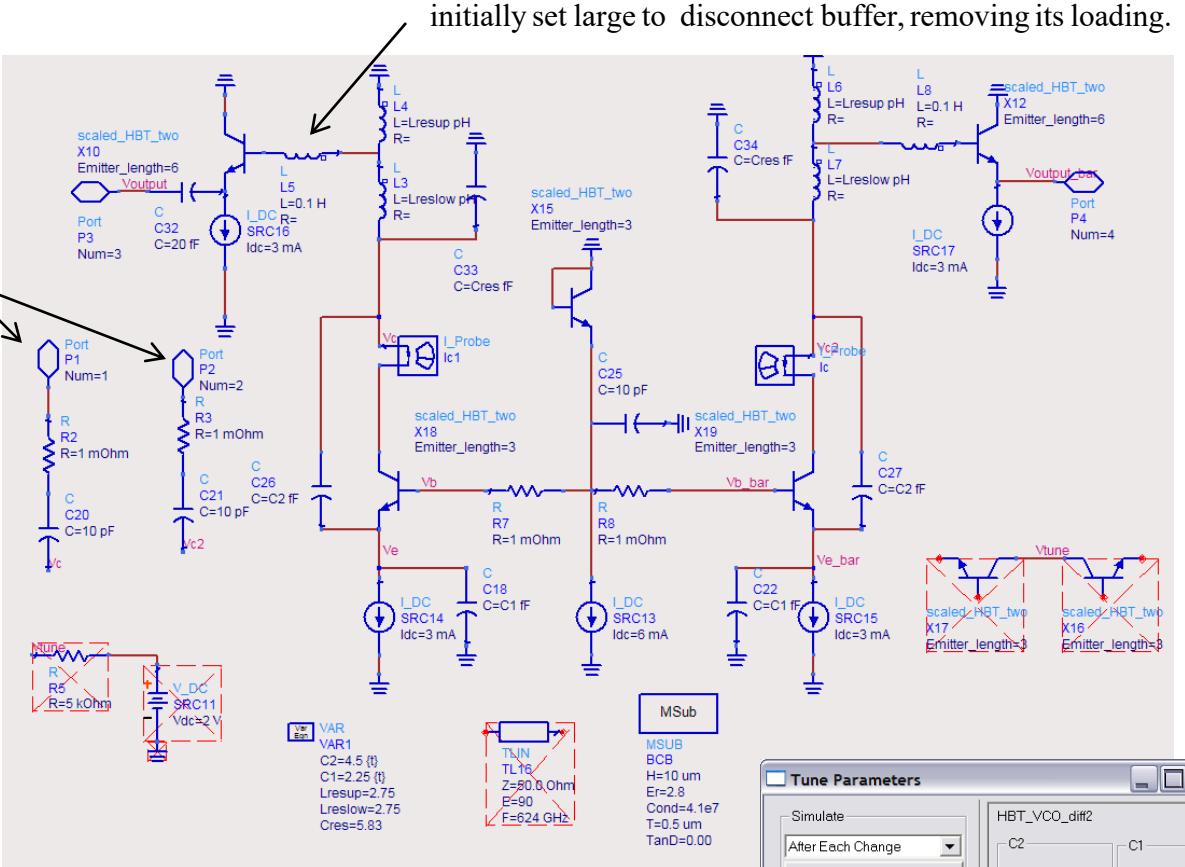
# 620 GHz Common - Base Colpitts with $\sim 800$ GHz $f_{\max}$ HBT

Test port connected to transistor collectors



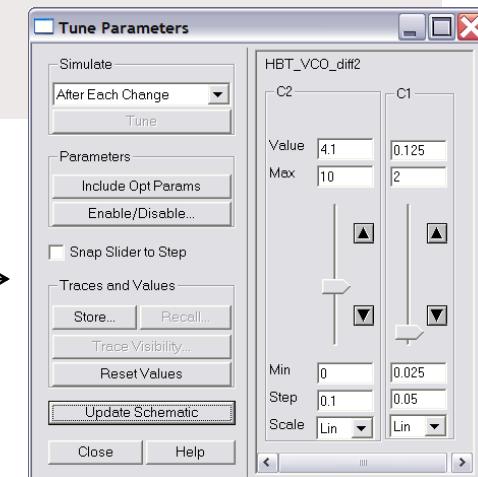$C_1$  and  $C_2$  are tuned to produce maximum negative conductance at the collectors:





# Design Example (2): Resonator Admittance

Port admittance observed at the collectors.

$C_1$  and  $C_2$  have been tuned for maximum negative  $G_{11}$ .

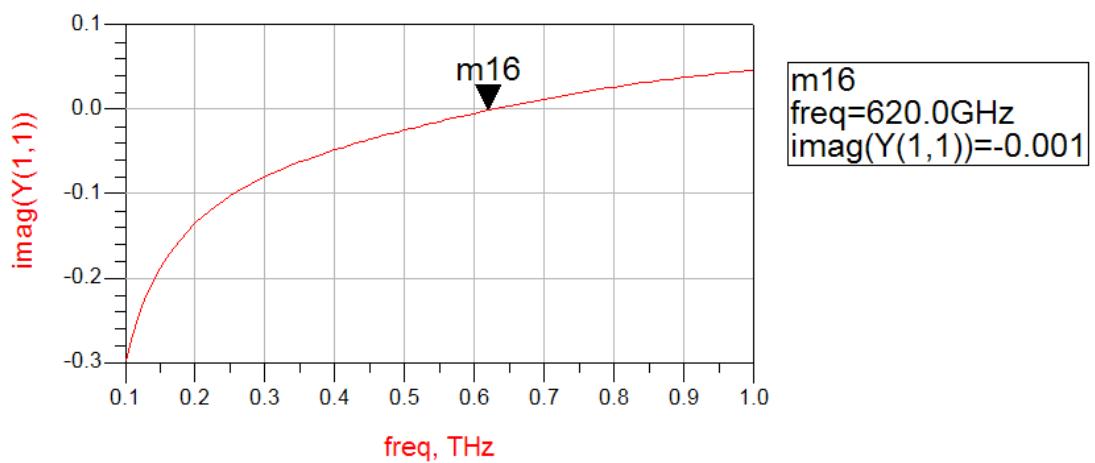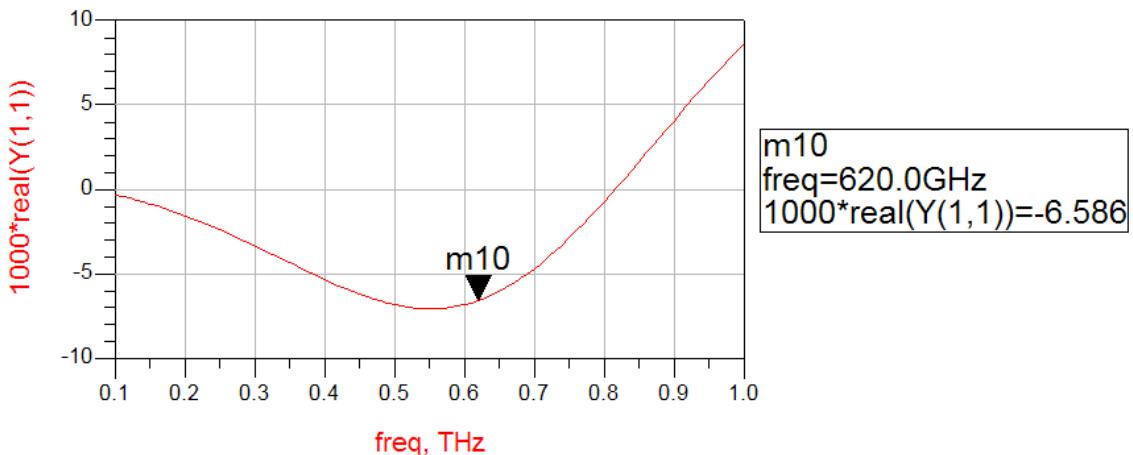
The resonator inductance has been tuned for zero  $B_{11}$ .



# Design Example (3): Connection of Buffer

L is now small; buffer is connected.


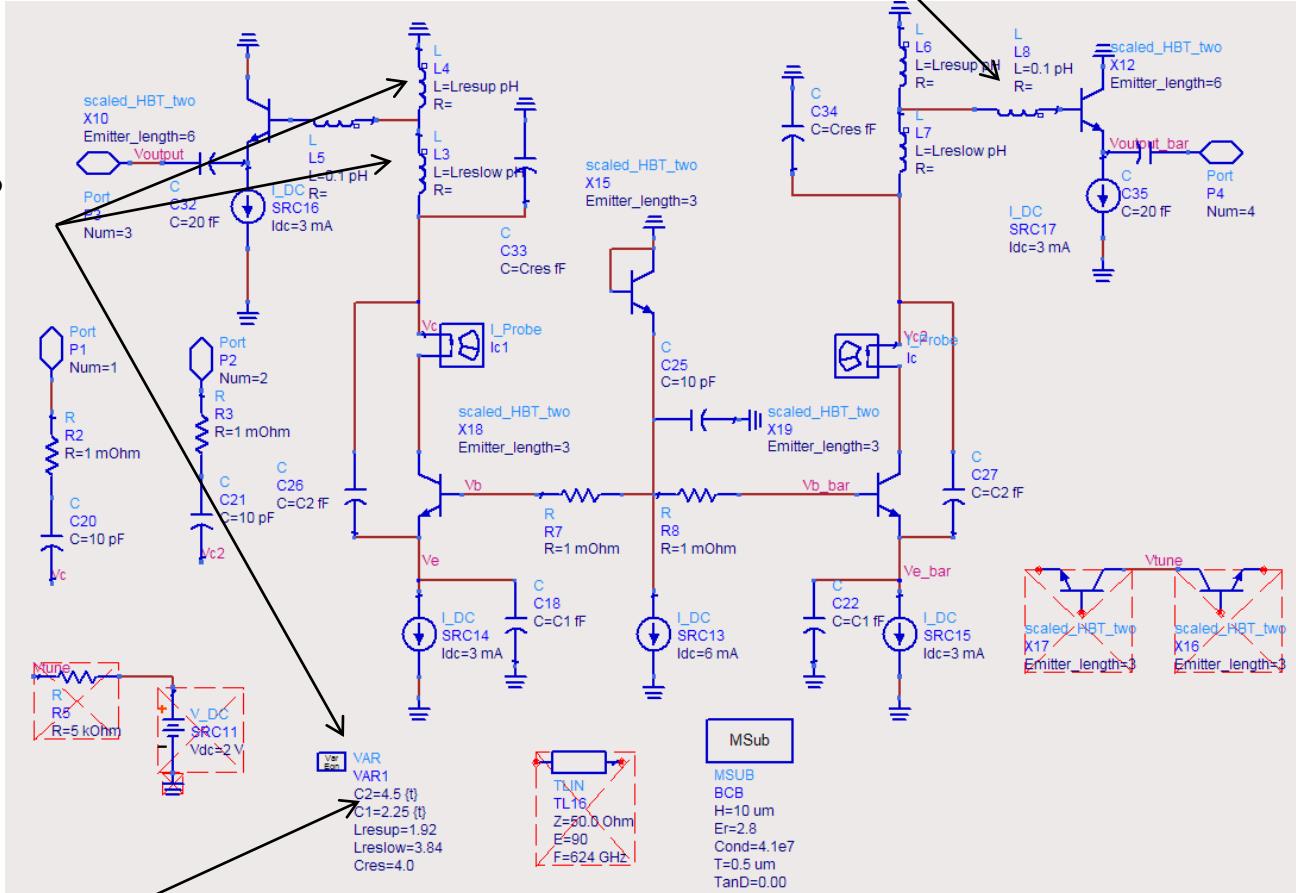
3 : 1 inductor step - down ratio  
reduces loading of buffer on  
oscillator core.



The feedback elements must be re - tuned

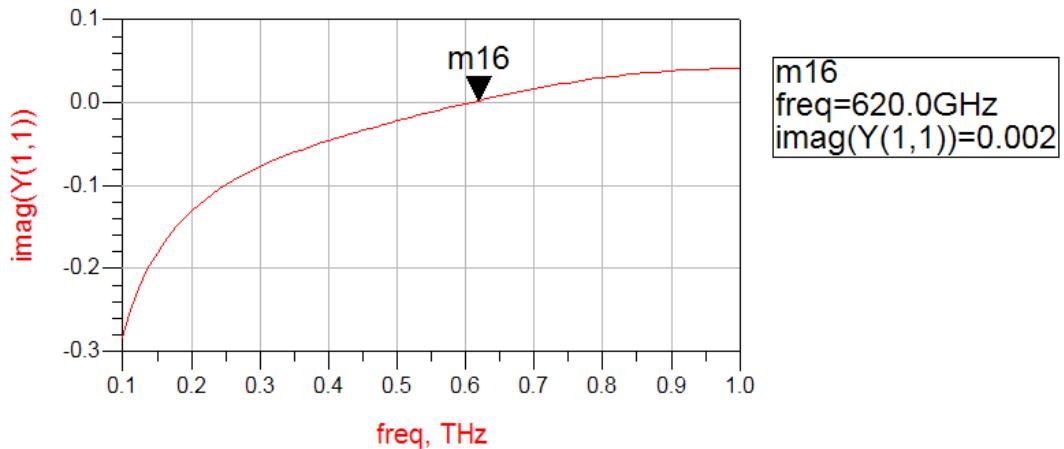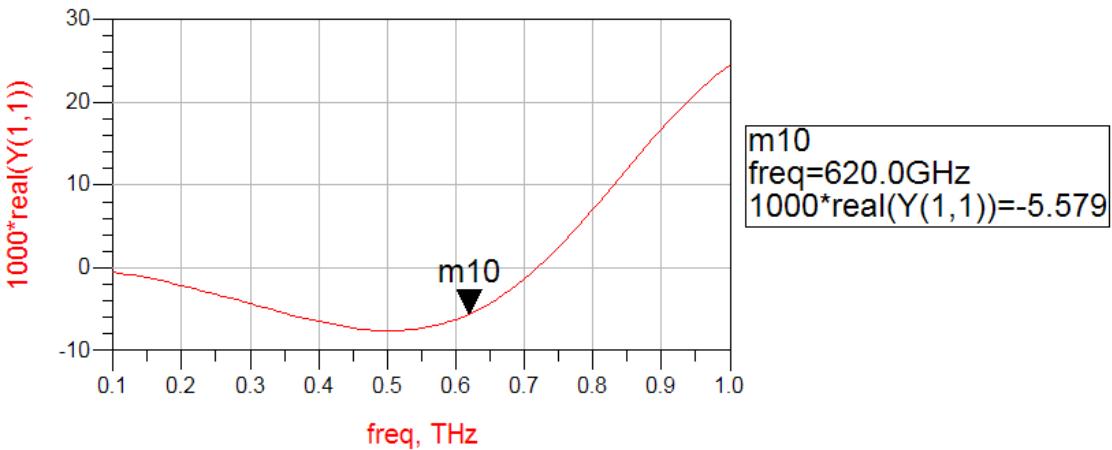
# Design Example (4): Negative G given Buffer

Note that the negative conductance has been somewhat suppressed by the output loading.


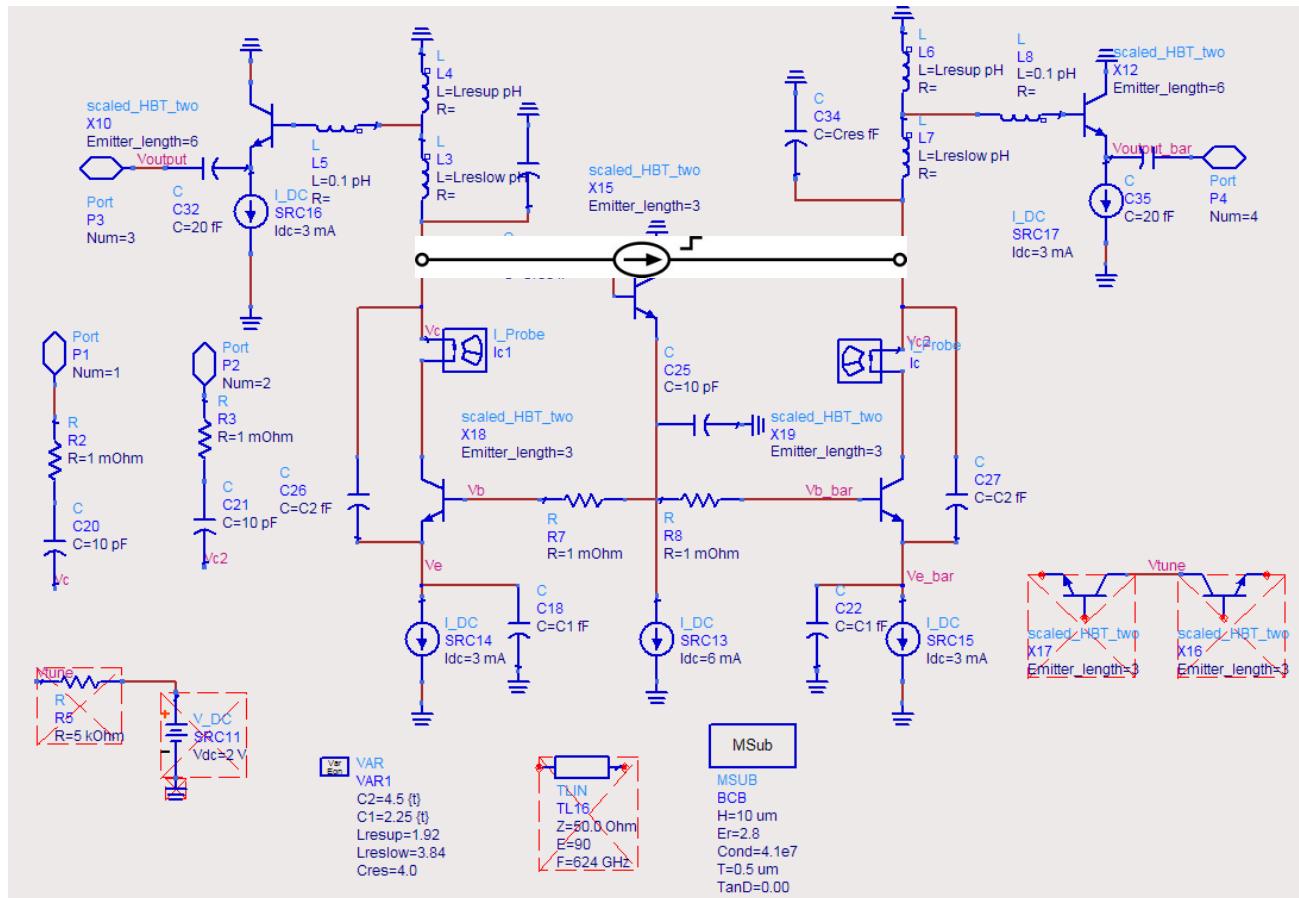
# Design Example (5): Transient Simulation


Transient simulation :  
 a small ( $\sim 10\mu\text{A}$ ) current pulse is injected into the resonator and the circuit is simulated.


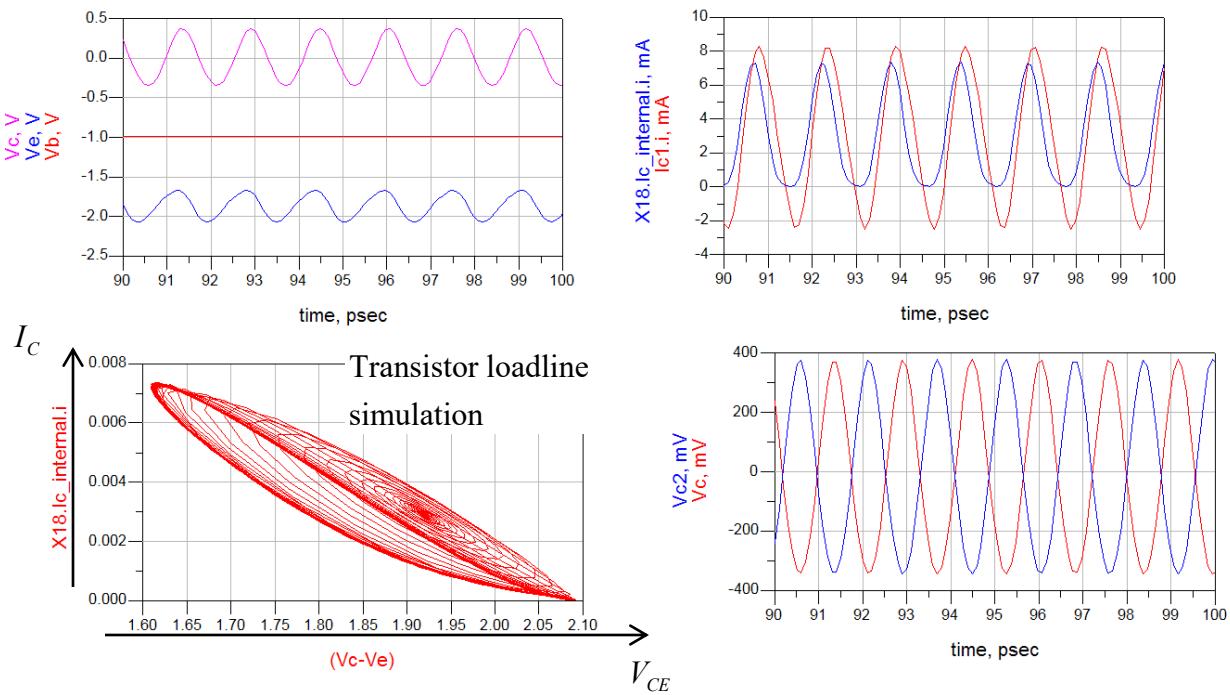
# Design Example (5): Transient Simulation

Build - up of oscillation  
is not shown here.

Note that the time axis  
starts at 90 ps.




# 2nd Example : Common-Collector Colpitts

Capacitor reduces loading of oscillator by common-base output buffer

resonator inductor


feedback network

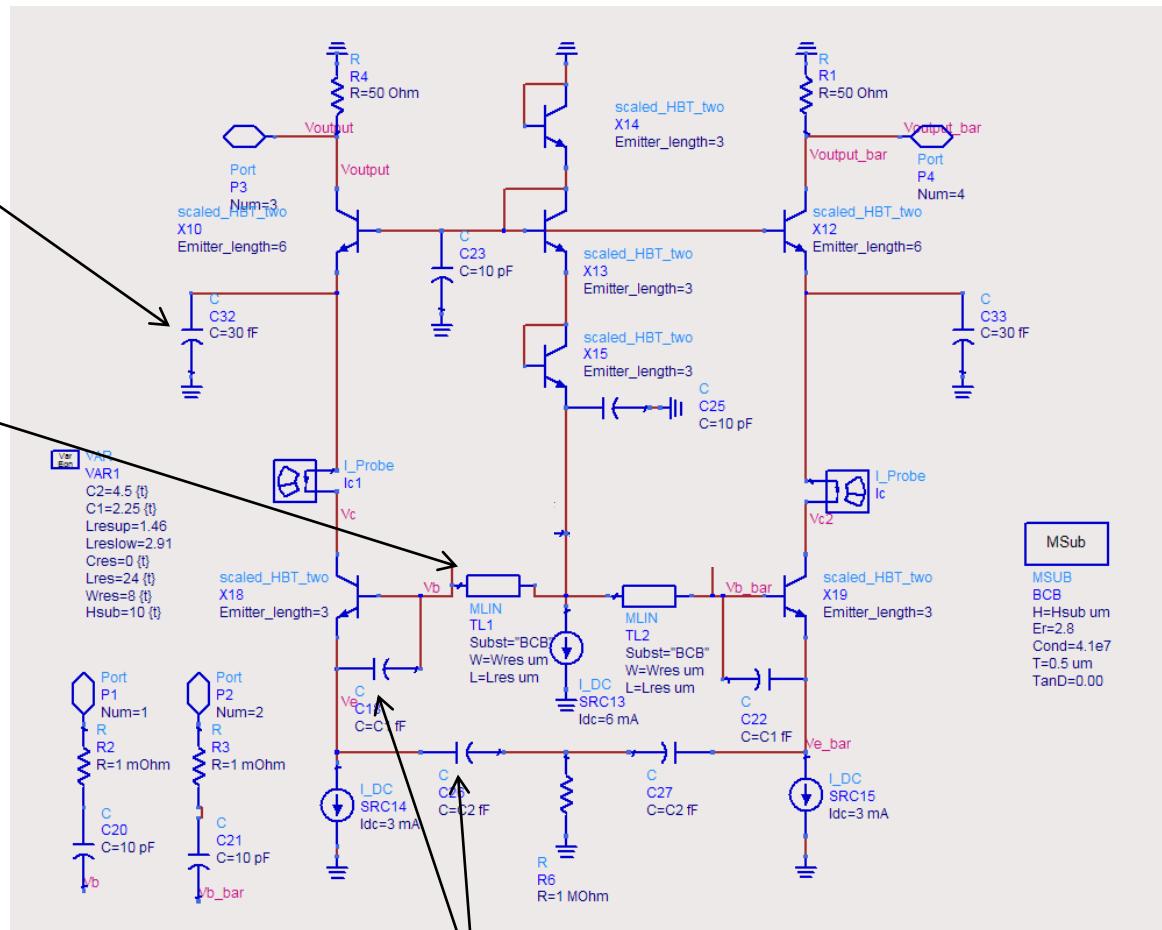


Common - collector Colpitts with common - base output buffer.

# 2nd Example : Common-Collector Colpitts

Port admittance




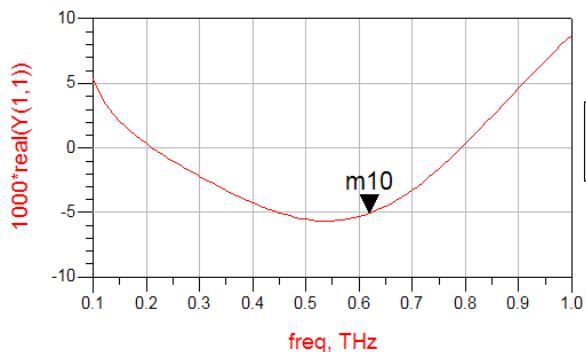


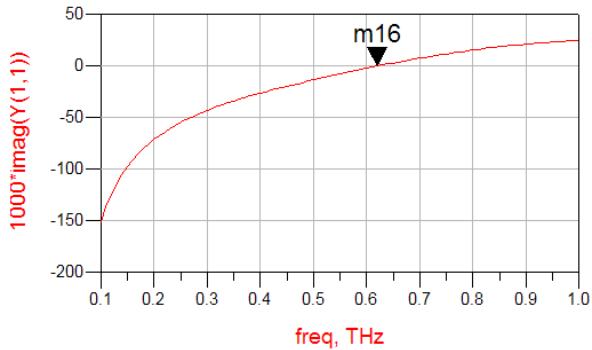m10  
freq=620.0GHz  
 $1000 \cdot \text{real}(Y(1,1)) = -5.093$



m16  
freq=620.0GHz  
 $1000 \cdot \text{imag}(Y(1,1)) = 0.116$



Transient Simulation

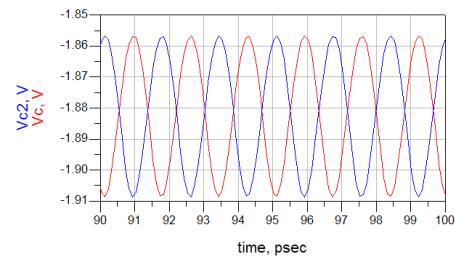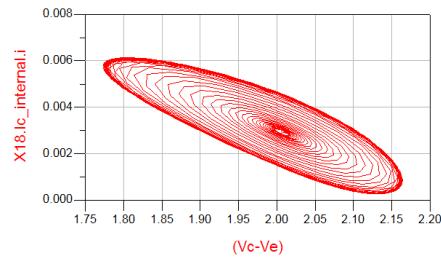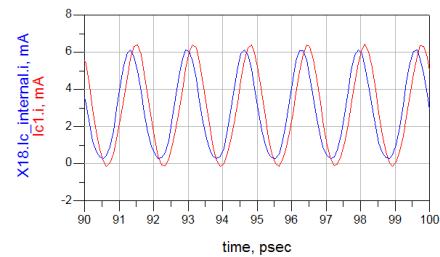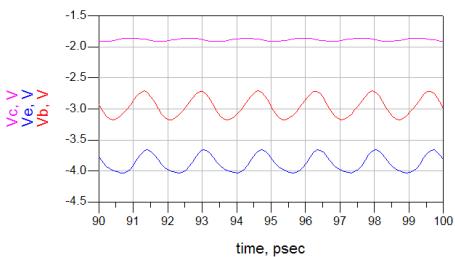



# 3nd Example : The Real Design
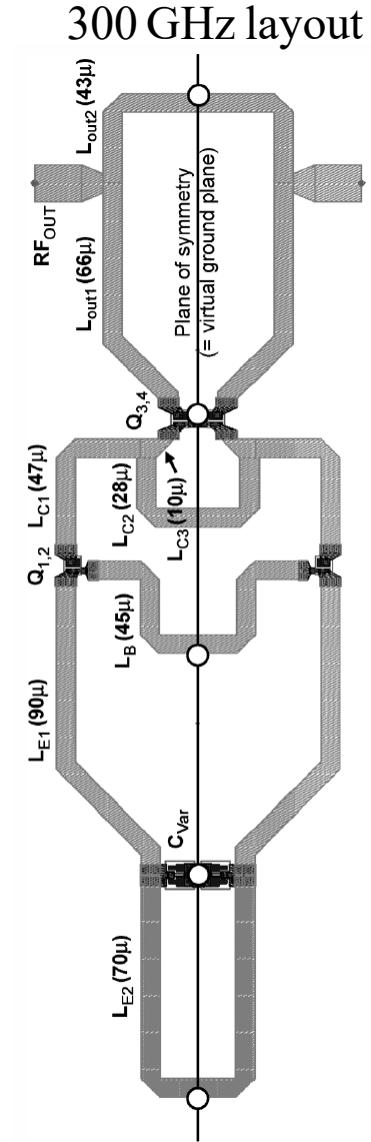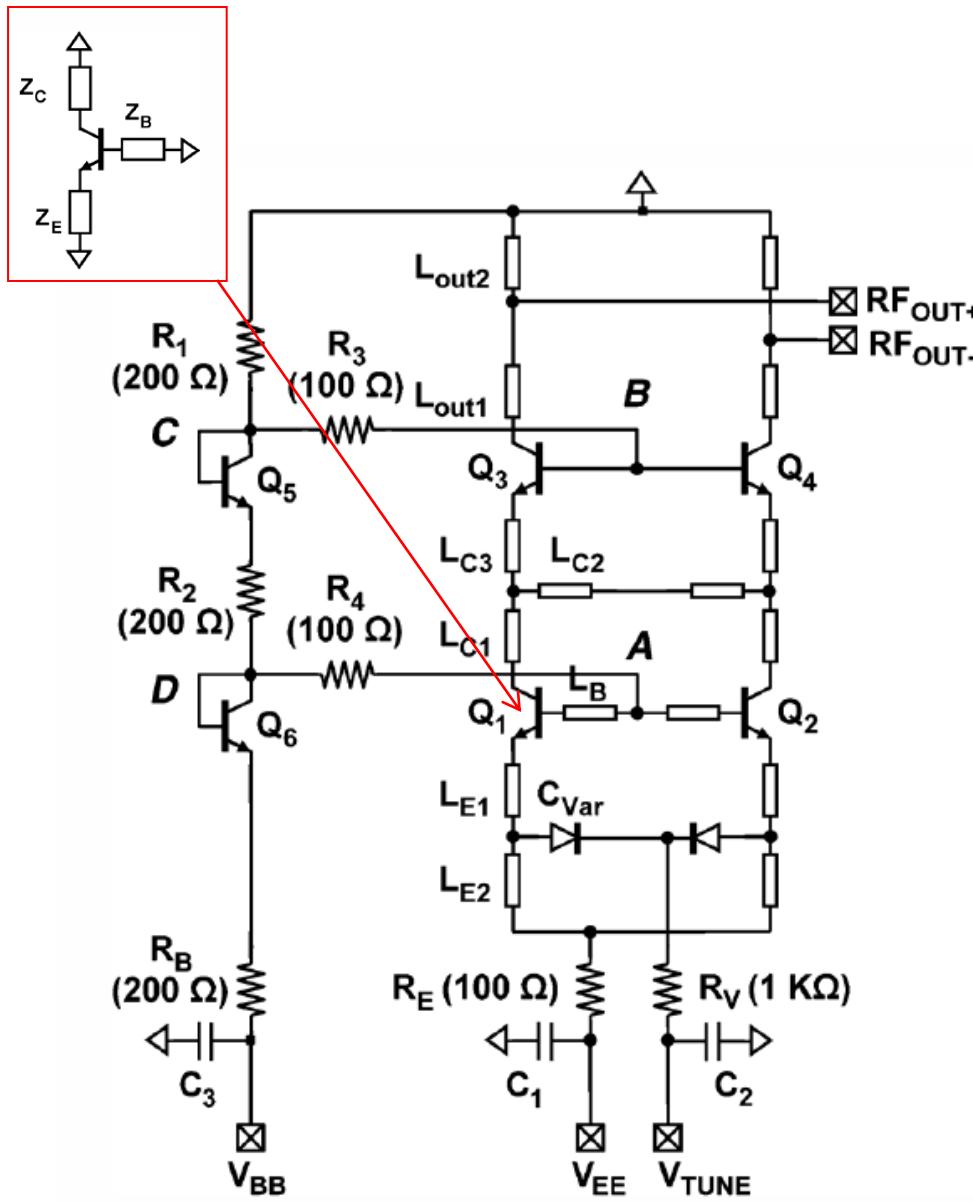
## InP HBT IC Technology for Terahertz Frequencies: Fundamental Oscillators Up to 0.57 THZ






Munkyo Seo, Senior Member, IEEE, Miguel Uribeaga, Member, IEEE, Jonathan Hacker, Senior Member, IEEE, Adam Young, Member, IEEE, Zach Griffith, Member, IEEE, Vibhor Jain, Richard Pierson, Petra Rowell, Anders Skalare, Member, IEEE, Alejandro Peralta, Robert Lin, David Pukala, and Mark Rodwell, Fellow, IEEE



# 3nd Example : The Real Design

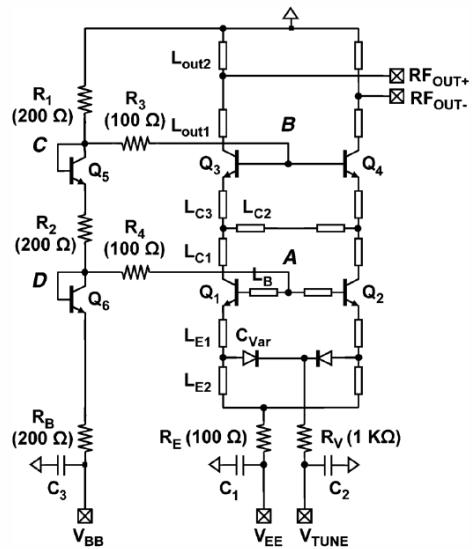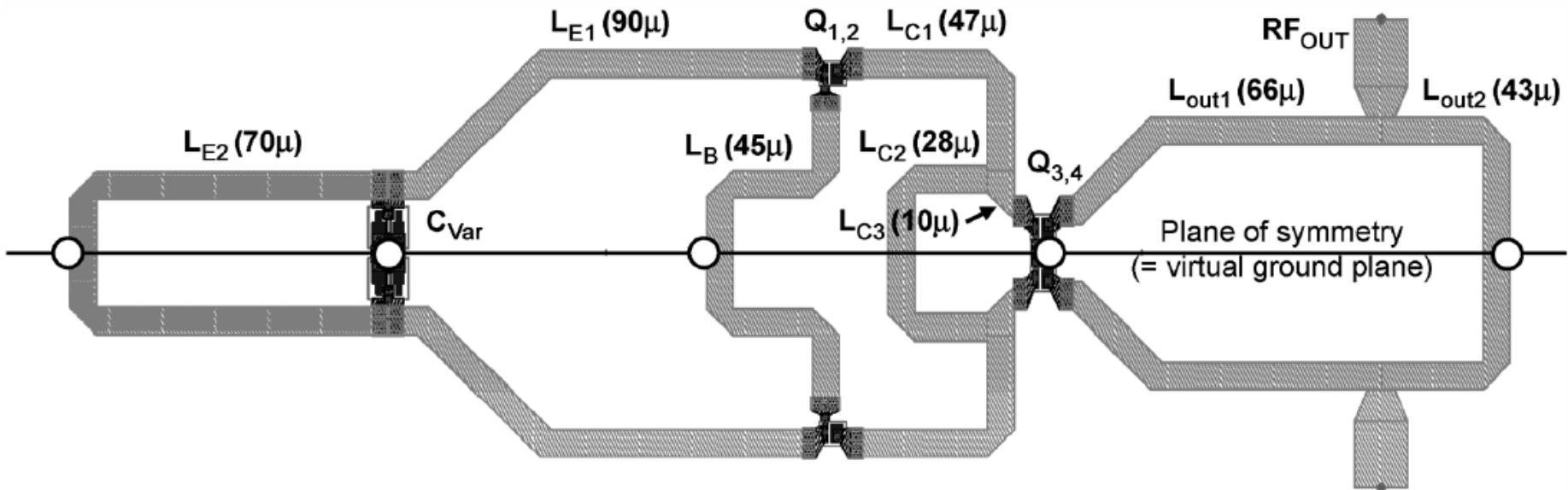

# 3nd Example : The Real Design

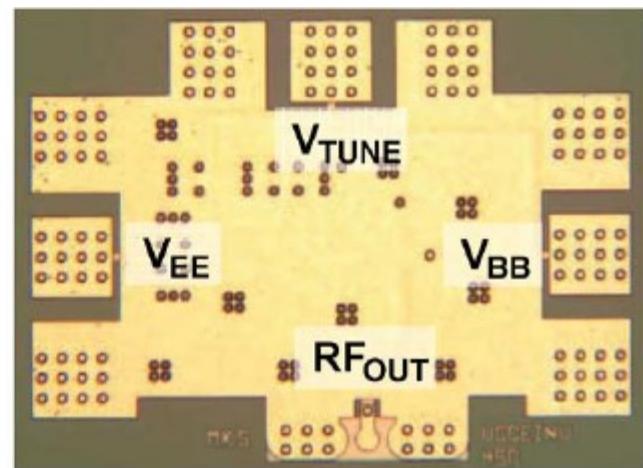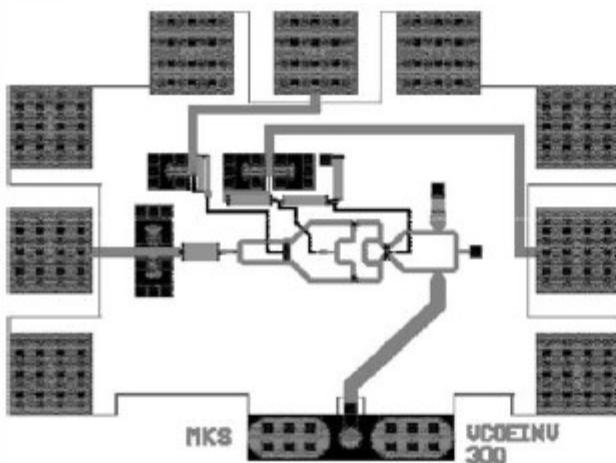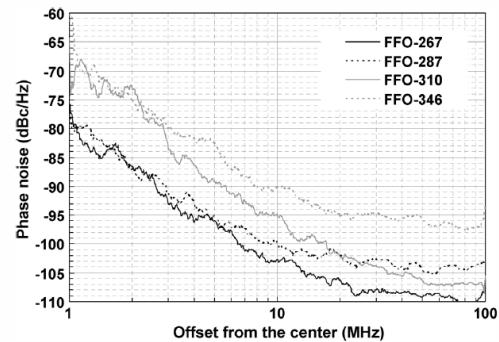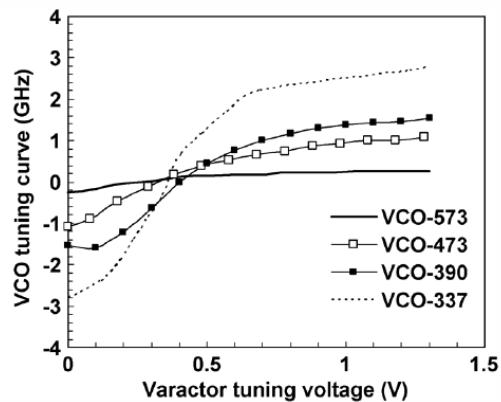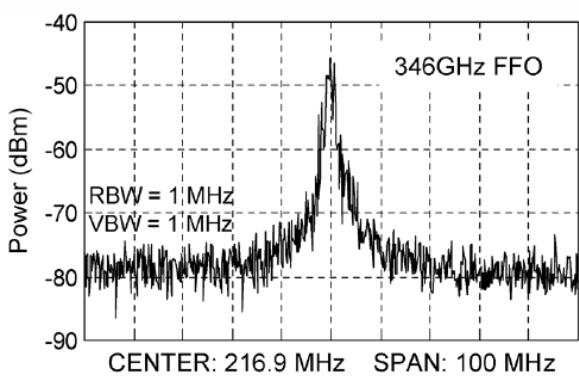

Process Technology	Oscillation Frequency			Single-ended output power <sup>1</sup> (dBm)			Phase noise @ 10 MHz offset
	Design	Measured	Simulation w/ revised HBT model	Simulation w/ revised HBT model <sup>2</sup>	Measured (uncorrected)	Measured (corrected <sup>3</sup> )	
THzIC1	292.4 GHz	267.4 GHz	261.5 GHz	-3.6 dBm	-5.1 dBm	-2.1 dBm	-102.4 dBc/Hz
THzIC1	315.4 GHz	286.8 GHz	280.6 GHz	-4.7 dBm	-6.9 dBm	-3.9 dBm	-99.8 dBc/Hz
THzIC1	336.5 GHz	310.2 GHz	303.7 GHz	-6.4 dBm	-9.2 dBm	-6.2 dBm	-95.6 dBc/Hz
THzIC1	387.8 GHz	346.2 GHz	346.0 GHz	-7.7 dBm	-11.0 dBm	-7.0 dBm	-88.8 dBc/Hz
THzIC2	397.0 GHz	412.9 GHz	394.5 GHz	-3.5 dBm	-11.1 dBm	-5.6 dBm	-
THzIC2	508.0 GHz	487.7 GHz	505.9 GHz	-5.2 dBm	-16.4 dBm	-8.9 dBm	-
THzIC2	587.9 GHz	573.1 GHz	586.3 GHz	-9.0 dBm	-36.2 dBm	-19.2 dBm	-