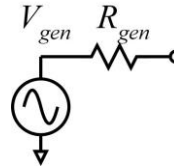


ECE 145b first problem set (noise)

Problem 1: In a communication channel, the received binary signal is + or - 10 mV, representing binary values. To this is added noise with a Gaussian distribution (zero mean) having 1 mV standard deviation. (a) Setting a decision threshold at 0 mV, what is the probability of error? You will need the integral of a Gaussian distribution....please see notes set 7, pages 40-41.

Problem 2: A noise voltage $V_{in}(t)$, a zero-mean Gaussian random process, has spectral density $\tilde{S}_{V_{in}V_{in}} = 4kTR_0FG$ (V^2/Hz), where $R_0 = 50$ Ohms, $F=5$ dB, and $G=40$ dB, i.e., $F=3.16$ and $G=10^4$ in linear units (but of W/W gain, not V/V). This noise is passed through low-pass RC filters having transfer function $h_1(j2\pi f) = (1 + j2\pi f / 2\pi f_1)^{-1}$ and $h_2(j2\pi f) = (1 + j2\pi f / 2\pi f_2)^{-1}$ to produce $V_{out1}(t)$ and $V_{out2}(t)$. (a) Determine the spectral densities and cross spectral density of V_{out1} and V_{out2} . (b) From these quantities, determine the spectral density of $V_{out3} = V_{out1} + V_{out2}$.

Problem 3: The generator is a 1 Volt sine wave at 1 GHz. R_{gen} is 10 Ohms, and is a physical resistor at room temperature. (a) find the spectral density of the noise voltage in V^2/Hz and (b) Find the signal/noise ratio in a 10 Hz bandwidth centered around 1 GHz.




Problem 4: A noise voltage $V_{in}(t)$, a zero-mean Gaussian random process, has spectral density $\tilde{S}_{V_{in}V_{in}} = 4kTR_0FG$ (V^2/Hz), where $R_0 = 50$ Ohms, $F=5$ dB, and $G=40$ dB. This noise is passed through a low-pass RC filter having transfer function $h(j2\pi f) = (1 + j2\pi f / 2\pi f_0)^{-1}$ to produce $V_{out}(t)$. (a) If the 3-dB bandwidth of the filter is 500 MHz, give the power spectral density $V_{out}(t)$.

218B additional problems:

(a) If the 3-dB bandwidth of the filter is 500 MHz, compute the autocorrelation function and variance of $V_{out}(t)$. (b) Compute the cross spectral density and cross correlation function of $V_{in}(t)$ and $V_{out}(t)$.

Problem 5: In the diagram to the right, L and C are open- and short-circuits at the frequencies of interest. The diode is ideal. Compute a Thevenin noise model (rightmost diagram) as a function of DC current I_0 , finding the spectral density of E_n and the equivalent resistance R_{th} . Assume that I_0 is much greater than the diode saturation current I_s . What is the available noise power in units of Watts/Hz or Joules? How does this compare to a physical resistance.

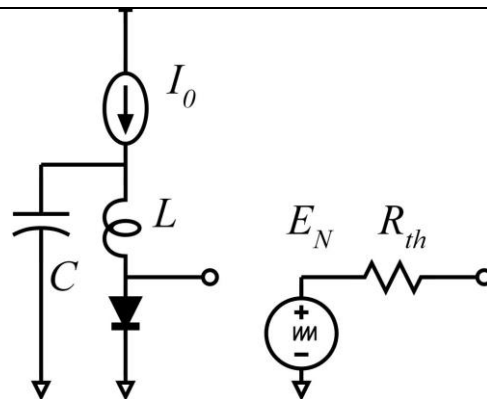

Problem 6: (a) Compute the power spectral density of V_o as a function of R and C .

218B additional problem: (b) Compute the total RMS noise voltage as a function of R and C .

