
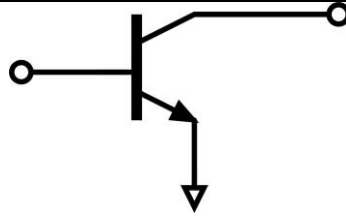


**ECE 145b problem set (noise)**

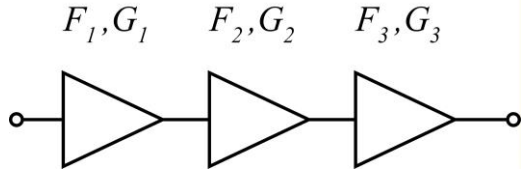Problem 1: The transistor has  $\beta=200$ ,  $R_{bb}=50\Omega$ ,  $R_{ex}=R_c=0\ \Omega$ . (a) At  $f\sim 0\text{Hz}$ , and  $I_C=1\ \text{mA}$ , find  $F_{\text{min}}$  and  $Z_{\text{opt}}$ . (b) if  $Z_{\text{gen}}=1\text{k}\ \Omega$ , find the spectral density of the *total* input referred noise voltage. (c) if  $Z_{\text{gen}}=1\text{k}\ \Omega$ , what collector bias current minimizes the noise figure?




Problem 2: Stages 1,2, and 3 have noise figures of 2, 4 and 6 dB respectively, and gains of 6, 9, and 12 dB respectively. What is the noise figure of the overall system (answer in linear units and in dB)? What is the noise measure of the overall system (answer in linear units)? What is the noise temperature of the overall system, assuming that the reference temperature is 290 Kelvin.




**ECE 218B problem set (noise)**

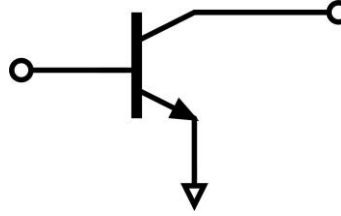Problem 1: The transistor has  $\beta=200$ ,  $R_{bb}=50\Omega$ ,  $R_{ex}=R_c=0\Omega$ . (a) At  $f\sim 0\text{Hz}$ , and  $I_C=1\text{mA}$ , find  $F_{\min}$  and  $Z_{\text{opt}}$ . (b) if  $Z_{\text{gen}}=1\text{k}\Omega$ , find the spectral density of the *total* input referred noise voltage. (c) if  $Z_{\text{gen}}=1\text{k}\Omega$ , what collector bias current minimizes the noise figure?



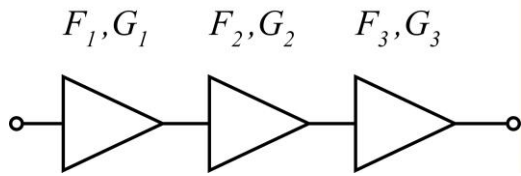Problem 2: Stages 1,2, and 3 have noise figures of 2, 4 and 6 dB respectively, and gains of 6, 9, and 12 dB respectively. What is the noise figure of the overall system (answer in linear units and in dB)? What is the noise measure of the overall system (answer in linear units)? What is the noise temperature of the overall system, assuming that the reference temperature is 290 Kelvin.



Problem 3: With the source grounded, (a) calculate the spectral densities of  $E_n$ , the total input short-circuit noise voltage,  $I_n$ , the total input open-circuit noise current, and the cross spectral density of  $E_n$  and  $I_n$ , assuming that the spectral density of  $I_{n,ch}$  is  $4kT\Gamma g_m$ , that  $R_g$  has normal thermal noise, and that  $R_{DS}$  is noiseless (b) With  $f_t=200\text{GHz}$ ,  $R_g=1/g_m$ ,  $\Gamma=1$ ,  $R_{\text{gen}}=50\Omega$ ,  $g_m=50\text{mS}$ , find the (50 Ohm source impedance) noise figure at 10 GHz. (c) With these same values, find  $F_{\min}$  and  $Z_{\text{opt}}$ .

