

# ***Distributed Amplifiers:***

## ***A quick review***

***Mark Rodwell,***  
***University of California, Santa Barbara***

# Distributed Amplifiers: Why ?


---

- 1) Used in a few applications :  
instrument front - ends,  
wideband (military) receivers,  
optical modulator drivers
- 2) Distribution concepts apply more broadly  
phase - matching of traveling waves.  
accumulated attenuation  
synthetic transmission - lines.

#2 is our main motivation...

Also known as traveling - wave amplifiers
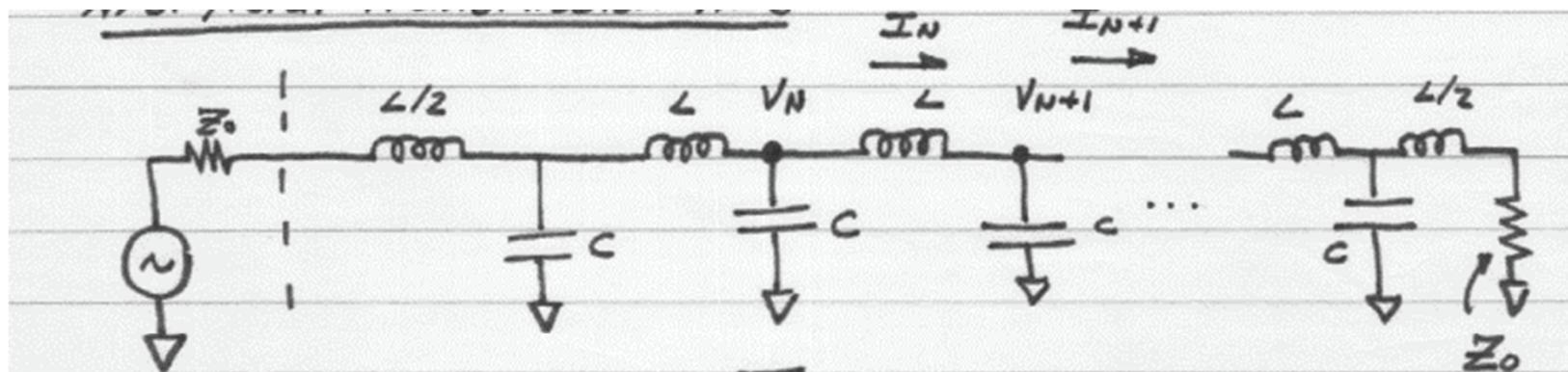
# Synthetic (artificial) transmission-line



$$\text{Design: } Z_0 = \sqrt{\frac{L}{C}} \text{ by choice.}$$

$$\text{To analyze: } V_{N+1} = e^{-\Gamma} V_N \quad I_N = e^{-\Gamma} e^{-jB} V_N$$

$$\begin{aligned} V_N (e^{-\Gamma}) &= -j\omega L I_N \\ I_N (e^{-\Gamma}) &= -j\omega C V_{N+1} \end{aligned} \quad \left. \begin{aligned} &\text{solve for} \\ &e^{\Gamma} \end{aligned} \right\}$$

$$\Rightarrow \cosh \Gamma = 1 - \frac{\omega^2 LC}{2}$$

define a cutoff (or Bragg) frequency

$$\omega_c = \sqrt{\frac{2}{LC}}$$

# Synthetic transmission-line

Then  $\cosh \Gamma = 1 - 2\omega^2/\omega_c^2$

but  $\cosh \Gamma = \cosh(A + jB)$   
 $= \cosh(A) \cos(B)$   
 $+ j \sinh(A) \sin(B)$

so

$$(\cosh(A) \cos(B) + j \sinh(A) \sin(B) = 1 - 2\omega^2/\omega_c^2)$$

examine how this behaves:

# Synthetic transmission-line

$$(\cosh(A)\cos(B) + j \sinh(A)\sin(B) = 1 - 2\omega^2/\omega_c^2)$$

examine how this behaves:

Case 1:  $\omega < \omega_c$  : then complex term = 0 and

$$\text{real term} = 1 - 2\omega^2/\omega_c^2$$

$$\Rightarrow A = 0 \text{ and}$$

$$\cos B = 1 - 2\omega^2/\omega_c^2$$

So wave propagates without attenuation.

# Synthetic transmission-line

$$(\cosh(A)\cos(B) + j \sinh(A)\sin(B) = 1 - 2\omega^2/\omega_c^2)$$

Case 2  $\omega > \omega_c$  : then we can no longer have

$$\cos B = 1 - 2\omega^2/\omega_c^2 \leftarrow \text{less than } -1$$

hence  $A \neq 0 \Rightarrow$  this means wave attenuates.

(note also  $A \neq 0 \Rightarrow \sin B = 0 \Rightarrow B = \pi$ )

So: Signals propagate only below the Bragg frequency  $\omega_c = 2/\sqrt{LC}$

# Below cutoff

---

Below cutoff:  $A=0$        $\cos B = 1 - 2\omega^2/\omega_c^2$   
 $= 1 - \omega^2 LC/2$

Far below cutoff  $B \ll 1$ ,  $\cos B \approx 1 - B^2/2 + (\frac{B}{\omega})^4$   
 drop.

$\therefore 1 - B^2/2 \approx 1 - \omega^2 LC/2$


$$\Rightarrow B \approx \omega \sqrt{LC}$$

phase delay =  $\frac{B}{\omega} \approx \sqrt{LC}$

# Propagation characteristics


$\beta$  : phase constant

$\alpha$  : attenuation constant

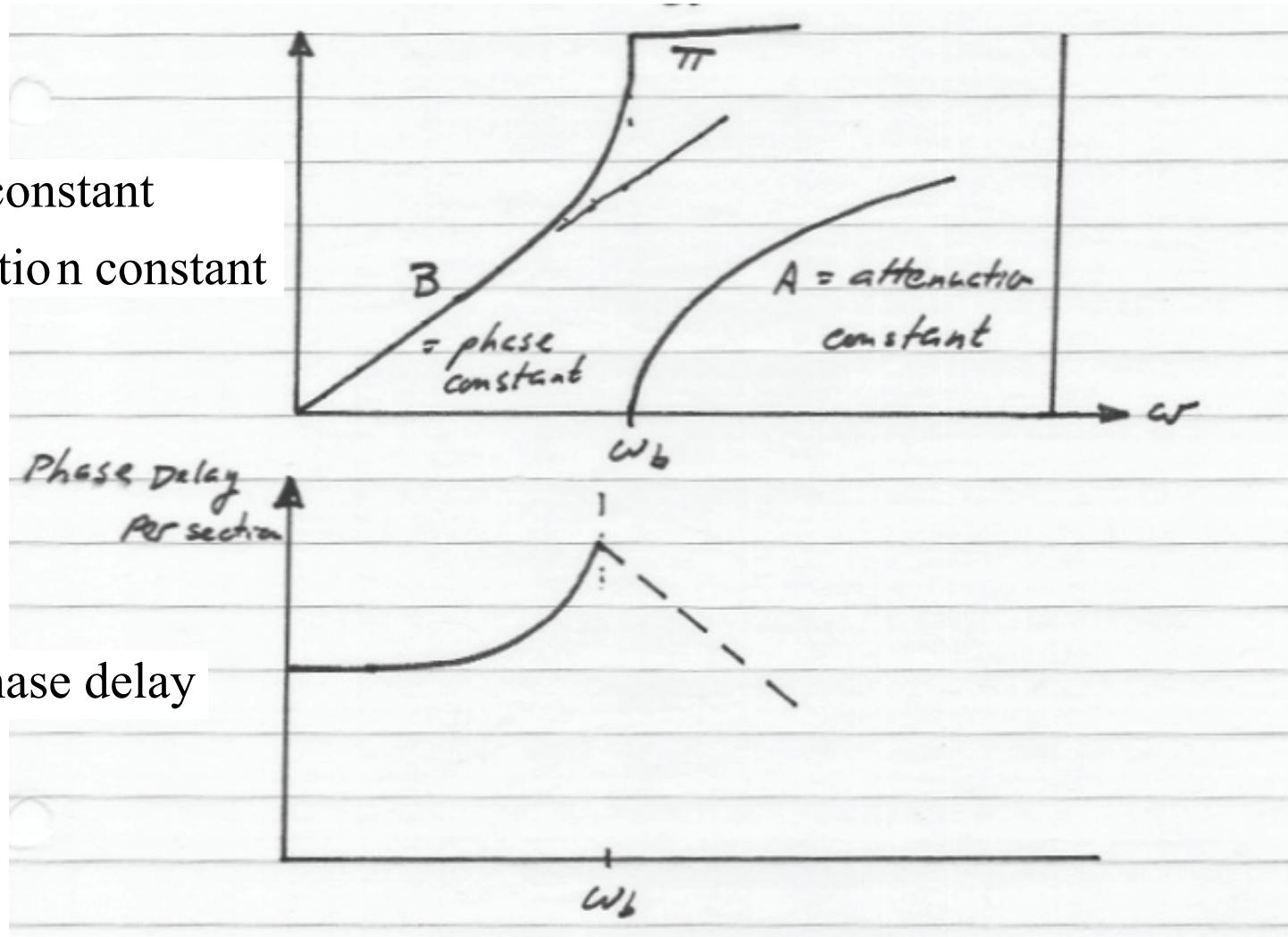


# Characteristic Impedance

---

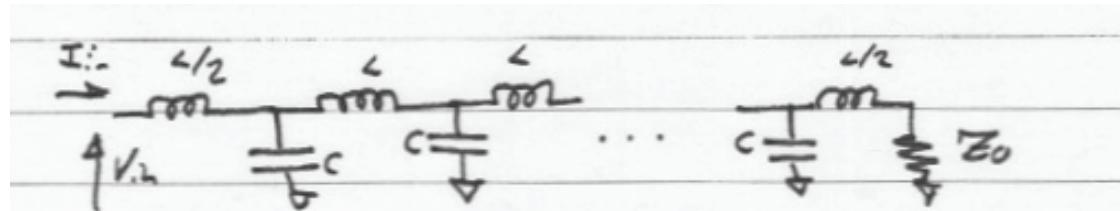


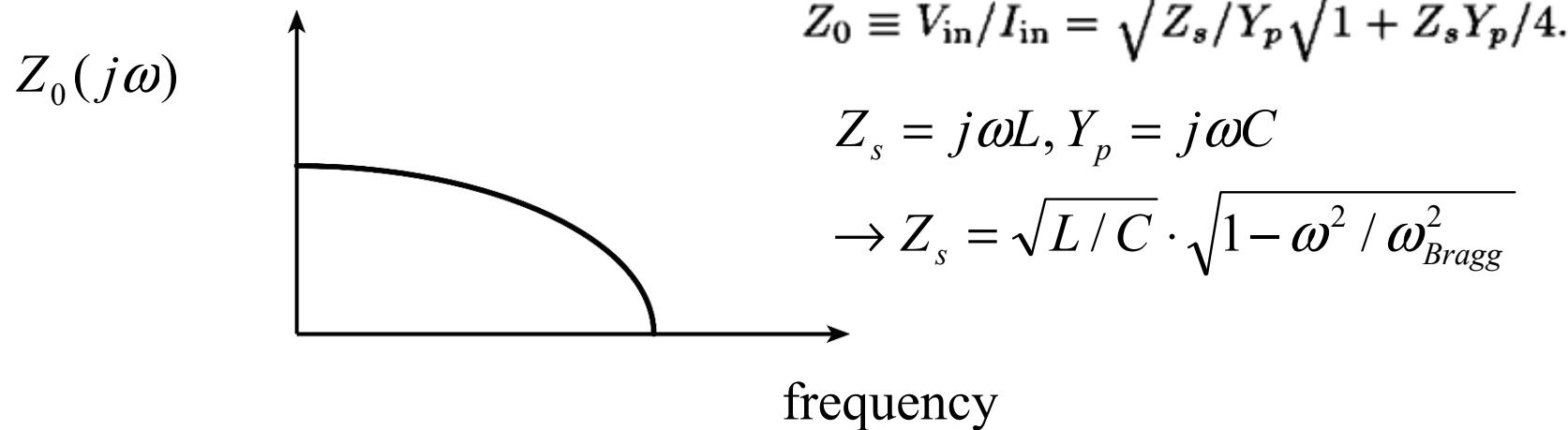Defining  $Z_0(\omega) = V_{in}(\omega) / I_{in}(\omega)$  a similar calculation can be made. (won't repeat)



# Synthetic transmission-line: summary

---

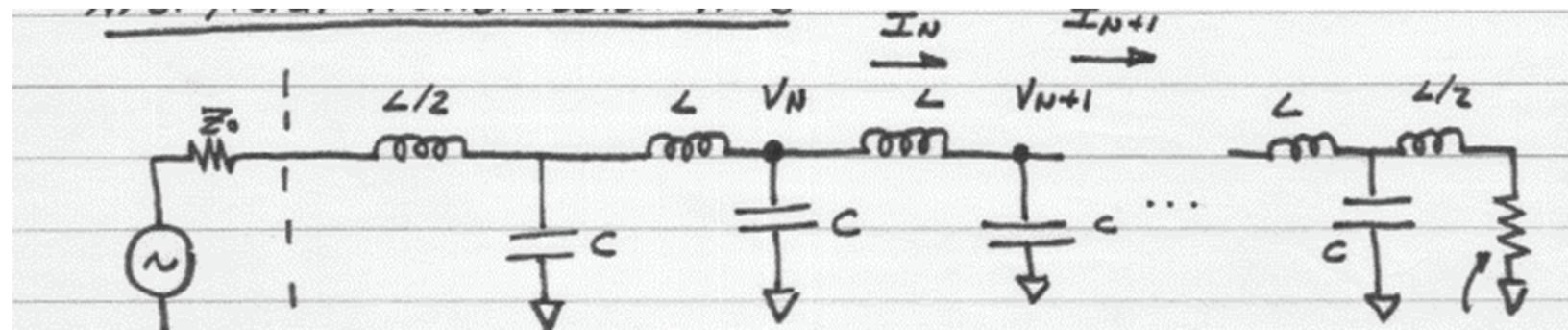



$$Z_0 \approx \sqrt{L/C} \text{ for } \omega \ll \omega_c$$

delay per section  $\approx \sqrt{LC}$  for  $\omega \ll \omega_c$

$$\omega_c = \frac{1}{\sqrt{LC}} \quad \text{or} \quad f_c = \frac{1}{2\pi\sqrt{LC}}$$

# Realization with distributed elements

---

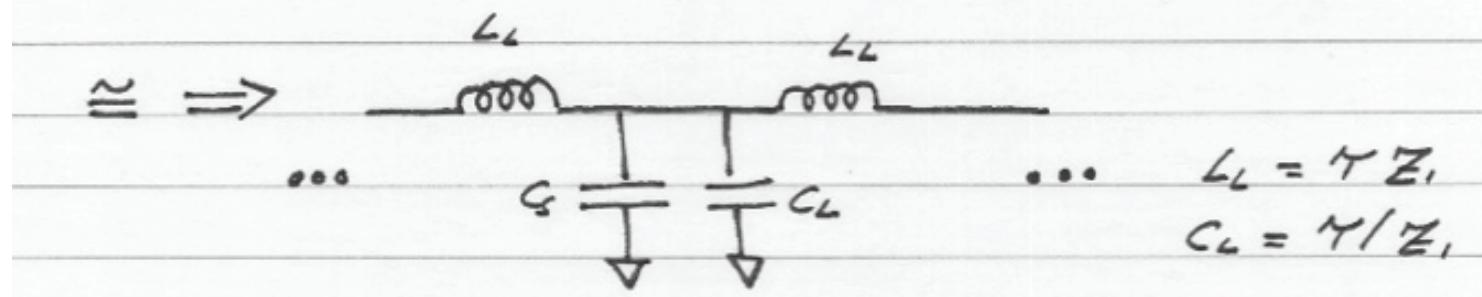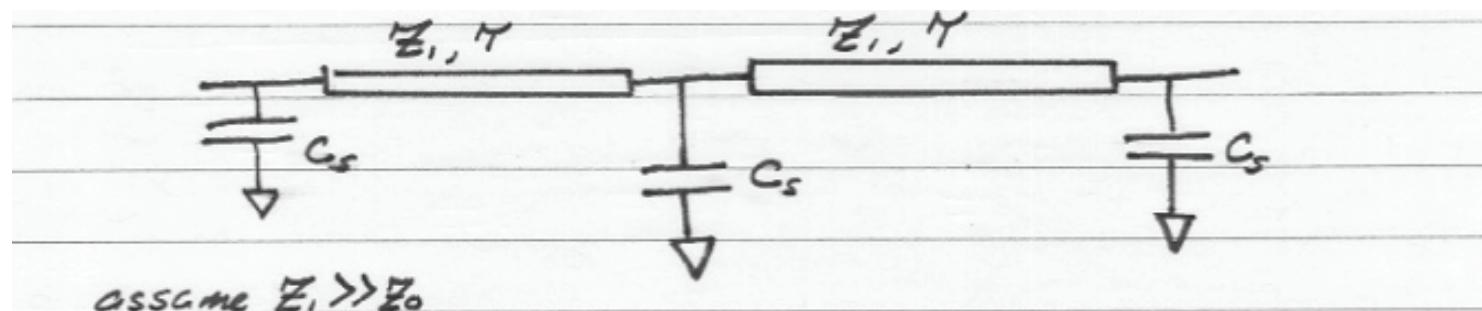



$$\Rightarrow Z_0 \approx \sqrt{\frac{L_L}{C_s + C_L}} = \sqrt{\frac{\gamma Z_1}{C_s + \gamma / Z_1}} \quad \leftarrow \omega \ll \omega_c$$

$$T = \text{delay per section} \approx \sqrt{L_L(C_s + C_L)} = \sqrt{\gamma Z_1 (C_s + \frac{\gamma}{Z_1})}$$

$$\omega_c \approx \frac{2}{\sqrt{L_L(C_s + C_L)}} = \frac{2}{\sqrt{\gamma Z_1 (C_s + \gamma / Z_1)}}$$

# Another realization with distributed elements

---

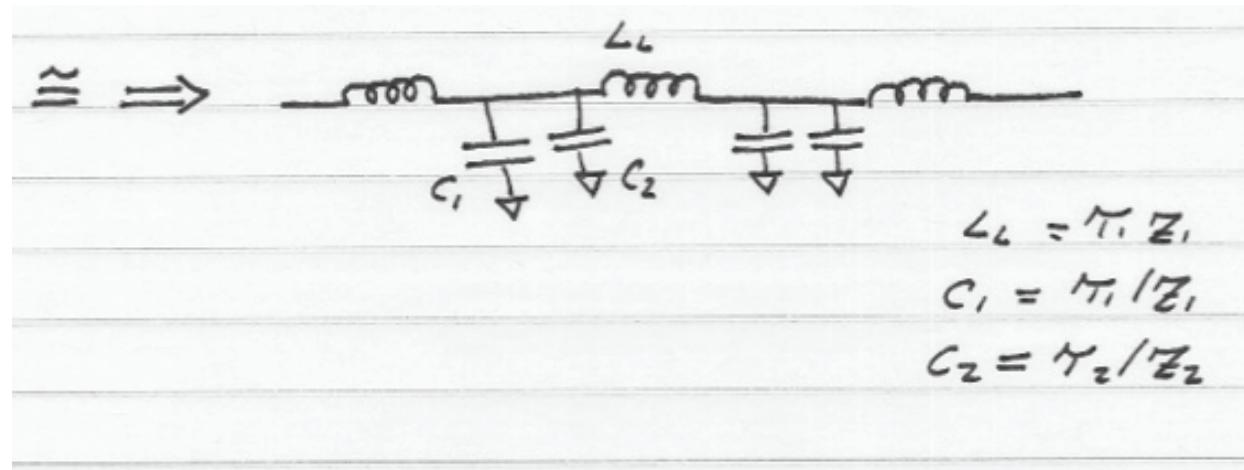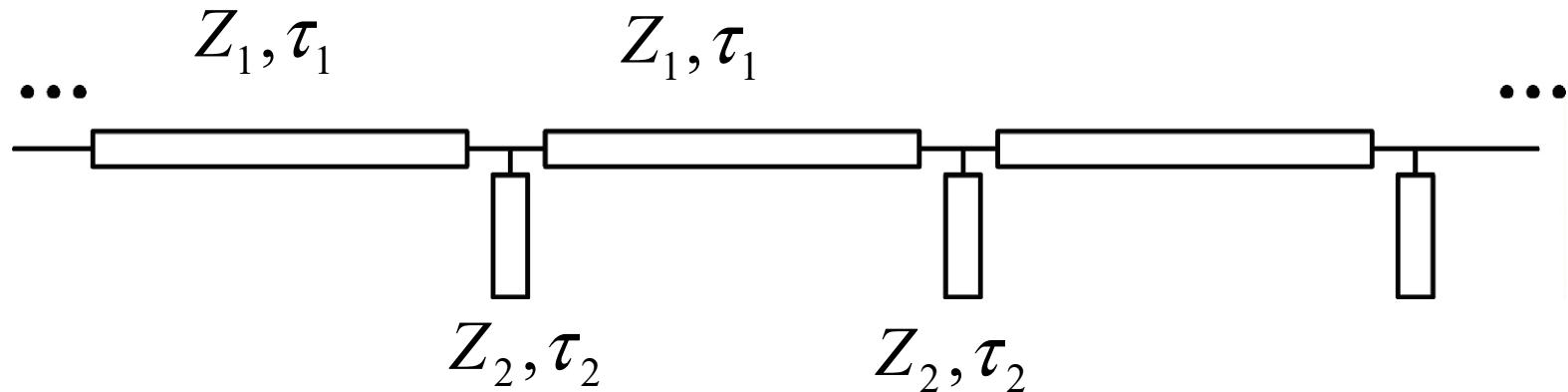


These are rough approximations.

You can (1) do more careful derivations  
or (2) check with a circuit simulator
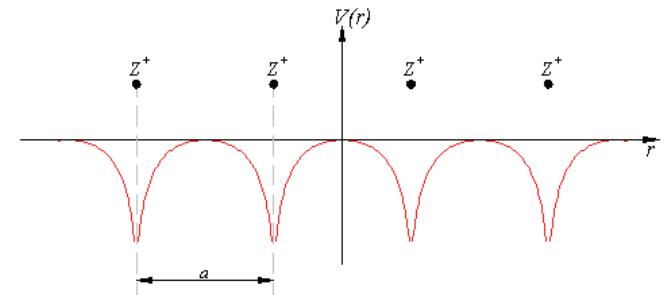
# Very broad applications of these concepts:

---


Kronig - Penney atomic lattice model  
→ band structure




X - ray diffraction in crystals (Bragg)

[https://en.wikipedia.org/wiki/Particle\\_in\\_a\\_one-dimensional\\_lattice](https://en.wikipedia.org/wiki/Particle_in_a_one-dimensional_lattice)

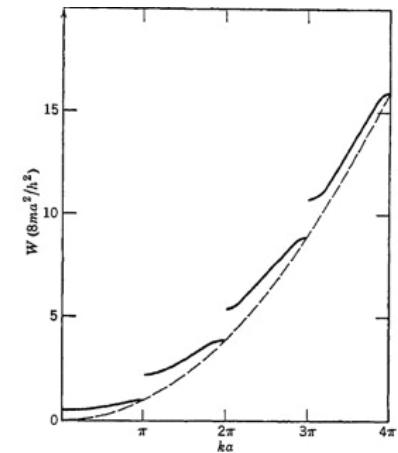Wave propagation in periodic structures  
→ (1) filters and (2) physics




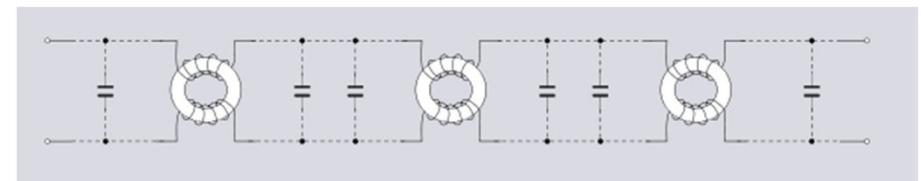Earliest history : telegraph loading coils  
Heaviside (1881)




[https://en.wikipedia.org/wiki>Loading\\_coil](https://en.wikipedia.org/wiki>Loading_coil)

# Distributed Amplifier

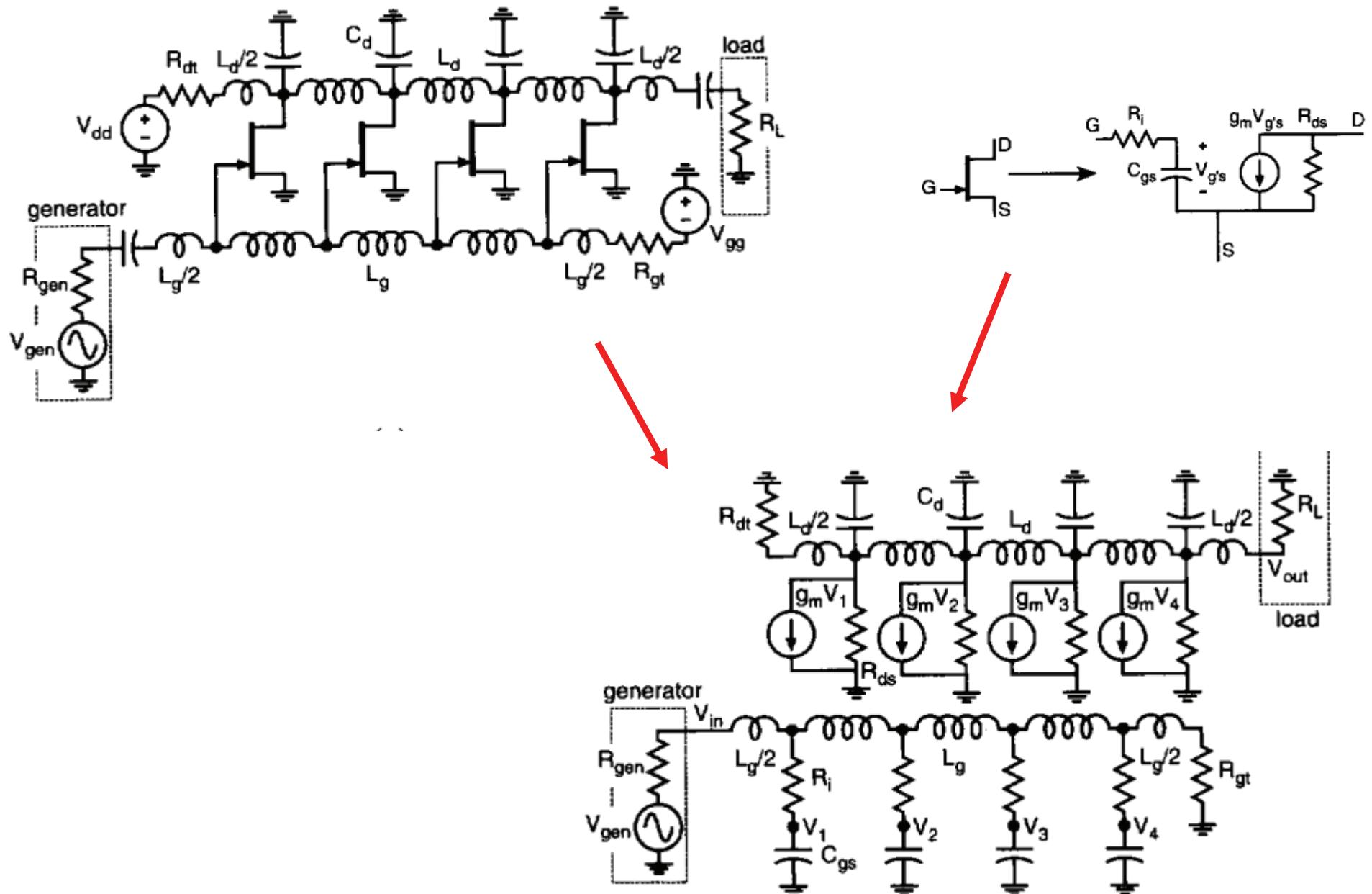


# Over-simplifying the model:

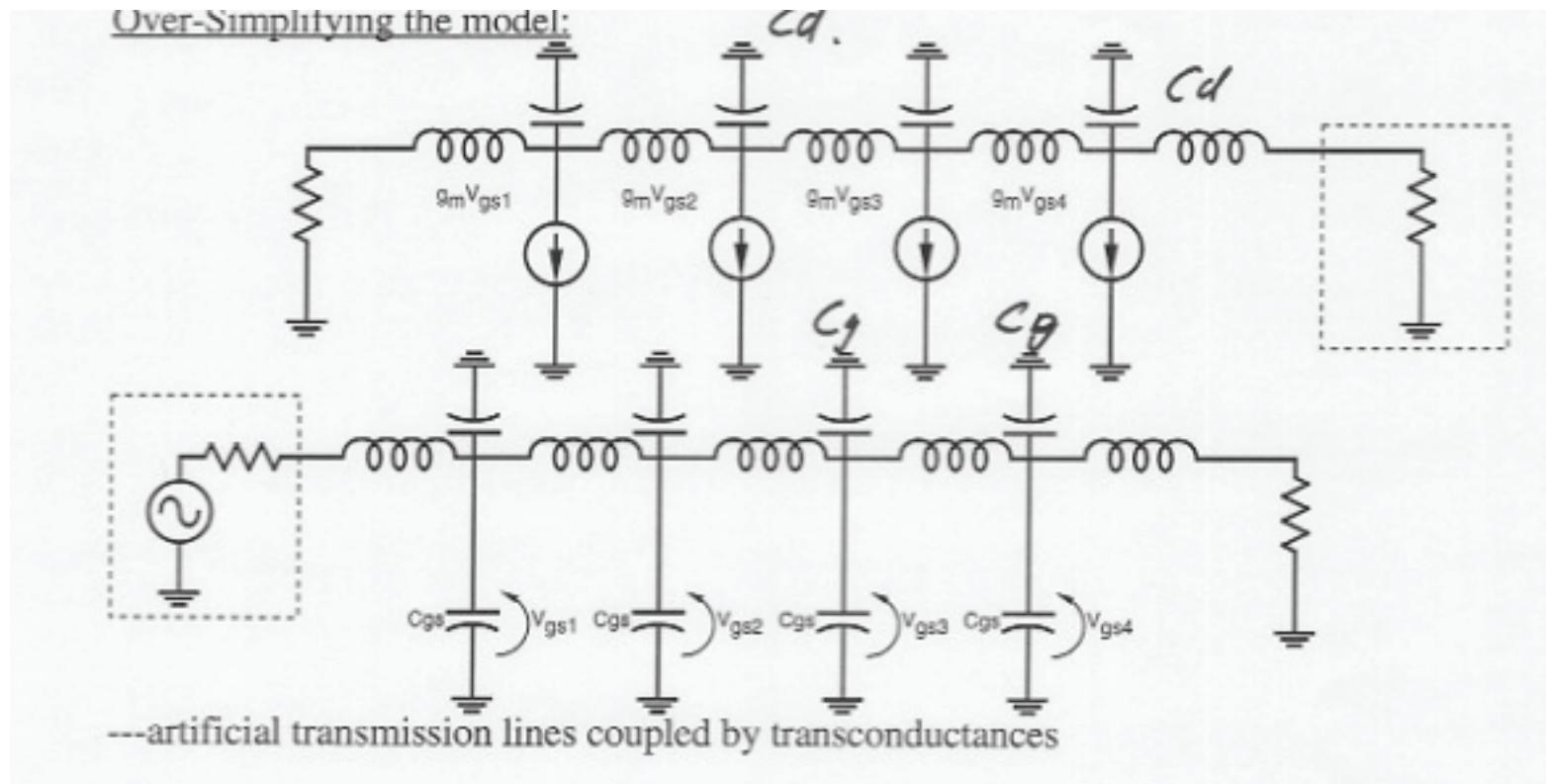

# Really over-simplifying the model:

---

Really-over simplifying the model

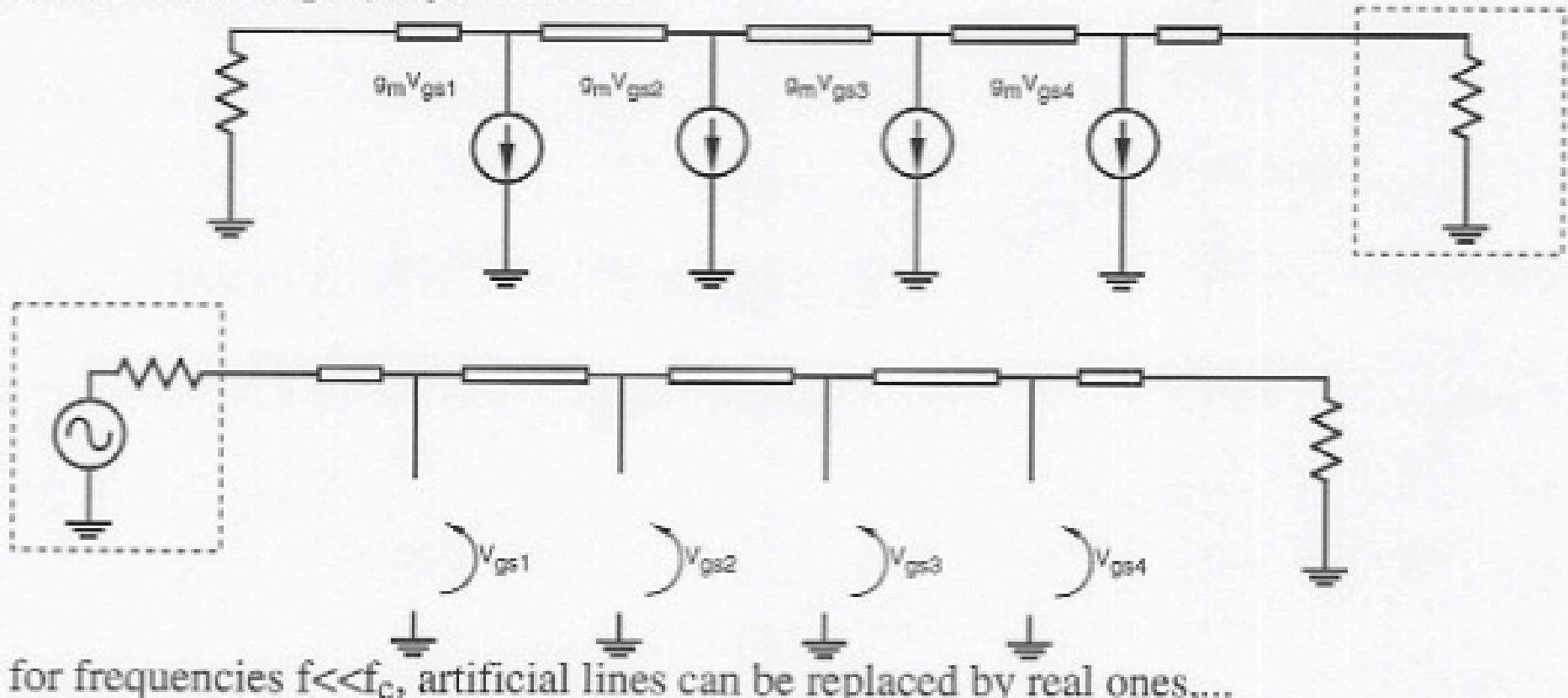


for frequencies  $f \ll f_c$ , artificial lines can be replaced by real ones,...

$$T_d = \sqrt{L_d C_d} \quad Z_d = \sqrt{L_d / C_d} \quad T_g = \sqrt{L_g (C_g + C_{gs})} \quad Z_g = \sqrt{L_g / (C_g + C_{gs})}$$

Clearly we want  $Z_d = Z_g = 50\Omega$ ; we also want  $T_d = T_g$ .

Above model shows that bandwidth  $\approx 1/\pi\sqrt{L_g(C_g + C_{gs})}$  if  $T_g = T_d$

# Distributed amplifier gain

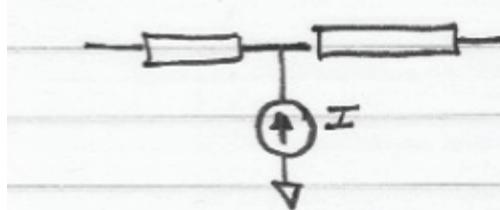

From symmetry, individual current generator develops equal waves in both directions.

$$\begin{array}{c} +V \\ -V \\ \leftarrow \overbrace{\quad}^{\rightarrow} \\ I^- = V^- / Z_0 \end{array}$$

$$\begin{array}{c} +V^+ \\ -V^- \\ \leftarrow \overbrace{\quad}^{\rightarrow} \\ I^+ = V^+ / Z_0 \end{array}$$

$$I^+ + I^- = I$$

Hence  $I^+ = I/2$   
and  $V^+ = Z_0 I/2$

each successive device (FET) adds a current  $I/2$  to the forward wave.

If they add in phase (If ..)

then total voltage after  $n$  devices


$$V^+ = n Z_0 I/2 = -\frac{n}{2} Z_0 g_m V_{gs} = -\frac{n}{2} Z_0 g_m V_{in}$$

Forward gain =  $-n g_m Z_0 / 2$

Approaching the Bragg Frequency, the line will no longer transmit signals.

# Distributed amplifier gain: simplest model

---

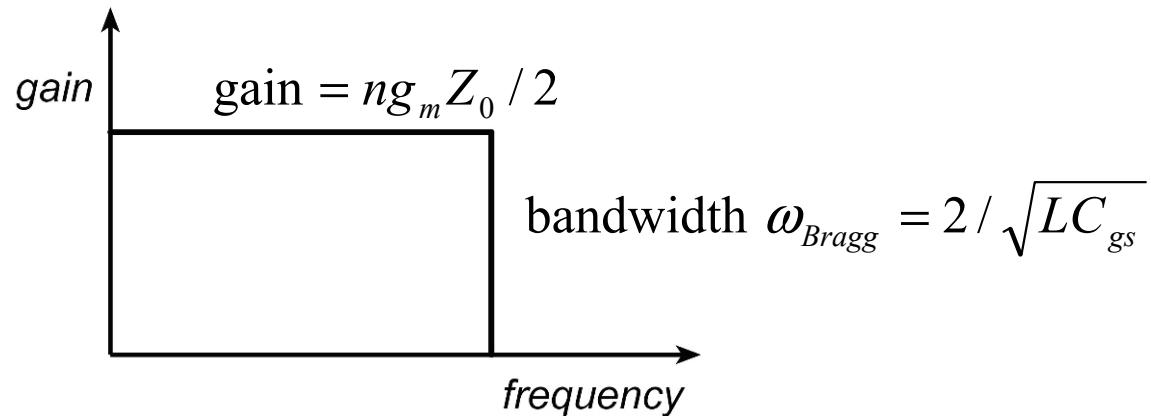

In this case, only the periodic lines limit the amplifier bandwidth.

Other limits :  
velocity mismatch  
losses (transistor and line resistances)


# Delay mismatch

---

on the issue of delays:

$T_d$  = inter-device delay on drain line

$T_g$  = " " " " " gate "

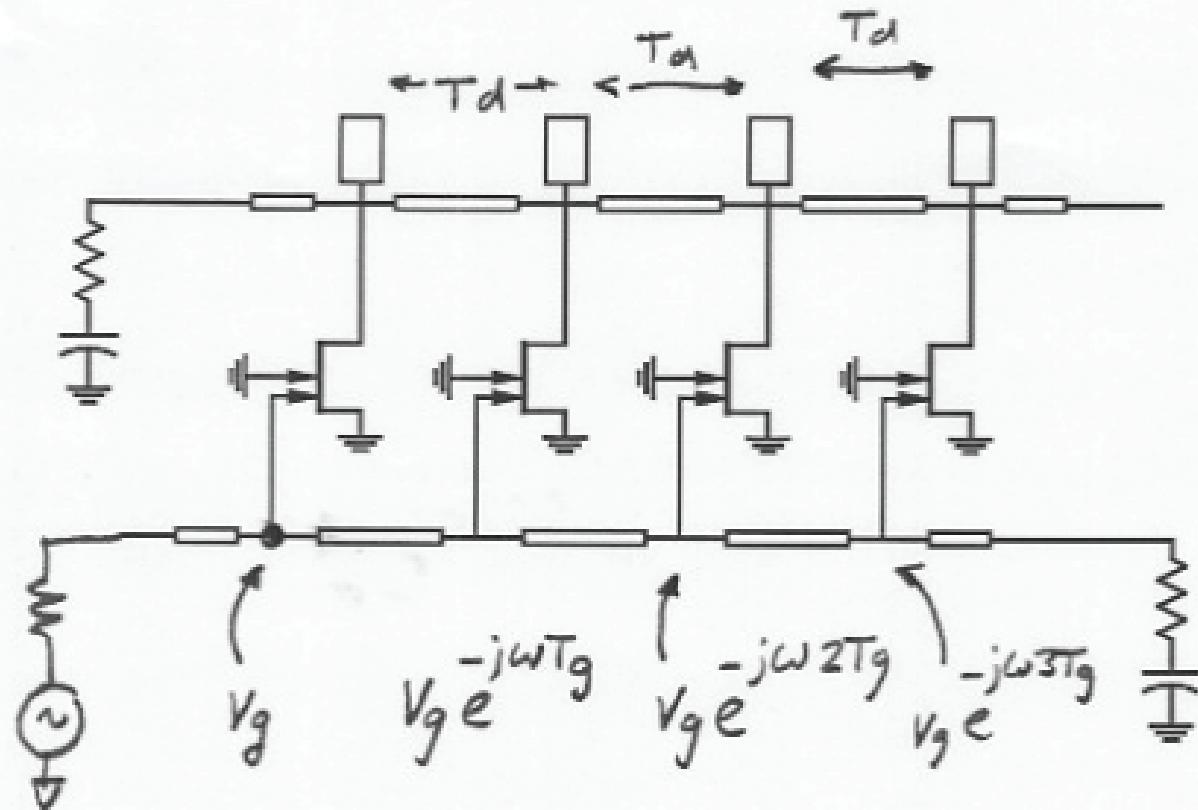

# Delay mismatch

---

Neglect the delays of the first gate-line section and the last drain-line section, as these are common to all signals:

FET #1

$$\begin{cases} \text{gate}_1 & V_g e^{-j\omega T_g} \\ \text{drain}_1 & g_m V_g e^{-j\omega T_g} \end{cases}$$

$$\text{after reaching output: } -\frac{Z_0 g_m}{2} V_g e^{-j\omega T_g} e^{-j\omega 3T_d}$$

FET #2

$$\begin{cases} \text{gate}_1 & V_g e^{-j\omega T_g} \\ \text{drain}_1 & g_m V_g e^{-j\omega T_g} \end{cases}$$

$$\text{after reaching output: } -\frac{Z_0 g_m}{2} V_g e^{-j\omega T_g} e^{-j\omega 2T_d}$$

# Delay mismatch

Neglect the delays of the first gate-line section and the last drain-line section, as these are common to all signals:

FET #1  
1 gate  $V_o e^{-j\omega T_g}$   
Total output (4 Fets)

$$V_{out} = -V_g \cdot \frac{Z_0 g_m}{z} \left[ e^{-j\omega T_g} e^{-j3\omega T_d} + e^{-j\omega T_g} e^{-j\omega 2T_d} \right. \\ \left. + e^{-j2\omega T_g} e^{-j\omega T_d} + e^{-j3\omega T_g} e^{-j\omega T_d} \right]$$

phase factors (or delays) must all be equal for outputs to add in-phase.

# Delay mismatch


---

Suppose  $T_g$  &  $T_d$  are mismatched by  $\Delta T = T_d - T_g$




$V_{out}$  delay  $T_{fixed}$ , so who cares?

$$V_{out} = -V_g \frac{Z_0 g_m}{2} e^{-3j\omega T_g} \times \left[ e^{-j3\omega \Delta T} + e^{-j2\omega \Delta T} + e^{-j\omega \Delta T} + 1 \right]$$

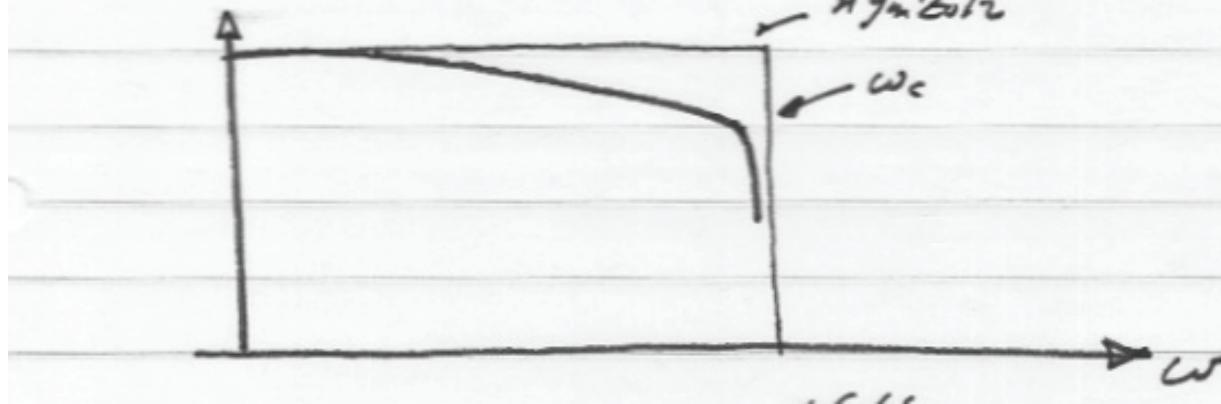This will result in a roll-off in the frequency response:


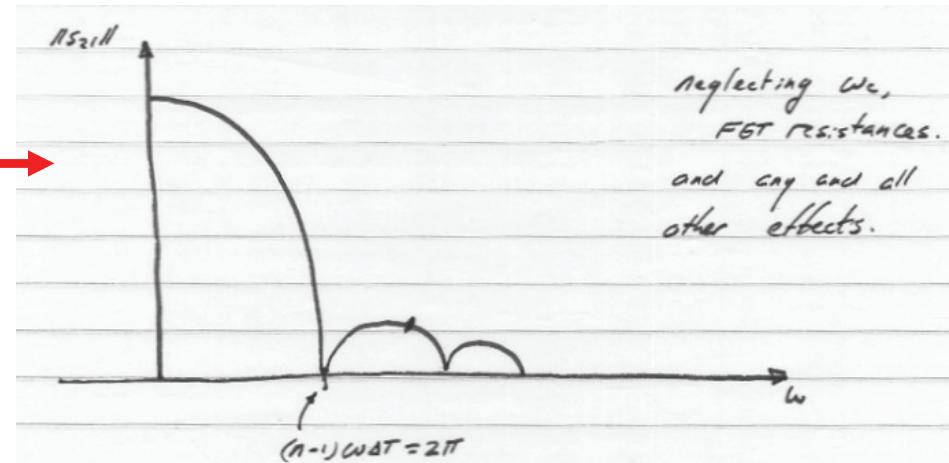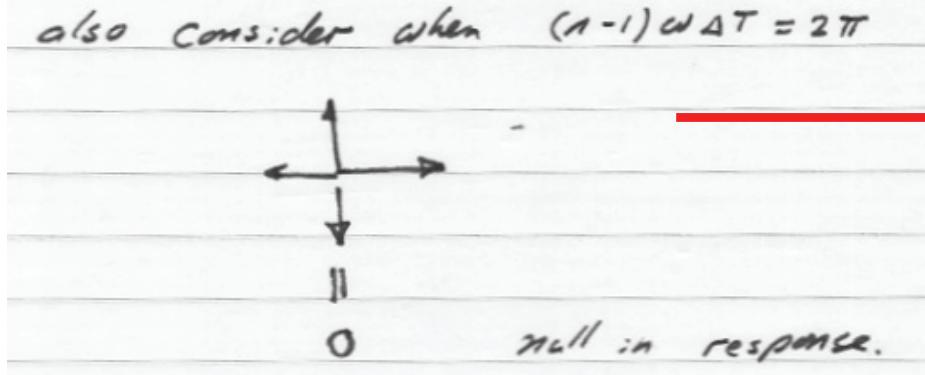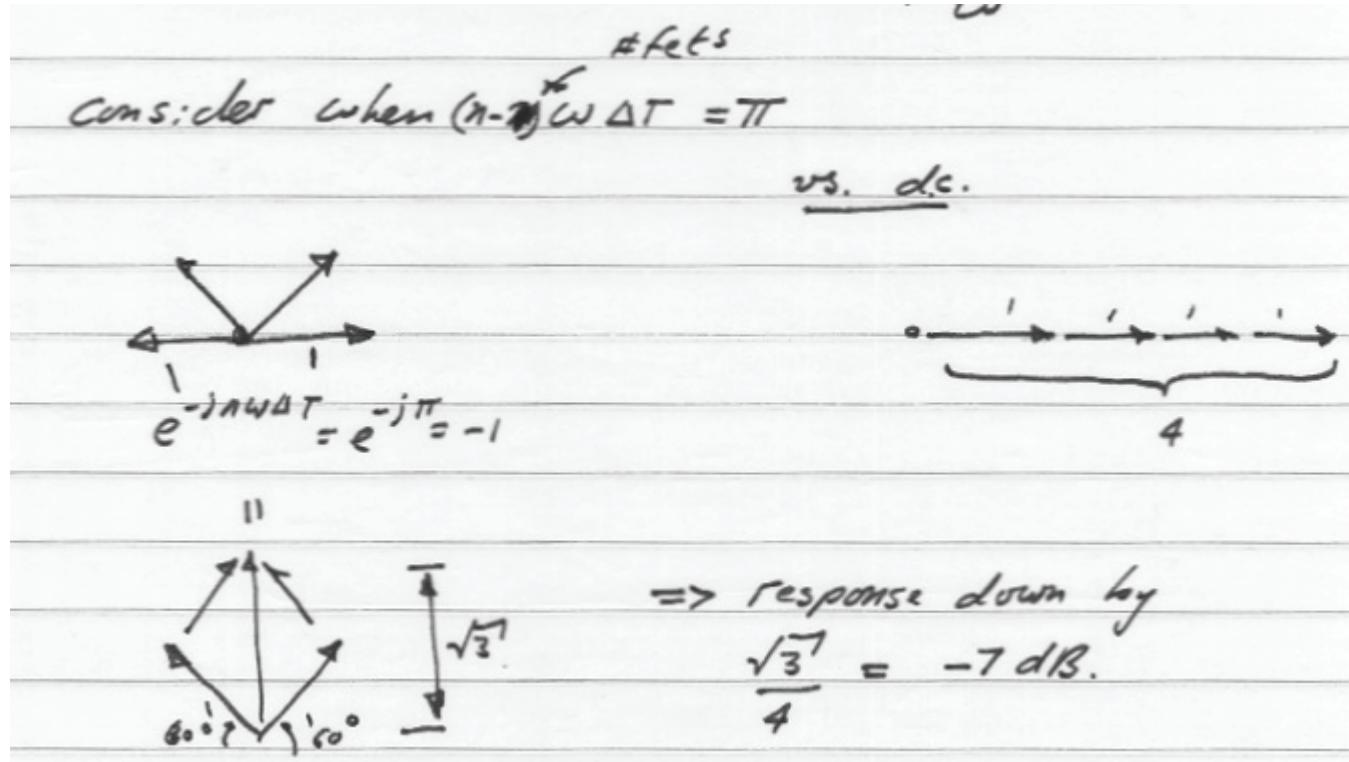
# Delay mismatch → out-of-phase signals → rolloff



# Input resistance: series-parallel transformation


---

$$\begin{aligned}
 Z &\Rightarrow \text{Circuit Diagram} & Z = r + \frac{1}{j\omega C} \\
 Y &= \frac{1}{Z} = \frac{1}{r + \frac{1}{j\omega C}} = \frac{j\omega C}{1 + j\omega rC} = \frac{j\omega C}{1 + \omega^2 r^2 C^2} \\
 &= \frac{j\omega C(1 - j\omega rC)}{(1 + \omega^2 r^2 C^2)} = \frac{j\omega C}{1 + \omega^2 r^2 C^2} + \frac{-\omega^2 C^2 r}{1 + \omega^2 r^2 C^2} \\
 &= jb + g
 \end{aligned}$$

$$\begin{aligned}
 \Rightarrow \tilde{r} \parallel \frac{1}{\tilde{c}} & \quad \tilde{r} = \frac{1}{\omega^2 C^2 r} (1 + \omega^2 C^2 r^2) \\
 & \quad \tilde{c} = c / (1 + \omega^2 C^2 r^2) \\
 \tilde{r} \parallel \frac{1}{\tilde{c}} & \quad \left. \begin{array}{l} \tilde{r} \approx \frac{1}{\omega^2 C^2 r} \\ \tilde{c} \approx c \end{array} \right\} \begin{array}{l} \text{for} \\ \omega \ll 1/rC \\ (\text{good approx}) \end{array}
 \end{aligned}$$


# With transistor resistances (1):

---

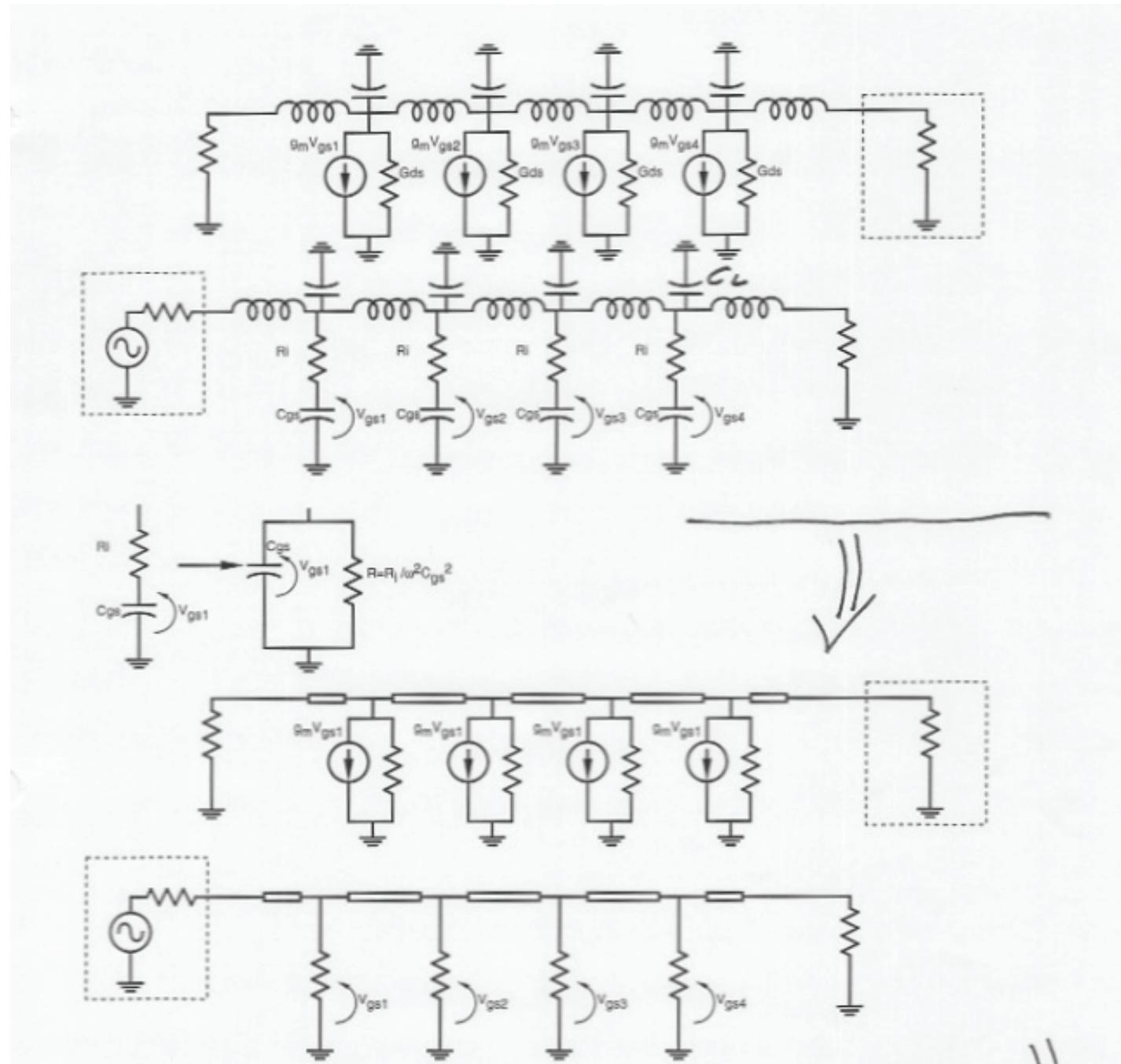

# With transistor resistances (1):


---

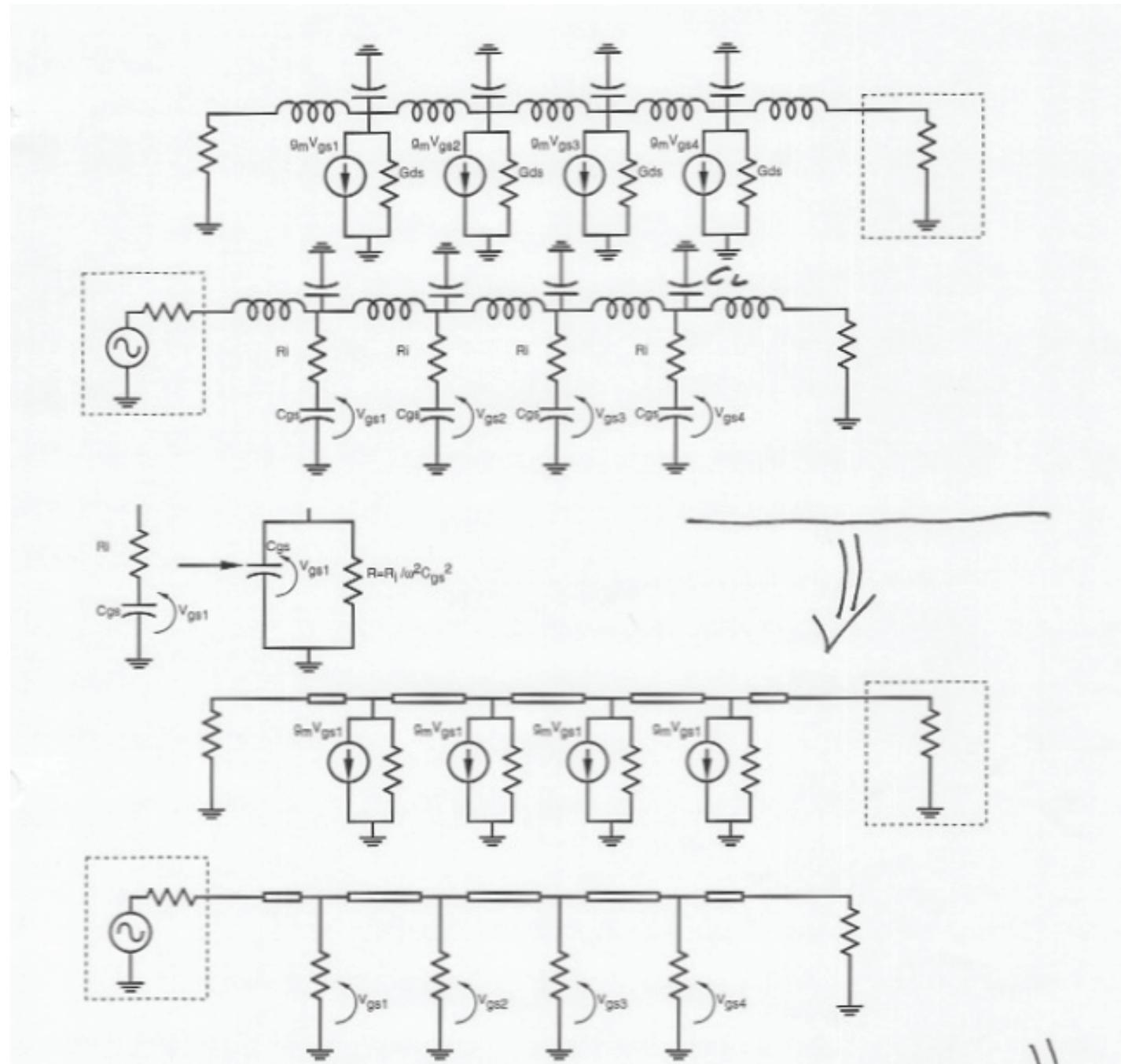
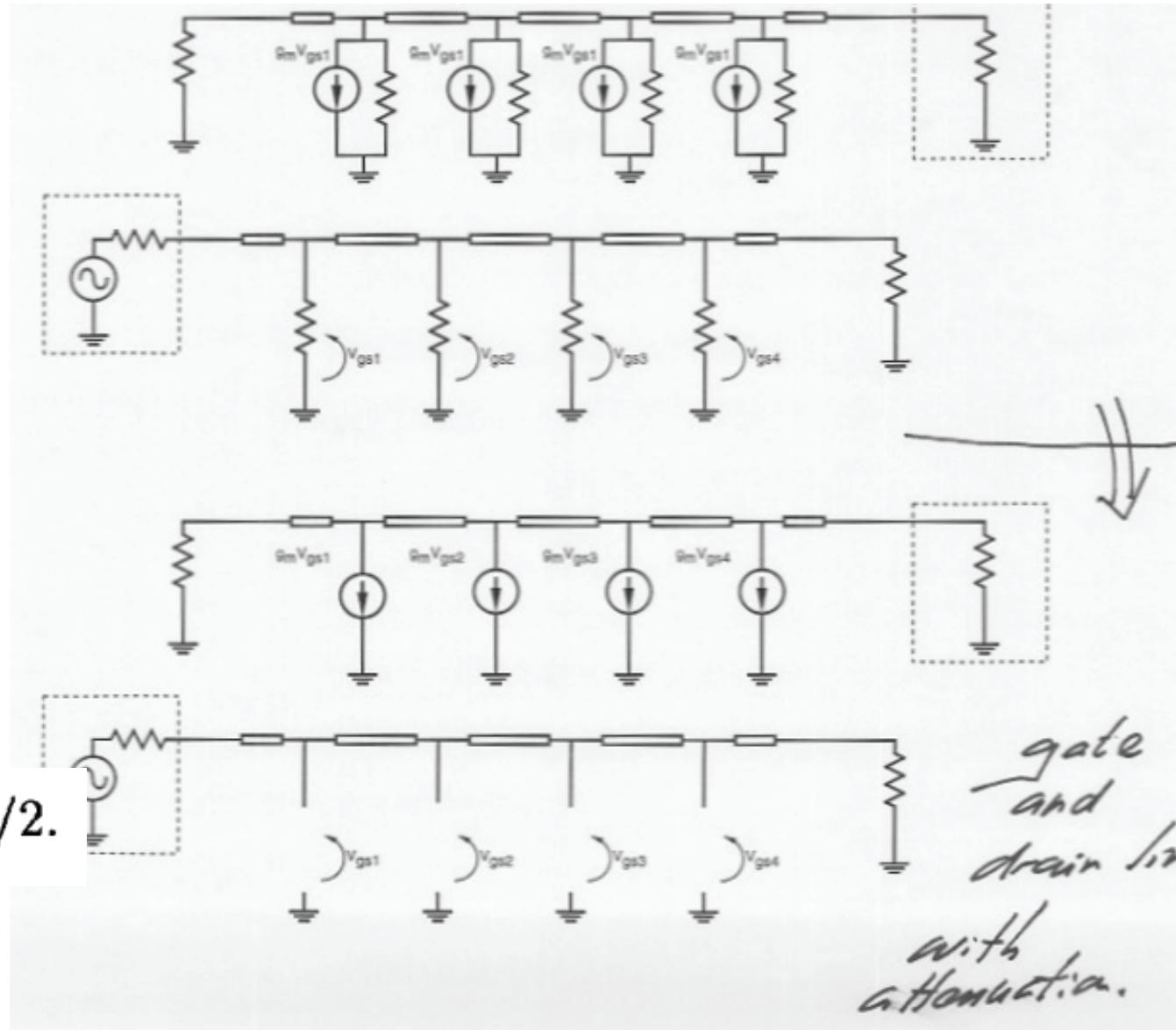
# With transistor resistances (2):

$$\alpha_d \cong Z_d / 2R_{ds}.$$

$$\alpha_g \cong \omega^2 C_{gs}^2 R_i Z_g / 2.$$



# Line losses and bandwidth

---

Attenuation per section on gate line:

$$A_g \approx \frac{Z_0}{2r} \quad \text{for } f \gg Z_0$$

$$= \omega^2 C_p^2 r_i Z_0 / 2$$

Attenuation per section on drain line

$$A_d \approx \frac{Z_0}{2r_{ds}} = Z_d G_{ds}/2 \quad \text{for } G_{ds} \ll 1/Z_0$$

Gate line attenuation generally dominates, particularly  
when dual-gate Fets are used (very low  $G_{ds}$ )

# Line losses and bandwidth

Analyze, neglecting all other effects

Fet #1

$$\text{gate 1: } V_g e^{-A_g/2} \leftarrow \frac{1}{2} \text{ line section}$$

$$\text{drain 1: } g_m V_g e^{-A_g/2}$$

after reaching output:

$$-g_m \frac{Z_0}{2} V_g e^{-A_g/2} e^{-Ad(3\frac{1}{2})}$$

Fet #2

$$\text{gate 2 } V_g e^{-A_g(1\frac{1}{2})}$$

$$\text{drain 2 } g_m V_g e^{-A_g \frac{3}{2}}$$

after reaching output:

$$-g_m \frac{Z_0}{2} V_g e^{-A_g \frac{3}{2}} e^{-Ad(2\frac{1}{2})}$$

etc

Total Output (4 fets)

$$V_{out} = -(V_g Z_0 g_m / 2) \times e^{-A_g/2} e^{-Ad/2} \times$$

$$\left[ e^{-3Ad} + e^{-A_g - 2Ad} + e^{-2A_g - Ad} + e^{-3A_g} \right]$$

# Line losses and bandwidth

---

A more simple interpretation :

Examining gate-line losses, the input voltage to the  $N$ th transistor is attenuated by  $e^{-(N-1/2)\alpha_g}$ . Given a desired high-frequency cutoff  $\omega_{\text{high}}$ , increasing the number of transistors beyond  $N_{\text{max}}$ , given by

$$N_{\text{max}}\omega_{\text{high}}^2 C_{\text{gs}}^2 R_i Z_g \simeq 1 \quad (5)$$

does not increase the high-frequency gain because transistors far from the input are not driven. This is Ayasli's criterion [42].

Examining the drain-line losses, the output of the 1st transistor is attenuated by  $e^{-(N-1/2)\alpha_d}$ . Increasing the number of transistors beyond  $N_{\text{max}}$  given by

$$N_{\text{max}} Z_d / R_{ds} \simeq 1 \quad (6)$$

does not increase the amplifier gain because transistors near the input do not contribute to the amplifier output.

# To summarize

---

- Analyze input & output structures as synthetic lines, determine  $Z_g, Z_d, T_g, T_d, \omega_c$
- D.C. Gain is  $-g_m n Z_0 / 2$
- Bandwidth limits are  $\omega_c$ , delay mismatch on the z lines, and gate-line attenuation  $\propto \omega^2$
- Design requirements of  $Z_g = Z_d = Z_0$  and  $T_g = T_d$  force  $L_g = L_d$  and  $C_d = C_{gs}$
- As  $C_{gs} \gg C_{dss}$  for Fets, drain line must have the added capacitors to equalize delays

within the bandwidth, we have:

$$\omega < \omega_c$$

$$n \omega^2 C_{gs}^2 r_i Z_g \leq 1$$

$$(n-1) C_{dss} T \leq \pi / 2$$


$$A_o \approx -g_m Z_0 / 2$$

$$\text{also } n Z_d G_{ds} \leq 1$$

# Why use distributed amplifiers ?

Answer: Increased gain-bandwidth product  
without the use of matching (resonant) networks.

Simple Amplifier:

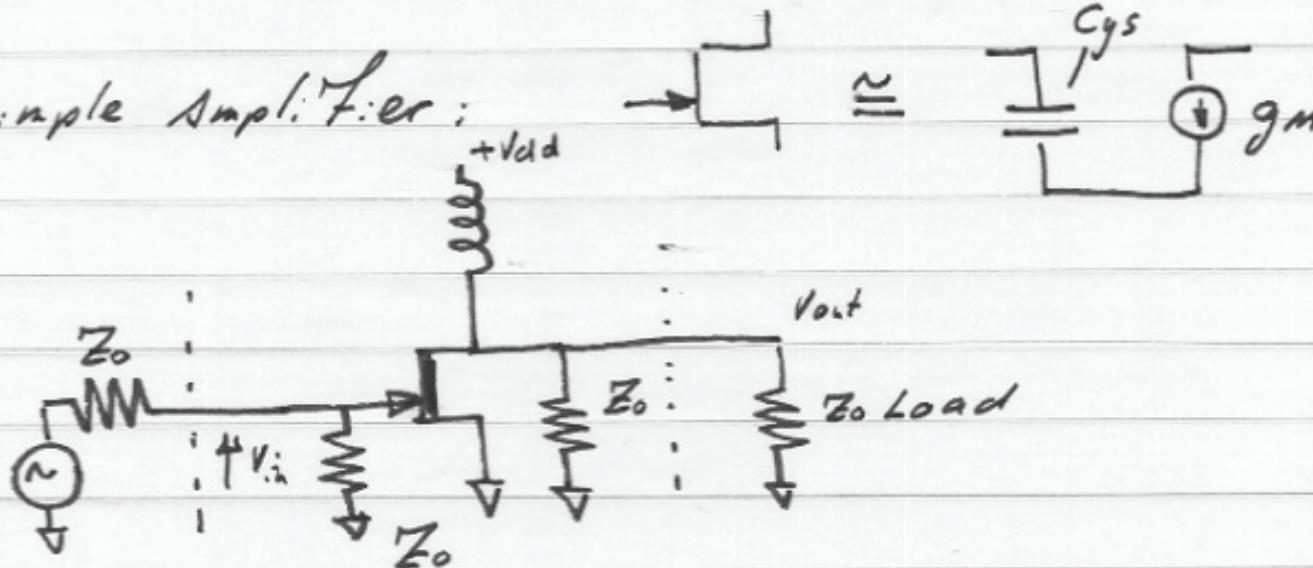

$$A_o = \text{DC gain} = g_m Z_0 / 2$$

$$\omega_m = \text{bandwidth} = \frac{1}{C_{gs} Z_0 / 2}$$

gain-bandwidth product




$$= A_o \omega_m = g_m / C_{gs} 2\pi = f_T$$

Increase transistor size :  $g_m, C_{gs}$  will increase. Increased gain, decreased bandwidth  
gain - bandwidth produce remains at  $f_T$  (less when all parasitics are included)

# Bandwidth of distributed amplifier

First : consider two forms of degeneration.

Model of  
unilateral device

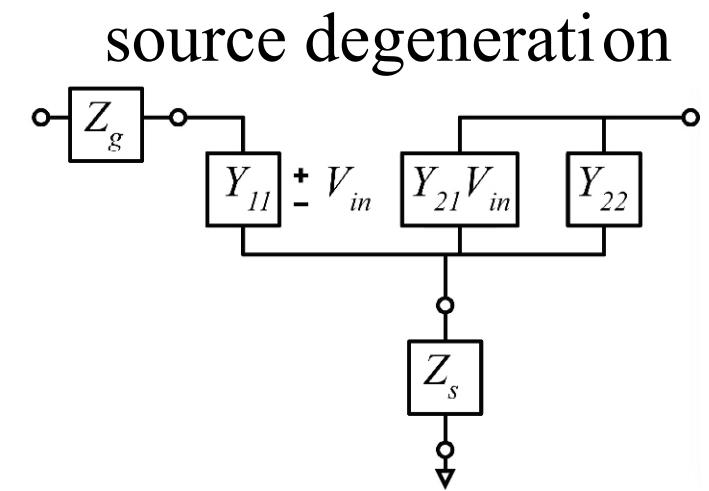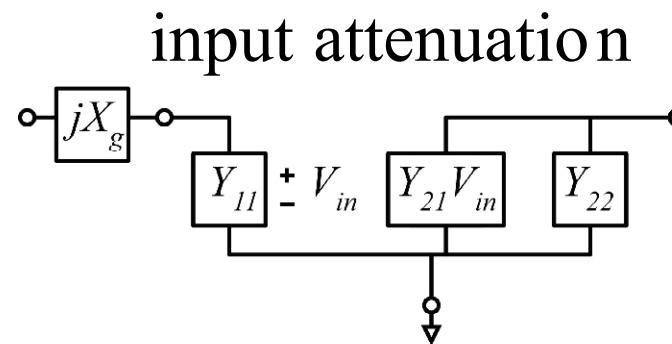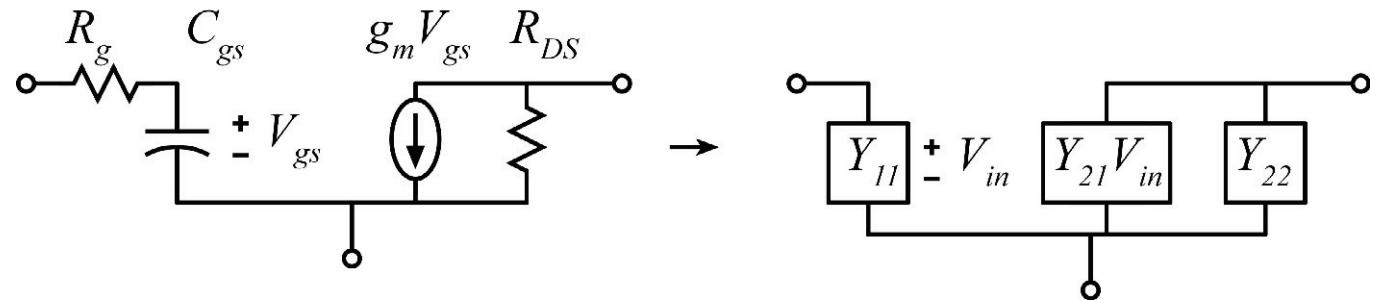


For brevity : analyze only input attenuation

Source degeneration with parallel RC combination also useful
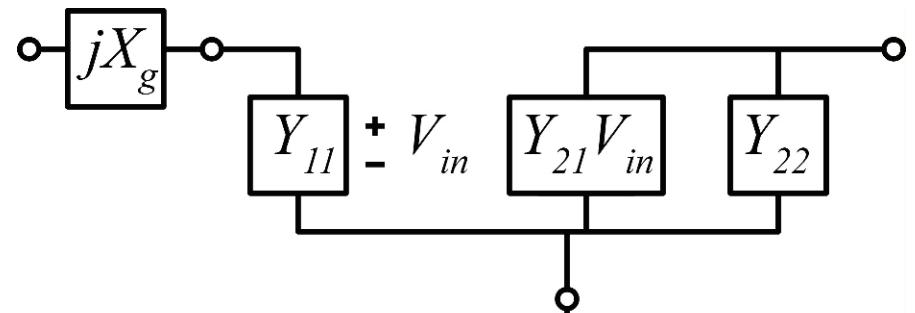
# Input degeneration

Overall network Y - parameters :  $Y_{new,ij}$



$$Y_{new,21} = \frac{1/Y_{11}}{1/jB_g + 1/Y_{11}} \cdot Y_{21} = \frac{jB_g}{G_{11} + jB_g + jB_{11}} \cdot Y_{21} \rightarrow \|Y_{new,21}\| = \frac{B_g}{(G_{11}^2 + (B_g + B_{11})^2)^{1/2}} \cdot \|Y_{21}\|$$

$$Y_{new,11} = \frac{1}{jX_g + 1/Y_{11}} = \frac{jB_g Y_{11}}{jB_g + Y_{11}} = \frac{jB_g (G_{11} + jB_{11})}{G_{11} + jB_g + jB_{11}} = \frac{jB_g (G_{11} + jB_{11})(G_{11} - jB_g - jB_{11})}{(G_{11}^2 + (B_g + B_{11})^2)}$$

$$Y_{new,11} = \frac{jB_g (G_{11}^2 - jG_{11}B_g - B_{11}(B_{11} + B_g))}{(G_{11}^2 + (B_g + B_{11})^2)}$$

$$G_{new,11} = \frac{B_g^2 G_{11}}{(G_{11}^2 + (B_g + B_{11})^2)} = G_{11} \cdot \frac{\|Y_{new,21}\|^2}{\|Y_{21}\|^2} \text{ and } G_{new,22} = G_{22}$$

$G_{11}$  is reduced,  $G_{22}$  is unchanged,  $\|Y_{21}\|$  is reduced,


and, as expected ( $jX_g$  is lossless),  $G_{max} = \|Y_{21}\|^2 / 4G_{11}G_{22}$  is unchanged

# Input degeneration with distributed amplifier

Suppose we apply degeneration to make

$$G_{11,new} = G_{22,new}$$

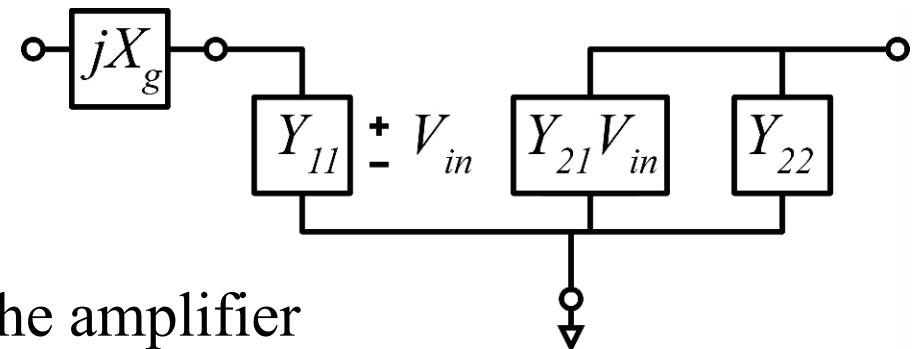at the upper 3-dB design frequency of the amplifier



Line losses per section :

$$\alpha_{in} = G_{new,11} Z_0 / 2, \quad \alpha_{out} = G_{22} Z_0 / 2 = G_{new,11} Z_0 / 2$$

Maximum # sections :  $n_{max} \alpha = 1/2$

$$\rightarrow n_{max} G_{new,11} Z_0 = n_{max} G_{22} Z_0 = 1$$

Circuit power gain


$$\|S_{21}\|^2 = \frac{n_{max}^2 \|Y_{new,21}\|^2 Z_0^2}{4} = \frac{\|Y_{new,21}\|^2}{4 G_{new,11} G_{22}} = \frac{\|Y_{21}\|^2}{4 G_{11} G_{22}} = G_{max}$$

# Maximum feasible TWA gain-bandwidth

---

Circuit power gain

$$\|S_{21}\|^2 = \frac{n_{\max}^2 \|Y_{new,21}\|^2 Z_0^2}{4} = \frac{\|Y_{new,21}\|^2}{4G_{new,11}G_{22}} = \frac{\|Y_{21}\|^2}{4G_{11}G_{22}} = G_{\max}$$

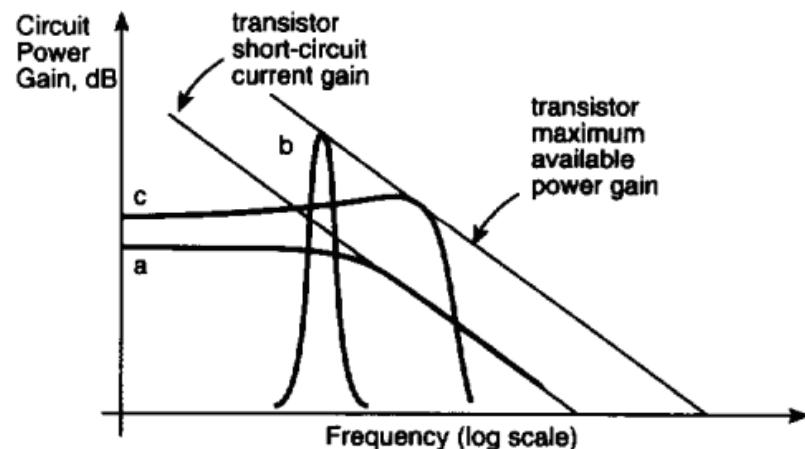


**Fig. 8.** Gain-frequency constraints of wideband lumped-element (a), resonant (b), and distributed (c) amplifiers .

A perfectly - designed TWA can attain gain =  $G_{\max}$   
 at the amplifier upper bandwidth limit

# Examples


112-GHz, 157-GHz, and 180-GHz InP HEMT  
Traveling-Wave Amplifiers

Agarwal, Trans. MTT, 12/1998

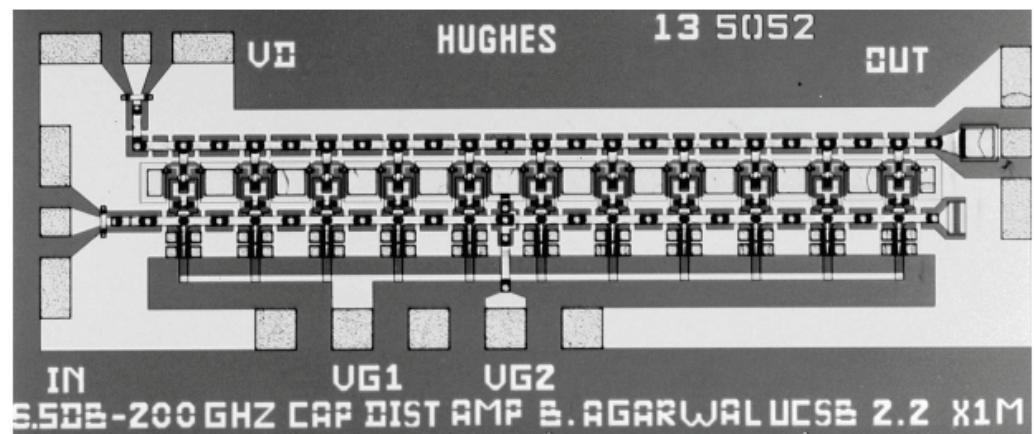

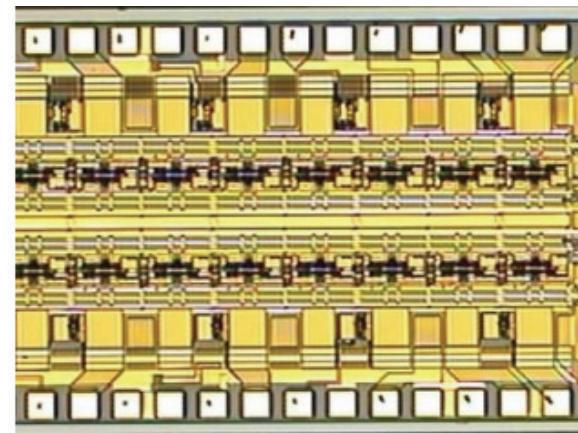**0.1–42 GHz InP DHBT distributed amplifiers  
with 35 dB gain and 15 dBm output**

Modulator driver for 40Gb/s optical links  
Krishnamurthy, Electronics letters, 2003



# Examples



In this power amplifier,  
we needed lines with  $Z_0 = 25\Omega$

A  $25\Omega$  line would have  
been much too wide

→ realized using  
synthetic line


arrows point to vias connecting  
to MIM capacitors

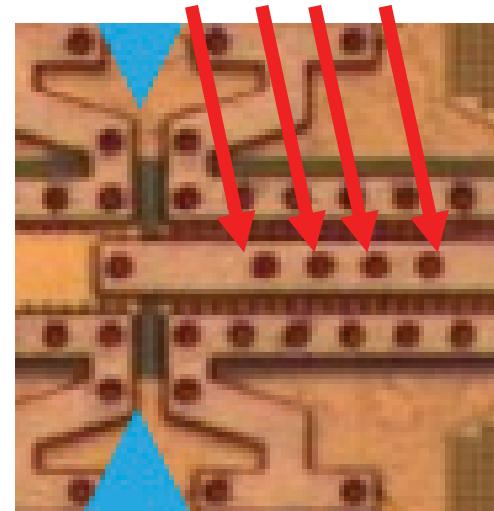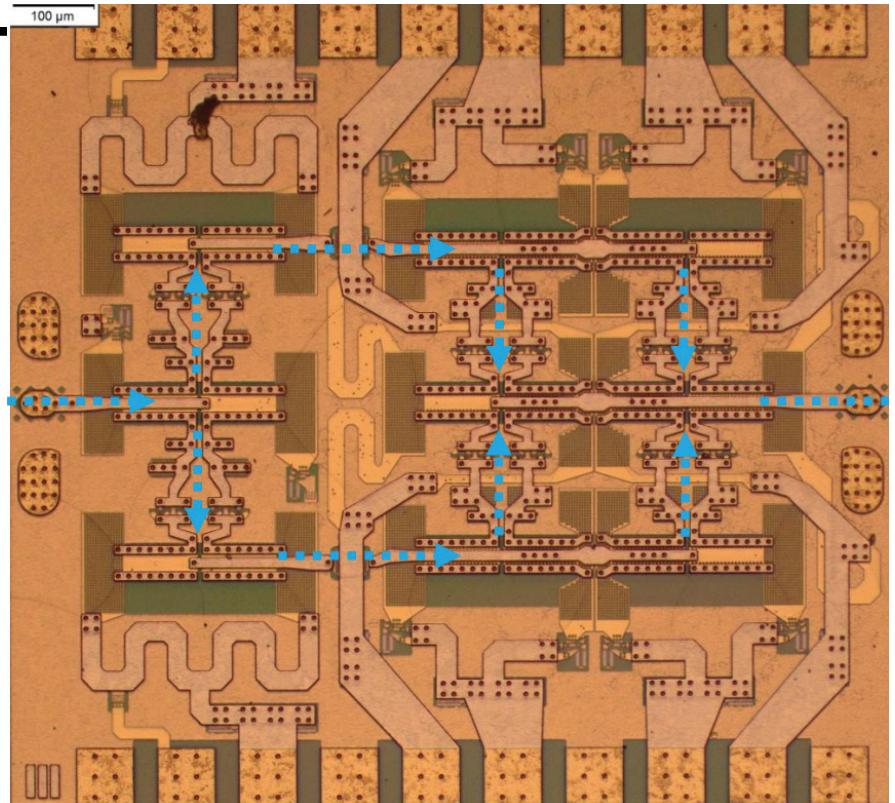86GHz power amplifier  
Park, Trans. MTT, 10/2014



# Examples

traveling wave optical modulator

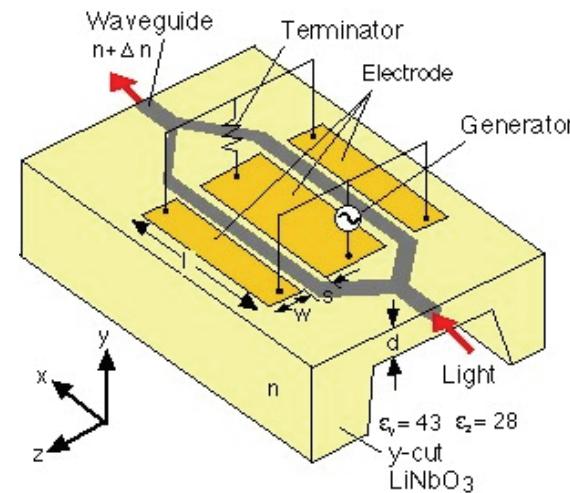

traveling wave tube

