

ECE 2C Final Exam

A

June 7, 2011

Do not open exam until instructed to.

Closed book: Crib sheet and 2 pages personal notes permitted

There are 4 problems on this exam, and you have 3 hours.


Use any and all reasonable approximations (5% accuracy is fine.) , ***AFTER STATING and approximately Justifying them.***

Name: Solut. on. A

Problem	Points Received	Points Possible
1a		5
1b		2
1c		5
1d		5
1e		5
1f		3
1g		10
2a		10
2b		10
3a		10
3b		10
3c		5
3d		5
3e		5
4a		10
4b		5
4c		5
4d		5
4e		5
total		100

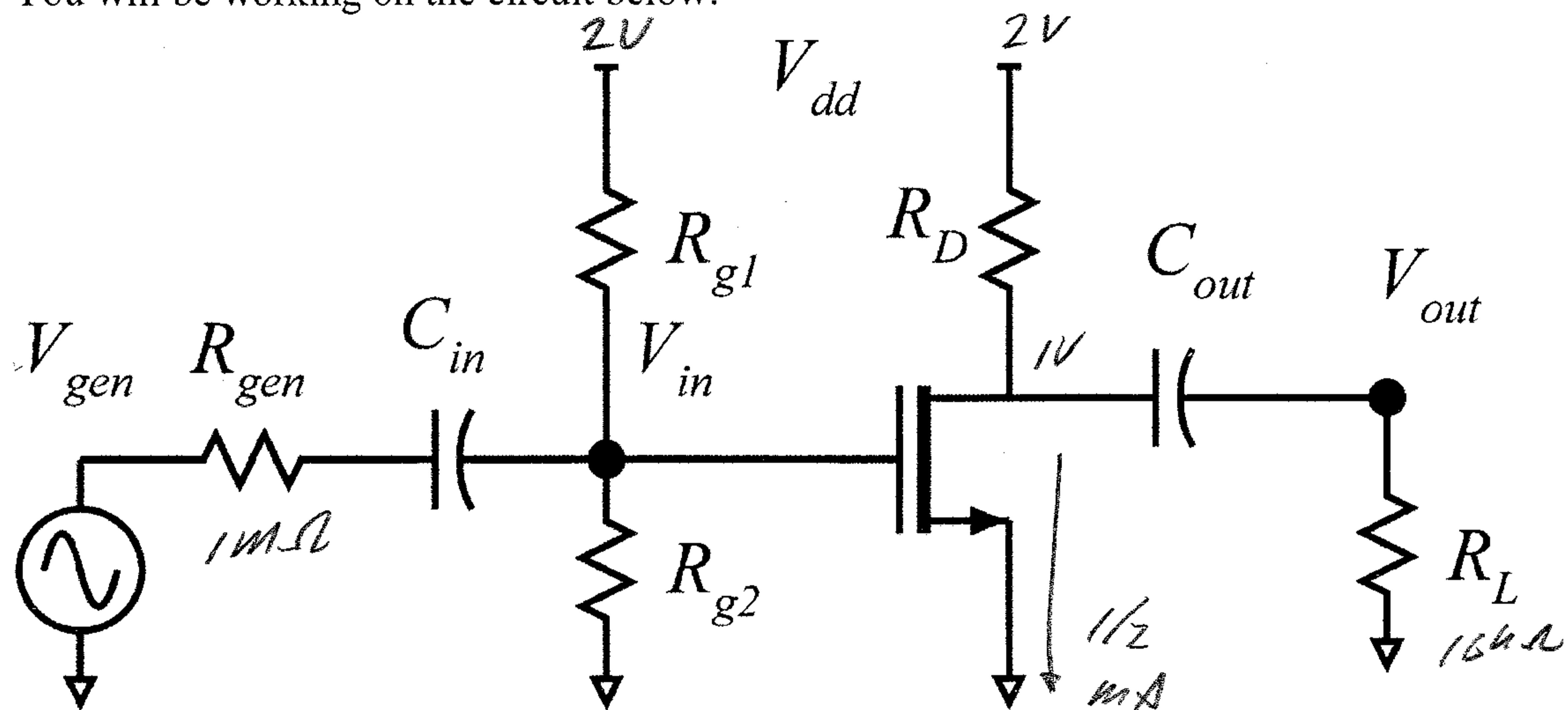Problem 1, 25 points

You will be working on the circuit below:



Q1 is a mobility-limited FET, i.e. $I_d = (\mu c_{ox} W_g / 2L_g)(V_{gs} - V_{th})^2(1 + \lambda V_{ds})$ where $(\mu c_{ox} W_g / 2L_g) = 4 \text{ mA/V}^2$, $\lambda = 0.05 \text{ V}^{-1}$, and $V_{th} = 0.30 \text{ V}$.

$$V_{dd} = +2.0 \text{ volts}$$

C_{in} and C_{out} are very big and have negligible AC impedance.

$$R_L = 10 \text{ k}\Omega$$

$$R_{gen} = 1 \text{ M}\Omega$$

Part A
soltu^z

$$I_d = 4 \text{ mA/V}^2 \cdot (V_{gs} - V_{th})^2 = 1/2 \text{ mA}$$

$$V_{gs} - V_{th} = \sqrt{1/8} \text{ V} = 0.354 \text{ V} \quad \textcircled{1}$$

$$V_{gs} = 0.654 \text{ V} \quad \textcircled{1}$$

$$\text{Current} = \mu s (R_{g1}, R_{g2})$$

$$R_{g2} = \frac{0.654 \text{ V}}{\mu s} = 654 \text{ k}\Omega \quad \textcircled{1}$$

$$R_{g1} = \frac{2 \text{ V} - 0.654 \text{ V}}{\mu s} = \frac{1.346 \text{ V}}{\mu s} = 1.346 \text{ M}\Omega \quad \textcircled{1}$$

$$R_{d1} = \frac{2 \text{ V} - 1/2}{1/2 \text{ mA}} = 2 \text{ k}\Omega \quad \textcircled{1}$$

Part a, 5 points

DC bias.


Q1 is to be biased with 1/2 mA drain current, and with 1.0 Volts drain voltage.
Ignore λ while solving this part.

Find: $R_{g1} = \frac{1.346\text{m}\Omega}{}, R_{g2} = \frac{654\text{k}\Omega}{}, R_d = \frac{246}{}$
The DC voltage at the gate of Q1. = 1V

Soln'ta on page 2.

Part b, 2 points

DC bias

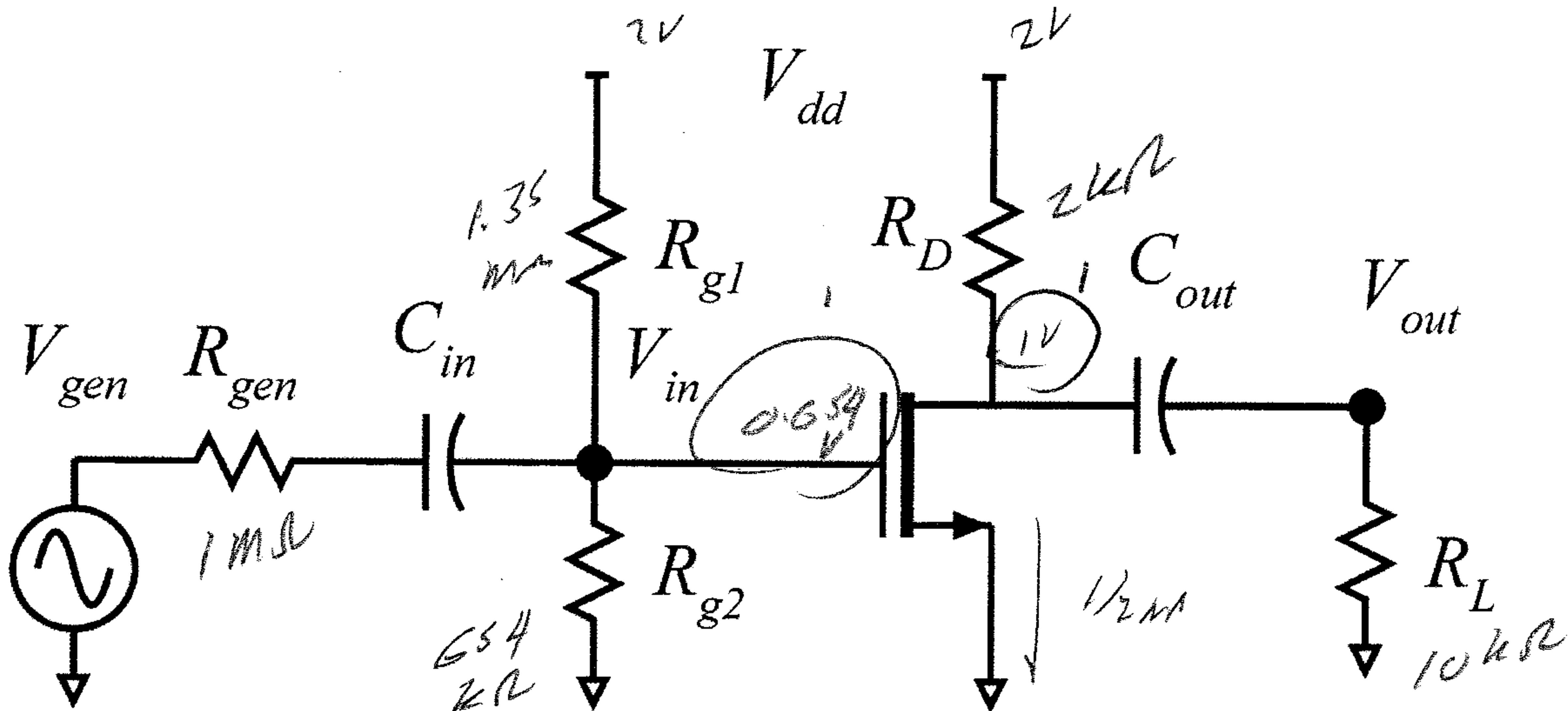

On the circuit diagram above, label the DC voltages at **ALL** nodes and the DC currents through **ALL** resistors

$$I_{ds} = 4 \text{ mA/V}^2 (V_{gs} - V_{th}) (1 + 1/k_m) \\ V_{th} = 0.3V$$

$$V_{gs} - V_{th} = 0.354V.$$

$$V_{dd} = 2.0V.$$

Part c:

$$g_m \geq \frac{4 \text{ mA}}{\text{V}^2} \cdot (V_{gs} - V_{th}) \cdot 2 = 0.25$$

$$\text{ok with or without } (1 + 1/k_m) = \frac{8 \text{ mA}}{\text{V}^2} \cdot (0.354V) = 2.832 \text{ mV/V} \\ \text{or } 2.832 \text{ mV/V} \approx 2.8 \text{ mV}$$

$$R_{ds} \approx \frac{V_{dd} + V_A}{I_{ds}} = \frac{16 + 2.0V}{1.2 \text{ mA}} = 212 \text{ k}\Omega$$

$$\text{or } \frac{1}{f_{tr}} = 40 \text{ Hz ok.}$$

25

Part c, 5 points


Find the small signal parameters of Q1. Use the mobility-limited model.

$$gm = \frac{2.83mA/V}{40m\Omega}$$

see page 4.

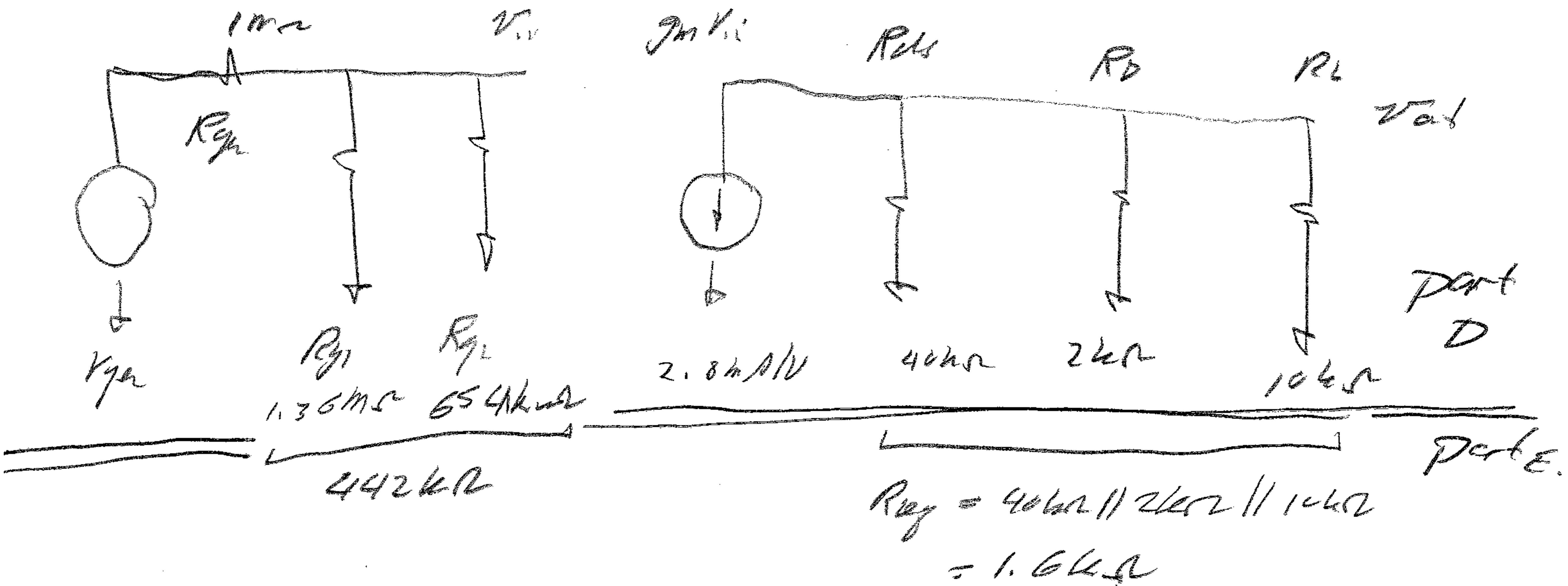Part d, 5 points

Replacing the transistor with its small-signal model, draw a small-signal equivalent circuit diagram for the amplifier. Give values for all elements on the diagram.



Part e, 5 points.

Find the small signal voltage gain (V_{out}/V_{in}) of Q1.

$$V_{out}/V_{in} = \underline{-4.48}$$

(2.5) $\left[\frac{V_{out}}{V_{in}} = -g_m R_{eq} = -2.8mS \cdot 1.6k\Omega = -4.48 \right]$

(2.5) $\left[R_{eq} = R_b \parallel R_{os} \parallel R_{RE} = 1.6k\Omega \right]$

Part f, 3 points

Find the *** amplifier *** input resistance, Vin/Vgen, and Vout/Vgen

$$R_{in, \text{amplifier}} = 442 \text{ k}\Omega$$

$$V_{in}/V_{gen} = 0.307$$

$$(V_{out}/V_{gen}) = -1.37$$

① $R_{in, \text{amp}} = R_p \parallel R_{g2} = 442 \text{ k}\Omega$

② $V_{in}/V_{gen} = \frac{R_{in}}{R_{in} + R_{gen}} = \frac{442 \text{ k}\Omega}{442 \text{ k}\Omega + 1 \text{ M}\Omega} = 0.307$

③ $\frac{V_o}{V_{gen}} = \frac{R_o}{R_i} \cdot \frac{V_i}{V_{gen}} = 0.207 \cdot (-4.48) = -1.37$

Part g, 10 points

Now you must find the maximum signal swings. Find the output voltage due to the knee voltage and due to cutoff in Q1.

Cutoff of Q1; Maximum ΔV_{out} resulting = + 0.80V

Knee voltage of Q1; Maximum ΔV_{out} resulting = - 0.354V

⑤ Cutoff

$$R_D = 1.6 \text{ k}\Omega$$

$$I_{out} = I_{DQ}$$

$$\Delta I_{DQ, max} = 1/2 \text{ mA decrease}$$

$$\Delta V_{D, max} = V_{DQ} \cdot 1.6 \text{ k}\Omega = 0.80 \text{ V}$$

positive.

⑥ Knee.

Bias

$$0.654V -$$

knee.

$$0.654V -$$

$$+ 0.3V \rightarrow 0.654V - 0.3V = 0.354V$$


(2.5)

$\Delta V_{out} = 1V - 0.354V = 0.645V$

(2.5)

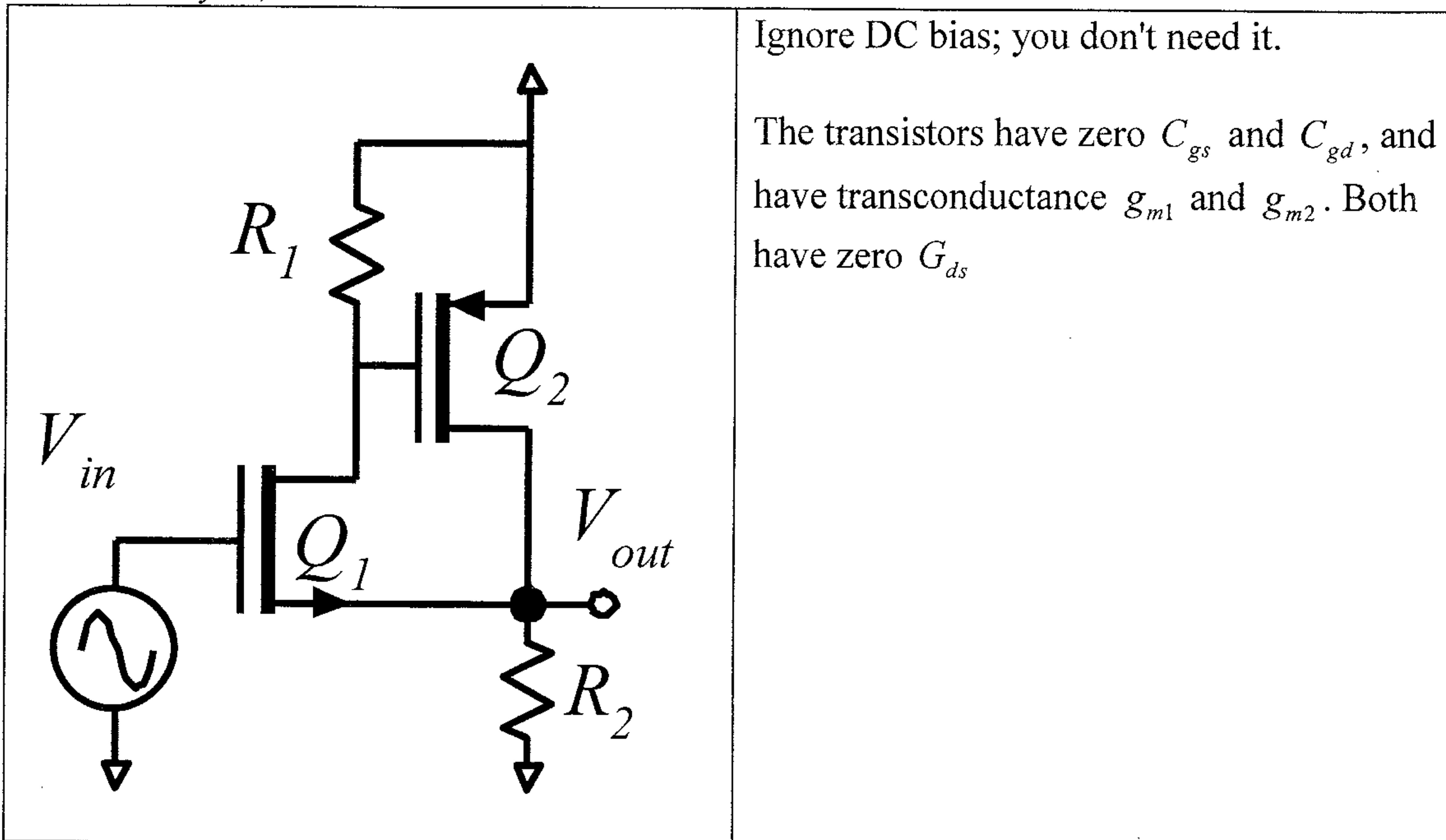
Problem 2: 20 points

Nodal analysis, transistor circuit models



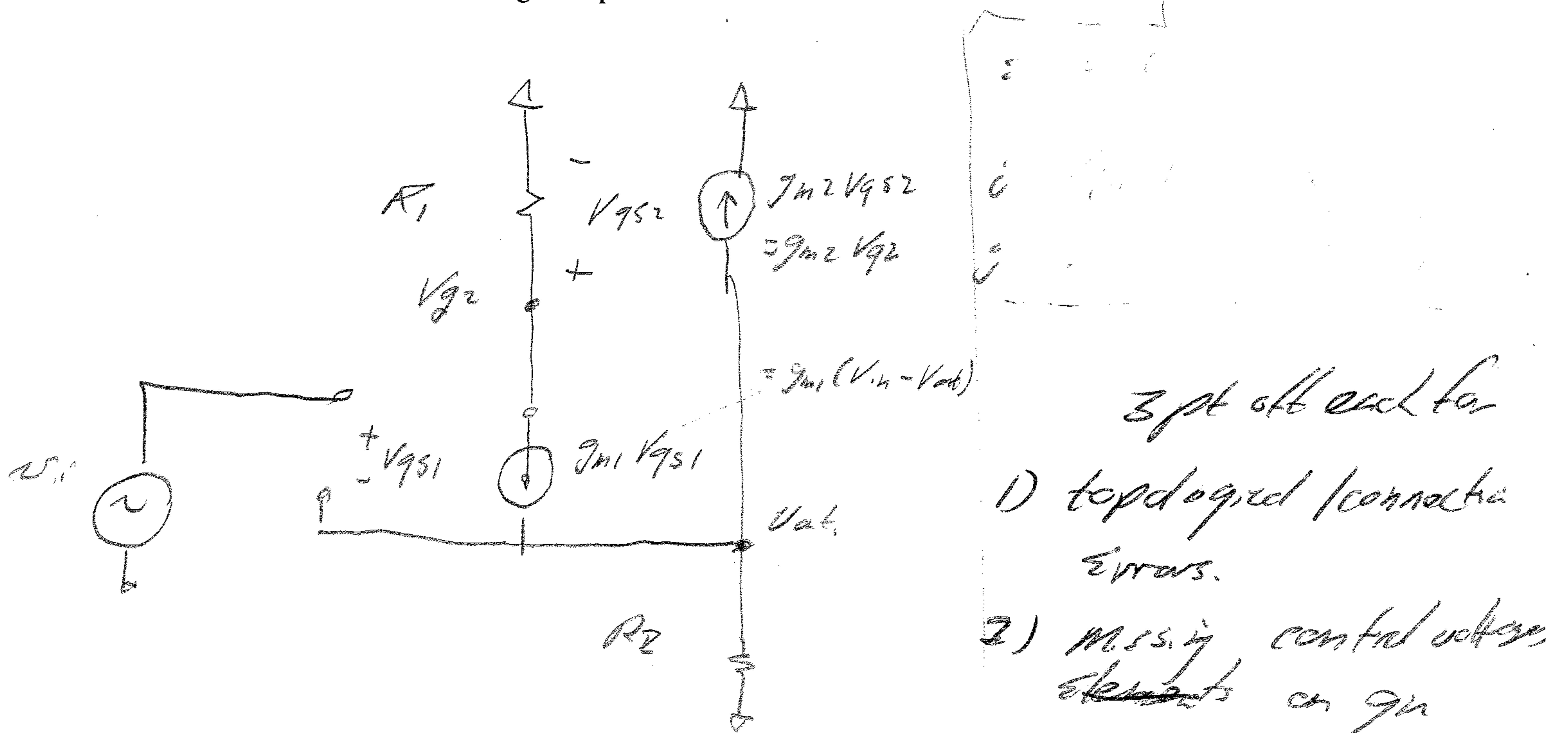Part a, 10 points

Draw an accurate small-signal equivalent circuit model of the circuit above.



Part b, 10 points

Using NODAL ANALYSIS, find V_{out}/V_{in} . Give both an algebraic expression, then find the numerical value with $gm_1=10 \text{ mS}$, $gm_2=20 \text{ mS}$, $R_1=1000 \text{ Ohms}$, $R_2=10,000 \text{ Ohms}$.

$$\frac{V_o}{V_{in}} = \frac{g_{m1} (g_{m2} + 1/R_1)}{g_{m1} g_{m2} + (g_{m1} + 1/R_1) \cdot 1/R_2} \quad (\text{algebraic expression})$$

$$\frac{V_o}{V_{in}} = \frac{0.9995}{1} \quad (1)$$

(value with $gm_1=10 \text{ mS}$, $gm_2=20 \text{ mS}$, $R_1=1000 \text{ Ohms}$, $R_2=10,000 \text{ Ohms}$)

$$\sum I = 0 \quad @ V_{g2}$$

$$g_{m1} V_{gs1} + V_{g2}/R_2 = 0$$

$$g_{m1} (V_{in} - V_{out}) + V_{g2}/R_2 = 0$$

$$\begin{matrix} V_{out} \\ V_{g2} \\ V_{in} \end{matrix}$$

$$\boxed{V_{out}(+g_{m1}) + V_{g2}(-1/R_2) = +V_{in} g_{m1}} \quad (3)$$

$$\sum I = 0 \quad @ V_{out}$$

$$V_{out}/R_2 + g_{m2} V_{g2} - g_{m1} (V_{gs1}) = 0$$

$$V_{out}/R_2 + g_{m2} V_{g2} - g_{m1} (V_{in} - V_{out}) = 0$$

$$V_{out}/R_2 + g_{m2} V_{g2} - g_{m1} V_{in} + g_{m1} V_{out} = 0$$

$$\boxed{V_{g2}(g_{m2}) + V_{out}(g_{m1} + 1/R_2) = g_{m1} V_{in}} \quad (3)$$

$$\frac{V_{out}}{V_{in}} = g_{m1} + g_{m2} \cdot \frac{1}{R_2}$$

$$\frac{V_{out}}{V_{in}} = g_{m1} + g_{m2} \cdot \frac{1}{R_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{N}{D}$$

$$N = \begin{vmatrix} g_{m1} & -1/R_2 \\ g_{m2} & g_{m2} \end{vmatrix} = g_{m1}g_{m2} + g_{m1}/R_2$$

$$= g_{m1}(g_{m2} + 1/R_2)$$

$$D = \begin{vmatrix} g_{m1} & -1/R_1 \\ g_{m1} + 1/R_2 & g_{m2} \end{vmatrix} = g_{m1}g_{m2} + (g_{m1} + 1/R_2) \cdot 1/R_1$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1}(g_{m2} + 1/R_1)}{g_{m1}g_{m2} + (g_{m1} + 1/R_2) \cdot 1/R_1}$$

2

$$g_{m1} = 10 \text{ mS}, g_{m2} = 20 \text{ mS}, R_1 = 1 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega$$

$$= \frac{10 \text{ mS} (20 \text{ mS} + 1 \text{ mS})}{10 \text{ mS} (20 \text{ mS}) + (10 \text{ mS} + 0.1 \text{ mS}) \cdot 1 \text{ mS}} = \frac{10(21)}{10(20) + (0.1) \cdot 1}$$


$$= \frac{210}{200 + 10} = 0.9995 \quad \textcircled{1}$$

$$g_{m2} = g_{m2} \cdot (1 + g_{m2} R)$$

$$R = \frac{g_{m2} R}{g_{m2} R + 1}$$

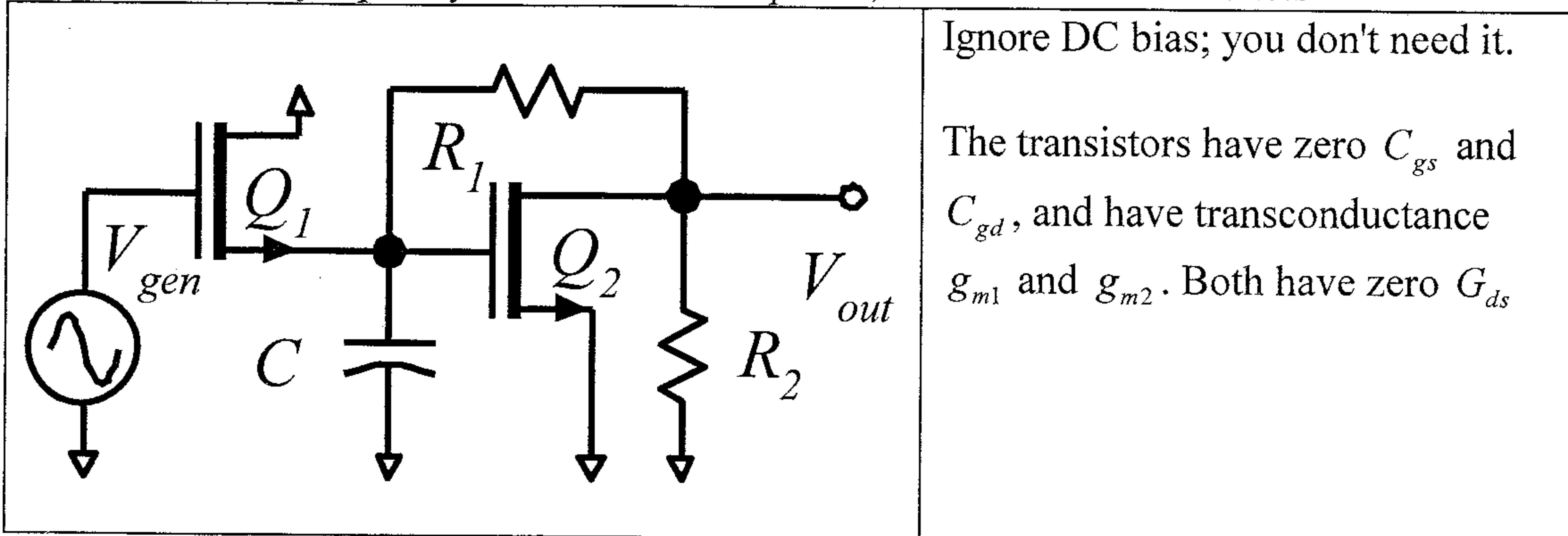
Problem 3: 35 points

Nodal analysis, frequency and transient response, transistor circuit models



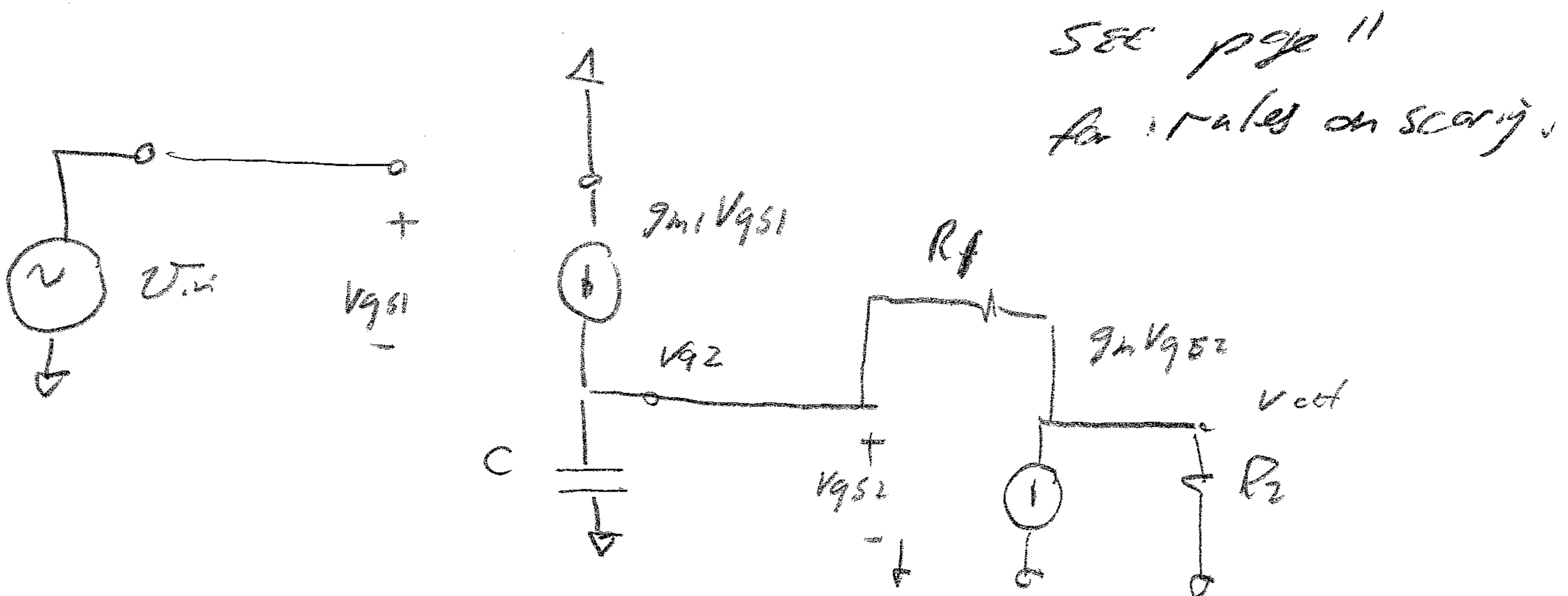Part a, 10 points

Draw an accurate small-signal equivalent circuit model of the circuit above.



$$Z_I = 0 \text{ @ } V_{g2}$$

part (b)

$$-g_m1(V_{g1}) + SC V_{g2} + GA(V_{g2} - V_{out}) = 0$$

$$-g_m1(V_{in} - V_{g2}) + SC V_{g2} + GA V_{g2} - GA V_{out} = 0$$

$$V_{g2}(g_m1 + GA + SC) + V_{out}(-GA) = g_m1 V_{in} \quad (3)$$

$$Z_I = 0 \text{ @ } V_{out}$$

$$g_m2 V_{g2} + V_{out} G_2 + (V_{out} - V_{g2}) G_1 = 0$$

$$g_m2 V_{g2} + V_{out} G_2 + V_{out} G_1 - V_{g2} G_1 = 0$$

14

$$V_{g2}(g_m2 - G_1) + V_{out}(G_1 + G_2) = 0 \quad (3)$$

Part b, 10 points

Using NODAL ANALYSIS, find the transfer function $V_o(s)/V_{gen}(s)$

The answer must be in standard form $\frac{V_o(s)}{V_{gen}(s)} = \frac{V_o}{V_{gen}} \Big|_{low-frequency-value} \times \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$,

$$\frac{V_o(s)}{V_{gen}(s)} = \frac{\text{[redacted]}}{\text{[redacted]}}$$

$$(g_m + G_1 + SC) V_{q2} + (-G_1) V_{out} = g_m V_i$$

$$(g_{m2} - G_1) V_{q2} + (G_1 + G_2) V_{out} = 0$$

$$\frac{V_{out}}{V_i} = \frac{N}{D} \quad \text{where}$$

$$N = \begin{vmatrix} g_m + G_1 + SC & g_m \\ g_{m2} - G_1 & 0 \end{vmatrix} = -g_m (g_{m2} - G_1)$$

$$D = \begin{vmatrix} g_m + G_1 + SC & -G_1 \\ g_{m2} - G_1 & G_1 + G_2 \end{vmatrix}$$

$$= (g_m + G_1)(G_1 + G_2) + SC(G_1 + G_2) + G_1 g_{m2} - G_1^2$$

$$= g_m G_1 + g_m G_2 + G_1 G_2 + g_{m2} G_1 + SC(G_1 + G_2)$$

$$\frac{V_{ext}}{V_{ee}} = \frac{-g_{m1}(g_{m2} - G_1)}{g_{m1}G_1 + g_{m1}G_2 + G_1G_2 + g_{m2}G_1 + SC(G_1 + G_2)}$$

$$= \frac{-g_{m1}(g_{m2} - G_1)}{g_{m1}G_1 + g_{m1}G_2 + G_1G_2 + g_{m2}G_1}$$

(4)

credit
 2 of 4
 I done
 numerically
 only.

$$1 + SC \left/ \frac{G_1 + G_2}{g_{m1}G_1 + g_{m1}G_2 + G_1G_2 + g_{m2}G_1} \right.$$

P.D. $g_{m1} = 10ms$, $g_{m2} < 5ms$ $G_1 = 1ms$, $G_2 = 0.1ms$

$C = 1pt$

so : $\frac{G_1 + G_2}{g_{m1}G_1 + g_{m1}G_2 + G_1G_2 + g_{m2}G_1} = \frac{1.1ms}{10ms \cdot 1ms + 10ms \cdot 0.1ms + 1ms \cdot 1ms}$

$$= \frac{1.1}{10 + 1 + 0.1 + 0} = 0.11$$

$16 \times 0.11 = 1.76$

$$= \frac{1.1}{16} \times 16 = 1.1 \times 16 = 16.1$$

~~16.1~~

Part c, 5 points

$g_{m1} = 10 \text{ mS}$, $g_{m2} = 5 \text{ mS}$. $R_1 = 1,000 \text{ Ohms}$. $R_2 = 10,000 \text{ Ohms}$. $C = 1 \text{ pF}$.

How many poles are there in the transfer function?

Give its frequency / their frequencies:

$$f_{p1} = \underline{2.36 \text{ K}}, f_{p2} = \underline{\chi}, f_{p3} = \underline{\chi} \dots$$

$$\textcircled{2} \quad \boxed{T = \frac{G_1 + G_2}{g_{m1}G_1 + g_{m1}G_2 + G_1G_2 + g_{m2}G_1} \cdot C = 68 \text{ n.s.c}}$$

$$\begin{aligned} \textcircled{1} \quad T &= 68 \text{ n.s.c} \\ &= 68 \text{ n} \cdot 1 \text{ pF} = 68 \text{ pS} \end{aligned}$$

$$\textcircled{1} \quad \omega_p = \frac{2.34 \cdot 10^9 \text{ Hz}}{68 \text{ pS}} = \underline{\underline{2.34 \text{ GHz}}}$$

$$\frac{g_{m1}(g_{m2} - G_1)}{g_{m1}G_1 + g_{m1}G_2 + G_1G_2 + g_{m2}G_1} = \frac{10 \text{ mS}(5 \text{ mS} - 1 \text{ mS})}{10 \text{ mS}(1 \text{ mS} + 0.1 \text{ mS}) + 1 \text{ mS} \cdot 0.1 \text{ mS} + 0.1 \text{ mS} \cdot 1 \text{ mS}}$$

$$= \frac{40}{11 + 0.1 + 5} = \frac{40}{16.1} = \underline{\underline{2.48}}$$


Low frequency $\omega_0 = \underline{\underline{-2.48}}$

Part d, 5 points

Make an accurate Bode plot of V_{out}/V_{gen} , labeling all slopes, and all key gain and frequency values. Make sure you draw the straight-line asymptotes, and then sketch the true curve.

$$\textcircled{1} f_{pc} = 2.36k$$

Bode Magnitude plot-please label axes

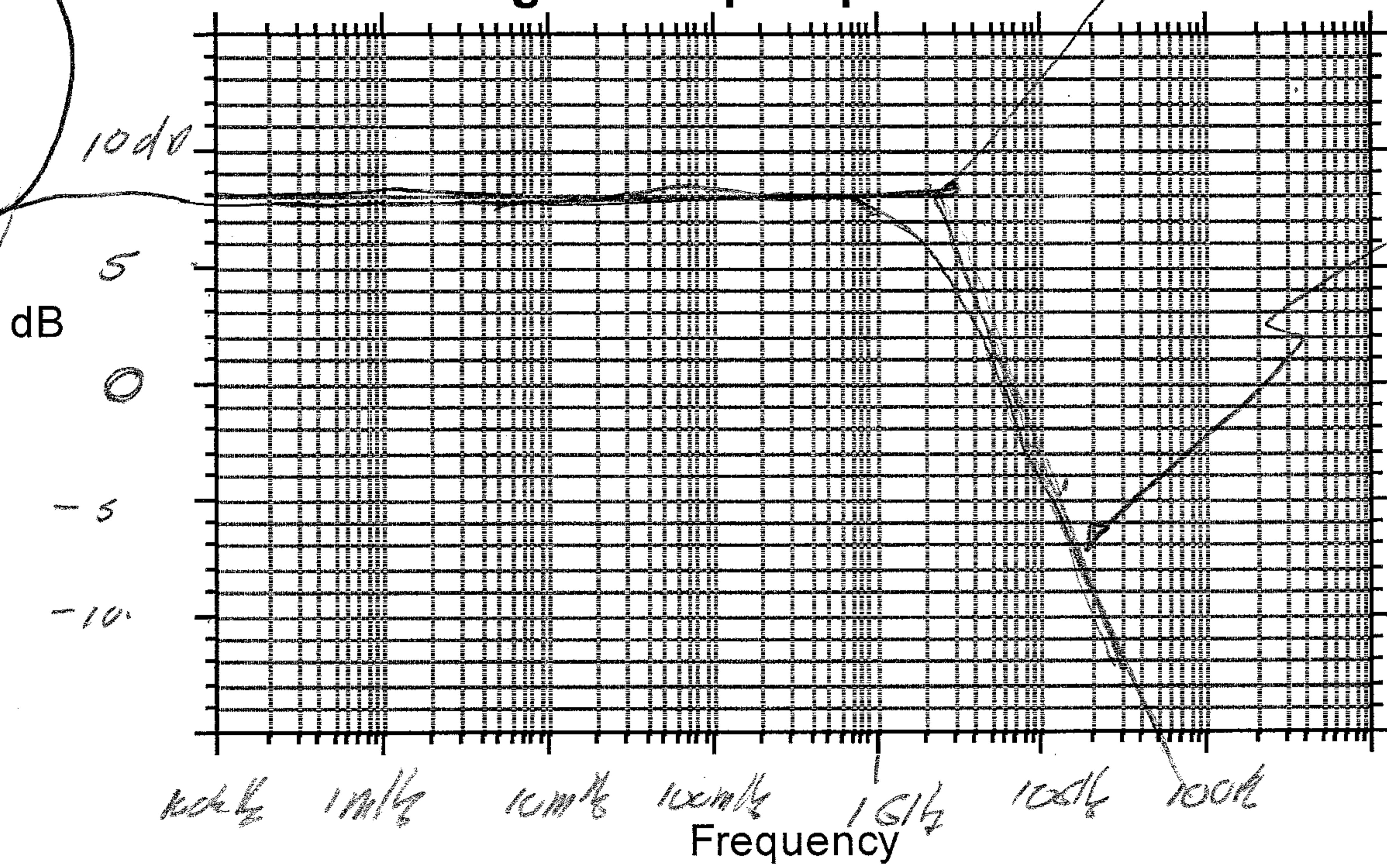

$$\textcircled{2} \quad \frac{V_{out}(s)}{V_{gen}(s)} = \frac{-g_m(G_m + G_1)}{g_m(G_1 + G_2) + (g_m + g_n)G_1} \quad z = -2.48$$

$$\frac{V_{out}(s)}{V_{gen}(s)} = \frac{v_o}{v_x} \cdot \frac{1}{1 + sT}$$

$$T = 68\mu s \rightarrow f_{3dB} = \frac{0.157}{68\mu s} = 2.36k$$


$$\frac{v_o}{v_x} \cdot \frac{1}{1 + sT} = -2.48 \rightarrow$$

$$20 \log_{10}(-2.48) = 7.7 \text{ dB} \approx 8 \text{ dB}$$

Part e, 5 points

If $V_{gen}(t)$ is a 10 mV step-function, find and *accurately* plot $V_{out}(t)$. *Be sure to label both axes and give units.*

$V_{out}(t) =$ _____

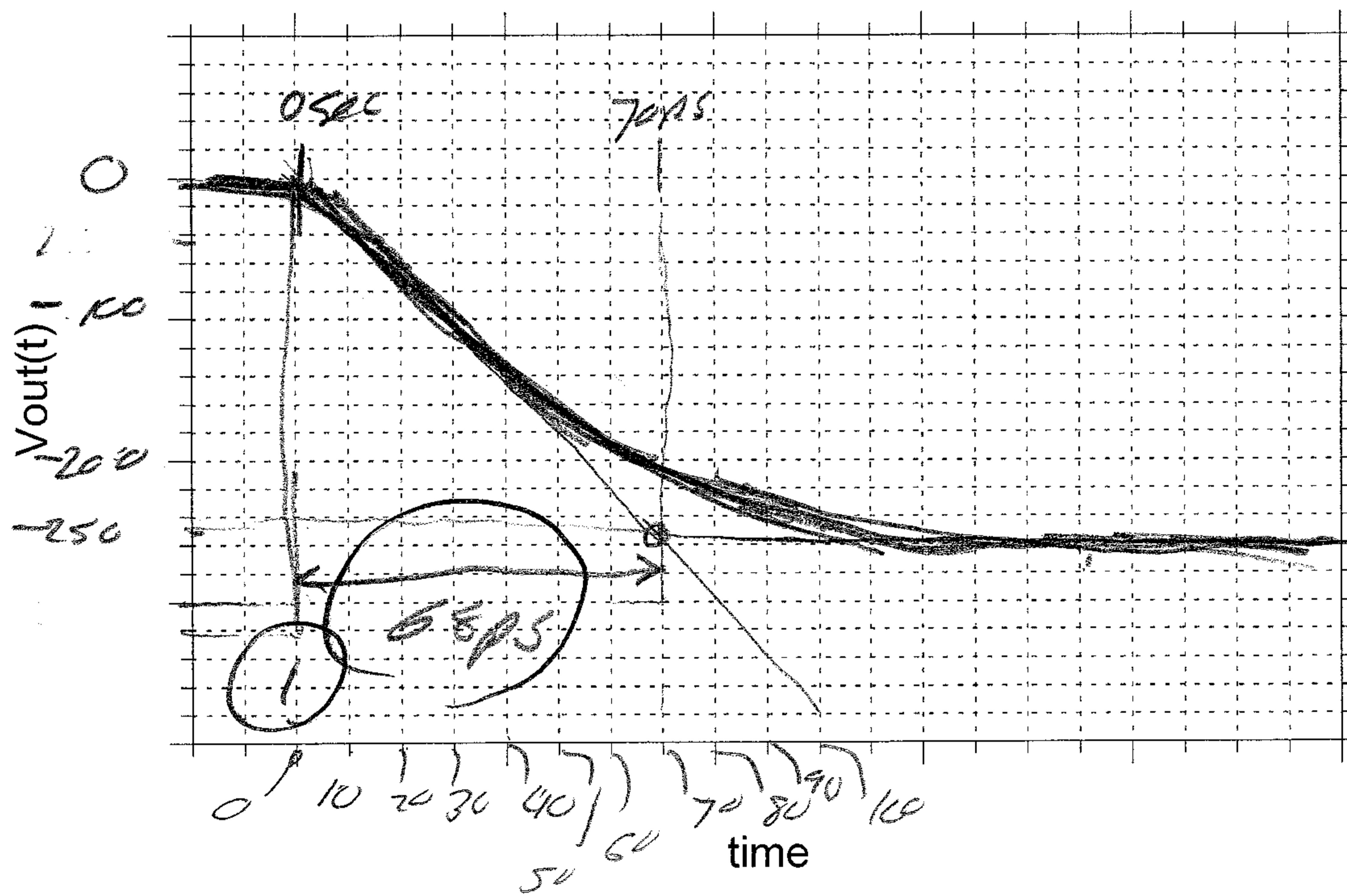


$$A_L C = -2.48, \quad \tau = 68 \text{ ps}$$

③
$$V_{out}(t) = -248 \text{ mV} \left(1 - e^{-t/68 \text{ ps}}\right) + 670$$

Problem 4: 25 points

frequency and transient response

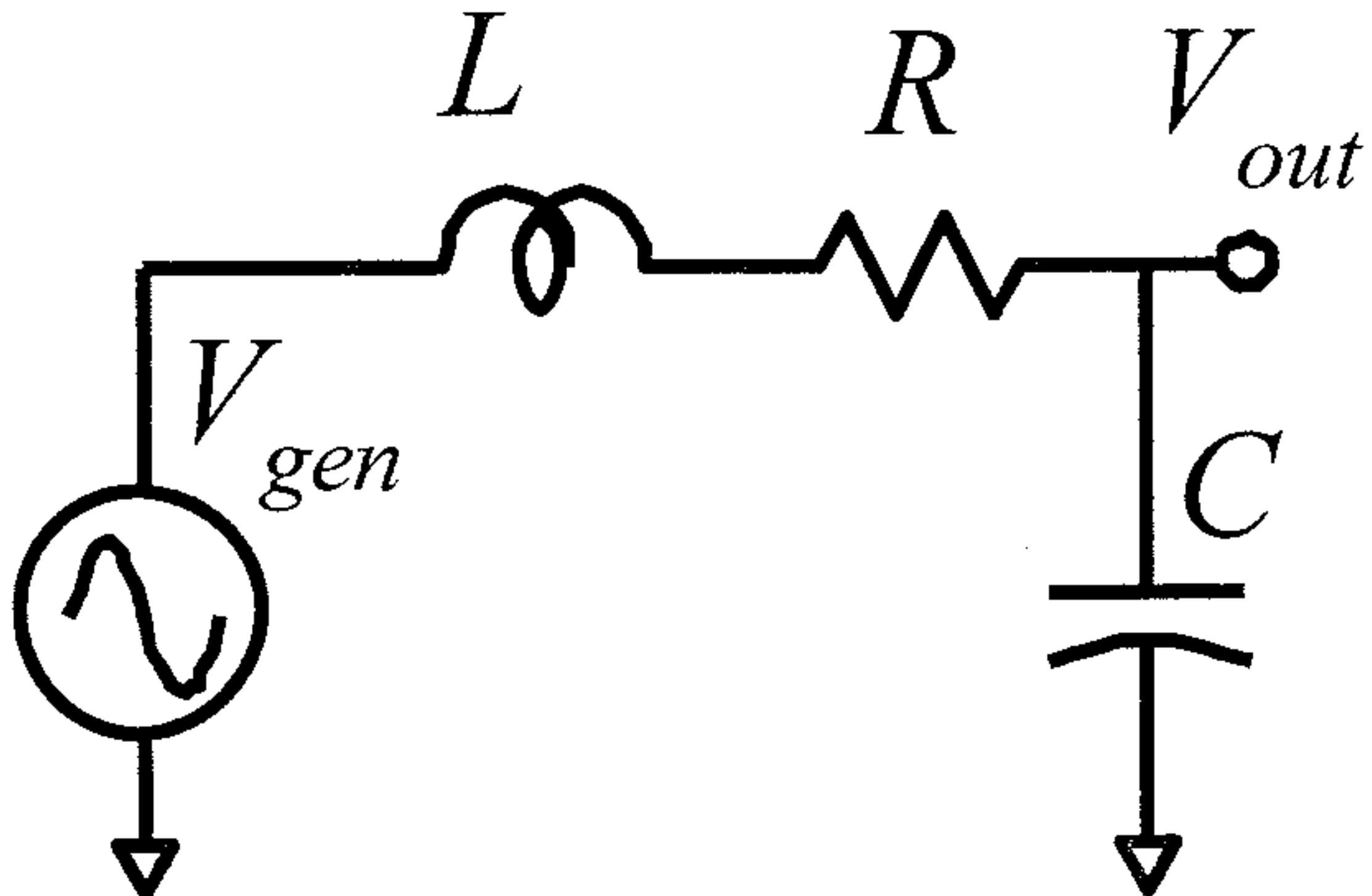

You are solving frequency and transient response of the network to the left.

Part a , 10 points

Using NODAL ANALYSIS, find the transfer function $V_o(s)/V_{gen}(s)$

The answer must be in standard form $\frac{V_o(s)}{V_{gen}(s)} = \left. \frac{V_o}{V_{gen}} \right|_{low-frequency-value} \times \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$,

$$\frac{V_o(s)}{V_{gen}(s)} = \frac{\text{_____}}{\text{_____}}$$

$$\textcircled{5} \quad V_{out}(s) + (V_{at} - V_i) \left(\frac{1}{R + jL} \right) = 0$$

$$\frac{V_{at}}{V_i} = \frac{V_c}{1/jC + R + jL} = \frac{1}{1 + jCR + j^2 LC}$$

$$\textcircled{5} \quad \frac{V_{out}}{V_{in}} = \frac{1}{1 + jRC + j^2 LC}$$

Part b, 5 points

Now evaluate with $L=3.98 \mu\text{H}$, $C=0.637 \text{ pF}$, $R=1000 \text{ Ohm}$.

How many poles are there in the transfer function?

If there are one or two poles, and if they are real, give f_{p1} and possibly f_{p2} :

$$f_{p1} = \underline{\hspace{2cm}}, f_{p2} = \underline{\hspace{2cm}}$$

If the two dominant poles are complex, give $f_n = \omega_n / 2\pi$ and ζ :


$$f_n = \omega_n / 2\pi = \underline{10^{8.1/2}}, \zeta = \underline{0.1}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + sCR + s^2LC}$$

$$= \frac{1}{1 + s \frac{2\zeta}{\omega_n} + s^2/\omega_n^2} \quad (3)$$


$$\omega_n = \frac{1}{\sqrt{LC}} = 6.28(10^8) \text{ rad/sec} \Rightarrow 10^8 \text{ Hz.} = f_n$$
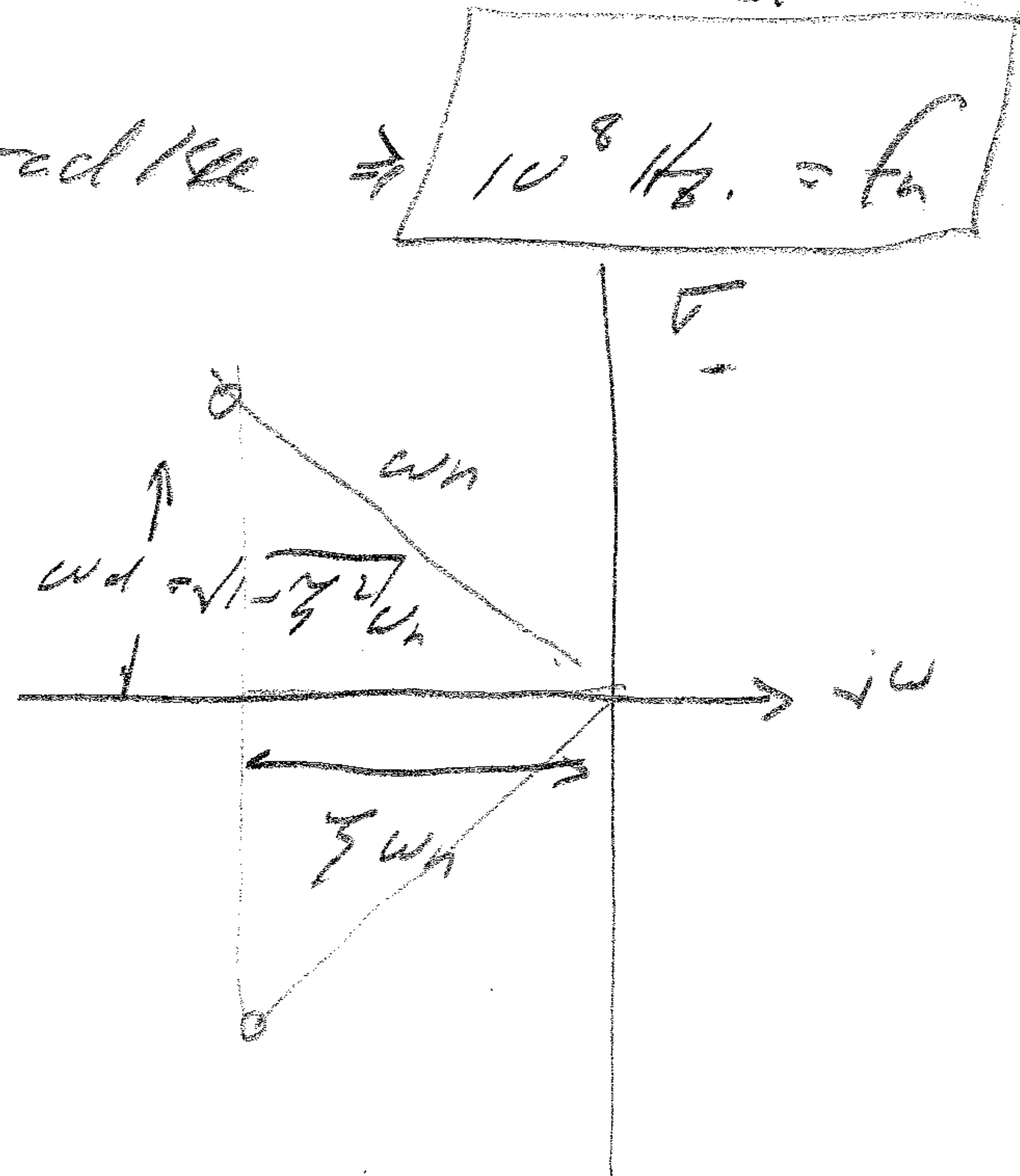
$$\zeta = \frac{R}{2\sqrt{LC}} = \underline{0.20}$$



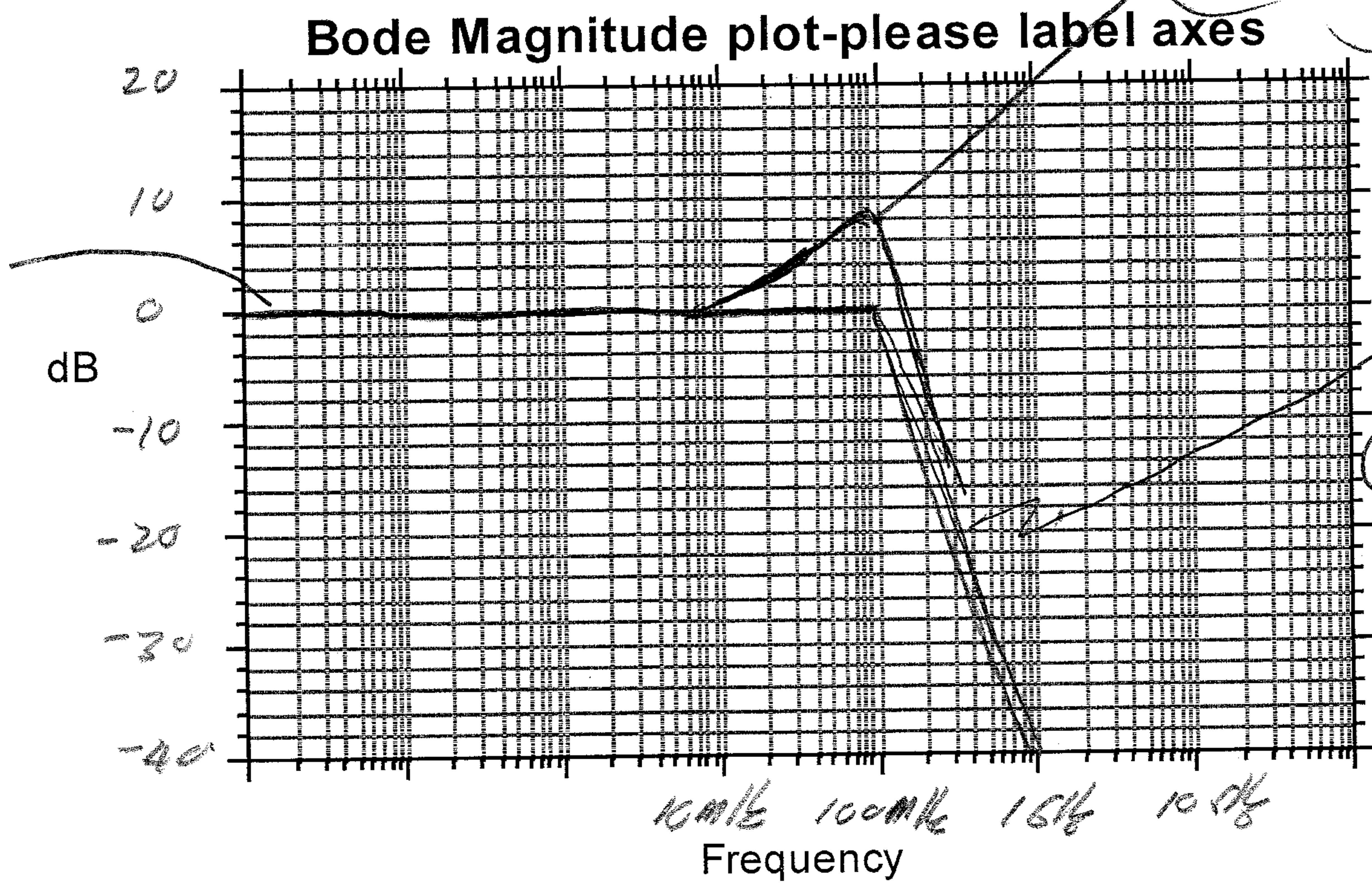Part d, 5 points

Make an accurate Bode plot of V_{out}/V_{gen} , labeling all slopes, and all key gain and frequency values. Make sure you draw the straight-line asymptotes, and then sketch the true curve.




$$H(j\omega) = \frac{1}{1 + 2j\omega T_m + \omega^2 T_m^2} = \begin{cases} 1 & \omega \ll \omega_n \\ \frac{\omega_n}{\omega} \cdot \frac{1}{1 + \frac{\omega^2}{\omega_n^2}} & \omega = \omega_n \\ \frac{\omega_n^2}{\omega^2} & \omega \gg \omega_n \end{cases}$$

$$T_m = 0.2 \text{ sec} \quad 1/2T_m = \underline{2.5} = 8.0 \text{ rad/sec}$$

Part e. 5 points

If $V_{in}(t)$ is a 10 mV step-function, find and accurately plot $V_{out}(t)$. Be sure to label both axes and give units.

$V_{out}(t) =$ _____

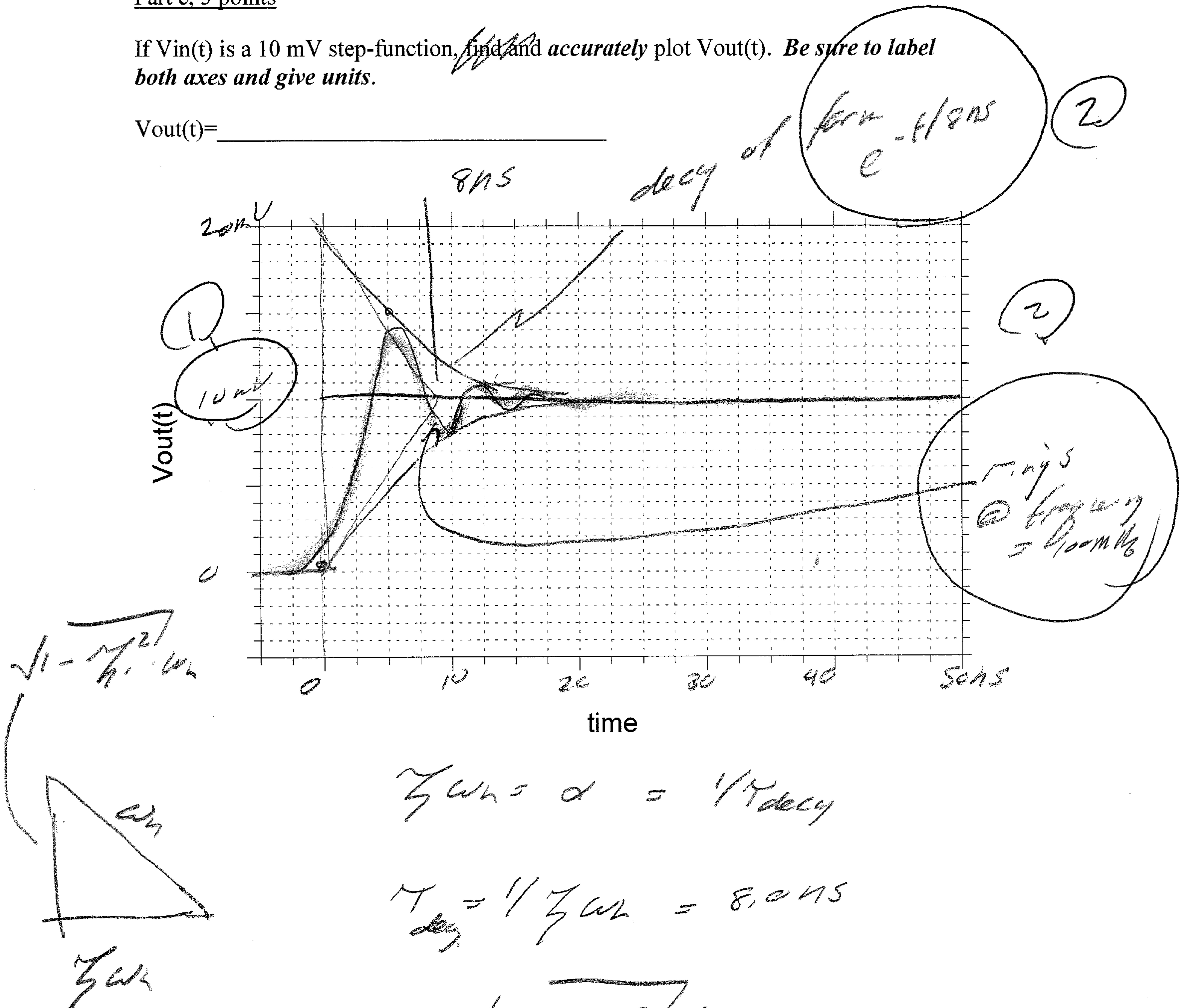

$$\gamma_{ar} = \alpha = 1/\tau_{decay}$$

$$\tau_{decay} = 1/\gamma_{ar} = 8.0\text{ ns}$$

$$\omega_d = \sqrt{1 - \gamma^2_{ar}} \omega_0 = 0.98 \omega_0 \approx \omega_0$$

Step response $v_{out} @ \frac{\omega_0}{2\pi} = 100\text{ MHz} = 6.28 \cdot 10^9 \text{ rad/s}$

" " decays exponentially as $e^{-t/8\text{ ns}}$