

B

ECE 2C Final Exam

June 7, 2011

Do not open exam until instructed to.

Closed book: Crib sheet and 2 pages personal notes permitted

There are 4 problems on this exam, and you have 3 hours.


Use any and all reasonable approximations (5% accuracy is fine.) , **AFTER STATING and approximately Justifying them.**

Name: Selafia B

Problem	Points Received	Points Possible
1a		5
1b		2
1c		5
1d		5
1e		5
1f		3
1g		10
2a		10
2b		10
3a		10
3b		10
3c		5
3d		5
3e		5
4a		10
4b		5
4c		5
4d		5
4e		5
total		100

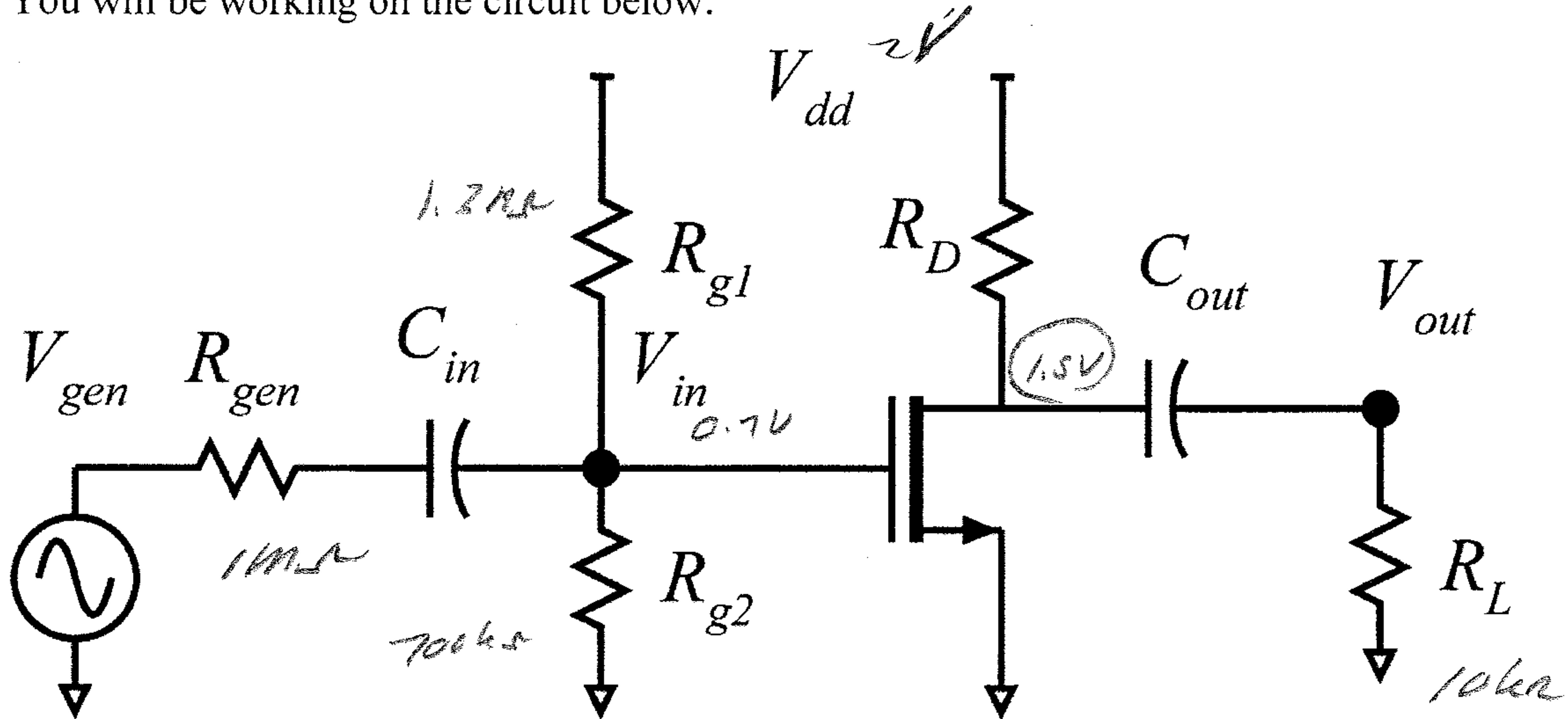Problem 1, 25 points

You will be working on the circuit below:



Q1 is a mobility-limited FET, i.e. $I_d = (\mu c_{ox} W_g / 2L_g)(V_{gs} - V_{th})^2(1 + \lambda V_{ds})$ where $(\mu c_{ox} W_g / 2L_g) = 1 \text{ mA/V}^2$, $\lambda = 0.05 \text{ V}^{-1}$, and $V_{th} = 0.20 \text{ V}$.

$$V_{dd} = +2.0 \text{ volts}$$

C_{in} and C_{out} are very big and have negligible AC impedance.

$$R_L = 10 \text{ kOhm}$$

$$R_{gen} = 1 \text{ MOhm}$$

$$I_d = 1 \text{ mA/V}^2 \cdot (V_{gs} - V_{th})^2 = 1 \text{ μA} \quad \text{Part A} \\ \text{sdn.}$$

$$\frac{V_{gs} - V_{th}}{V_{gs} - 0.20} = \frac{(1 \text{ μA})^{1/2}}{1 \text{ μA}} = 1 \text{ mV} \quad \textcircled{1}$$

$$\text{Current} = 1 \text{ μA} (R_{g1}, R_{g2})$$

$$R_{g2} = 0.20 \text{ V} = 100 \text{ k} \quad \textcircled{1}$$

$$R_{g1} = \frac{1.3 \text{ V}}{1 \text{ μA}} = 1.3 \text{ M} \quad \textcircled{1}$$

$$R_D = \frac{2 \text{ V} - 1.8 \text{ V}}{1 \text{ μA}} = 2 \text{ M} \rightarrow \frac{2 \text{ V}}{0.2 \text{ mA}} = 10 \text{ k} \quad \textcircled{1}$$

Part a, 5 points

DC bias.

Q1 is to be biased with 1/4 mA drain current, and with 1.5 Volts drain voltage.


Ignore λ while solving this part.

Find: $R_{g1} = \frac{700\text{ k}\Omega}{}, R_{g2} = \frac{1.3\text{ M}\Omega}{}, R_d = \underline{2\text{ k}\Omega}$
The DC voltage at the gate of Q1. = 0.7V

Solutions on page 2

Part b, 2 points

DC bias

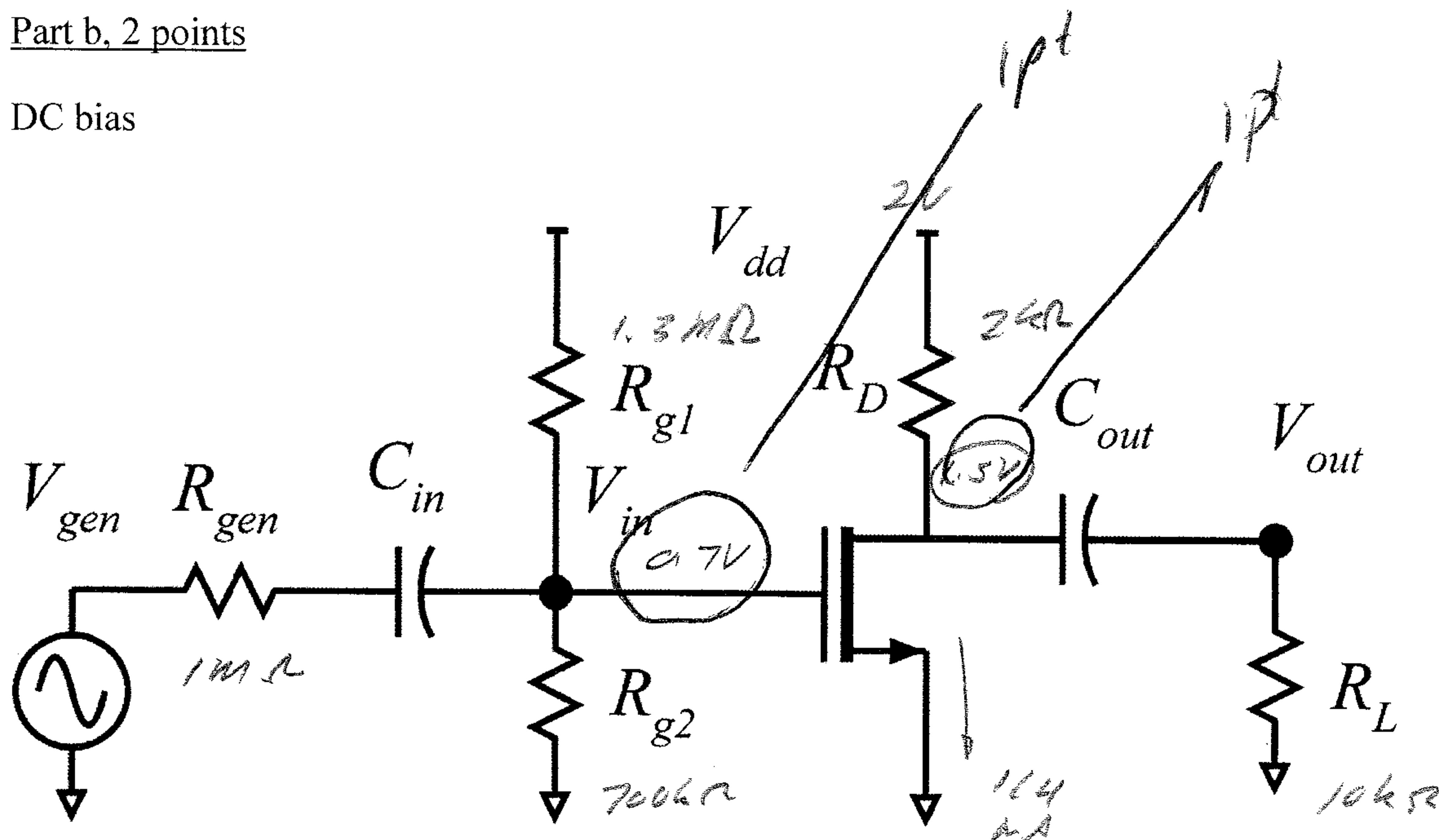

On the circuit diagram above, label the DC voltages at **ALL nodes** and the DC currents through **ALL resistors**

$$I_{d1} = \frac{1mA}{V^2} \cdot (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

Part c:

$$\begin{aligned} g_m &= \frac{1mA}{V^2} \cdot (V_{gs} - V_{th}) \cdot Z = \frac{2mA}{V^2} \cdot 0.5V \\ &= 1mA/V^2 \quad \text{oh with or without } (1 + \lambda V_{ds}) \end{aligned}$$

(2.5)

$$\begin{aligned} R_{ds} &= \frac{1/\lambda + V_{ds}}{I_d} = \frac{20V + 1.5V}{I_d = 1mA} = 85k\Omega \text{ answer ok.} \\ &\approx \frac{1}{\lambda I_d} = 80k\Omega \text{ answer ok} \end{aligned}$$

Part c, 5 points


Find the small signal parameters of Q1. Use the mobility-limited model.

$$gm = \frac{1.115}{80 \text{ mV}}$$

SEE page 4

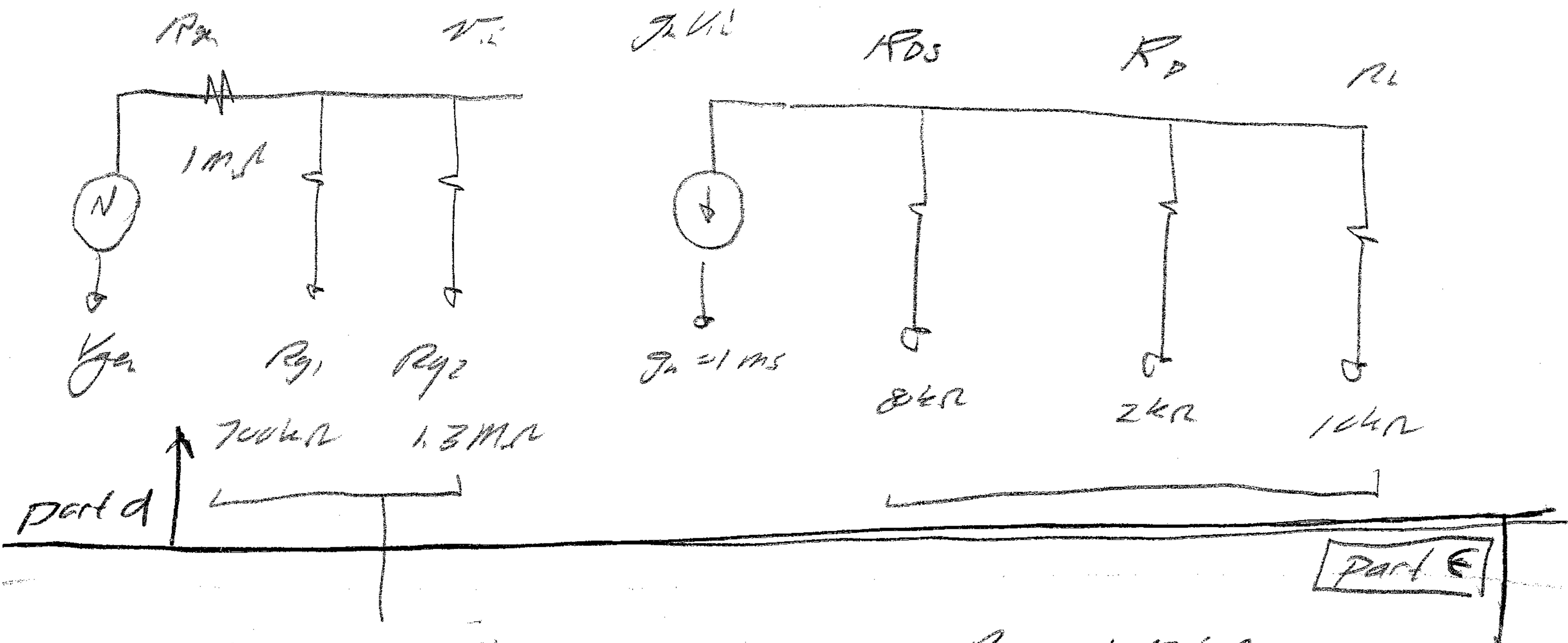Part d, 5 points

Replacing the transistor with its small-signal model, draw a small-signal equivalent circuit diagram for the amplifier. Give values for all elements on the diagram.



$$R_{in} = 700\text{k}\Omega // 1.3\text{M}\Omega \\ = \approx 455\text{k}\Omega$$

$$R_{out} = 1.63\text{k}\Omega$$

$$V_{in} / V_{in} =$$

Part e, 5 points.

Find the small signal voltage gain (V_{out}/V_{in}) of Q1.

$$V_{out}/V_{in} = \underline{-1.63}$$

$$\begin{aligned} R_{eq} &= R_D \parallel R_{DS} \parallel R_L \\ &= 1.63 \text{ k}\Omega \end{aligned} \quad \boxed{2.5}$$

$$\begin{aligned} V_o/V_{in} &= -g_m R_{eq} \\ &= -1.63 \cdot 1.63 \text{ k}\Omega \\ &= -1.63 \end{aligned} \quad \boxed{2.5}$$

Part f, 3 points

Find the *** amplifier *** input resistance, Vin/Vgen, and Vout/Vgen

$$R_{in, \text{amplifier}} = \underline{455 \text{ k}\Omega}$$

$$\frac{V_{in}}{V_{gen}} = \underline{0.31}$$

$$(V_{out}/V_{gen}) = \underline{-0.51}$$

$$R_{in} = R_1 \parallel R_2 = 455\text{k}\Omega \quad] ①$$

$$\frac{V_{in}}{V_{in}} = \frac{R_{in}}{R_{in} + R_{bf}} = \frac{455\text{k}\Omega}{455\text{k}\Omega + 1\text{M}\Omega} = 0.31 \quad] ②$$

$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_{in}} \cdot \frac{R_{in}}{R_{in}} = 0.31 \cdot (-1.63) \quad] ③$$



= -0.51

Part g, 10 points

Now you must find the maximum signal swings. Find the output voltage due to the knee voltage and due to cutoff in Q1.


Cutoff of Q1; Maximum ΔV_{out} resulting = $+ 0.41V$

Knee voltage of Q1; Maximum ΔV_{out} resulting = $- 1.0V$

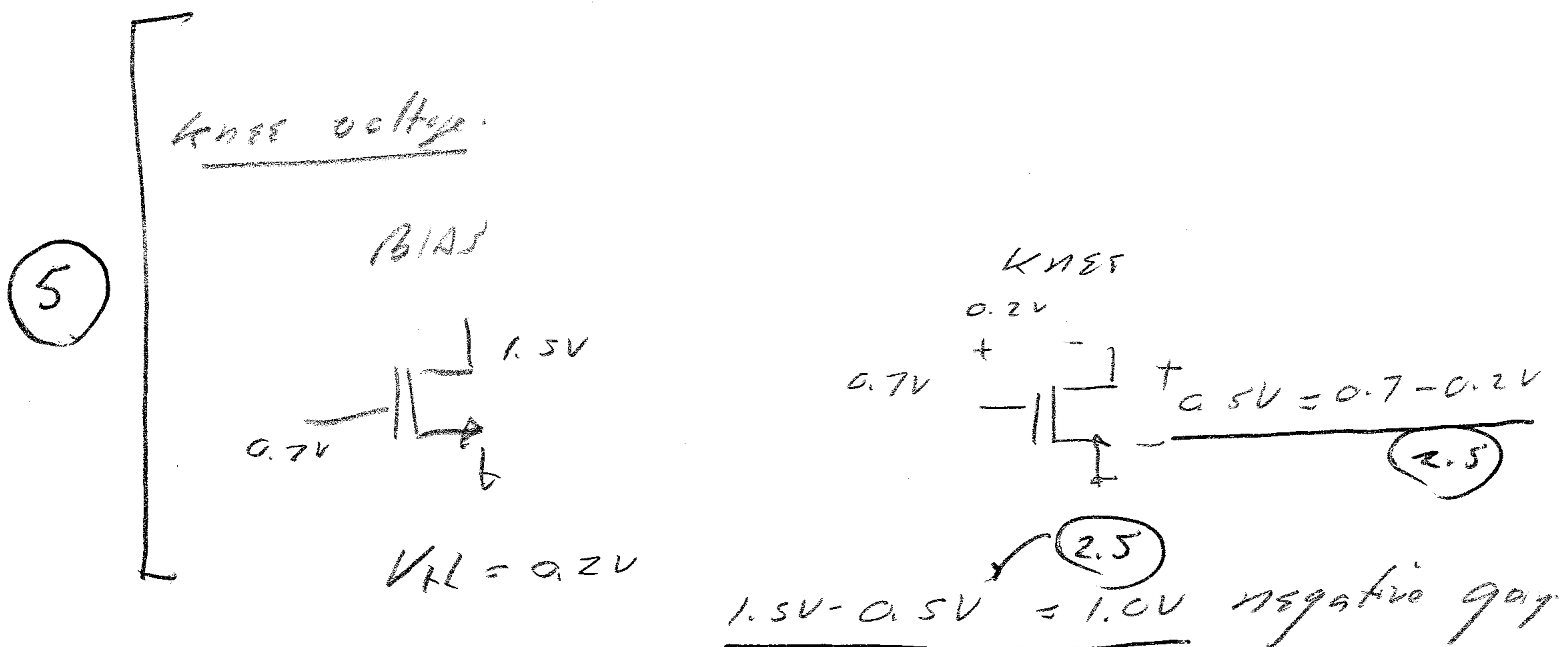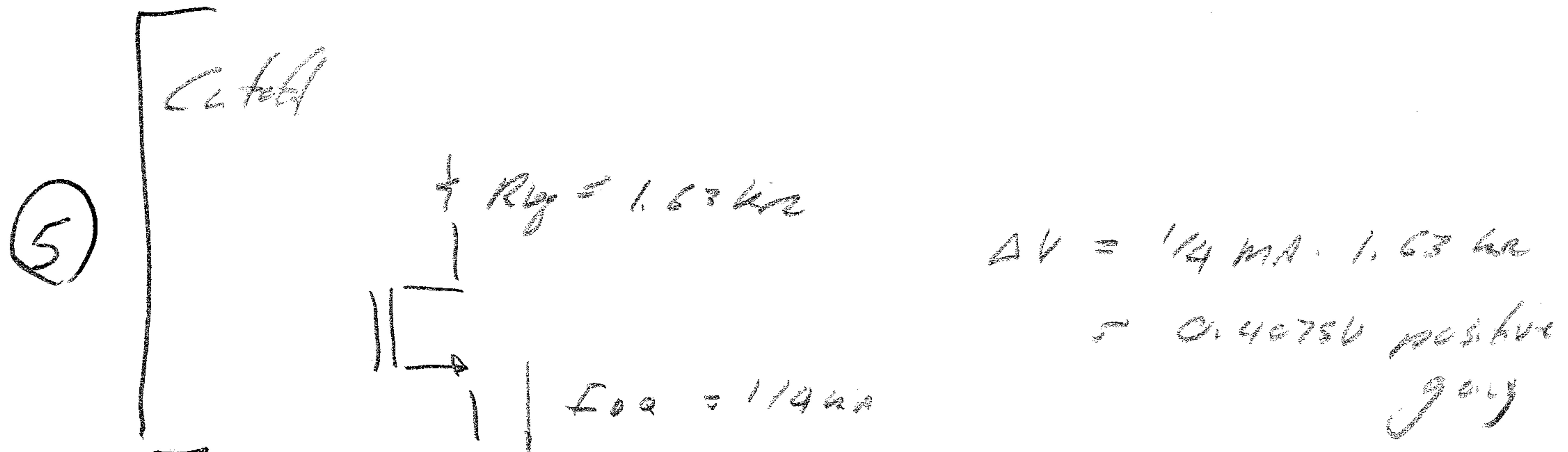

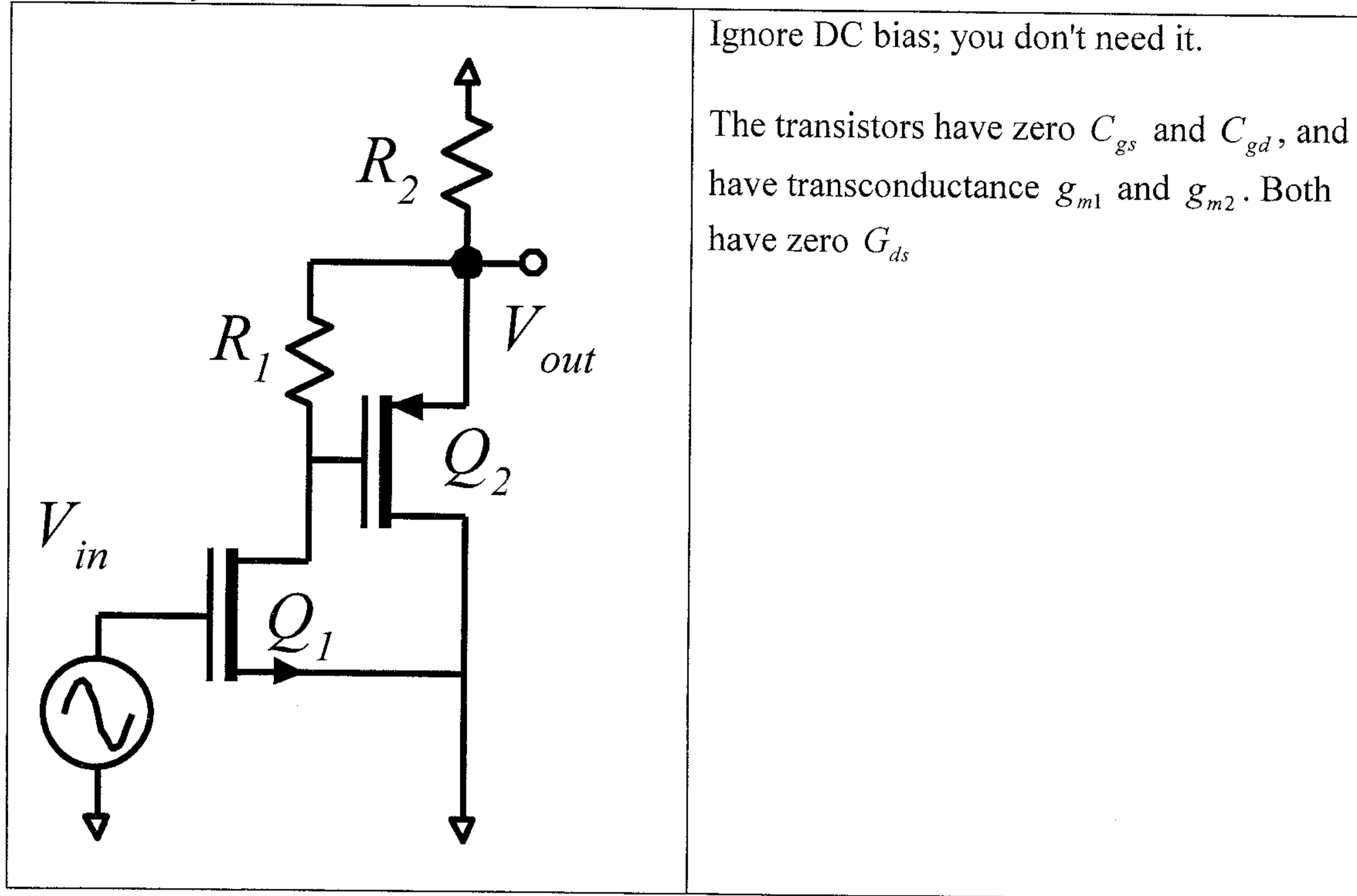
Problem 2: 20 points

Nodal analysis, transistor circuit models



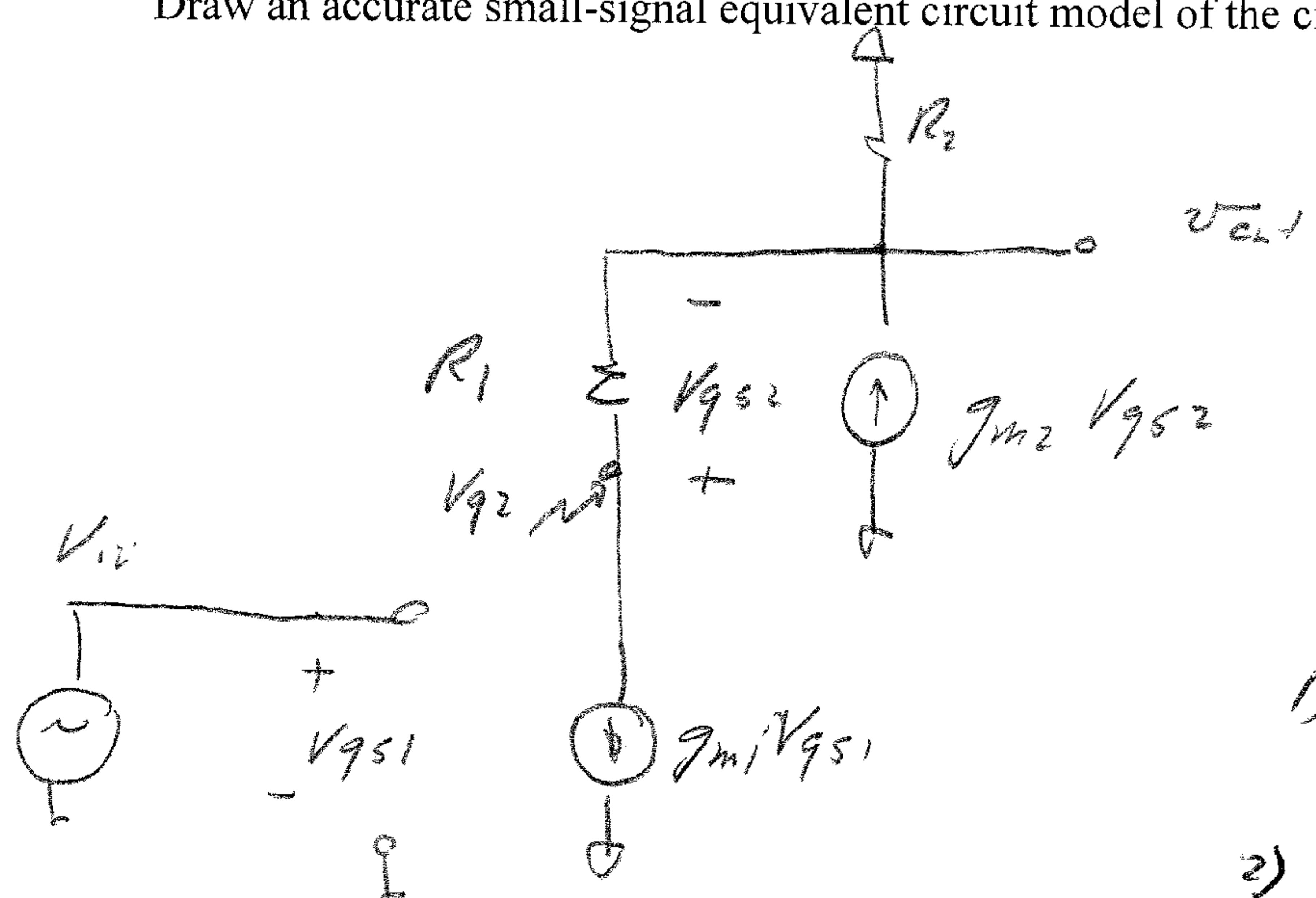Part a, 10 points

Draw an accurate small-signal equivalent circuit model of the circuit above.



-3 pts Penalty
each for:

- 1) topological / connection errors
- 2) Missing control voltages on g_m elements.
- 3) No ~~or~~ unlabelled control voltages

Part b, 10 points

Using NODAL ANALYSIS, find V_{out}/V_{in} . Give both an algebraic expression, then find the numerical value with with $gm1=10 \text{ mS}$, $gm2=20 \text{ mS}$, $R1=1000 \text{ Ohms}$, $R2=10,000 \text{ Ohms}$.

$$\frac{V_o}{V_{in}} = \frac{-g_{m1}(R_1 R_2)(g_{m2} + G_1)}{1} \quad (\text{algebraic expression})$$

$$\frac{V_o}{V_{in}} = \frac{-2,100}{1} \quad (1)$$

(value with $gm1=10 \text{ mS}$, $gm2=20 \text{ mS}$, $R1=1000 \text{ Ohms}$, $R2=10,000 \text{ Ohms}$)

$\Sigma I = 0 @ V_{g2}$

$$g_{m1} V_{gs1} + (V_{g2} - V_{out}) G_1 = 0$$

$$g_{m1} V_{in} + G_1 V_{g2} + V_{out}(-G_1) = 0$$

$$[V_{g2}(-G_1) + V_{out}(+G_1)] = +g_{m1} V_{in} \leftarrow (3)$$

$\Sigma I = 0 @ V_{out}$

$$V_{out}(G_2) - g_{m2} V_{gs2} + (V_{out} - V_{g2}) G_1 = 0$$

$$V_{out}(G_1 + G_2) + g_{m2}(V_{out} - V_{g2}) - V_{g2} G_1 = 0$$

$$[V_{out}(G_1 + G_2 + g_{m2}) + V_{g2}[-g_{m2} - G_1]] = 0 \quad (3)$$

$$V_{92}(+G_1) + V_{ab}(-G_1) = -g_{m1}V_{1b}$$

$$V_{92}(-G_1 - g_{m2}) + V_{ab}(G_1 + G_2 + g_{m2}) = 0$$

$$\frac{V_{ab}}{V_{1b}} = \frac{N}{D}$$

$$N = \begin{vmatrix} G_1 & -g_{m1} \\ -G_1 - g_{m2} & 0 \end{vmatrix} = -g_{m1}(g_{m2} + G_1)$$


$$D = \begin{vmatrix} G_1 & -G_1 \\ -G_1 - g_{m2} & G_1 + G_2 + g_{m2} \end{vmatrix} = G_1 G_2$$

$$G_1 G_1 + G_1 G_2 + G_2 g_{m2} \\ = -G_1 G_1 - G_1 g_{m2}$$

$$\frac{V_{ab}}{V_{1b}} = \frac{-g_{m1}(g_{m2} + G_1)}{G_1 G_2} = \boxed{\frac{-g_{m1} R_1 R_2 (g_{m2} + G_1) / \pi \cdot 2k}{\textcircled{2}}} \quad \text{or} \quad \boxed{= -g_{m1} (1 + g_{m2} R_2) R_2}$$

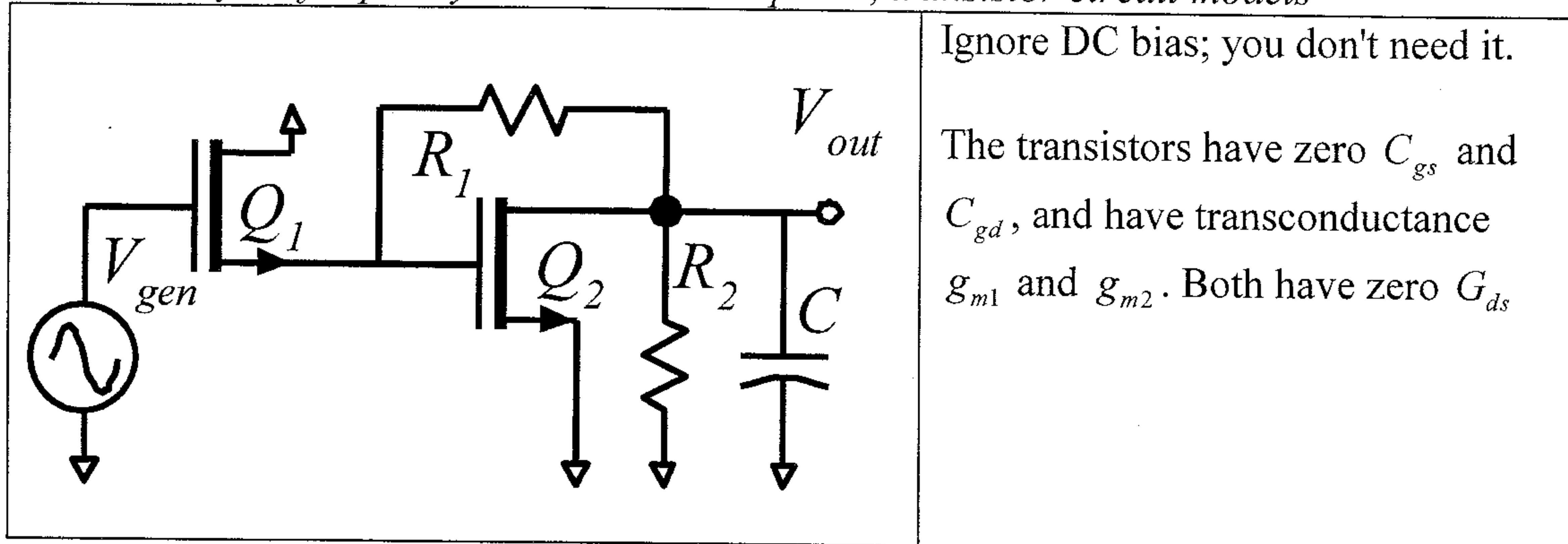
Problem 3: 35 points

Nodal analysis, frequency and transient response, transistor circuit models



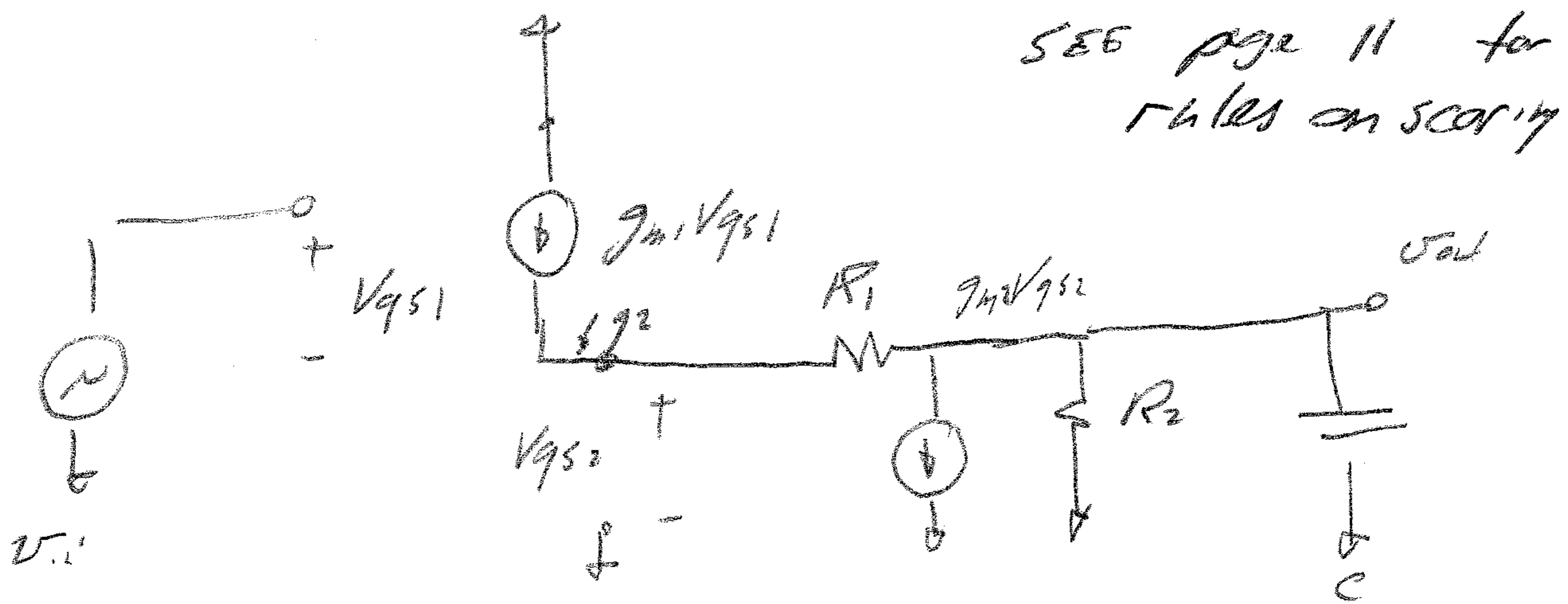Part a. 10 points

Draw an accurate small-signal equivalent circuit model of the circuit above.



$$\Sigma I = 0 \text{ @ } V_{gs2}$$

$$V_{gs2} [g_m1 + G_1] + V_{out} [-G_1] = V_{in} [g_m2] \quad \boxed{3}$$

$$\Sigma I = 0 \text{ @ } V_{in}$$

$$V_{gs1} [g_m2 - G_1] + V_{out} [G_1 + G_2 + jC] = 0 \quad \boxed{3}$$

Part b, 10 points

Using NODAL ANALYSIS, find the transfer function $V_o(s)/V_{gen}(s)$

The answer must be in standard form $\frac{V_o(s)}{V_{gen}(s)} = \left. \frac{V_o}{V_{gen}} \right|_{low-frequency-value} \times \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$,

$$\frac{V_o(s)}{V_{gen}(s)} = \frac{\text{[Matrix]}}{\text{[Matrix]}}$$

$$\begin{bmatrix} g_{m1} + G_1 & -G_1 \\ g_{m2} - G_1 & G_1 + G_2 + SC \end{bmatrix} \begin{bmatrix} V_{q1} \\ V_{q2} \end{bmatrix} = \begin{bmatrix} g_{m1} \\ g_{m2} \end{bmatrix} - \begin{bmatrix} V_{in} \\ V_{out} \end{bmatrix}$$

$$\frac{V_{out}}{V_{in}} = \frac{N}{D}$$

$$N = \begin{bmatrix} g_{m1} + G_1 & g_{m1} \\ g_{m2} - G_1 & C \end{bmatrix} = -g_{m1} (g_{m2} - G_1)$$

$$D = \begin{bmatrix} g_{m1} + G_1 & -G_1 \\ g_{m2} - G_1 & G_1 + G_2 + SC \end{bmatrix} = \begin{aligned} & g_{m1} G_1 + g_{m1} G_2 + G_1 G_2 + G_1 G_2 \\ & + g_{m2} G_1 - G_1 G_1 \\ & + SC(g_{m1} + G_1) \end{aligned}$$

$$= g_{m1} (G_1 + G_2) + (g_{m2} + G_2) G_1 + SC (g_{m1} + G_1)$$

$$\frac{V_{o(1s)}}{V_{in}} = \frac{-g_{m1} (g_{m2} - G_1)}{g_{m1} (G_1 + G_2) + (g_{m2} + G_2) G_1 + AC(g_{m1} + G_1)}$$

Low frequency gain

$$= \frac{-g_{m1} (g_{m2} - G_1)}{g_{m1} (G_1 + G_2) + (g_{m2} + G_2) G_1} \cdot \frac{1}{1 + \delta T}$$

(4)

where $T = C \frac{g_{m1} + G_1}{g_{m1} (G_1 + G_2) + (g_{m2} + G_2) G_1}$ credit 2 of 4
 if denominator numerically
 large

Part c, D $g_{m1} = 10ms, g_{m2} = 5ms, R_1 = 1k\Omega, R_2 = 10k\Omega$
 $C = 1pt, G_1 = 1ms, G_2 = 0.1ms$

Low frequency gain $= \frac{-g_{m1} (g_{m2} - G_1)}{g_{m1} (G_1 + G_2) + (g_{m2} + G_2) G_1} = \frac{-10ms \cdot (4ms)}{10ms(1.1ms) + (5.1ms)1ms}$
 $\approx -2.48 \rightarrow 20 \log_{10}(2.48) = -7.90 dB$

$$\frac{g_{m1} + G_1}{g_{m1} (G_1 + G_2) + (g_{m2} + G_2) G_1} = \frac{10ms + 1ms}{16.1ms} = 683 \Omega$$

$$T = 683 \Omega \cdot 1pt = 683ps$$

Part c, 5 points

$g_{m1}=10 \text{ mS}$, $g_{m2}=5 \text{ mS}$. $R_1=1,000 \text{ Ohms}$. $R_2=10,000 \text{ Ohms}$. $C=1 \text{ pF}$.

How many poles are there in the transfer function?

Give its frequency // their frequencies:

$$f_{p1} = \underline{\underline{233 \text{ MHz}}}, f_{p2} = \underline{\underline{Y}}, f_{p3} = \underline{\underline{X}} \dots$$

② $\boxed{\tau} = \frac{R_m + G_1}{R_m(G_1 + G_2) + (G_{2n} + G_2)G_1} \cdot C = 683 \text{ n.s.}$

① $\boxed{\tau} = 683 \text{ ps}$


① $\boxed{f_p} = \frac{1}{2\pi\tau} = \underline{\underline{233 \text{ MHz}}}$

Part d, 5 points

Make an Bode plot of V_{out}/V_{gen} , labeling all slopes, and all key gain and frequency values. Make sure you draw the straight-line asymptotes, and then sketch the true curve.

① $f_c = 233 \text{ mHz}$

Bode Magnitude plot-please label axes

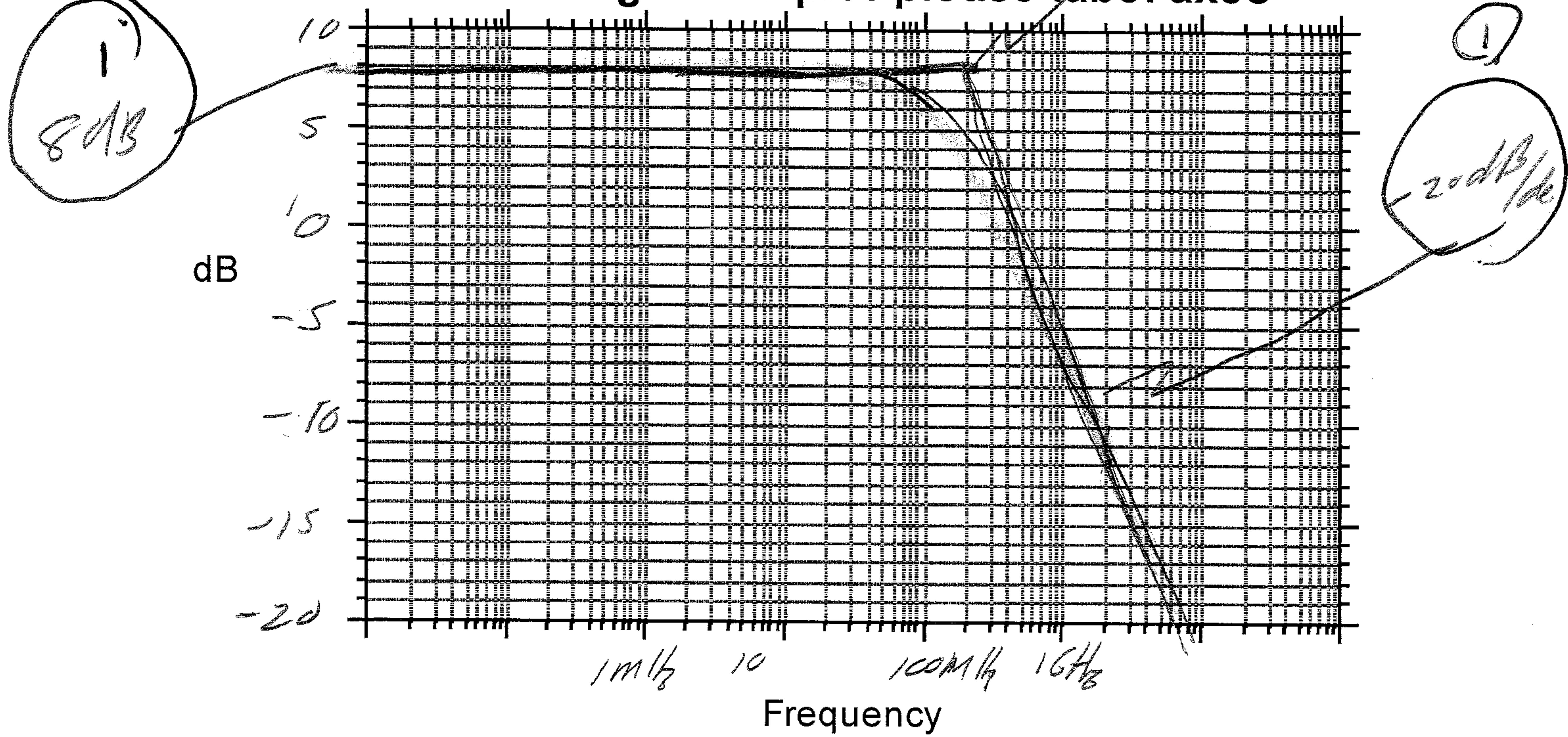

②

Set pop 11 $\frac{-g_m(G_1+G_2)}{R_1(G_1+G_2) + (G_1+G_2)C_1} = -242$

- low frequency $g_m = 7.9 \text{ dB}$


$T_{pole} = 683 \mu\text{s}$

$f_{pole} = 233 \text{ mHz}$

Part e, 5 points

If $V_{gen}(t)$ is a 10 mV step-function, find and *accurately* plot $V_{out}(t)$. **Be sure to label both axes and give units.**


$V_{out}(t) =$ _____

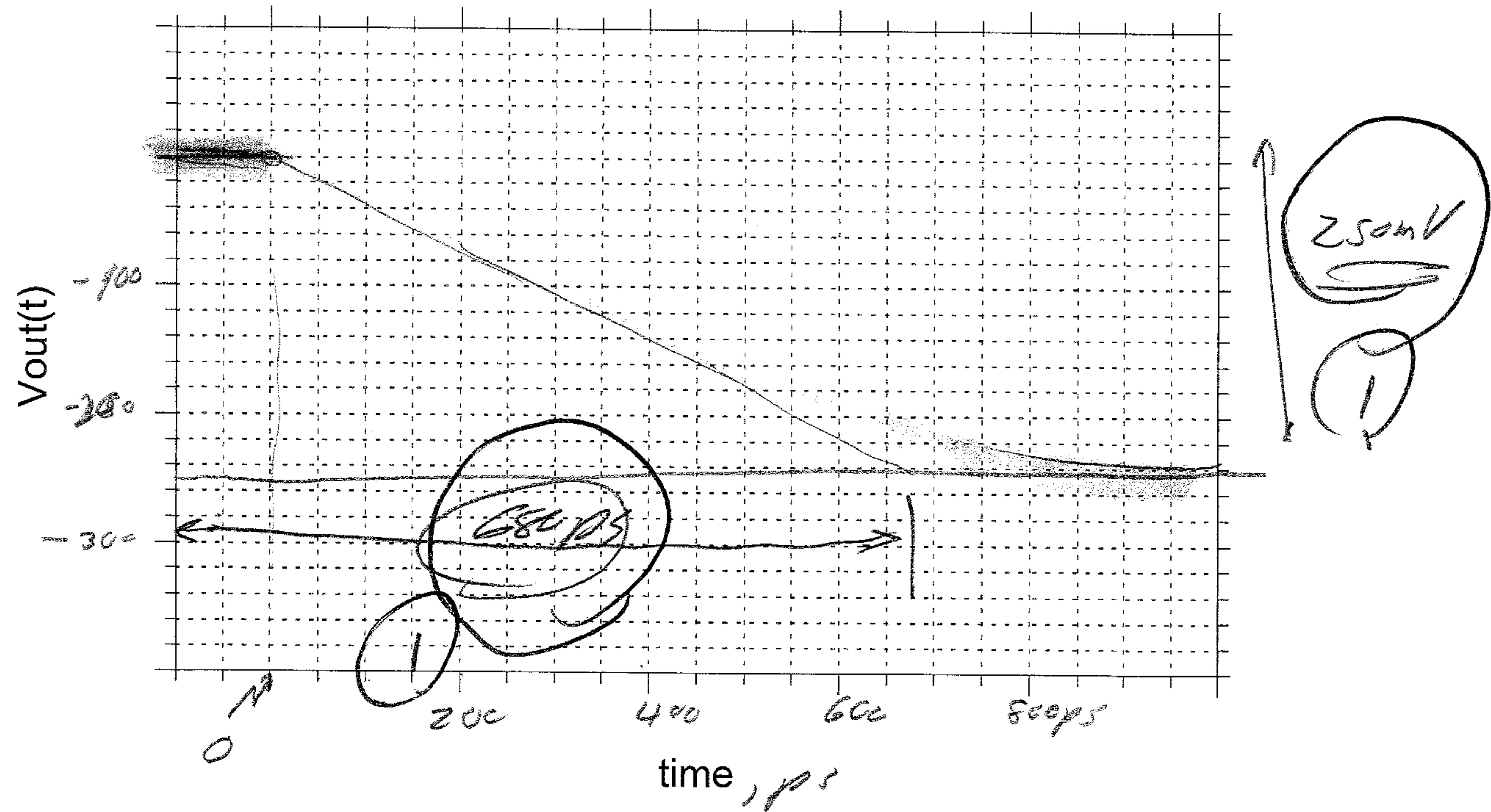

$$A_v = -2.48, \quad T = 680 \text{ ps.}$$

③
$$V_{out}(t) = -248 \text{ mV} \cdot \left(1 - e^{-\frac{t}{680 \text{ ps}}}\right) \text{ mV.}$$

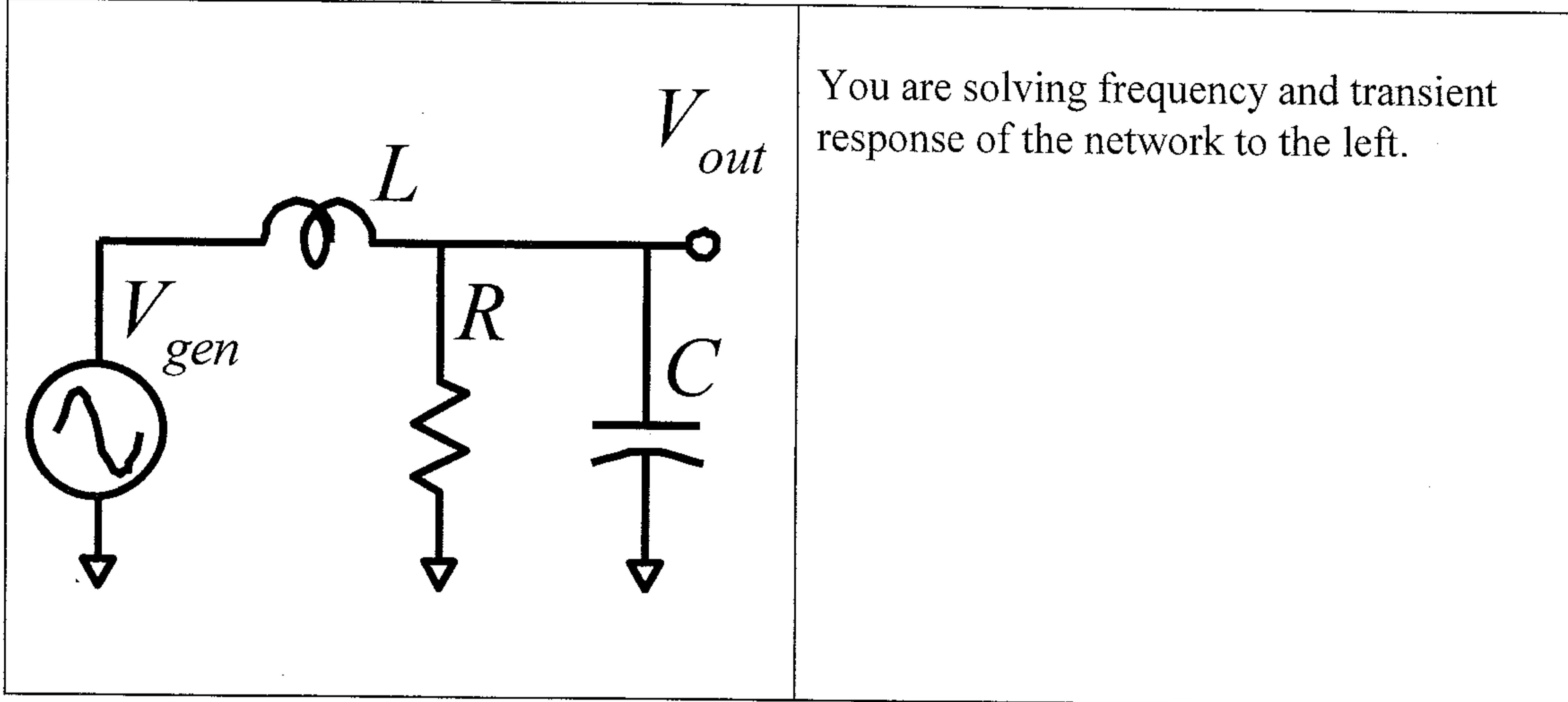Problem 4: 25 points
frequency and transient response



Part a , 10 points

Using NODAL ANALYSIS, find the transfer function $V_o(s)/V_{gen}(s)$

The answer must be in standard form $\frac{V_o(s)}{V_{gen}(s)} = \left. \frac{V_o}{V_{gen}} \right|_{low-frequency-value} \times \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$,

$$\frac{V_o(s)}{V_{gen}(s)} = \frac{1}{1 + jL/R + j^2 LC}$$

⑤ $\left[\sum I = 0 \quad \text{at } V_{out} \right]$
 $V_{out} (jC + G + j/L) + v_L (-j/L) = 0$

⑥ $\left[\frac{V_{out}}{V_{in}} = \frac{-j/L}{jC + G + j/L} = \frac{1}{1 + jLG + j^2 LC} \right]$

Part b, 5 points

Now evaluate with L=31.8 nH, C=0.796 pF, R=1000 Ohm

How many poles are there in the transfer function ?

If there are one or two poles, and if they are real, give f_{p1} and possibly f_{p2} :

$$f_{p1} = \underline{\hspace{2cm}}, f_{p2} = \underline{\hspace{2cm}}$$

If the two dominant poles are complex, give $f_n = \omega_n / 2\pi$ and ζ :

$$f_n = \omega_n / 2\pi = \underline{10^9 1/2}, \zeta = \underline{0.10}$$

$$H(s) = \frac{1}{1 + sL/R + s^2LC} = \frac{1}{1 + s2\zeta/\omega_n + s^2/\omega_n^2}$$

$$\Rightarrow \omega_n = \sqrt{\frac{1}{LC}} \rightarrow f_n = \frac{1/2\pi}{\sqrt{LC}} = \underline{10^9 1/2}$$

$$\Rightarrow \zeta = \frac{1}{2\pi} \sqrt{\frac{C}{L}} = \underline{0.10}$$

(2)


(3)

Part d, 5 points

Make an accurate Bode plot of V_{out}/V_{gen} , labeling all slopes, and all key gain and frequency values. Make sure you draw the straight-line asymptotes, and then sketch the true curve.

1
14dB per decade @ 1kHz

Bode Magnitude plot-please label axes

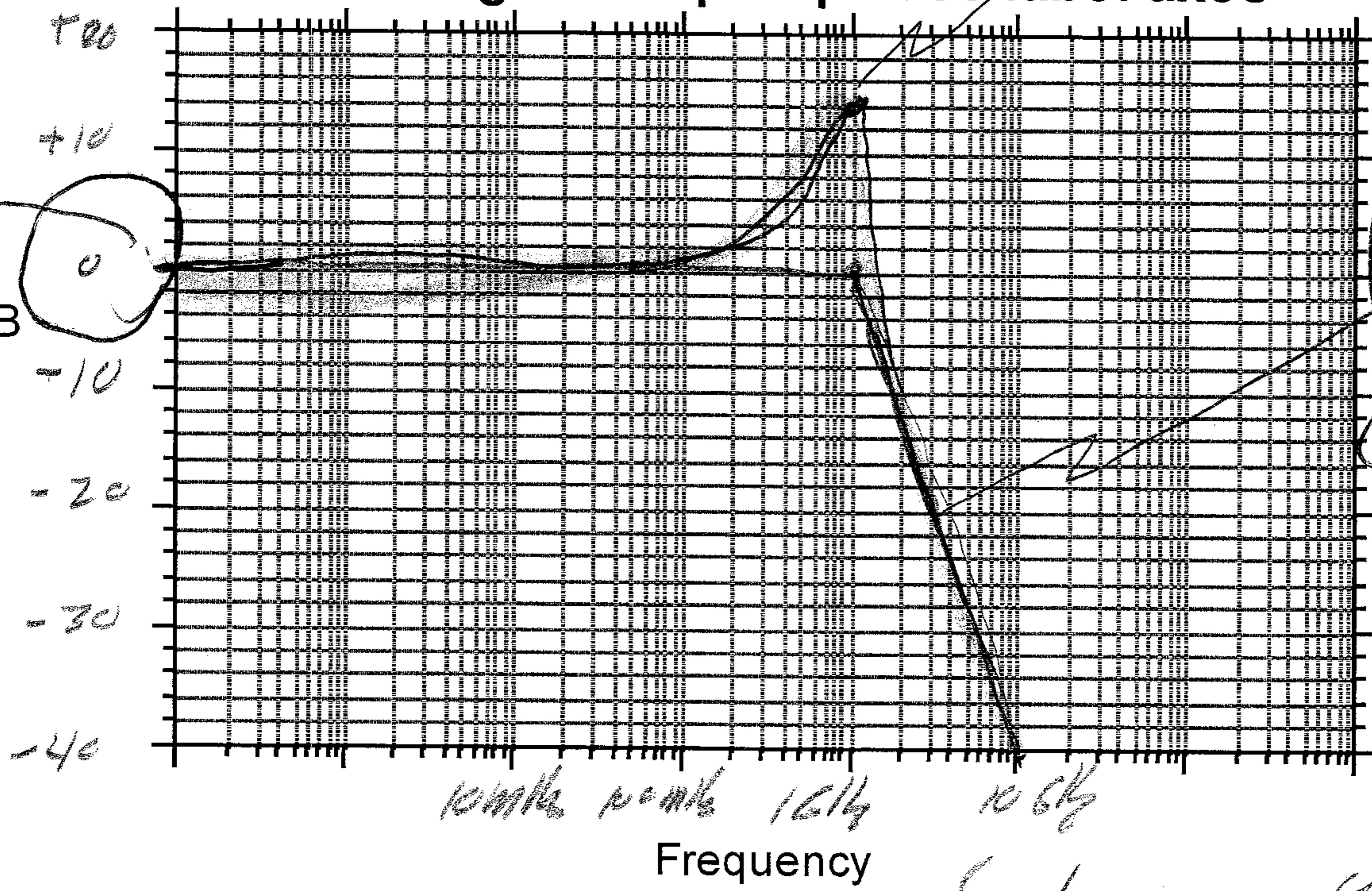

$$H(\omega) = \frac{1}{1 + j\omega 2\zeta/\omega_n - \omega^2/\omega_n^2}$$

$$\begin{aligned} & \text{at } \omega = \omega_n: \quad H(1) \\ & \text{at } \omega \gg \omega_n: \quad H \approx \frac{-j\omega}{2\zeta} \\ & \text{at } \omega = 0: \quad H = \frac{\omega_n^2}{\omega^2} \end{aligned}$$

$$\frac{1}{2\zeta} = \frac{1}{\omega_n} = 14 \text{ dB}$$

$$f_n = 1 \text{ kHz}$$