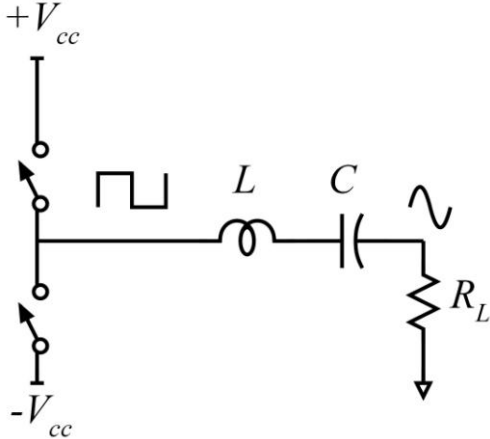
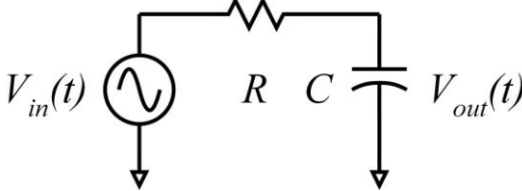


ECE 2c problem set 1 (Fourier Series and Fourier Transforms)

<p>Problem 1: <i>Practical application of Fourier series.</i> The drawing shows the concept of a switched-mode radio-frequency transmitter. These use switches to generate a square wave signal which is then filtered to produce the desired sine-wave. The 2 switches are in opposite phase and produce a 1 GHz square wave at their junction point. The LC filter passes only the 1 GHz fundamental component to the load. (a) Find the AC voltage at the load and (b) if the load is 50 Ohms, find the power.</p>	 <p style="text-align: center;">$V_{cc} = 5.0 \text{ Volts}$</p>
<p>(c) if we change the filter so that it passes only *3GHz*, again find the AC voltage at the load and the load power.</p>	
<p>Problem 2: (a) Plot the following functions over one cycle, where $f = 100 \text{ MHz}$. Plot at least 32 points/waveform. To keep it from getting tedious, please use Excel, Matlab, or some other computer program to calculate and to plot. (b) what do you think $V_n(t)$ becomes when n is very large?</p>	$V_1(t) = 1V \cdot \sin(2\pi ft)$ $V_3(t) = V_1(t) + (1/3) \cdot 1V \cdot \sin(3 \cdot 2\pi ft)$ $V_5(t) = V_3(t) + (1/5) \cdot 1V \cdot \sin(5 \cdot 2\pi ft)$ $V_7(t) = V_5(t) + (1/7) \cdot 1V \cdot \sin(7 \cdot 2\pi ft)$ $V_9(t) = V_7(t) + (1/9) \cdot 1V \cdot \sin(9 \cdot 2\pi ft)$
<p>Problem 3: $R=100 \text{ Ohms}$ and $RC=1 \text{ nS}$. $f=100 \text{ MHz}$. (a) Using Phasor analysis, compute note the correction $\rightarrow V_{out}(t)$ if $V_{in}(t) = 1V \cdot \sin(2\pi ft)$. \leftarrow</p>	
<p>(b) repeat with $V_{in}(t) = (1/3) \cdot 1V \cdot \sin(3 \cdot 2\pi ft)$ (c) repeat with $V_{in}(t) = (1/5) \cdot 1V \cdot \sin(5 \cdot 2\pi ft)$ (d) repeat with $V_{in}(t) = (1/7) \cdot 1V \cdot \sin(7 \cdot 2\pi ft)$ (e) repeat with $V_{in}(t) = (1/9) \cdot 1V \cdot \sin(9 \cdot 2\pi ft)$ use Excel, Matlab, or some other computer program to calculate and to plot the sum of the answers you found in parts (a-e).</p>	
<p>Problem 4: (a) Plot the following functions over one cycle, where $f = 100 \text{ MHz}$. Plot at least 32 points/waveform. To keep it from getting tedious, please use Excel, Matlab, or some other</p>	$V_1(t) = 1V \cdot \sin(2\pi ft)$ $V_2(t) = V_1(t) - (1/2) \cdot 1V \cdot \sin(2 \cdot 2\pi ft)$ $V_3(t) = V_2(t) + (1/3) \cdot 1V \cdot \sin(3 \cdot 2\pi ft)$ $V_4(t) = V_3(t) - (1/4) \cdot 1V \cdot \sin(4 \cdot 2\pi ft)$

computer program to calculate and to plot. (b) what do you think $V_n(t)$ becomes when n is very large ?.


Problem 5: Understanding Fourier Transforms. In the graphs at right, the steps in time are 1 ns, so each waveform lasts 4 ns. V_{sig} has amplitudes of +1 V and -1 V. The basis signals $V_1(t)$, $V_2(t)$, $V_3(t)$ and $V_4(t)$ are as sketched, and have voltage values of either +1V or -1V.

(a) Writing $V_{sig}(t) = a_1V_1(t) + a_2V_2(t) + a_3V_3(t) + a_4V_4(t)$, find the values for a_1 through a_4 .

(b) please check the dot products of $V_3(t)$ and $V_4(t)$, where we have defined

$$\bar{V}_a \cdot \bar{V}_b = \langle V_a | V_b \rangle = \frac{1}{T} \int_0^T V_a(t)V_b(t)dt$$

where $T=4$ ns.

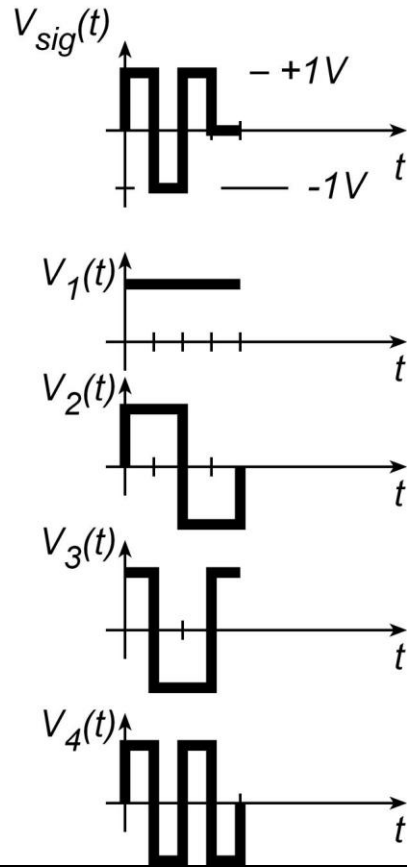

We can view V_1 as the DC component, V_2 and V_3 as the sine and cosine components of the first harmonic, and V_4 as the 2nd harmonic