

ECE2c Problem set #6:


model statement: for old-fashioned mobility-limited NFETs,

$$I_d = (\mu C_{ox} W_g / 2L_g)(V_{gs} - V_{th})^2(1 + \lambda V_{ds}) \text{ for } V_D > V_g - V_{th} \text{ and}$$

$$I_d = (\mu C_{ox} W_g / 2L_g)(2(V_{gs} - V_{th})V_{DS} - V_{DS}^2)(1 + \lambda V_{ds}) \text{ for } V_D < V_g - V_{th}.$$

As is discussed in the notes, for PFETs, the polarities of  $V_{gs}$  and  $V_{ds}$ , and the direction of  $I_D$ , are all reversed.

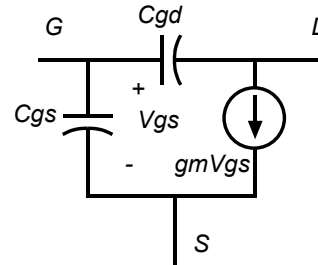Problem 1: The problem uses the MOSFET equivalent circuit to the right. Note the capacitances  $C_{gs}$  and  $C_{gd}$  which model high-frequency effects.



The circuit is called a super-buffer. Ignore DC bias; you don't need it.

Q1:  $C_{gs} = C_{gd} = 0$ .  $R_{ds} = \text{infinity}$ .


Q2:  $C_{gs} = 200 \text{ fF}$ ,  $C_{gd} = 0$ .  $R_{ds} = \text{infinity}$

$g_{m1} = 100 \text{ mS}$ ,  $g_{m2} = 200 \text{ mS}$ ,  $R = 1000 \text{ Ohm}$ ,  $C = 400 \text{ fF}$

- (a) Draw a small-signal equivalent circuit of the circuit.
- (b) Compute by nodal analysis the small signal transfer function  $V_{out}/V_{gen}$ , with the answer given in dimensionless ratio-of-polynomials form:


$$Ks^m \frac{1 + a_1s + a_2s^2 + \dots}{1 + b_1s + b_2s^2 + \dots}$$

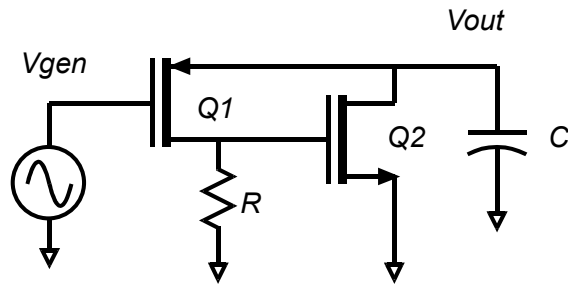- (c) Find the damping factor  $\zeta$  and the resulting natural resonant frequency  $f_n$ .



- (d) Plot an accurate root locus.
- (e) Accurately plot the Magnitude of the frequency response in Bode Form on semilog paper.
- (f) If  $V_{gen}(t)$  is a 1 mV step-function, compute and plot  $V_{out}(t)$ .

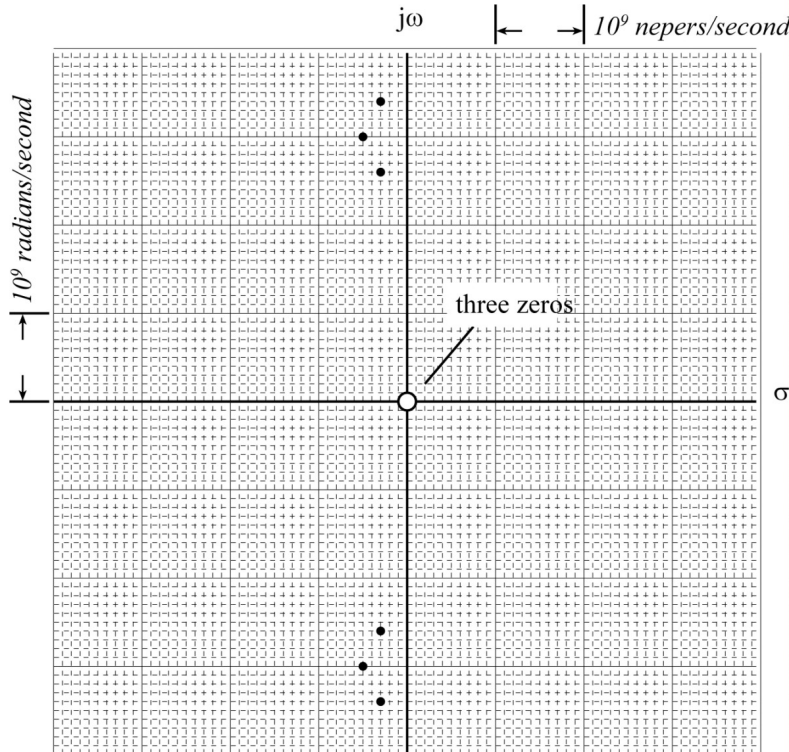Problem 2: A circuit has a transfer function  $H(s)$  with root locus as below.  $H(s) = 1$  when  $s = \sigma + j\omega = 0 + j(3 \cdot 10^9) \text{ rad/sec}$



(a) The answer must be in this standard form:


$$H(s) = Ks^3 \times \frac{1}{(1-s/s_{p1})(1-s/s_{p2})\dots}$$

where K has units of (seconds)<sup>3</sup>.

(b) By measuring distances on the the graph itself with a rule , hand-draw a **Bode** plot of  $\|H(j2\pi f)\|$  from 1MHz to 1 GHz, with at least 3 points in the (500MHz +/- 100MHz) filter passband, and other points at 159, 318, 636, and 795 MHz.

(c) using your favorite computer program (spreadsheets, matlab...), generate a similar graph by computer.

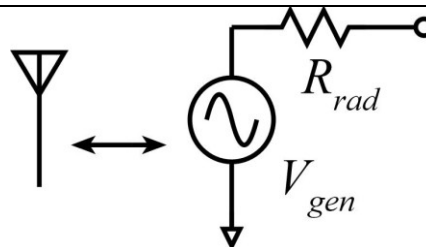Problem 3: The problem concerns the input stage of a radio receiver. To the right is shown a Thevenin equivalent model of an antenna. Please assume  $R_{rad} = 50 \Omega$ . In the lower circuit, the FET has  $(\mu C_{ox} W_g / 2L_g) = 1 \text{ mA/V}^2$ ,  $\lambda = 0.05 \text{ V}^{-1}$ , and  $V_{th} = 0.3 \text{ V}$ .




(a) Find  $V_{in,DC}$  such that the drain current of Q1 is 0.1 mA. (b) Setting  $V_{DD} = 3.3 \text{ V}$ , select  $R_L$  such that the DC drain voltage of

Q1 is 1.5 V. (c) find the small-signal parameters of Q1. The FET has  $C_{gd} = 0$  fF and  $C_{gs} = 31.8$  pF. (d) replacing the FET and the antenna with their equivalent (small signal) models, draw a small-signal diagram of the overall circuit. (e) Setting  $L = 0.797$  nH, compute  $V_{out}(s)/V_{gen}(s)$ . The answer must be in this standard form:

$$H(s) = Ks^1 \times \frac{1}{(1-s/s_{p1})(1-s/s_{p2})\dots}$$

where

K has units of (seconds)<sup>1</sup>.

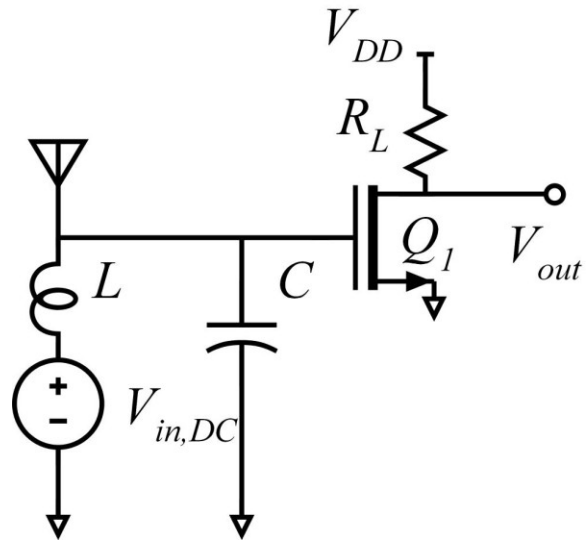

(f) Plot an accurate root locus. (g) Accurately plot the Magnitude of the frequency response in Bode Form on semilog paper. (h) If  $V_{gen}(t)$  is a 1 mV step-function, compute and plot  $V_{out}(t)$ .

larger copy of graph from problem 2

