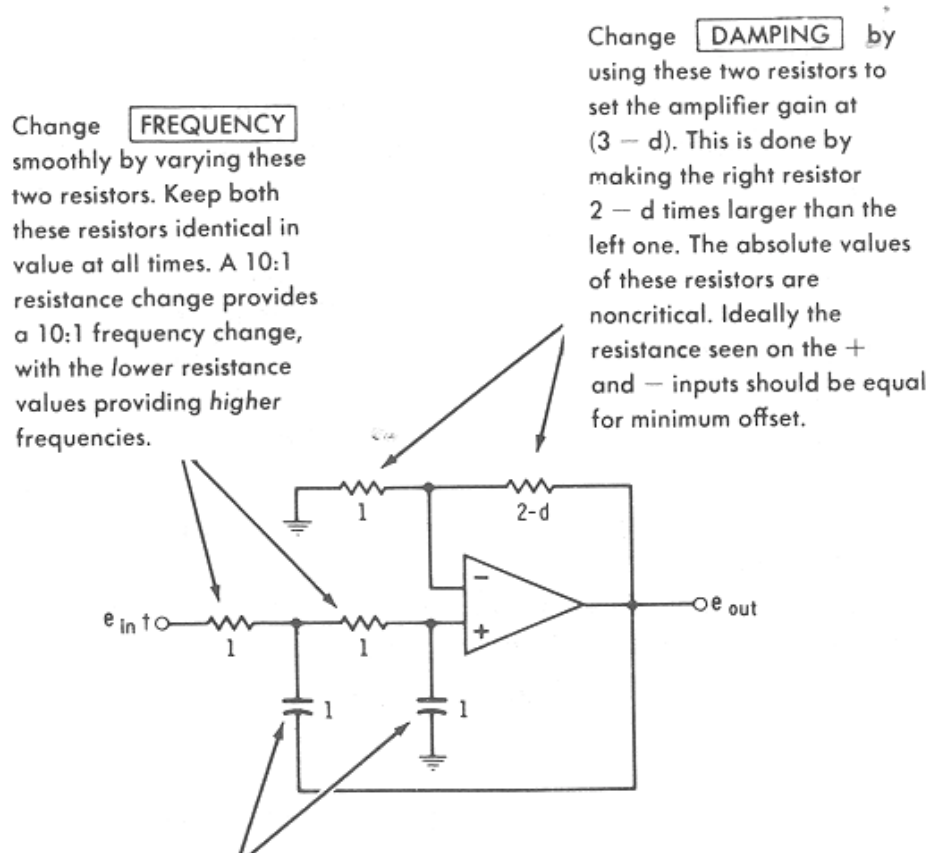


2nd-Order Sallen-Key Filters

Sallen-Key 2nd-order Low-Pass

Below is a normalized 2nd-order low-pass based on the Sallen-Key (voltage-controlled voltage source, or VCVS) topology. The element values shown are for a cutoff frequency of 1 rad/sec. Note that the damping factor d in this figure is related to the damping factor discussed in class as $d = 2\xi$.



Change **FREQUENCY** in steps by switching these capacitors. Keep both capacitors identical in value at all times. Doubling the capacitors halves the frequency and vice versa.

GAIN of this circuit is fixed at $3 - d$ or roughly 2:1 (+6 decibels). Adjust signal levels elsewhere in the system.


† must return to ground via low-impedance dc path.

(Circuit becomes high-pass by switching positions of frequency-determining resistors and capacitors.)

Sallen-Key equal-component 2nd-order active low-pass (from D. Lancaster, *Active Filter Cookbook*, Sams Books: New York, 1980).

Sallen-Key 2nd-order High-Pass

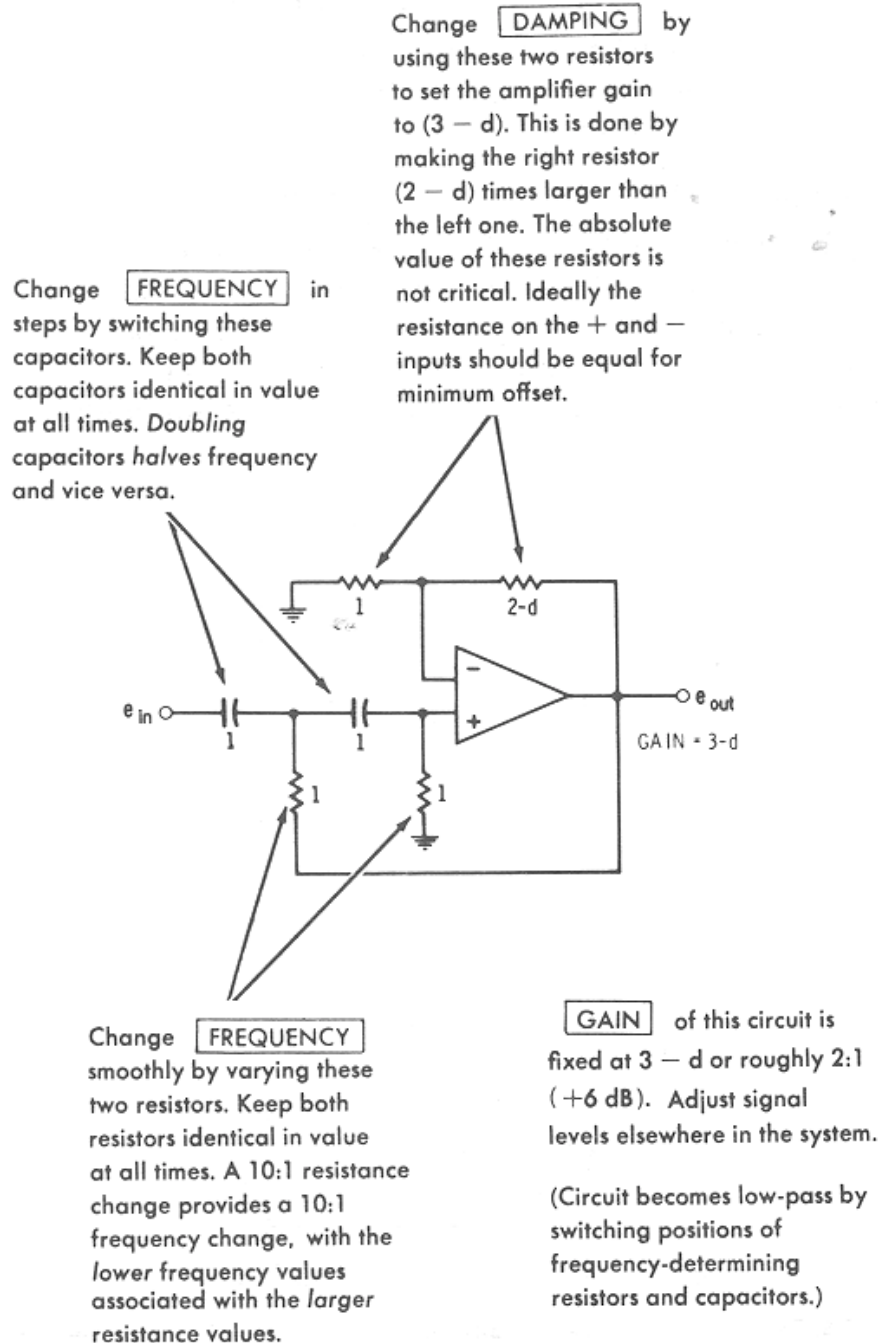Below is a normalized 2nd-order high-pass based on the Sallen-Key topology. The element values shown are for a cutoff frequency of 1 rad/sec. Note that the damping factor d in this figures is related to the damping factor discussed in class as $d = 2\xi$.



Sallen-Key equal-component 2nd-order active high-pass (from D. Lancaster, *Active Filter Cookbook*, Sams Books: New York, 1980).