
ECE594I Notes set 11: Methods for Circuit Noise Analysis

Mark Rodwell

University of California, Santa Barbara

References and Citations:

Sources / Citations :

Kittel and Kroemer : Thermal Physics

Van der Ziel : Noise in Solid - State Devices

Papoulis : Probability and Random Variables (hard, comprehensive)

Peyton Z. Peebles : Probability, Random Variables, Random Signal Principles (introductory)

Wozencraft & Jacobs : Principles of Communications Engineering.

Motchenbaker : Low Noise Electronic Design

Information theory lecture notes : Thomas Cover, Stanford, circa 1982

Probability lecture notes : Martin Hellman, Stanford, circa 1982

National Semiconductor Linear Applications Notes : Noise in circuits.

Suggested references for study.

Van der Ziel, Wozencraft & Jacobs, Peebles, Kittel and Kroemer

Papers by Fukui(device noise), Smith & Personik (optical receiver design)


National Semi. App. Notes (!)

Cover and Williams : Elements of Information Theory


summary

Goal: Computing Signal/Noise Ratio and Sensitivity

Radio Receiver

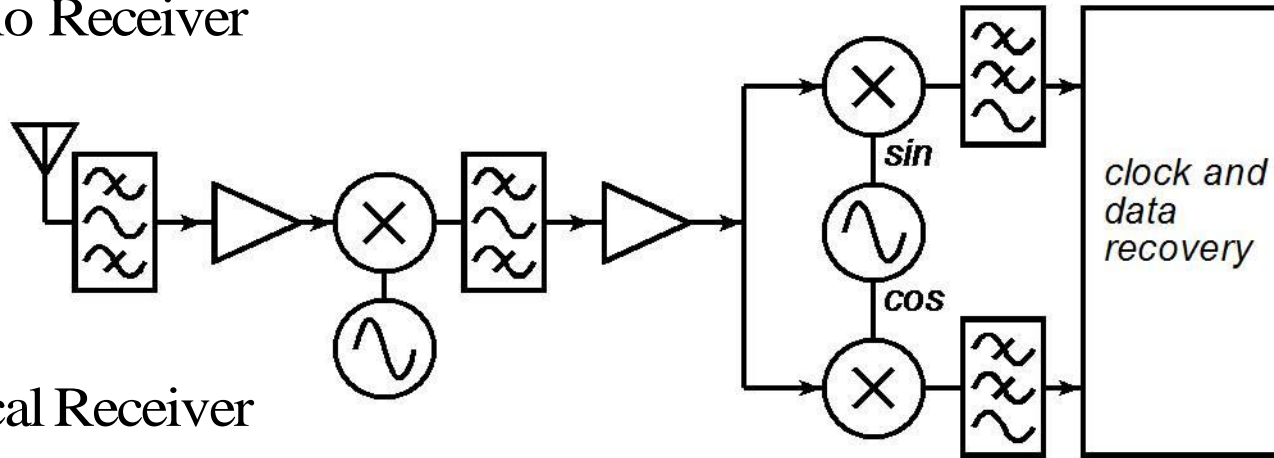


Optical Receiver

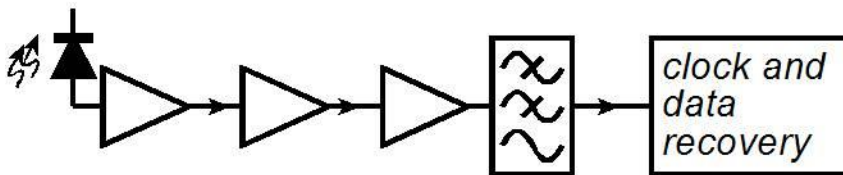

To compute the receiver sensitivity,
we must find the signal/noise ratio at the decision circuit input.

It is often convenient to compare the input signal magnitude
to the equivalent input-referred noise.

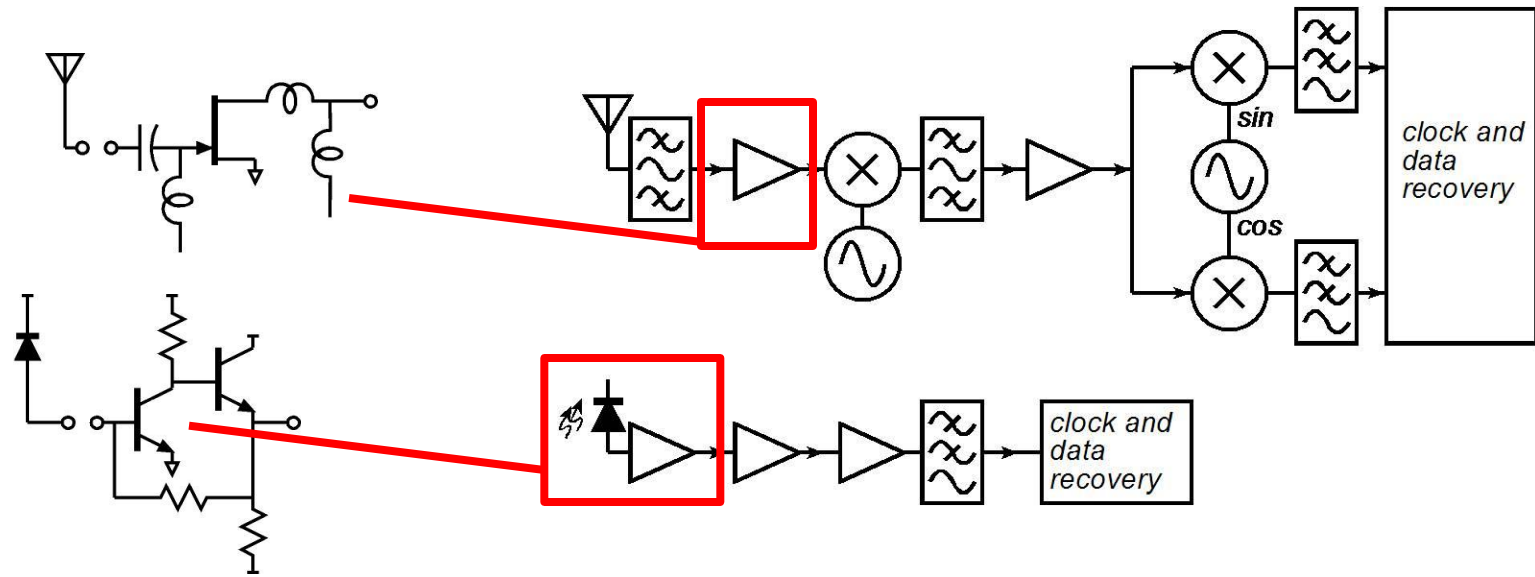
Goal: Computing Signal/Noise Ratio and Sensitivity



Each functional block of the radio receiver is a subcircuit

Each sub - circuit contains active and passive devices, all having noise models

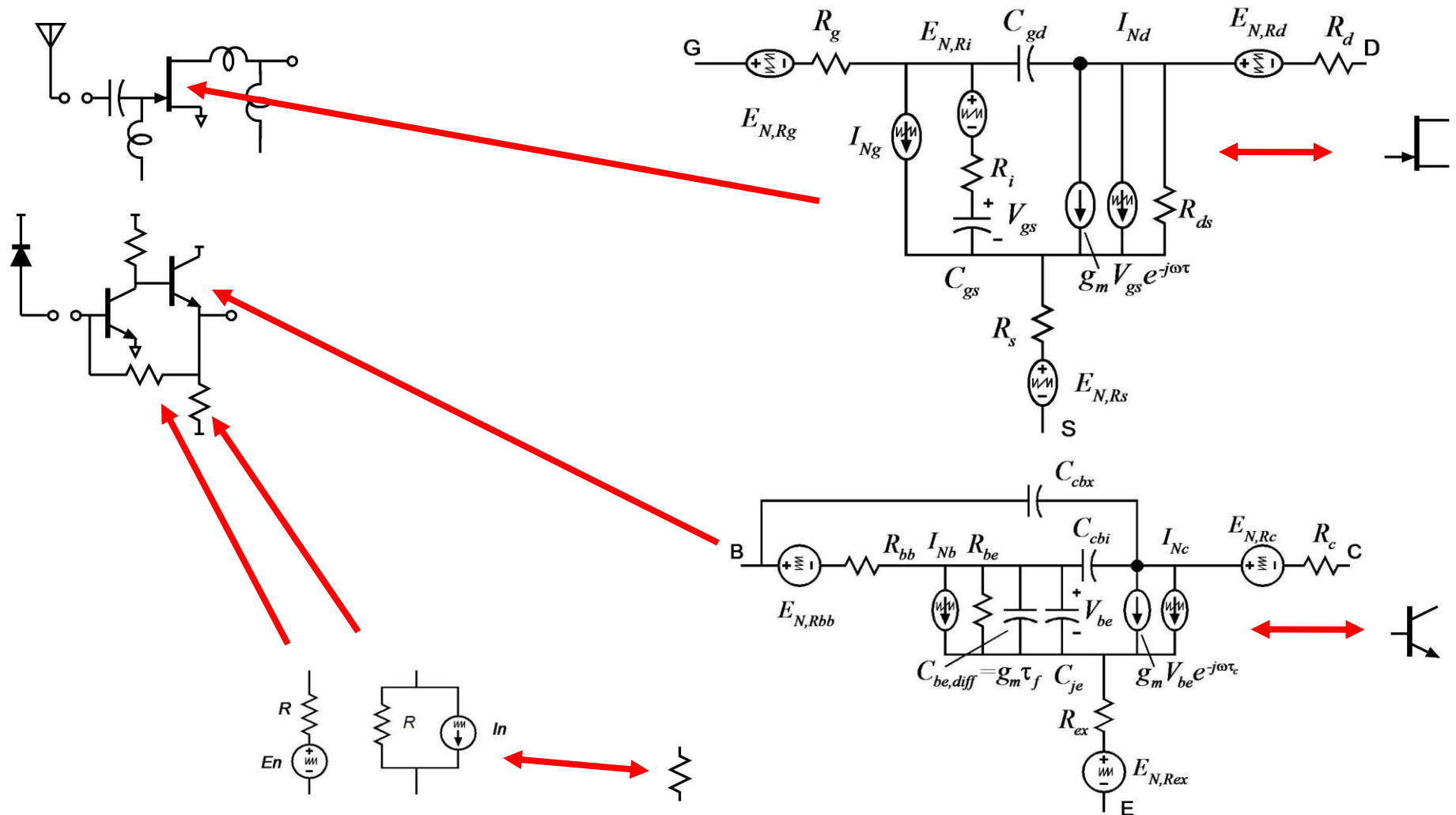Goal: Computing Signal/Noise Ratio and Sensitivity





There are a large # of noise generators within each circuit block



Goal: Computing Signal/Noise Ratio and Sensitivity

Earlier we found device terminal noise arising from internal fluctuations.

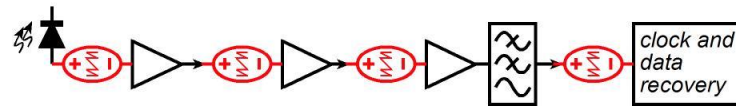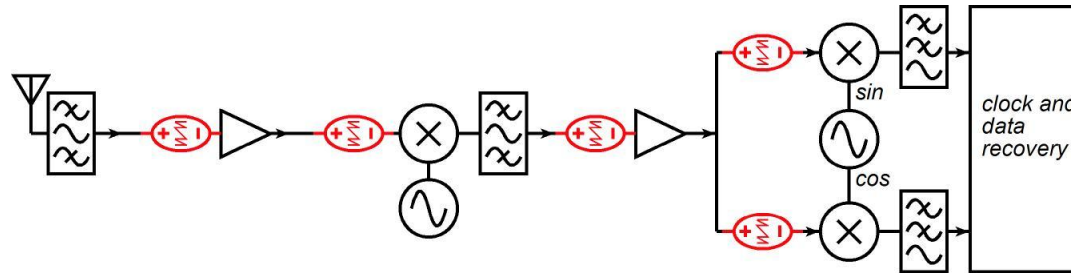Next we learn to compute the equivalent input noise of each sub-circuit :



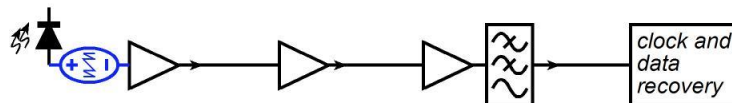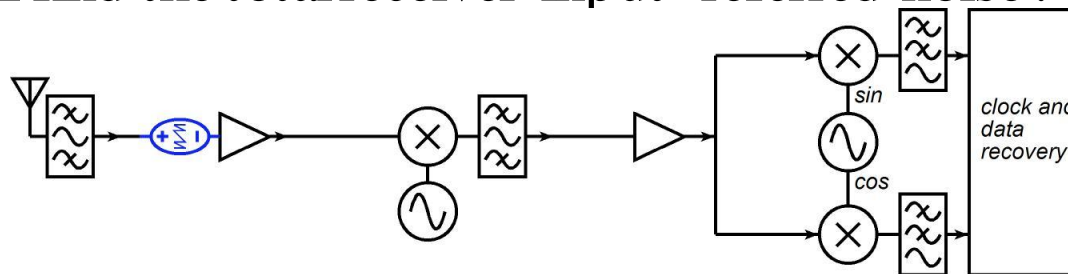From this we will find the total receiver input-referred noise :




Receiver SNR and sensitivity can then be found.

**device noise models
(collecting results
from prior lectures)**

Thermal Noise

$$\tilde{S}_{E_n E_n}(jf) = 4R * \left[\frac{hf}{2} + \frac{hf}{\exp(hf/kT) - 1} \right]$$

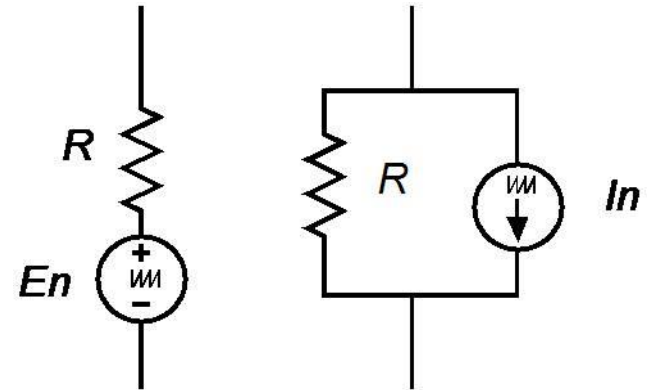
$$\tilde{S}_{I_n I_n}(jf) = \frac{4}{R} * \left[\frac{hf}{2} + \frac{hf}{\exp(hf/kT) - 1} \right]$$



For $hf \ll kT$ these become

$$\tilde{S}_{E_n E_n}(jf) = 4kTR$$
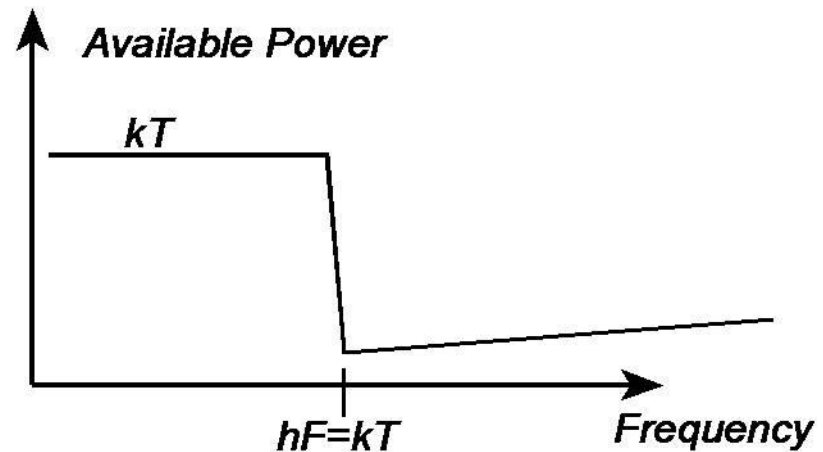
$$\tilde{S}_{I_n I_n}(jf) = \frac{4kT}{R}$$




Noise from any impedance under thermal equilibrium

For any component or complex network under thermal equilibrium
(no energy supply)

$$\frac{dP_{\text{available noise}}}{df} = kT$$
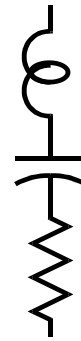
$$\Rightarrow \tilde{S}_{E_n E_n}(jf) = 4kT \operatorname{Re}(Z) \quad \text{or} \quad \tilde{S}_{I_n I_n}(jf) = 4kT \operatorname{Re}(Y)$$



This follows from the 2nd law of thermodynamics.

This allows quick noise calculation of complex passive networks

This allows quick noise calculation of antennas.

Biased semiconductor devices are NOT in thermal equilibrium.

Noise from an Antenna


$$\frac{dP_{\text{available noise}}}{df} = kT \Rightarrow \tilde{S}_{E_n E_n}(jf) = 4kT \operatorname{Re}(Z)$$

The antenna has both Ohmic and radiation resistances.

The Ohmic resistance has a noise voltage of spectral density $4kT_{\text{ambient}} R_{\text{Ohmic}}$, where T_{ambient} is the physical antenna temperature

By the 2nd law, the radiation resistance has a noise voltage of spectral density $4kT_{\text{field}} R_{\text{rad}}$, where T_{field} is the average temperature of the region from which the antenna receives signal power

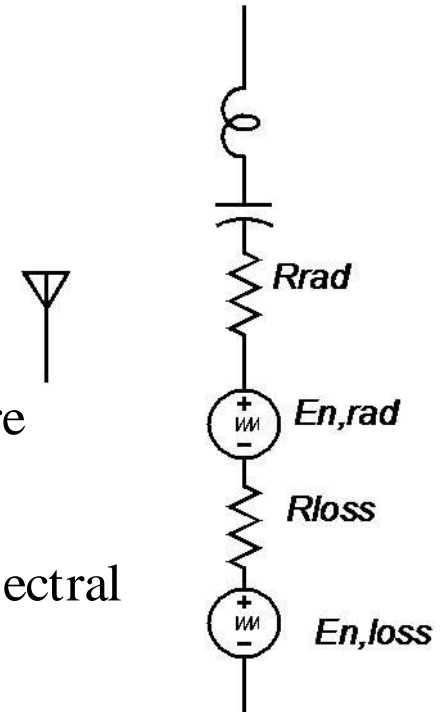Inter - galactic space is at 3.8 Kelvin....



Noise in PN and Schottky junctions

The diode current is

$$I_{diode} = I_s (e^{qV/kT} - 1) = I_s e^{qV/kT} - I_s = I_{forward} + I_{reverse}$$



Both the forward and reverse currents have shot noise, hence

$$\tilde{S}_{I_{diode}} = 2qI_{forward} + 2qI_{reverse} = 2q(I_{diode} + 2I_s)$$

Under strong forward bias, $\tilde{S}_{I_{diode}} = 2qI_{diode}$

Under strong reverse bias, $\tilde{S}_{I_{diode}} = 2qI_s$

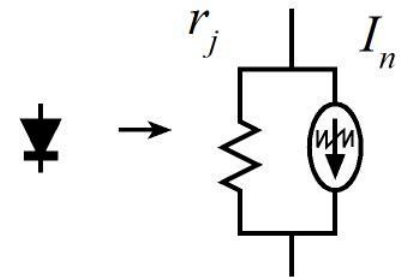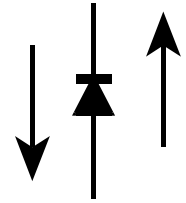Under zero bias, $\tilde{S}_{I_{diode}} = 4kT / r_{diode}$, as required by the 2nd law.



Shot noise and PN junctions: another model

For a strongly forward biased junction


$$\tilde{S}_{I_{diode}} = 2qI_{diode} = 2kT / r_{diode} \text{ where } r_{diode} = kT / qI_{diode}$$

or

$$\tilde{S}_{V_{diode}} = 2kTr_{diode}$$

hence


$$\frac{dP_{diode}}{df} = kT / 2$$

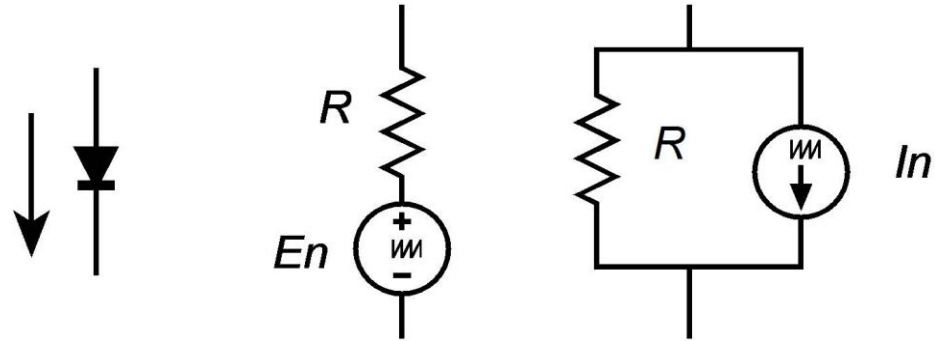

A biased diode has noise 1/2 that of a resistor of equal small - signal impedance.

The factor of 2 arises from one - way current flow.

Bipolar Transistor Model--with Noise

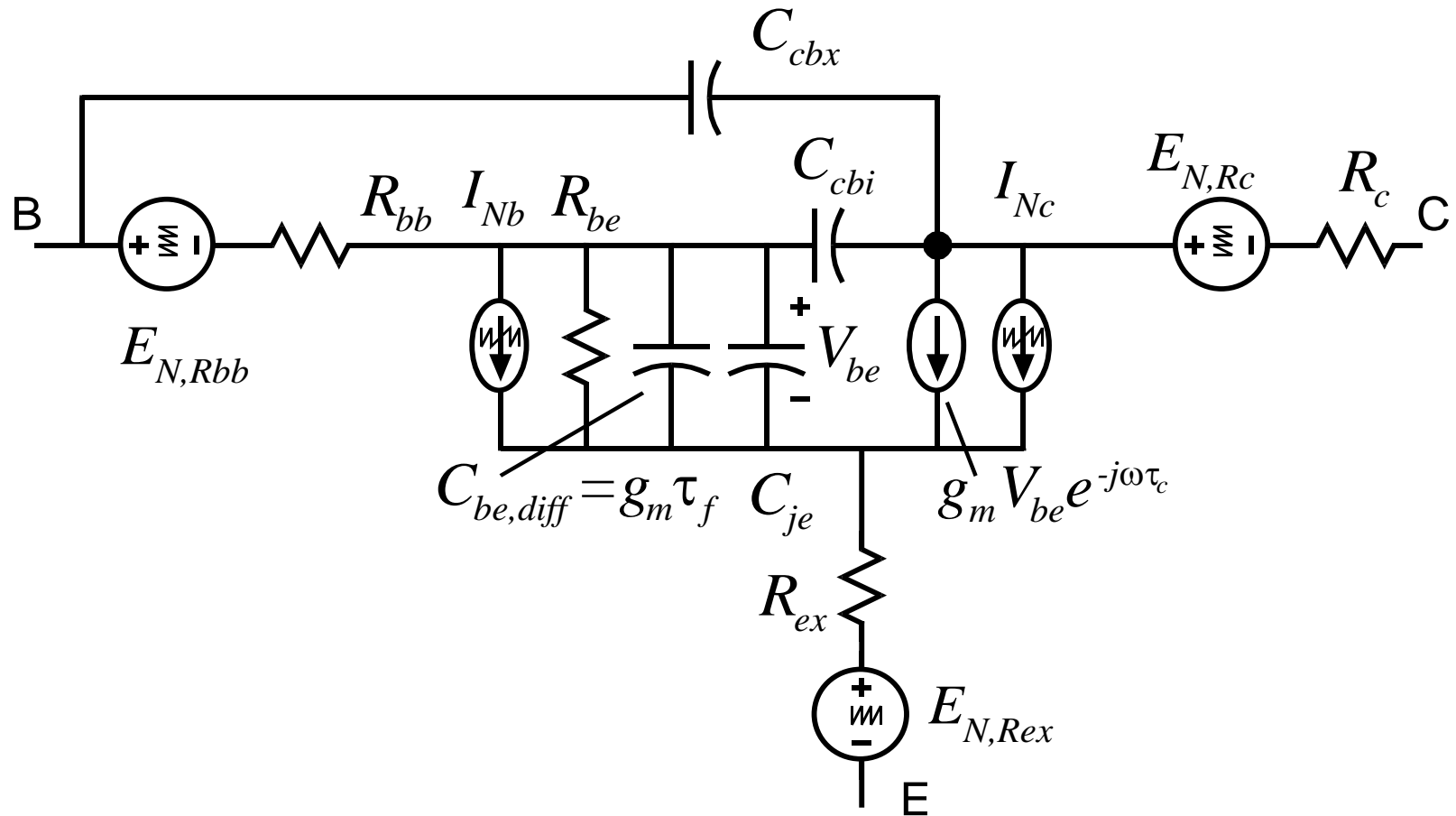

Bipolar Noise Model

Collector shot noise

$$\tilde{S}_{I_{nc}} = 2qI_c = 2kT / r_e = 2kTg_m$$

Base shot noise

$$\tilde{S}_{I_{nb}} = 2qI_b = 2kT / r_{be}$$


We have found a slight correlation of I_{nb} and I_{nc} (a cross - spectral density) when $2\pi f(\tau_b + \tau_c)$ approaches 1. We will ignore this small effect.

The physical resistors (R_{bb} , R_{ex} , R_c) have thermal noise of spectral density $\tilde{S}_V = 4kTR$

R_{be} and $r_e = 1 / g_m$ are not physical resistors.


The noise of R_{be} and r_e are the base and the collector shot* noise generators.

FET Noise Model

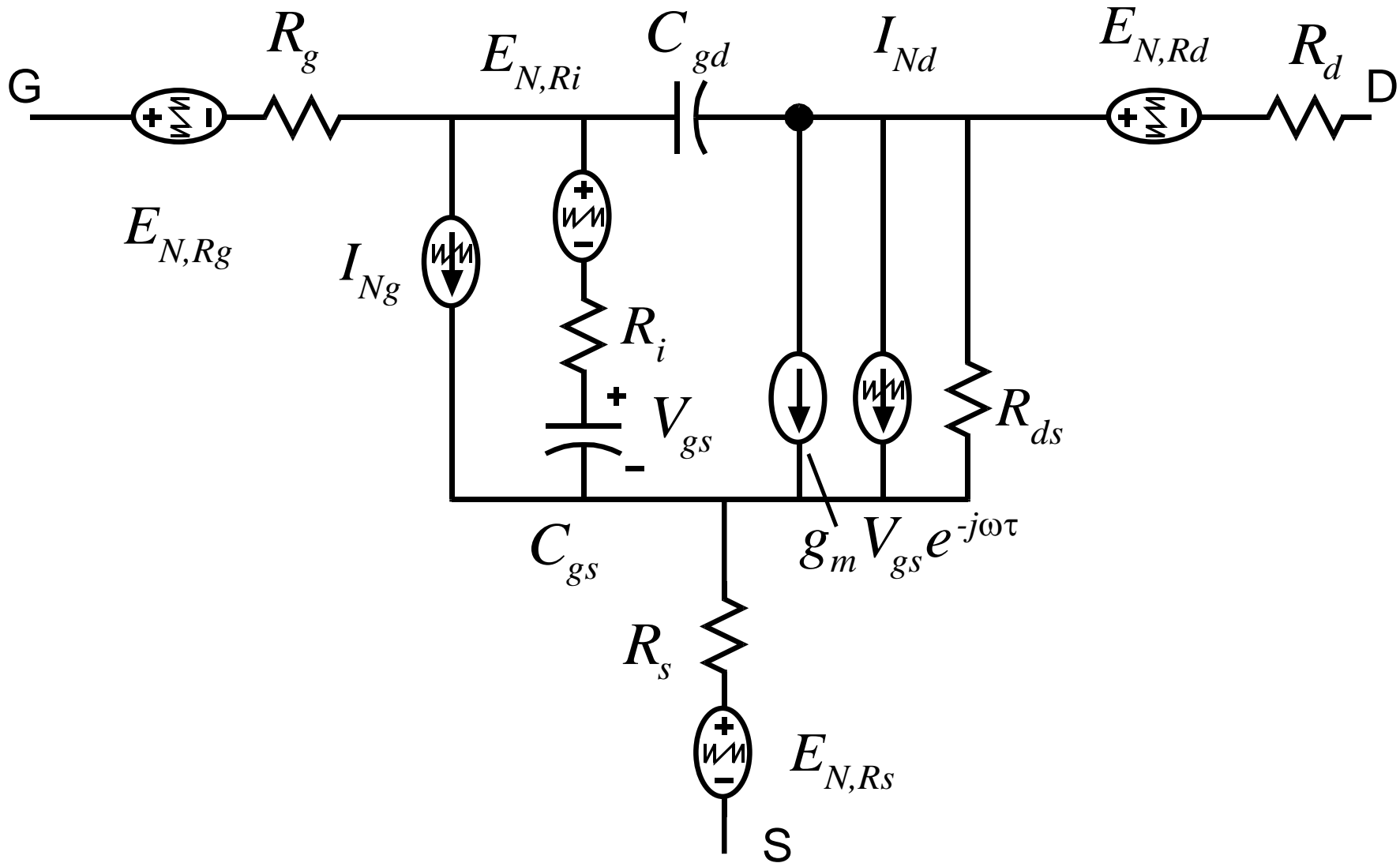

Shot Noise of Heavily Attenuated Light

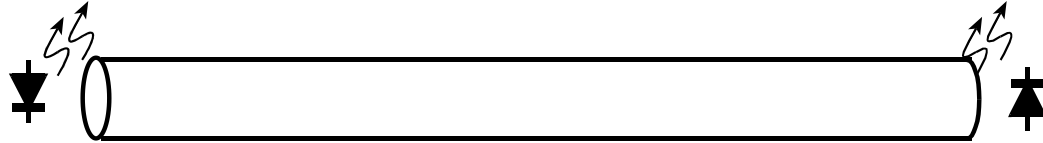If the received power is much smaller than the transmitted power (losses are high) then the received power statistics will be dominated by the statistics of photon loss (Bernoulli trials).



With a mean received optical power \bar{P}_{out} , the received power has fluctuations with spectral density

$$\tilde{S}_{P_{out}P_{out}} = 2h\nu\bar{P}_{out}$$

This produces on a photodetector with quantum efficiency η a photocurrent

$I_{ph} = (\eta q / h\nu)P_{out}$ with a spectral density


$$\tilde{S}_{I_{out}I_{out}} = 2q\bar{I}_{out}$$

If attenuation between source and detector is not small, it is easy to construct

cases where $\tilde{S}_{P_{out}P_{out}} \neq 2h\nu\bar{P}_{out}$

circuit noise calculations

Circuit noise analysis: Goals

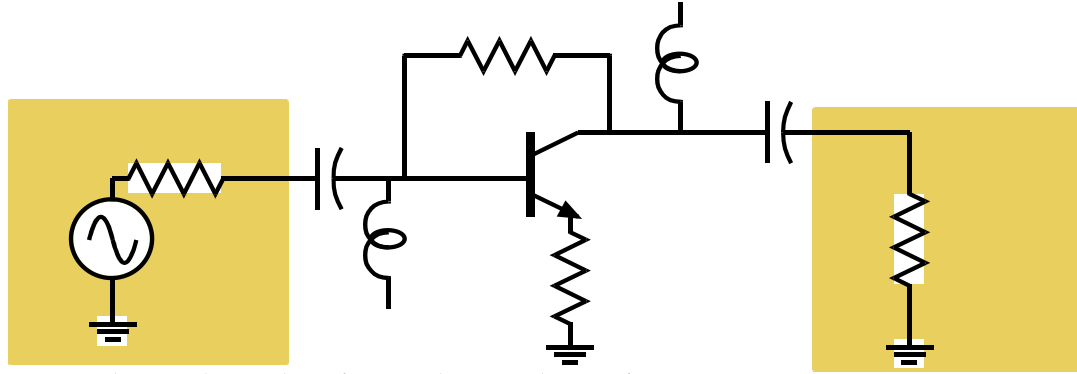

The circuit output has both signal and noise.

$$V_{out} = A_v V_{in} + V_{noise,output}$$

Noise arises from the generator, the amplifier, and the load


$$V_{noise,output} = V_{noise,generator} + V_{noise,amplifier} + V_{noise,load}$$

These noise terms can be represented by fictitious input terms :

$$V_{out} = A_v V_{in} + V_{noise,output} = A_v (V_{in} + V_{noise,input}), \text{ where } V_{noise,input} = V_{noise,output} / A_v$$

How do we calculate the output-referred noise ?

Noise model of this circuit

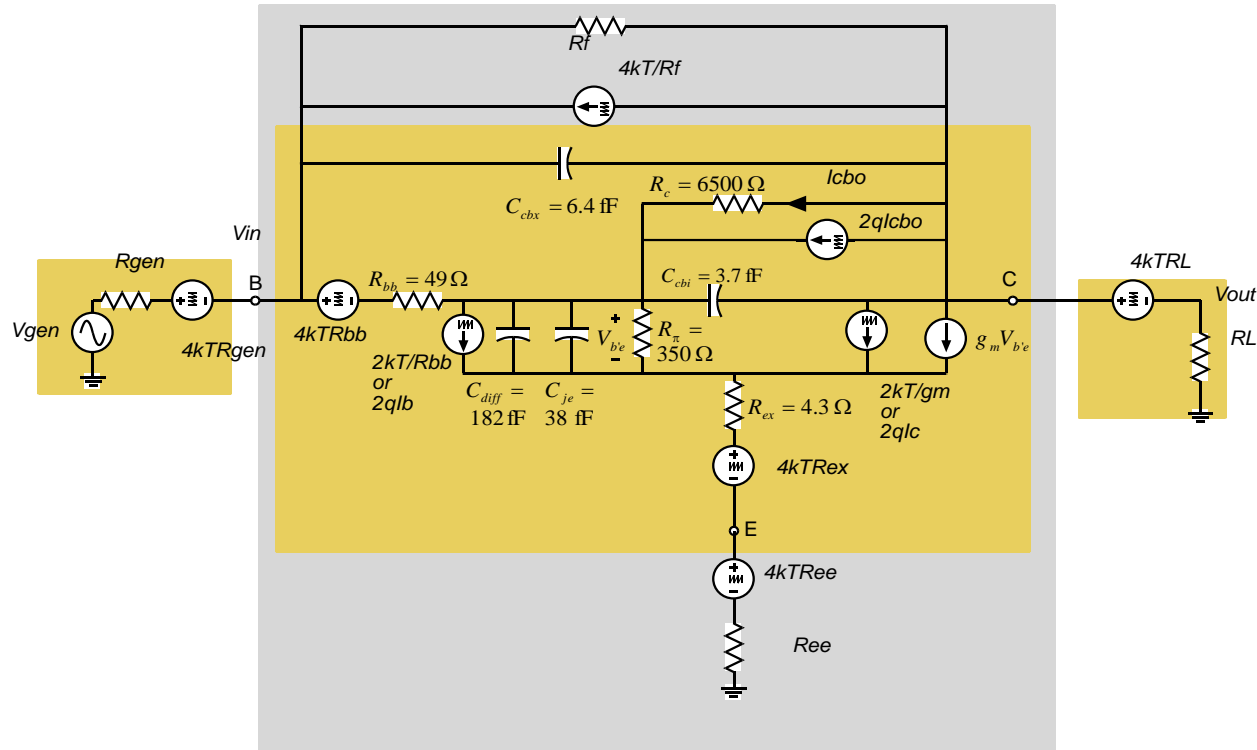

The circuit has a large number of noise generators.



Noise analysis of most practical circuits is of formidable complexity.

Brute-force methods are too hard for hand analysis.

We will learn more efficient techniques.

We will illustrate calculations with a very simple circuit.

Circuit Noise Analysis: 1st Example (a)

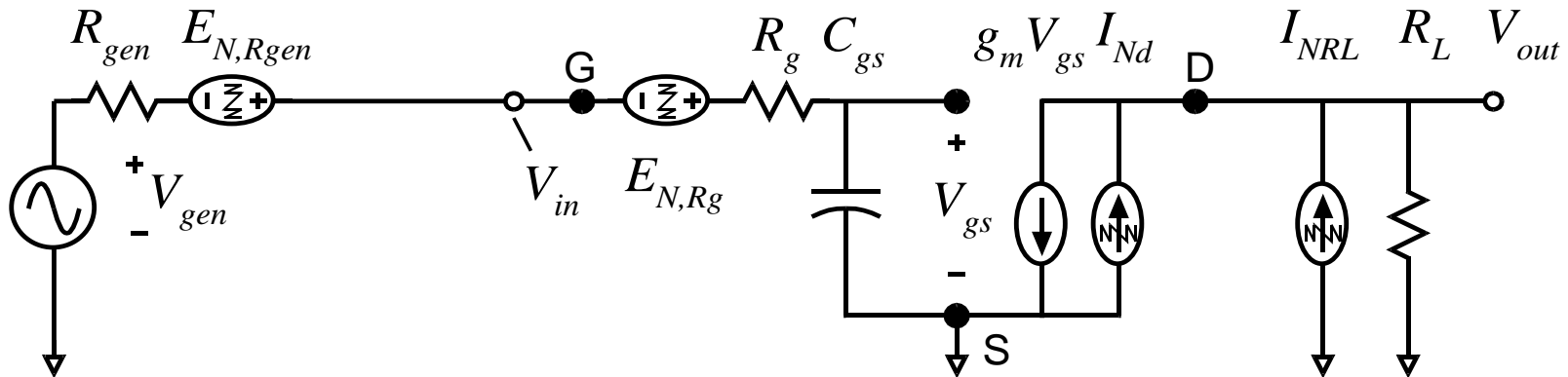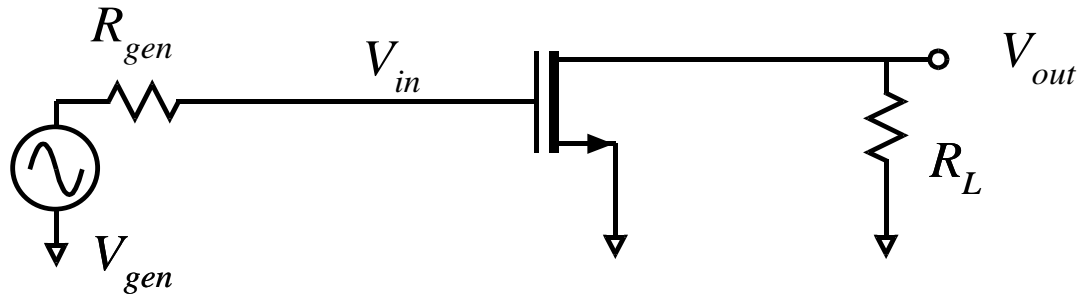


Simple amplifier, with simplified noise model.

Notation: Single - sided, Hz - based spectral densities

$$\tilde{S}_{V_n V_n} = 4kTR \text{ or } \tilde{S}_{I_n I_n} = 4kTG \text{ for all resistors}$$

$$\tilde{S}_{I_{nd} I_{nd}} = 4kT\Gamma g_m \text{ for the FET channel noise.}$$

Circuit Noise Analysis: 1st Example (b)

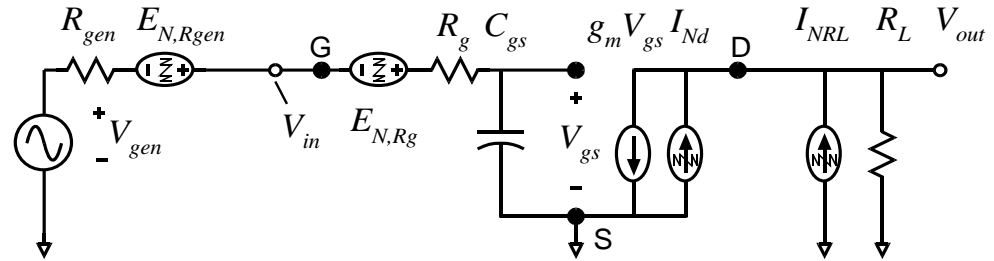

Now calculate the output voltage :

$$\begin{aligned}
 V_{out} &= \left(V_{gen} + E_{N,R_{gen}} + E_{N,R_g} \right) \left(1 + j2\pi f C_{gs} (R_g + R_{gen}) \right)^{-1} (-g_m R_L) \\
 &\quad + \left(I_{N,d} + I_{N,R_L} \right) R_L \\
 &= V_{out,signal} + V_{out,amp_noise} + V_{out,gen_noise}
 \end{aligned}$$

$$V_{out,signal} = V_{gen} \left(1 + j2\pi f C_{gs} (R_g + R_{gen}) \right)^{-1} (-g_m R_L)$$

$$V_{out,amp_noise} = E_{N,R_g} \left(1 + j2\pi f C_{gs} (R_g + R_{gen}) \right)^{-1} (-g_m R_L) + \left(I_{N,d} + I_{N,R_L} \right) R_L$$

$$V_{out,gen_noise} = E_{N,R_{gen}} \left(1 + j2\pi f C_{gs} (R_g + R_{gen}) \right)^{-1} (-g_m R_L)$$

where

$$\tilde{S}_{V_n V_n}(jf) = 4kTR \text{ or } \tilde{S}_{I_n I_n}(jf) = 4kTG \text{ for all resistors}$$

$$\tilde{S}_{I_{nd} I_{nd}}(jf) = 4kTg_m \text{ for the FET channel noise.}$$

Reminder

If

$$V_y(jf) = H(jf)V_x(jf)$$

Then


$$\tilde{S}_{V_y V_x}(jf) = H(jf)\tilde{S}_{V_y V_x}(jf)$$

$$\tilde{S}_{V_x V_y}(jf) = \tilde{S}_{V_x V_y}(jf)H^*(jf)$$

and

$$\tilde{S}_{V_y V_y}(jf) = \|H(jf)\|^2 \tilde{S}_{V_x V_x}(jf)$$

Circuit Noise Analysis: 1st Example (c)

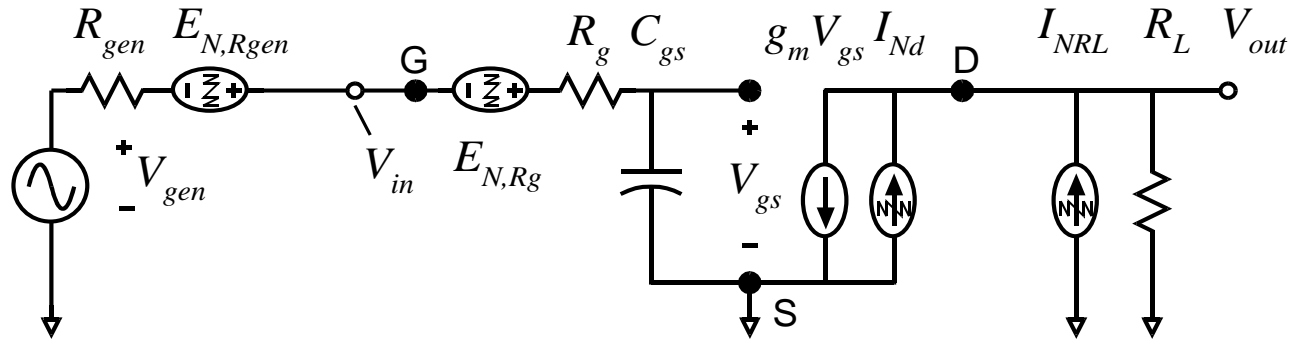

So :

$$V_{\text{out;signal}} = V_{\text{gen}} \left(1 + j2\pi f C_{gs} (R_g + R_{gen}) \right)^{-1} (-g_m R_L)$$

$$\tilde{S}_{V_{amp,out}}(jf) = \tilde{S}_{N,R_g} \frac{(g_m R_L)^2}{1 + (2\pi f C_{gs})^2 (R_g + R_{gen})^2} + (\tilde{S}_{I_{N,d}} + \tilde{S}_{I_{N,R_L}}) (R_L)^2$$


$$\tilde{S}_{V_{gen,out}}(jf) = \tilde{S}_{N,R_{gen}} \frac{(g_m R_L)^2}{1 + (2\pi f C_{gs})^2 (R_g + R_{gen})^2}$$

where

$$\tilde{S}_{V_n V_n}(jf) = 4kTR \text{ or } \tilde{S}_{I_n I_n}(jf) = 4kTG \text{ for all resistors}$$

$$\tilde{S}_{I_{nd} I_{nd}}(jf) = 4kT\Gamma g_m \text{ for the FET channel noise.}$$

Circuit Noise Analysis: 1st Example (d)

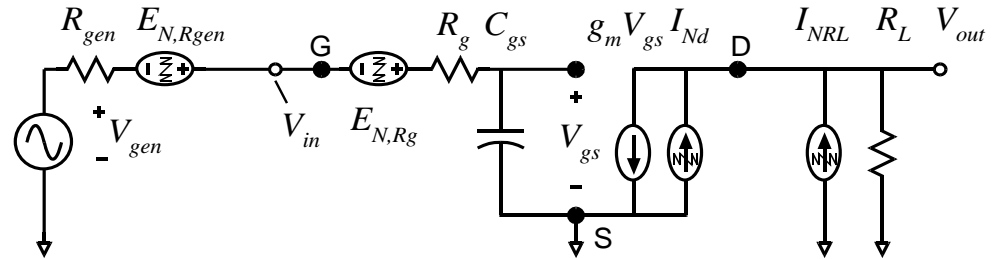

The outputsignal

$$V_{\text{out,signal}} = V_{\text{gen}} \left(1 + j2\pi f C_{gs} (R_g + R_{gen}) \right)^{-1} (-g_m R_L)$$

$$= A_v(j2\pi f) V_{\text{gen}}$$


The outputnoise * due to the amplifier *

$$\tilde{S}_{V_{\text{amp,out}}}(jf) = 4kTR_g \frac{(g_m R_L)^2}{1 + (2\pi f C_{gs})^2 (R_g + R_{gen})^2} + \left(4kT \Pi g_m + \frac{4kT}{R_L} \right) (R_L)^2$$

The outputnoise * due to the generator *

$$\tilde{S}_{V_{\text{gen,out}}}(jf) = 4kTR_{gen} \frac{(g_m R_L)^2}{1 + (2\pi f C_{gs})^2 (R_g + R_{gen})^2}$$

Circuit Noise Analysis: 1st Example (e)

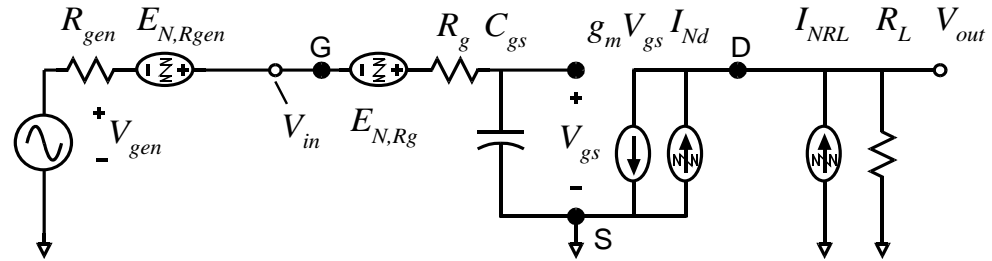

Now Define *equivalent input noise*

$$V_{out} = A_v(jf) * V_{gen} + V_{out,amp_noise} + V_{out,gen_noise}$$

$$= A_v(jf) * (V_{gen} + V_{in,amp_noise} + V_{in,gen_noise})$$

This means simply: $V_{in,gen_noise} = E_{N,gen}$ and $V_{in,amp_noise} = V_{out,amp_noise} / A_v(jf)$


So the amplifier input-referred noise is :

$$\tilde{S}_{V_{amp,in}}(jf) = \frac{\tilde{S}_{V_{amp,out}}(jf)}{\|A_v(jf)\|^2} = \tilde{S}_{V_{amp,out}}(jf) \cdot \frac{1 + (2\pi f C_{gs})^2 (R_g + R_{gen})^2}{(g_m R_L)^2}$$

And the input noise * due to the generator * is :

$$\tilde{S}_{V_{gen,in}}(jf) = 4kTR_{gen}$$

Circuit Noise Analysis: 1st Example (f)

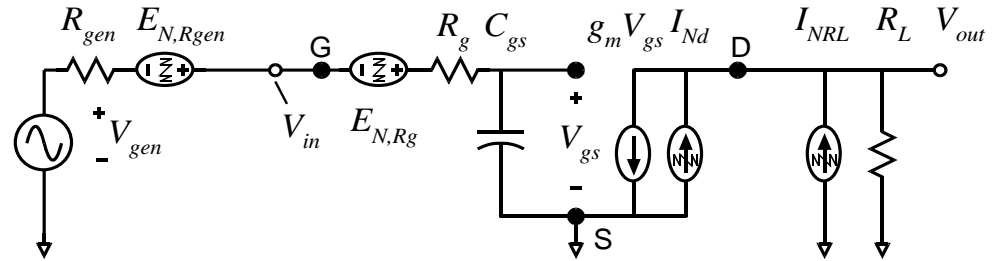

$$\tilde{S}_{V_{amp,in}}(jf) = 4kTR_g \text{ input-referred noise from } R_g$$

$$+ 4kT\Gamma g_m \cdot \left(\frac{1}{g_m^2}\right)^2 \left(1 + (2\pi f C_{gs})^2 (R_g + R_{gen})^2\right)$$

input referred channel noise

$$+ \left(\frac{4kT}{R_L}\right) \left(\frac{1}{g_m^2}\right)^2 \left(1 + (2\pi f C_{gs})^2 (R_g + R_{gen})^2\right)$$

input-referred load resistor noise


Input noise * from the generator *

$$\tilde{S}_{V_{gen,in}}(jf) = 4kTR_{gen}$$

Circuit Noise Analysis: 1st Example (g)

Noise Figure definition :
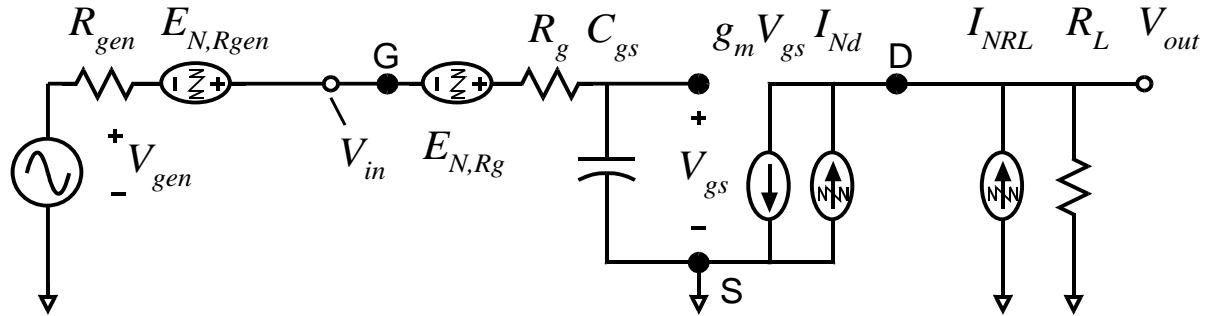
$$F = \frac{\tilde{S}_{V_{gen,in}}(jf) + \tilde{S}_{V_{amp,in}}(jf)}{\tilde{S}_{V_{gen,in}}(jf)}$$



From which we can write


$$\tilde{S}_{V_{in,total_noise}}(jf) = 4kTR_{gen}F$$

Signal/Noise ratio :

$$SNR = \frac{\tilde{S}_{V_{signal}}(jf)}{\tilde{S}_{V_{in,total_noise}}(jf)}$$

Where $\tilde{S}_{V_{signal}}(jf)$ is the input signal's power spectral density

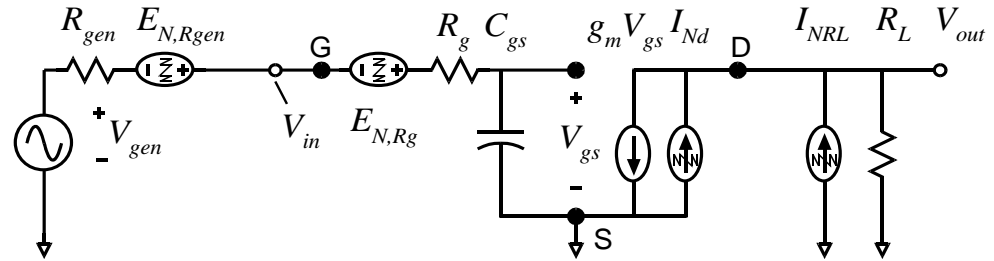Circuit Noise Analysis: 1st Example: Summary



These are the exact steps for calculation of input-referred noise, output-referred noise, SNR, and noise figure.

This is how a computer might calculate these.

The method is extremely tedious, even for a small circuit.

Note that, in computing input-referred noise, many of our calculation steps were cancelled one we found the final answer.

Clearly, then, our method must be inefficient.

Circuit Noise Analysis: 1st Example: Summary

Analysis was hard because we

.....propagated the circuit noise generators to the circuit output,
...then propagated them back to the input.

This involves cancelled steps - - - extra work.

It is particularly inefficient because


*** The most important noise sources are near the input ***

Circuit Noise Analysis: Source Transposition Method

Let us move all the circuit noise generators to the circuit input.

We must restrict ourselves to transformations which do not change the

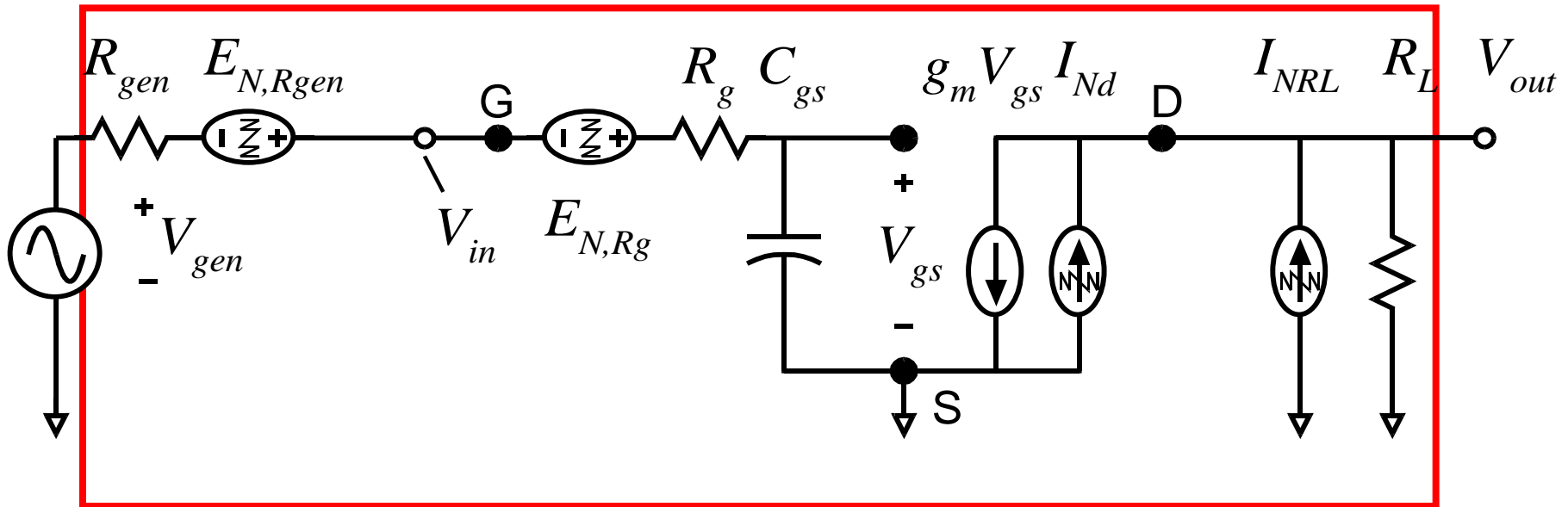
2 - port input - output characteristics of the network between input and output.




This means, make transformations only inside red box

Circuit Noise Analysis: Source Transposition Method


Thevenin - Norton

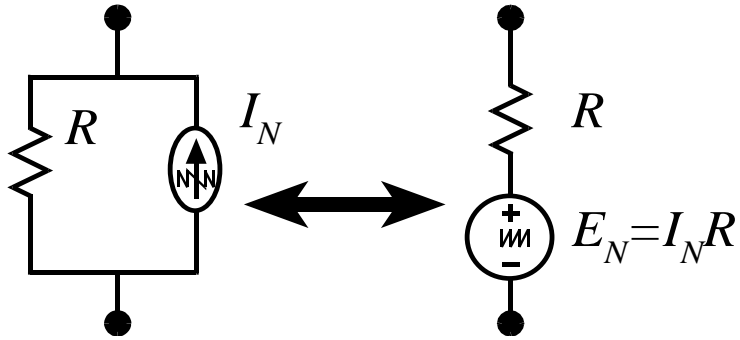


Moving Current Across A Branch

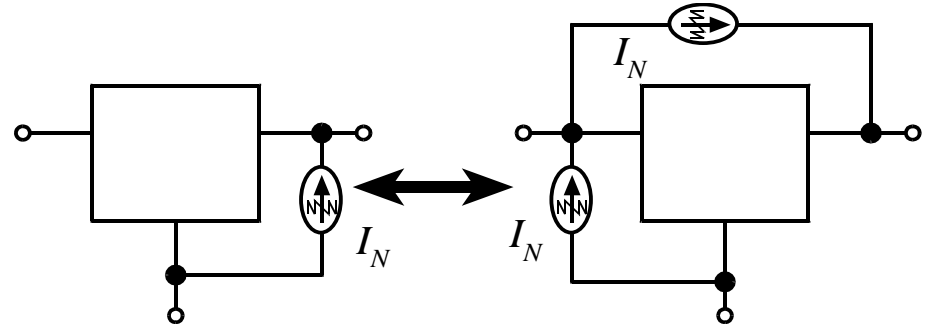

Output-Input



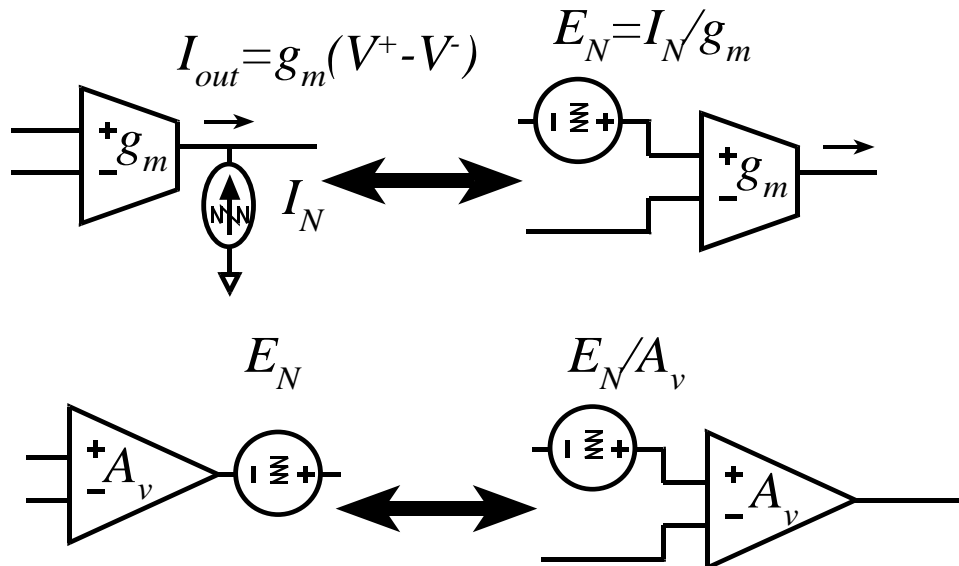


Moving Voltage Through A Node



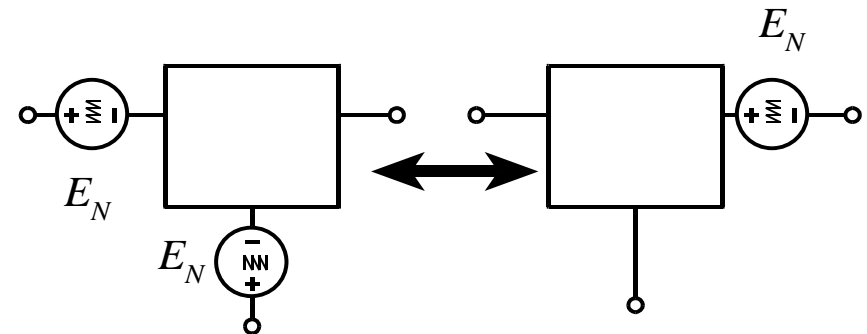


Circuit Noise Analysis: Source Transposition Method

"Walk" I_{NRL} to the input

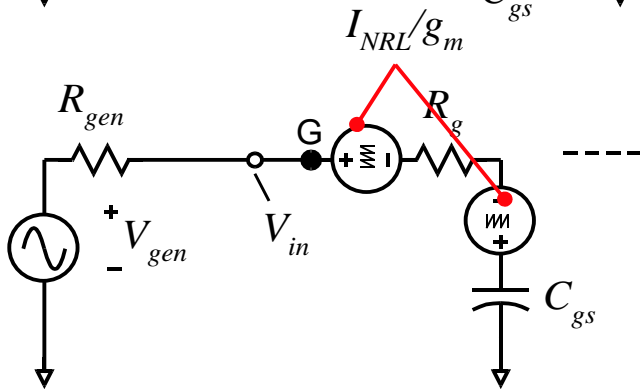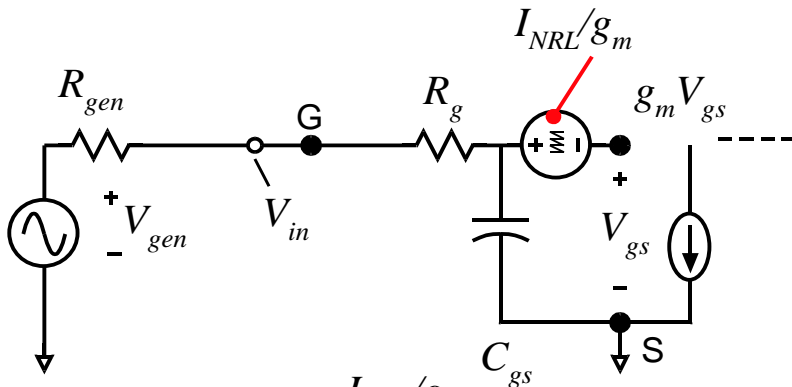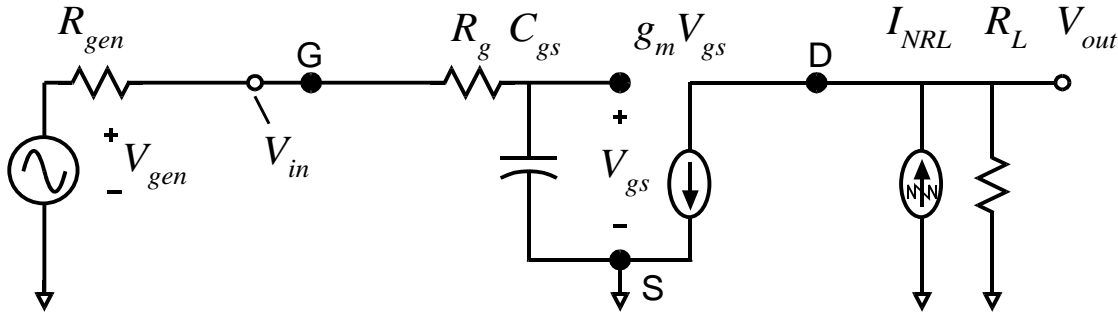

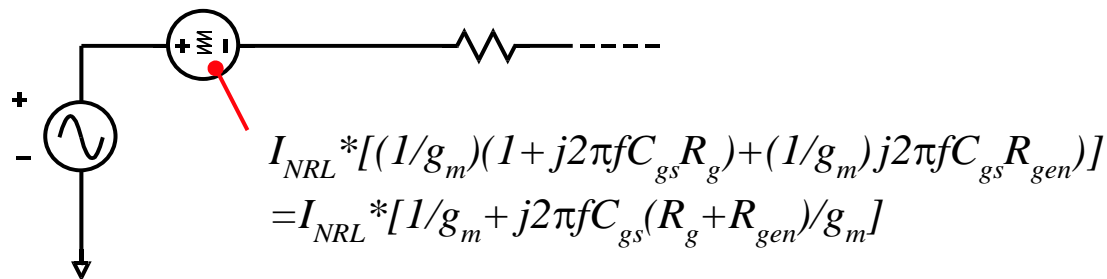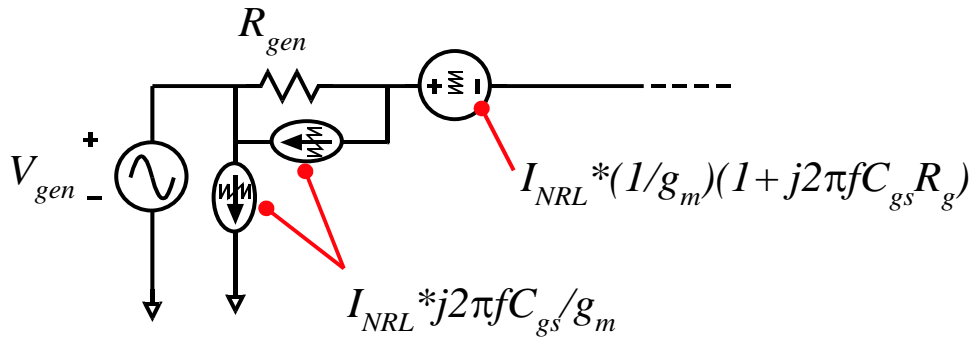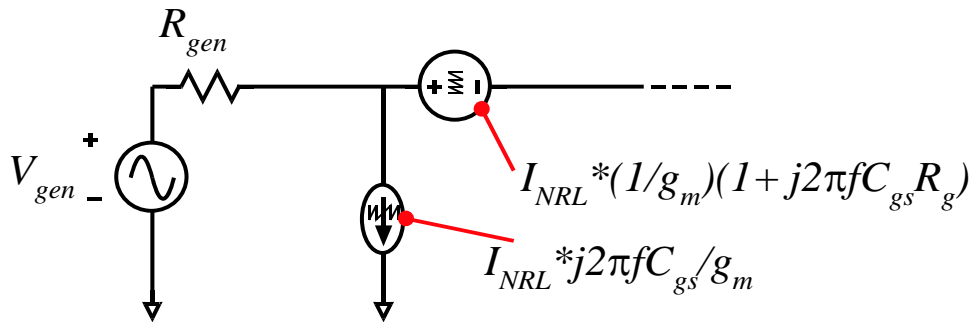Circuit Noise Analysis: Source Transposition Method



Circuit Noise Analysis: Source Transposition Method


$$\tilde{S}_{V_{input};R_L noise}(jf) = \left(\frac{4kT}{R_L} \right) \left(\frac{1}{g_m^2} + \frac{(2\pi f C_{gs})^2 (R_g + R_{gen})^2}{g_m^2} \right)$$

This was certainly not an easy calculation, but because R_L is far from the input, it was the single hardest calculation to make.

The channel noise current generator is in parallel with that of R_L so,

$$\tilde{S}_{V_{input};channel_noise}(jf) = (4kT \Gamma g_m) \left(\frac{1}{g_m^2} + \frac{(2\pi f C_{gs})^2 (R_g + R_{gen})^2}{g_m^2} \right)$$

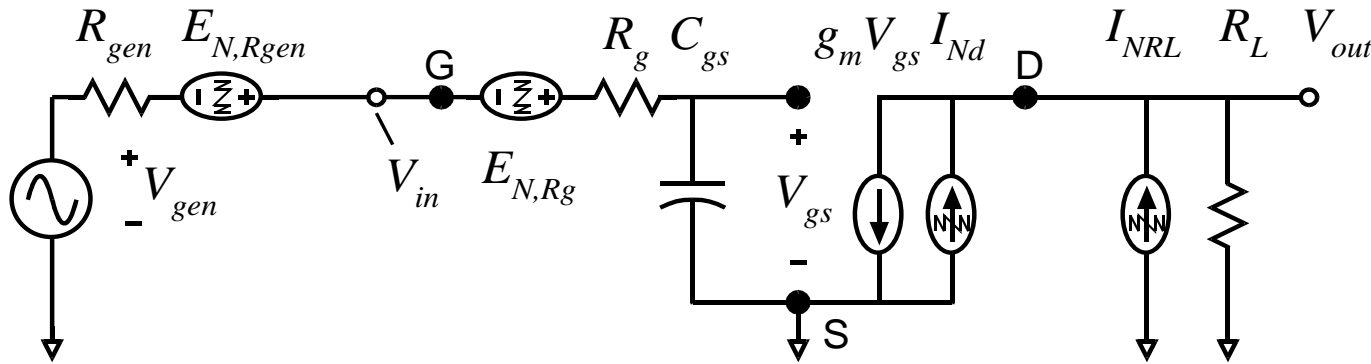Circuit Noise Analysis: Source Transposition Method



In this particularly easy example, we can also see that

$$\tilde{S}_{V_{input};R_g}(jf) = 4kTR_g \quad \tilde{S}_{V_{input};generator}(jf) = 4kTR_{gen}$$


so

$$\tilde{S}_{V_{input};amplifier}(jf) = 4kTR_g + \left(4kT\pi g_m + \frac{4kT}{R_L} \right) \left(\frac{1}{g_m^2} + \frac{(2\pi f C_{gs})^2 (R_g + R_{gen})^2}{g_m^2} \right)$$

hence

$$F = 1 + \frac{\tilde{S}_{V_{input};amplifier}}{\tilde{S}_{V_{input};generator}} = 1 + \frac{R_g}{R_{gen}} + \frac{1}{R_{gen}} \left(\frac{4kT\pi}{g_m} + \frac{4kT}{g_m^2 R_L} \right) \left(1 + (2\pi f C_{gs})^2 (R_g + R_{gen})^2 \right)$$

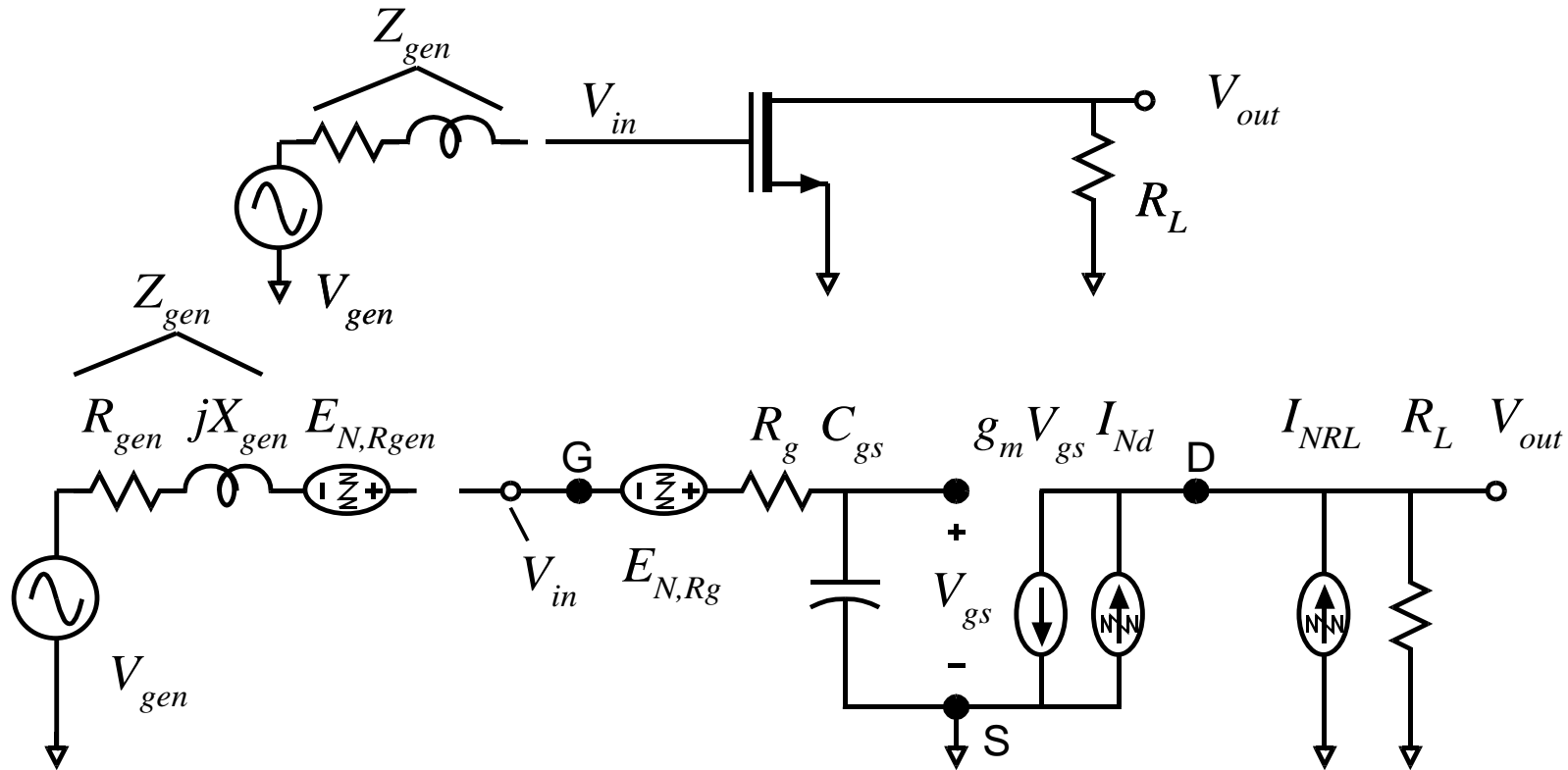Input Noise Voltage / Input Noise Current Model






We frequently wish to specify noise of a device or circuit with the generator impedance unknown and unspecified



The $E_n - I_n$ representation allows this.

En-In Model: Source Transposition Again

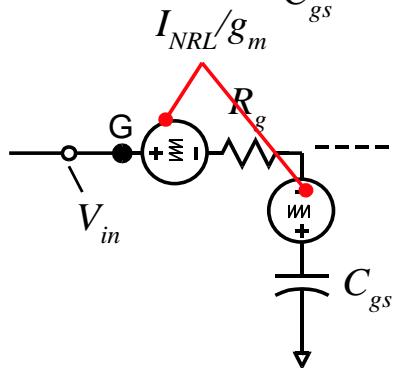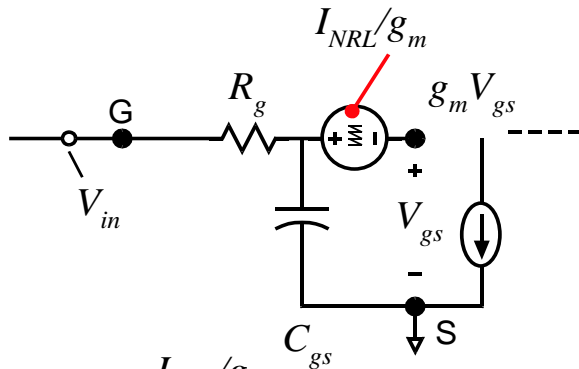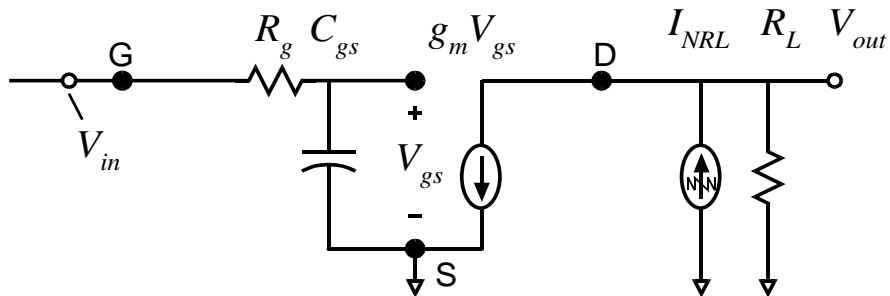Once again, "walk" sources to input - -but not into the generator
 illustration of load resistor noise only.




En-In Model: Source Transposition Again

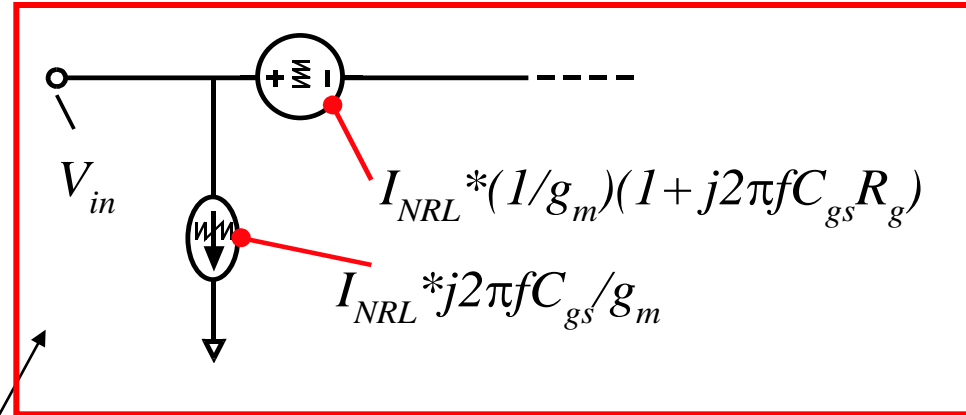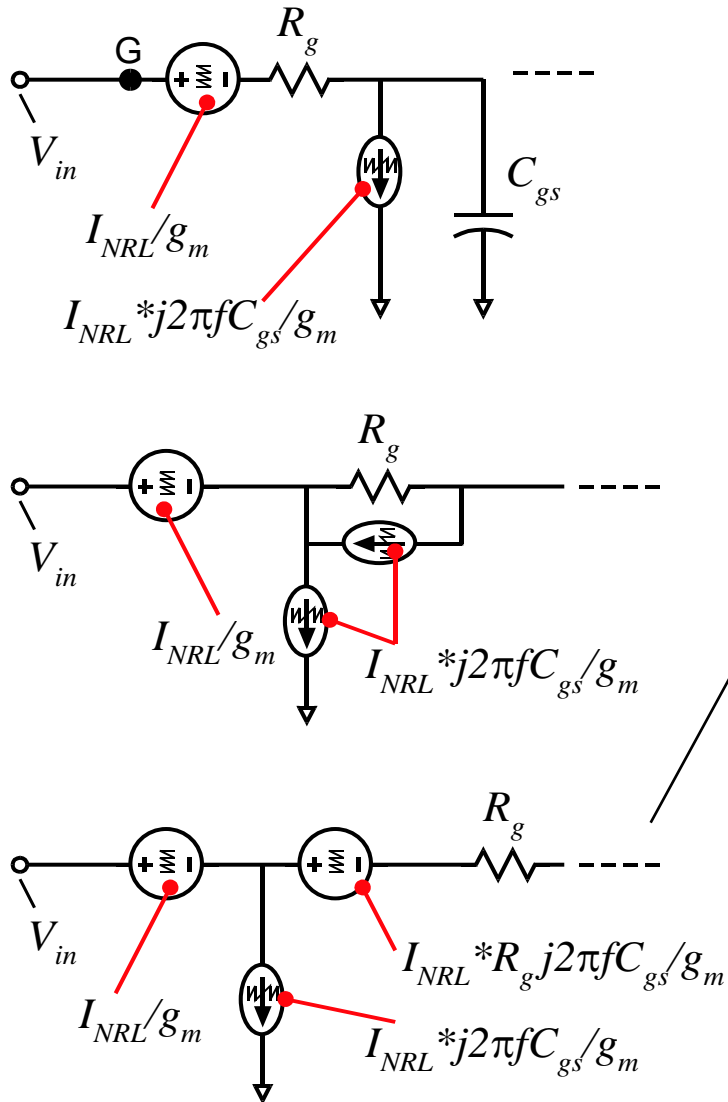

The output noise is represented at V_{in} by a combination of a voltage source and a current source.

As they are both related 1:1 to I_{NRL} , they are 100% correlated.

En-In Model: With All Sources

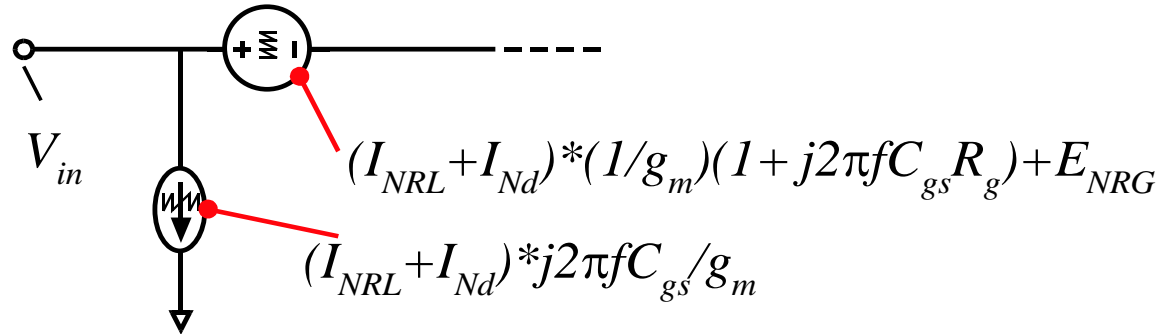

Because

$$E_{n,total} = I_{NRL} \left(\frac{1}{g_m} \right) (1 + j2\pi f C_{gs} R_g) + I_{nd} \left(\frac{1}{g_m} \right) (1 + j2\pi f C_{gs} R_g) + E_{NRG}$$

$$I_{n,total} = I_{NRL} (j2\pi f C_{gs} / g_m) + I_{nd} (j2\pi f C_{gs} / g_m)$$

And Because $\tilde{S}_{E_{NRG}}(jf) = 4kTR_g$ $\tilde{S}_{I_{NRL}}(jf) = 4kT / R_L$ $\tilde{S}_{I_{Nd}}(jf) = 4kT \Gamma g_m$


$$\tilde{S}_{E_{n,total}E_{n,total}}(jf) = \left(\frac{4kT}{R_L} + 4kT \Gamma g_m \right) \left(\frac{1}{g_m} \right)^2 (1 + (2\pi f C_{gs} R_g)^2) + 4kTR_g$$

$$\tilde{S}_{I_{n,total}I_{n,total}}(jf) = \left(\frac{4kT}{R_L} + 4kT \Gamma g_m \right) (2\pi f C_{gs} / g_m)^2$$

$$\tilde{S}_{E_{n,total}I_{n,total}}(jf) = \left(\frac{4kT}{R_L} + 4kT \Gamma g_m \right) \left(\frac{1}{g_m} \right) (1 + j2\pi f C_{gs} R_g) (j2\pi f C_{gs})^*$$

Note in particular the cross spectral density.

En-In Model: With All Sources


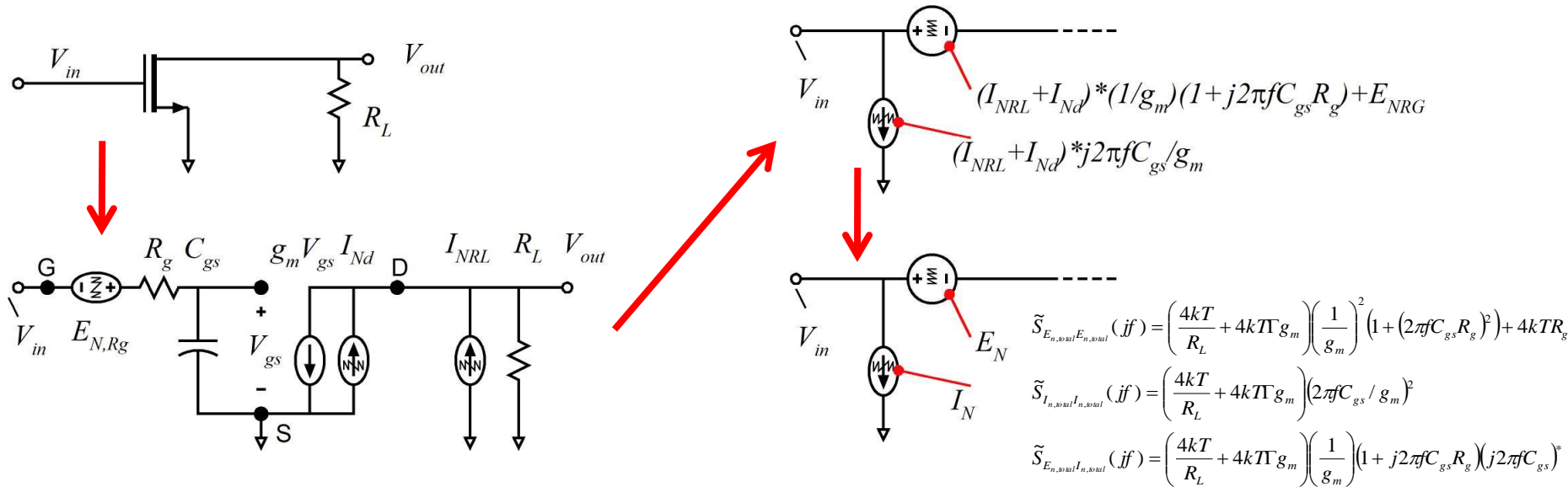


Consider what we have done :

An amplifier, with the generator not specified or present, is represented by a pair of correlated noise generators at its input.

Later, when a generator impedance is specified, \tilde{S}_{E_n} , \tilde{S}_{I_n} , and $\tilde{S}_{E_n I_n}$ can be used to calculate the total input noise (voltage, current, or available power).

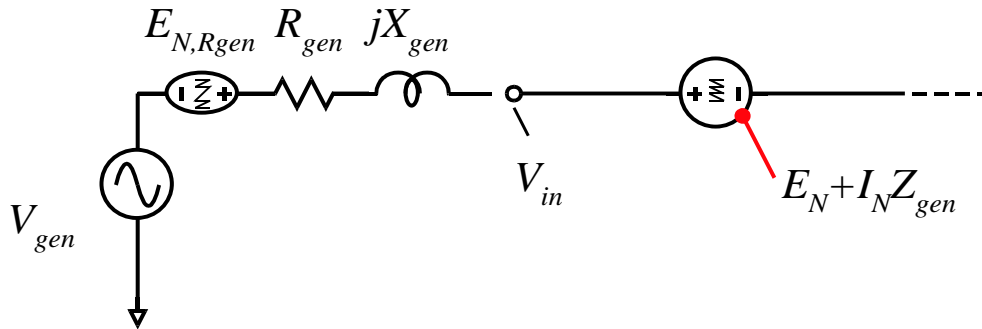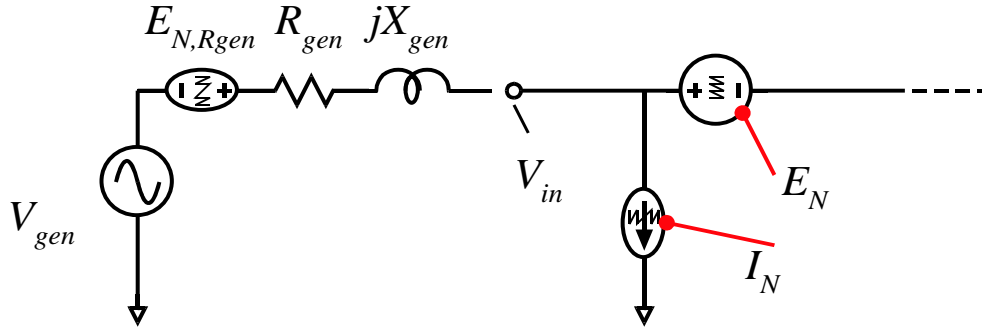Using the En-In Model to Compute total Noise



Given a circuit with specified $\tilde{S}_{E_n, total E_n, total}(jf)$, $\tilde{S}_{I_n, total I_n, total}(jf)$, and $\tilde{S}_{E_n, total I_n, total}(jf)$, and given a specified generator impedance $Z_{gen} = R_{gen} + jX_{gen}$

$$E_{n, total, amplifier} = E_n + I_N Z_g$$

So

$$\begin{aligned} \tilde{S}_{E_n, total, amplifier} &= \tilde{S}_{E_n} + \|Z_g\|^2 \tilde{S}_{I_n} + 2 \operatorname{Re}\{\tilde{S}_{E_n I_n} Z_g^*\} \\ &= \tilde{S}_{E_n} + \|Z_g\|^2 \tilde{S}_{I_n} + 2 \operatorname{Re}\{\tilde{S}_{E_n I_n} (R_{gen} - jX_{gen})\} \end{aligned}$$

Using the En-In Model--Conclusion

If we use the circuit relationship

$$\begin{aligned}\tilde{S}_{E_n, \text{total, amplifier}} &= \tilde{S}_{E_n} + \|Z_g\|^2 \tilde{S}_{I_n} + 2 \operatorname{Re}\{\tilde{S}_{E_n I_n} Z_g^*\} \\ &= \tilde{S}_{E_n} + \|Z_g\|^2 \tilde{S}_{I_n} + 2 \operatorname{Re}\{\tilde{S}_{E_n I_n} (R_{gen} - jX_{gen})\}\end{aligned}$$



and the device relationships

$$\tilde{S}_{E_n, \text{total} E_n, \text{total}}(jf) = \left(\frac{4kT}{R_L} + 4kT\Gamma g_m \right) \left(\frac{1}{g_m} \right)^2 \left(1 + (2\pi f C_{gs} R_g)^2 \right) + 4kT R_g$$

$$\tilde{S}_{I_n, \text{total} I_n, \text{total}}(jf) = \left(\frac{4kT}{R_L} + 4kT\Gamma g_m \right) (2\pi f C_{gs} / g_m)^2$$

$$\tilde{S}_{E_n, \text{total} I_n, \text{total}}(jf) = \left(\frac{4kT}{R_L} + 4kT\Gamma g_m \right) \left(\frac{1}{g_m} \right) \left(1 + j2\pi f C_{gs} R_g \right) (j2\pi f C_{gs})^*$$

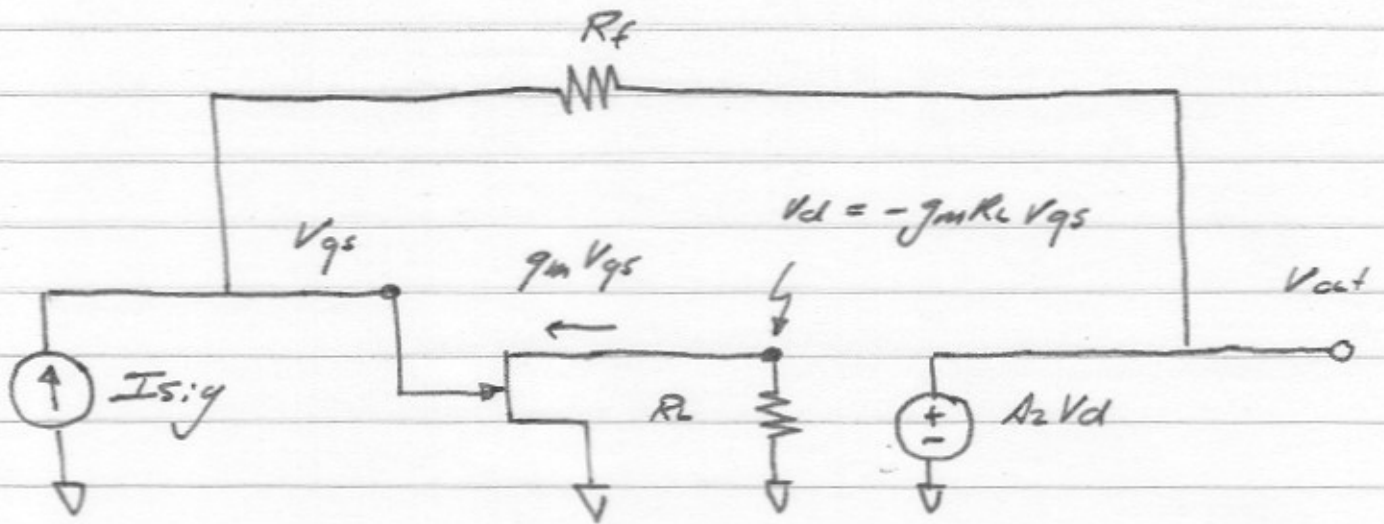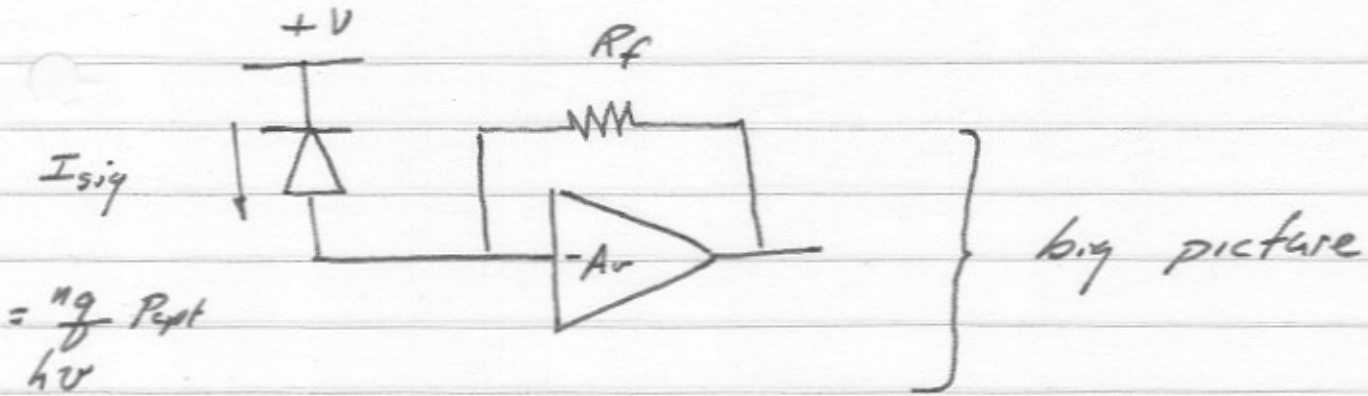
Then by varying Z_g (calculus), we can find the device minimum noise figure and the optimum source impedance which provides this, i.e. we can calculate the Fukui FET noise figure expression.



amplifier 1st stage
detailed model

amplifier 2nd stage
highly idealized.


$$A_v = A_2 \cdot (g_m R_L)$$



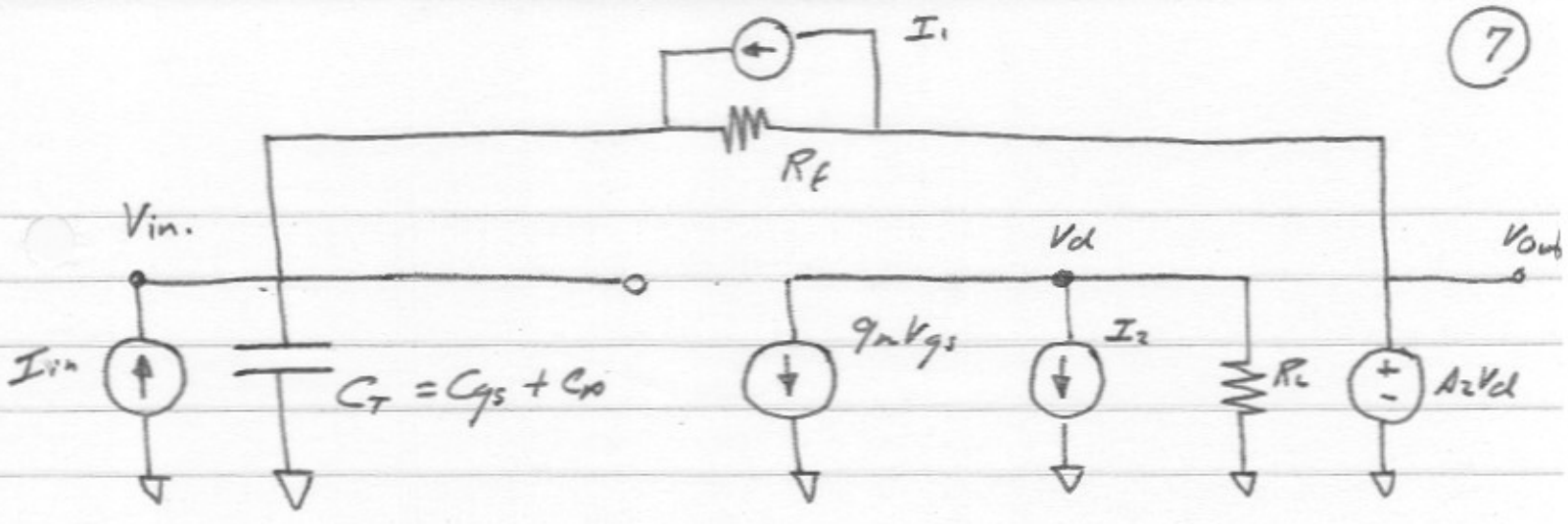


$I_1: S_{I_1 I_1} = 4kT / R_f$

$I_2: S_{I_2 I_2} = 4kT \Gamma g_m + 4kT / R_L$

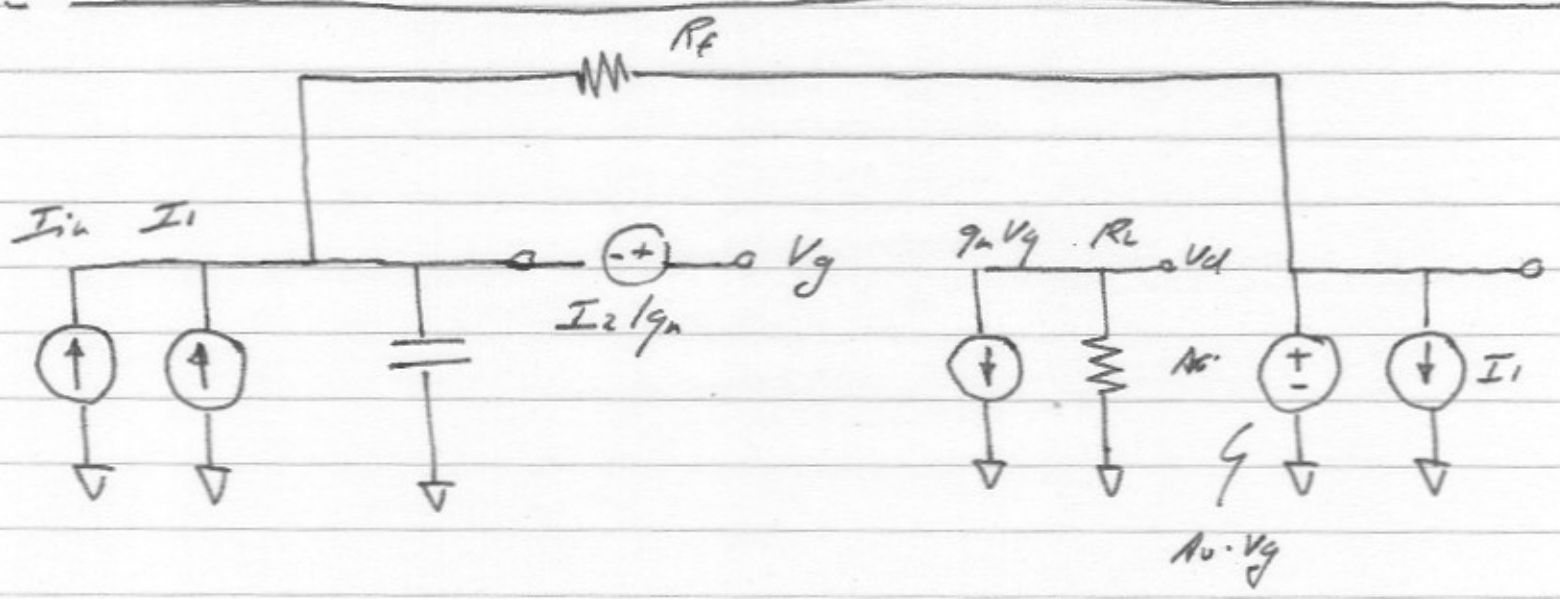apply transformations which do not change V_{in} or V_{d1}



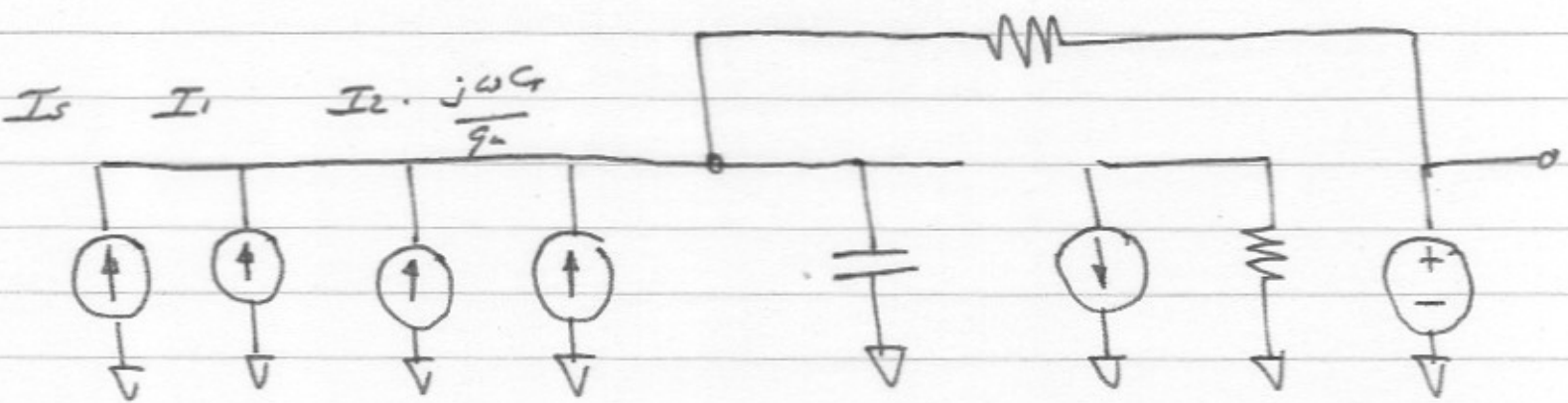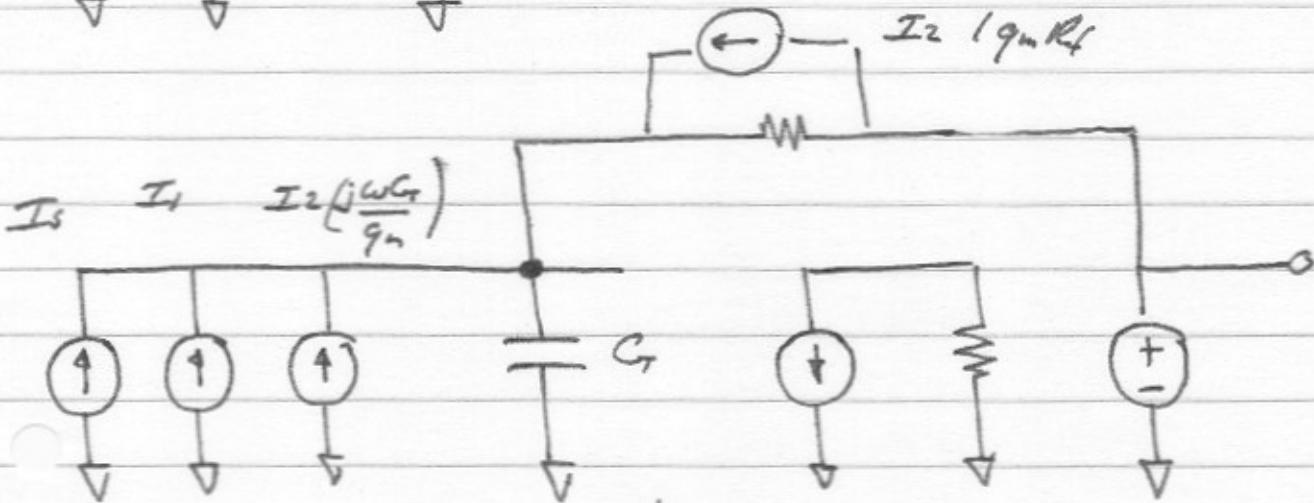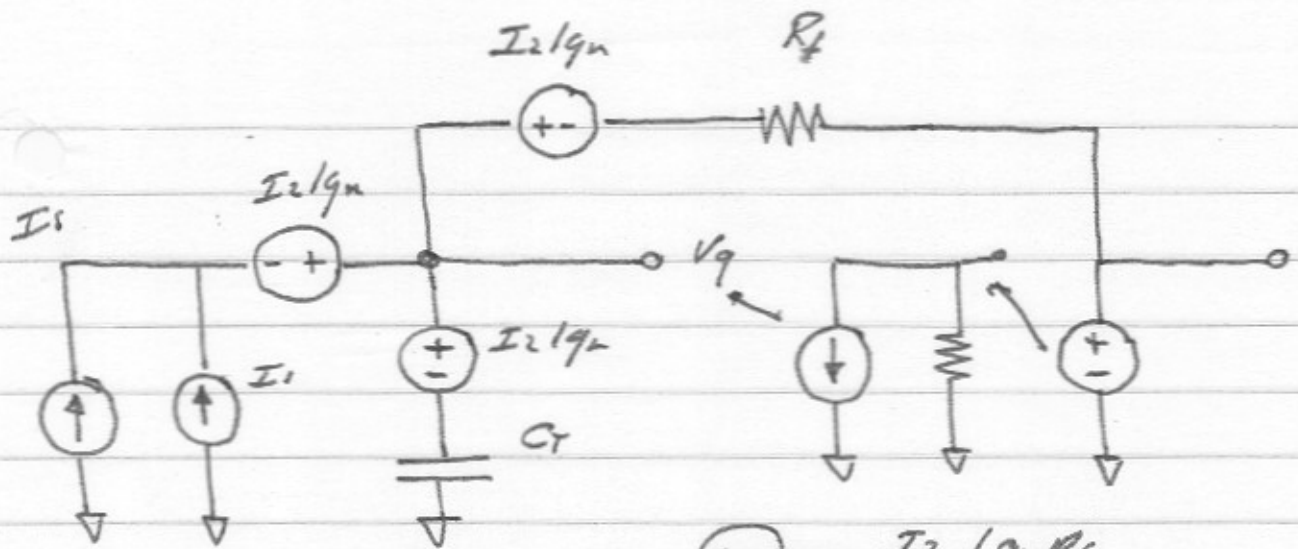

$I_2/g_n R_f$

(9)

So the total input-referred noise-current spectral density is

$$\frac{d \langle I_T I_T^* \rangle}{df} = \frac{4kT}{R_f}$$


$$+ 4kT \Gamma g_m \left[\frac{\omega^2 C_T^2}{g_m^2} + \frac{1}{g_m^2 R_f^2} \right]$$

$$= \frac{4kT}{R_f} + \frac{4kT \Gamma}{g_m} \left[\omega^2 C_T^2 + \frac{1}{R_f^2} \right]$$

[... the method is faster than the lecture showed, as we can move generators on 1 drawing ...]


Cautionary Comment about Biasing

bias fees are noiseless:

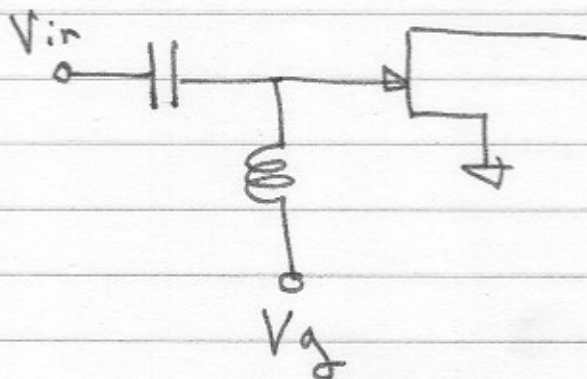


... but their low-frequency cutoff precludes their use in a number of applications.

IF we need a bias current I:

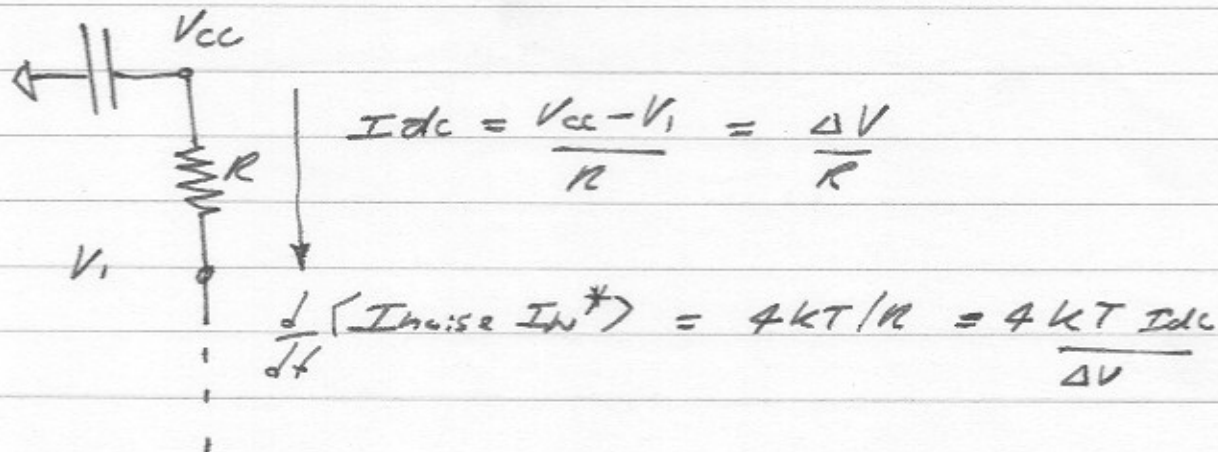

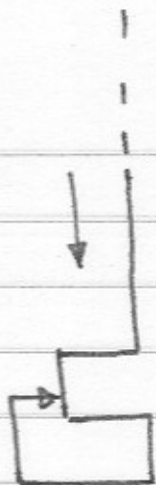Make ΔV big to make the current source noiseless.



Fet Constant-current source

at low frequencies:

$$\frac{d}{df} \langle I_n I_n^* \rangle = 4kT \Pi g_m$$

$$= 4kT \Pi \cdot \left(\frac{g_m}{I_{dc}} \right) \cdot I_{dc}$$


Since $(g_m I_{dc})^{-1} \sim O(V_p)$, ...

$$\frac{d}{df} \langle I_n I_n^* \rangle \sim O \left[4kT \Pi \frac{I_{dc}}{V_p} \right]$$

... this is noisier than the resistor by the


$$\text{ratio} \sim \left(\Delta V \cdot \frac{\Pi}{V_p} \right)$$

ouch !

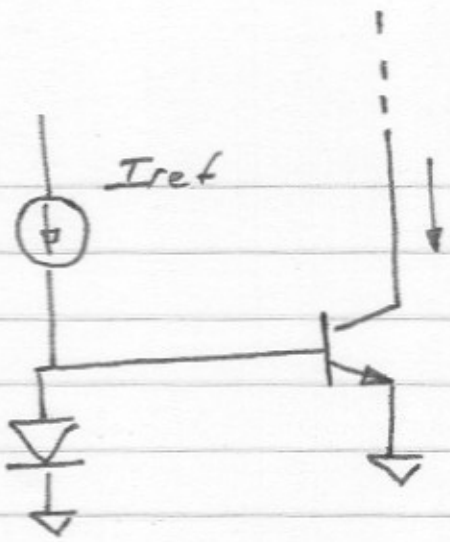

Bipolar current mirror

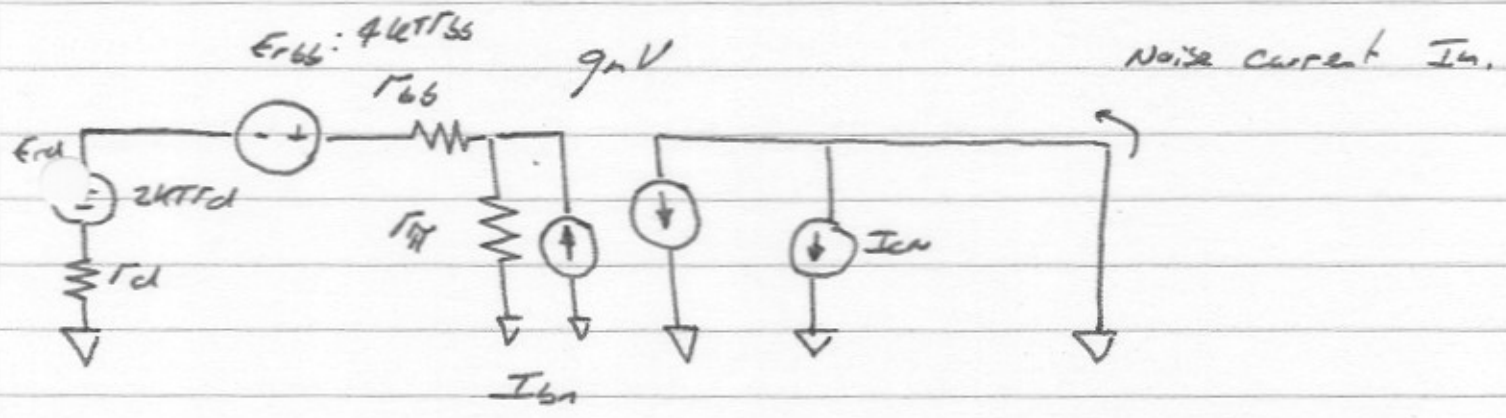I_{ref} noiseless (?) \rightarrow (really $4kT I_{ref} / \Delta V$)



$$I_n = (E_{rd} + E_{rs}) \cdot \frac{r_{\pi}}{r_{\pi} + r_d + r_{bb}} \cdot g_m$$

$$+ (r_{bb} + r_d) \frac{r_{\pi}}{r_{\pi} + r_d + r_{bb}} \cdot I_{bn} \cdot g_m + I_{cn}$$

use $\beta / g_m = r_{\pi}$:

$$S_{I_n I_n}(f) = 4KT \left(r_{bb} + \frac{r_d}{2} \right) \left(\frac{\beta}{r_{bb} + r_d + \beta / g_m} \right)^2$$

$$+ 2g I_b \left(\frac{\beta}{r_{bb} + r_d + \beta / g_m} \right)^2 (r_{bb} + r_d)^2$$

$$+ 2g I_{dc}$$


This gets complicated. The last term alone ($2g I_c$)

is bigger than resistor-current-source noise by

the ratio $\left[\Delta V / 2(KT/g) \right]$


- oach!

Simple Common-source amplifier:

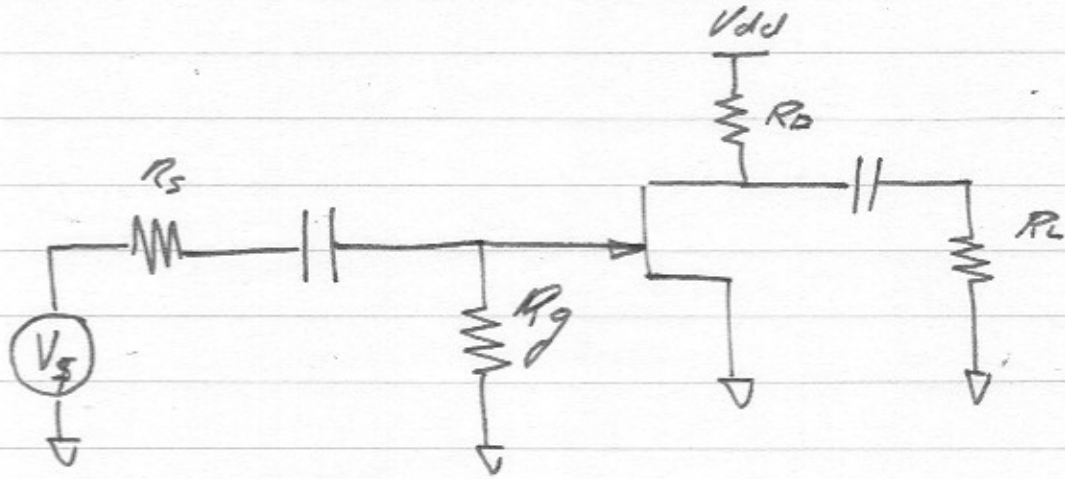


Since this is just an example, pick a simplified

FET Model

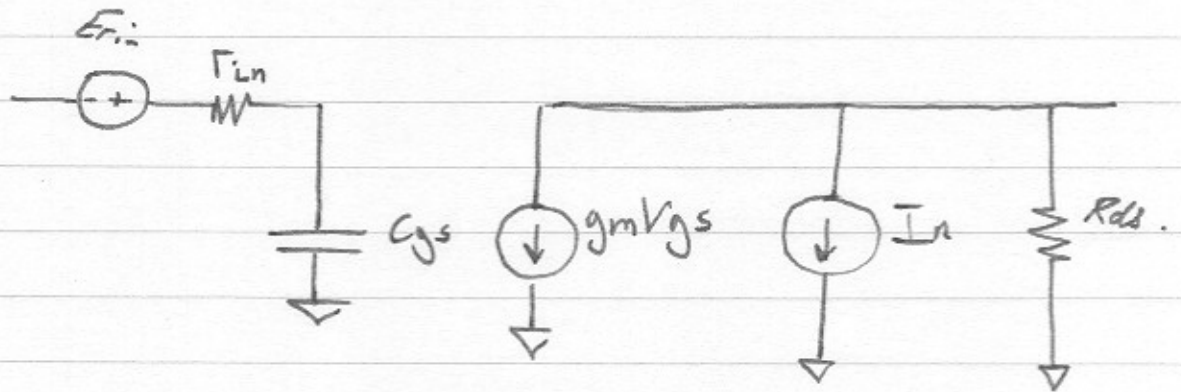
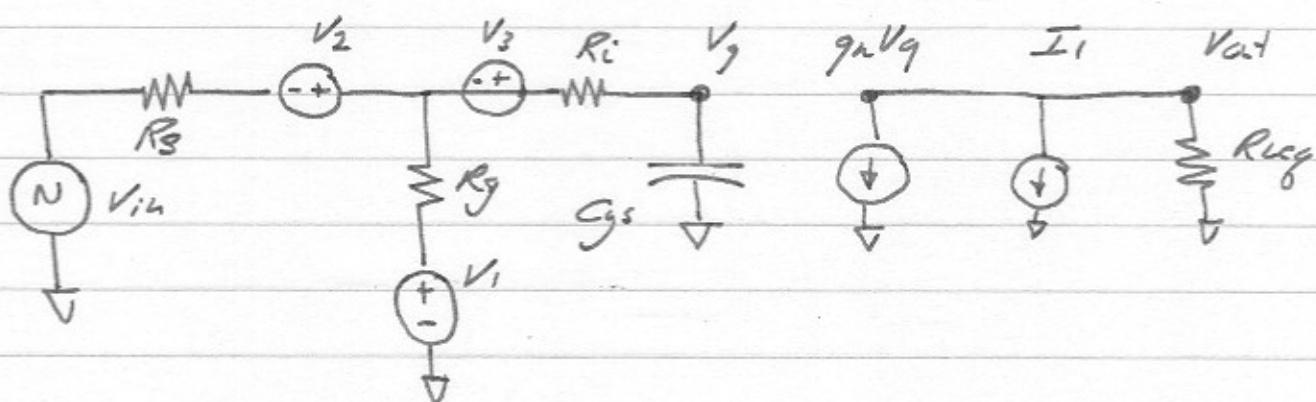
$$\left. \begin{aligned} E_{in}: S &= 4kT\Gamma_{Ln} \\ I_n: S &= 4kT\Gamma_{gm} \end{aligned} \right\} \text{zero cross-spectral density.}$$



$$V_1: 4kTR_g$$

$$V_2: 4kTR_S$$

$$V_3: 4kTR_i$$

$$I_1: 4kT[7g_m + 4kT(1/R_L + 1/R_i)] : R_{eq}^{-1} = R_{ds}^{-1} + R_L^{-1} + R_i^{-1}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_g}{R_g + R_S} \frac{1}{1 + j\omega C_{gs}(R_i + R_S \parallel R_g)} \cdot (-g_m R_{eq})$$


Most efficient to work this by a mixture of methods.

* V_2 already at input: leave it there...


$$\frac{V_{out}}{I_1} = R_{eq}$$

So, we can Model I_1 by an input voltage of


$$V_{eq|I_1} = \frac{-I_1}{g_m} \cdot \frac{R_g + R_s}{R_g} (1 + j\omega C_{gs}(R_i + R_s || R_g))$$

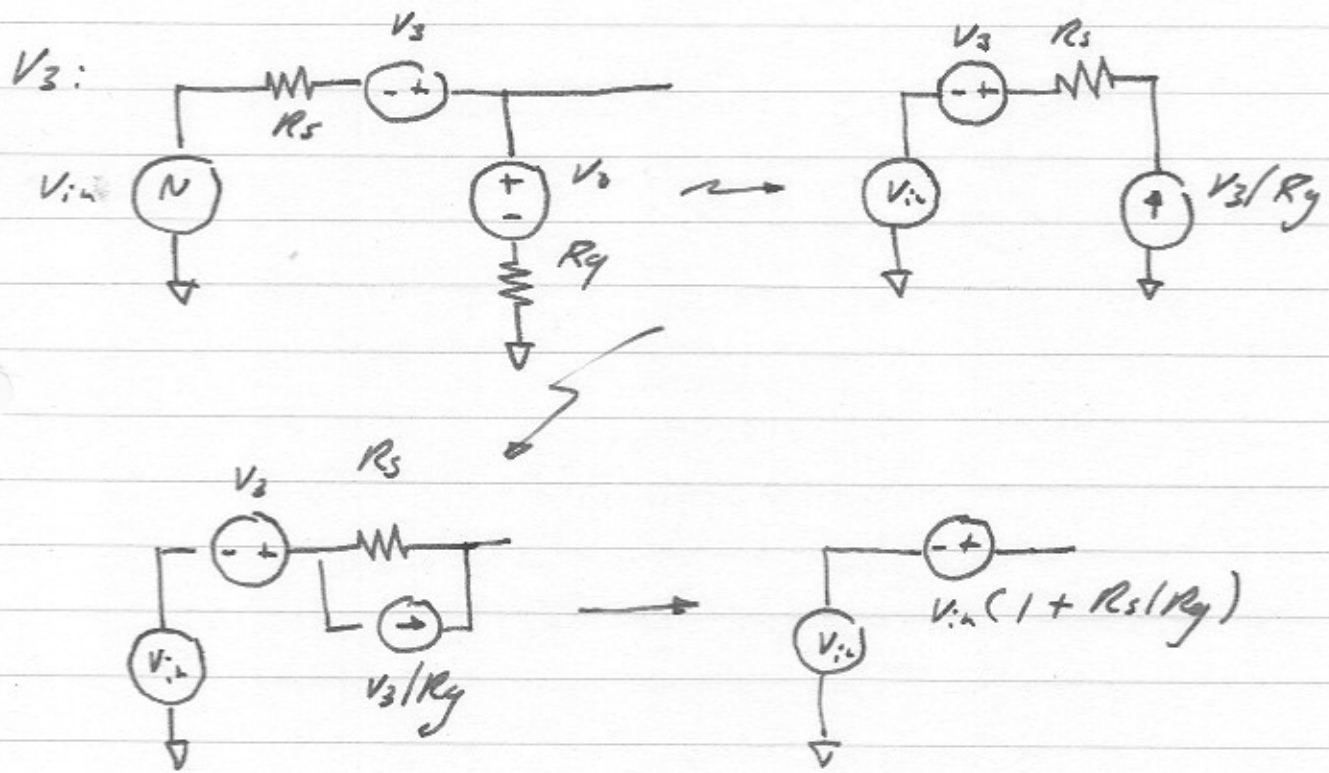

... easier to do than draw ...

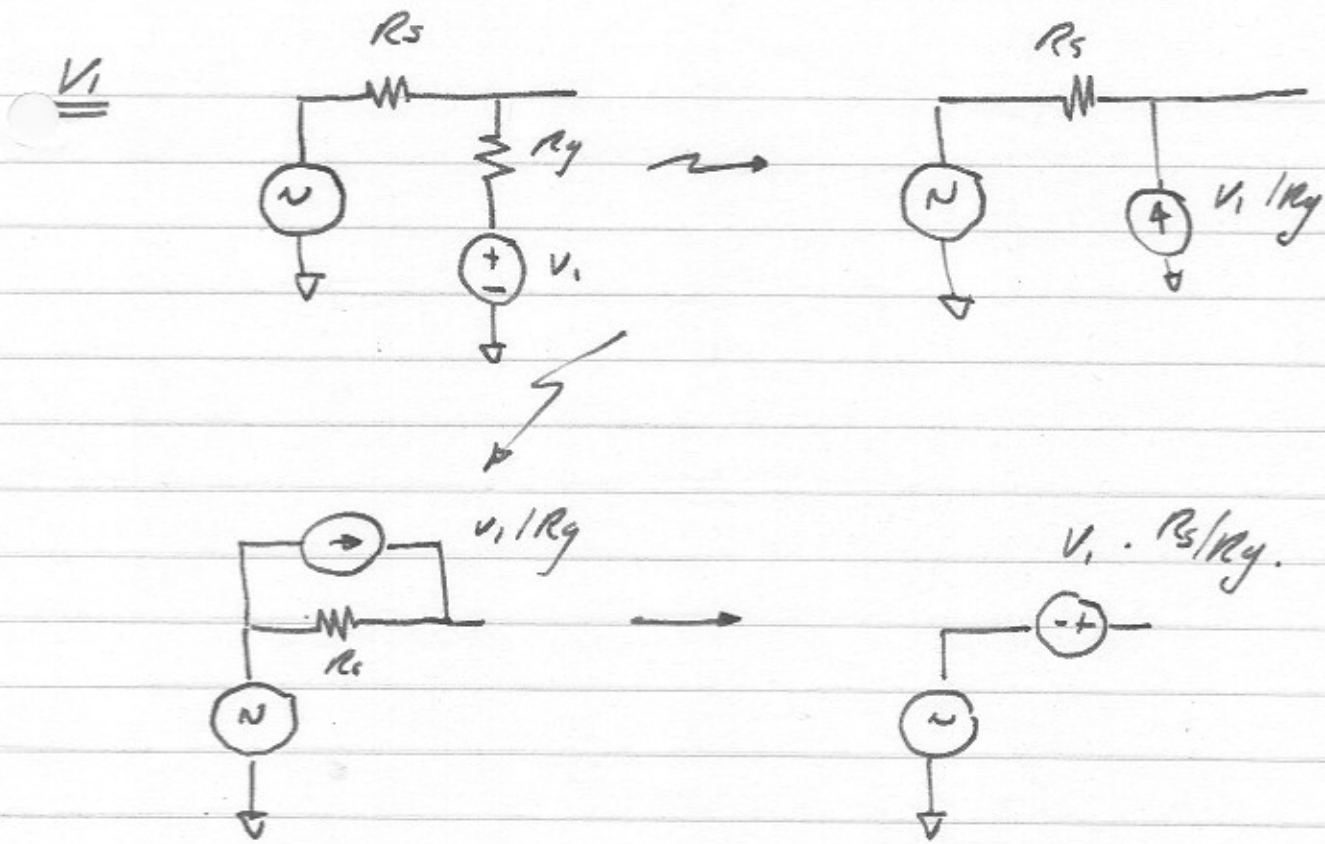

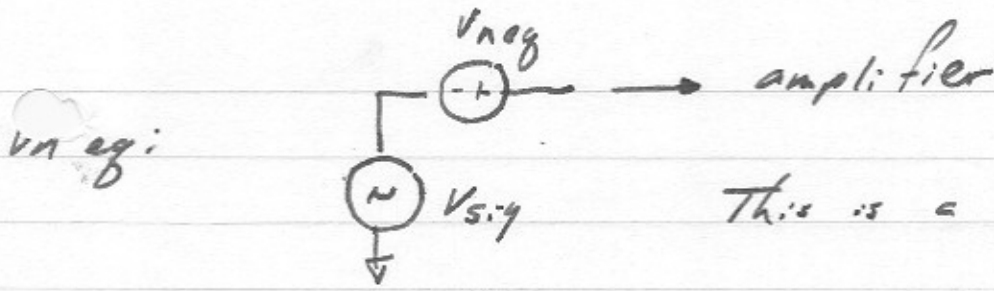So we can now gather terms & write the input-referred noise voltage ...



This is a total noise voltage model

$$S_{v_{n,eq}}(f) = 4kT \Gamma g_m \cdot \left[\frac{R_g + R_s}{g_m R_g} \right]^2 \left[1 + \omega^2 C_{gs}^2 \cdot (R_i + R_s \parallel R_g) \right]^2$$

$$+ 4kT R_s$$

$$+ 4kT R_i \left[1 + R_s \parallel R_g \right]^2$$

$$+ 4kT R_g \cdot \left[R_s \parallel R_g \right]^2$$

you may simplify further...

input
referred
total noise voltage
spectral
density, v^2/Hz

