

- Notes Set 15: FET minimum noise figure

- proof (and disproof...) of Fukui's FET noise relationships
- impact of DC power constraints on low noise FET radio receivers

ECE — Notes set 14


Consisting of:

- 1) Derivation of the FET Minimum noise figure of a FET, together with some corrections.
- 2) Comments regarding minimum noise figures obtainable for receivers operating with a DC power constraint.

How to build a CMOS LNA:

No on-wafer inductors:


chip boundary.

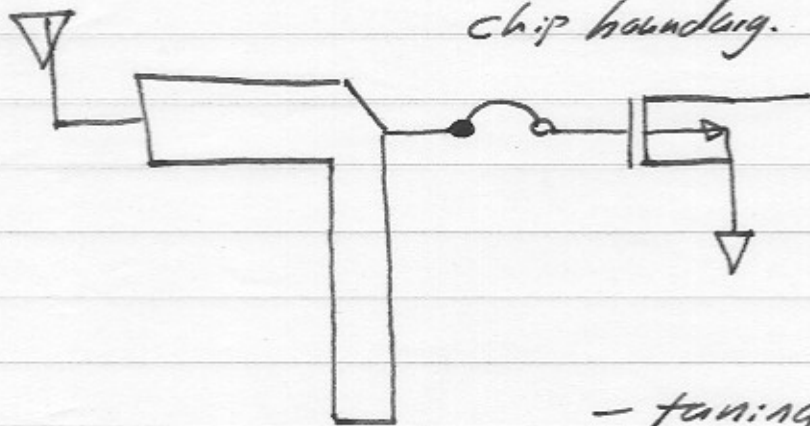

- tuning network for

noise match on hybrid-

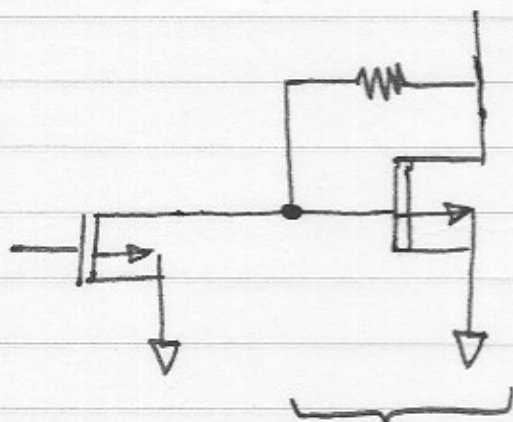what does the rest of the circuit look like:-



antuned resistive - feedback stages. High circuit density.

(2)

What are the other issues?

Minimum noise figure with very low d.c. power.

* $Z_{opt} \propto (\text{device periphery})^{-1}$

[So optimum source impedance varies inversely with d.c. power consumption.


High ratios of impedance transformation are desirable... what do we do about this?

- Off-water impedance matching...

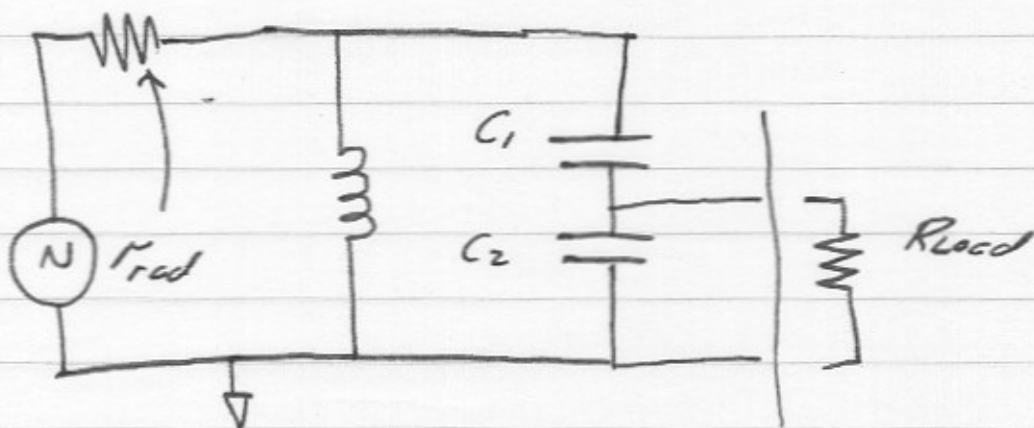(3)

Some thoughts on impedance matching:


one way to transform impedances up, so that a low Z_{opt} at the transistor terminals can be matched to a much-higher antenna impedance:




in the limit $\omega C_2 \gg 1/R_{load}$, impedances are scaled by the square of the voltage division ratio.

unfortunately, we wish to scale a high R_{opt} @ the transistor to a much lower generator impedance...

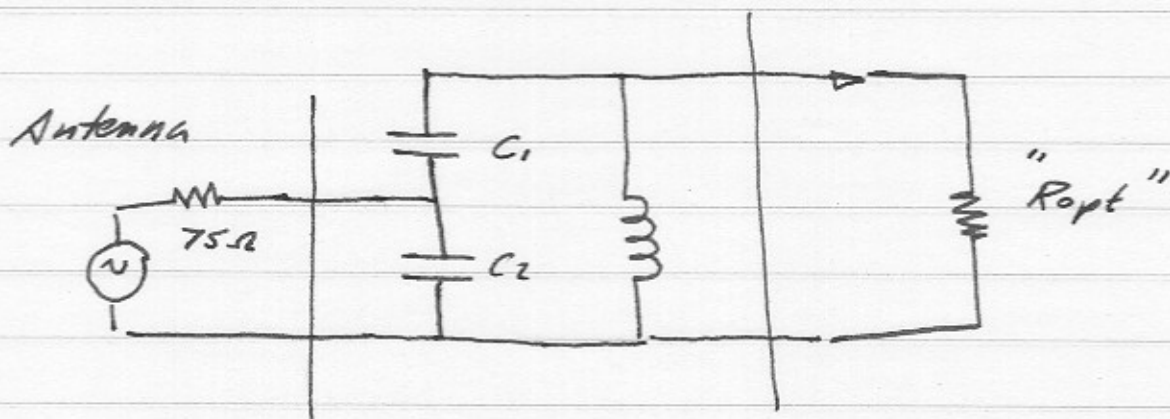we can, of course, do this transformation also:



or the second implementation..

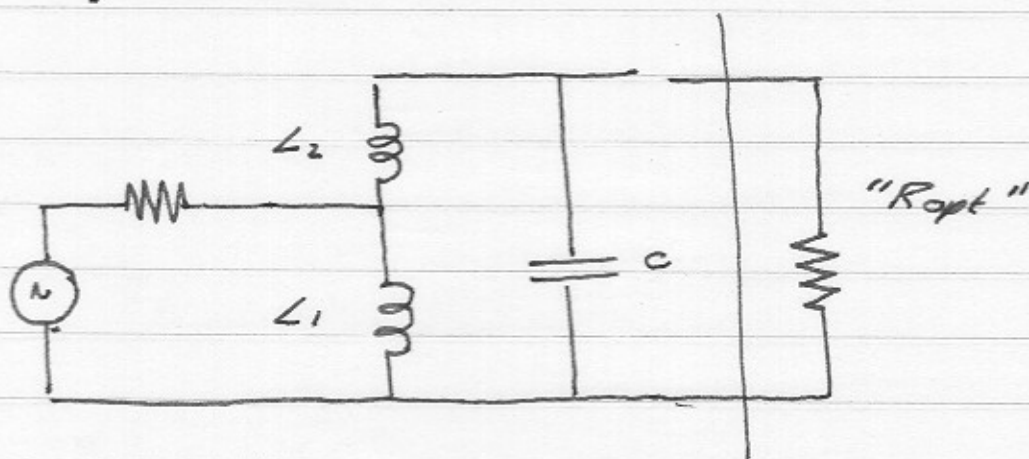

this looks attractive in the sense that only 1 connection need be made to the device.

L_1 & L_2 become inductive microstrip elements on the hybrid, while C is ~~an~~ also preferably off-wafer.

red questions would be:

- * what values of L_1 & L_2 are required?
- * how big are the resulting microstrip lines?
- * what Q will the lines have, & how big an effect will this have on f_{min} .
- * How does the above limit the minimum feasible device size, hence power consumption?

Tasks:

- develop estimated model of the low noise SiGe MOSFET.
- do an elementary ccd exercise!


6

Note that the radio receiver must have considerable pre-selection before mixing : if it is to operate ~~sp~~ spurious-free.


It is particularly convenient for the input noise-matching network to perform this function...

Design approaches using on-water inductors:


Propose to look at this:

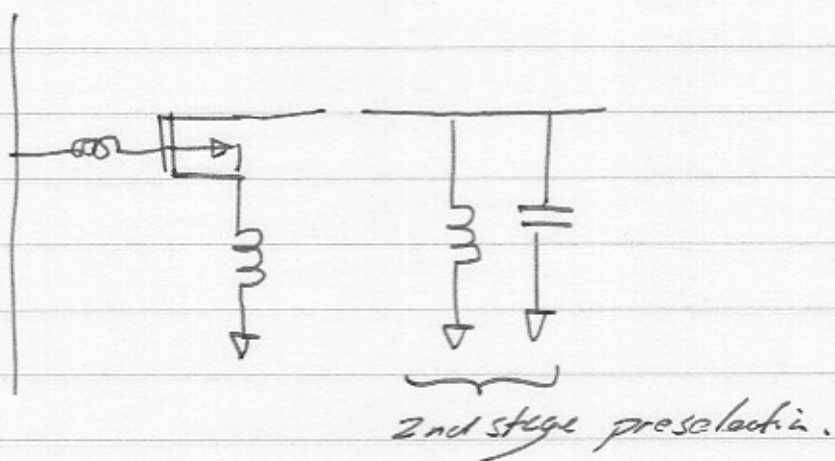

and also propose to look at this:

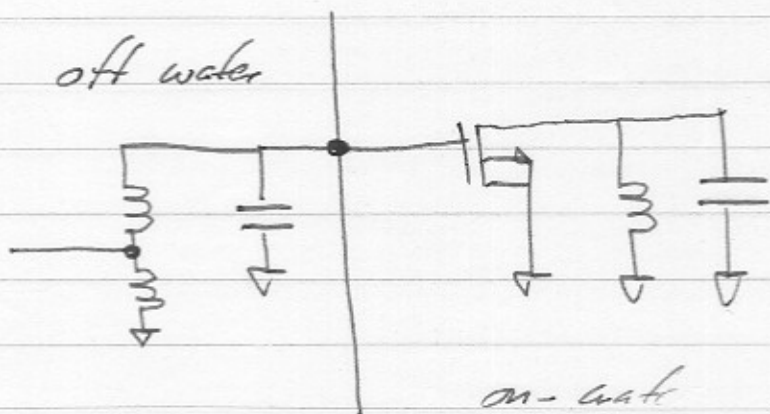

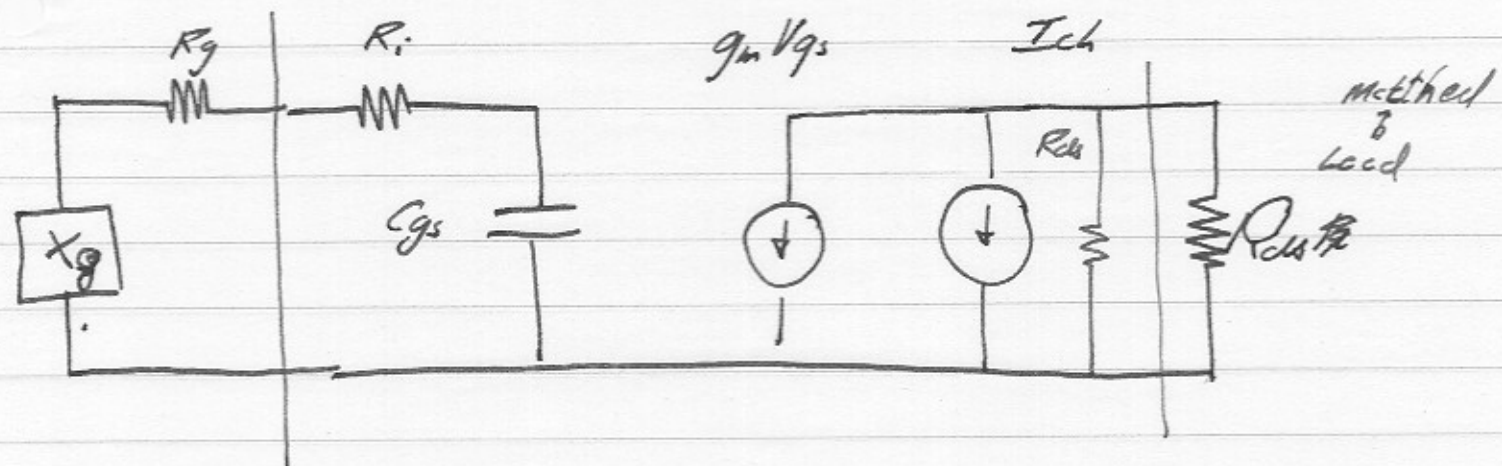and comment that feasibility of approach depends on inductor Q. will use on-water over on input if F_{min} allows it. Not if otherwise.



$$S_{out} = 4KT R_g \cdot \left[\frac{1}{R_g + R_i + X_{gs} + X_g} \cdot \frac{g_m}{\omega C_{gs}} \right]^2 \cdot \frac{R_{ds}}{2}$$

$$N_{out} = 4KT (R_g + R_i) \left[\frac{1}{R_g + R_i + jX_{gs} + jX_g} \cdot \frac{g_m}{\omega C_{gs}} \right]^2 R_{ds}/2 + 4KT \Gamma g_m R_{ds}/2$$

$$F = 1 + 4KT \left(\frac{R_i}{R_g} \right) + \frac{\Gamma g_m}{R_g} \left(R_i + R_g + jX_g + \frac{1}{j\omega C_{gs}} \right)^2 \frac{\omega^2}{\omega_T^2}$$

exact expression for noise figure with

$$Z_{gen} = R_g + jX_g$$

input
noise
signal

$$F = 1 + \frac{R_i}{R_g} + \left(\frac{\omega}{\omega_H}\right)^2 \frac{1}{R_g} \left\| R_i + R_g + jX_g + \frac{1}{j\omega C_{gs}} \right\|^2$$

So what is the minimum noise figure?

Clearly, we pick $jX_g = \frac{-1}{j\omega C_{gs}}$

lets call this F_x for F with the right value of source reactance...

$$F_x = 1 + \frac{R_i}{R_g} + \left(\frac{\omega}{\omega_T}\right)^2 \frac{\Gamma g_m}{R_g} (R_i + R_g)^2$$

now, what value of R_g minimizes F_x ?

$$F_x = 1 + \frac{R_i}{R_g} + \left(\frac{\omega}{\omega_T}\right)^2 \frac{\Gamma g_m R_i^2}{R_g} + \left(\frac{\omega}{\omega_T}\right)^2 \Gamma g_m R_g$$

$$+ \left(\frac{\omega}{\omega_T}\right)^2 \Gamma g_m (2R_i)$$

$$F_x = \left[1 + \left(\frac{\omega}{\omega_T}\right)^2 \Gamma g_m 2R_i \right] + \left[R_i + \left(\frac{\omega}{\omega_T}\right)^2 \Gamma g_m R_i^2 \right] \frac{1}{R_g}$$

$$+ \left[\left(\frac{\omega}{\omega_T}\right)^2 \Gamma g_m \right] R_g$$

ahc, we can do calculus by inspection!

F_x minimized when the last 2 terms are equal!

hence:

$$\left[R_i + \left(\frac{\omega}{\omega_T} \right)^2 \Delta g_m R_i^2 \right] \cdot \frac{1}{R_g} = \left[\left(\frac{\omega}{\omega_T} \right)^2 \Delta g_m \right] R_g$$

$$R_g^2 = \frac{R_i + \left(\frac{\omega}{\omega_T} \right)^2 \Delta g_m R_i^2}{\left(\frac{\omega}{\omega_T} \right)^2 \Delta g_m}$$

$$= \frac{R_i}{\Delta g_m} \left(\frac{\omega_T}{\omega} \right)^2 + R_i^2$$

$$R_g = \sqrt{R_i^2 + \frac{R_i}{\Delta g_m} \left(\frac{\omega_T}{\omega} \right)^2}$$

So here is the whole answer:


$$F_{min} = 1 + \left(\frac{\omega}{\omega_T}\right)^2 \square g_m 2r_i$$

$$+ 2 \square g_m \left(\frac{\omega}{\omega_T}\right)^2 \sqrt{R_i^2 + \frac{R_i}{\square g_m} \left(\frac{\omega_T}{\omega}\right)^2}$$

$$jX_{opt} = \frac{1}{j\omega C_{gs}}$$

$$R_{opt} = \sqrt{R_i^2 + \frac{R_i}{\square g_m} \left(\frac{\omega_T}{\omega}\right)^2}$$

Now lets look at this:

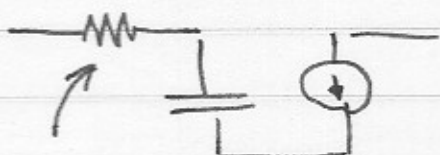

R_i is modelling gate resistance, source & channel resistance.

$$R_i \sim 1/g_m, \quad \Gamma = \begin{cases} 1.5 & \text{Crosst Fet, strong IV section} \\ 1 & \\ 0.75 & \text{grad. cl.} \end{cases}$$

use $\Gamma=1$

$$F_{min} \sim 1 + 2 \left(\frac{\omega}{\omega_T} \right)^2 + 2 \left(\frac{\omega}{\omega_T} \right)^2 \sqrt{1 + \left(\frac{\omega_T}{\omega} \right)^2}$$

$$\downarrow X_{cgt} \sim \frac{1}{j\omega C_{gs}}, \quad R_{opt} \sim \frac{1}{g_m} \sqrt{1 + \left(\frac{\omega_T}{\omega} \right)^2}$$

Now lets look at limiting behaviour:

$$\boxed{\omega \ll \omega_T} : \rightarrow \sqrt{1 + \left(\frac{\omega_T}{\omega}\right)^2} \approx \frac{\omega_T}{\omega}$$



$$F_{min} \sim 1 + 2 \left(\frac{\omega}{\omega_T}\right) + 2 \left(\frac{\omega}{\omega_T}\right)^2$$

$$jX_{opt} \sim \frac{1}{j\omega C_{gs}}$$

$$R_{opt} \sim \frac{1}{g_m} \frac{\omega_T}{\omega}$$

$$\omega \gg \omega_T$$

$$F_{min} \sim 1 + 4 \left(\frac{\omega}{\omega_T}\right)^2$$

$$jX_{opt} \sim \frac{1}{j\omega C_{gs}}$$

$$R_{opt} \sim \frac{1}{g_m}$$

in reality, we are probably not interested in $\omega \gg \omega_T$, so lets focus on the first approximation.

\swarrow 2.5 if $\Gamma = 1.5$ \searrow 3 if $\Gamma = 1.5$

$$F_{min} \sim 1 + 2 \left(\frac{\omega}{\omega_T} \right) + 2 \left(\frac{\omega}{\omega_T} \right)^2$$

$$\downarrow X_{opt} \sim 1 / j\omega C_{gs}$$

$$R_{opt} \sim (1/g_m) (\omega_T / \omega)$$

($R_i = 1/g_m, \Gamma = 1$)

org putting back the R_i 's:

$$F_{min} \sim 1 + 2 \sqrt{\Gamma R_i g_m} \left(\frac{\omega}{\omega_T} \right) + 2 (\Gamma R_i g_m) \left(\frac{\omega}{\omega_T} \right)^2$$

$$\downarrow X_{opt} \sim 1 / j\omega C_{gs}$$

$$R_{opt} \sim \sqrt{\frac{R_i}{\Gamma g_m}} \left(\frac{\omega_T}{\omega} \right)$$

lets do a sanity check:

InGaAs hemt with $f_T \approx 160 \text{ GHz}$.

f_{sig}	F	f, dB
10	1.133	<u>0.5 dB</u>
60	2.03	3.1 dB

10 GHz noise figure, Si-Ge:

30 GHz f_T : $F_{\text{min}} \approx 2.2 \text{ dB}$
 $X_{\text{opt}} \approx (1/9\mu) \cdot 3$
 $R_{\text{opt}} \approx (1/9\mu) \cdot 3$

50 GHz f_T : $F_{\text{min}} \approx 1.5 \text{ dB}$.
 $X_{\text{opt}} \approx 5/9\mu$
 $R_{\text{opt}} \approx 5/9\mu$

Fickai gives

$$F_{min} \approx 1 + K_1 \neq C_{gs} \sqrt{\frac{R_g + R_s}{g_m}}$$

$$= 1 + \frac{K_1}{2\pi} \frac{\omega C_{gs}}{g_m} \sqrt{(R_g + R_s) g_m}$$

$$= 1 + \left(\frac{K_1}{2\pi}\right) \frac{\omega}{\omega_T} \sqrt{(R_g + R_s) g_m}$$

where $K_1 \approx 0.16$

$K_{int} = \underline{0.03}$

my expression is

$$F_{min} = 1 + 2\sqrt{\pi} \sqrt{(R_i + R_g + R_s) g_m} (\omega/\omega_T)$$

which correlates only if $2\sqrt{\pi} \approx 0.03$

this is confusing! - check units!

IEEE TED J-ly 1979

F444i: $F_0 = 1 + 2\pi K_f f C_{gs} \sqrt{\frac{R_g + R_s}{g_m}} \cdot 10^{-3}$

$K_f \approx 2.5$

f in GHz, g_m in 1/ohm

C_{gs} in pF.

so going to MKS units:

$F_0 = 1 + 2\pi K_f \frac{f}{10^9} \cdot \frac{C_{gs}}{10^{-12}} \sqrt{\frac{R_g + R_s}{g_m}} \cdot 10^{-3}$

$= 1 + 2\pi K_f f C_{gs} \sqrt{(R_g + R_s) / g_m}$

$F_0 = 1 + K_f \left(\frac{\omega}{\omega_T} \right) \sqrt{(R_g + R_s) \cdot g_m}$
 $K_f \approx 2.5$

my derivation is

$F_0 = 1 + 2\sqrt{I_T} \sqrt{(R_i + R_g + R_s) g_m} (\omega / \omega_T)$

note first that $\sqrt{(R_i + R_g + R_s) g_m}$

$$\approx \sqrt{(1/g_m + R_g + R_s) g_m} = \sqrt{1 + (R_g + R_s) g_m}$$

so there is a slight inconsistency in the radicals in the 2 equations.

Beyond this small correction

Fukui: $K_F = \underline{2.5}$

Rodwell $K_F = 2\sqrt{\Gamma}$

$$\Gamma \sim 0.75 - 1.5$$

$$= \underline{1.7 \text{ to } 2.4}$$

given the slightly bigger radical in my expression, the correlation is excellent!

I will get good fits if I use $\Gamma \sim 1.5$.

Fuku: says:

$$R_{opt} \sim K_3 \left[\frac{1}{49a} + R_g + R_s \right]$$

$$X_{opt} \sim K_4 / f_{cs} = 0.16 / f_{cs} = 1 / \omega_{cs}$$

note that his expression for X_{opt} is exactly
 the same as mine, but that the R_{opt}
 doesn't have the same frequency dependence at all
 But note that Fuku's expression is empirical.

Brick Hughes' expressions are given as:

IEE Trans MTT 20 Feb '93 page 190
 " " " " 24 '92 page 1821.

His agree with mine

Transistor				
	gm/I ratio	2.00E+00	1/Volts	equals 1/2/(Vgs-Vt)
	FET gm	6.67E-03	1/Ω	
	FET ft	5.00E+10	Hz	
	Gamma	1.50E+00		
	Fet Ri	1.50E+02	Ω	
	Fet Cgs	2.12E-14	F	
Signal				
	Frequency	1.00E+10	Hz	
Generator				
	Rg, optimum	7.50E+02	Ω	
	Xg, optimum	7.50E+02	Ω	
	Rg	2.00E+02	Ω	
	Xg	2.00E+02	Ω	
Noise Performance				
	Fmin	1.49E+00	linear	Very simplified Expression
	Fmin	1.73E+00	dB	Very simplified Expression
	Fmin	1.61E+00	linear	Slightly simplified Expression
	Fmin	2.07E+00	dB	Slightly simplified Expression
	F	2.60E+00	linear	Exact expression
	F	4.15E+00	dB	Exact expression
DC Power Consumption				
	Vcc	1.50E+00	Volts	
	Id	3.33E-03	amps	
	Pdc	5.00E-03	Watts	
Frequency				
	Frequency	10	GHz	
Fet Ft				
	Fet Ft	50	GHz	
Rg				
	Rg	200	Ω	
Xg				
	Xg	200	Ω	
DC Power				
	DC Power	5.0	mW	
	Fmin	2.1	dB	2.068
	F	4.1	dB	4.150

To repeat

$$F_{min} \approx 1 + 2\sqrt{\Gamma} \sqrt{g_m(R_i + R_s + R_g)} \cdot \frac{\omega}{\omega_T}$$

$$\sqrt{X_{opt}} \approx \frac{1}{j\omega C_{gs}}$$

$$R_{opt} = \sqrt{\frac{R_i}{\Gamma g_m}} \left(\frac{\omega_T}{\omega} \right)$$

Approximate

$$= \sqrt{\frac{R_i g_m}{\Gamma}} \frac{1}{\omega C_{gs}}$$

Less Approximate.

$$F_{min} = 1 + \left(\frac{\omega}{\omega_T} \right)^2 2\sqrt{\Gamma} g_m \sqrt{\frac{R_i}{\Gamma g_m} \left(\frac{\omega_T}{\omega} \right)^2 + R_i^2} + \left(\frac{\omega}{\omega_T} \right)^2 \cdot \Gamma g_m \cdot 2R_i$$

$$\sqrt{X_{opt}} = \frac{1}{j\omega C_{gs}}$$

~~R_{opt}~~

$$R_{opt} = \sqrt{R_i + \frac{R_i}{\Gamma g_m} \left(\frac{\omega_T}{\omega} \right)^2}$$

Note that:

- no gate leakage shot noise has been modelled.
- Quadratic term in (ω/ω_T) is real & observed.
- The optimum generator impedance, for $(\omega \ll \omega_T)$, has equal resistive & inductive components, both of which have the same magnitude as the capacitive reactance of C_{gs} .
- This means that for $\omega \gg \omega_T$ $\omega \ll \omega_T$ the generator impedance becomes very big.

The full expression for noise figure is:

$$F = 1 + \frac{R_i + R_s + R_g}{R_{gen}}$$

$$+ \left(\frac{\omega}{\omega_T} \right)^2 \cdot \frac{I^2 q_m}{R_{gen}} \cdot \left[(R_i + R_s + R_g + R_{gen})^2 + \left(X_{gen} - \frac{1}{\omega C_{gs}} \right)^2 \right]$$

... This will vary as $\sim \frac{1}{R_{gen}}$ for $R_{gen} \ll R_{opt}$.

Lets consider a specific example:

deep submicron MOSFET as $\approx 1-10$ GHz

low-power radio receiver. what noise figure can we obtain?

- Block diagrams of the receiver & preamplifier are shown on the next pages.


The Problem:


* Difficult to transform to high impedances at microwave frequencies; $\|Z_{eq}\| < 300 \Omega$.

* With a fixed device g_m / I_{dc} ratio, a dc power constraint becomes a constraint on g_m .


* Antenna & device are then no longer noise-matched.

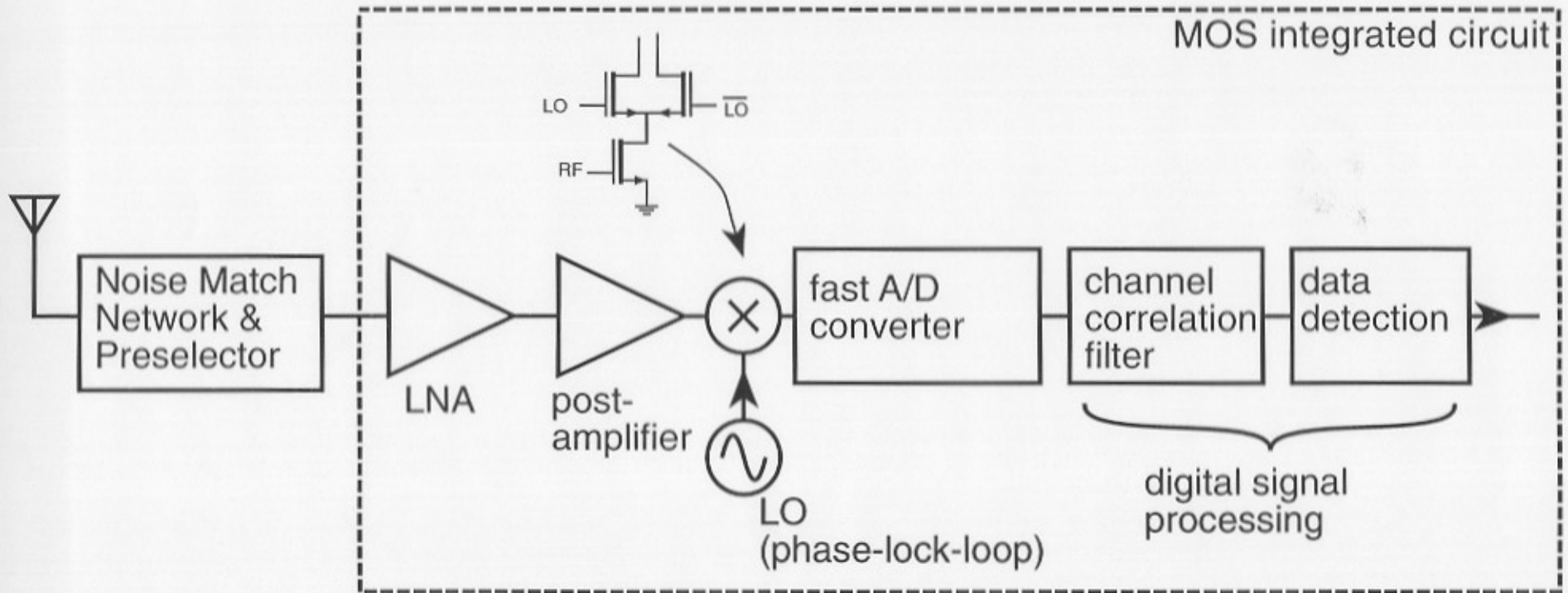Emerging IC topology for monolithic mobile radio communications receivers (Berkeley, UCLA)



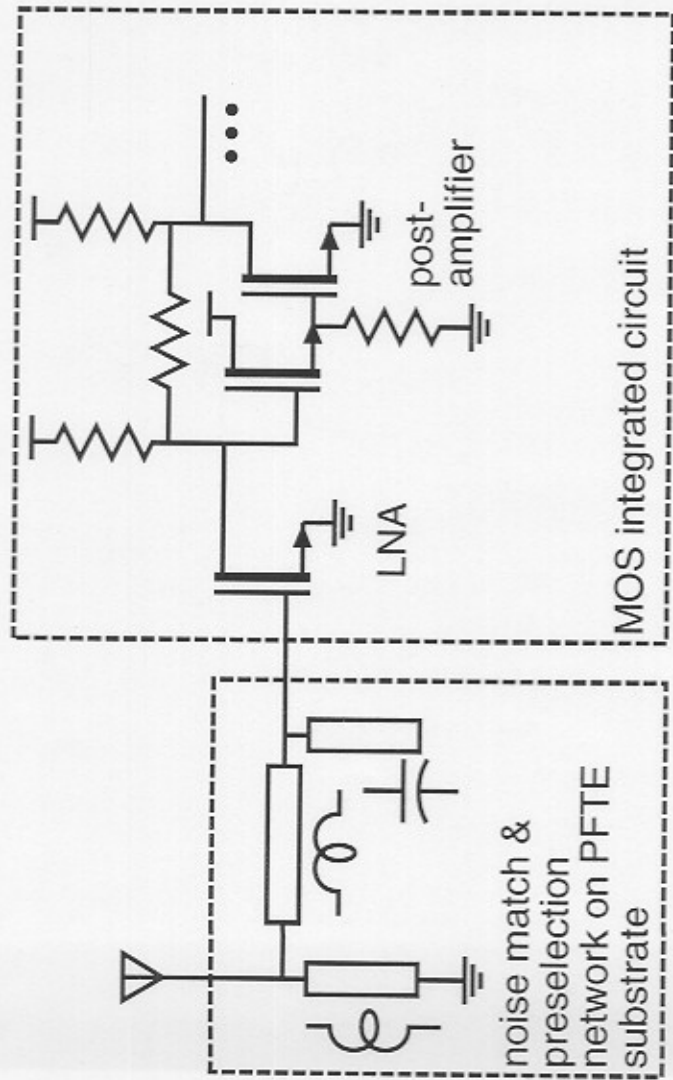

a)

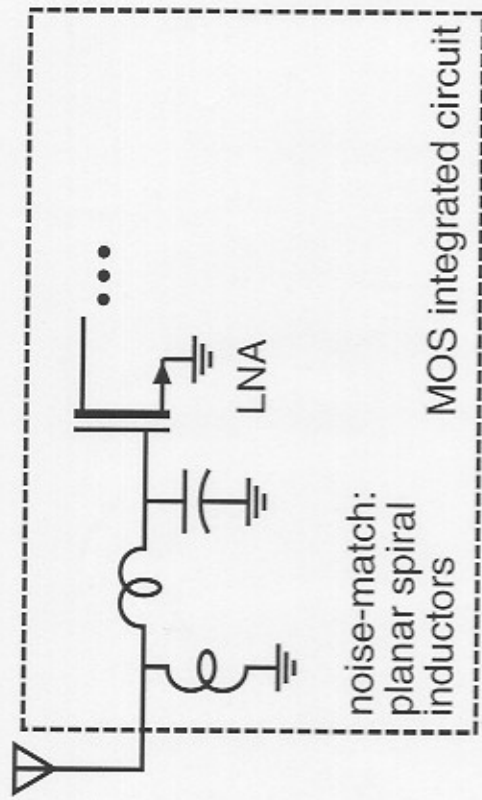

b)

Assumptions:

$$\frac{g_m}{I} = \frac{1}{2(V_{gs} - V_t)}$$

square law device.

$$g_m \cdot (R_s + R_g + R_s) = 1, \quad \Gamma = 1.5$$

Noise Figure vs. DC Power Consumption

