

ECE ECE145C (undergrad) and ECE218c (graduate)

Mid-Term Exam. Nov 7, 2002

Do not open exam until instructed to.


Open book

Use any and all reasonable approximations (5% accuracy is fine.), ***AFTER STATING THEM.***

Name: Solution.

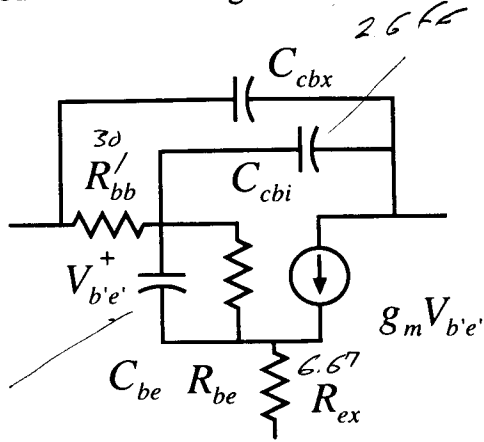Problem 1, xx points


You will be working on the circuit below:




$17 \text{ fF} + g_m \tau_f$
 $\tau_f = 0.44 \text{ ps}$

To the left is the device model . Recall that $C_{be} = C_{be,depl} + g_m \tau_f$. Let us take $C_{je}=17 \text{ fF}$, $\beta=\infty$, $C_{cbi}=2.6 \text{ fF}$, $C_{cbx}=0 \text{ fF}$, $R_{bb}=30 \text{ Ohms}$, $R_{ex}=6.67 \text{ Ohms}$, and $\tau_f=0.44 \text{ ps}$. The transistor, has 3 um^2 emitter area

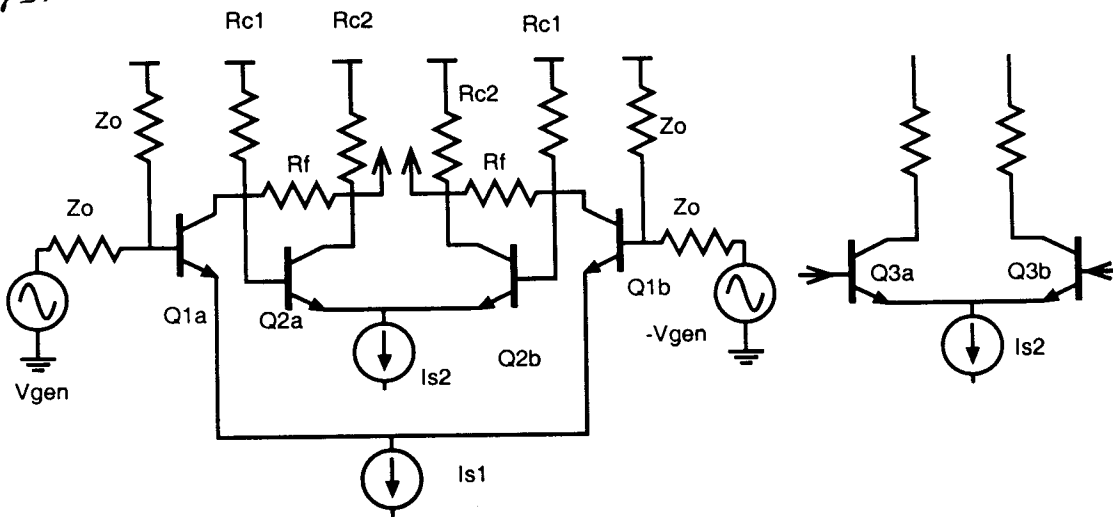We are once again analyzing one stage in a cascade of amplifiers. This always involves bookkeeping headaches, so for clarity the problem will be exactly defined as below.




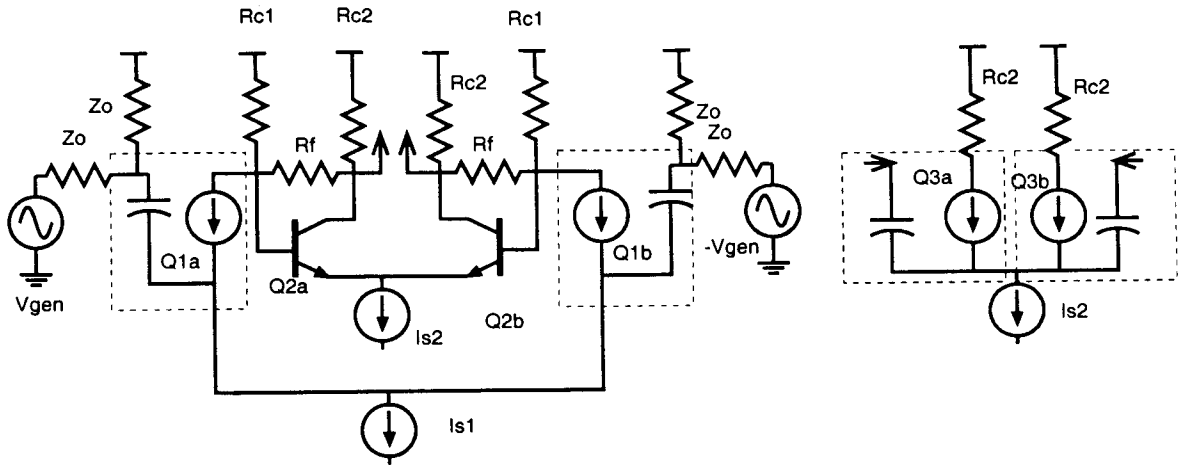The arrows indicate connections between points. To simplify the problem to the point at which it can be worked on an exam, Q1a/b and Q3a/b will use highly simplified models, wherein the transistor is given infinite beta, zero R_{ex} and R_{bb} , and zero C_{cb} .




Part a, xx points

DC bias.

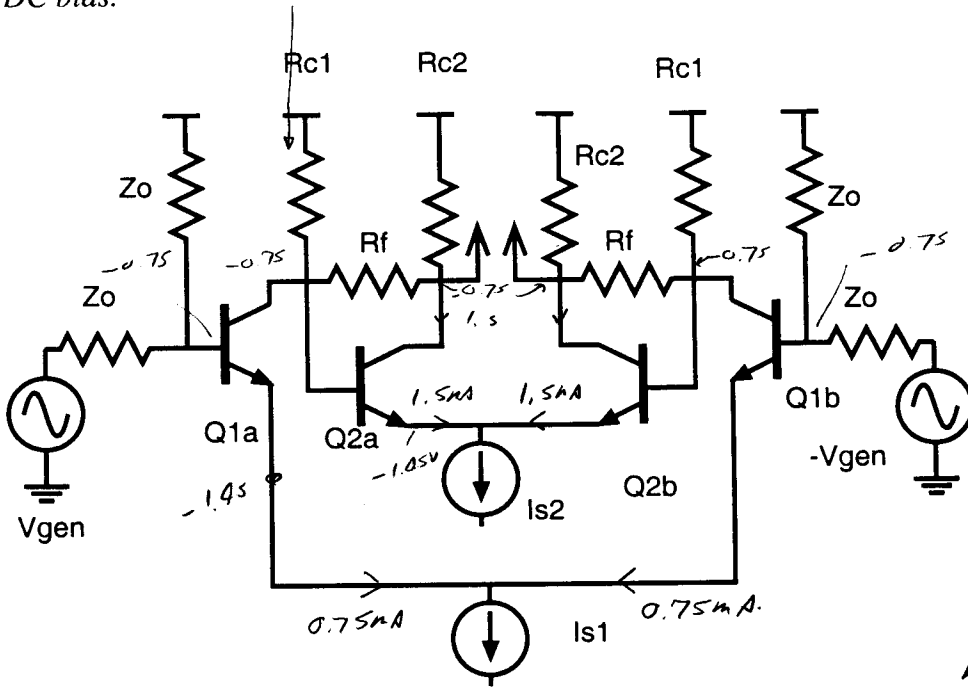

note. no ^{DC} current through Rf.

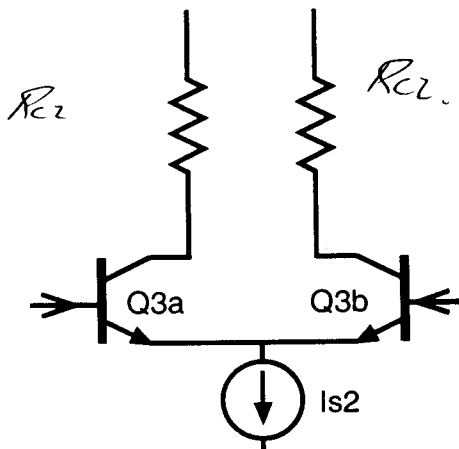

$$R_{c1} = \frac{0.75V}{0.75mA} = 1000\Omega$$

$$R_{c2} = \frac{0.75V}{1.5mA} = 500\Omega$$

Vgen has a DC level chosen so that the base of Q1 is at the same DC voltage as the base and the collector of Q2 (all are at -750 mV). Zo is 50 Ohms. Is1 is 1.5 mA, Is2 is 3 mA. Find Rc1, Rc2, and the DC voltages at all nodes within the circuit. Draw all DC node voltages and branch currents directly on the circuit diagram. Rf is 300 Ohms.

Part b, xx points

Midband gains

Find the differential voltage gain of the circuit, which we will here define as $2 \cdot (V_{out} / V_{gen})$, where V_{out} is the AC voltage at the collector of Q3a. Show the intermediate results indicated.



transconductance of Q1a = 28.8 mS

transimpedance of Q2a = -254 Ω

voltage gain of the Q1a/Q2a combination = +7.315

voltage gain of Q3a = 28.9

overall voltage gain = 211.4

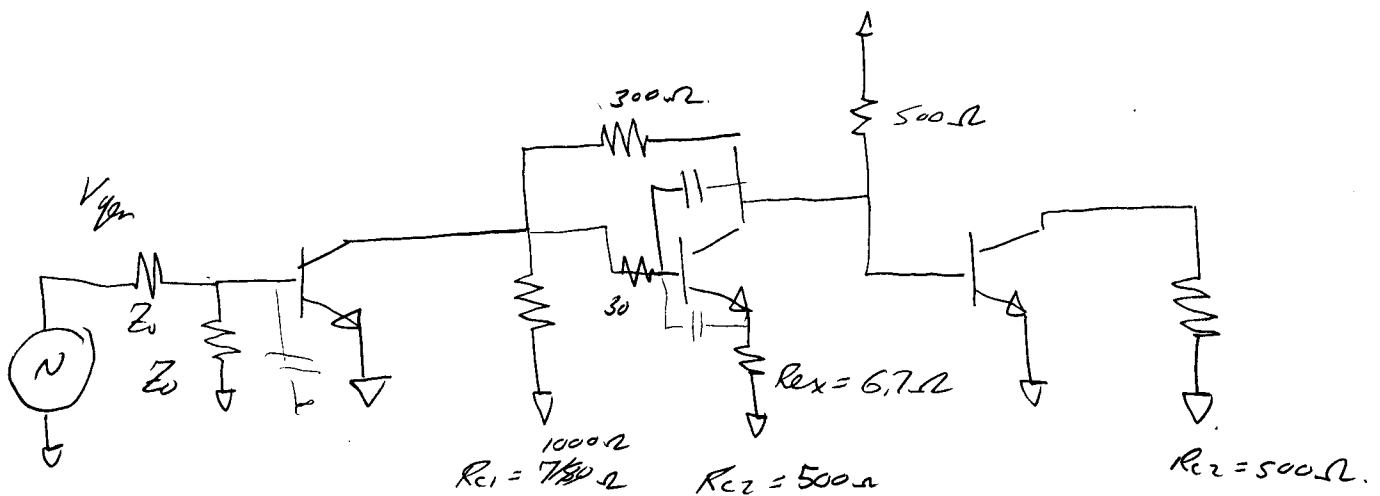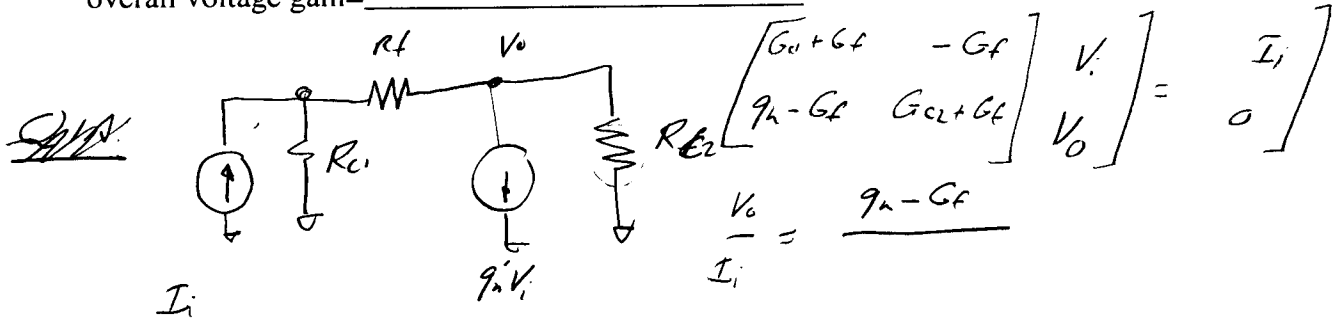


$I_E = 0.75 \text{ mA}$
 $1/g_m = 34.6 \Omega$
 $r_e = 29.8 \text{ m}\Omega$

$I_E = 1.5 \text{ mA}$
 $1/g_m = 17.3 \Omega$
 $r_e = 57.8 \text{ m}\Omega$
 $r_e' = \frac{1}{6} = 41.67 \text{ m}\Omega$
 $r_m = 24 \Omega$

$I_E = 1.5 \text{ mA}$
 $r_e = 57.8 \text{ m}\Omega$

Z_T ~~same~~ stage

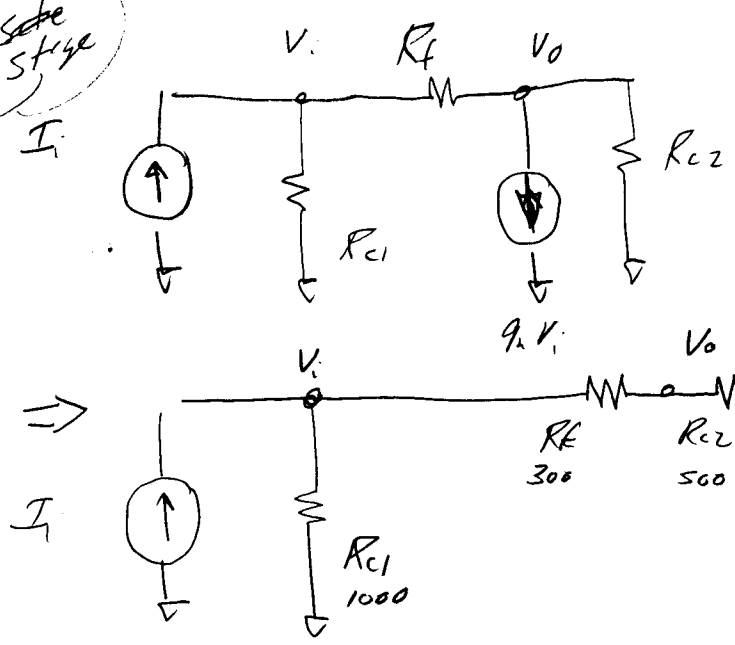

$$g_m' = \frac{1}{24 \Omega}$$

$$Z_{in} = R_{c1} \parallel \left(\frac{R_f + R_{c2}}{1 + g_m R_{c2}} \right) = 1000 \Omega \parallel \frac{300 + 500 \Omega}{1 + \frac{500 \Omega}{24 \Omega}}$$

$$= 1000 \Omega \parallel 36.6 \Omega = 35.34 \Omega$$

$$\frac{V_o}{V_i} = \frac{R_{c2}}{R_{c2} + R_f} - \frac{g_m' R_{c2} R_f}{R_f + R_{c2}} = \frac{R_{c2} - g_m' R_{c2} R_f}{R_f + R_{c2}}$$

$$= \frac{R_{c2} (1 - g_m' R_f)}{R_f + R_{c2}} = \frac{500 \Omega (1 - \frac{300 \Omega}{24 \Omega})}{800 \Omega} = -7.19 V/V$$

$$Z_T = Z_{in} \cdot \frac{V_o}{V_i} = -7.19 \cdot 35.34 = -254 \Omega$$

Q3 gain $g_m = \frac{1}{17.3 \Omega}$ $R_L = R_{c2} = 500 \Omega$

$$A_v = \frac{-500}{17.3} = -28.9$$

Part c, xx points
device models

Please enter the device parameter values below.

transistor	Rbe	Rbb	Rex	Cbe	Ccbi	gm
Q1	∞	0	0	29.6 fF	0	28.8 mS
Q2	∞	30	6.67	42.4 fF	2.6 fF	57.8 mS
Q3	∞	0	0	42.4 fF	0	57.8 mS
Q4						


If you plan to use degenerated models (absorbing Rex) for Q2, please draw the resulting transistor equivalent circuit and indicate element values below.

$$Q1: C_{be} = g_m + 9.4 \text{ TF} = 17 \text{ fF} + 9.4 (0.44 \text{ pS})$$


$$=$$

$$Q2: 25.4 \text{ fF}$$

Degenerated model for Q2.
before

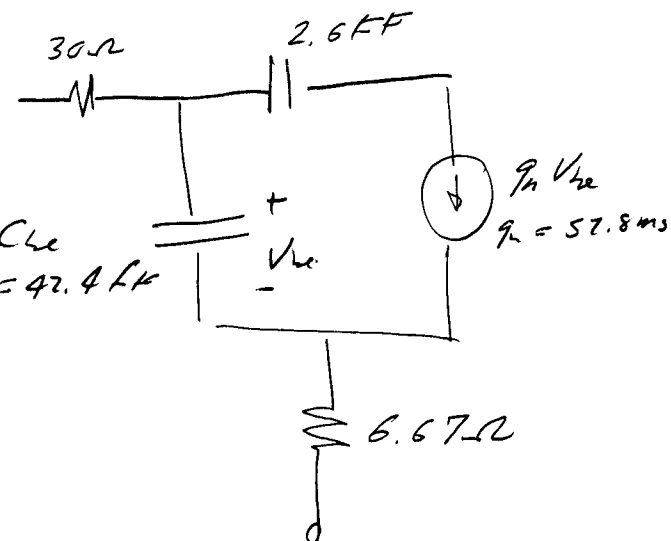


after.

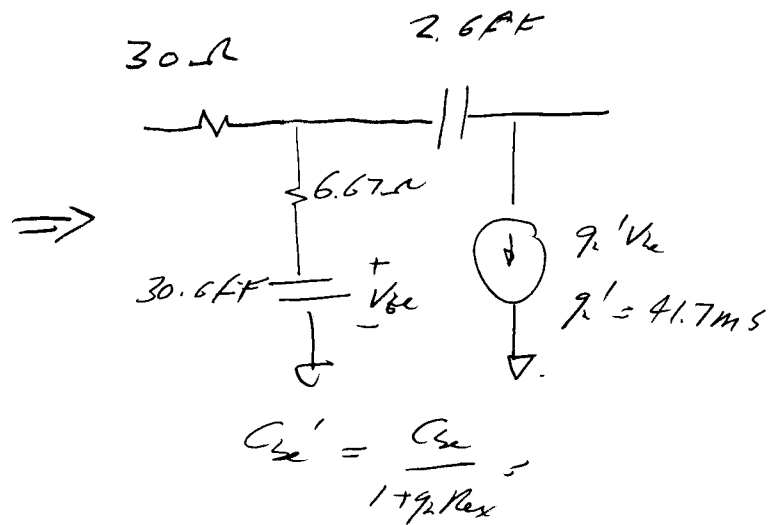

Part d, xx points

high frequency analysis

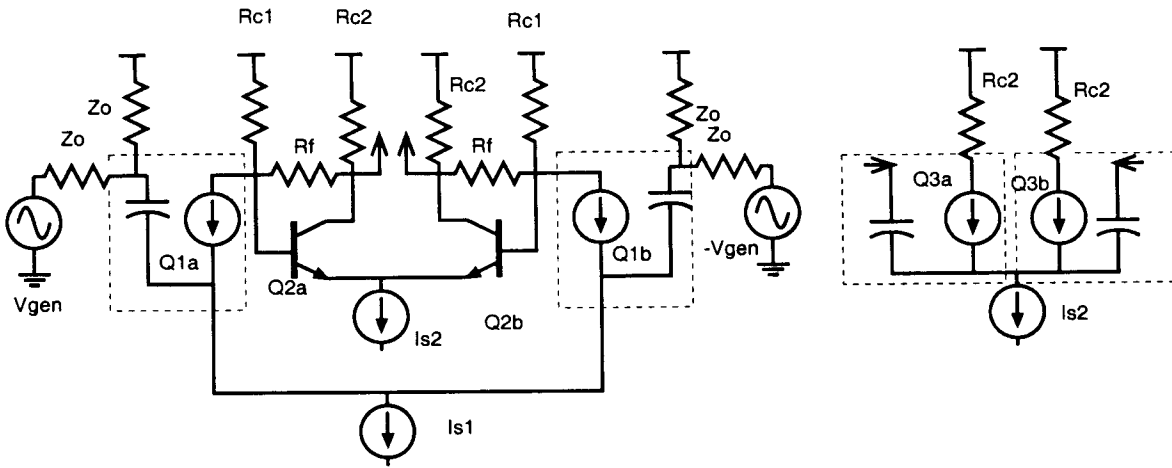

Please note that the overall circuit simplifies considerably because (1) we can use half-ckt models for differential operation and (2) the simplified model of Q1 results in Cbe1 being part of a completely separate network from the remainder of the problem.

Using MOTC, find the following:

charging time constant associated with Cbe1a = $\frac{29.6 \text{ fF} \times 50 \Omega}{2} = 0.74 \text{ ps}$

resulting pole frequency in the transfer function = $\frac{215 \text{ GHz}}{\text{Hz}}$
(not rad/sec)

first-order time constant associated with Cbe2a = $35.6 \Omega \times 30.6 \text{ fF} = 1.09 \text{ ps}$

first-order time constant associated with Ccbi2a = $28.7 \Omega \times 42.4 \text{ fF} = 1.22 \text{ ps}$

first-order time constant associated with Cbe3a = $296 \Omega \times 2.6 \text{ fF} = 0.77 \text{ ps}$

2nd-order time constant associated with Cbe2a and Ccbi2a = $5.39 (10^{-25}) \text{ sec}^2$

2nd-order time constant associated with Cbe2a and Cbe3a = $8.77 (10^{-24}) \text{ sec}^2$

2nd-order time constant associated with Ccbi2a and Cbe3a = $7.7 (10^{-25}) \text{ sec}^2$

the 2 pole frequencies (if real), or the natural resonance frequency (Hz) and damping factor (if complex)

$$1 + a_1 j\omega + a_2 (j\omega)^2 = 1 + (2\zeta/\omega_n) (j\omega) - \omega^2/\omega_n^2$$


$$\omega_n = 3.15 (10^{11}) \text{ rad/sec} \rightarrow 50.2 \text{ GHz}$$

$$\zeta = \frac{a_1}{2\sqrt{a_2}} = 0.487$$

$$a_1 = 3.08 \text{ ps}$$





$$a_2 = 1.003 (10^{-23}) \text{ sec}^2$$

9A

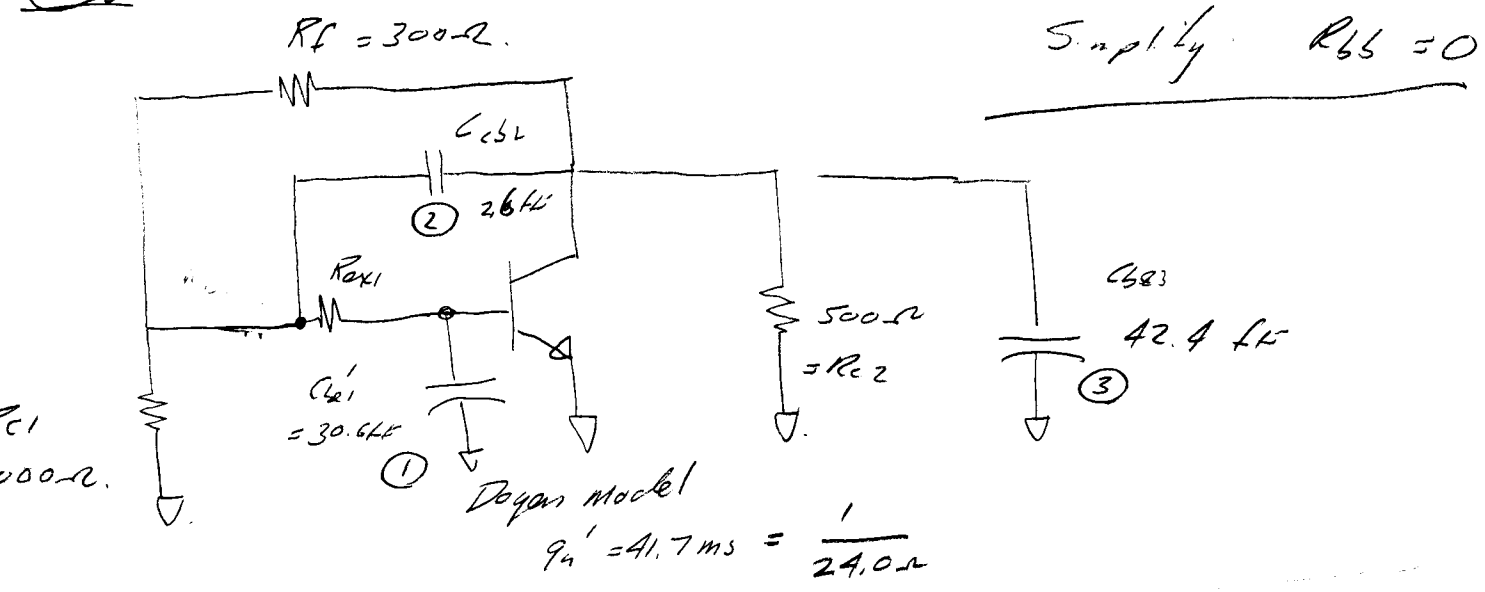

Simplify $R_{B5} = 0$

Impedance seen by C_{E3} = R_{E3}^0

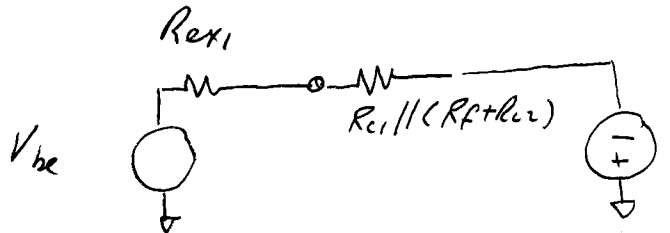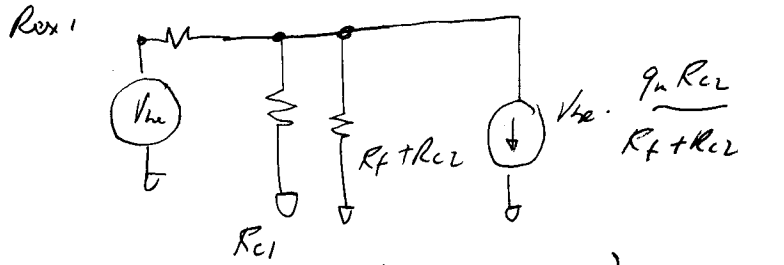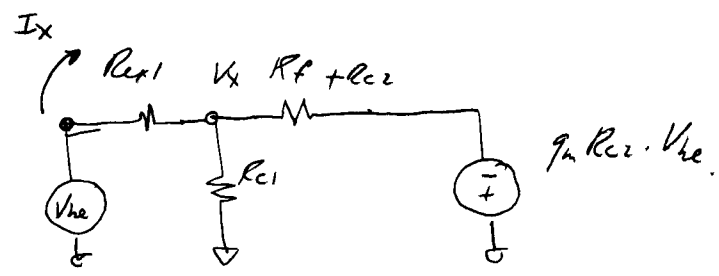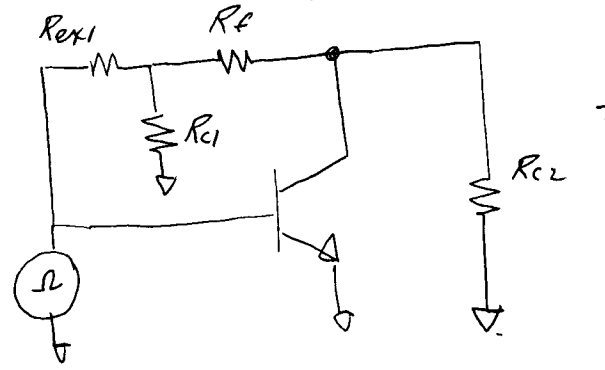


$$R_{E3}^0 = \frac{R_{ex1}}{1 + \beta \left(\frac{R_{E2}}{R_{E2} + R_F} \right) (R_{C1} \parallel (R_F + R_{E2}))} + \frac{R_{C1} \parallel (R_F + R_{E2})}{1 + \beta \left(\frac{R_{E2}}{R_{E2} + R_F} \right) (R_{C1} \parallel (R_F + R_{E2}))}$$

$$= \frac{6.7\Omega + 444\Omega}{1 + 42ms \left(\frac{5}{8} \right) 444\Omega} = \frac{450.7\Omega}{1 + 11.66} = 35.6\Omega$$

9B

Impedance seen by C_{e3} :

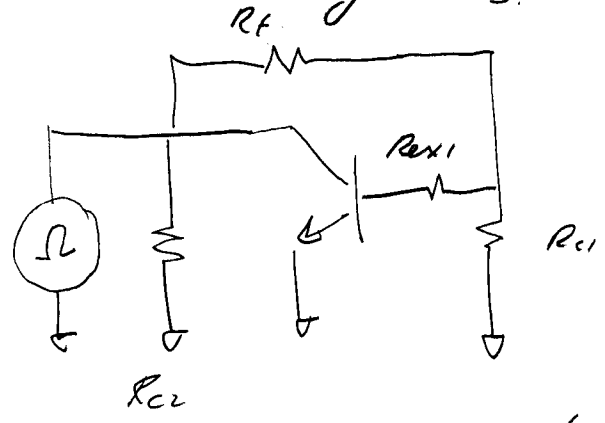


$$R_{33}^0 = R_{c2} \parallel (R_f + R_{c1}) \parallel \left(\frac{R_f + R_{c1}}{R_{c1}} \cdot \frac{1}{g_m'} \right)$$

$$= 500\Omega \parallel 1300\Omega \parallel \left(\frac{1300\Omega}{1000\Omega} \cdot \frac{1}{41.7\text{ms}^{-1}} \right)$$

$$= 500\Omega \parallel 1300\Omega \parallel 31.17\Omega = 28.7\Omega$$

9C

Impedance seen by C_{cb2} :

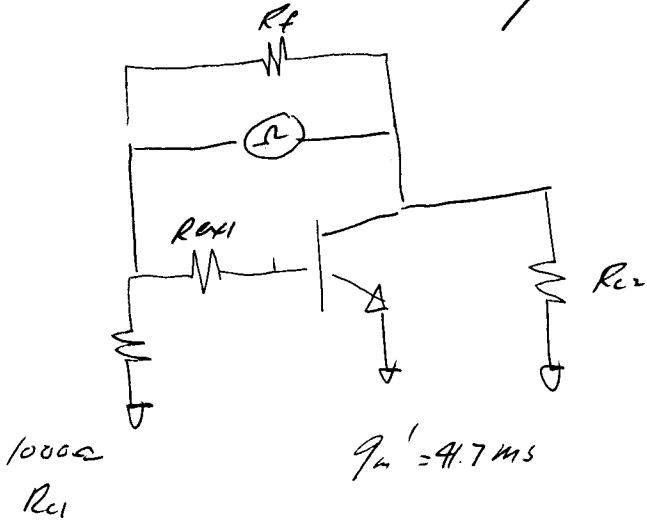


$$\begin{aligned}
 R_{in}^o &= R_f \parallel \left\{ R_{e1} (1 + g_m' R_{e2}) + R_{e2} \right\} \\
 &= 300 \Omega \parallel \left\{ 1000 \Omega (1 + 41 \text{ ms} \cdot 500 \Omega) + 500 \Omega \right\} \\
 &= 300 \Omega \parallel \left\{ 1000 \Omega (1 + 20.65) + 500 \Omega \right\} \\
 &= 300 \Omega \parallel \left\{ 21.64 \text{ k}\Omega + 500 \Omega \right\} \\
 &= \underline{\underline{296 \Omega}} \cong \underline{\underline{R_f !!!}}
 \end{aligned}$$

9d

$$R_{11}^0 C_1 C_2 R_{22}' = ? = 35.6 \Omega \cdot 30.6 \mu F \cdot 2.6 \mu F \cdot 188.4 \Omega$$

$$= 5.337 (10^{-25}) \text{ Sec}^2$$

$R_{22}' = ?$

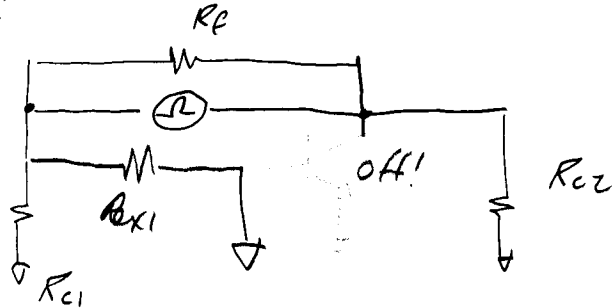


$$R_{22}' = [(R_{ci} \parallel R_{ex1}) + R_{cz}] \parallel R_f \approx [6.7 \Omega + 500 \Omega] \parallel 300 \Omega$$

$$= \underline{188.4 \Omega}$$

$$R_{11}^0 C_1 C_3 R_{33}' = 35.6 \Omega \times 30.6 \mu F \times 42.4 \mu F \times 190 \Omega$$

$$= 8.77 (10^{-24}) \text{ Sec}^2$$

$R_{33}' = ?$

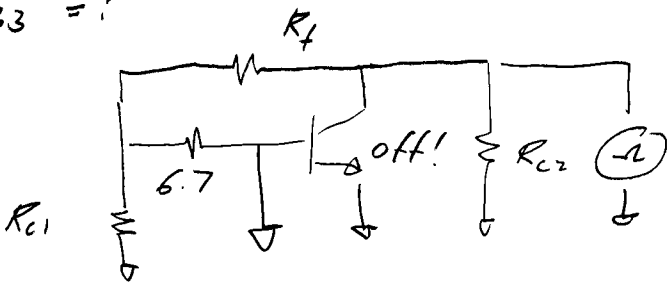

$$R_{33}' \approx R_{cz} \parallel (R_f + R_{ex1})$$

$$= 500 \parallel (300 + 6.7)$$

$$= 190 \Omega$$

96


~~R₂₂⁰~~ C₂ C₃ R₃₃²

OR

$$= R_{33}^0 C_3 C_2 R_{22}^3 = 28.7\Omega (42.4\text{fF})(2.6\text{fF})(230.8\Omega)$$

$$= 7.30(10^{-25})\text{sec}^2$$

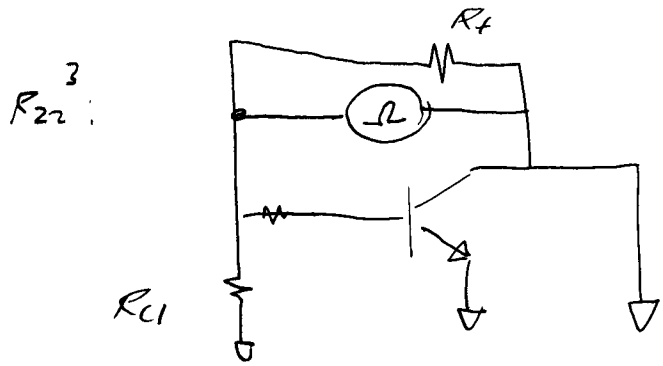28.7Ω \uparrow \uparrow \uparrow \uparrow
~~299k Ω~~ 42.4fF 2.6fF What?




$$R_{22}^3 = R_4 \parallel R_{21} = 300 \parallel 1000 = 230.8\Omega$$

6.63.

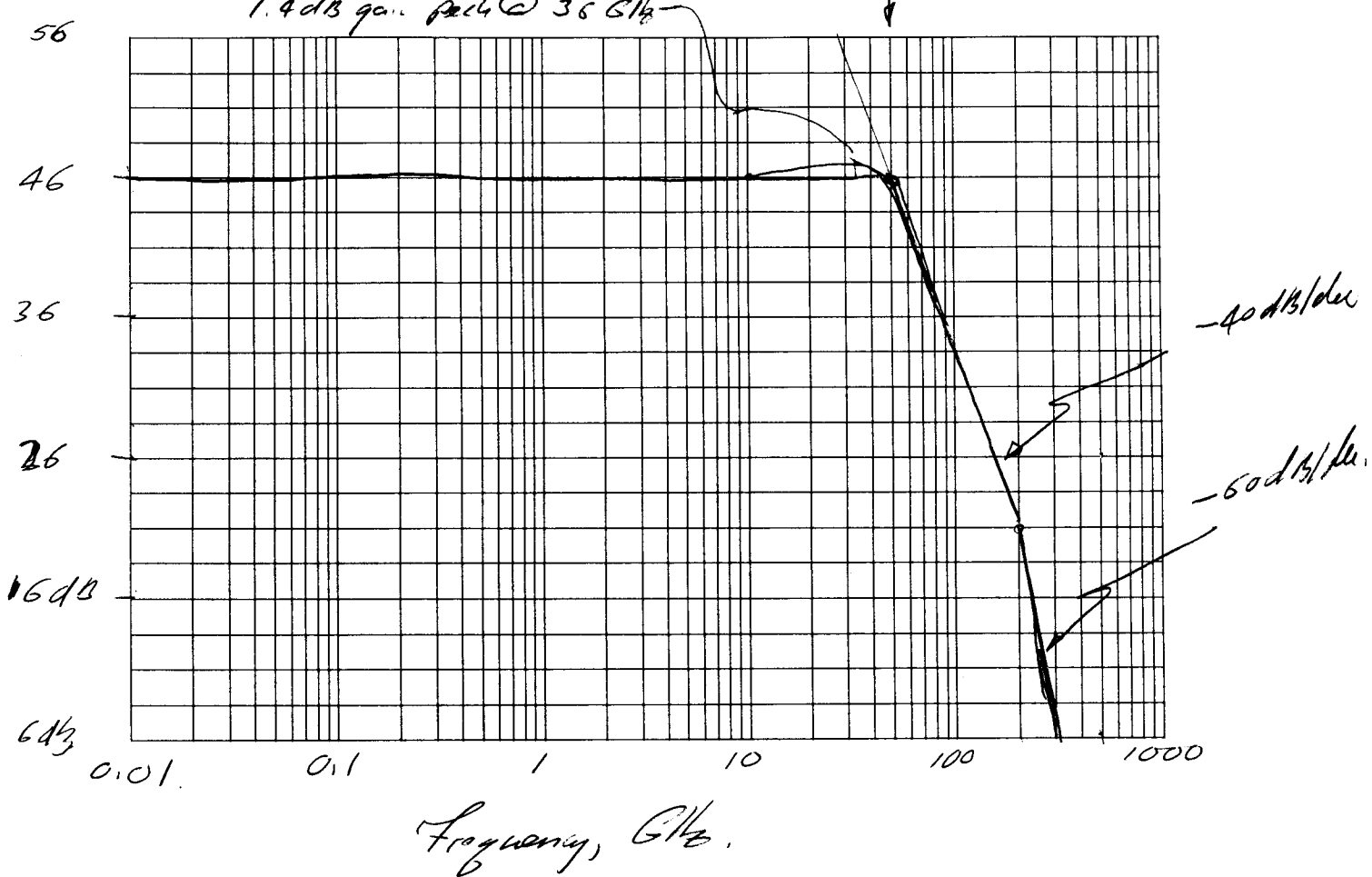Part e, xx points

Please make a **quantitative** bode plot of the transfer function (label both axes, draw pole frequencies in the right places, and slopes correctly)



at the input, we have a simple real pole with $f_p = 215 \text{ GHz}$.

At the Zr-9m stage, we have complex poles with $f_n = 50 \text{ GHz}$ and $\zeta = 0.487$



$$211 = A_v \rightarrow 46.5 \text{ dB}$$

$$\text{Value of peak at } \omega = \omega_n \rightarrow \frac{1}{2\zeta} = \frac{1}{2(0.487)} \approx 1 = 0 \text{ dB}$$

however, full peak is at ω_d , and is higher \rightarrow approx 10 dB gain peak

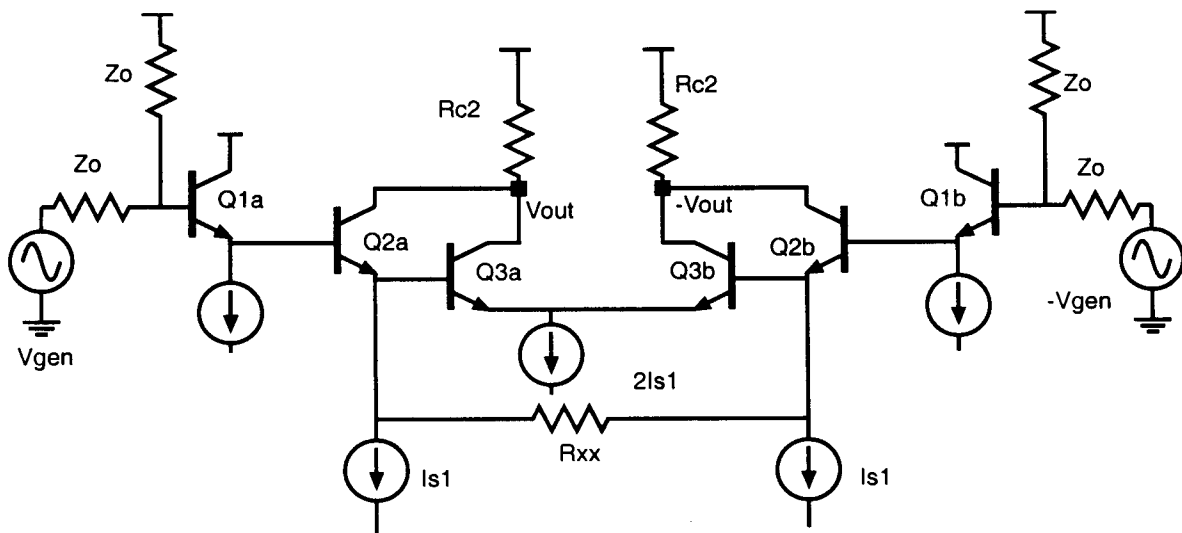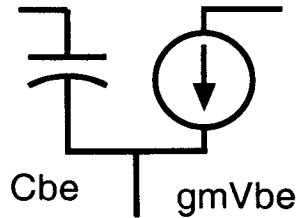Problem 2, xx points

Our transistor model is now much simpler, with a transistor f_t of 300 GHz:



The circuit has all transistors biased at 1 mA each. R_{xx} is 52 Ohms. R_{c2} has a 300 mV DC drop across it.

actual peak lies at $\omega_p = \omega_n \sqrt{1 - 2\zeta^2} = 0.725 \omega_n = 36.5\%$
 peak magnitude is $A_p = \frac{1}{2\zeta \sqrt{1 - \zeta^2}} = 1.17:1 = 1.4 \text{ dB gain peak}$

$$1 + \frac{2\zeta(j\omega)}{\omega_n} = \frac{\omega^2}{\omega_n^2} = \left(1 - \frac{\omega^2}{\omega_n^2}\right) + \frac{2\zeta}{\omega_n} j\omega$$

$$\frac{1}{|M|} = \sqrt{\left(1 - \left(\frac{\omega}{\omega_n}\right)^2\right)^2 + \left(\frac{2\zeta}{\omega_n} \frac{\omega}{\omega_n}\right)^2}$$

$$\sqrt{1 - \zeta^2}$$

Part a, xx points

DC bias

Draw all DC node voltages and branch currents on the circuit diagram below

