

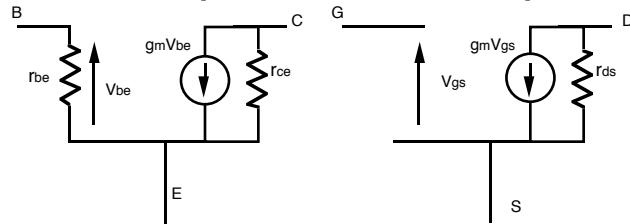


Basics: Amplifiers at Low Frequencies

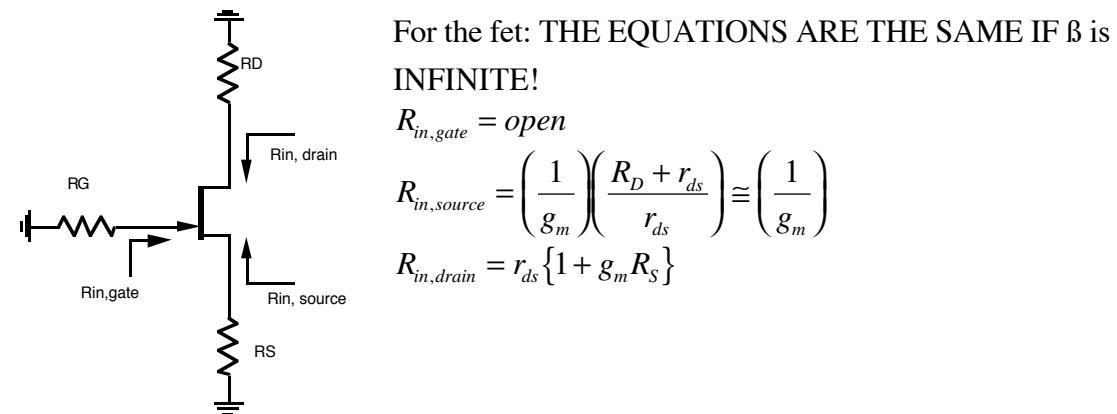


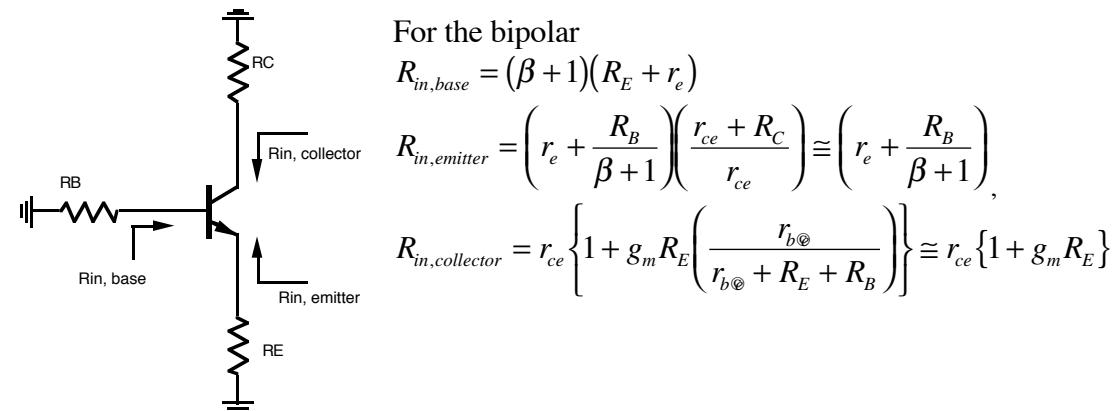
Left is the equivalent circuit of a bipolar transistor; $g_m = I_E/V_T = 1/r_e$, $V_T = kT/q$, $r_{be} = \beta r_e = \beta/g_m$. On the right is the FET model. Below is a transistor with ac equivalent load resistances R_C , R_E , and R_B .



Be warned that in the equations above R_C , R_E and R_B are the equivalent resistances seen by the transistor. So in, the amplifier circuits below, THINK: "what is the effective resistance seen by the transistor?", before plugging into the equations.

Amplifier Stages

Common Emitter and Common Source

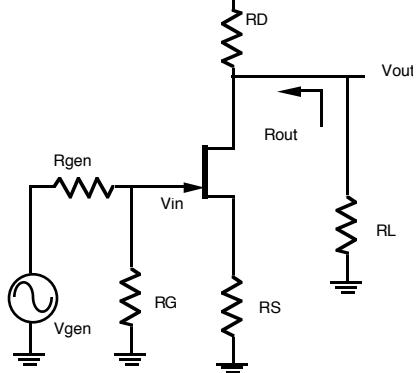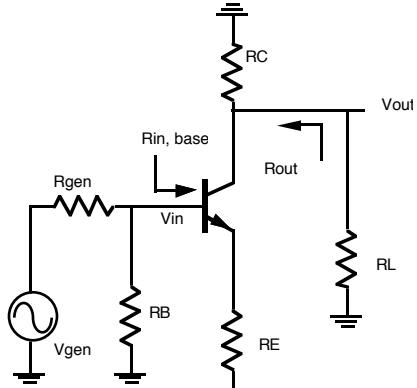

Common emitter:

$$R_{in} = R_B \parallel R_{in,base} = R_B \parallel (\beta + 1)(R_E + r_e)$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{-(R_C \parallel R_L \parallel R_{out,collector})}{r_e + R_E} = \frac{-(R_C \parallel R_L \parallel R_{out,collector})}{r_e + R_E}$$

$$R_{out} = (R_C \parallel R_{out,collector})$$

Common source:


$$R_{in} = R_G$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{-(R_D \parallel R_L \parallel R_{out,drain})}{1/g_m + R_S} = \frac{-(R_D \parallel R_L \parallel R_{out,drain})}{1/g_m + R_S}$$

$$R_{out} = R_D \parallel R_{out,drain}$$

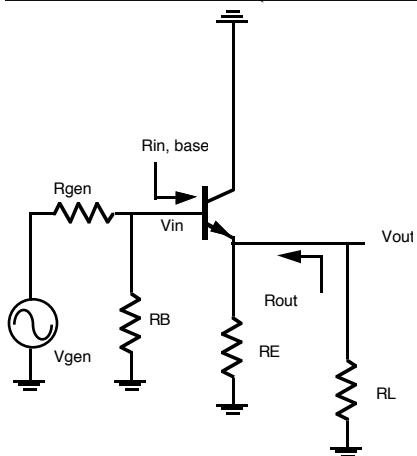Common Collector (emitter follower) and common drain (source follower)




for the emitter follower:

$$R_{in} = R_B \parallel R_{in,base} = R_B \parallel (\beta + 1)(R_E \parallel R_L + r_e)$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_{Leq}}{r_e + R_{Leq}} = \frac{R_E \parallel R_L}{r_e + R_E \parallel R_L}$$
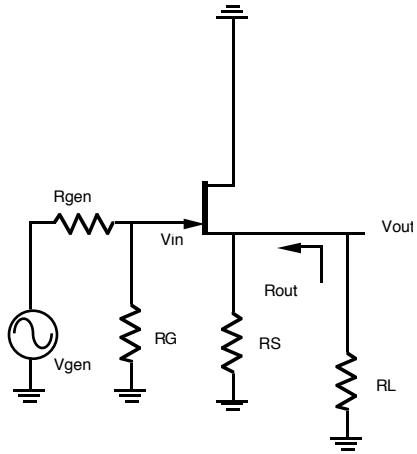
$$R_{out} = R_E \parallel R_{in,emitter} = R_E \left(r_e + \frac{R_B}{\beta + 1} \right)$$



For the source follower:


$$R_{in} = R_G$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_{L,eq}}{1/g_m + R_{L,eq}} = \frac{R_S \| R_L}{1/g_m + R_S \| R_L}$$

$$R_{out} = R_S \| R_{in,source} = R_S \| \frac{1}{g_m}$$

Common Base and common gate

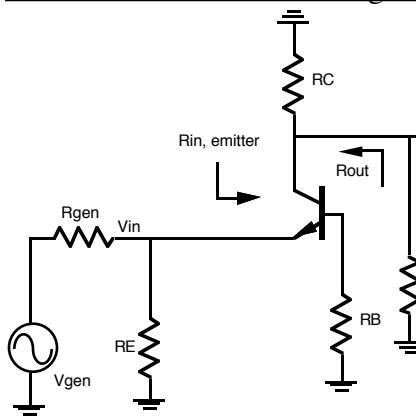

For the common base:


$$R_{in} = R_E \| R_{in,emitter}$$

$$R_{in,emitter} = \left(r_e + \frac{R_B}{\beta + 1} \right) \left(\frac{r_{ce} + R_C \| R_L}{r_{ce}} \right) \approx \left(r_e + \frac{R_B}{\beta + 1} \right)$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_{L,eq}}{R_{in,emitter}} = \frac{R_C \| R_L}{R_{in,emitter}}$$

$$R_{out} = (R_C \| R_{out,collector})$$

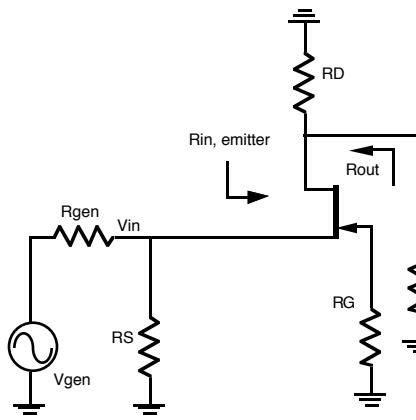

For the common gate

$$R_{in} = R_S \| R_{in,source}$$

$$R_{in,source} = \left(\frac{1}{g_m} \right) \left(\frac{R_D \| R_L + r_{ds}}{r_{ds}} \right) \approx \left(\frac{1}{g_m} \right)$$

$$\frac{V_{in}}{V_{gen}} = \frac{R_{in}}{R_{in} + R_{gen}}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_{L,eq}}{R_{in,source}} = \frac{R_D \| R_L}{R_{in,source}}$$

$$R_{out} = R_D \| R_{out,drain}$$