
Mixed Signal IC Design
Notes set 4:
Broadband Design Techniques

Mark Rodwell

University of California, Santa Barbara

rodwell@ece.ucsb.edu 805-893-3244, 805-893-3262 fax

Getting more bandwidth

At this point we have learned basics (MOTC etc)

How can we get more bandwidth.... ?

Resistive feedback

transconductance-transimpedance

emitter-follower buffers, benefits and headaches

emitter degeneration...basics

emitter degeneration and area scaling


ft-doubler stages..

distributed amplifiers

broadbanding / peaking with LC networks....


examples....

Emitter Degeneration, I

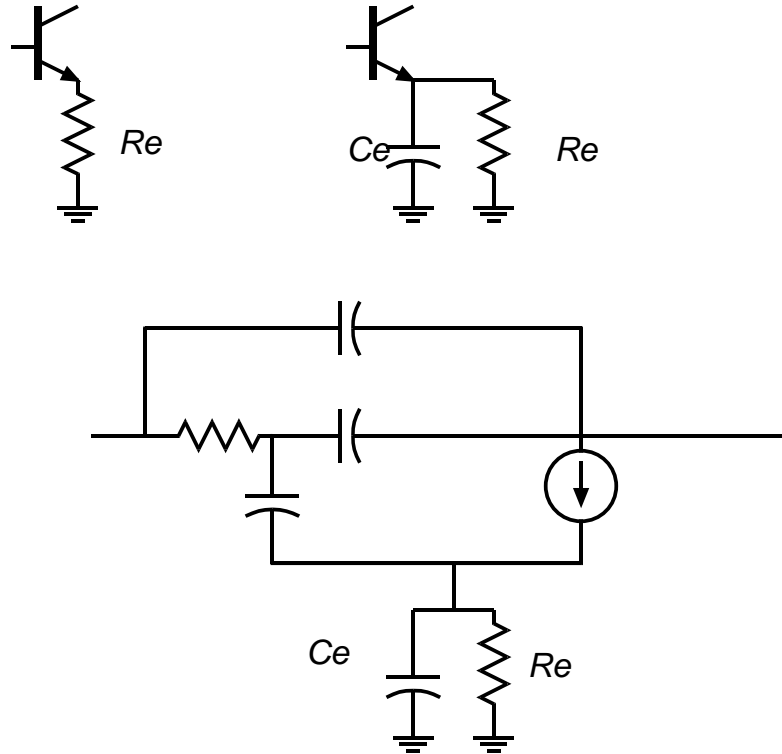


Emitter degeneration was introduced using only an emitter resistance. We will find we instead want an RC combination such that $R_e C_e = C_{be} / g_m$.

Emitter Degeneration, 2

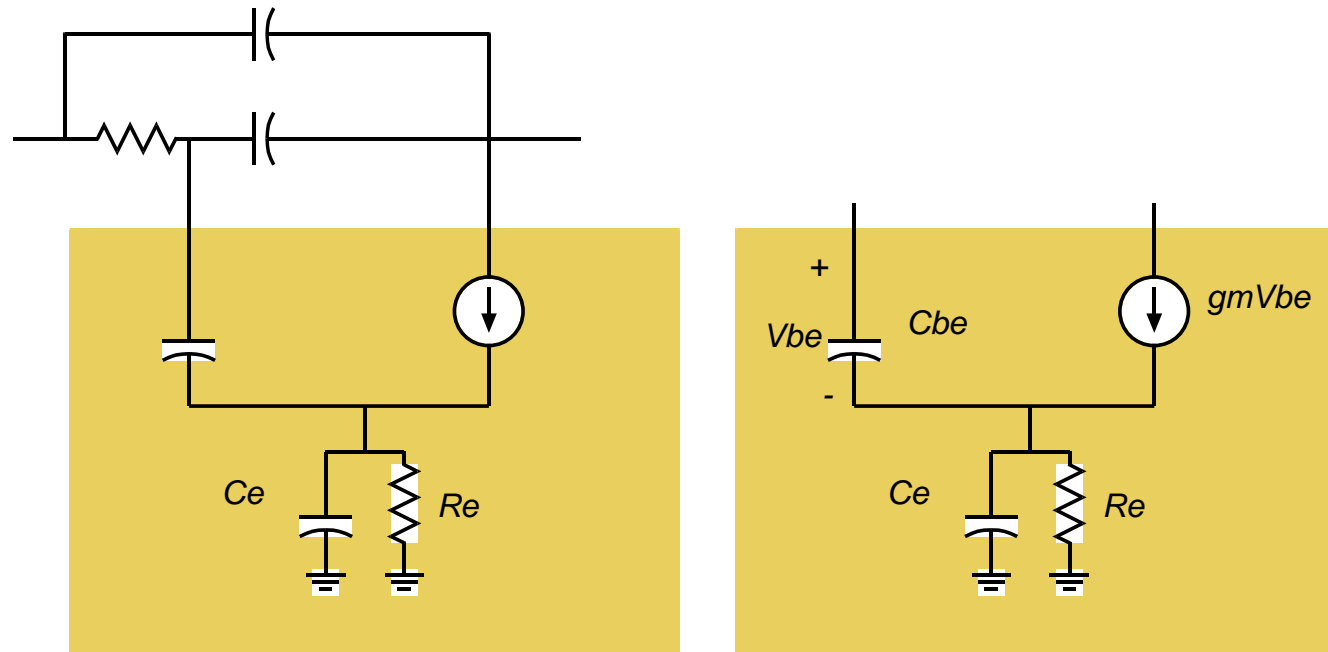

Next note that the topology is such that we can work with R_{bb} , C_{cb} etc removed, and add them back later....

Emitter Degeneration, 3

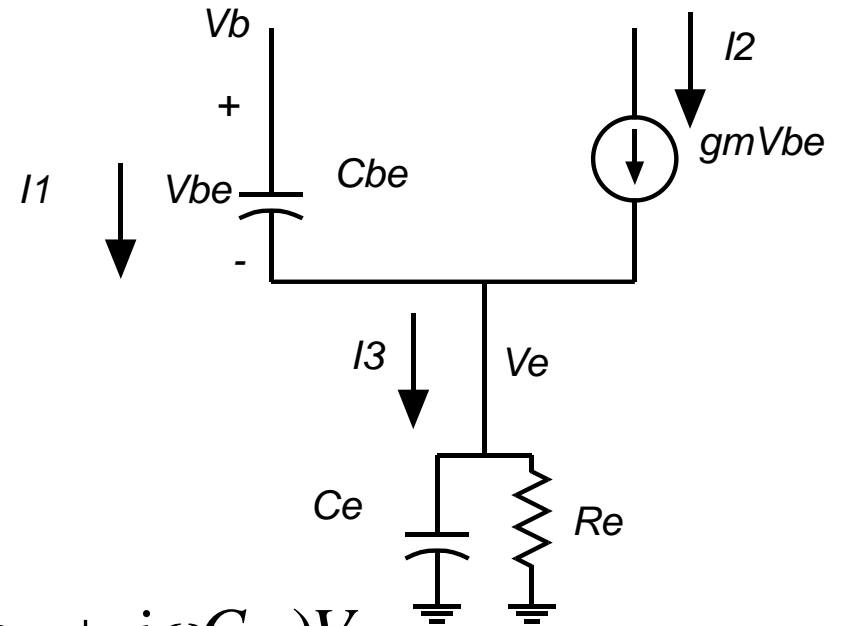

Working from V_{be} :

$$I_1 = j\omega C_{be} V_{be} \quad I_2 = g_m V_{be} \quad \text{so} \quad I_3 = (g_m + j\omega C_{be}) V_{be}$$

$$\text{But } V_E = I_3 (1/R_E + j\omega C_E)^{-1} = V_{be} * g_m R_E$$



(note that the frequency dependent terms cancel)

$$\text{So, } I_2 = V_{be} / (R_E + 1/g_m) \text{ and}$$

$$Z_{in} = j\omega C_{in} = j\omega C_{be} (1 + g_m R_E)^{-1}$$


R_{bb} and C_{cb} etc can now be added back...they dont change

Emitter Degeneration, Summary

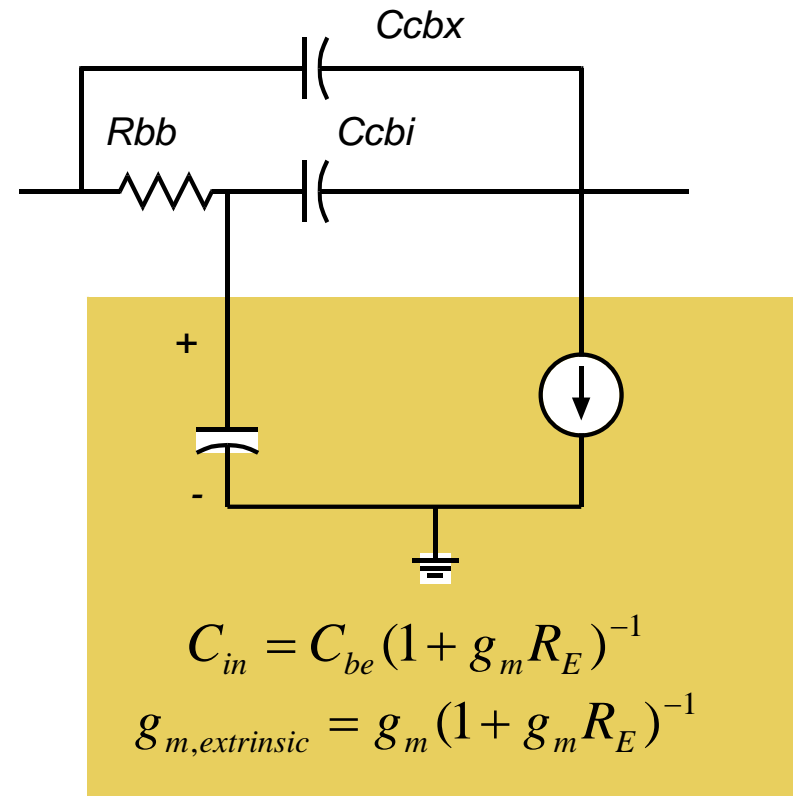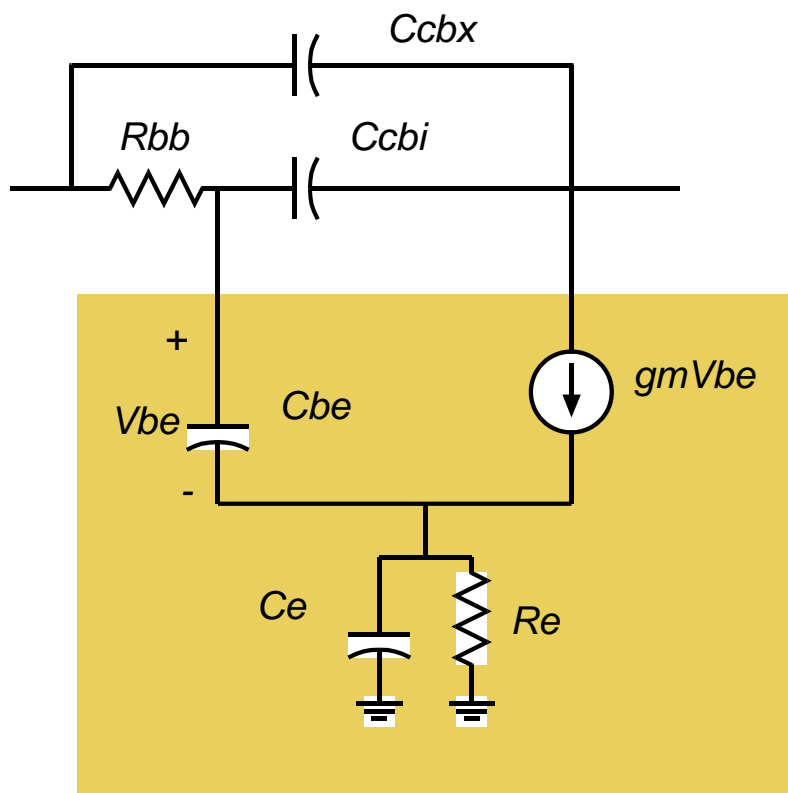

Other element values do not change...

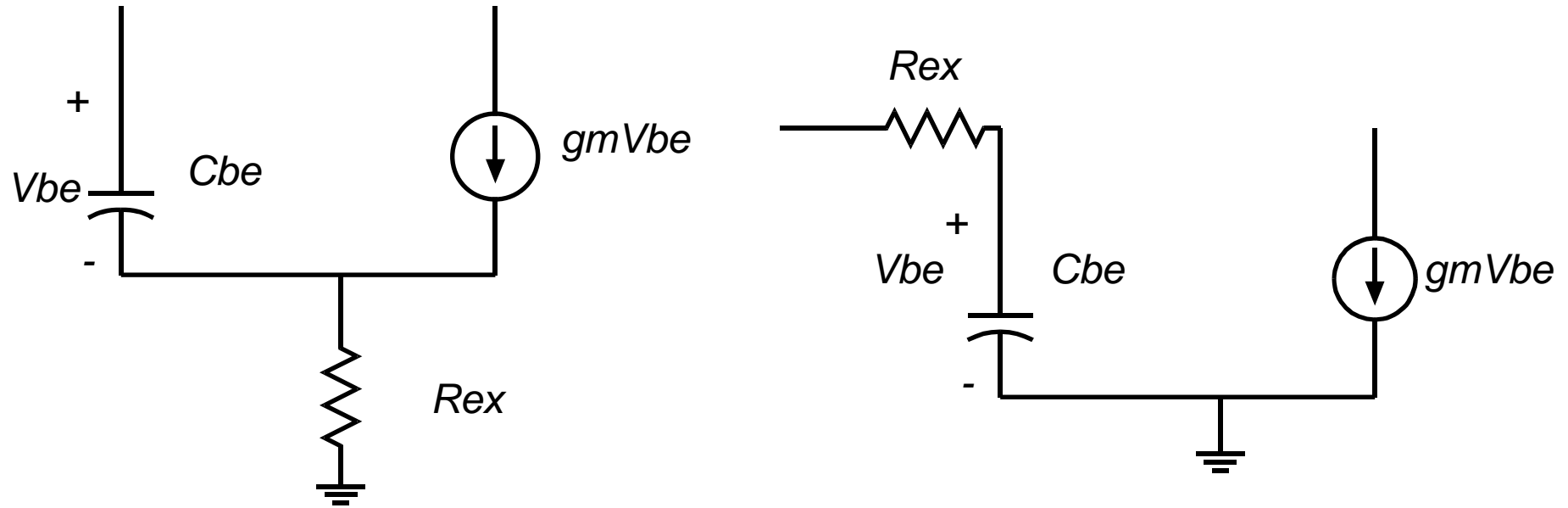Emitter Degeneration, Unbypassed emitter resistance





$$g_{m,extrinsic} = g_m (1 + g_m R_E)^{-1}$$


can be shown by elementary nodal analysis, work through...

Key observation: degeneration by this method results in a series input resistance, which can increase C_{be} charging time.

Emitter Degeneration, combination case

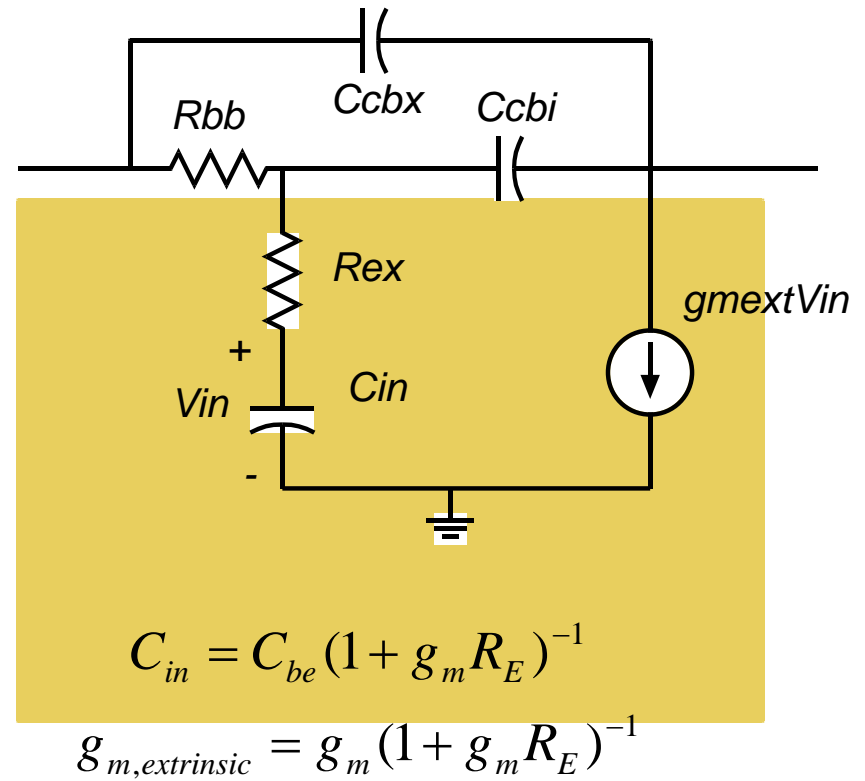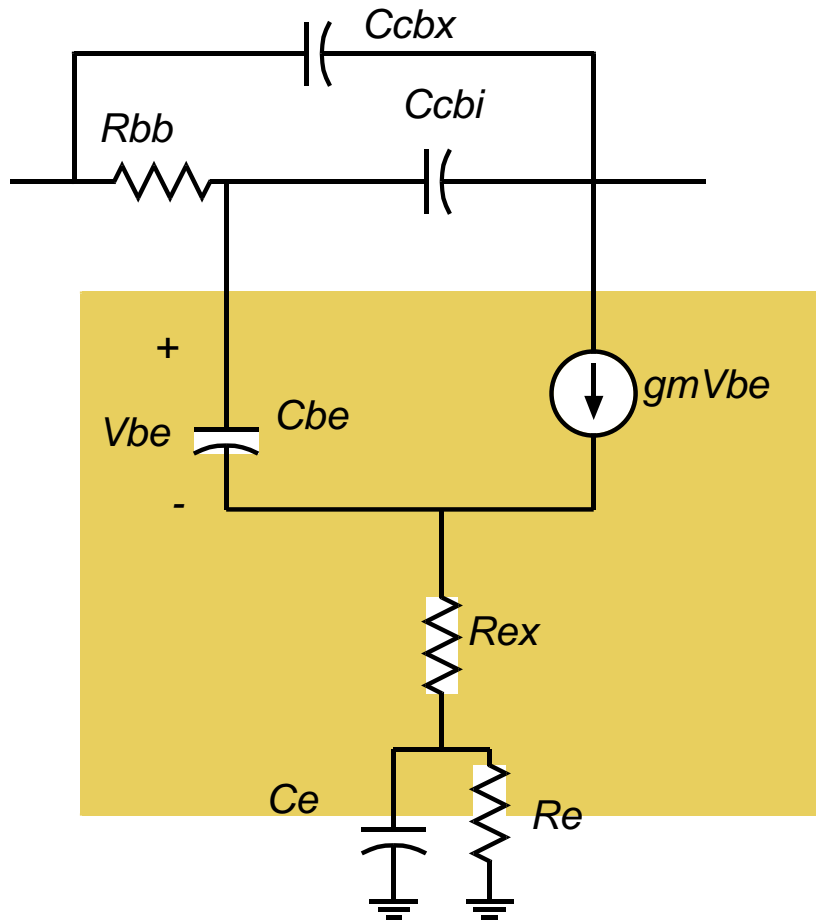

Emitter Degeneration and Area Scaling 1

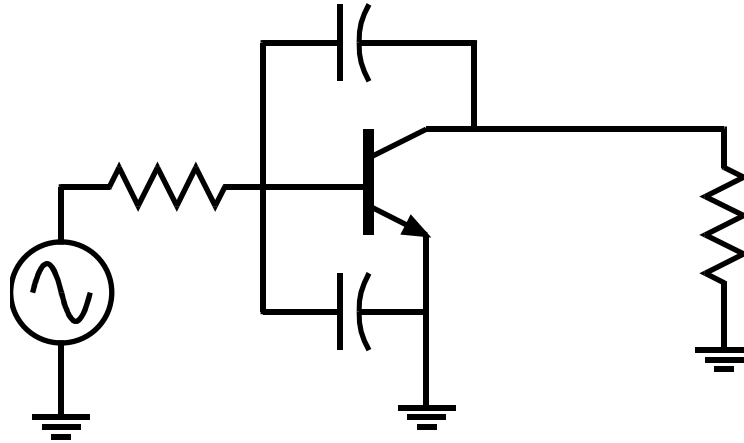


emitter area = A_e
current density = J_e
*Current = $A_e * J_e = I_e$*
transconductance = g_m
input capacitance = C_{be}
collector capacitance = C_{cb}
base resistance = R_{bb}

Consider the CS stage. If we desire a gain $A_V = -g_{m,ext} R_L$,


then we have

$$a_1 = C_{be} (R_{gen} + R_{bb}) + C_{cb} \left[(R_{gen} + R_{bb})(1 + g_{m,ext} R_L) + R_L \right]$$

Emitter Degeneration and Area Scaling 2

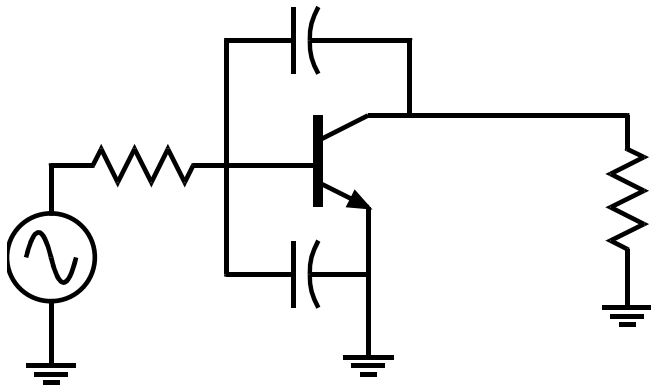

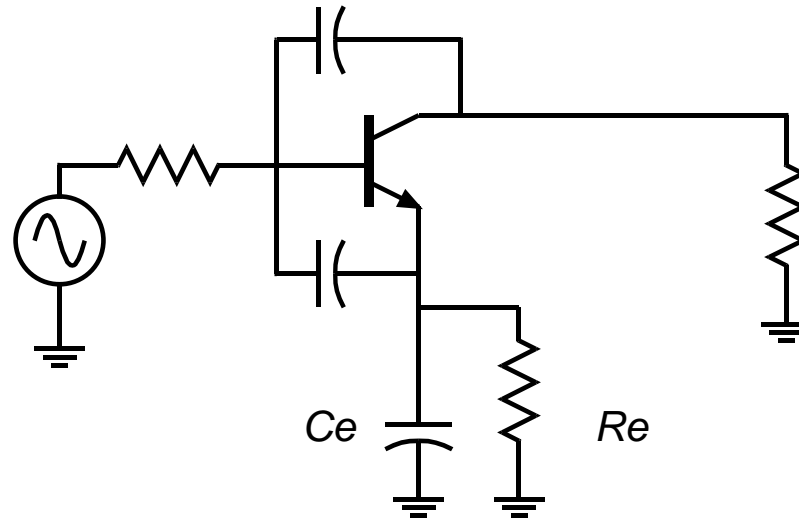
emitter area = A_e
 current density = J_e
 Current = $A_e * J_e = I_e$
 transconductance = g_m
 input capacitance = C_{be}
 collector capacitance = C_{cb}
 base resistance = R_{bb}



Bigger transistor, before degeneration
 emitter area = kA_e
 current density = J_e
 Current = $kA_e * J_e = I_{ke}$
 transconductance = kg_m
 input capacitance = kC_{be}
 collector capacitance = kC_{cb}
 base resistance = R_{bb}/k

now degenerate:
 R_e picked such that $(1 + g_m R_e) = k$
 intrinsic transconductance = kg_m
 extrinsic transconductance = $kg_m / (1 + g_m R_e) = g_m$
 input capacitance = $kC_{be} / (1 + g_m R_e) = C_{be}$
 collector capacitance = kC_{cb}
 base resistance = R_{bb}/k

Emitter Degeneration and Area Scaling 3

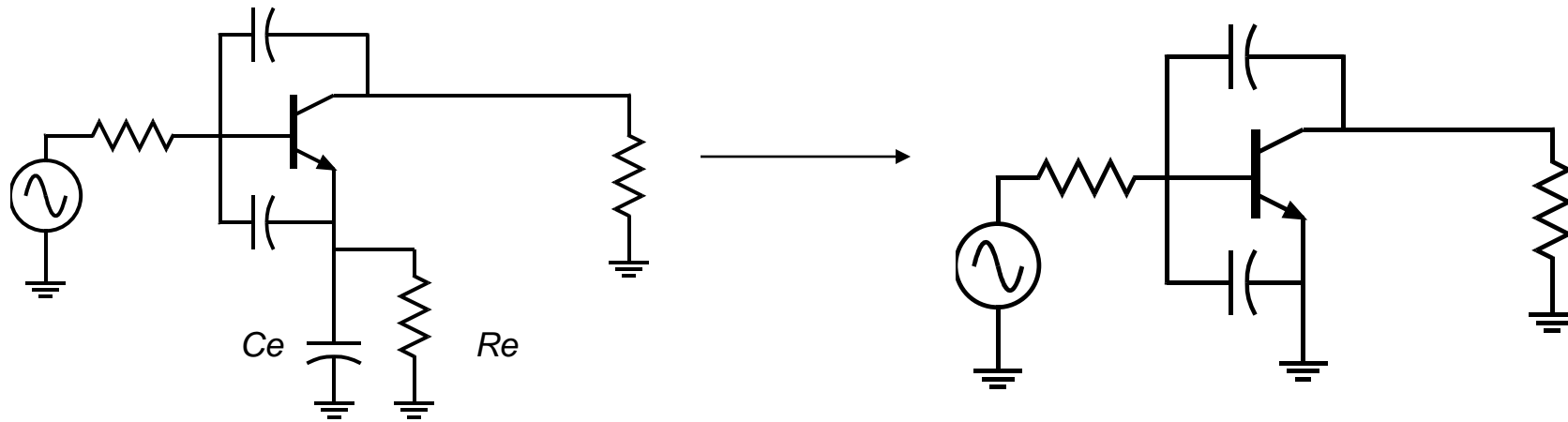


We have made the transistor K times bigger, then degenerated by $K : 1$. We are left with the original g_m and C_{in} , but have increased C_{cb} by $K : 1$ and decreased R_{bb} by $K : 1$

$$a_1 = C_{be} \left(R_{gen} + \frac{R_{bb}}{k} \right) + kC_{cb} \left[\left(R_{gen} + \frac{R_{bb}}{k} \right) (1 + g_{m,ext} R_L) + R_L \right]$$

$$a_1 = R_{gen} C_{be} + C_{cb} [R_{bb} (1 + g_{m,ext} R_L)] + \frac{C_{be} R_{bb}}{k} + kC_{cb} [R_{gen} (1 + g_{m,ext} R_L) + R_L]$$


So, appropriate choice of k exchanges delay terms associated with R_{bb} vs C_{cb} , and gives the highest bandwidth

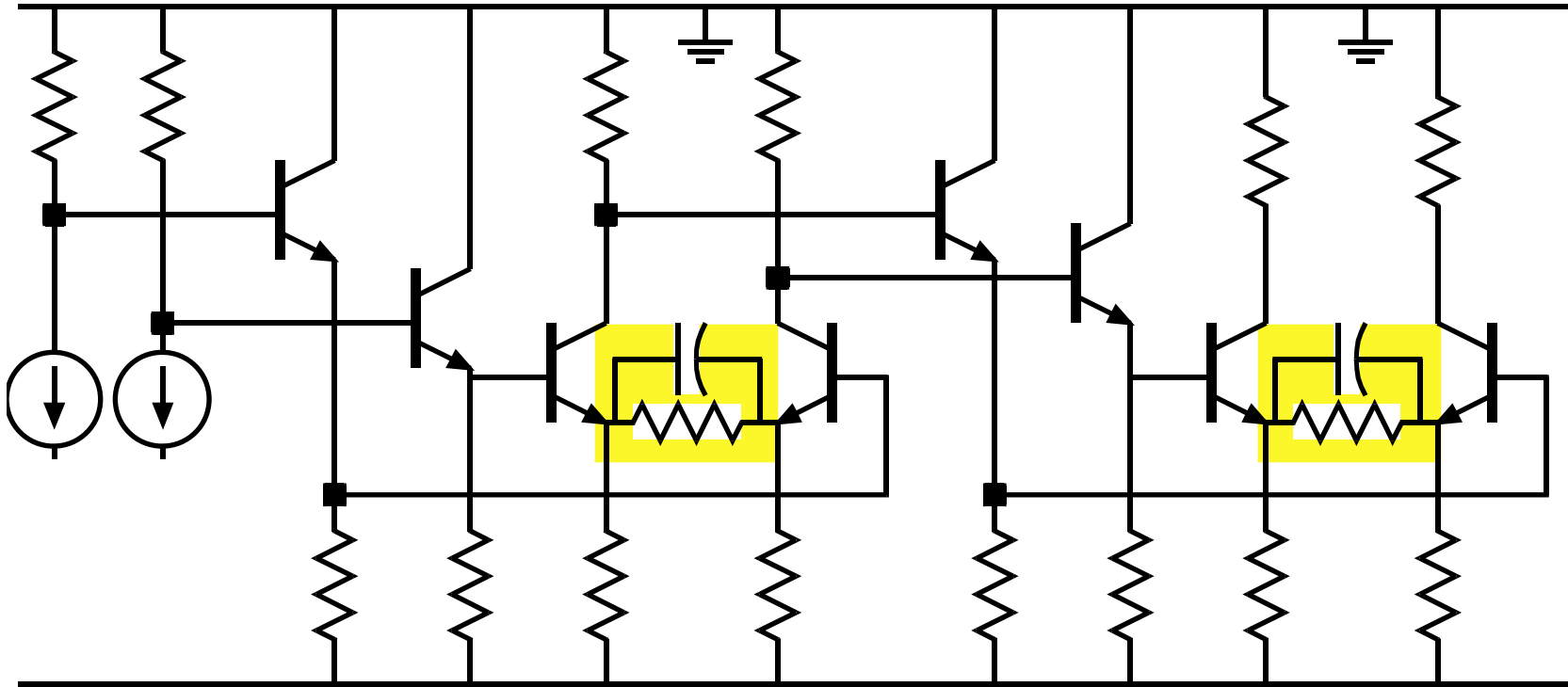Emitter Degeneration and Area Scaling 4: Emitter Follower Case



Why might we want to do this ?

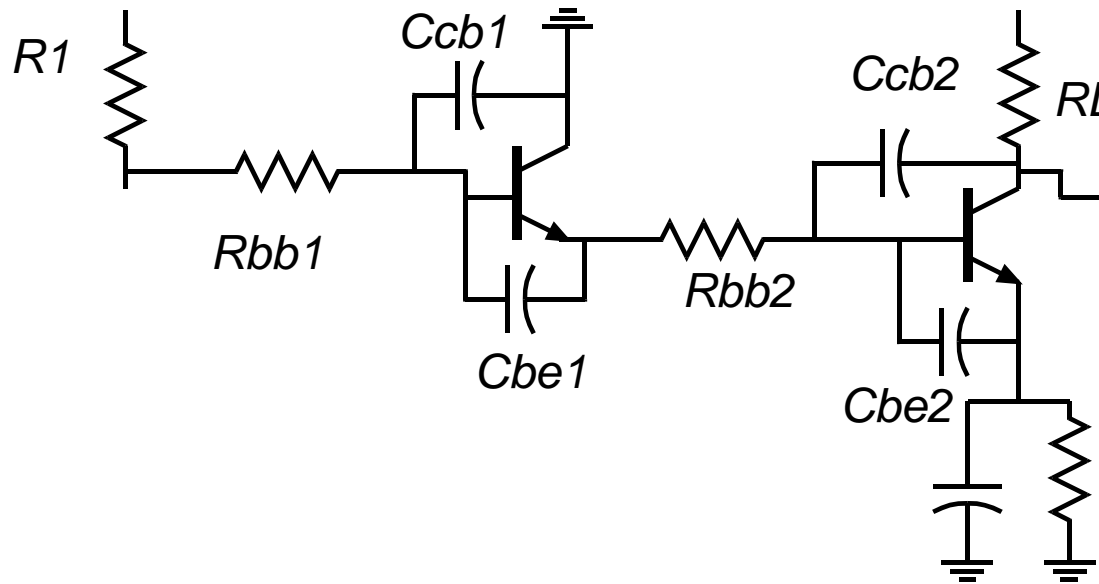Emitter Degeneration and Area Scaling 5: Emitter Follower Case




Considering only terms in a_1 associated with the CE stage,

$$a_1 = \dots + kC_{cb2} \left(\left(\frac{R_{bb2}}{k} + R_{out,1} \right) (1 + g_{m,ext} R_L) + R_L \right) + C_{be2} \left(\frac{R_{bb2}}{k} + R_{out,1} \right)$$

Note that the undegenerated $R_{bb} C_{be}$ time constant of an HBT is several times $1 / 2\pi f_\tau$, and can be a major bandwidth limit.


Area scaling/degeneration as above is one method to address this.

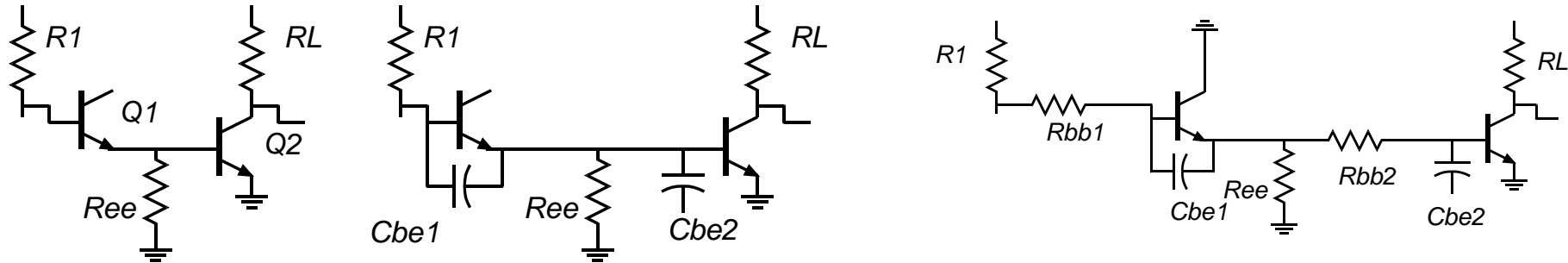Ft-doubler stages...the Darlington Revisited




Recall the improvement in Damping provided by Ree
 ...is there a larger lesson here ?

2 Kinds of Darlington:

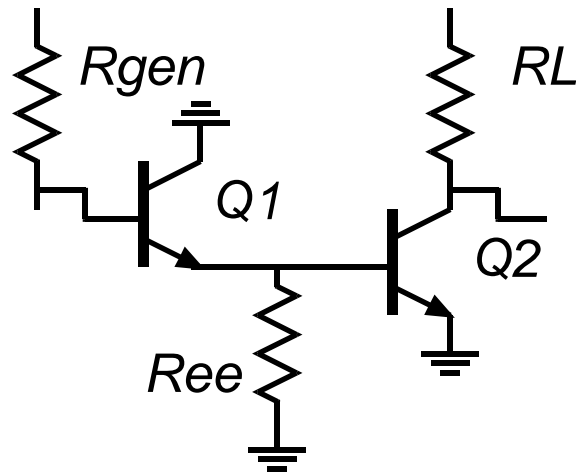

EF collector grounded

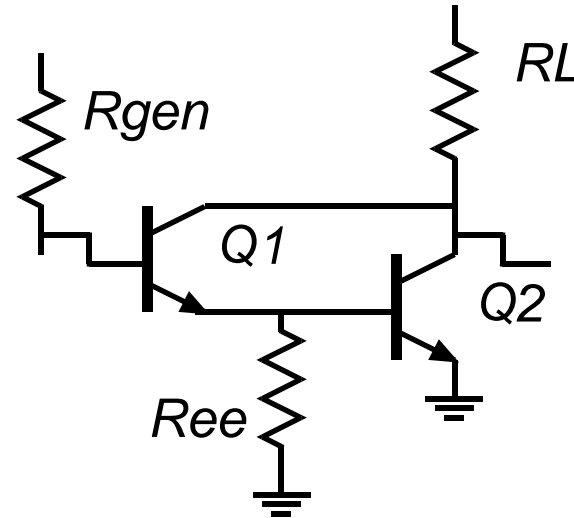



Collectors tied together

If collectors are tied together:


AC collector currents of both transistors contribute to output :)

Both transistor C_{cb} 's undergo Miller multiplication :(

Ft-doubler stages 2

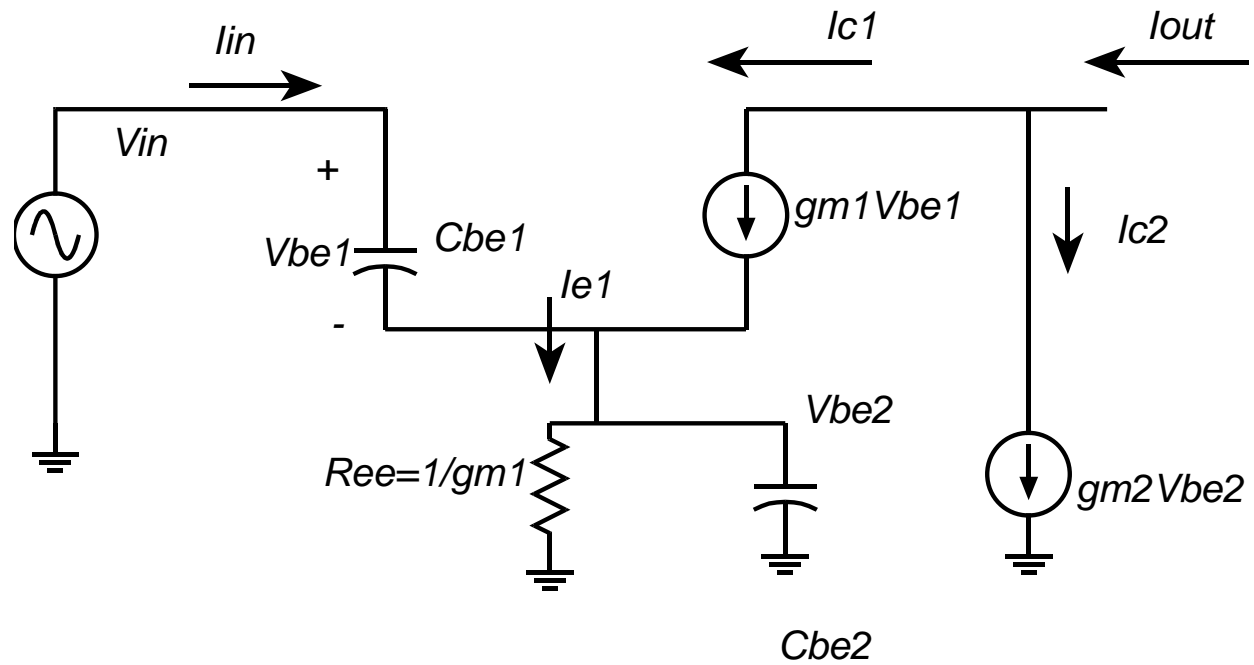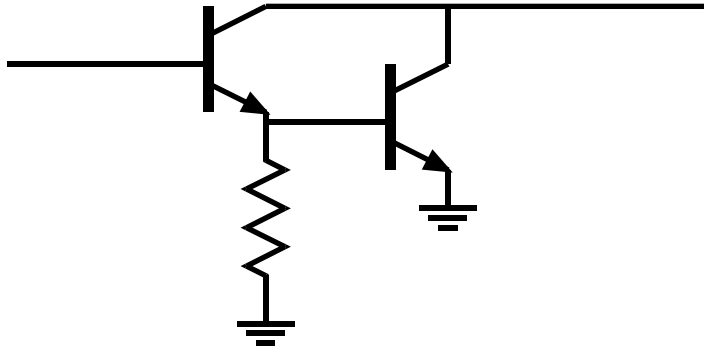

Ft-doubler stages 3

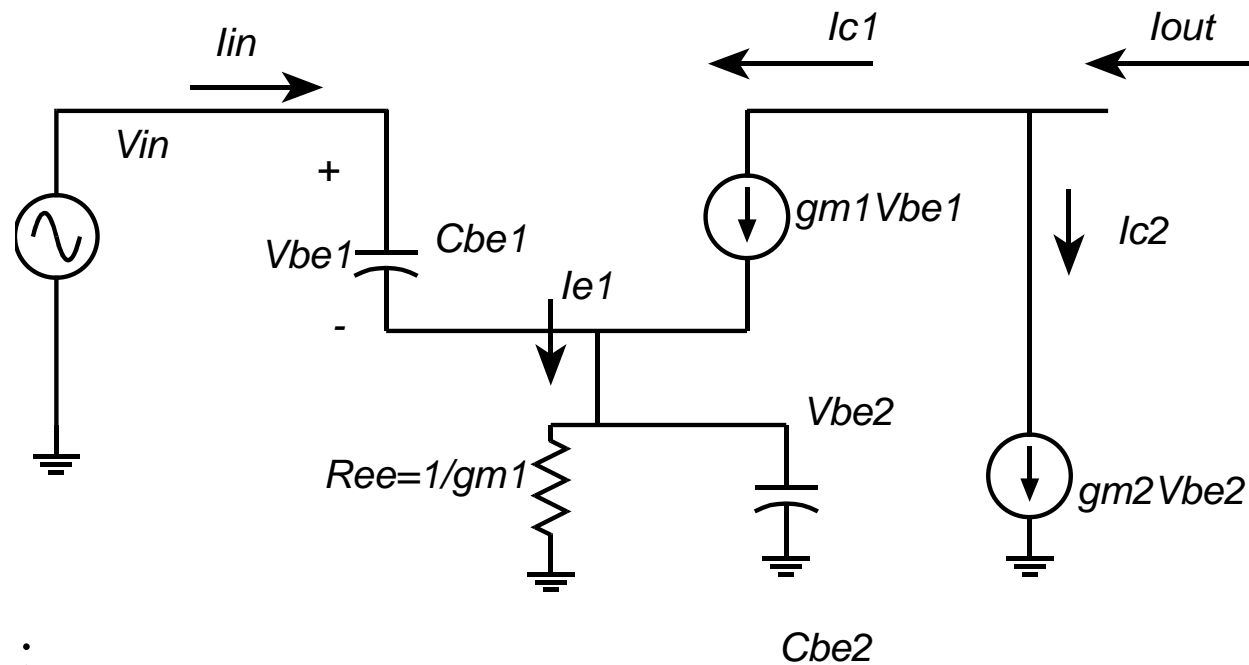

Work from V_{be1} :

$$I_{in1} = j\omega C_{be} V_{be1}, I_{c1} = g_m V_{be1}, I_{e1} = g_m V_{be1} (1 + j\omega C_{be} / g_m)$$


$$V_{be2} = I_{e1} R_{ee} / (1 + j\omega C_{be} R_{ee}) = g_m V_{be1} R_{ee} \frac{(1 + j\omega C_{be} / g_m)}{(1 + j\omega C_{be} R_{ee})}$$

Choose R_{ee} such that $C_{be} R_{ee} = C_{be} / g_m \dots$ hence $R_{ee} = 1 / g_m$

$$V_{be2} = (g_m R_{ee}) V_{be1} = V_{be1} \dots \text{so } V_{be1} = V_{be2} = V_{in} / 2$$

$$I_{in} = j\omega C_{be} / 2 \text{ and } I_{out} = g_m V_{be} \text{ hence } I_{out} / I_{in} = 2g_m / j\omega C_{be}$$

Ft-doubler stages 4

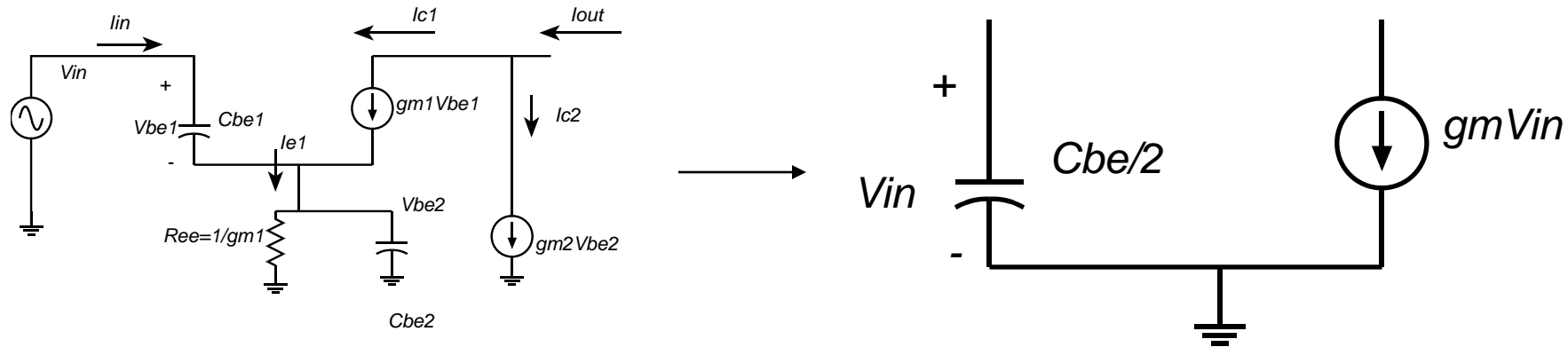


$$I_{in} = j\omega C_{be} / 2 \text{ and } I_{out} = g_m V_{be}$$

$$I_{out} / I_{in} = 2g_m / j\omega C_{be} = 2f_\tau / jf$$

..we have doubled f_τ !

Note that this analysis has ignored R_{bb} and C_{cb} ...we have certainly not doubled f_{max} , nor will we have doubled overall circuit bandwidth, given the presence of these other parasitics.

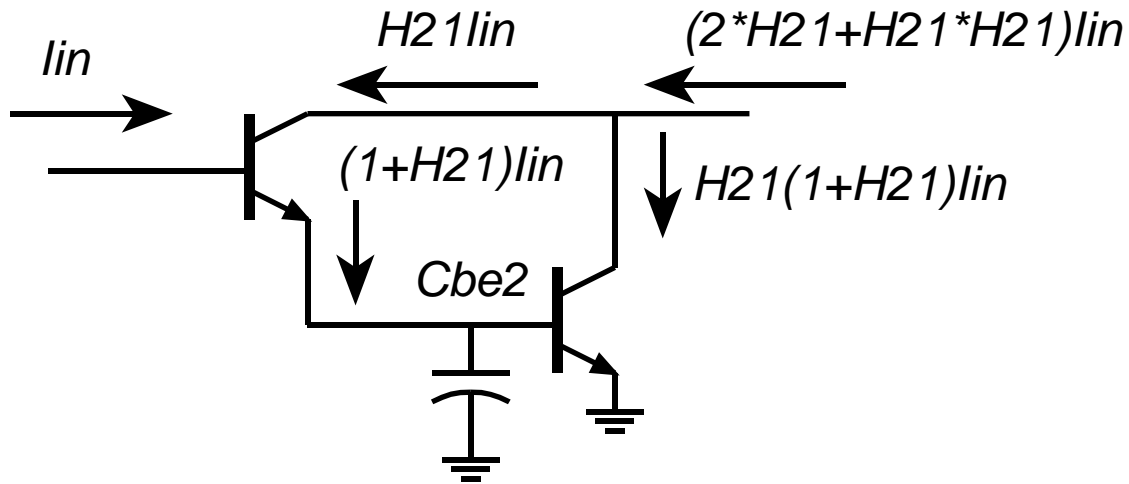ft-doubler vs Darlington...thinking in terms of current gains:



Current gain is $I_{out} / I_{in} = 2H_{21} + (H_{21})^2$ where $H_{21} = f_{\tau} / jf$


Since $I_{out} = I_{c1} + I_{c2} = g_m V_{be1} + g_m V_{be2} = g_m (V_{be1} + V_{be2}) = g_m V_{in}$

$$I_{in} / V_{in} = Y_{in} = \frac{g_m}{2H_{21} + (H_{21})^2} = \frac{g_m}{2(f_{\tau} / jf) + (f_{\tau} / jf)^2} = \dots$$

Current gain varies at lower frequencies as $(f_{\tau} / jf)^2$

which gives high current gain but negative input conductance

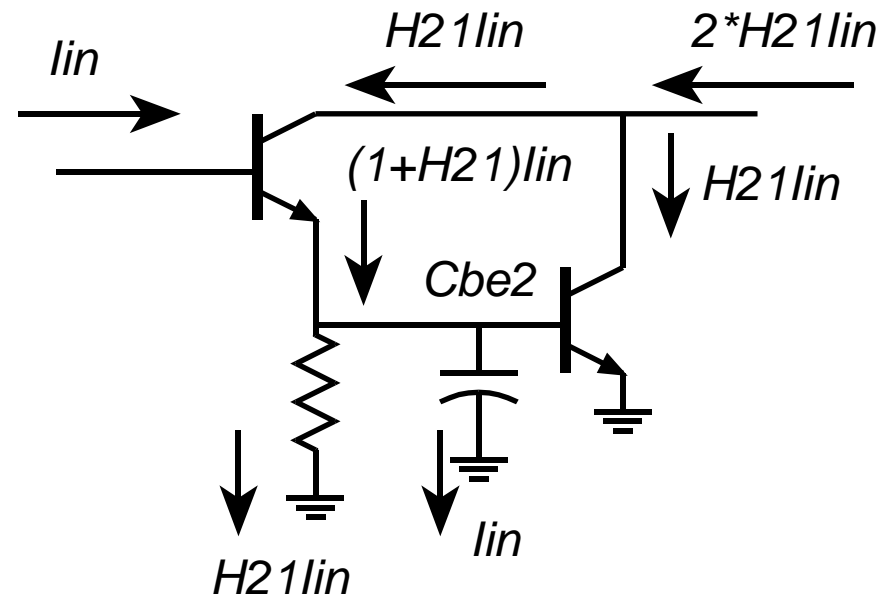ft-doubler vs Darlington...thinking in terms of current gains:




Current gain is $I_{out} / I_{in} = 2H_{21}$ where $H_{21} = f_{\tau} / jf$

Since $I_{out} = I_{c1} + I_{c2} = g_m V_{be1} + g_m V_{be2} = g_m (V_{be1} + V_{be2}) = g_m V_{in}$


$$I_{in} / V_{in} = Y_{in} = \frac{g_m}{2H_{21}} = \frac{g_m}{2(f_{\tau} / jf)} = \frac{jfg_m}{2f_{\tau}} = jf(2\pi C_{be} / 2)$$

Current gain varies at all frequencies as $(2f_{\tau} / jf)$

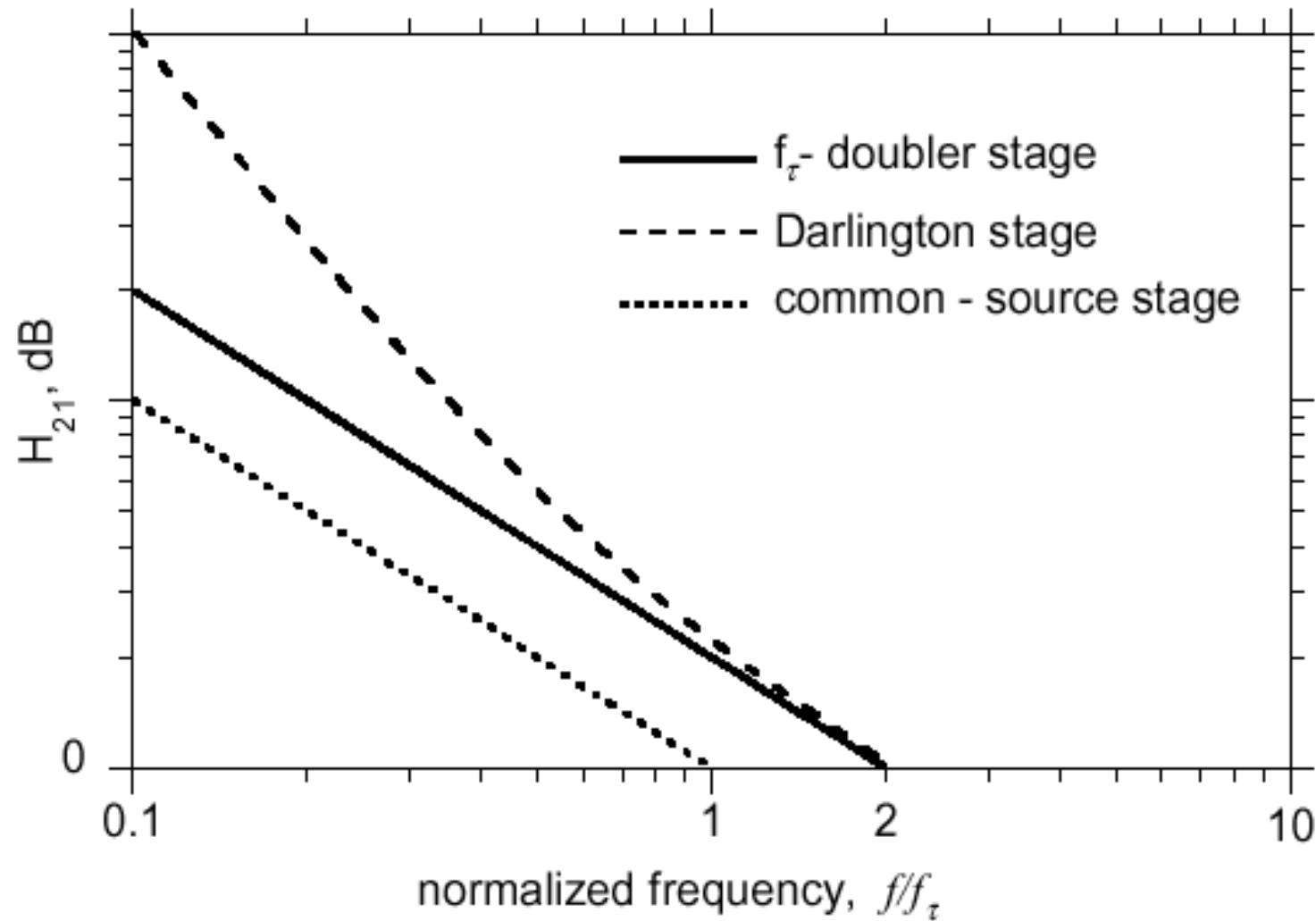ft-doubler vs Darlington...current gains:



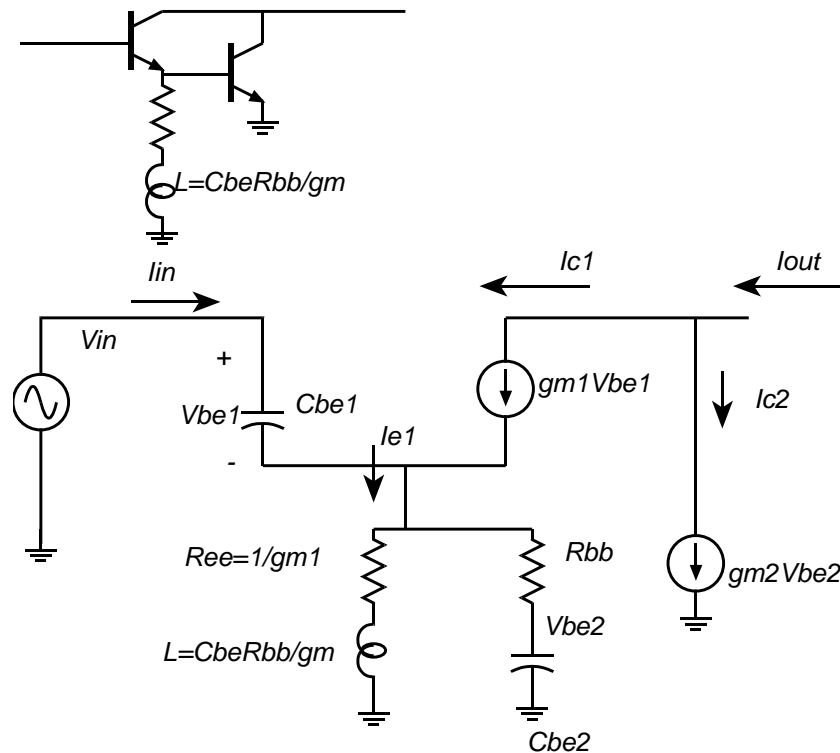ft-doubler ...correction for Base resistance




The indicated inductance is necessary for equal current splitting between the 2 transistors in the presence of R_{bb} . In this case the input impedance is $C_{be}/2$ in series with $R_{bb}/2$...again note that this correction is significant because $R_{bb}C_{be} \gg C_{be}/g_m$

ft-doubler vs Darlington

What is the conclusion of all this ? We can view the ft-doubler as a special case of the connected-collector Darlington with heavy emitter-follower loading: in this case the second-order (resonant) response is entirely suppressed. More generally we might vary the EF loading to vary the damping. (The particular case of power amplifiers favors the ft-doubler due to efficiency reasons...)

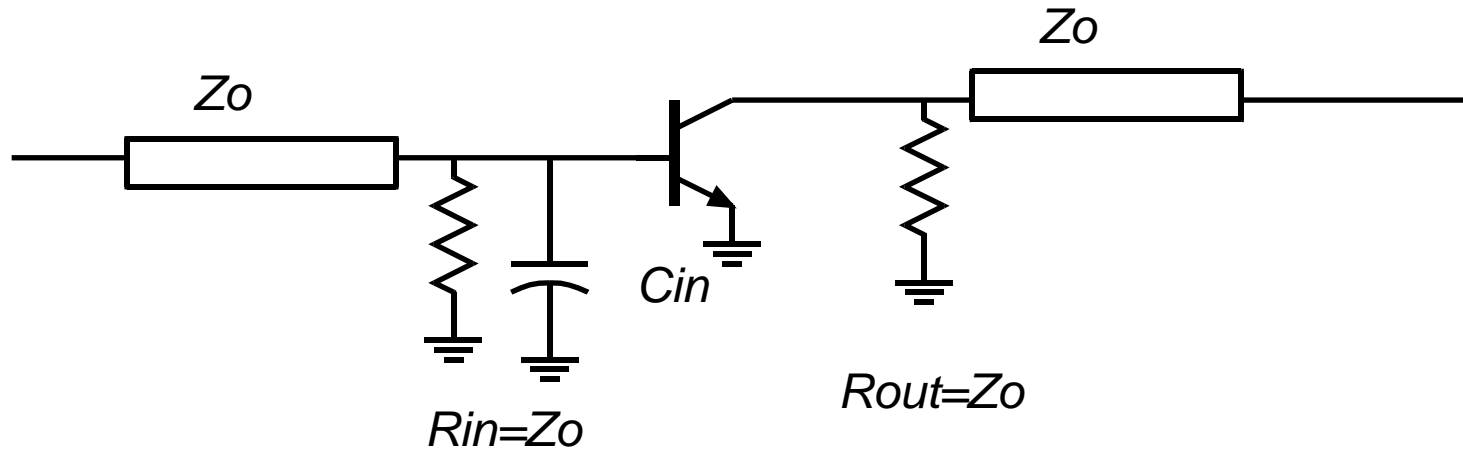Tuning: to prevent reflections, to peak gain




$$S_{21} = \frac{-g_m Z_o / 2}{1 + j\omega C Z_o / 2}$$

$$S_{11} = \frac{j\omega C Z_o / 2}{1 + j\omega C Z_o / 2}, \text{ where } Z_{in} = \left(Z_o \parallel \frac{1}{j\omega C} \right)$$

The input capacitance has hurt both S_{11} and S_{21} ,
input match and gain

Pi-section input tuning....

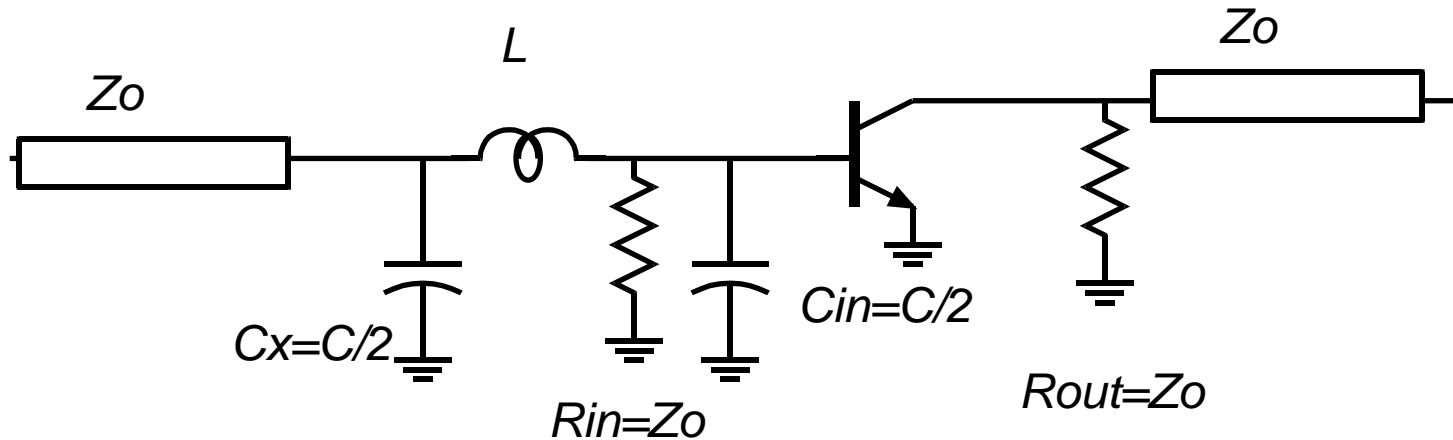

Absorb the transistor input capacitance into a pi - section

$$C_{in} = C_{be} = C/2 = \tau / Z_o 2$$


$$L = \tau Z_o = (2C_{in} Z_o) Z_o$$

Effective for frequencies such that the pi - section is short

(hence $f_0 < 1 / \pi Z_o C$)

Gain flatness and match improved for $f < f_0$, but made worse for $f > f_0$

T-section input tuning....

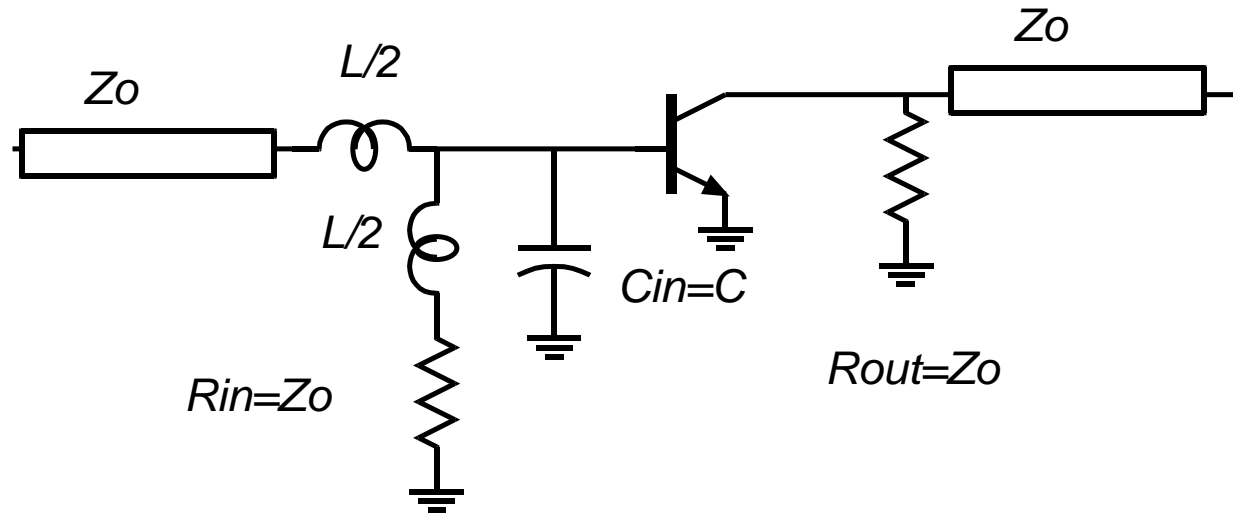

Absorb the transistor input capacitance into a T - section


$$C_{in} = C_{be} = C = \tau / Z_o$$

$$L = \tau Z_o = (2C_{in} Z_o) Z_o$$

Effective for frequencies such that the pi - section is short
(hence $f_0 < 1 / \pi Z_o C$)

Note that for a given C_{in} , we have doubled f_0 relative to the pi - section case...

T-section tuning in feedback amplifiers

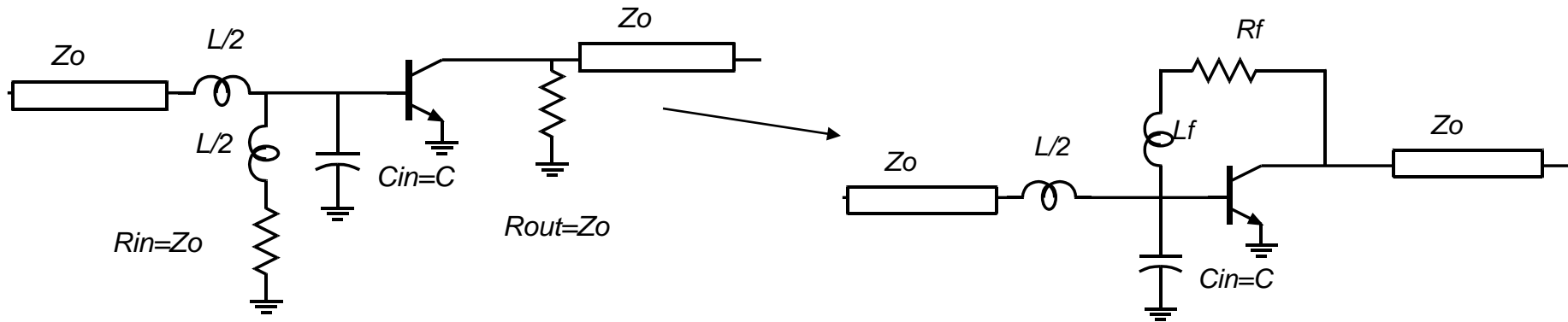


By Miller Approximation :

$$R_f = Z_o(1 - A)$$

$$L_f = (L/2)(1 - A)$$

This is frequently used in 50 Ohm FBAs...danger is reduced stability.

Bridged-T-section input tuning....


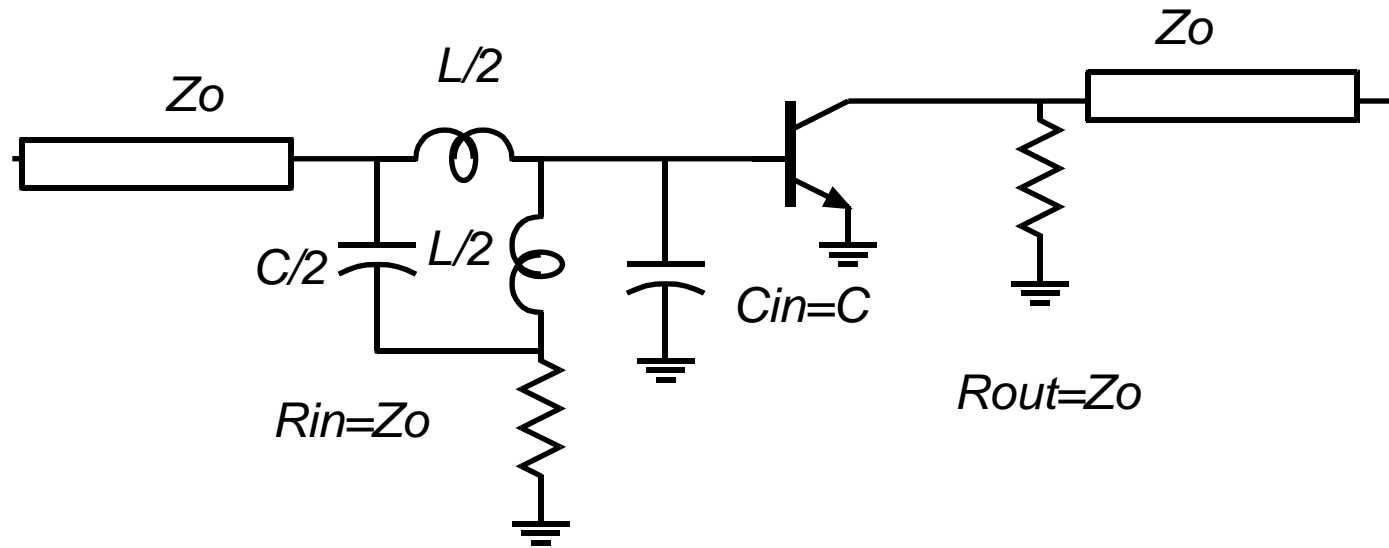


$$C_{in} = C_{be} = C = \tau / Z_o$$

$$L = \tau Z_o = (2C_{in} Z_o) Z_o$$

Insofar as the transistor has an input impedance modeled by C_{be} , S_{11} is exactly zero. S_{21} nevertheless rolls off at about the same frequency as the T-section case...

Bridged-T-section input tuning....

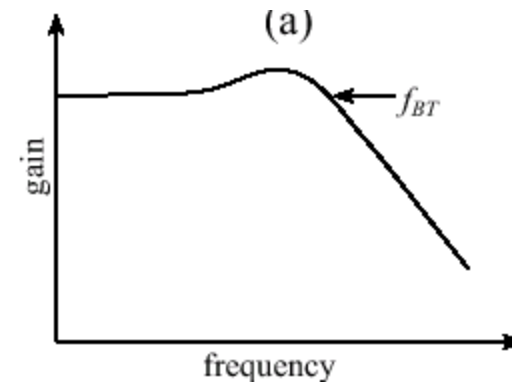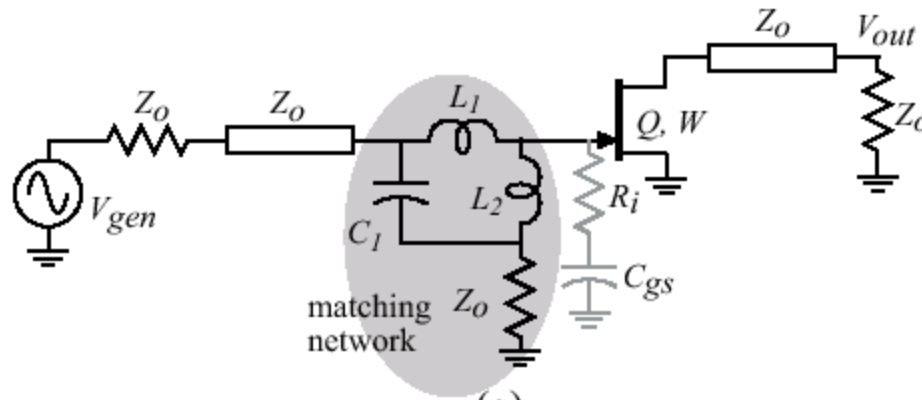





$$\begin{aligned}
 L_1 &= (Z_o - R_i)Z_o C_{gs}/2, \\
 L_2 &= (Z_o + R_i)Z_o C_{gs}/2, \\
 C_1 &= (1 - R_i^2/Z_o^2)C_{gs}/4.
 \end{aligned} \tag{3.19}$$

The mid-band voltage gain and transducer power gain are same as the common source case (eq. 3.7), but the amplifier exhibits a gain peaking and the gain falls to the low frequency value at


$$\Delta f_{BT} = \frac{1}{\pi Z_o C_{gs}} \sqrt{\frac{(1 - 3(R_i/Z_o))}{(1 - (R_i/Z_o))(1 - (R_i/Z_o)^2)}} \simeq \frac{1}{\pi Z_o C_{gs}}, \tag{3.20}$$

for $R_i \ll Z_o$. Note that the -3 dB bandwidth is somewhat larger than Δf_{BT} (exact expressions for f_{3dB} are intractable).

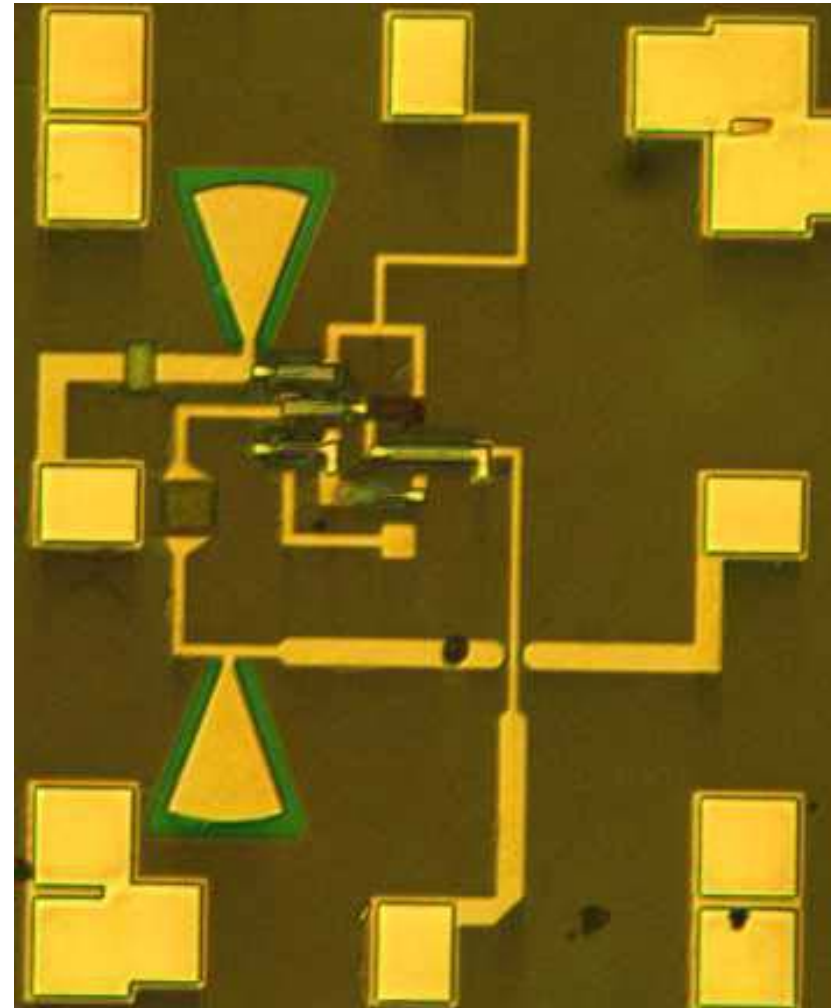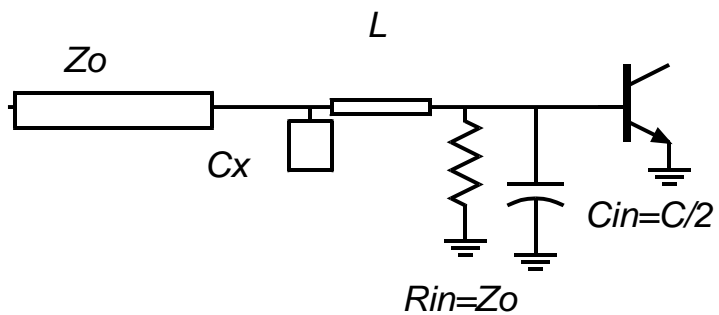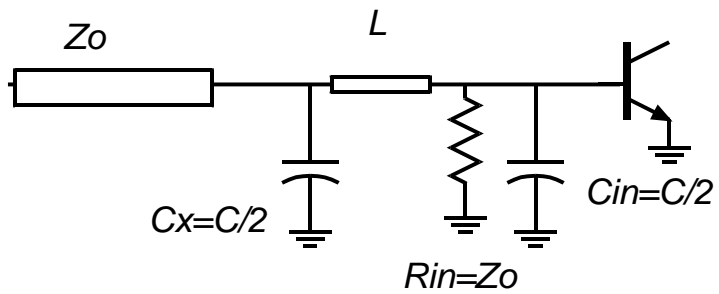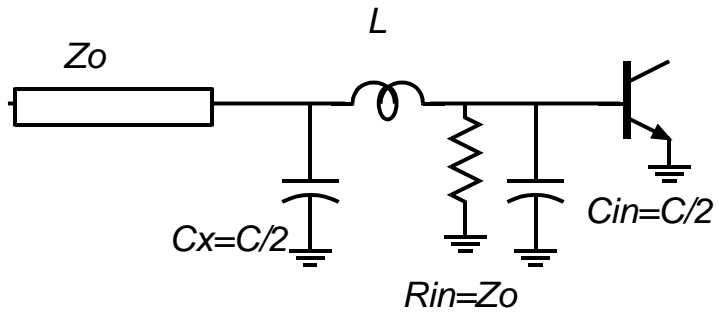Tuning Networks use Microstrip elements...




Distributed Amplifiers : Theory

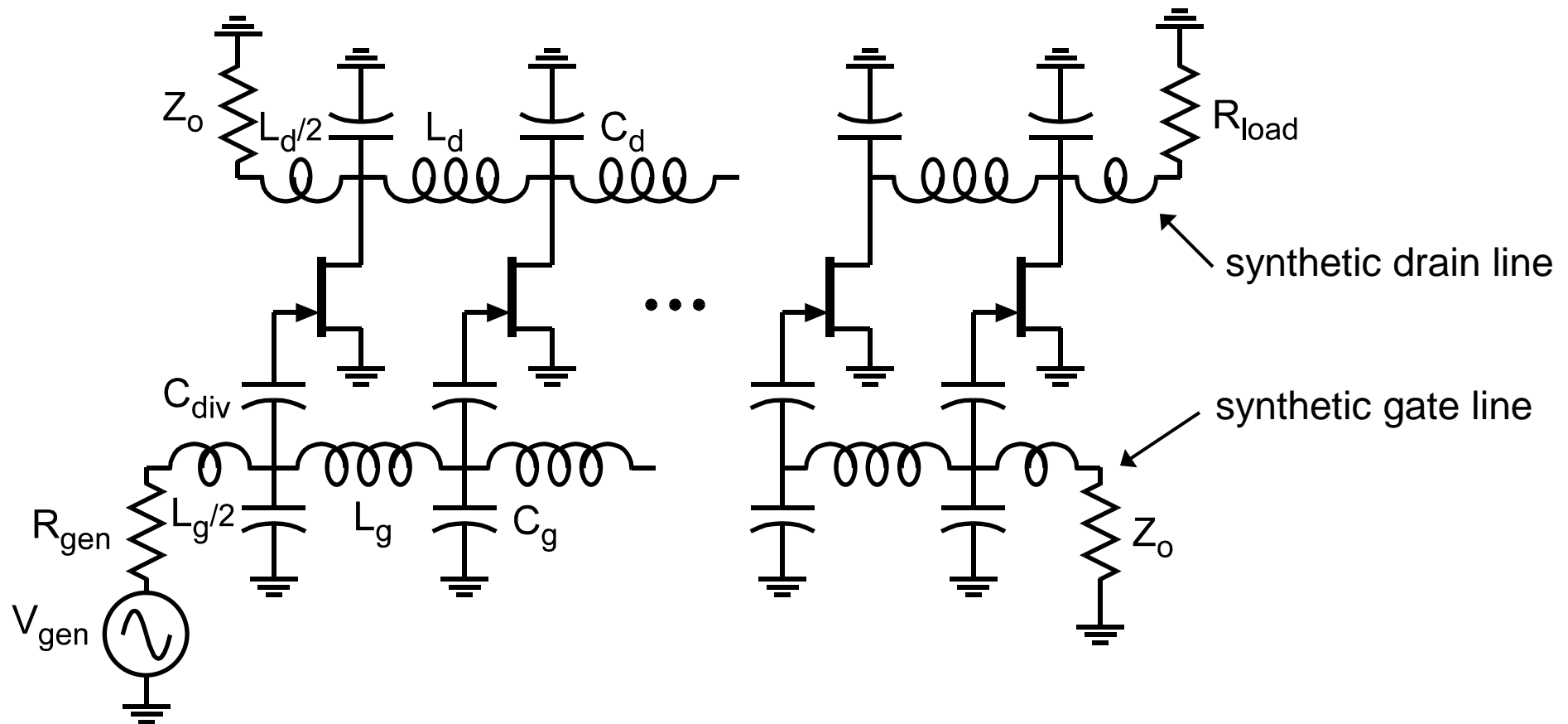

- HEMT input/output capacitances absorbed into artificial input/output lines
- broadband circuit ; gain/bandwidth limited by
 - HEMT resistive parasitics (f_{max})
 - distributed structure Bragg frequency
 - input/output transmission line skin-effect losses


Synthetic Transmission Lines

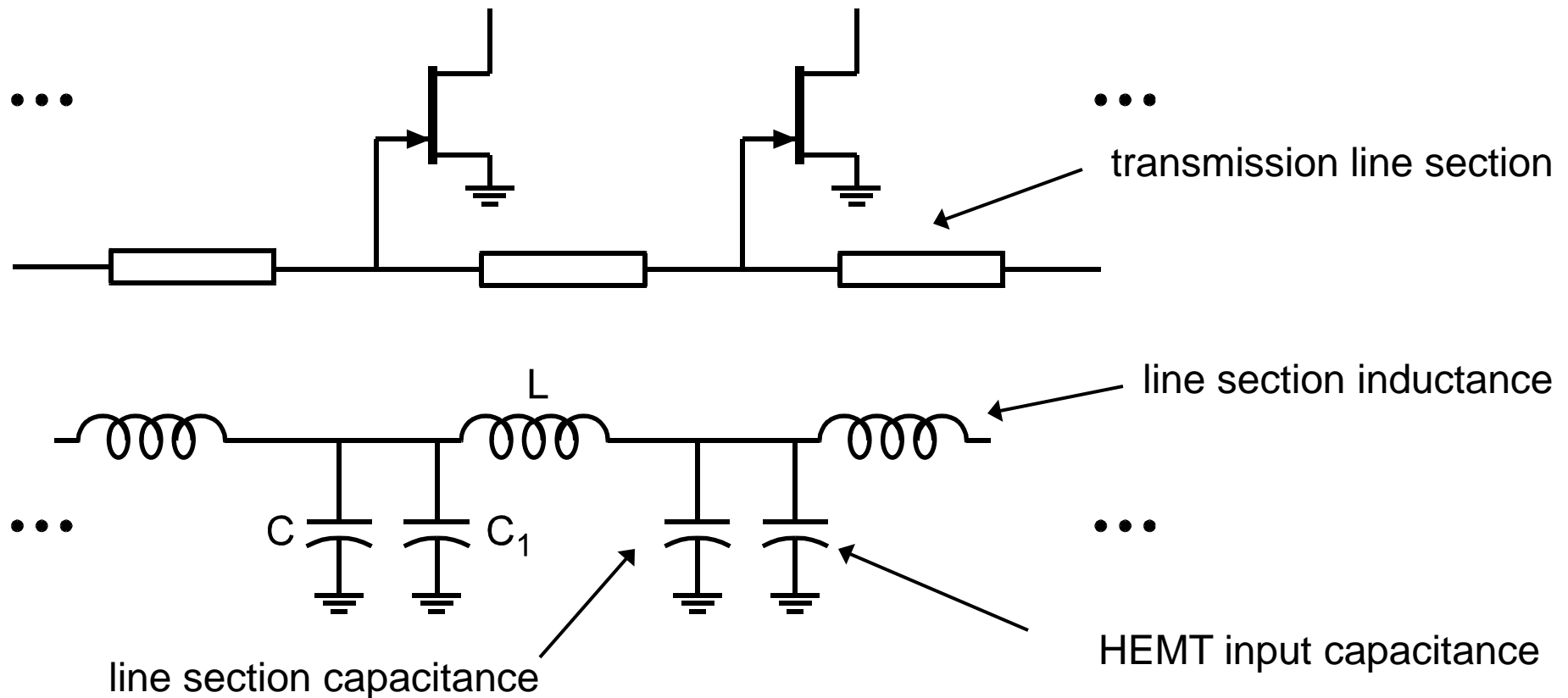


- synthetic input/output line formed by transmission line sections
- transmission line

characteristic impedance	$Z = \sqrt{L/C}$
cutoff (Bragg) frequency	$f_B = 1/\pi\sqrt{LC}$
delay	$T = \sqrt{LC}$

Transmission Line Loss

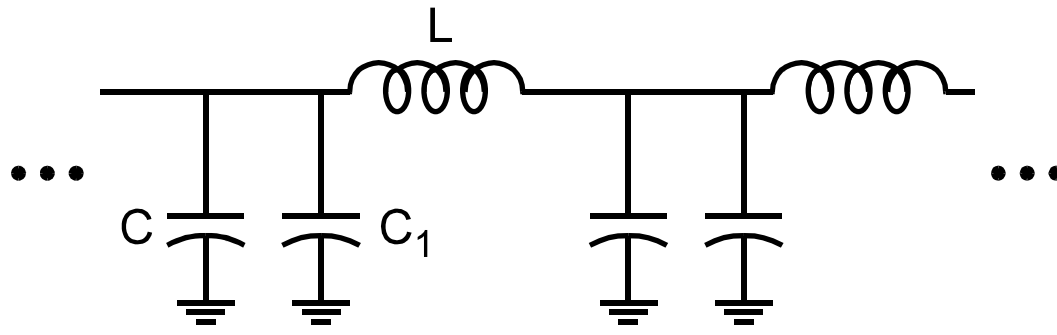


lossless line

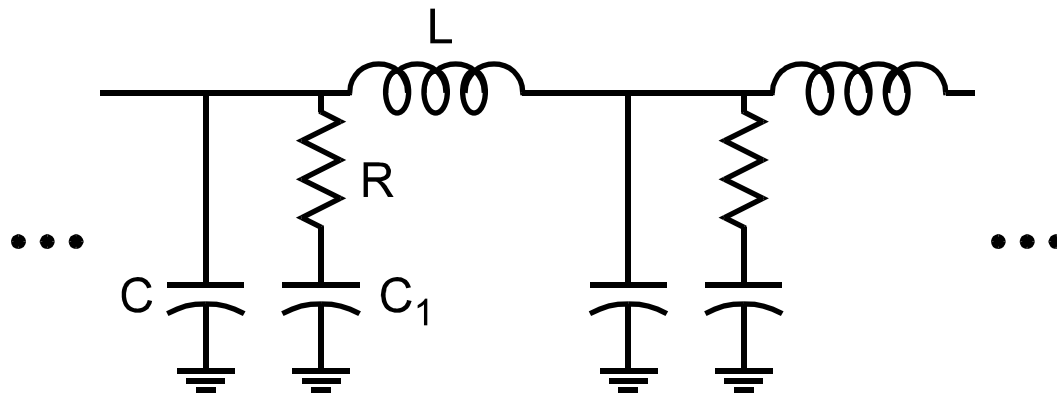

frequency-dependent loss


$$\alpha = 4\pi^2 f^2 C_1^2 R Z_0 / 2$$

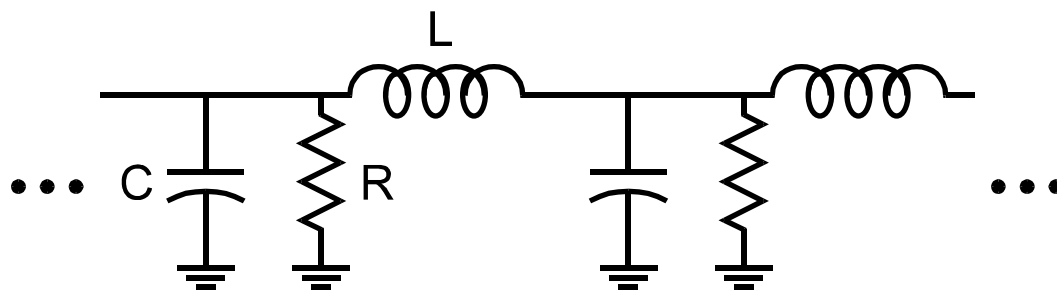

frequency-independent loss

$$\alpha = Z_0 / 2R$$


HEMT Equivalent Circuit

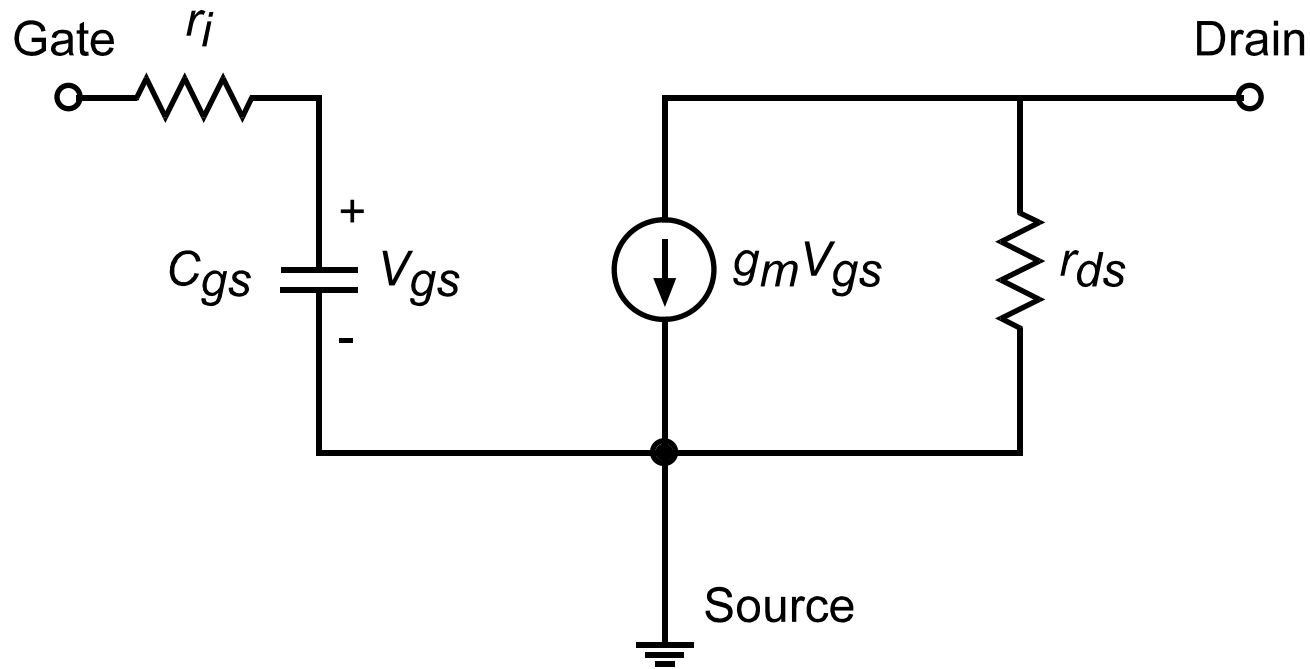


- simplified equivalent circuit
- element values scale with HEMT size

- $f_{\tau} = g_m / 2\pi C_{gs}$ $f_{\max} = f_{\tau} \sqrt{r_{ds} / 4r_i}$


CS HEMT TWA

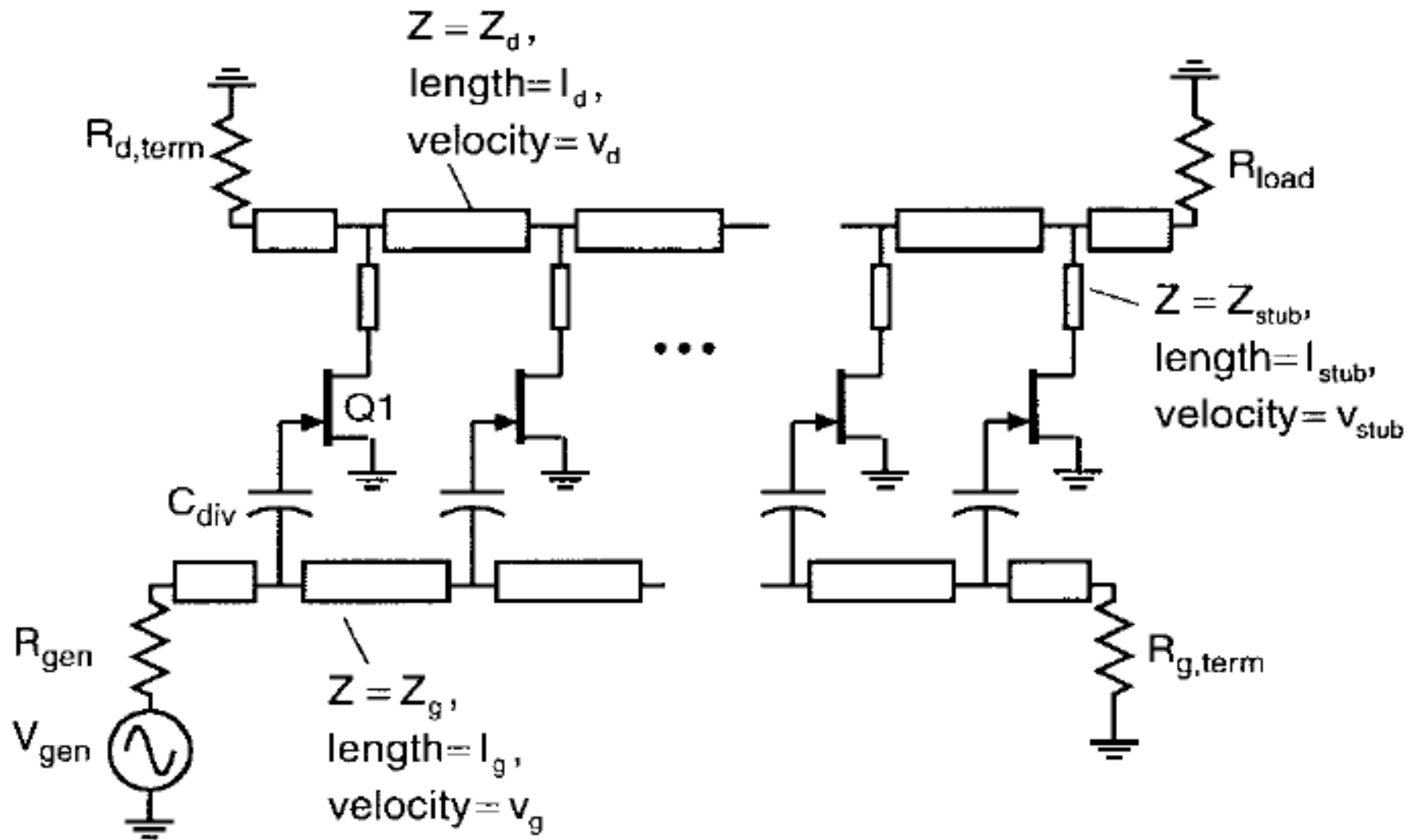

CS HEMT TWA--LC equivalent

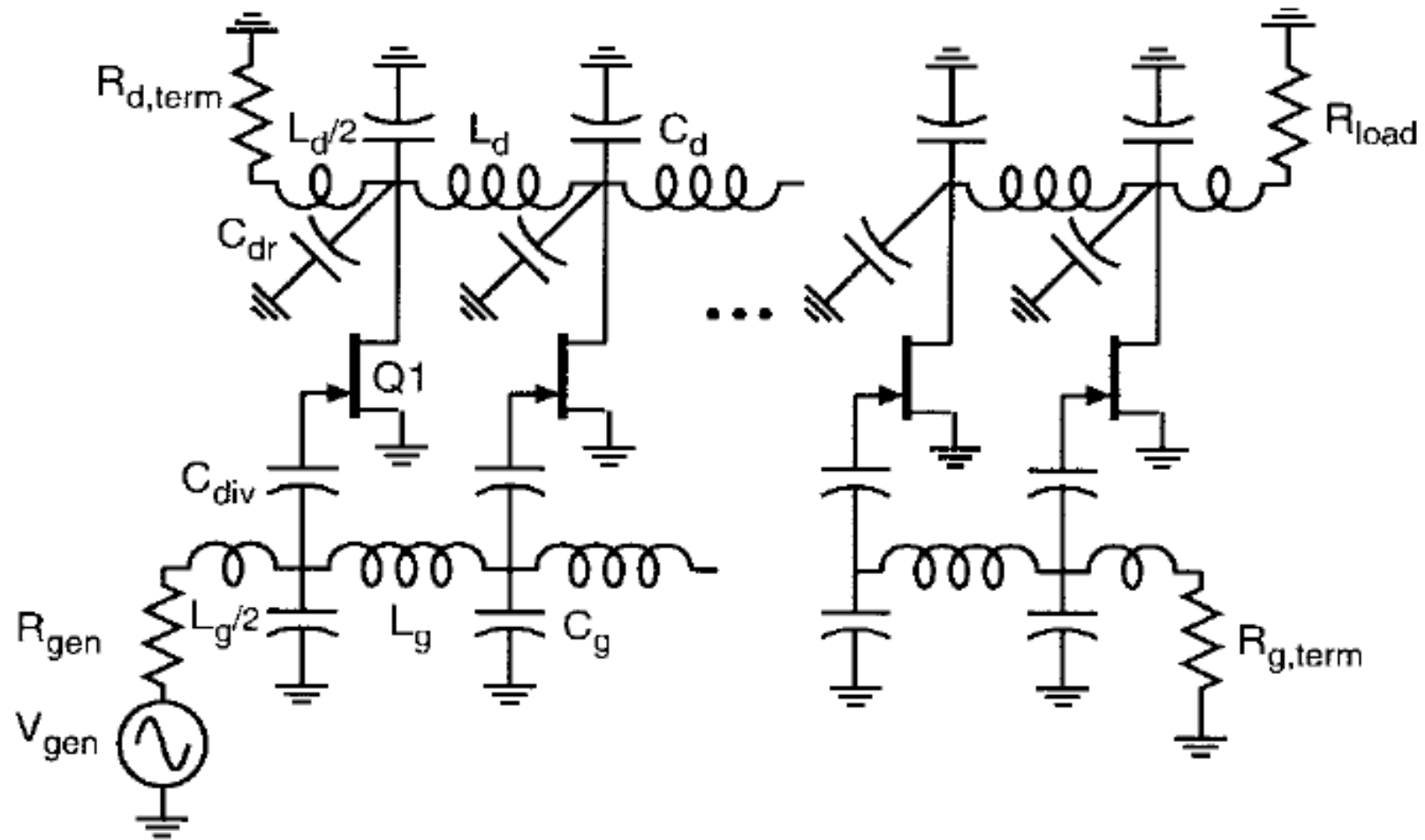

CS HEMT TWA--SS model

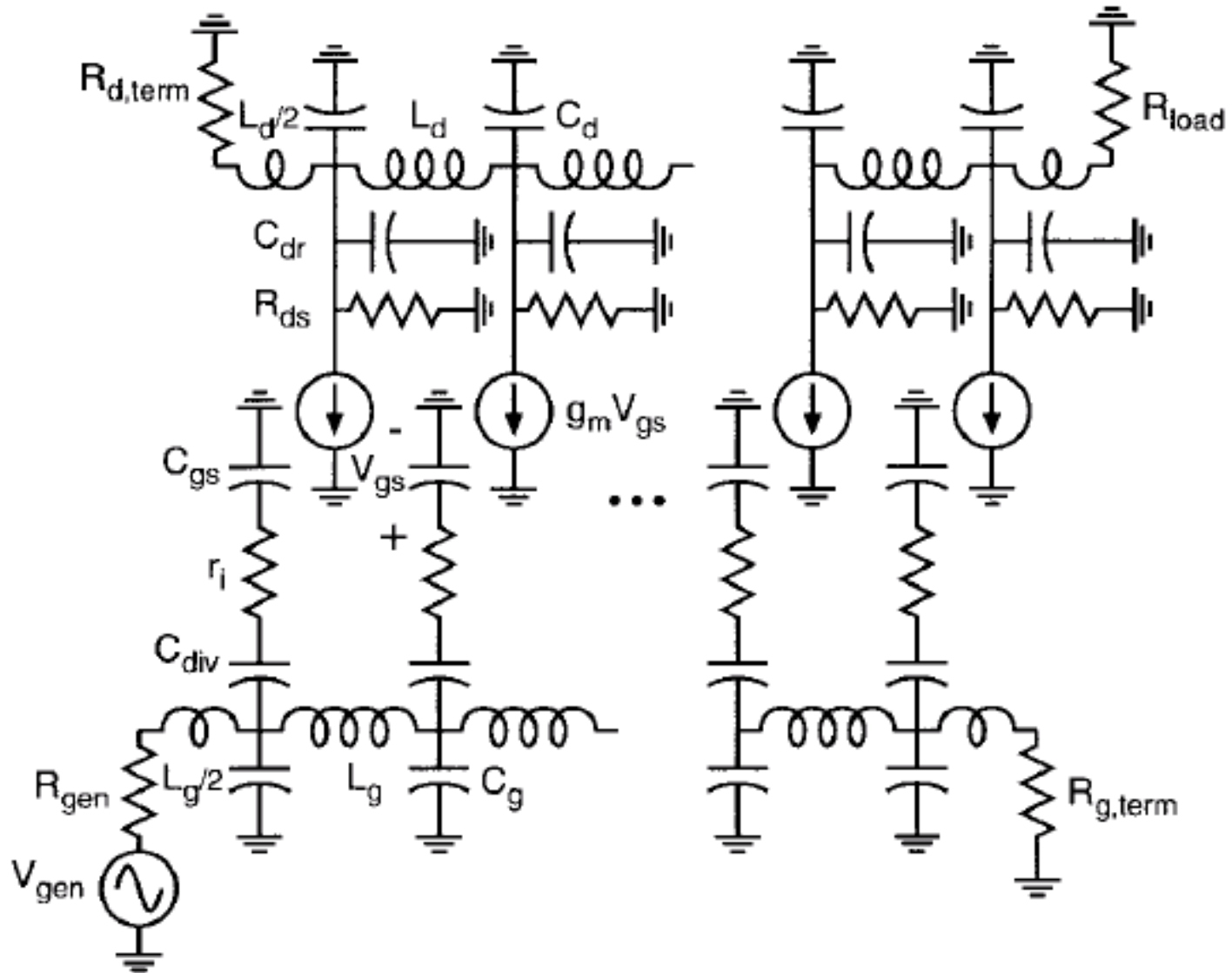

TWA...limits to gain and bandwidth...

Gate (input)line loss :

$N\alpha_g < 1/2$...sets a high frequency limit because $\alpha_g = \omega^2 C^2 R_i$...

Drain (output) Line Loss

$N\alpha_d < 1/2$...sets a gain limit because $\alpha_d = Z_o / 2R_{ds}$

Input - Output Delay Mismatch

$N(T_{gate} - T_{drain}) < 90^\circ$...just requires we get design right...

Low - Frequency Gain




$S_{21} = Ng_m (Z_o / 2)$ (capacitive degeneration ratio)

...together with above limits, sets feasible gain - bandwidth




Bragg Frequency

$f < 1 / \pi \sqrt{LC}$...can be made very high with lots of very small transistors....no problem...

Undamped Darlington FBA

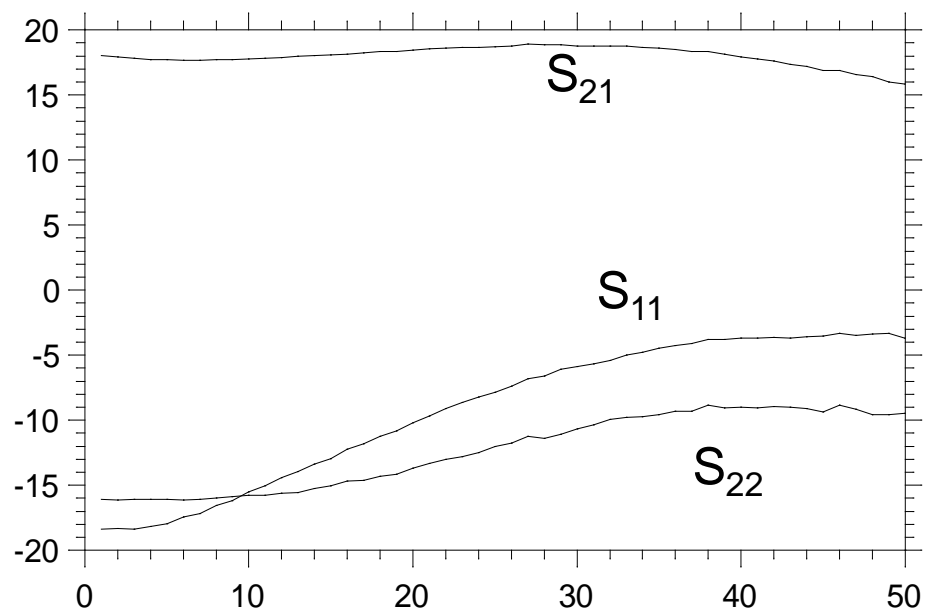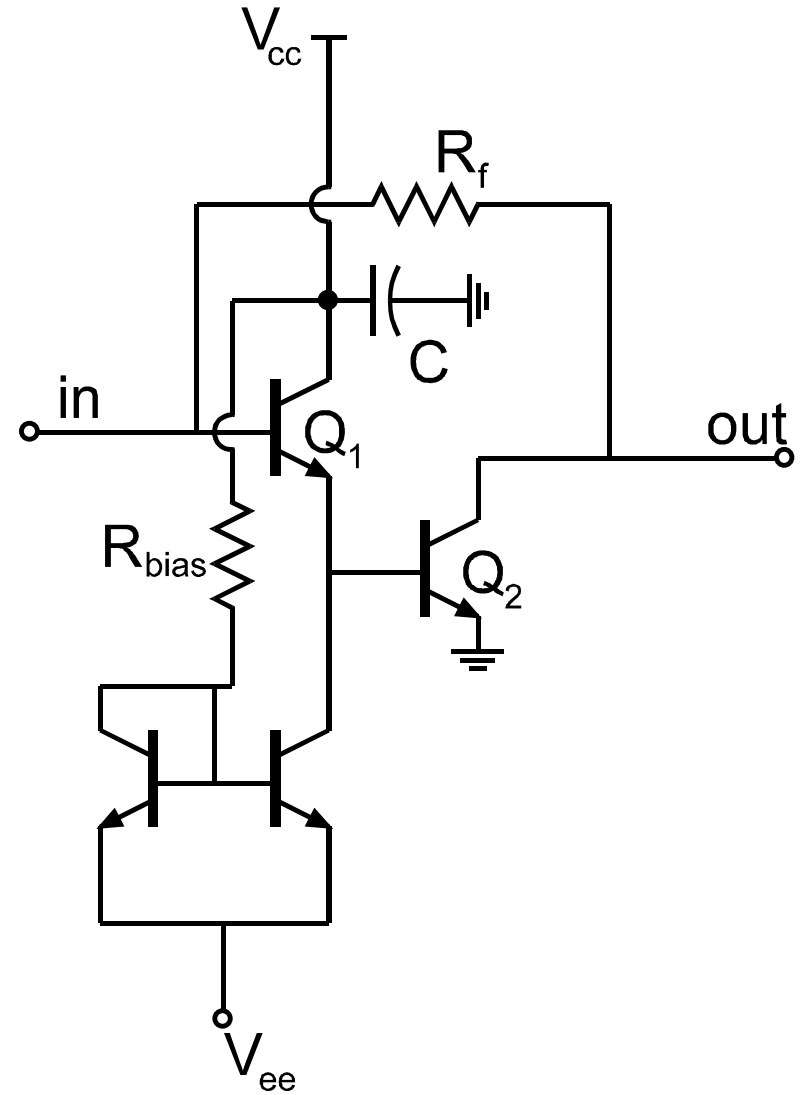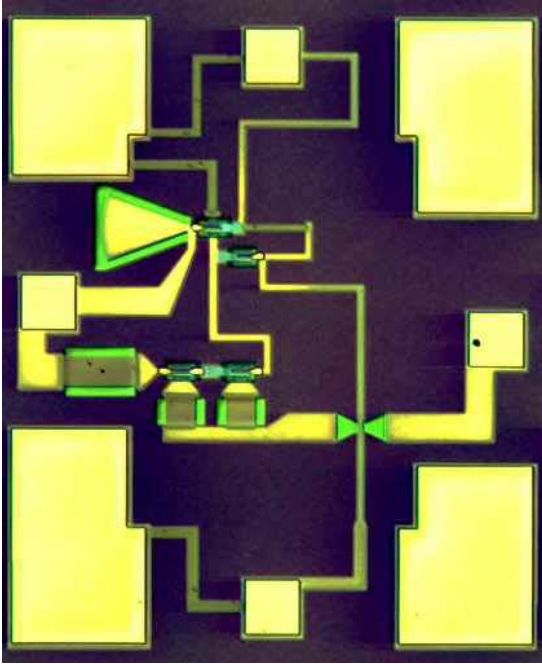

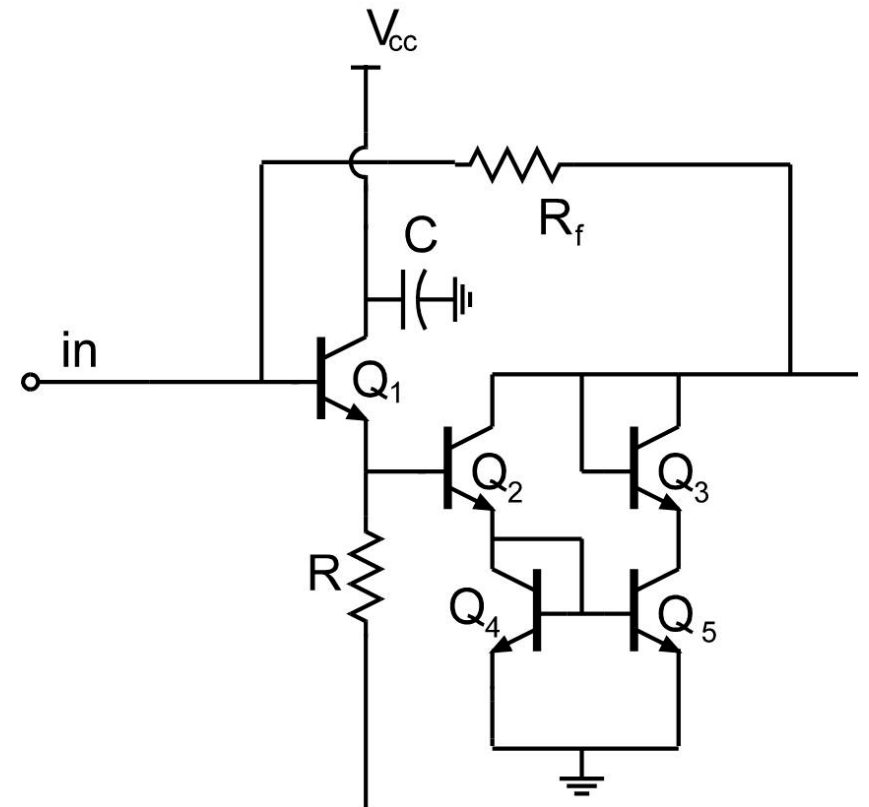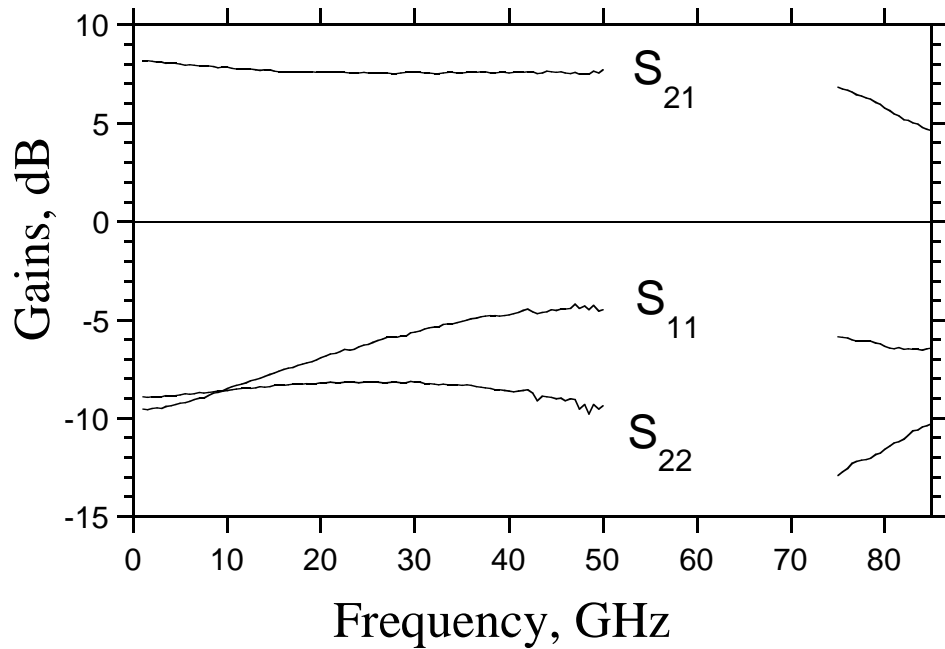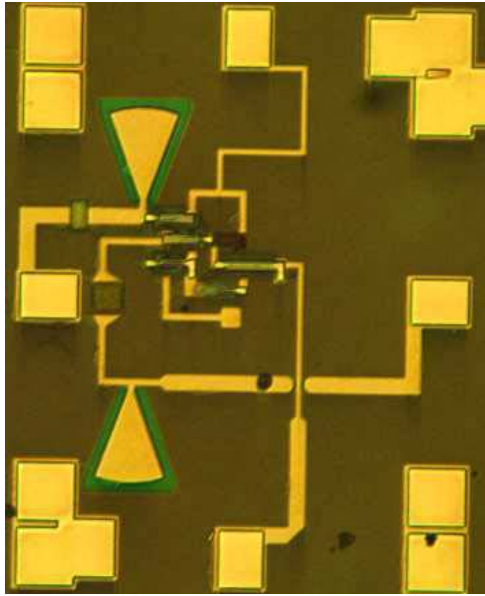Feedback Amplifier with Follower Driving ft-doubler



80 GHz HBT Distributed Amplifier

