

# ***100-1000 GHz Bipolar ICs: Device and Circuit Design Principles***

***Mark Rodwell, UCSB  
Munkyo Seo, Teledyne Scientific***

---

***Collaborators:***

***Teledyne HBT Team:***

***M. Urteaga, R. Pierson, P. Rowell, B. Brar, Teledyne Scientific Company***

***Teledyne IC Design Team:***

***J. Hacker, Z. Griffith, A. Young, M. J. Choe, Teledyne Scientific Company***

***UCSB HBT Team:***

***V. Jain, E. Lobisser, A. Baraskar, J. Rode, H.W. Chiang, A. C. Gossard, B. J. Thibeault, W. Mitchell***


***UCSB IC Design Team:***

***S. Danesgar, T. Reed, Eli Bloch, H-C Park, J-H Kim***

# ***Motivation / Overview***


# DC to Daylight. Far-Infrared Electronics

 **How high in frequency can we push electronics ?**




**...and what would be do with it ?**

 
**0.3-3 THz radio: vast capacity bandwidth, # channels**




**0.3- 3 THz imaging systems**

 

**0.1-1 Tb/s optical fiber links**

 

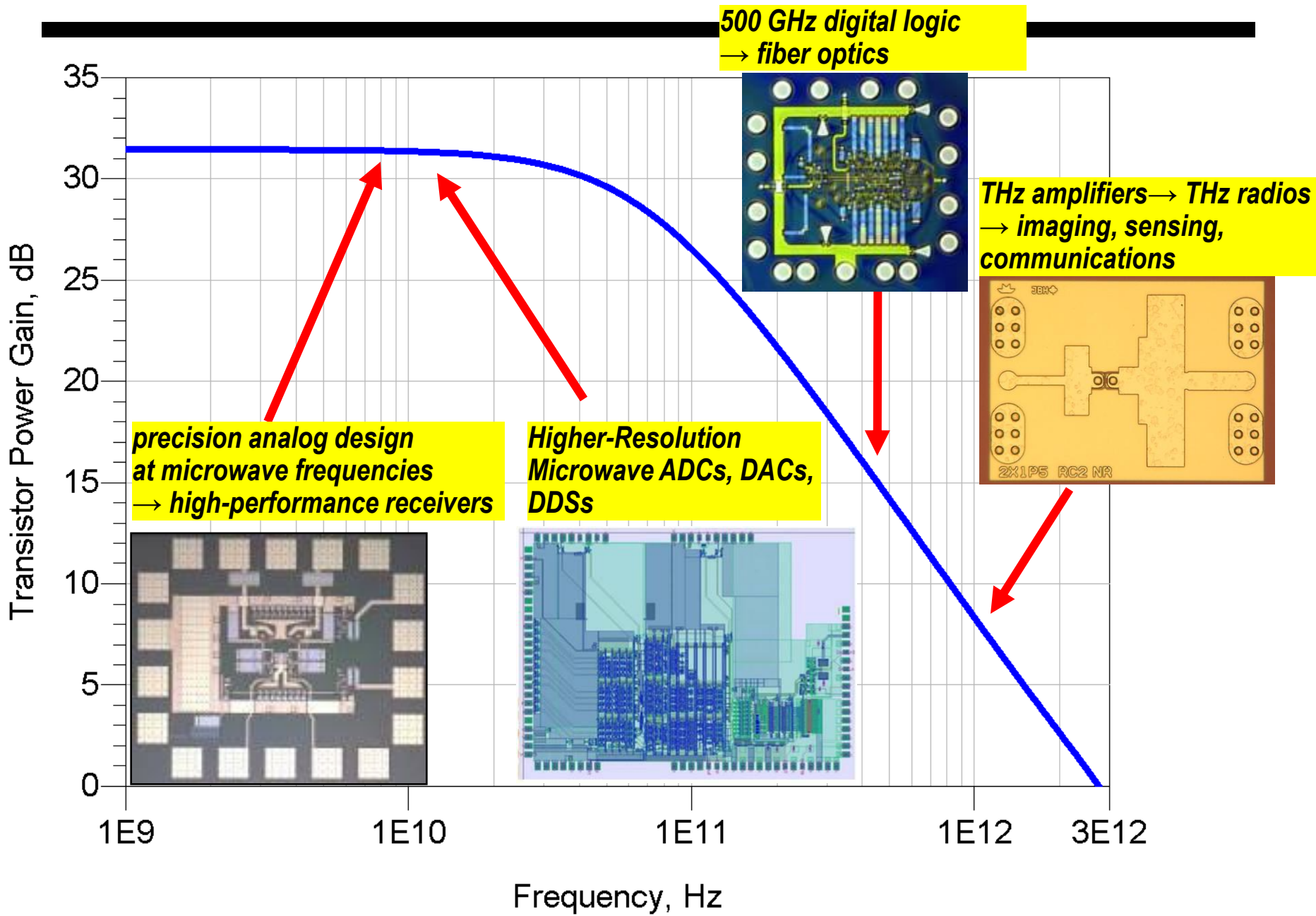
# THz Transistors: Not Only For THz Circuits



# ICs to 600 GHz : Teledyne and UCSB


## 570 GHz fundamental VCO

M. Seo, TSC  
CSIC 2010

 


## 430 GHz low-noise amplifier

M. Seo, TSC  
other ICs by J. Hacker

 


## 204 GHz static frequency divider (ECL master-slave latch)

Z. Griffith, TSC  
CSIC 2010

 


## 340 GHz dynamic frequency divider

M. Seo, TSC  
IEEE MWCL 2010

 


## 300 GHz fundamental PLL

M. Seo, TSC  
IMS 2011

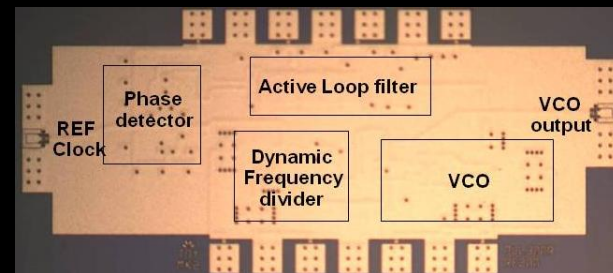


## 40 GHz op-amp with 54 dBm IP3 at 2 GHz

Z. Griffith, TSC  
IMS 2011

 

## 220 GHz 48 mW power amplifier

T. Reed, UCSB  
CSIC 2011

 


## Other ICs in design:

30-40 GS/s track/hold  
optical PLLs  
coherent optical receivers  
340 GHz arrays



# At High Frequencies The Atmosphere Is Opaque


Mark Rosker  
IEEE IMS 2007

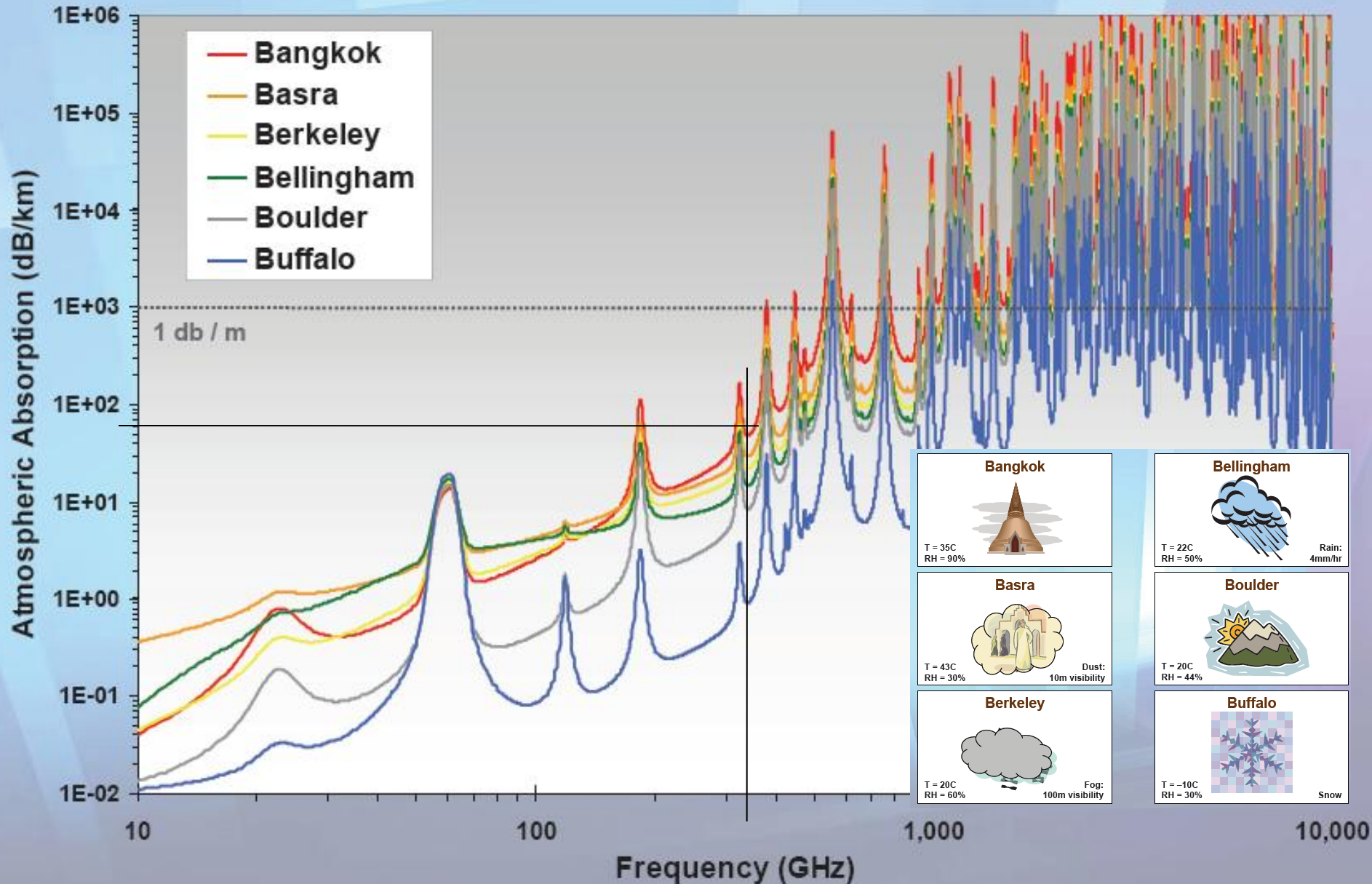
 
# THz Bipolar Transistors: Where Next ?




array transmitters: critical for sub-mm-wave radio / radar

$$\frac{P_{received}}{P_{transmit}} = \frac{N_{receive} N_{transmit}}{16} \frac{\lambda^2}{R^2} e^{-\alpha R}$$



32 x 32 array → 60-90 dB increased SNR → vastly increased range

 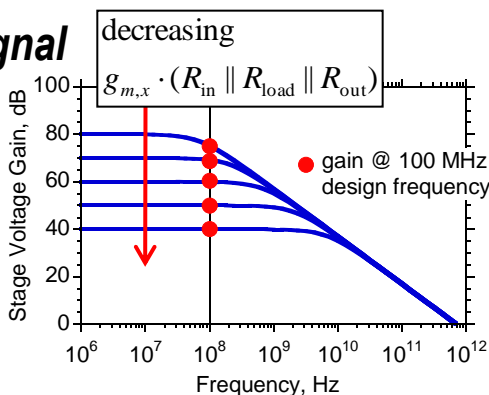 
## HBT / HEMT integration for mixed-signal



III-V NFET vs. Si PFET  
active loads:  
much lower  $C_{load}/I_{bias}$

LSI @ 128 nm node:  
scaled interconnects  
high packing density  
→ speed, power

## 32 nm / 3 THz node, beyond

 



## Transition to production

R&D → pilot → foundry  
design tools, reliability, scaled interconnects  
CMOS control integration: 3-D, flip chip

***Bipolar Transistors:  
Models,  
Scaling Laws,  
State of Art,  
Roadmaps***



# Bipolar Transistor: Structure & Models

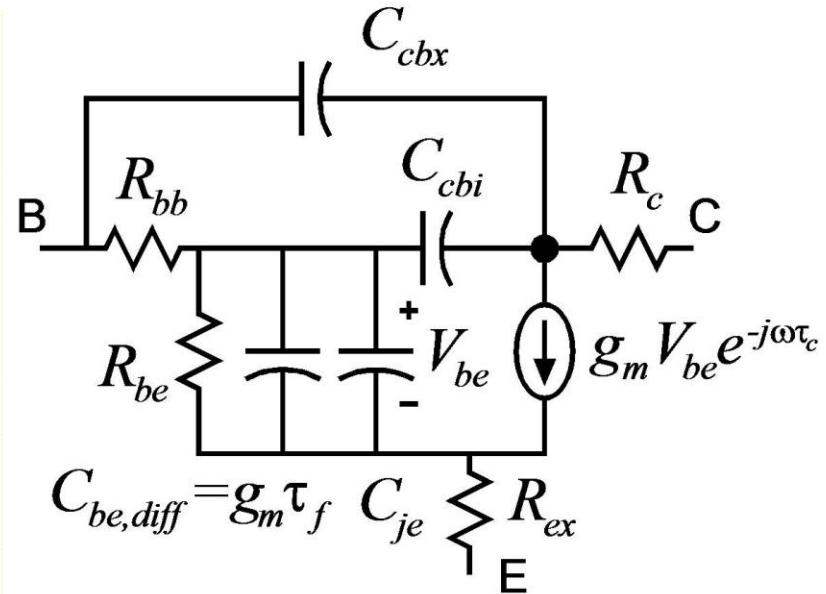 

$$R_{be} = \beta / g_m$$

$$g_m = qI_E / nkT$$


$$C_{be} = C_{je} + g_m (\tau_b + \tau_c)$$

$$\tau_b \approx T_b^2 / 2D_n + T_b / v_{thermal}$$

$$\tau_c \approx T_c / 2v_{sat}$$

$$\frac{1}{2\pi f_\tau} = \tau_{base} + \tau_{collector} + C_{je} \frac{nkT}{qI_E} + C_{bc} \left( \frac{nkT}{qI_E} + R_{ex} + R_{coll} \right)$$
 
# Base-Collector Distributed RC Parasitics



$$R_{ex} = \rho_{contact,emitter} / A_{emitter}$$

$$R_{spread} = \rho_s W_e / 12 L_E$$

$$R_{gap} = \rho_s W_{gap} / 4 L_E$$

$$R_{spread,contact} = \rho_s W_{bc} / 6 L_E$$

$$R_{contact} = \rho_{contact,base} / A_{base\_contacts}$$

$$C_{cb,e} = \epsilon A_{emitter} / T_c$$

$$C_{cb,gap} = \epsilon A_{gap} / T_c$$

$$C_{cb,contact} = \epsilon A_{base\_contacts} / T_c$$

# $R_{bb}C_{cb}$ Time Constant, $f_{max}$ , Simple Hybrid- $\pi$ model


Vaidyanathan & Pulfrey  
IEEE Trans. Elect. Dev.  
Feb. 1999

$f_{max} \cong \sqrt{f_{\tau} / 8\pi R_{bb} C_{cbi}}$  where

$$\tau_{cb} = R_{bb} C_{cbi} = C_{cb,contact} R_{contact}$$

$$+ C_{cb,gap} (R_{contact} + R_{spread,contact} + R_{gap} / 2)$$

 
$$+ C_{cb,e} (R_{contact} + R_{spread,contact} + R_{gap} + R_{spread})$$



$R_{bb}$  = true total base resistance

$C_{cbi} + C_{cbx}$  = true total  $C_{cb}$

 $C_{cbi} : C_{cbx}$  ratio set to fit  $f_{max}$  from above



# Key 2<sup>nd</sup>-Order Effects in III-V HBTs: Omitted for Brevity

Current - induced velocity overshoot : decreases  $\tau_c$

*Nakajima, Japanese Journal of Applied Physics, Feb. 1997*

Voltage modulation of collector velocity : increases  $\tau_c$

Partial  $C_{cb}$  cancellation by collector velocity modulation.




*Betser and Ritter, IEEE Trans. Elect. Dev., April 1999*

*Urteaga & Rodwell, IEEE Trans. Elect. Dev., July 2003*

Degenerate electron injection into base : increases  $R_{ex}$

*Rodwell, Le, Brar, Proc IEEE, February 2008*

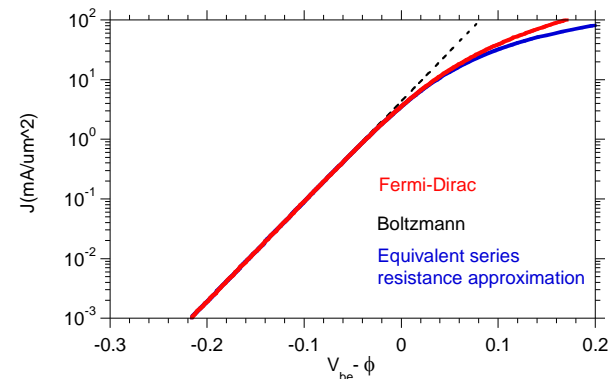 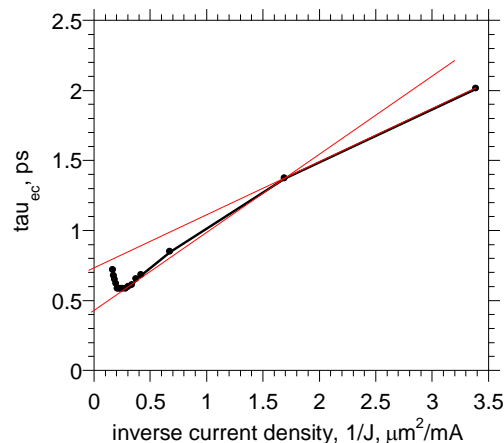*Jain & Rodwell, IEEE Electron. Dev. Lett., to be published (2011)*





More detailed information regarding III-V bipolar transistor physics and design:

[http://www.ece.ucsb.edu/Faculty/rodwell/publications\\_and\\_presentations/publications/2009\\_may\\_IPRM\\_short\\_course\\_rodwell.pdf](http://www.ece.ucsb.edu/Faculty/rodwell/publications_and_presentations/publications/2009_may_IPRM_short_course_rodwell.pdf)

# Space Charge, Kirk Effect, Minimum $C_{cb}$ charging time



## SiGe HBT

## InP DHBT

  
  
## Collector Depletion Layer Collapse

$$V_{cb,\min} + \phi > +(qN_d)(T_c^2 / 2\epsilon)$$



## Collector Field Collapse

$$V_{cb} + \phi > +(J / v_{sat} - qN_d)(T_c^2 / 2\epsilon)$$

$$\Rightarrow J_{\max} = 2\epsilon v_{eff} (V_{cb} + V_{cb,\min} + 2\phi) / T_c^2$$

Note that  $V_{be} \cong \phi$ , hence  $(V_{cb} + \phi) \cong V_{ce}$



$$C_{cb} \Delta V_{LOGIC} / I_C = (\epsilon A_{\text{collector}} / T_c) (\Delta V_{LOGIC} / I_C) = \frac{\Delta V_{LOGIC}}{(V_{CE} + V_{CE,\min})} \left( \frac{A_{\text{collector}}}{A_{\text{emitter}}} \right) \left( \frac{T_C}{2v_{eff}} \right)$$

Collector capacitance charging time **minimized** by setting  $J = J_{\max}$   
 ...if so, charging time **scales linearly** with collector thickness.
  
# Space-Charge-Limited Current (Kirk effect) in BJTs

Decreased  $(f_\tau, f_{\max})$ , increased  $C_{cb}$  at high  $J$ .

Kirk threshold increases with increased  $V_{ce}$ .




Increase in  $V_{ce,sat}$  with increased  $J$

$$\frac{dV_{ce}}{dI_c} = R_{\text{space-charge}} = \frac{T_c^2}{2\epsilon v_{sat} A_{\text{effective}}}$$

where the effective collector current flux area is
 
$$A_{\text{effective}} \approx L_E (W_E + 2T_C)$$





# Bipolar Transistor Design

---

$$\tau_b \approx T_b^2 / 2D_n$$

$$\tau_c = T_c / 2v_{sat}$$

$$C_{cb} = \epsilon A_c / T_c$$

$$I_{c,max} \propto v_{sat} A_e (V_{ce,operating} + V_{ce,punch-through}) / T_c^2$$


---

$$\Delta T \propto \frac{P}{L_E} \left[ 1 + \ln \left( \frac{L_e}{W_e} \right) \right]$$

---

$$R_{ex} = \rho_{contact} / A_e$$
 
$$R_{bb} = \rho_{sheet} \left( \frac{W_e}{12L_e} + \frac{W_{bc}}{6L_e} \right) + \frac{\rho_{contact}}{A_{contacts}}$$



(emitter length  $L_E$ )


# Bipolar Transistor Design: Scaling

$$\tau_b \approx T_b^2 / 2D_n$$

$$\tau_c = T_c / 2v_{sat}$$

$$C_{cb} = \epsilon A_c / T_c$$
 
$$I_{c,max} \propto v_{sat} A_e (V_{ce,operating} + V_{ce,punch-through}) / T_c^2$$




(emitter length  $L_E$ )

$$\Delta T \propto \frac{P}{L_E} \left[ 1 + \ln \left( \frac{L_E}{W_e} \right) \right]$$

$$R_{ex} = \rho_{contact} / A_e$$

$$R_{bb} = \rho_{sheet} \left( \frac{W_e}{12L_e} + \frac{W_{bc}}{6L_e} \right) + \frac{\rho_{contact}}{A_{contacts}}$$

 
# Breakdown is Never Less Than The Bandgap



# Bipolar Transistors: Scaling Laws, Scaling Roadmap

## scaling laws: to double bandwidth


HBT parameter	change
emitter & collector junction widths	decrease 4:1
current density ( $\text{mA}/\mu\text{m}^2$ )	increase 4:1
current density ( $\text{mA}/\mu\text{m}$ )	constant
collector depletion thickness	decrease 2:1
base thickness	decrease 1.4:1
emitter & base contact resistivities	decrease 4:1

 

(emitter length  $L_E$ )

## InP HBT scaling roadmap

emitter	512	256	128	64	32 nm width
	16	8	4	2	$1 \Omega \cdot \mu\text{m}^2$ access $\rho$
base	300	175	120	60	30 nm contact width,
	20	10	5	2.5	$1.25 \Omega \cdot \mu\text{m}^2$ contact $\rho$
collector	150	106	75	53	37.5 nm thick,
	4.5	9	18	36	$72 \text{ mA}/\mu\text{m}^2$ current density
	4.9	4	3.3	2.75	2-2.5 V, breakdown
$f_t$	370	520	730	1000	1400 GHz
$f_{\text{max}}$	490	850	1300	2000	2800 GHz
power amplifiers	245	430	660	1000	1400 GHz
digital 2:1 divider	150	240	330	480	660 GHz

 

# Recent InP HBT Results: Urteaga et al, DRC 2011

 


Fig. 3 RF gains of  $0.13 \times 2 \mu\text{m}^2$  HBT

 


Fig. 2 Common-emitter IV characteristics of 130nm HBT normalized to emitter area

 


Fig. 4  $f_t$  and  $f_{max}$  versus collector current at varying values of  $V_{CE}$  for  $0.13 \times 2 \mu\text{m}^2$  HBT

130nm InP DHBTs with  $f_t > 0.52 \text{ THz}$  and  $f_{max} > 1.1 \text{ THz}$

M. Urteaga<sup>1</sup>, R. Pierson<sup>1</sup>, P. Rowell<sup>1</sup>, V. Jain<sup>2</sup>, E. Lobisser<sup>2</sup>, M.J.W. Rodwell<sup>2</sup>

<sup>1</sup>Teledyne Scientific Company, Thousand Oaks, CA 93160. <sup>2</sup>Department of ECE, University of California, Santa Barbara, CA 93106. E-mail: murteaga@teledyne-si.com

# Recent InP HBT Results: Jain et al, DRC 2011

30nm emitter, 30nm base, 100nm collector

1.0 THz  $f_{max}$  InP DHBTs in a refractory emitter and self-aligned base process for reduced base access resistance





Vibhor Jain<sup>1</sup>, Johann C. Rode<sup>1</sup>, Han-Wei Chiang<sup>1</sup>, Ashish Baraskar<sup>1</sup>, Evan Lobisser<sup>1</sup>, Brian J. Thibeault<sup>1</sup>, Mark Rodwell<sup>1</sup>, Miguel Urteaga<sup>2</sup>, D. Loubychev<sup>3</sup>, A. Snyder<sup>3</sup>, Y. Wu<sup>3</sup>, J. M. Fastenau<sup>3</sup>, W.K. Liu<sup>3</sup>

<sup>1</sup>ECE Department, University of California, Santa Barbara, CA 93106-9560

Phone: 805-893-3273, Fax: 805-893-3262, Email: vibhor@ece.ucsb.edu

<sup>2</sup>Teledyne Scientific & Imaging, Thousand Oaks, CA 91360
    
<sup>3</sup>IOE, Inc., 119 Technology Drive, Bethlehem, PA 18015





# Can we make a 1 THz SiGe Bipolar Transistor ?

## Simple physics clearly drives scaling

transit times,  $C_{cb}/I_c$

→ thinner layers, higher current density

high power density → narrow junctions

small junctions → low resistance contacts

## Key challenge: Breakdown

15 nm collector → very low breakdown

## Also required:

low resistivity Ohmic contacts to Si

very high current densities: heat

	InP	SiGe	
<u>emitter</u>	64	18	nm width
	2	<b>0.6</b>	$\Omega \cdot \mu\text{m}^2$ access $\rho$

<u>base</u>	64	18	nm contact width,
	2.5	<b>0.7</b>	$\Omega \cdot \mu\text{m}^2$ contact $\rho$

<u>collector</u>	53	<b>15</b>	nm thick
	36	125	$\text{mA}/\mu\text{m}^2$
	2.75	<b>1.3?</b>	V, breakdown

$f_\tau$	<b>1000</b>	<b>1000</b>	GHz
$f_{\text{max}}$	<b>2000</b>	<b>2000</b>	GHz

PAs	1000	1000	GHz
digital	480	480	GHz
(2:1 static divider metric)			

Assumes collector junction 3:1 wider than emitter.  
Assumes SiGe contacts no wider than junctions


***Interconnects***
 
# III-V MIMIC Interconnects -- Classic Substrate Microstrip

**Thick Substrate**  
→ low skin loss




$$\alpha_{skin} \propto \frac{1}{\epsilon_r^{1/2} H}$$




**Zero ground inductance in package**



**No ground plane breaks in IC**

 


**High via inductance**

 


12 pH for 100 μm substrate -- 7.5 Ω @ 100 GHz

**TM substrate mode coupling**

 


Strong coupling when substrate approaches ~λ<sub>d</sub>/4 thickness

**lines must be widely spaced**

 

Line spacings must be ~3\*(substrate thickness)


**ground vias must be widely spaced**

 


**all factors require very thin substrates for >100 GHz ICs**  
→ lapping to ~50 μm substrate thickness typical for 100+ GHz
 
# Coplanar Waveguide


No ground vias  
No need (???) to thin substrate




Hard to ground IC  
to package

 

0V  
Parasitic microstrip mode

 


 ground plane breaks → loss of ground integrity



0V  
Parasitic slot mode

 
substrate mode coupling  
or substrate losses




III-V: semi-insulating substrate → substrate mode coupling

Silicon conducting substrate → substrate conductivity losses

 
Repairing ground plane with ground straps is effective only in simple ICs  
In more complex CPW ICs, ground plane rapidly vanishes  
→ common-lead inductance → strong circuit-circuit coupling



 40 Gb/s differential TWA modulator driver  
note CPW lines, fragmented ground plane



 35 GHz master-slave latch in CPW  
note fragmented ground plane



175 GHz tuned amplifier in CPW  
note fragmented ground plane

poor ground integrity



loss of impedance control



ground bounce



coupling, EMI, oscillation



# III-V MIMIC Interconnects -- Thin-Film Microstrip

narrow line spacing → IC density



no substrate radiation, no substrate losses



fewer breaks in ground plane than CPW



... but ground breaks at device placements





still have problem with package grounding




...need to flip-chip bond

  thin dielectrics → narrow lines  
 → high line losses  
 → low current capability  
 → no high- $Z_o$  lines



InP 34 GHz PA  
 (Jon Hacker, Teledyne)
 
$$Z_o \sim \frac{\eta_o}{\epsilon_r^{1/2}} \left( \frac{H}{W + H} \right)$$



# III-V MIMIC Interconnects -- Inverted Thin-Film Microstrip

narrow line spacing → IC density



Some substrate radiation / substrate losses



No breaks in ground plane



... no ground breaks at device placements





still have problem with package grounding





...need to flip-chip bond

  
thin dielectrics → narrow lines  
 → high line losses  
 → low current capability  
 → no high- $Z_0$  lines



InP 150 GHz master-slave latch

 
 


InP 8 GHz clock rate delta-sigma ADC



 




  
# If It Has Breaks, It Is Not A Ground Plane !



   
*coupling / EMI due to poor ground system integrity is common in high-frequency systems whether on PC boards ...or on ICs.*



 
# No clean ground return ? → interconnects can't be modeled !



 *35 GHz static divider  
interconnects have no clear local ground return  
interconnect inductance is non-local  
interconnect inductance has no compact model*



 *8 GHz clock-rate delta-sigma ADC  
thin-film microstrip wiring  
every interconnect can be modeled as microstrip  
some interconnects are terminated in their  $Z_0$   
some interconnects are not terminated  
...but ALL are precisely modeled*



# VLSI mm-wave interconnects with ground integrity

narrow line spacing → IC density



no substrate radiation, no substrate losses



negligible breaks in ground plane



negligible ground breaks @ device placements




still have problem with package grounding



...need to flip-chip bond

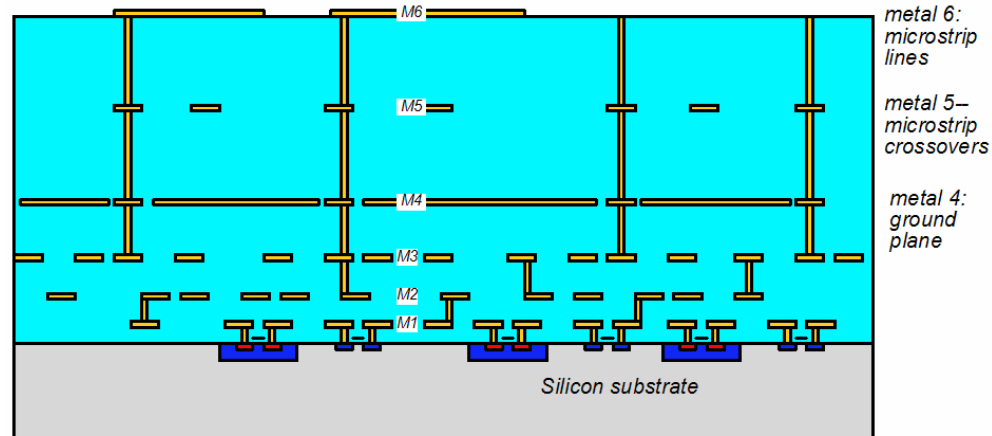thin dielectrics → narrow lines  
 → high line losses  
 → low current capability  
 → no high- $Z_0$  lines



Also:

Ground plane at *\*intermediate level\** permits critical signal paths to cross supply lines, or other interconnects without coupling.

(critical signal line is placed above ground, other lines and supplies are placed below ground)

# Modeling Interconnects, Passives in Tuned ( RF ) IC's




Interconnects are tuning elements

*Narrow bandwidths* → *precision is critical*

*Initial IC simulation uses CAD-systems' library of passive element models.*

*Final design: 2.5-Dimensional electromagnetic simulation of:  
lines, junctions, stubs, capacitors, resistors, pads.*

   150-200 GHz HBT amplifier, Urteaga et al, IEEE JSSCC, Sept. 2003




185GHz HBT amplifier, Urteaga et al,  
IEEE IMS, May. 2001


1-180GHz HBT amplifier, Agarwal et al,  
IEEE Trans MTT, Dec.. 1998



 
# Modeling Interconnects: Digital & Mixed-Signal IC's


**longer interconnects:**   
**lines terminated in  $Z_0$  → no reflections.**



 **Shorter interconnects:**   
**lines NOT terminated in  $Z_0$  .**  
**But they are \*still\* transmission-lines.**  
**Ignore their effect at your peril !**





 
**If length  $\ll$  wavelength,**  
**or line delay  $\ll$  risetime,**  
**short interconnects behave**  
**as lumped L and C.**



$$L = Z_0 \tau ,$$

$$C = \tau / Z_0 ,$$


$$\tau = l / v$$

   

# Design Flow: Digital & Mixed-Signal IC's

**All interconnects: thin-film microstrip environment.  
Continuous ground on one plane.**

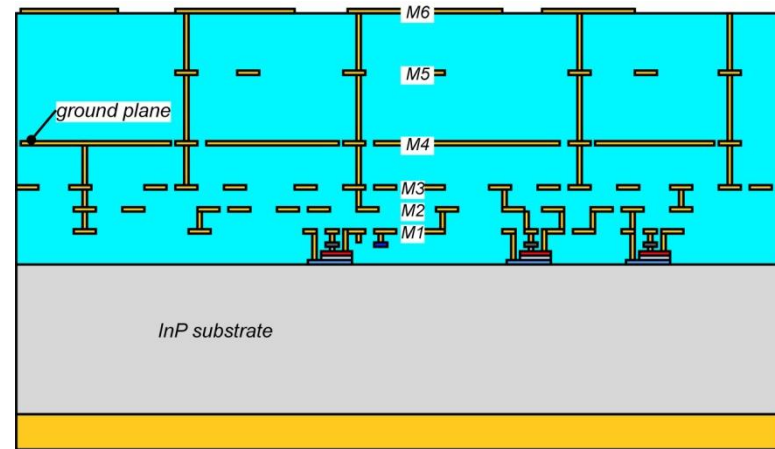
**2.5-D simulations run on representative lines.  
various widths, various planes  
same reference (ground) plane.**



**Simulation data manually fit to CAD line model  
effective substrate  $\epsilon_r$ , effective line-ground**

**Width, length, substrate of each line  
entered on CAD schematic.  
rapid data entry, rapid simulation.**

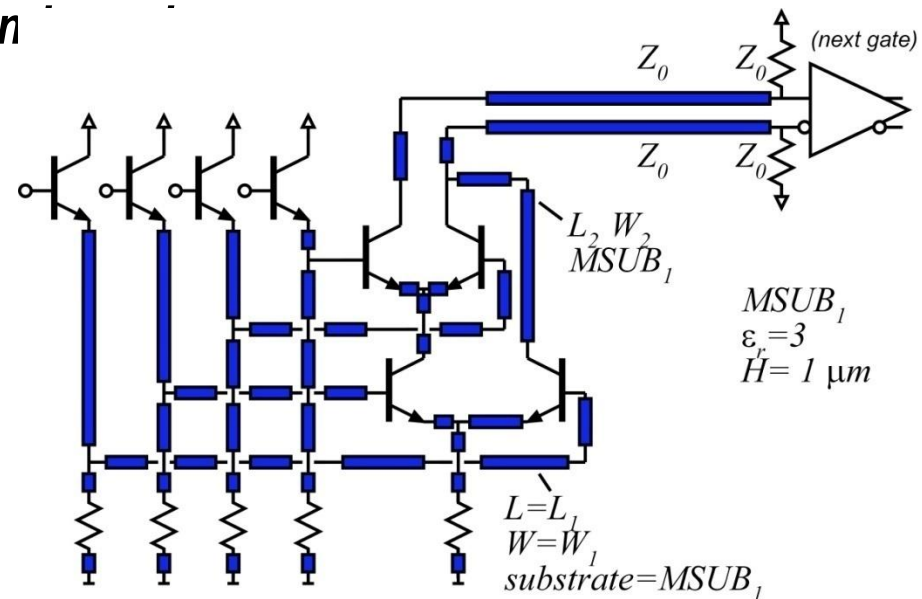**Resistors and capacitors:  
2.5-D simulation  $\rightarrow$  RLC fit  
RLC model used in simulation.**






***Network analyzer  
Calibration...  
on-wafer LRL***


# On-Wafer Through-Reflect-Line (TRL) Calibration

**Through**

 


*Through line should be long for large probe separation.  
Minimizes probe-probe coupling.  
Measurements normalized to the line characteristic impedance.*

**Reflect**

 


*open*

 

*short*


*Either open or short needed.  
Standards need not be accurate.  
"Open" must have  $\Gamma$  closer to  
that of open than that of short.  
Ports 1 & 2 must be symmetric.*

**Line**

 

*$\Delta L = 90 \text{ deg @center frequency.}$   
 $\lambda/8 < \Delta L < 3\lambda/8$*

**Device Under Test**

 

Please see also:

[http://www.ece.ucsb.edu/Faculty/rodwell/publications\\_and\\_presentations/publications/204vg.ppt](http://www.ece.ucsb.edu/Faculty/rodwell/publications_and_presentations/publications/204vg.ppt)

# On-Wafer TRL: Ongoing Issues

**High- $f_{max}$  transistors have very small ( $C_{cb} \rightarrow Y_{12} \rightarrow S_{12}$ )**

**Measurements show small background  $Y_{12}$ .**

**...even with extended reference planes.**

**Particular difficulty in extracting Mason's Unilateral gain.**

**→ Corrupts  $f_{max}$  measurement, model extraction.**

**Measurements normalized to line  $Z_0$ .**

**...line impedance is complex at lower frequencies.**

**→ must correct for complex  $Z_0$  in measurements.**

**excessive line resistance degrades precision.**



$$Z_0 = \sqrt{\frac{R(j\omega) + j\omega L}{j\omega C}}$$

**TRL precision greatly impaired if lines couple to substrate;  
CPW line standards do not work well.**


# Verification of 140-220GHz TRL Calibration

M. Seo


## Through

## Open


## Line

 





freq (140.0GHz to 200.0GHz)

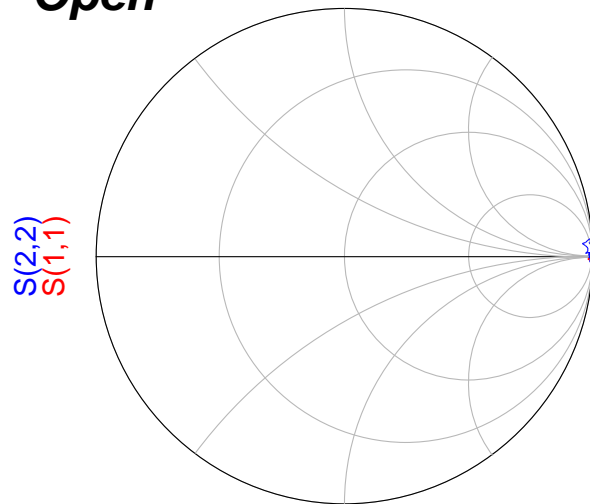

freq (140.0GHz to 200.0GHz)


 


freq (140.0GHz to 200.0GHz)

    

# Difficulties with 140-220GHz TRL Calibration

Data on two layouts of 65 nm MOSFET

  


**Measured Y-parameters correlate reasonably with expected device model.**

**Small errors in measured 2-port parameters result in large changes in Unilateral gain and Rollet's stability factor; neither measurement is credible.**

**$Y_{12}$  appears to be the key problem.**

 
**IC  $S_{ij}$  measurements are fine. Transistor  $f_{max}$  measurements are hard.**




***50+ GHz  
Mixed-Signal  
& ECL design:  
Principles &  
Examples***
 
# High Speed ECL Design


**Followers associated with inputs, not outputs**  
**Emitters never drive long wires.**  
**(instability with capacitive load)**



 **Double termination for least ringing, send or receive termination for moderate-length lines, high-Z loading saves power but kills speed.**



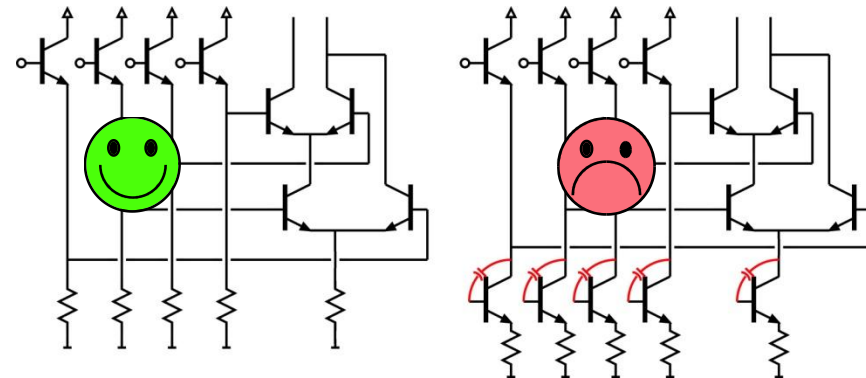**Current mirror biasing is more compact.**  
**Mirror capacitance → ringing, instability.**  
**Resistors provide follower damping.**






# High Speed ECL Design

**Layout: short signal paths at gate centers, bias sources surround core.**  
**Inverted thin film microstrip wiring.**




**Key: transistors in on-state operate at Kirk limited-current.**  
 → minimizes  $C_{cb}/I_c$  delay.

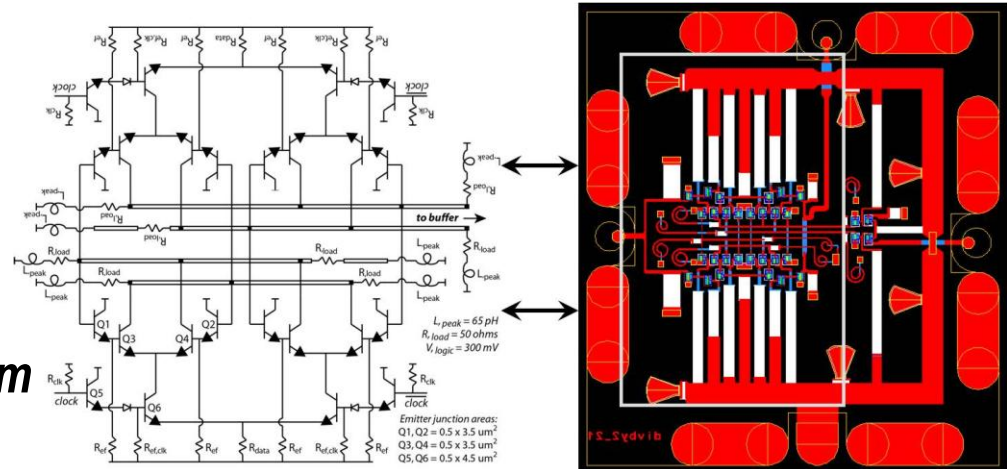**Key: transistors designed for minimum ECL gate delay\*, not peak ( $f_\tau$ ,  $f_{max}$ ).**  
 \*hand expression, charge-control analysis



205 GHz divider, Griffith et al, IEEE CSIC, Oct. 2010

  
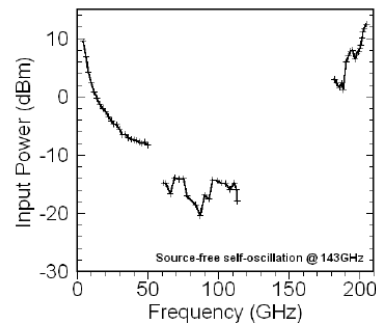
**Example: 8:1 205 GHz static divider in 256 nm InP HBT.**


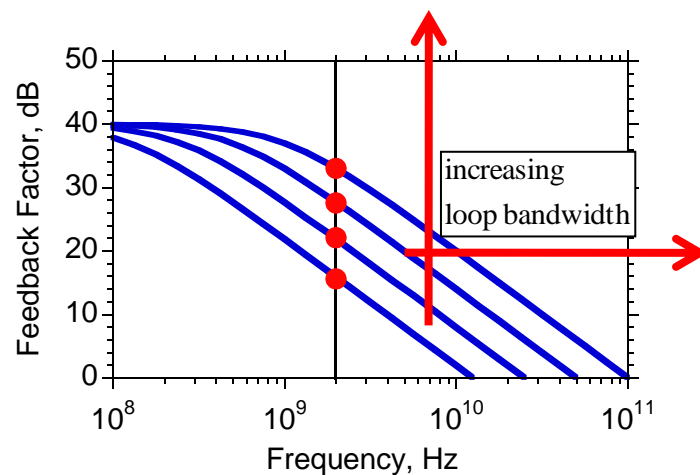 
# mm-wave Op-Amps for Linear Microwave Amplification


Griffith et al, IEEE IMS, June. 2011

*Reduce distortion with strong negative feedback*



*Even for 2 GHz operation,  
loop bandwidths must 20-40 GHz.*


*need very fast transistors*

 


*physically small feedback loop;  
bias components surround active core.*

# mm-wave Op-Amps for Linear Microwave Amplification


Griffith et al, IEEE IMS, June. 2011

 

current-mode analog design

 


 *...node impedances kept low  
with transimpedance loading  
→ high bandwidth*



*Virtual-ground input stage, Miller feedback  
around output stage, makes feedback  
insensitive to generator & load impedances.*




 
*...critical for stability in a 50 GHz loop!  
(what will the op-amp be connected to?)*



*Z<sub>f</sub>-stage and loop nesting for high gain  
even with fast resistor-loaded circuits*
    
# mm-wave Op-Amps for Linear Microwave Amplification

Griffith et al, IEEE IMS, June. 2011  
Griffith et al, IEEE IPRM, May. 2008







# 40 GSample/s Sample/Hold \*Design\*





master-slave track-and-hold  
 target 40 GS/s, 6 b (??)  
 256 nm InP HBT

Saeid Daneshgar

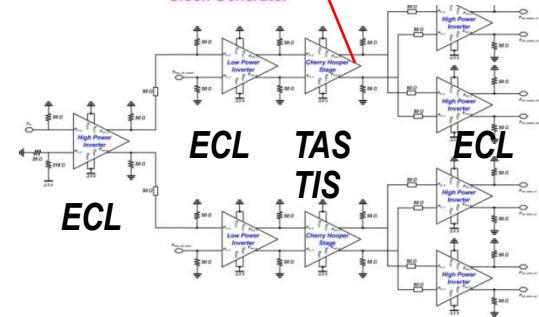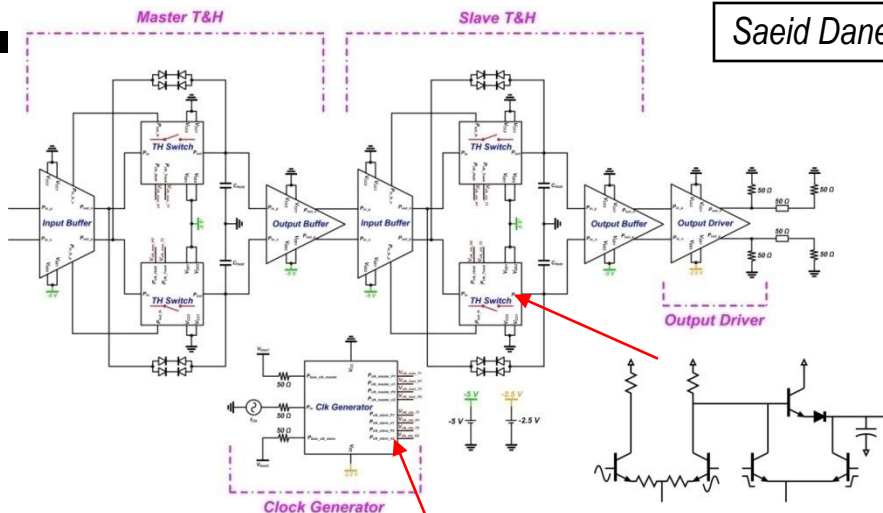

layout: ECL buffer.

layout: TASTIS.

    


**Bias and transmission-line design strongly follows controlled-impedance ECL examples.**

***RF-IC design***  
***Principles &***  
***Examples***

# RF-IC Design: Simple & Well-Known Procedures

 
- 1: (over)stabilize at the design frequency guided by stability circles
- 2: Tune input for  $F_{min}$  (LNAs) or output for  $P_{sat}$  (PAs)
- 3: Tune remaining port for maximum gain
- 4: Add out-of-band stabilization.



There are many ways to tune port impedances: microstrip lines, MIM capacitors, transformers  
Choice guided by tuning losses. No particular preferences.

For BJT's, MAG/MSG usually highest for common-base.  
→ preferred topology.

 Common-base gain is however reduced by:  
base (layout) inductance  
emitter-collector layout capacitance.









# Power Amplifier Design (Cripps method)

For maximum saturated output power,  
& maximum efficiency  
device intrinsic output must see  
optimum loadline set by:

$$P_{\max} = (1/8)(V_{\max} - V_{\min})I_{\max}$$

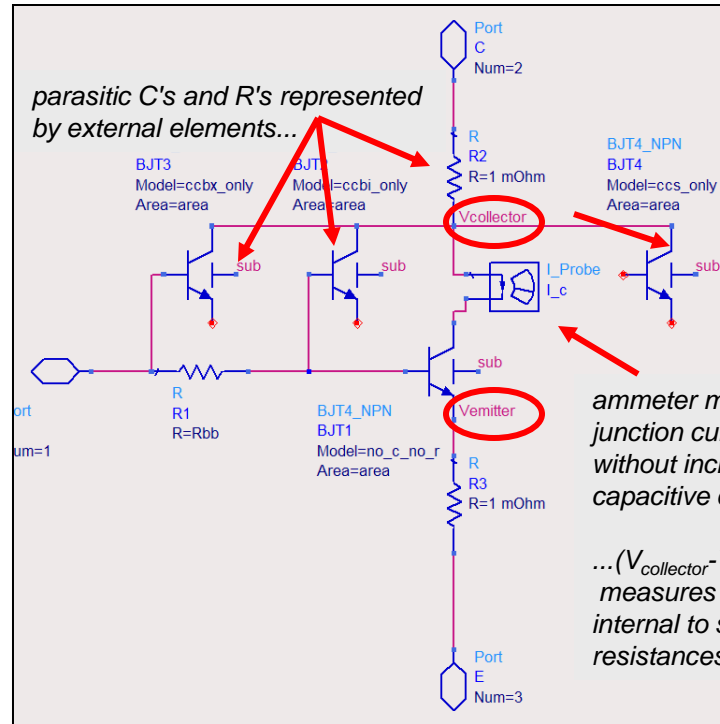
 
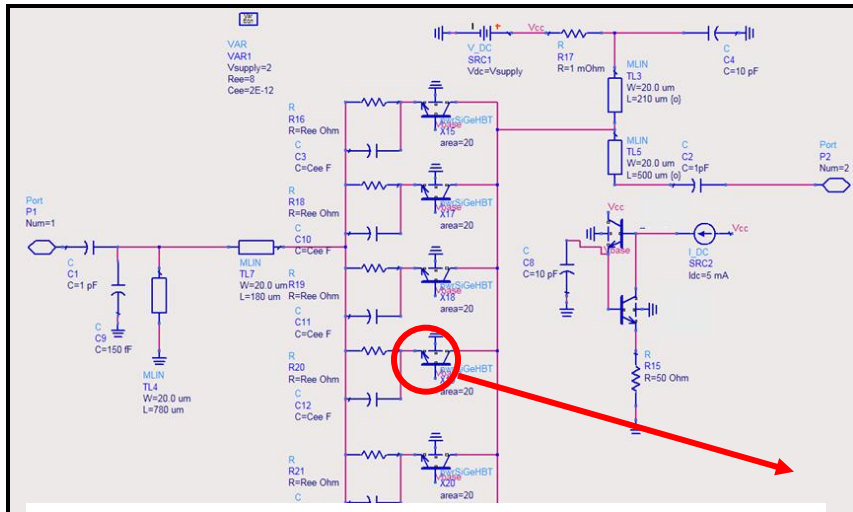
 
breakdown, maximum current, maximum power density.



   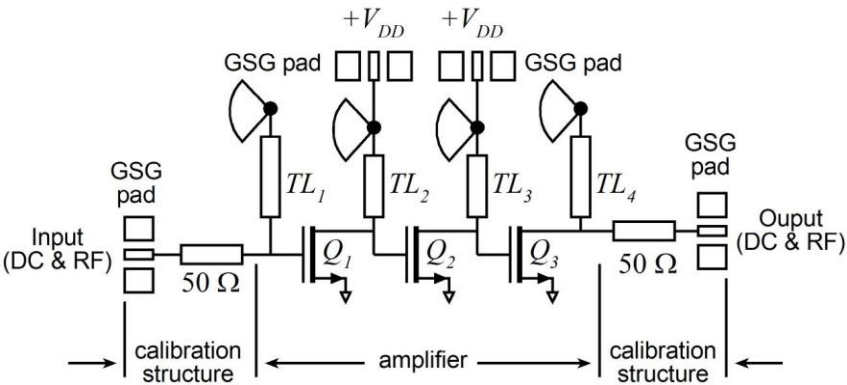
# 3-stage 150-GHz Amplifier; IBM 65 nm CMOS

Acknowledgement:  
IBM

M. Seo, B. Jagannathan, J. Pekarik, M. Rodwell, IEEE JSSCC, Dec. 2009





*Dummy-filled microstrip lines*

 


# 220 GHz, 48 mW HBT Power Amplifier

T. Reed et al, IEEE CSIC, Oct. 2011, to be presented.

 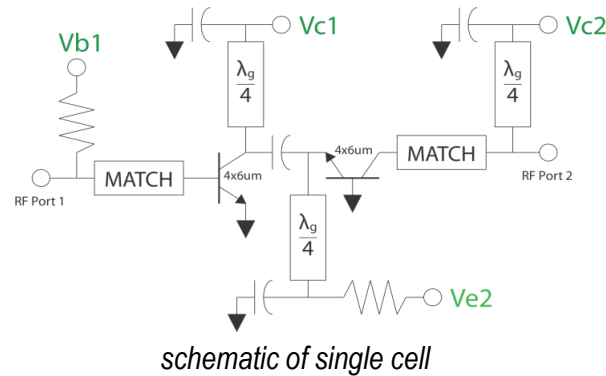**4-cell design:  $P_{sat} > 48 \text{ mW}$  @ 220 GHz**



 **8-cell design: not yet fully tested:  $P_{sat} = ?$**



**Technology:**

**Teledyne 250 nm InP HBT**

**Right-side-up thin-film microstrip wiring.**

**Breaks in ground plane minimized.**

# High Frequency Bipolar IC Design

---

*Digital, mixed-signal, RF-IC (tuned) IC designs----at very high frequencies*

*Even at 670 GHz, design procedures differ little from that at lower frequencies: classic IC design extends readily to the far-infrared.*

*Key considerations: Tuned ("RF") ICs*

*Rigorous E&M modeling of all interconnects & passive elements*

*Continuous ground plane → required for predicable interconnect models.*

*Higher frequencies → close conductor planes → higher loss, lower current*

*Key considerations: digital & mixed-signal :*

*Transmission-line modeling of all interconnects*

*Continuous ground plane → required for predicable interconnect models.*

*Unterminated lines within blocks; terminated lines interconnecting blocks.*

*Analog & digital blocks design to naturally interface to 50 or 75 $\Omega$ .*

*Next: TMIC designs for 340 GHz, 670 GHz transceivers.*