

**ECE 2C Circuits, Devices and Systems**

**Midterm Exam Sample#2**

**Instructor: Prof. C. Patrick Yue**

**Name: \_\_\_\_\_**

- **You have 1 hour and 15 min. to complete this quiz.**
- **Closed book, one 8.5"x11" equation sheet allowed.**
- **Calculators are allowed.**
- **Please turn off and put away your mobile phone**
- **Be sure to include the proper units in your answers.**
- **State all of your assumptions in your solutions in order to receive partial credits for incorrect answers.**
- **To receive credit, there must be sufficient evidence of your reasoning. Correct answers without correct reasoning or clear calculation steps will not receive full credits.**

**Problem 1 \_\_\_\_\_ / 50 (DC analysis PMOS circuits)**

**Problem 2 \_\_\_\_\_ / 50 (Frequency response of a NMOS amplifier)**

**Total \_\_\_\_\_ / 100**

Problem 1 (Total 50 pt.)


Given:  $0.5\mu\text{Cox}W/L = 50 \text{ mA/V}^2$ ,  $V_t = -1 \text{ V}$ , and  $\gamma = 0$ .

For  $\lambda=0$ :

- (a) Find  $V_{SG}$  to set  $I_{DS} = 25 \text{ mA}$ . (10 pt.)
- (b) If  $R_1 = 100 \Omega$ , find  $V_G$ . (10 pt.)
- (c) Find the max. value of  $R_2$  to keep  $M_1$  in saturation region. (10 pt.)

For  $\lambda=0.1$ :

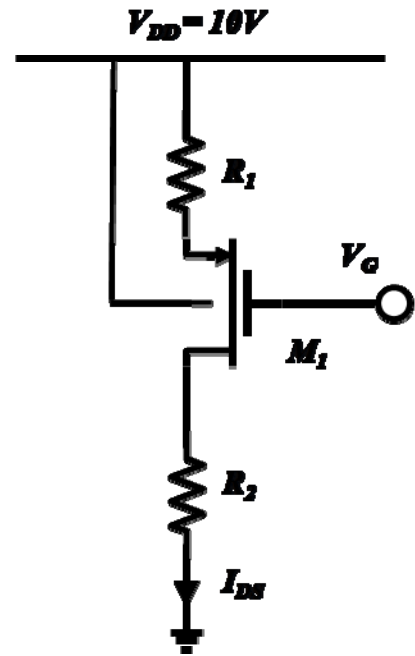- (d) Use  $R_1 = 100 \Omega$  and  $R_2 = 200 \Omega$ .  
If  $V_G = 6 \text{ V}$ , find the new  $I_{DS}$ . (20 pt.)



Problem 2 (Total 50 pt.)

Given:  $\lambda = 0$  and  $\gamma \neq 0$ .

- (a) Find the expression for the small-signal midband voltage gain,  $v_{out}/v_{in}$ . (10 pt.)
- (b) Find the lower  $-3$ dB corner frequency (10 pt.)
- (c) Find the upper  $-3$ dB corner frequency (10 pt.)
- (d) Write down the overall expression of  $v_{out}/v_{in}(s)$ . (10 pt.)
- (e) Sketch the Bode plot of  $v_{out}/v_{in}(s)$ . (10 pt.)

