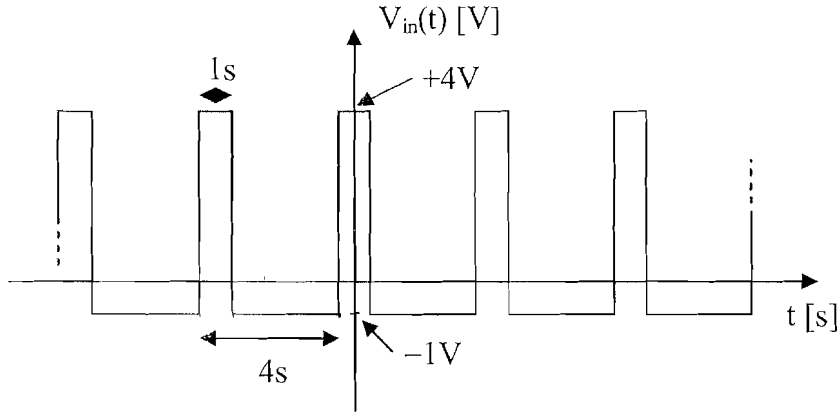





15

Problem 1 [Total 30 pt.]

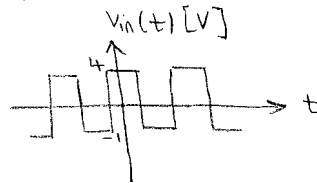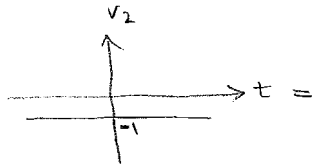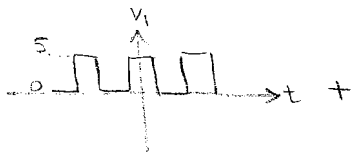(a) [15 pt.] Consider the periodic signal below, find the trigonometric Fourier series representation of this waveform. (A table of Fourier coefficients for commonly used waveforms is provided with the exam.)



$$f(t) = a_0 + \sum_{n=1}^{\infty} [a_n \cos(2\pi n f_0 t) + b_n \sin(2\pi n f_0 t)]$$



$$T_0 = 4s, T = 1s$$

$$A = 5, \frac{T}{T_0} = \frac{1}{4}$$

$$a_0 = \frac{AT}{T_0} = \frac{5}{4}$$

$$b_n = 0 \text{ for all } n$$

$$a_n = \frac{2A}{n\pi} \sin\left(\frac{n\pi T}{T_0}\right)$$

$$a_n = \frac{10}{n\pi} \sin\left(\frac{n\pi}{4}\right)$$

$$a_0 = -1$$

$$a_n = 0 \text{ for all } n$$

$$b_n = 0 \text{ for all } n.$$

$$a_0 = \frac{5}{4} - 1 = \frac{1}{4} \rightarrow a_0 = \frac{1}{4}$$

$$b_n = 0 \text{ for all } n$$

$$a_n = \frac{10}{n\pi} \sin\left(\frac{n\pi}{4}\right) \text{ for all } n$$

$$T_0 = 4s \rightarrow f_0 = \frac{1}{4} \text{ Hz}, \omega_0 = \frac{2\pi}{T} = \frac{2\pi}{4} = \frac{\pi}{2}$$

$$\rightarrow V_{in}(t) = \frac{1}{4} + \sum_{n=1}^{\infty} \left[\frac{10}{n\pi} \sin\left(\frac{n\pi}{4}\right) \cos\left(2\pi n \frac{1}{4} t\right) \right] \Rightarrow$$

$$V_{in}(t) = \frac{1}{4} + \sum_{n=1}^{\infty} \left[\frac{10}{n\pi} \sin\left(\frac{n\pi}{4}\right) \cos\left(\frac{n\pi t}{2}\right) \right] [V]$$


$$a_1 = \frac{10}{\pi} \sin\left(\frac{\pi}{4}\right) = \frac{10}{\pi} \cdot (0.71) = 2.25 \text{ V}$$

$$a_2 = \frac{10}{2\pi} \sin\left(\frac{2\pi}{4}\right) = \frac{5}{\pi} \sin\left(\frac{\pi}{2}\right) = 1.59 \text{ V}$$

(15)

Problem 1 (continued)

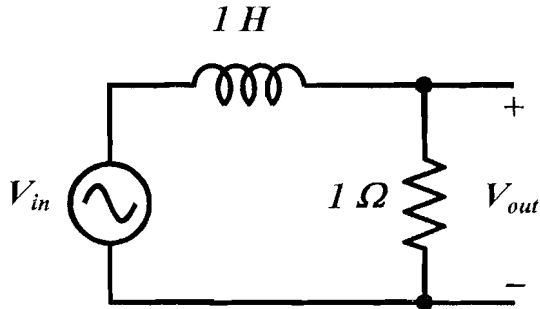(b) [15 pt.] Apply the above waveform as V_{in} to the single-time-constant circuit below. Write down the amplitude and phase of the first 2 non-zero components of V_{out} .



$$T(s) = \frac{1}{1+sL} = \frac{1}{1+s} \rightarrow T(j\omega) = \frac{1}{1+j\omega}$$

$$T(0) = 1 \rightarrow a_0 = (1)\left(\frac{1}{4}\right) = \frac{1}{4} \text{ amplitude} \quad \phi = 0 \quad : \text{dc term}$$


$$\left|T\left(j\frac{\pi}{2}\right)\right| = \frac{1}{\sqrt{1^2 + \left(\frac{\pi}{2}\right)^2}} = 0.54 \rightarrow a_1 = (0.54)(2.25) = 1.21 \text{ amplitude}$$
$$\phi = 0 - \tan^{-1}\left(\frac{\pi}{2}\right) = -57.5^\circ \text{ phase}$$

$$\left|T(j\pi)\right| = \frac{1}{\sqrt{1 + \pi^2}} = 0.30 \rightarrow a_2 = (0.30)(1.59) = 0.48 \text{ amplitude}$$
$$\phi = 0 - \tan^{-1}(\pi) = -72.34^\circ \text{ phase}$$

$$\rightarrow V_{out} = \frac{1}{4} + 1.21 \cos\left(\frac{\pi t}{2} - 57.5^\circ\right) + 0.48 \cos(\pi t - 72.34^\circ) + \dots$$

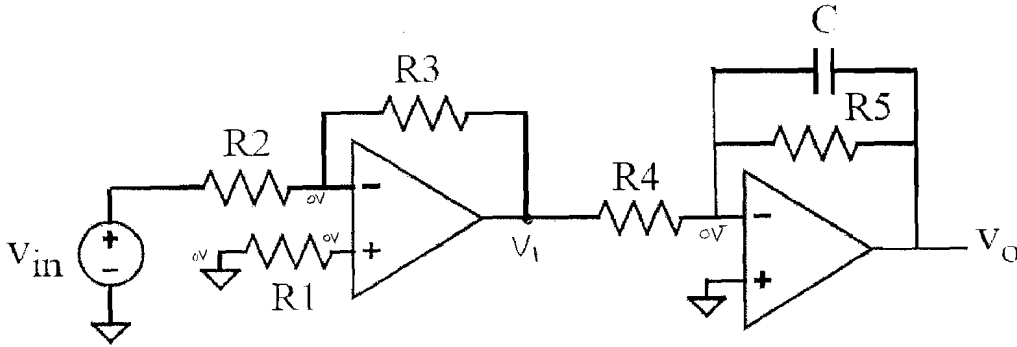Problem 2 [Total 30 pt.]

Calculate the transfer function, $H(s) = v_o/v_{in}$ assuming ideal op amps (the open loop gains are infinite as well as everything else being ideal).



$$V_o = \frac{-\frac{1}{sC} \cdot R_5}{\frac{1}{sC} + R_5} \cdot V_1 = \frac{-R_5}{R_5 sC + 1} V_1 = \frac{-R_5}{R_4 (R_5 sC + 1)} V_1 = \frac{-R_5}{R_4 R_5 sC + R_4} V_1 \quad (10)$$

$$V_1 = -\frac{R_3}{R_2} V_{in} \quad (10)$$

$$\rightarrow V_o = \frac{+R_5}{R_4 R_5 sC + R_4} \left(\frac{+R_3}{R_2} \right) V_{in} \rightarrow$$

$$H(s) = \frac{V_o}{V_{in}} = \left(\frac{R_5}{R_4 R_5 sC + R_4} \right) \left(\frac{R_3}{R_2} \right) = \frac{R_3 R_5}{R_2 R_4 R_5 sC + R_2 R_4} \quad (10)$$

20

Problem 3 [Total 40 pt.]

(a) [20 pt.] Find I_3 and V_4 , in the circuit shown below, for $\mu_n C_{ox} = 50 \mu A/V^2$, $\mu_p C_{ox} = 20 \mu A/V^2$, $V_{tn} = 1V$, $V_{tp} = -1V$, $\lambda_n = \lambda_p = 0$, $L_n = L_p = 10 \mu m$, $W_n = 30 \mu m$, and $W_p = 75 \mu m$.

$$\mu_n C_{ox} = 50 \times 10^{-6} \frac{A}{V^2}$$

$$\mu_p C_{ox} = 20 \times 10^{-6} \frac{A}{V^2}$$


$$V_{tn} = 1V, V_{tp} = -1V$$

$$\lambda_n = \lambda_p = 0$$

$$L_n = L_p = 10 \mu m$$

$$W_n = 30 \mu m$$

$$W_p = 75 \mu m$$

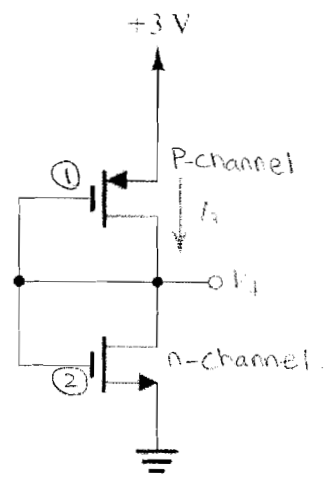

(b)

①:

$$i_D = \frac{1}{2} (\mu_p C_{ox}) \left(\frac{W_p}{L_p} \right) (V_{SG} - |V_t|)^2, \quad V_{S1} = 3V$$

For saturation we want

$$V_{sg} > 1 \rightarrow 3 - V_4 > 1 \rightarrow -V_4 > -2 \rightarrow V_4 < 2$$

$$i_3 = \frac{1}{2} (20 \times 10^{-6}) \left(\frac{75}{10} \right) (3 - V_4 - 1)^2$$

②:

$$i_D = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W_n}{L_n} \right) (V_{GS} - V_t)^2$$

$$V_{GS} = V_G - V_S = V_4 - 0 = V_4, \quad V_{S2} = 0$$

condition for saturation.

$$V_{GS} > 1 \rightarrow V_4 > 1$$

$$i_3 = \frac{1}{2} (50 \times 10^{-6}) \left(\frac{30}{10} \right) (V_4 - 1)^2$$

Dividing ① by ②:

$$1 = \frac{20 \times 75 (2 - V_4)^2}{50 \times 30 (V_4 - 1)^2} \rightarrow 50 \times 30 (V_4 - 1)^2 = 20 \times 75 (2 - V_4)^2 \rightarrow$$

$$(V_4 - 1)^2 = (2 - V_4)^2 \rightarrow \begin{cases} V_4 - 1 = 2 - V_4 \rightarrow 2V_4 = 3 \rightarrow V_4 = 1.5V \\ V_4 - 1 = V_4 - 2 \quad \times \end{cases}$$

which satisfies both conditions for saturation.

$$i_3 = \frac{1}{2} (50 \times 10^{-6}) (3) (1.5 - 1)^2 = 18.75 \mu A \rightarrow I_3 = 18.75 \mu A$$


nice!

20

Problem 3 (continued)

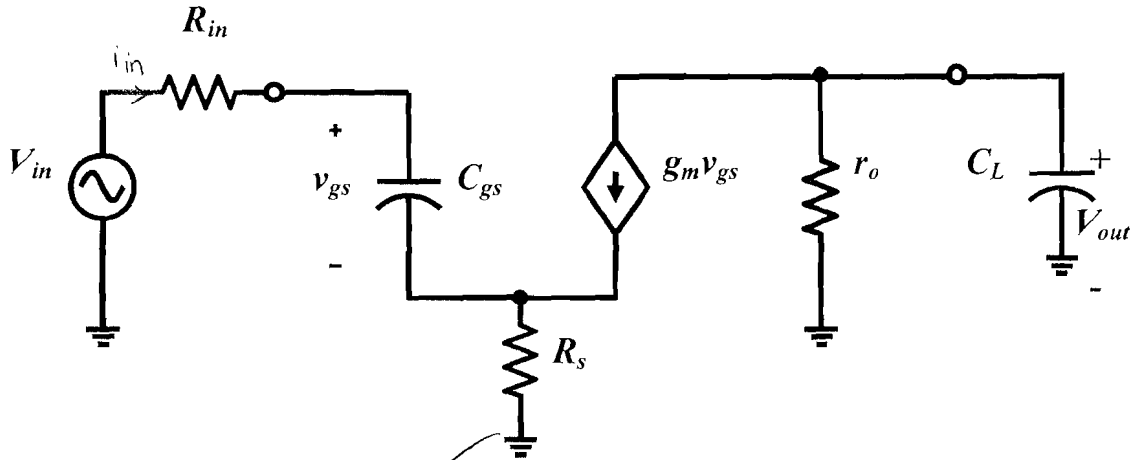(b) [20 pt.] Shown below is the simplified small-signal equivalent circuit of a common-source amplifier with source degeneration resistor. Find the transfer function, $V_{out}/V_{in}(s)$.

Hints: (1) the impedance of a capacitance, C , is $1/(sC)$. (2) find V_{out} in terms of V_{gs} and V_{in} in terms of V_{gs} , then take the ratio.



$$V_{out} = -g_m V_{gs} (r_o \parallel \frac{1}{sC_L})$$

$$V_{in} - i_{in} R_{in} - V_{gs} - R_s (g_m V_{gs} + i_{in}) = 0, \text{ and } V_{gs} = i_{in} (\frac{1}{sC_{gs}}), \text{ } i_{in} = V_{gs} \cdot sC_{gs}$$

$$\rightarrow V_{in} = R_{in} sC_{gs} V_{gs} + V_{gs} + R_s g_m V_{gs} + R_s sC_{gs} V_{gs} = V_{gs} (1 + g_m R_s + sC_{gs} (R_s + R_{in})).$$

$$\rightarrow \frac{V_{out}}{V_{in}} = \frac{-g_m (r_o \parallel \frac{1}{sC_L})}{1 + g_m R_s + sC_{gs} (R_s + R_{in})} = \frac{-g_m \left(\frac{r_o \cdot \frac{1}{sC_L}}{r_o + \frac{1}{sC_L}} \right)}{1 + g_m R_s + sC_{gs} (R_s + R_{in})}$$

$$\rightarrow \frac{V_{out}}{V_{in}} = \frac{-g_m \left(\frac{r_o}{r_o sC_L + 1} \right)}{1 + g_m R_s + sC_{gs} (R_s + R_{in})}$$