

Q4

$$V_t = 2V, \quad K_n = 200 \text{ mA/V}^2$$

$$K_n = 0.2 \text{ A/V}^2$$

$$|VA| = \infty$$

(a) For $I_d = 10 \text{ mA}$

$$\therefore V_s = 1V$$

Assuming the transistor operate in sat.

$$I_d = K_n (V_{GS} - V_t)^2$$

$$10 \text{ m} = 0.2 (V_{GS} - 2)^2$$

$$\therefore V_{GS} = 2.224V \Rightarrow V_g = 3.224V$$

$$V_g = 5 * \frac{R_{g2}}{R_{g1} + R_{g2}} = 5 \frac{1}{\frac{R_{g1}}{R_{g2}} + 1}$$


$$\therefore \frac{R_{g1}}{R_{g2}} = \frac{5}{V_g} - 1 \Rightarrow R_{g1} = 125 \text{ k}\Omega$$

$$V_{DS} = 5 - 10 \text{ m} * R_D - V_s$$

$$V_{DS} = 1.8V$$


$\therefore V_{DS} > V_{GS} - V_t \Rightarrow$ Device in saturation

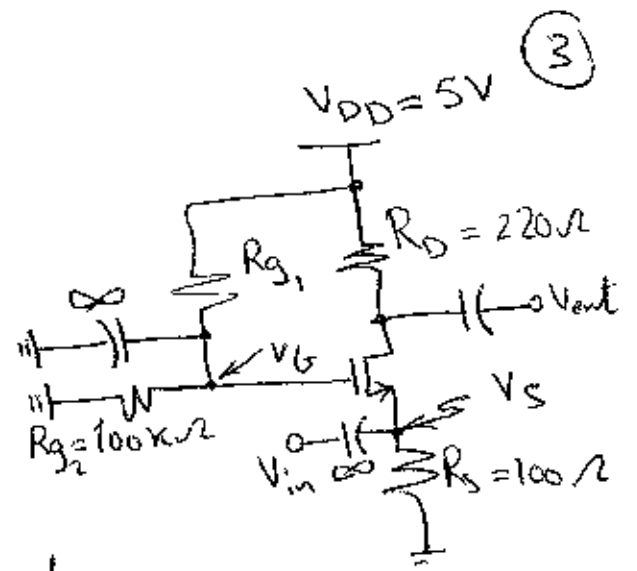(b) $g_m = 2 K_n (V_{GS} - V_t) = 2 \sqrt{I} \sqrt{K_n} \Rightarrow g_m = 89.4 \text{ mA/V}$



(3)

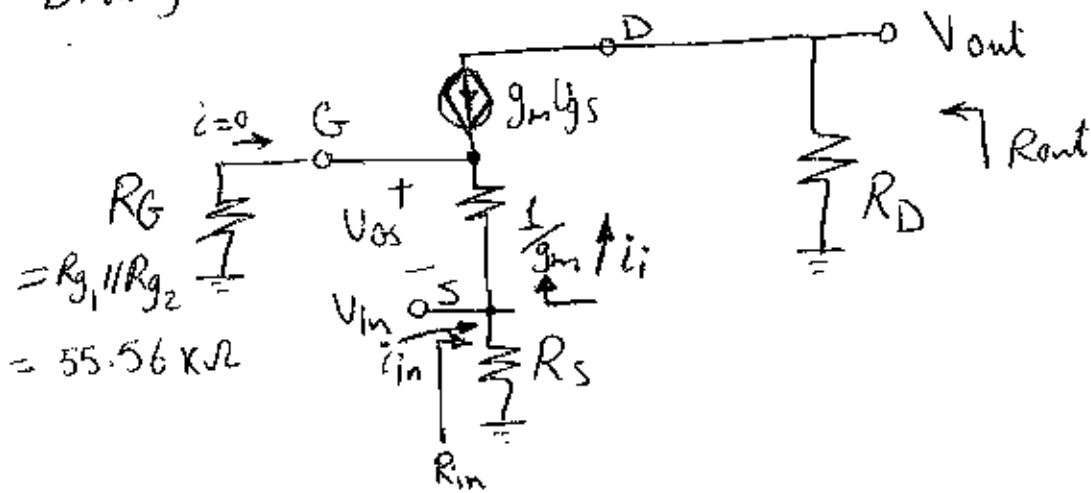(c) Drawing the small signal T-model for the CG stage. (4)



(d) $V_{out} = -g_m V_{gs} R_D \rightarrow \textcircled{1}$

$i_i = \frac{V_{in}}{1/g_m} = g_m V_{in}$

but $i_i = -g_m V_{gs} = g_m V_{in}$

$\Rightarrow V_{gs} = -V_{in}$ (which could have been written directly bec no ~~AC~~ current is flowing in the gate terminal \therefore AC voltage $V_g = 0$)

$\therefore \boxed{\frac{V_{out}}{V_{in}} = g_m R_D} = 19.668 \text{ V/V}$

$R_{in} = \frac{1}{g_m} \parallel R_S = \frac{R_S}{1 + g_m R_S} = 10.06 \Omega$

$R_{out} = R_D \parallel R_o = 220 \Omega$

(e) new gain = $g_m R_D \parallel R_L \leftarrow 1 \text{ k}\Omega$
 $= 16.12 \text{ V/V}$