

by Li Sun.

Problem 1: We know that  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $\mu_p C_{ox} = 80 \mu A/V^2$ ,  $V_{tn} = |V_{tp}| = 0.61$

$$V'_{A_n} = 10V/\mu m, \quad |V'_{A_p}| = 12V/\mu m \quad \text{for } L = 0.8 \mu m, \quad V_{A_n} = 8V, \quad V_{A_p} = 9.6V$$

$$\text{If } Q_2 \text{ works properly, } V_{SD} \geq V_{ov} = V_{Sg} - |V_{thp}|$$

Because the maximum value of  $V_S$  of  $Q_2$  can be as high as 1.3V, we can

choose  $V_{ov_{Q2}} = 1.5V - 1.3V = 0.2V$  to make sure  $Q_2$  stays in saturation.

$$\text{thus, for } Q_1: \quad I_{ref} = 20 \mu A = \frac{1}{2} \times \mu_p C_{ox} \times \left(\frac{W}{L}\right)_1 \cdot V_{ov1}^2 \left(1 + \frac{V_{Sg}}{V_{A_p}}\right)$$

$$\Rightarrow 20 \mu A = \frac{1}{2} \times 80 \mu A/V^2 \times \left(\frac{W}{L}\right)_1 \times 0.2^2 \left(1 + \frac{0.2 + 0.6}{9.6}\right)$$

$$\Rightarrow W_1 = 11.538 \times L_1 \approx 9.23 \mu m$$

$$\text{while } R = \frac{1.5 - V_{Sg}}{I_{ref}} = \frac{0.7V}{20 \mu A} = 35 K\Omega$$

Because  $I_3 = I_4 = I_{ref} = 20 \mu A$ ,  $I_5 = 50 \mu A$ ,  $I_2 = 100 \mu A$

$$\text{we have } W_2 = \frac{I_2}{I_{ref}} \cdot W_1 = 46.15 \mu m$$

$$W_3 = \frac{I_3}{I_{ref}} \cdot W_1 = 9.23 \mu m$$